

Announcements:

1. Final HW due Friday of 10th week
2. Professor Burke's office hours this week:
Tu 9:30-11:30 (EH 2230)
Th 9:30-11 (EG 2232)
Th 2-3:30 (EH 2230)
3. Exam :
 - Will cover all of Chs. 1,2,3,4,6, 7.1-7.3, 9 (not delta-Y), 14.1 14.2 14.3 14.5 14.6 14.7
 - Not covered: 3.6, 3.8, 4.9, 6.6.
 - No calculators. We will give sin, cos, tan tables as shown on last slide of today's notes..

EECS 70A: Network Analysis


Lecture 16

Comprehensive review

Topics covered

- KCL, KVL
- Nodal analysis
- Mesh analysis
- Thevenin/Norton theorem
- RL, RC circuits (time dependence)
- R,L,C circuits
 - Phasors
 - Impedances
 - Transfer function

Thevenin, Norton Theorems:

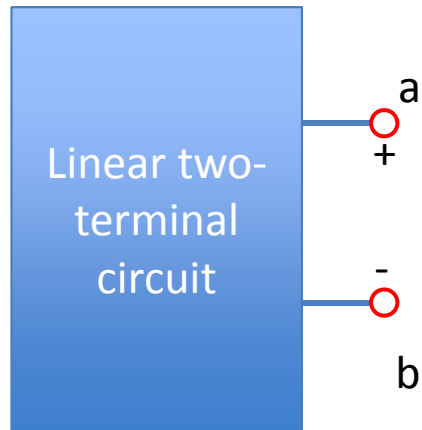

Thevenin:

1. Calculating V_{th} :

Connect nothing to a-b. Calculate voltage. This is V_{th} .

2. Calculating R_{th} :

Method 1:

Connect terminal a to b (short).

Calculate the current from a to b. This is call $I_{short\ circuit}$.

$$R_{th} = V_{th} / I_{short\ circuit}$$

Method 2:

Find the input resistance looking into terminals a-b after all the independent sources have been turned off.


(Voltage sources become shorts, current sources become opens.)

Trick (if dependent sources present):


Apply a 1 A current source to terminals a-b, find V_{ab}

$$R_{th} = V_{ab} / 1A.$$

Equivalent to:

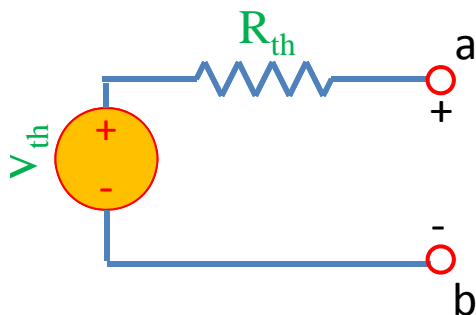

Equivalent to:

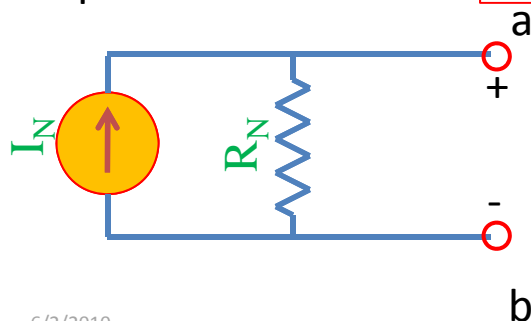

Norton:

1. Calculating R_N :


$$R_N = R_{th}$$

2. Calculating I_N :


$$I_N = V_{th} / R_{th}$$

RC circuit

Find $V(t)$, $q(t)$, $i(t)$

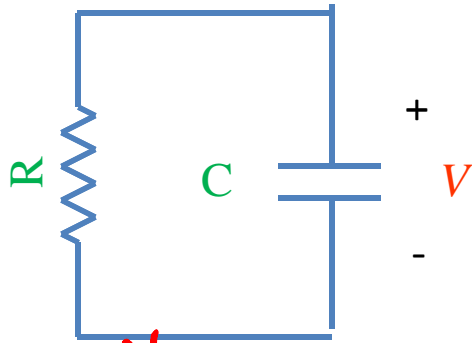


$$V(t) = V(t=0) e^{-t/RC}$$

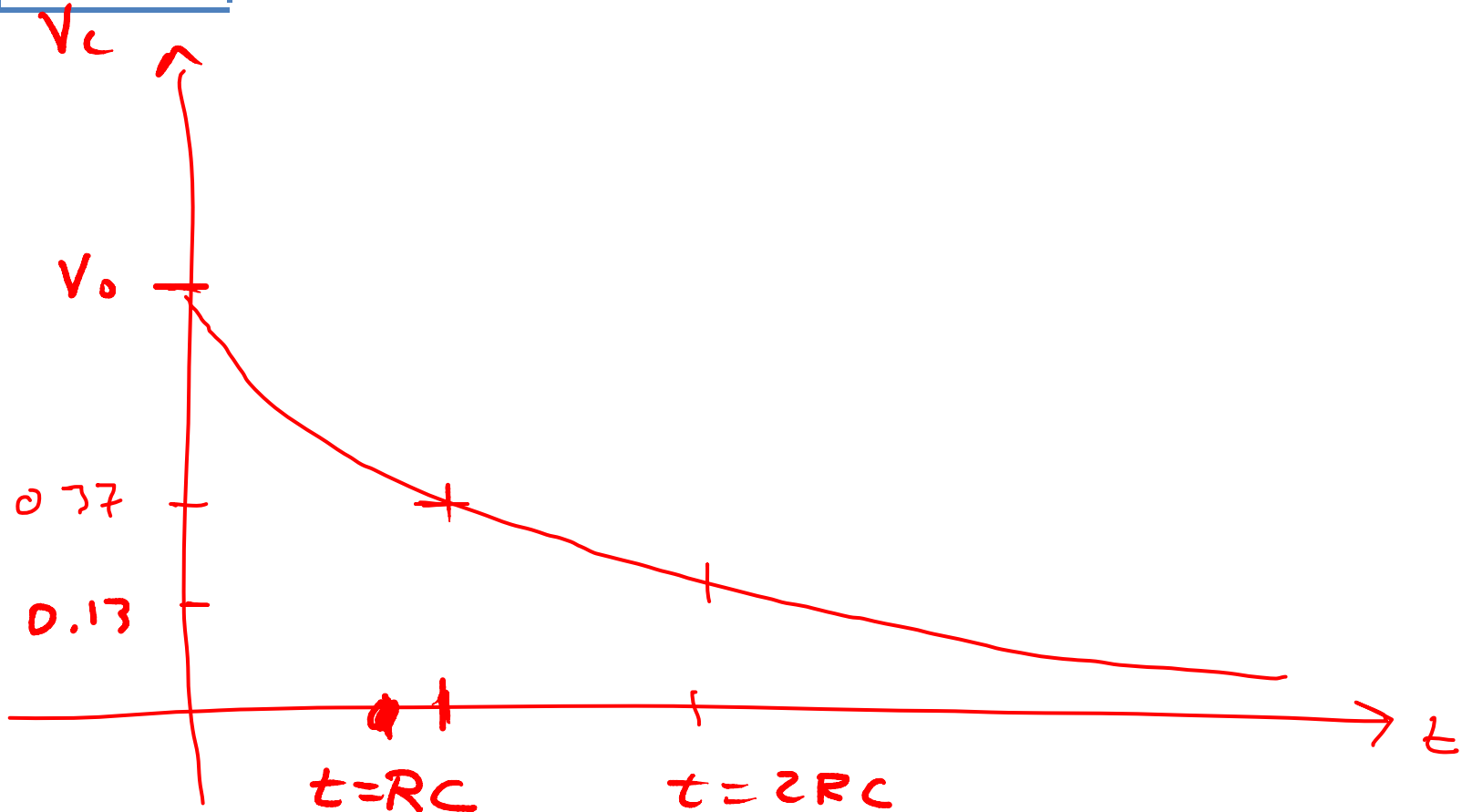

$$V_R = i_R R$$

LR circuit

Find $V(t)$, $i(t)$

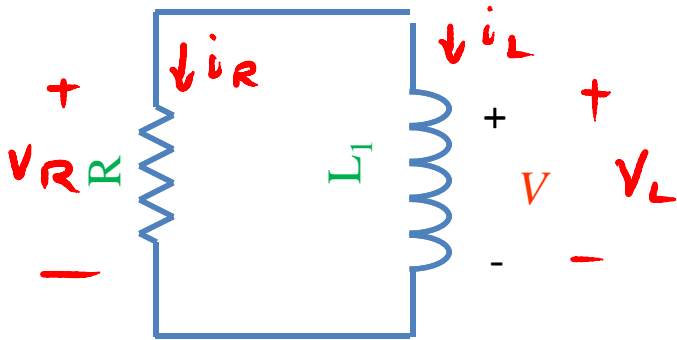

$$KVL \Rightarrow V_L = V_R$$

$$KCL \Rightarrow i_R = -i_L$$

$$L \frac{di_L}{dt} = i_R R$$


$$-i_L R = L \frac{di_L}{dt}$$

$$\Rightarrow \frac{di_L}{dt} = -\frac{1}{\tau} i_L$$


$$V_L = L \frac{di_L}{dt}$$

$$\tau \equiv \frac{L}{R} \quad \text{time constant}$$

$$i_L(t) = i_L(t=0) e^{-t/\tau}$$

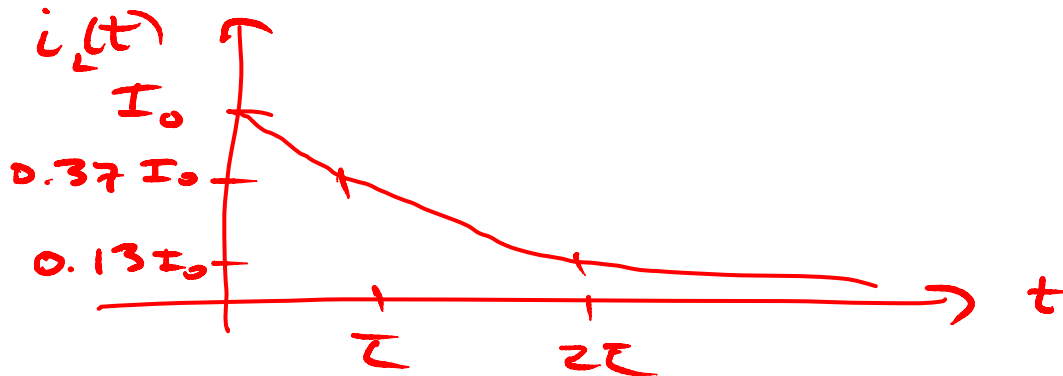


Comprehensive Example

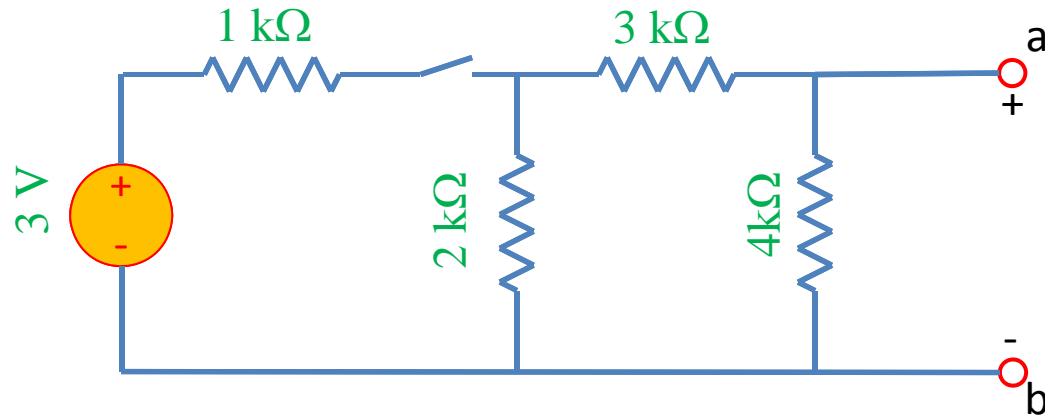


- A) This circuit is connected to a capacitor of value $1 \mu\text{F}$. The switch is in the closed position. After a long time, what are all the voltages and currents in this circuit?
- B) Next, the switch is opened. What are all the voltages and currents in this circuit as a function of time after the switch is opened?
- C) This circuit is now connected to a resistor R_0 . What is the power dissipated in R_0 ?
- D) If you were to pick a value of R_0 to absorb as much power as possible, what would it be?
- E) Exercise: Do the same as A,B with an inductor instead.

Comprehensive Example

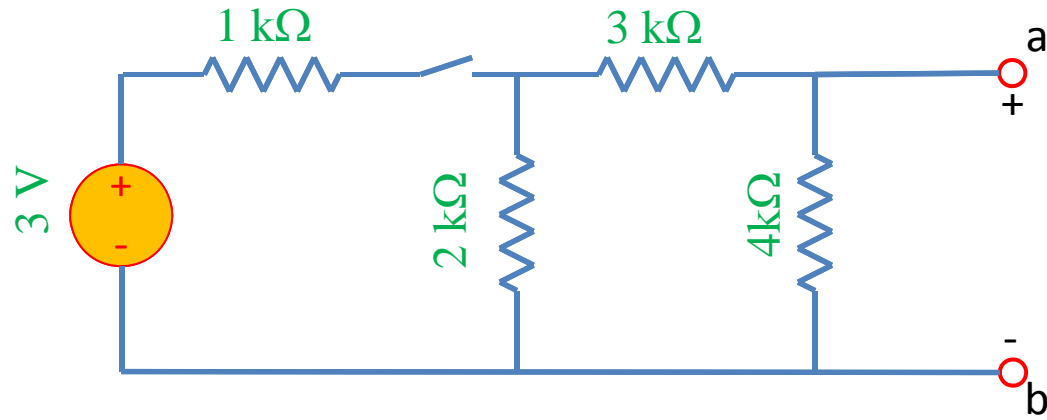

Comprehensive Example

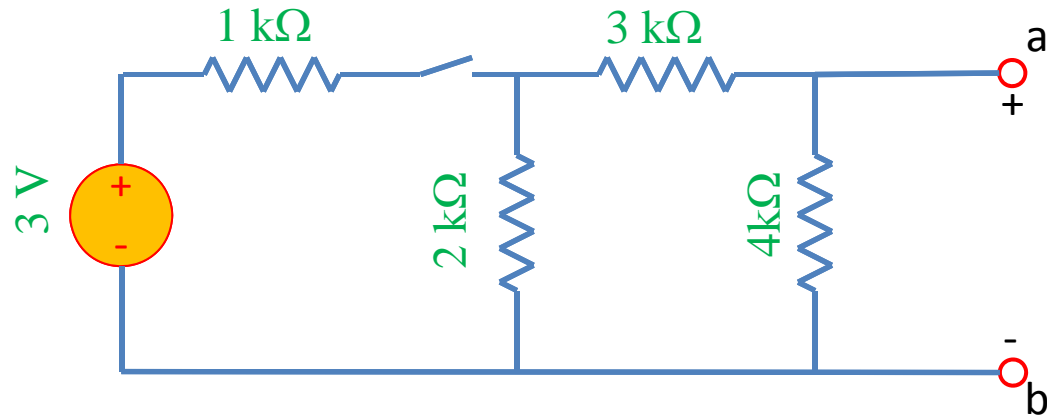

Conversion procedures

$$i(t) \rightarrow \mathbf{I}$$

$$i(t) = I_m \cos(\omega t + \phi) \Rightarrow \mathbf{I} = I_m e^{j\phi}$$

$$v(t) \rightarrow \mathbf{V}$$

$$v(t) = V_m \cos(\omega t + \phi) \Rightarrow \mathbf{V} = V_m e^{j\phi}$$

$$\mathbf{I} \rightarrow i(t)$$


$$i(t) = \operatorname{Re}(\mathbf{I} e^{j\omega t})$$

$$\mathbf{V} \rightarrow v(t)$$

$$v(t) = \operatorname{Re}(\mathbf{V} e^{j\omega t})$$

For the exam, you should know how to carry out these procedures.

Circuits

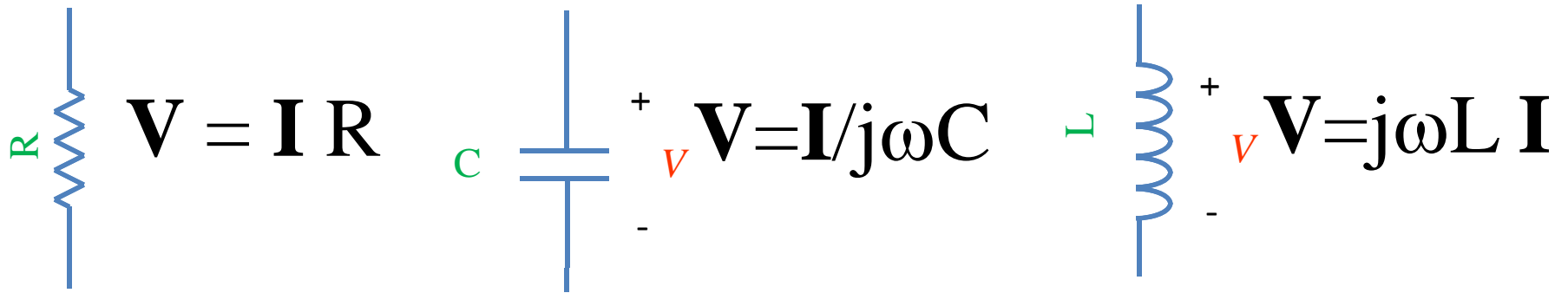

“Impedance”

$$Z = R$$

$$Z = 1 / j\omega C$$

$$Z = j\omega L$$

KCL, KVL hold for relationship
between \mathbf{V} , \mathbf{I} .

Series/Parallel Impedances




$$Z_{eq} = Z_1 + Z_2 + Z_3$$



$$Z_{eq}^{-1} = Z_1^{-1} + Z_2^{-1} + Z_3^{-1}$$

Conversion procedures

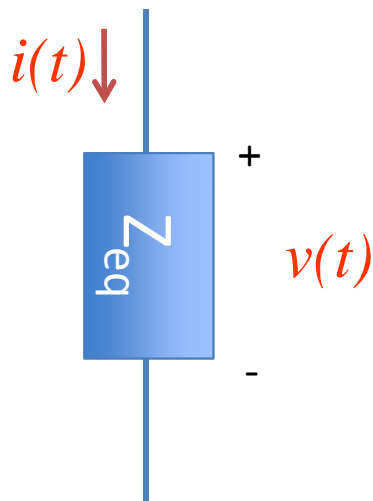

Given $i(t)$ find $v(t)$:

$$i(t) \rightarrow \mathbf{I} \rightarrow \mathbf{V} = \mathbf{I} Z_{eq} \rightarrow v(t)$$

Given $v(t)$ find $i(t)$:

$$v(t) \rightarrow \mathbf{V} \rightarrow \mathbf{I} = \mathbf{V} / Z_{eq} \rightarrow i(t)$$

For the exam, you should know how to carry out these procedures.


“Transfer Function”




$$H(\omega) = \mathbf{V}_{\text{out}} / \mathbf{V}_{\text{in}}$$

Phasor Example 1

Find $v(t)$.

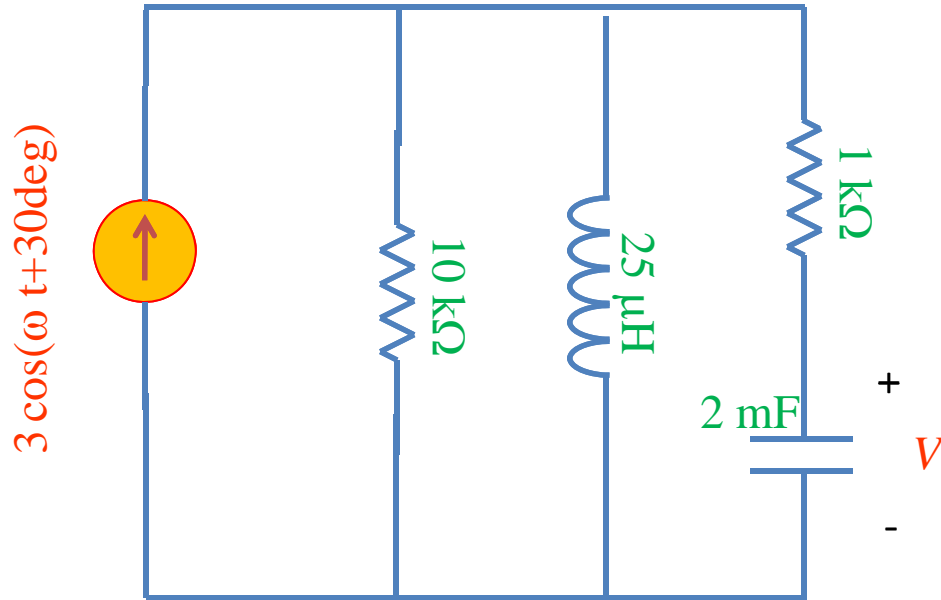


Phasor Example 2

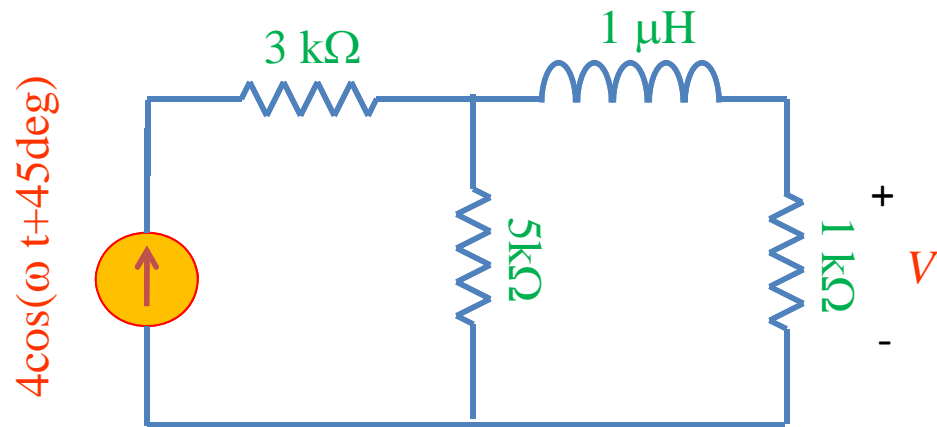



Find $v(t)$.

Example Transfer function

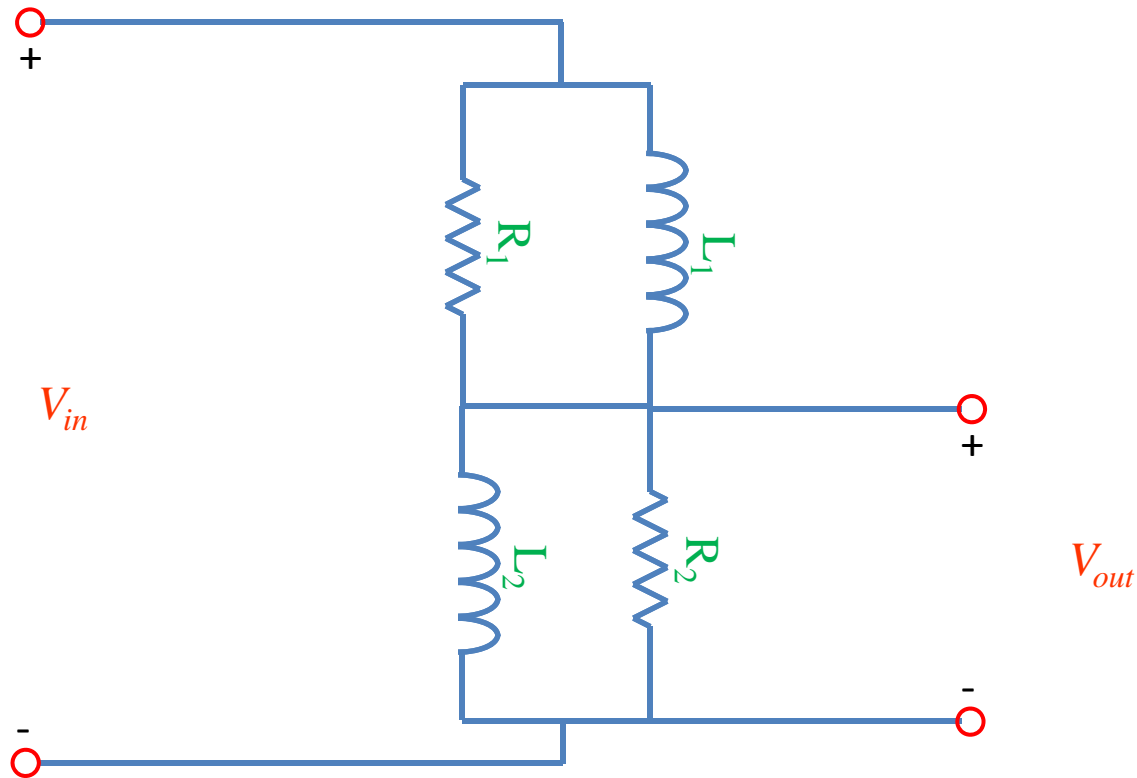

Calculate $H(\omega)$ for this circuit. Sketch the magnitude of $H(\omega)$ vs. ω .

Symbol library

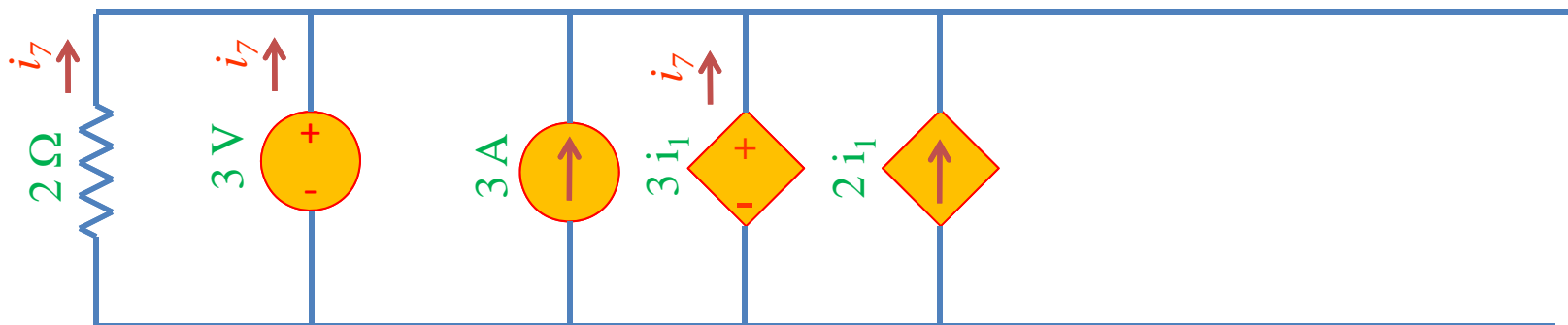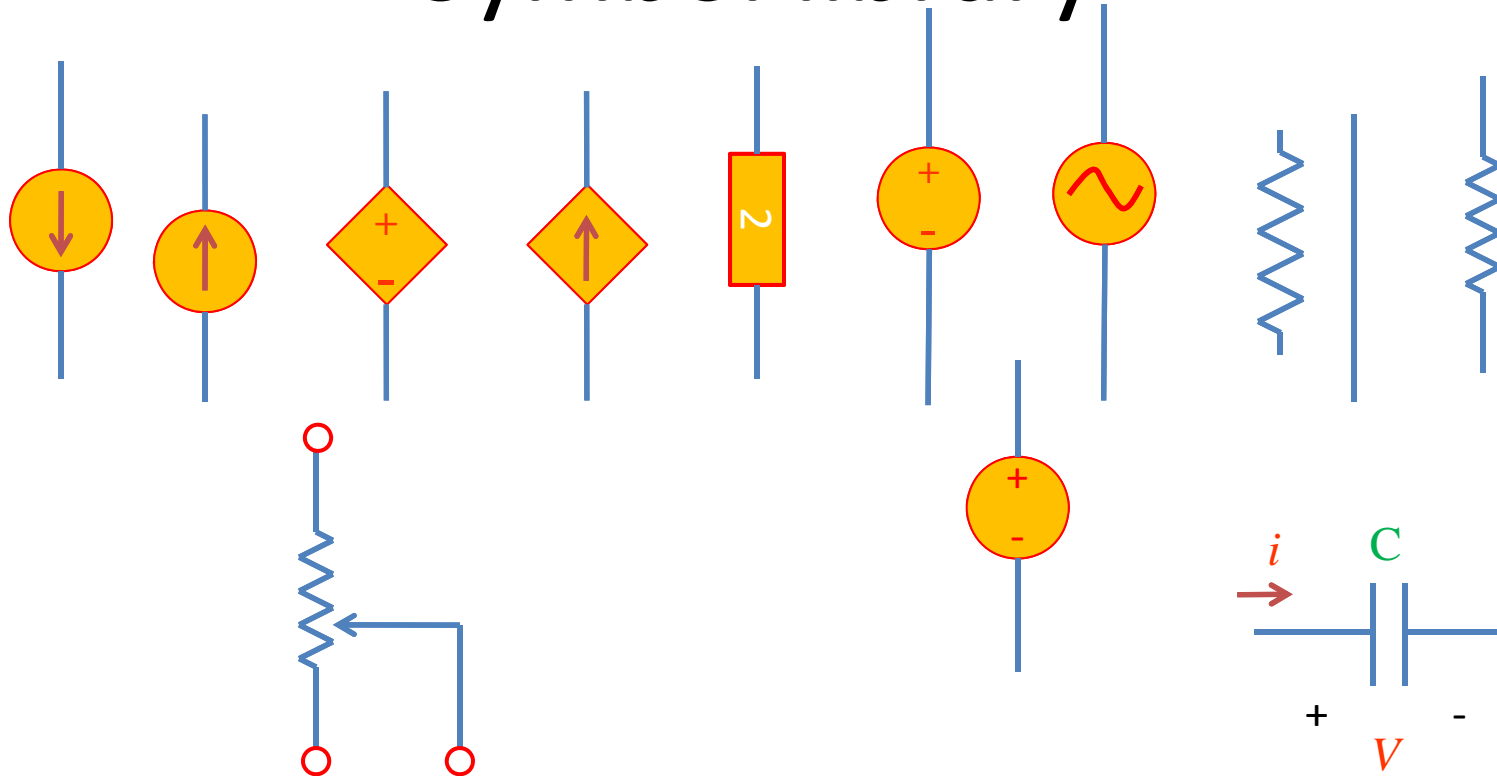

Exam cheat sheet

This will be provided with the exam.

| | | | | | | |
|-----------|-----------------------------|-----------------------------|-----------------------------|-----------------------------|----------------------|-------|
| radians : | 0 | $\frac{\pi}{6}$ | $\frac{\pi}{4}$ | $\frac{\pi}{3}$ | $\frac{\pi}{2}$ | π |
| sin | $\frac{\sqrt{0}}{2}$ | $\frac{\sqrt{1}}{2}$ | $\frac{\sqrt{2}}{2}$ | $\frac{\sqrt{3}}{2}$ | $\frac{\sqrt{4}}{2}$ | 0 |
| cos | $\frac{\sqrt{4}}{2}$ | $\frac{\sqrt{3}}{2}$ | $\frac{\sqrt{2}}{2}$ | $\frac{\sqrt{1}}{2}$ | $\frac{\sqrt{0}}{2}$ | -1 |
| tan | $\frac{\sqrt{0}}{\sqrt{4}}$ | $\frac{\sqrt{1}}{\sqrt{3}}$ | $\frac{\sqrt{2}}{\sqrt{2}}$ | $\frac{\sqrt{3}}{\sqrt{1}}$ | DNE | 0 |

where $\sqrt{\cdot}$ always denotes the positive square root, and DNE means does not exist.