

Announcements:

1. Final HW due Friday of 10<sup>th</sup> week
2. Professor Burke's office hours this week:
  - Tu 9:30-11:30 (EH 2230)
  - Th 9:30-11 (EG 2232)
  - Th 2-3:30 (EH 2230)
3. Exam :
  - Will cover all of Chs. 1,2,3,4,6, 7.1-7.3,  
9 (not delta-Y), 14.1 14.2 14.3 14.5 14.6 14.7
  - Not covered: 3.6, 3.8, 4.9, 6.6.
  - No calculators. We will give sin, cos, tan tables as  
shown on last slide of today's notes..
4. Extra credit (5pts) for students who fill out online course evals.

# EECS 70A: Network Analysis

## Lecture 16

### Comprehensive review


# Topics covered

- KCL, KVL
- Nodal analysis
- Mesh analysis
- Thevenin/Norton theorem
- RL, RC circuits (time dependence)
- R,L,C circuits
  - Phasors
  - Impedances
  - Transfer function


# Thevenin, Norton Theorems:



Equivalent to:

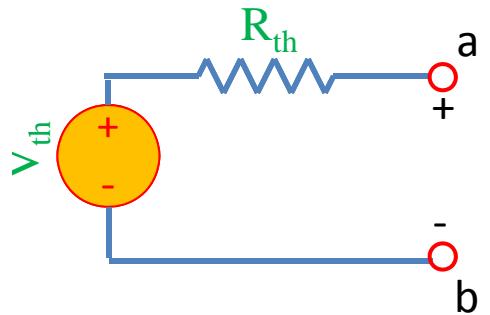

Equivalent to:

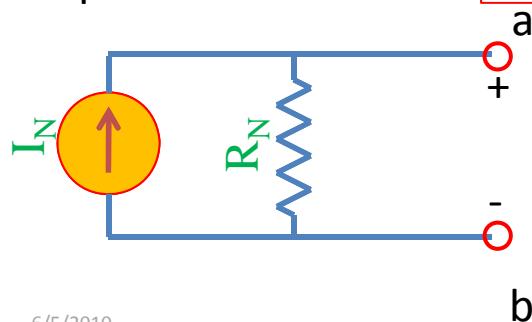

Thevenin:

1. **Calculating  $V_{th}$ :**

Connect nothing to a-b. Calculate voltage. This is  $V_{th}$ .

2. **Calculating  $R_{th}$ :**

Method 1:

Connect terminal a to b (short).

Calculate the current from a to b. This is call  $I_{\text{short circuit}}$ .

$$R_{th} = V_{th} / I_{\text{short circuit}}$$

Method 2:

Find the input resistance looking into terminals a-b after all the independent sources have been turned off.

(Voltage sources become shorts, current sources become opens.)

***Trick (if dependent sources present):***

Apply a 1 A current source to terminals a-b, find  $V_{ab}$

$$R_{th} = V_{ab} / 1A$$

Norton:


1. **Calculating  $R_N$ :**

$$R_N = R_{th}$$

2. **Calculating  $I_N$ :**

$$I_N = V_{th} / R_{th}$$

Find  $V(t)$ ,  $q(t)$ ,  $i(t)$

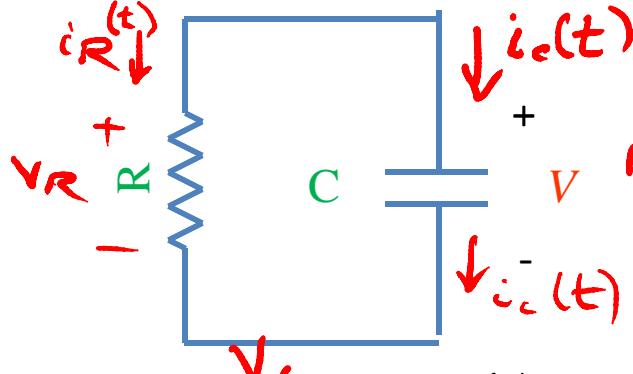


# RC circuit

What is  $i_R(t=0)$

If  $V_c(t=0) = 1 \text{ V}$ ?

$$A: \frac{V}{R}$$

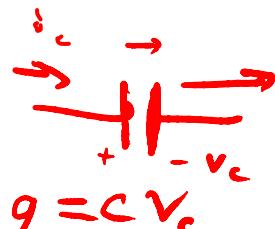


$$q = CV_C \quad i_C = \frac{dq}{dt} = C \frac{dV_C}{dt}$$

$$V_C(t) = V_{C0} e^{-t/RC}$$

NO TIME DEPENDENCE,

CAP = OPEN CIRCUIT

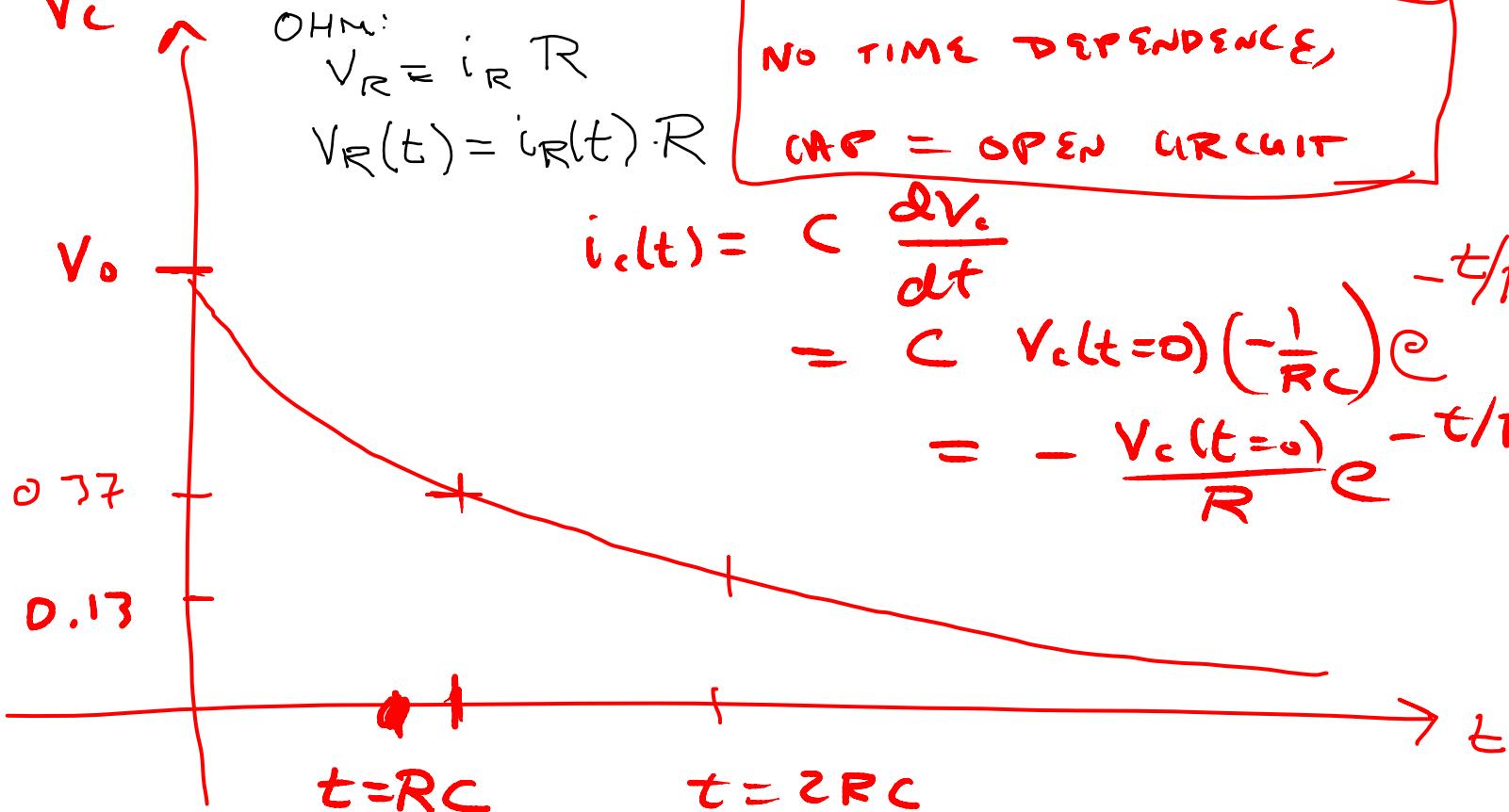
$$\begin{aligned} i_C(t) &= C \frac{dV_C}{dt} \\ &= C V_{C0} \left( -\frac{1}{RC} \right) e^{-t/RC} \\ &= -\frac{V_{C0}}{R} e^{-t/RC} \end{aligned}$$



$$V_R = i_R R$$

## LR circuit

Find  $V(t)$ ,  $i(t)$

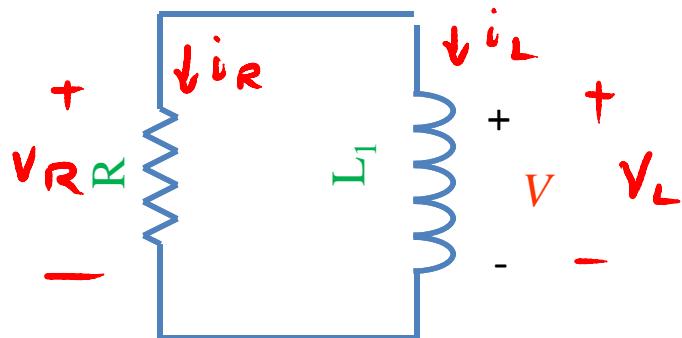

$$KVL \Rightarrow V_L = V_R$$

$$KCL \Rightarrow i_R = -i_L$$

$$L \frac{di_L}{dt} = i_L R$$

$$-i_L R = L \frac{di_L}{dt}$$

$$\Rightarrow \frac{di_L}{dt} = -\frac{1}{L/R} i_L$$



$$V_L = L \frac{di_L}{dt}$$

$$\tau \equiv \frac{L}{R} \quad \text{time constant}$$

$$i_L(t) = i_L(t=0) e^{-t/\tau}$$


$$i_L(t) = i_L(0) e^{-t/\tau}$$
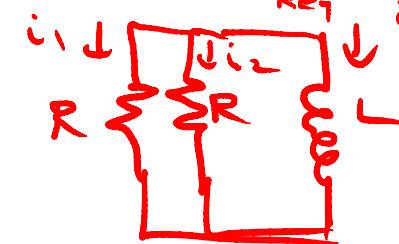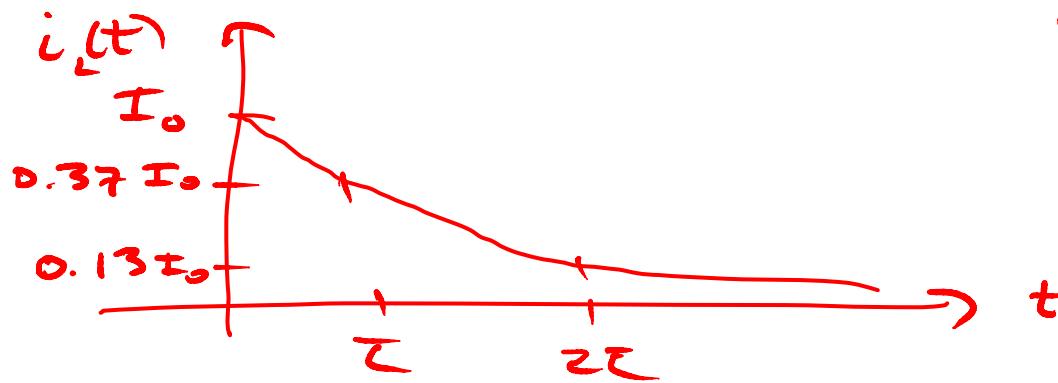
$$\tau = \frac{L}{R} = \frac{L}{i_L R} = \frac{i_L}{i_L R} = \frac{i_L}{R}$$



Given  $i_L(t=0)$   
Find  $i_L(t)$   
 $i_2(t)$


# Comprehensive Example

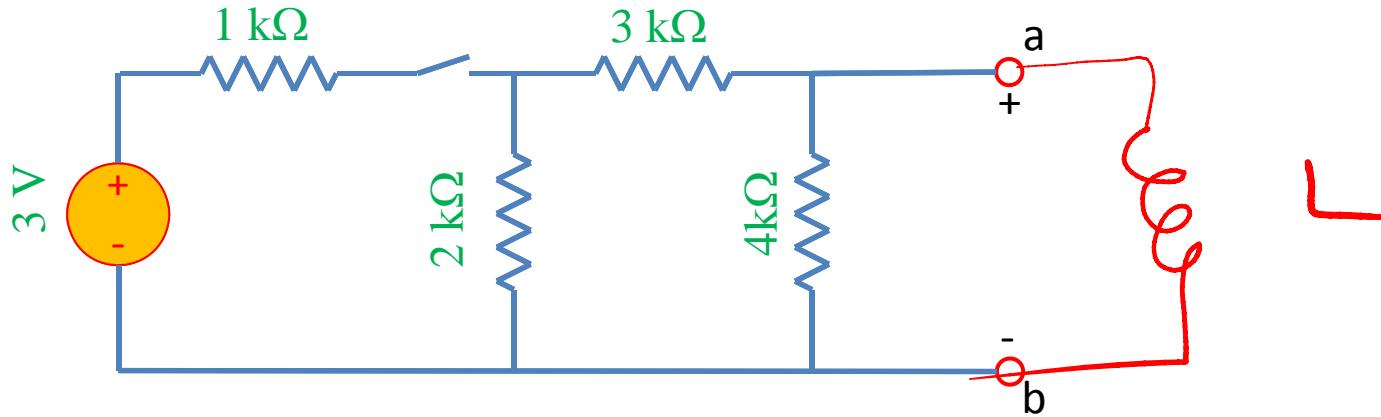

- A) This circuit is connected to a capacitor of value  $1 \mu\text{F}$ . The switch is in the closed position.  
After a long time, what are all the voltages and currents in this circuit?
- B) Next, the switch is opened.  
What are all the voltages and currents in this circuit as a function of time  
after the switch is opened?
- C) This circuit is now connected to a resistor  $R_0$ . What is the power dissipated in  $R_0$ ?
- D) If you were to pick a value of  $R_0$  to absorb as much power as possible, what would it be?
- E) Exercise: Do the same as A,B with an inductor instead.



(A)

# Comprehensive Example

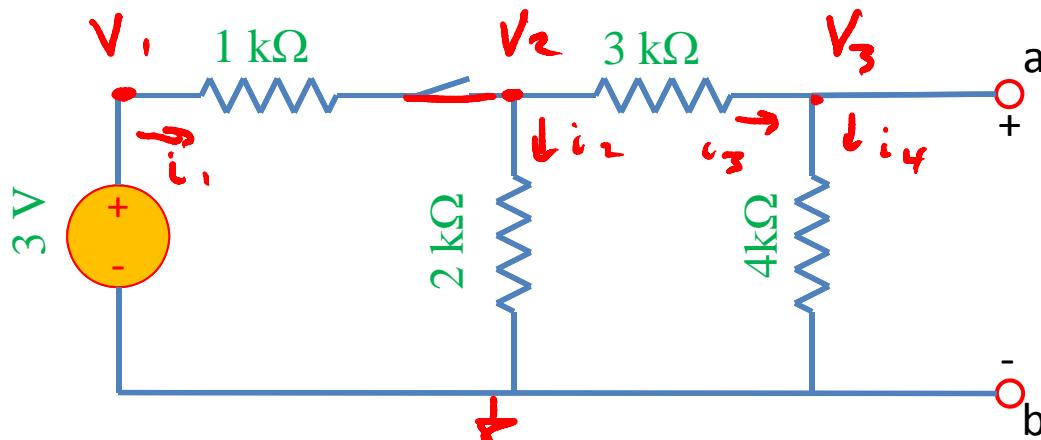

zways

- 1) Nodal
- 2) Ser./Par.

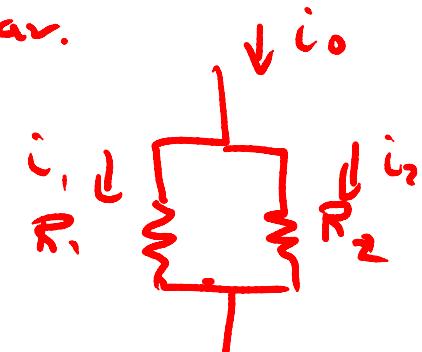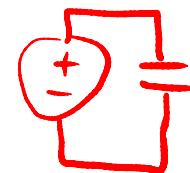Node :

$$V_1 = 3V$$


$$i_1 = i_2 + i_3 \Rightarrow \frac{V_2 - 3V}{1k\Omega} = \frac{V_2}{2k\Omega} + \frac{V_3 - V_2}{3k\Omega}$$

$$i_3 = i_4 \Rightarrow \frac{V_3 - V_2}{3k\Omega} = \frac{V_3}{4k\Omega}$$

Solve  $V_2, V_3$  then  $i_1 - i_4$ 

(1)

$$i_1 = \frac{R_2}{R_1 + R_2} i_o$$

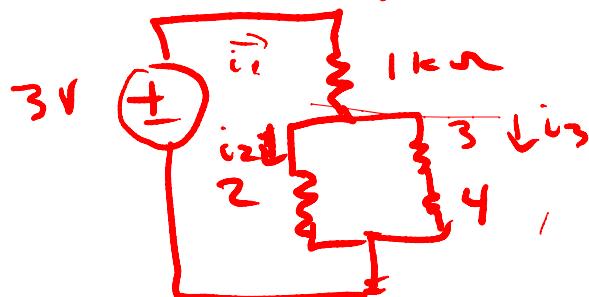"Easier way"

$$i_1 = \frac{3V}{1 + 2 \parallel (3+4) k\Omega} = \frac{3}{1 + 2 \parallel 7} \text{ mA}$$


$$= \frac{3}{1 + \frac{2 \cdot 7}{2+7}} = \dots$$

$$i_2 = i_1 \frac{3+4}{2 + (3+4)}$$


$$V_3 = \frac{24}{23} V$$

B

# Comprehensive Example

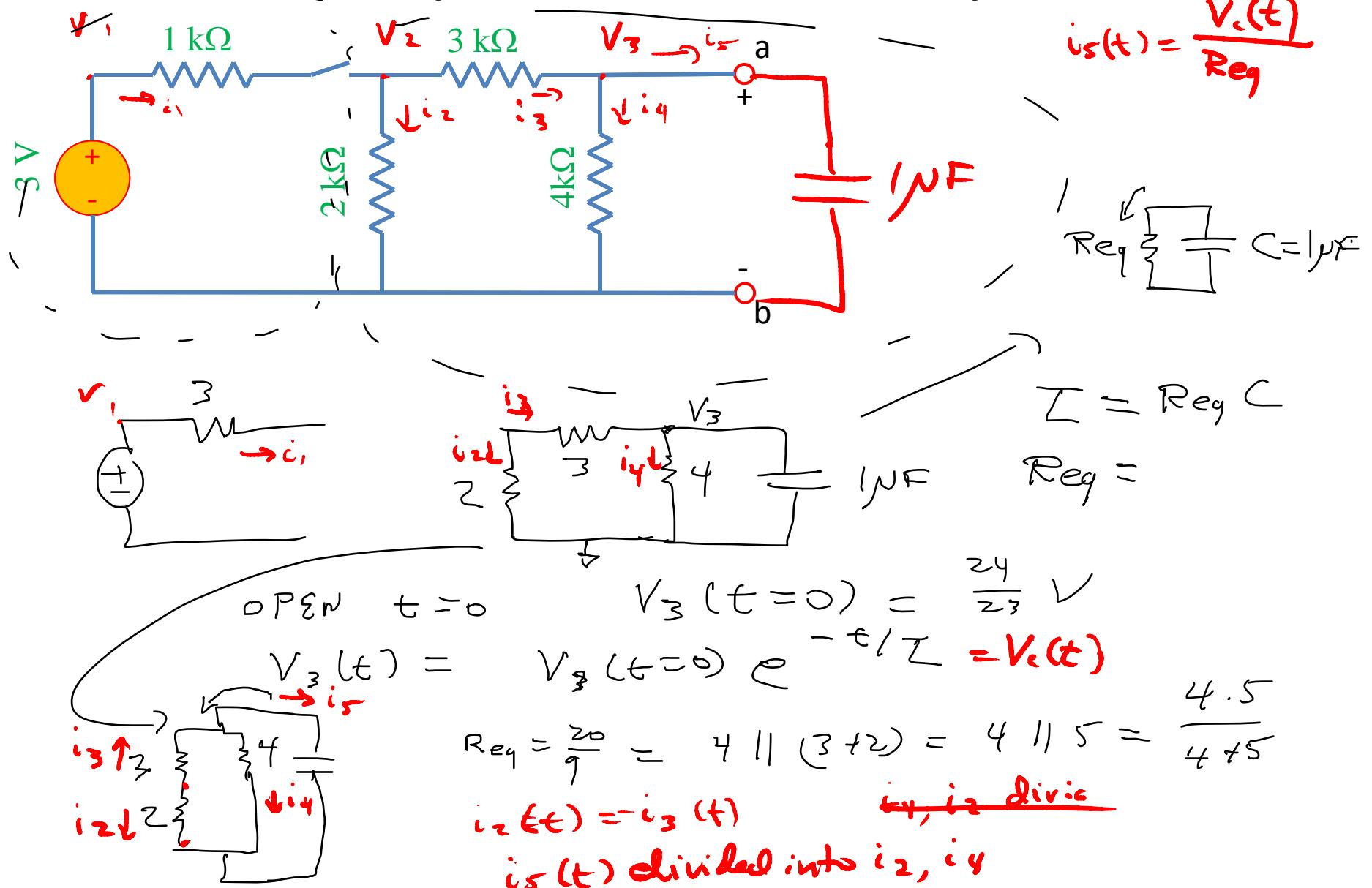

# Comprehensive Example

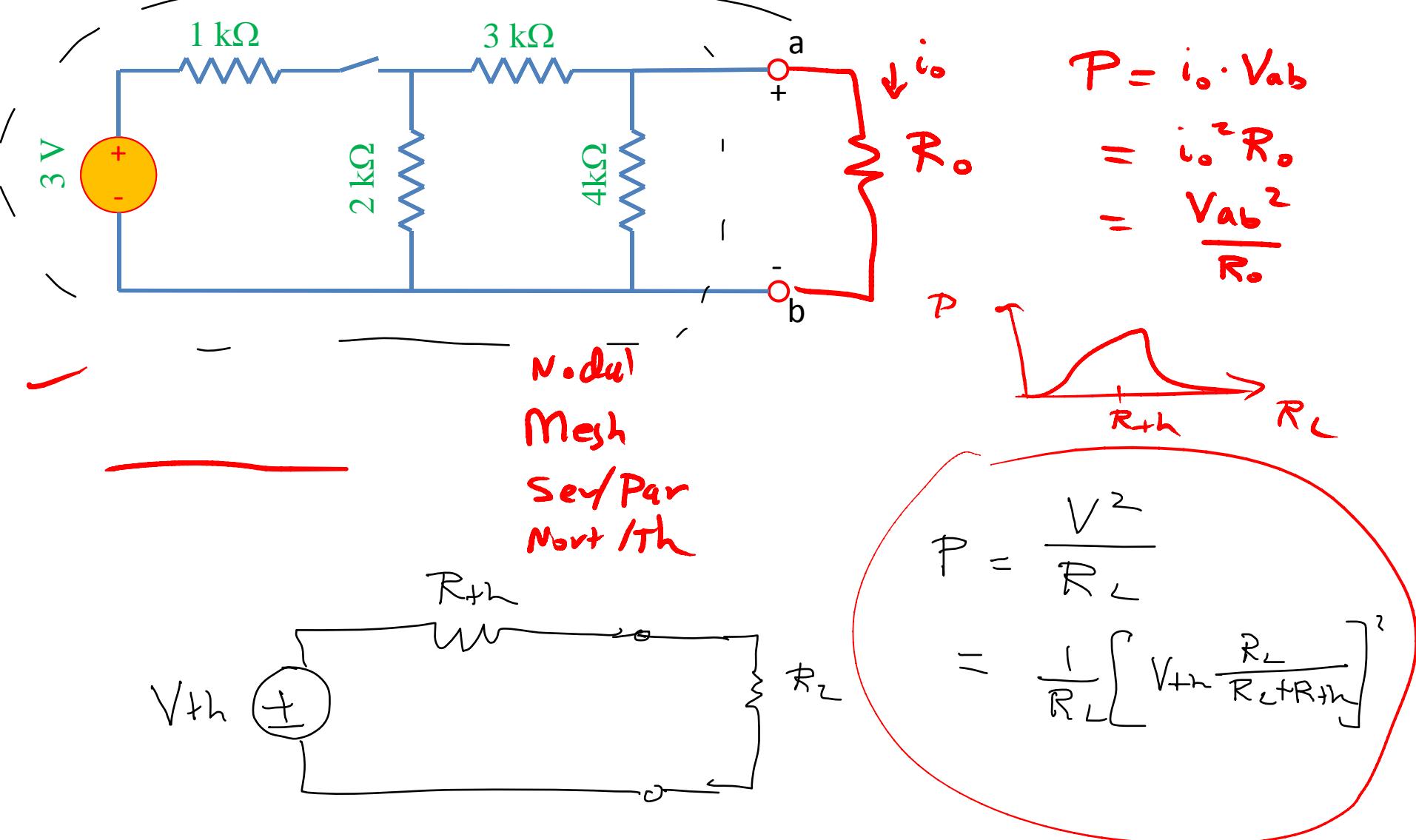

# Conversion procedures

$$\mathbf{i(t)} \rightarrow \mathbf{I} \quad i(t) = I_m \cos(\omega t + \phi) \Rightarrow \mathbf{I} = I_m e^{j\phi}$$

$$\mathbf{v(t)} \rightarrow \mathbf{V} \quad v(t) = V_m \cos(\omega t + \phi) \Rightarrow \mathbf{V} = V_m e^{j\phi}$$

$$\mathbf{I} \rightarrow \mathbf{i(t)} \quad i(t) = \operatorname{Re}(\mathbf{I} e^{j\omega t})$$

$$\mathbf{V} \rightarrow \mathbf{v(t)} \quad v(t) = \operatorname{Re}(\mathbf{V} e^{j\omega t})$$

For the exam, you should know how to carry out these procedures.

# Circuits

The diagram shows three circuit elements: a resistor ( $R$ ), a capacitor ( $C$ ), and an inductor ( $L$ ). Each element is shown with its symbol and a voltage drop  $V$  indicated by a red arrow pointing downwards across it. The resistor is represented by a blue zigzag line, the capacitor by two vertical lines with a horizontal bar between them, and the inductor by a blue coil.

$$V = I R \quad C \quad V = I/j\omega C \quad L \quad V = j\omega L I$$

“Impedance”

$$Z = R$$

$$Z = 1/j\omega C$$

$$Z = j\omega L$$

KCL, KVL hold for relationship  
between  $V$ ,  $I$ .

# Series/Parallel Impedances




$$Z_{\text{eq}} = Z_1 + Z_2 + Z_3$$



$$Z_{\text{eq}}^{-1} = Z_1^{-1} + Z_2^{-1} + Z_3^{-1}$$

# Conversion procedures

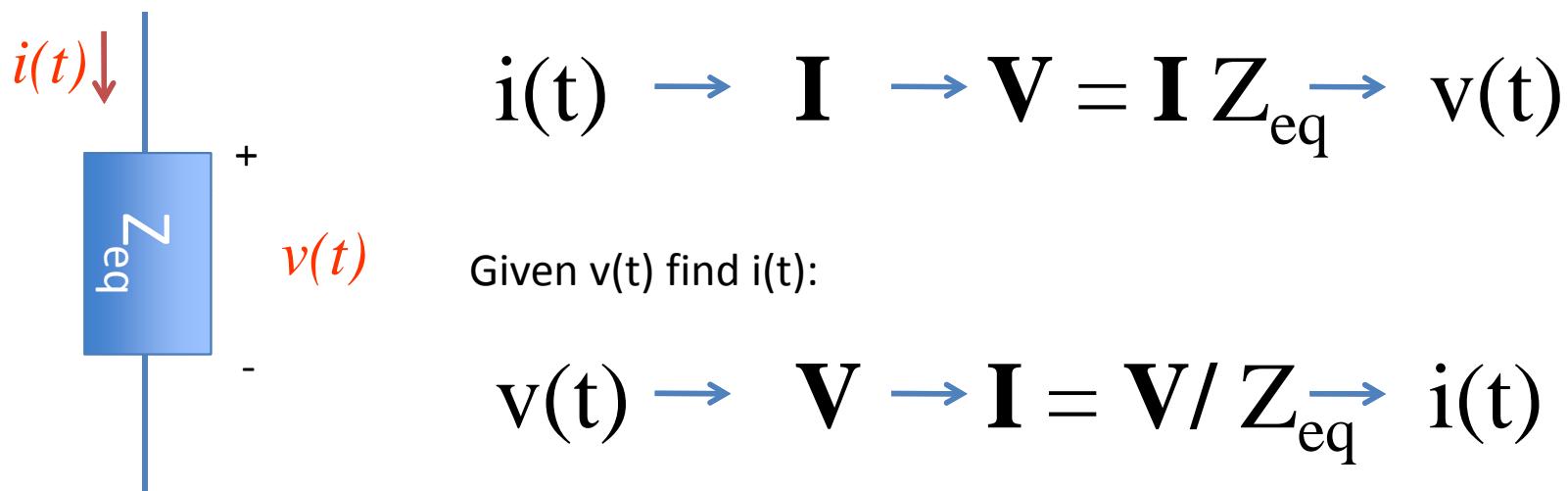




For the exam, you should know how to carry out these procedures.

# “Transfer Function”



$$H(\omega) = V_{\text{out}} / V_{\text{in}}$$

# Phasor Example 1

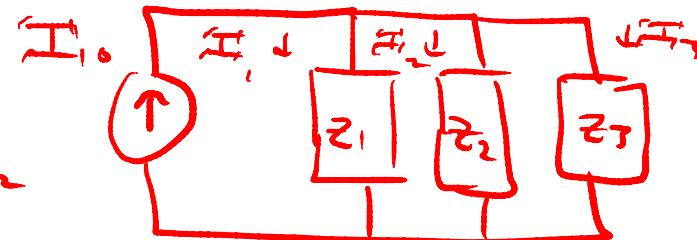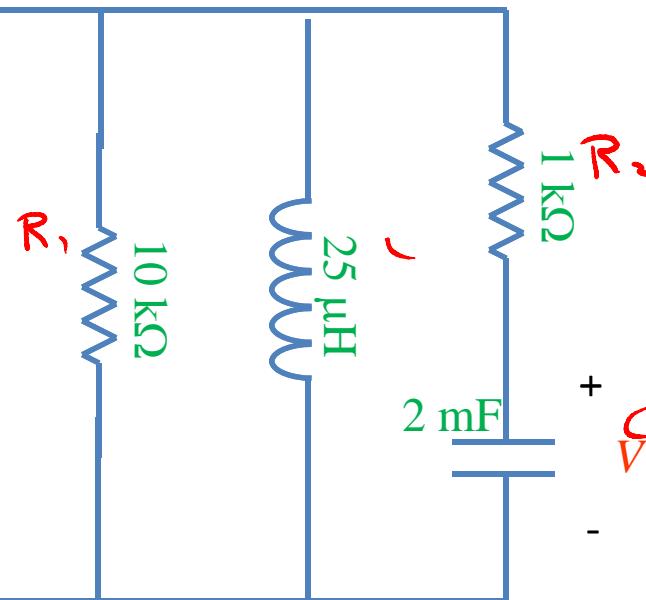
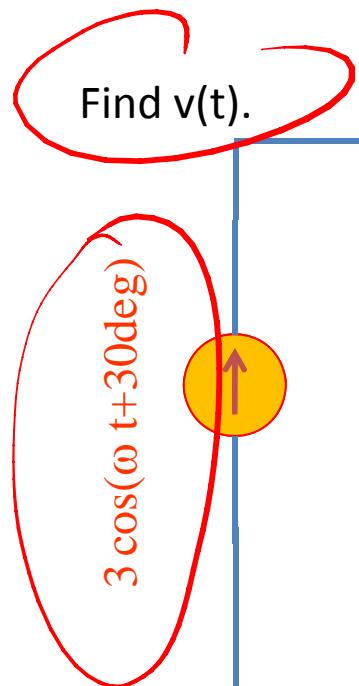


$$Z_1 = R_1$$

$$Z_2 = L_i \omega$$

$$Z_3 = R_2 + \frac{1}{j\omega C} e^{j30^\circ} \cdot \frac{\pi}{6}$$

$$H'_o = 3e^{j30^\circ} = 3e^{j\pi/6}$$

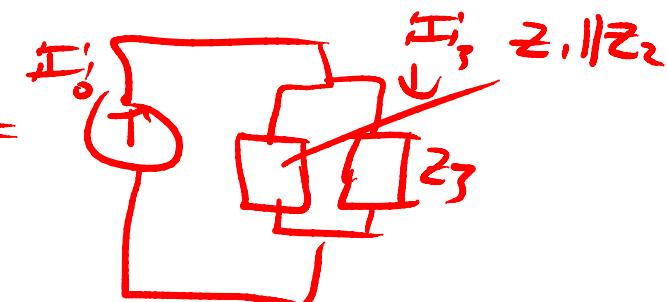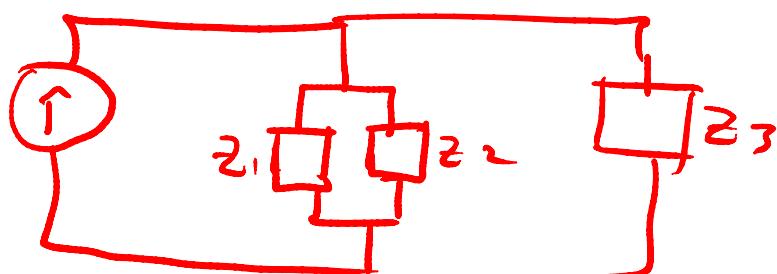

$$I'_3 = H'_o \frac{(Z_1 // Z_2)}{Z_3 + (Z_1 // Z_2)}$$

$$V_c = I'_3 \frac{1}{j\omega C}$$


$$v(t) = \operatorname{Re}(V_c e^{j\omega t})$$

answer

$$V(t) = \operatorname{Re} \left[ \frac{1}{j\omega C} \frac{\frac{R_1 j\omega L}{R_1 + j\omega L}}{\frac{R_1 j\omega L}{R_1 + j\omega L} + R_2 + \frac{1}{j\omega C}} 3e^{\frac{j\pi/6}{j\omega C}} e^{j\omega t} \right]$$



       . . -

# Phasor Example 2

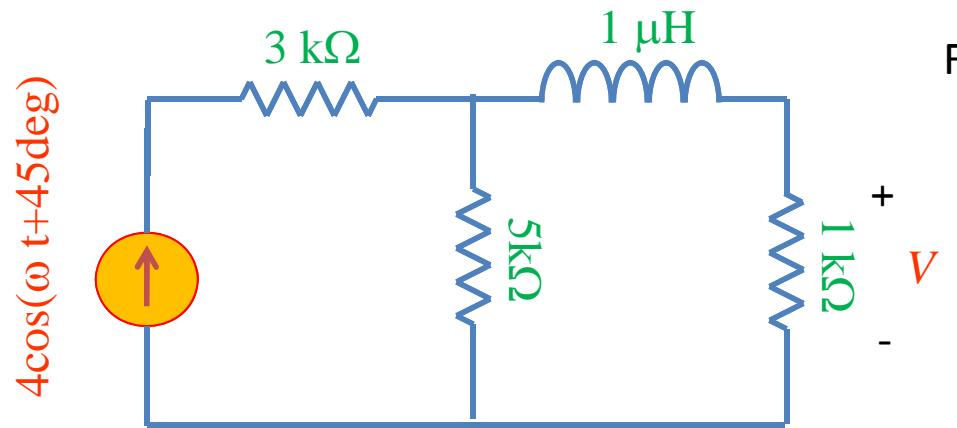


Find  $v(t)$ .

# Example Transfer function

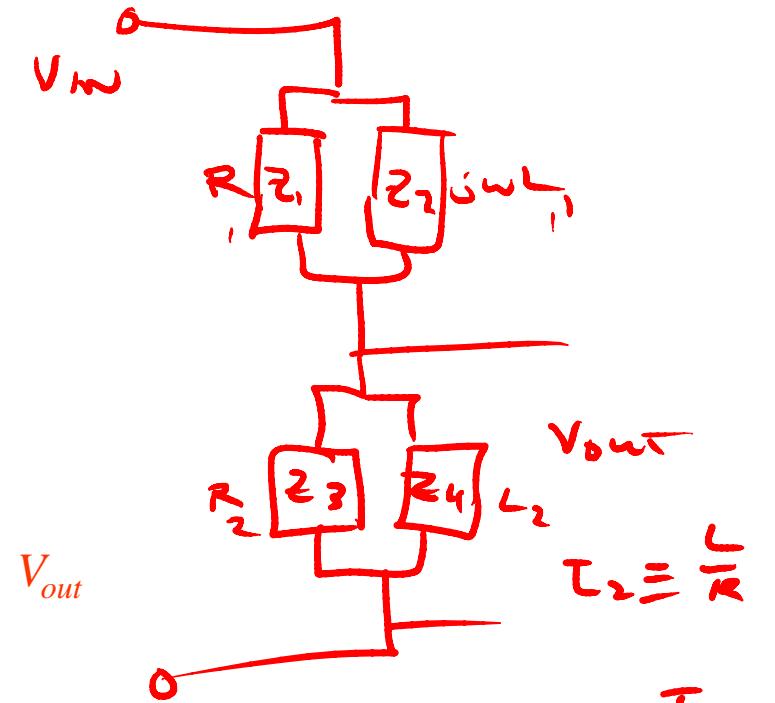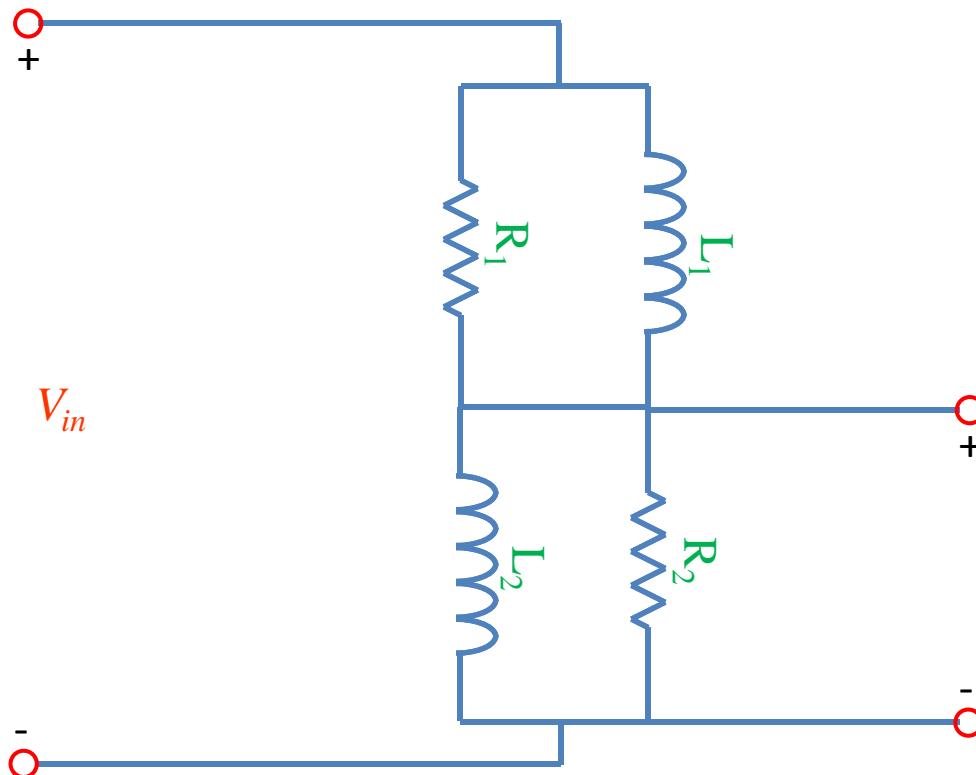

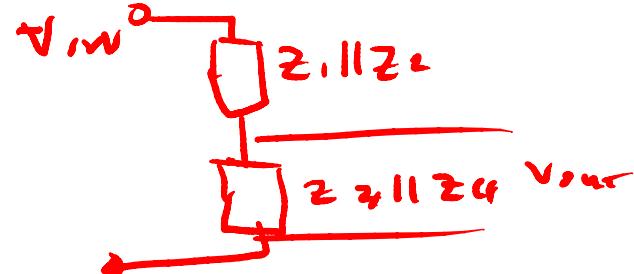Calculate  $H(\omega)$  for this circuit. Sketch the magnitude of  $H(\omega)$  vs.  $\omega$ .



$$\begin{aligned} \frac{V_{out}}{V_{in}} &= \frac{(Z_3 \parallel Z_4)}{(Z_3 \parallel Z_4) + (Z_1 \parallel Z_2)} \\ H(\omega) &= \frac{\frac{j\omega L_2}{1+j\omega\tau_2}}{Z_1 \parallel Z_2 + \frac{j\omega L_1}{1+j\omega\tau_1}} \end{aligned}$$

$$R \parallel L$$

$$\frac{j\omega L}{1 + j\omega\tau}$$

$$\tau \equiv \frac{L}{R}$$

$$H(\omega) =$$

$$\frac{j\omega L_1}{1 + j\omega\tau_1} + \frac{j\omega L_2}{1 + j\omega\tau_2}$$

~~$j\omega L_2$~~   
 ~~$1 + j\omega\tau_2$~~   
 ~~$j\omega L_1$~~   
 ~~$1 + j\omega\tau_1$~~


$$\tau_1 = \frac{L_1}{R_1}$$

$$\tau_2 = \frac{L_2}{R_2}$$


$$\tau_2 = L_2/R_2$$

$$\tau_1 = L_1/R_1$$
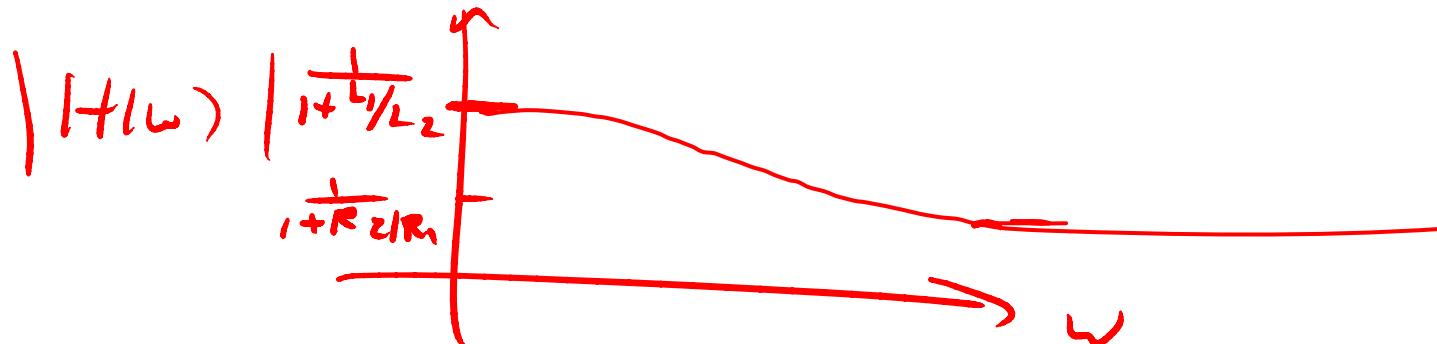
$$= \frac{1}{1 + \frac{1 + j\omega\tau_2}{1 + j\omega\tau_1} \frac{L_1}{L_2}}$$



# Symbol library

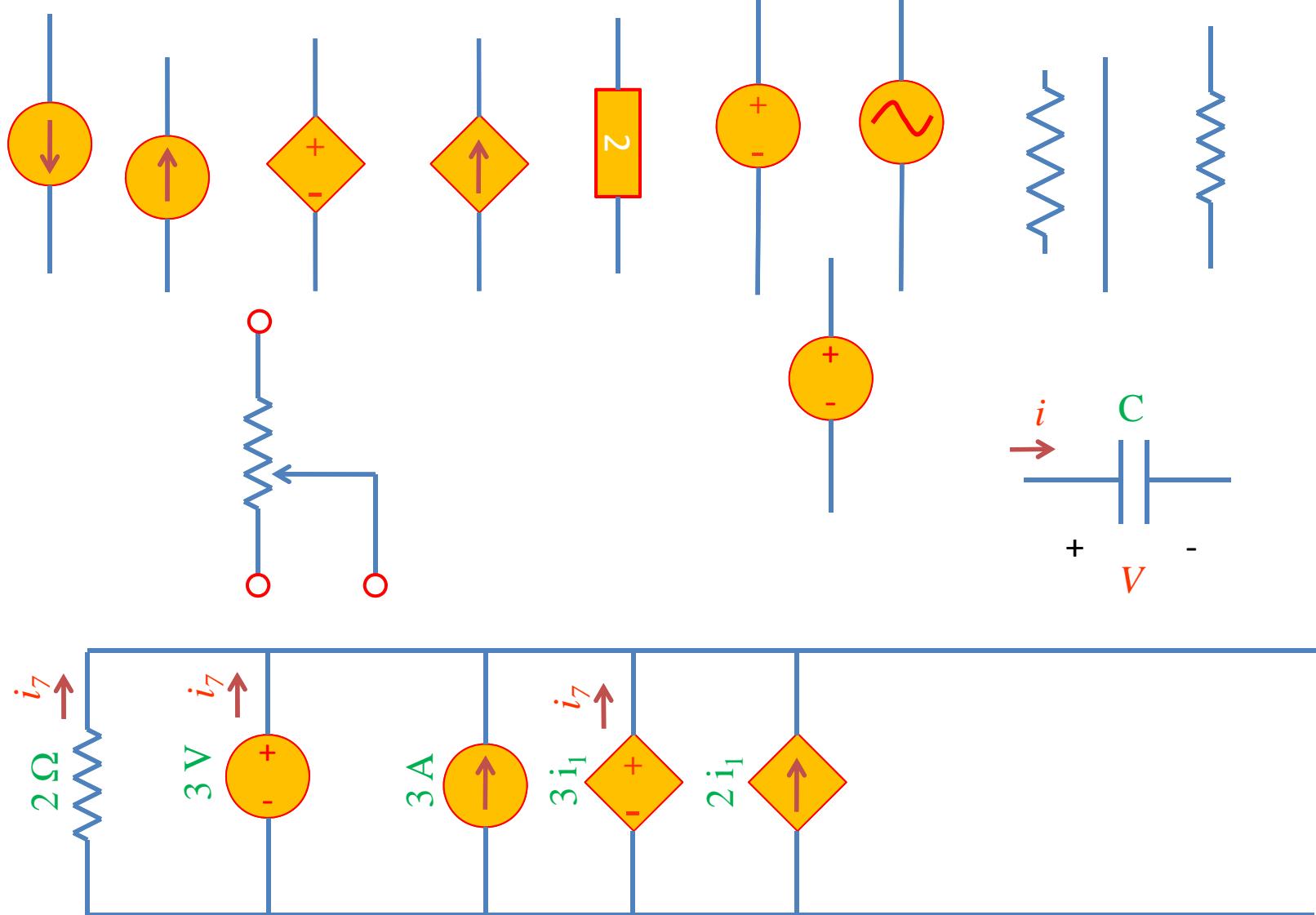

# Exam cheat sheet

This will be provided with the exam.

radians :	0	$\frac{\pi}{6}$	$\frac{\pi}{4}$	$\frac{\pi}{3}$	$\frac{\pi}{2}$	$\pi$
sin	$\frac{\sqrt{0}}{2}$	$\frac{\sqrt{1}}{2}$	$\frac{\sqrt{2}}{2}$	$\frac{\sqrt{3}}{2}$	$\frac{\sqrt{4}}{2}$	0
cos	$\frac{\sqrt{4}}{2}$	$\frac{\sqrt{3}}{2}$	$\frac{\sqrt{2}}{2}$	$\frac{\sqrt{1}}{2}$	$\frac{\sqrt{0}}{2}$	-1
tan	$\frac{\sqrt{0}}{\sqrt{4}}$	$\frac{\sqrt{1}}{\sqrt{3}}$	$\frac{\sqrt{2}}{\sqrt{2}}$	$\frac{\sqrt{3}}{\sqrt{1}}$	DNE	0

where  $\sqrt{\cdot}$  always denotes the positive square root, and DNE means does not exist.