

# EECS 70A: Network Analysis

## Lecture 1

# Northeast Blackout 2003


What:

- 256 power plants down
- 55 million people affected

How did this happen?


ISAT GeoStar 45  
23:15 EST 14 Aug. 2003

# Power Networks

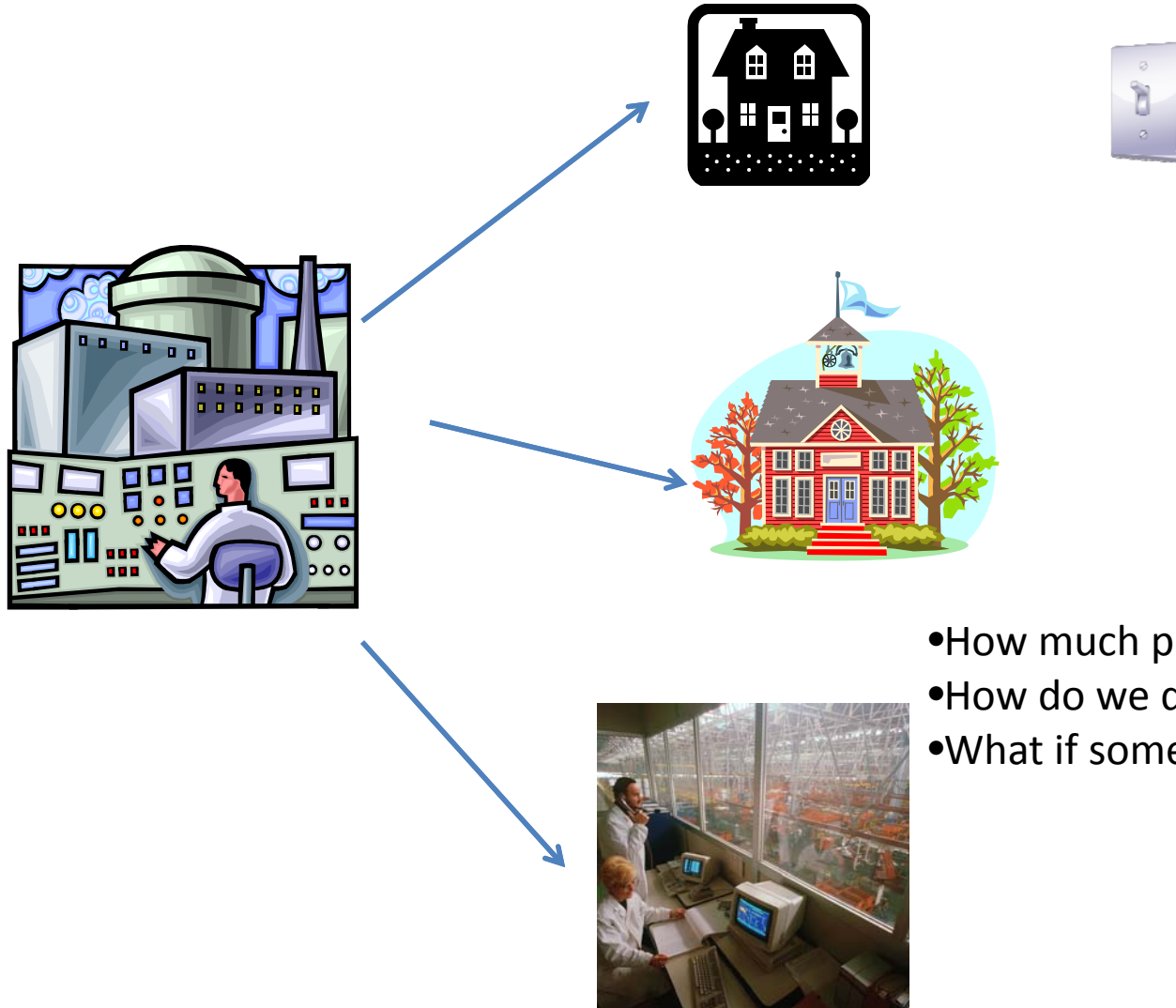

- How much power used?
- How do we quantify power?
- What if someone turns on one light?

# Digital circuits

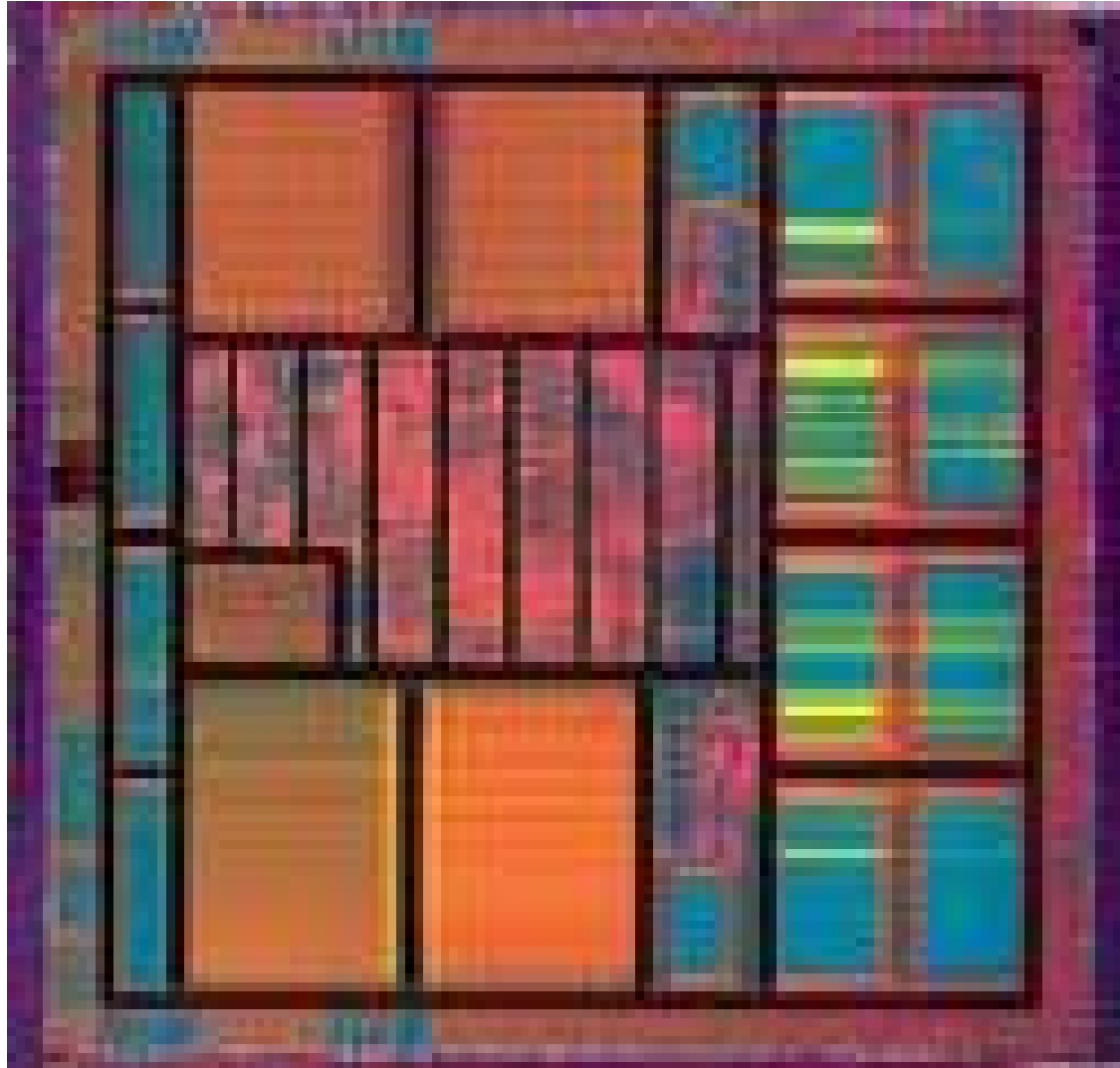

- How do we understand what every transistor is doing?
- There are *hundreds of millions...*

# Simplifications

Leon Charles Thevenin  
1857–1926



Edward Lawry Norton  
1898–1983



Ultimate problem solvers: Take a complex system, break it into its component parts:

***Network analysis***

# Current

*DEMO...*

Charge of an electron:


$$e = -1.6 \times 10^{-19} \text{ Coulomb [C]}$$

Current is flow of charge.

In a wire, charges are free electrons.

$$i = dq/dt$$
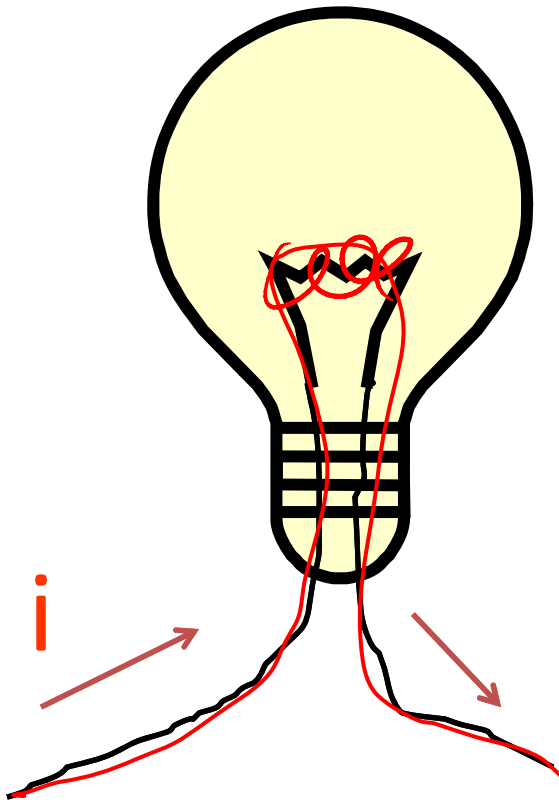
$$\text{Amperes [A]} = \text{Coulombs/second [C]/[s]}$$



# Examples

1 electron per second flows past a plane.

What is the current? (instructor)


$$i = \frac{dq}{dt} = \frac{1.6 \times 10^{-19} \text{ C}}{1 \text{ sec}} = 1.6 \times 10^{-19} \frac{\text{C}}{\text{s}} = \underline{1.6 \times 10^{-19} \text{ A}}$$

10 A of current flows.

How many electrons per second flow past a plane? (students)


$$i = 10 \text{ A} = 10 \frac{\text{C}}{\text{s}} \quad \# = \frac{10 \frac{\text{C}}{\text{s}}}{1.6 \times 10^{-19} \text{ C}} = \frac{1}{1.6} 10^{-18} \frac{1}{\text{s}}$$

# Demo circuit: Current source

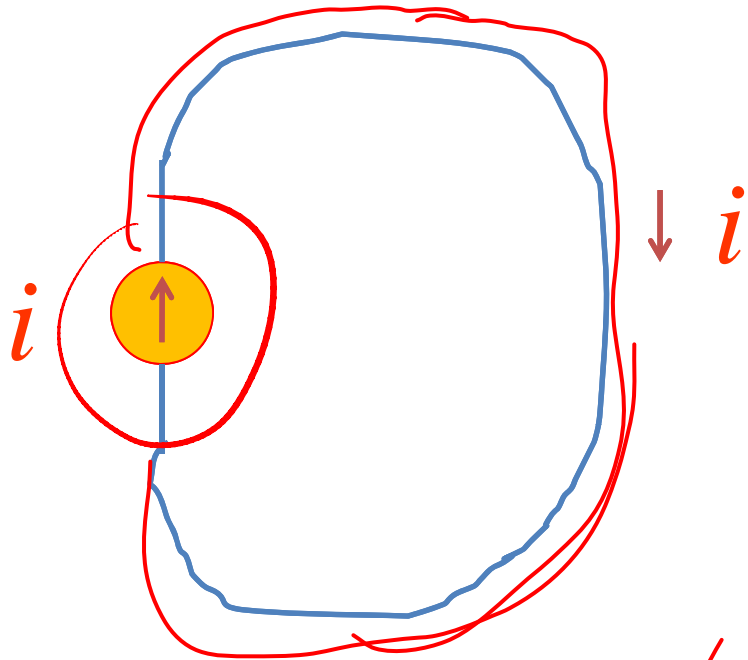

*DEMO...*

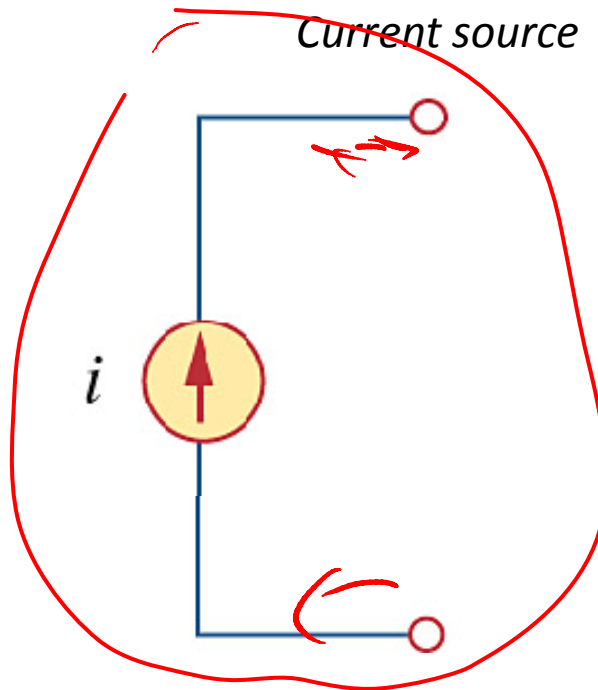Our first circuit element:  
*Current source*






# Voltage

Physically, how do we get electrons to move? Apply a force.

$$F = eE$$

$$\int_a^b E dx = V_{ab} = V_a - V_b = \Delta V$$

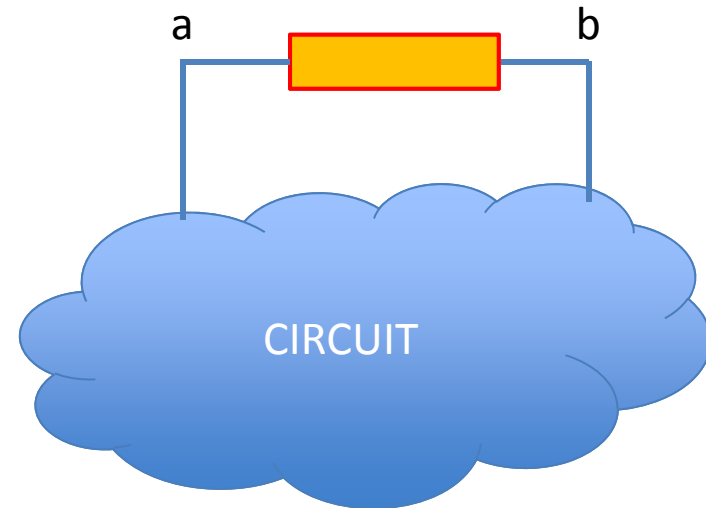$V_{ab} \neq 0 \Rightarrow$  electrons pushed  $a$  to  $b$ ,  
causing current to flow




E electric field: Volts/meter [V/m]

V voltage (aka potential difference): Volts [V]

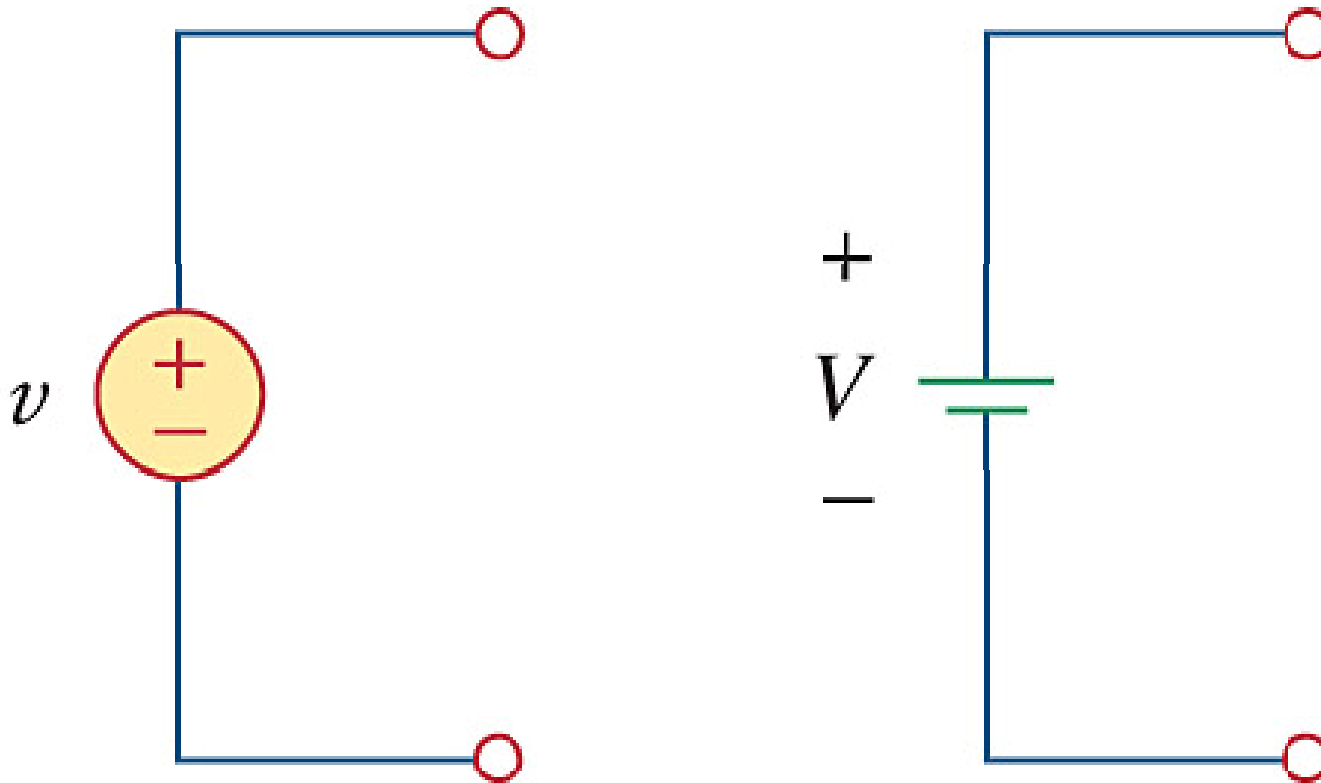
# Voltage source

Our next circuit element:  
*Voltage source*




Makes  $V_{ab}$  constant, regardless of how much current flows through it.

# Dependent sources

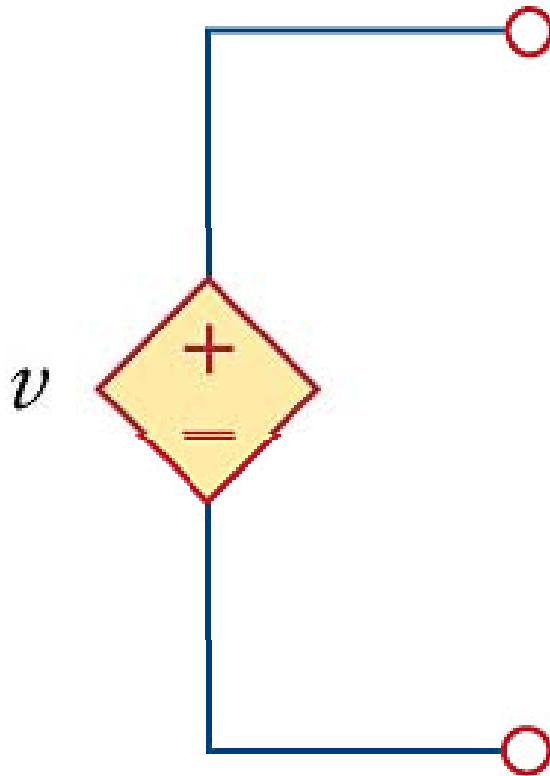

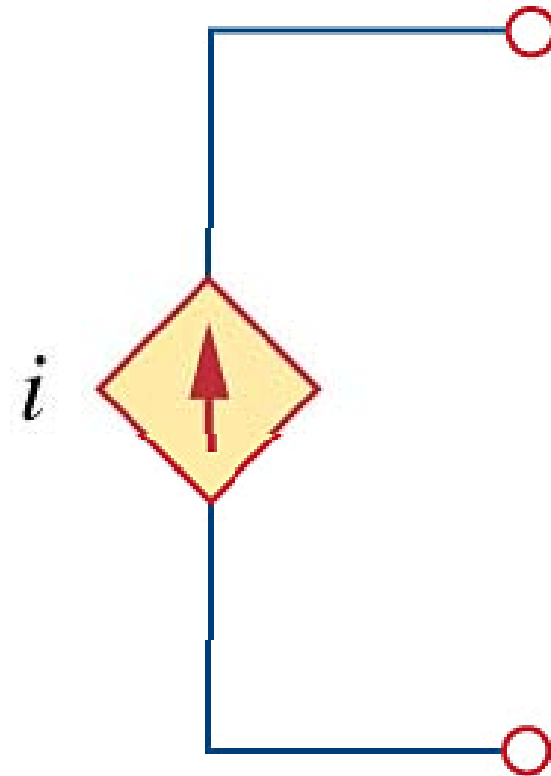Value of voltage is determined by something somewhere else in circuit.



Value of current is determined by something somewhere else in circuit.


b  $\left[ \begin{array}{l} \text{V (VS)} \\ \text{CCVS} \end{array} \right.$

voltage dependent voltage source  
curr. dep. volt source
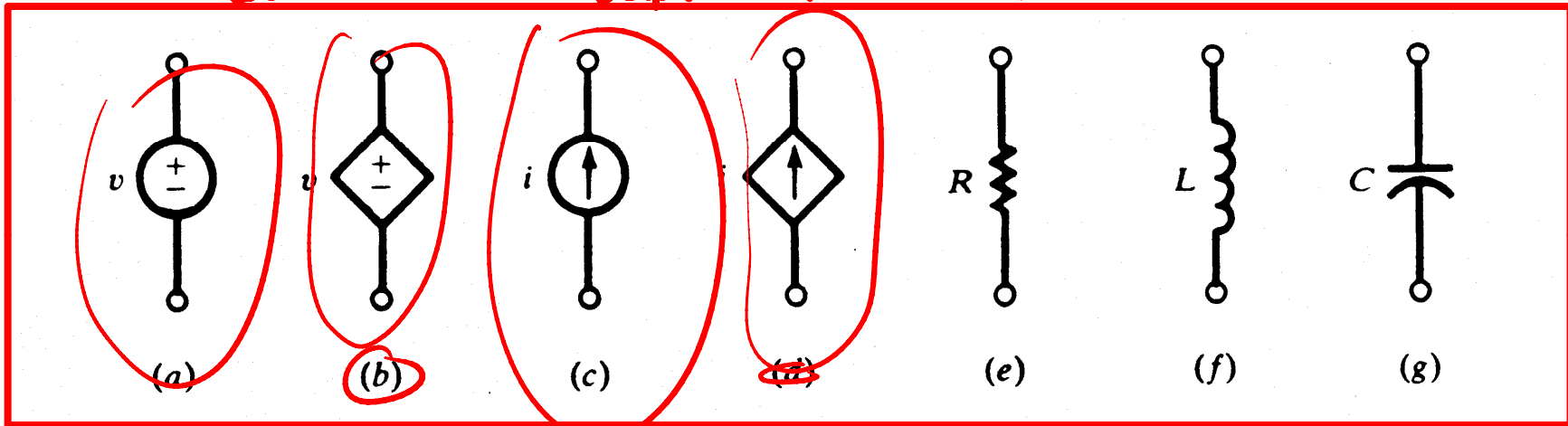
# Circuit elements

d  $\left[ \begin{array}{l} \text{VCCS} \\ \text{ECCS} \end{array} \right.$

Voltage dep curr. source  
curr. dep. curr source




Independent sources

Dependent sources

- A dependent source is an active element in which the source quantity is controlled by another voltage or current.
- They have four different types: VCVS, CCVS, VCCS, CCCS. Keep in mind the signs of dependent sources.

# Power

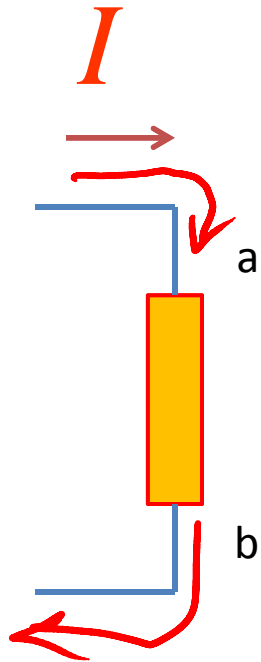

$$I \times V_{ab} = \text{power}$$


Watts [W] = Volt Amp [V-A]

Note: MKSA unit system:  
Meters Kilogram Second Amp

M K S A  
 e i e m  
 + i e m  
 e r o o P  
 r g o o P  
 m a s e


$\left\{ \begin{array}{l} C \text{ Coulomb} \\ W \text{ Watt} \\ J \text{ Joule} \\ V \text{ Volt} \end{array} \right.$

# Examples

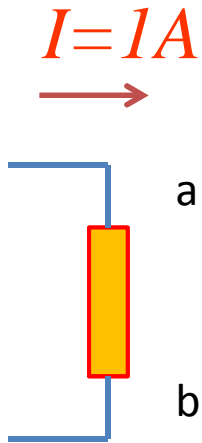

$V_{ab} = 100 \text{ Volts}$   
 $P = ?$  (instructor)

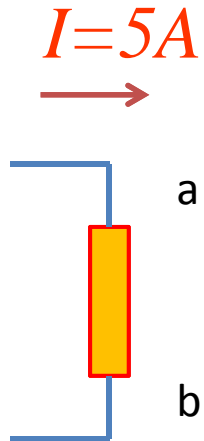
*current*  
 $P = I V_{ab} =$   
 $= 1 A = 100 V = 100 A \cdot V$   
*unit*      *unit* = 100W



$P = 10 \text{ W}$   
 $V_{ab} = ?$   
 (students)

$V_{ab} = 2V$   
 $W = A \cdot V$   
 $P = I V$        $V = \frac{P}{I} = \frac{10W}{5A} = 2 \frac{W}{A} = 2V$

# Sign convention

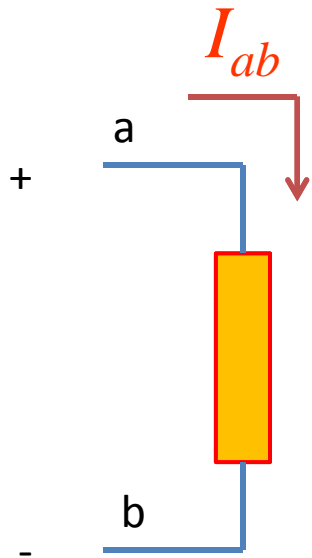

$V_{ab}$  positive  $\Rightarrow V_a > V_b$


$I_{ab}$  positive  $\Rightarrow$  current flows from a to b


$V_{ab}$  negative  $\Rightarrow V_a < V_b$

$I_{ab}$  negative  $\Rightarrow$  current flows from b to a

Define convention first, then solve problem.

- $P > 0$  means power flowing into element (e.g. resistor)
- $P < 0$  means power flowing out of element (e.g. battery)

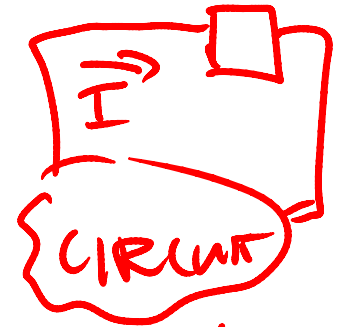

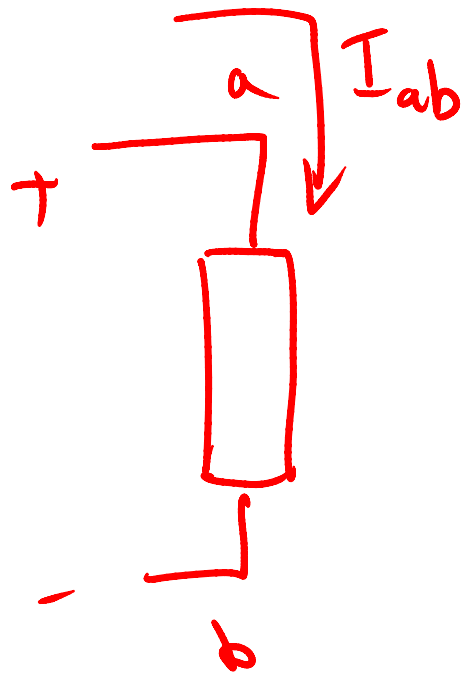

CASE I:

$$P = I_{ab} V_{ab}$$

$$\left. \begin{array}{l} I_{ab} > 0 \\ V_{ab} > 0 \end{array} \right] \Rightarrow P > 0$$


$\Rightarrow$  Energy Flowing into  
"element"

CASE II

$P < 0 \Rightarrow$  Energy flowing  
out of element

Source



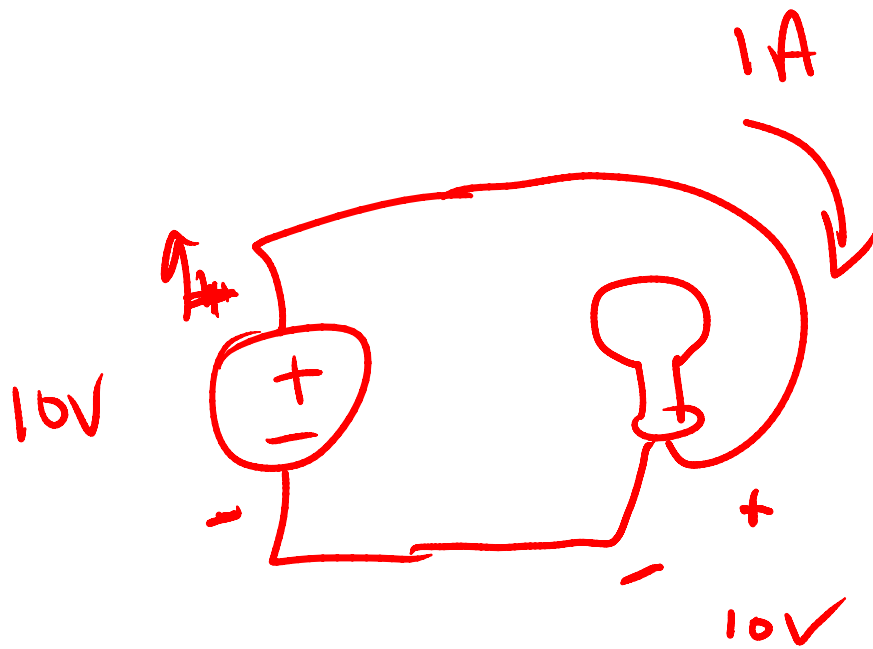


$$P_{\text{bulb}} = 1A \times 10V$$

$$= 10W > 0$$

$$P = 10V (-1A)$$

$$= -10W$$

source

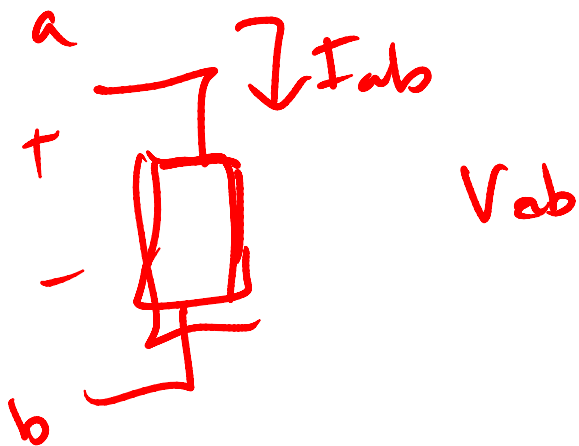

# Example

V = 120 V @ socket (assume DC). ~~→ TRICK~~

Cost of electricity is 10 cents/kW-h

Day nothing, night 10 light bulbs on (100 W bulbs) for 1 hr.


What is monthly electric bill?

(instructor)

$$P_{\text{TOTAL}} = 10 \times 100 \text{ W} = \underline{1 \text{ kW}}$$


$$\text{\$} = \frac{\text{\$ } 0.1}{\text{kW-h}} \quad 1 \text{ kW} \cdot 1 \text{ hour} \cdot 30 = \text{\$ } 3$$

# Topology

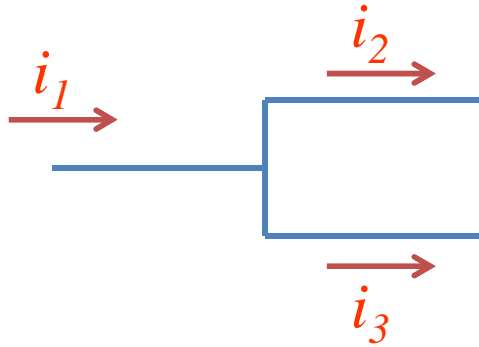


$$i_1 = i_2 + i_3$$

*Like water in a river...*

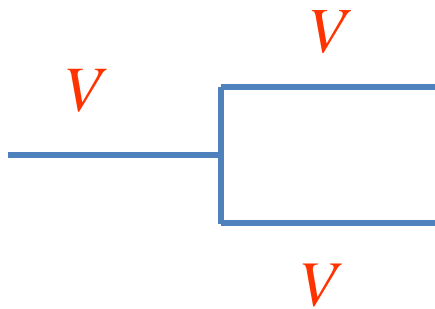

*Voltage same everywhere....  
Concept of a node*

# Example

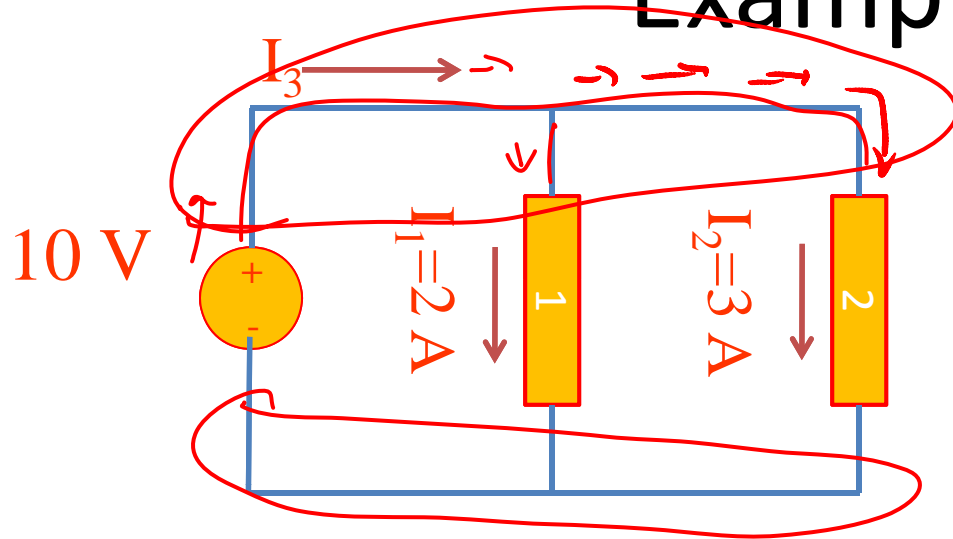

$$I_3 = ?$$

$$V_{\text{element 1}} = ?$$

$$V_{\text{element 2}} = ?$$

$$\text{Power supplied by source} = ?$$

(instructor)


$$I_3 = I_1 + I_2 = 2\text{A} + 3\text{A} = 5\text{A}$$

$$V_{\text{element 1}} = 10\text{V}$$

$$V_{\text{element 2}} = 10\text{V}$$

$$P = 10\text{V} (-5\text{A}) = -50\text{W}$$

# Example

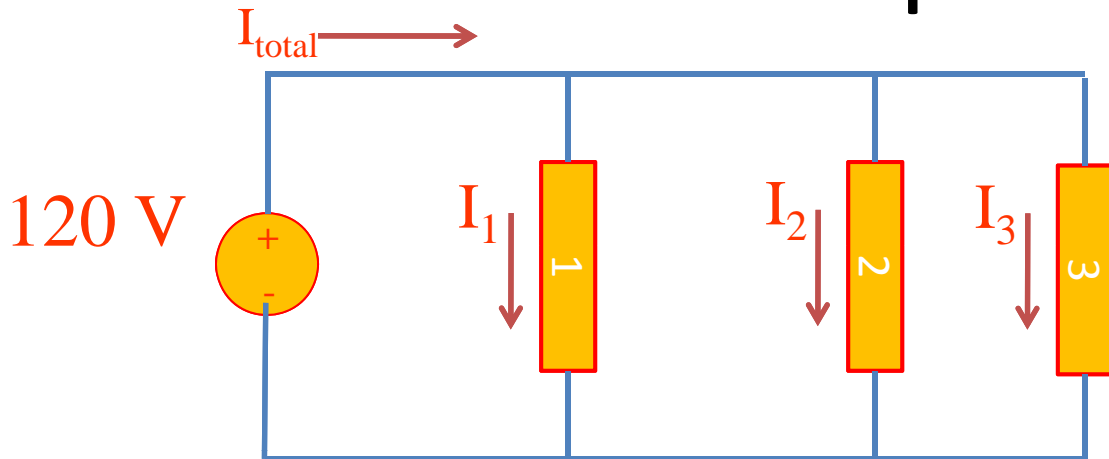

(student)

Three light bulbs (100 W each) on 1 hour/night. 120 V @ socket.

- A What is I per bulb?
- B What is  $I_{total}$  from supply?
- C ~~What is bill?~~


what is power sourced?

~~300W~~

$$120V \times \frac{15}{6}A = \underline{\underline{300W}}$$

$$\begin{aligned}
 \text{Hint } P_{bulb} &= 100W = V_{bulb} I_{bulb} = \frac{5}{6}A \\
 \underbrace{120V}_{120V} \quad I_{TOT} &= \sum = \frac{5}{6}A \\
 &+ \frac{5}{6}A + \frac{5}{6}A \\
 &= \frac{15}{6}A
 \end{aligned}$$

# Power failure example

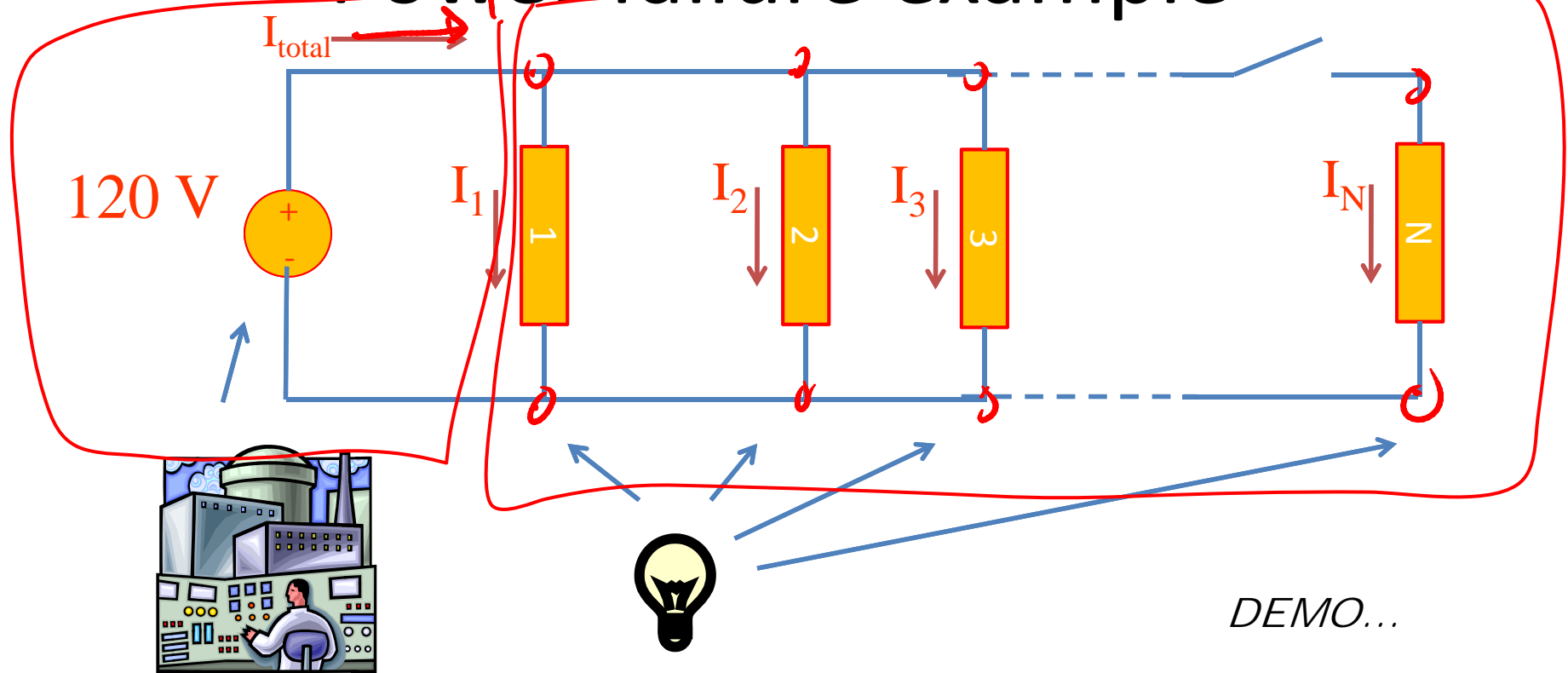

Generator will fail of power required  $> 1$  MW

How many light bulbs need to be turned on to damage the generator?