

EECS 70A: Network Analysis

Lecture 2

Announcements

- HW to be posted online- due Wed week 2 in disc.
- Quiz to be online eee- due Mon midnt. week 2
- Office hours posted online
- Lecture notes will be posted online
 - Skeleton before lecture
 - With annotation after lecture
- Please ask questions in lecture!
- Things will speed up...

Review & agenda


Last lecture:

- Current
- Voltage
- Power

Today:

- Examples
 - Power (sink/source)
 - Current (positive/negative)
 - Dependent sources
- Resistors
 - Series
 - Parallel

Power: Source vs. sink

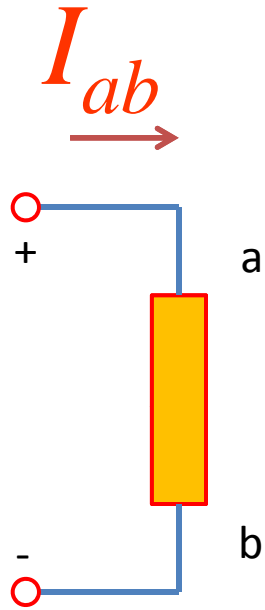

$$P = I_{ab} \times V_{ab}$$


$$P > 0$$

\Rightarrow "sink": power delivered to element


$$P < 0$$

\Rightarrow "source": power supplied by element


“source”

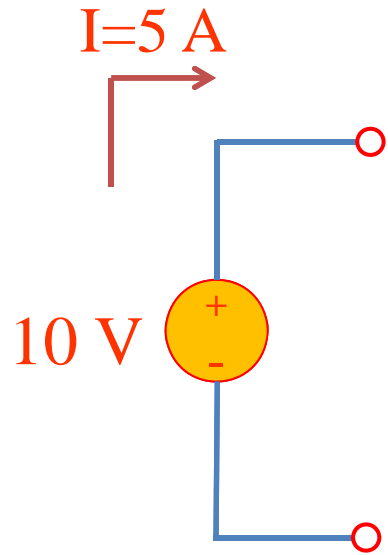

“source”

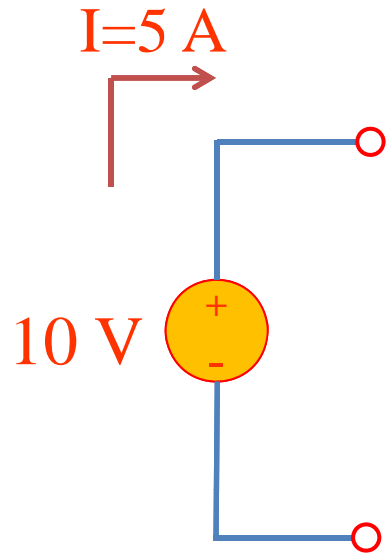


Draw or think of as:

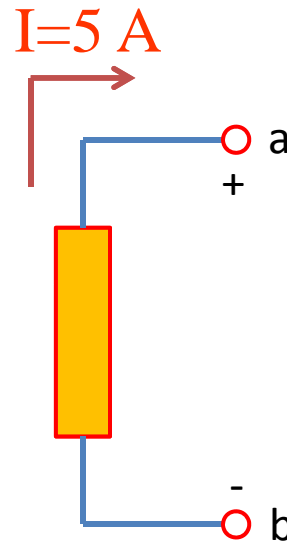

$$V_{ab} = 10\text{ V}$$

$$I_{ab} = -5\text{ A}$$

Same as:

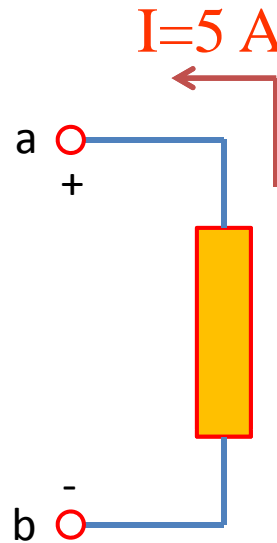


$$V_{ab} = 10\text{ V}$$

$$I_{ab} = -5\text{ A}$$


$$\begin{aligned} P &= I_{ab} \times V_{ab} \\ &= (-5\text{ A}) \times (10\text{ V}) \\ &= -50\text{ W} \end{aligned}$$

Practice problems

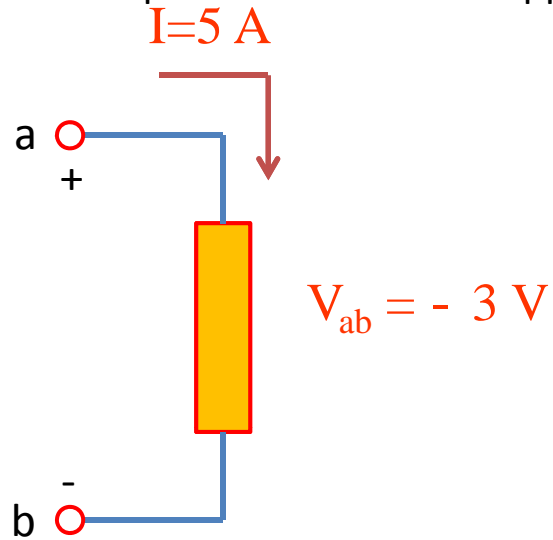Find the power absorbed or supplied by the element (instructor).




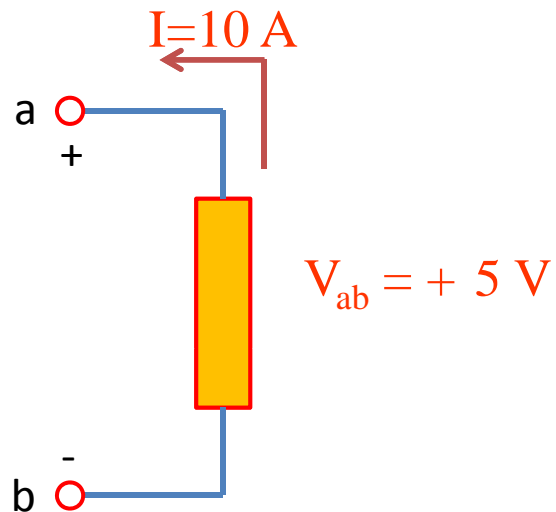Find the power absorbed or supplied by the element (instructor).




Practice problems

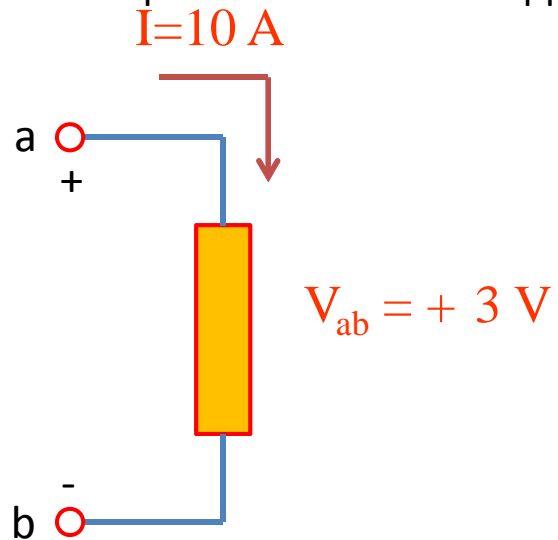Find the power absorbed or supplied by the element (student).




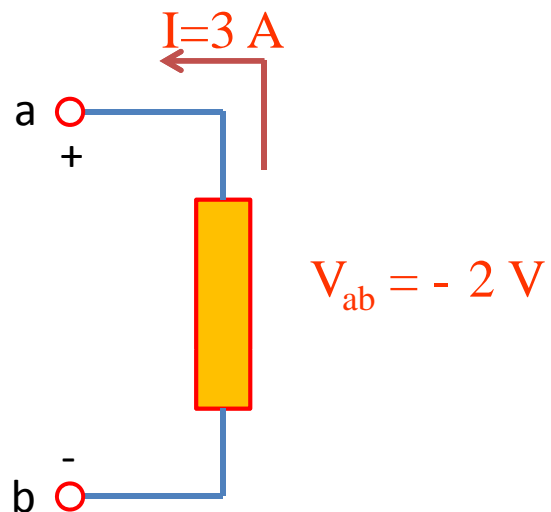Find the power absorbed or supplied by the element (student).




Example problem: Current (positive/negative)

Find the i_2 , i_3 (instructor).

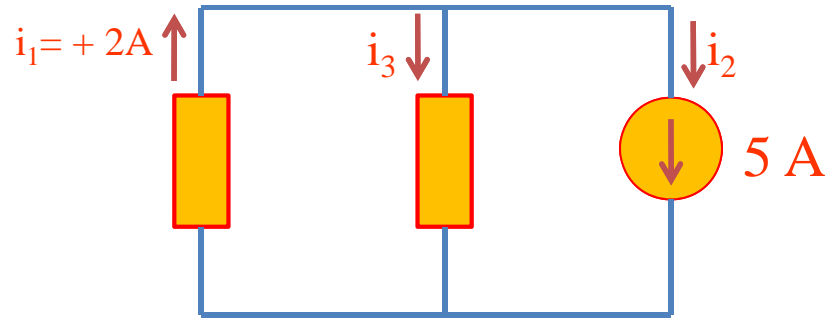


Recall:

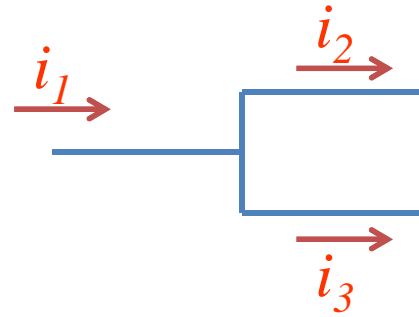


$$i_1 = i_2 + i_3$$

Like water in a river...

Dependent sources

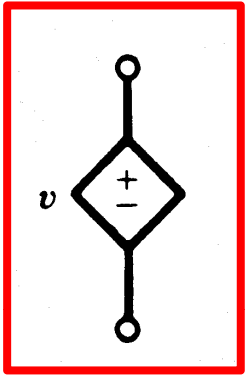

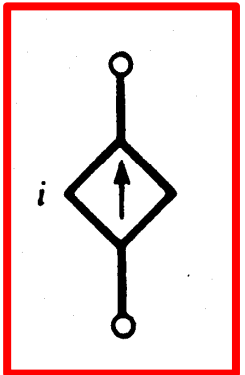
VCVS: Voltage controlled voltage source
CCVS: Current controlled voltage source



VCCS: Voltage controlled current source
CCCS: Current controlled current source


Voltage controlled voltage source (VCVS)

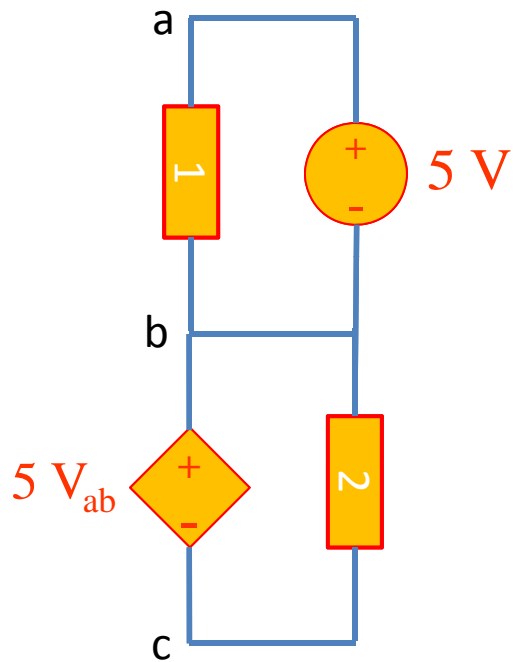Find the voltage drop across element 2 (instructor).




Voltage controlled current source (VCCS)

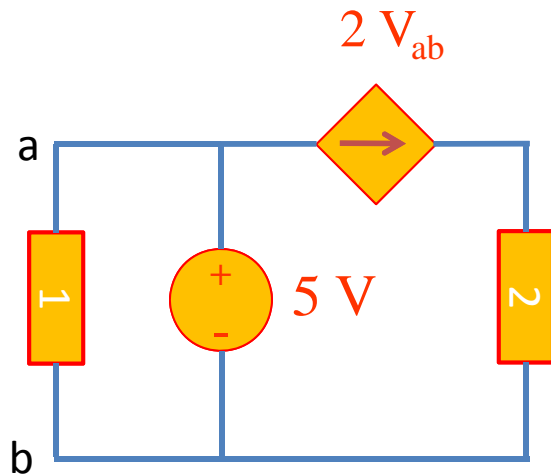Find the current through element 2 (student).





Example problem.

Find the V_{bc} (instructor).

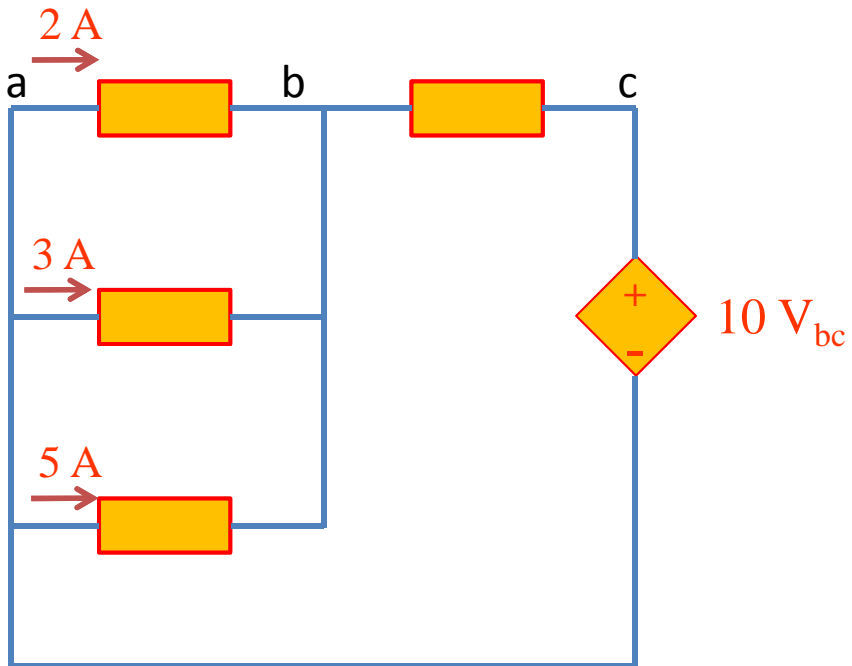

Practical example (demo).

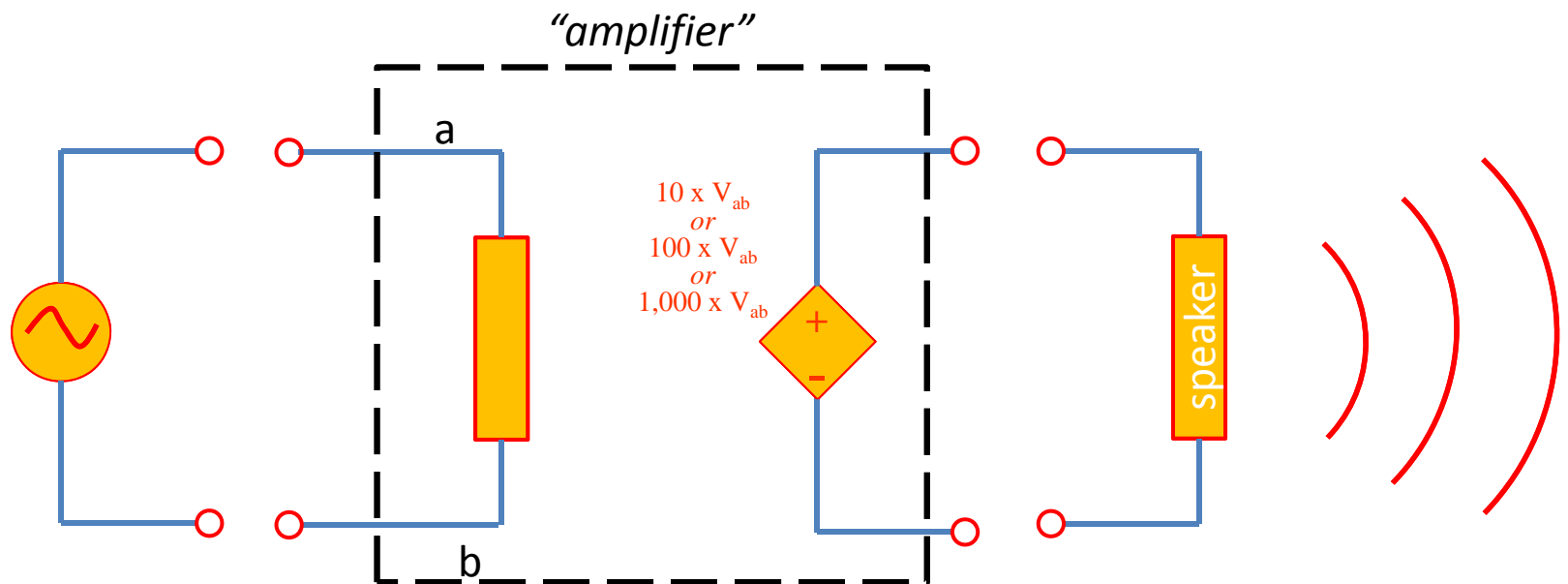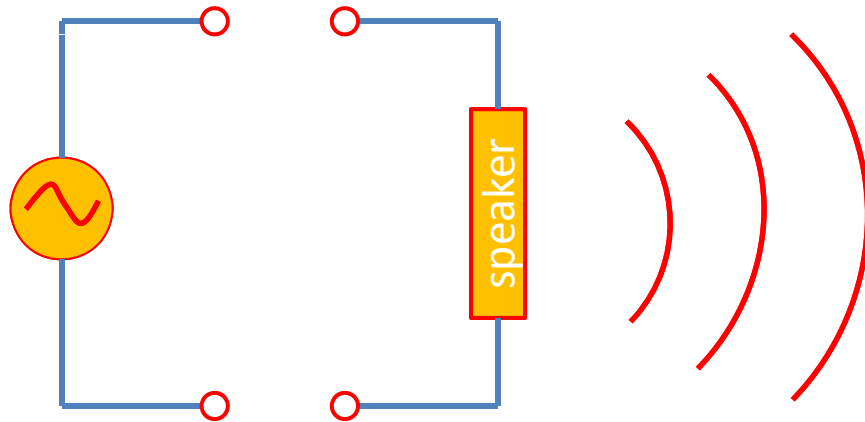


MKSA units-cheat sheet

Quantity	Name	Symbol	Expression in terms of other units	Expression in terms of MKSA base units
Frequency	Hertz	Hz		s^{-1}
Force	Newton	N		$m\text{-kg}/s^2$
Pressure	Pascal	Pa	N/m^2	$kg/m\text{-}s^2$
Energy	Joule	J	$N\text{-}m$	$kg\text{-}m^2/s^2$
Power	Watt	W	J/s	$kg\text{-}m^2/s^3$
Charge	Coulomb	C		$A\text{-}s$
Voltage	Volt	V	W/A	$kg\text{-}m^2/A\text{-}s^3$
Capacitance	Farad	F	C/V	$A^2\text{-}s^4/kg\text{-}m^2$
Resistance	Ohm	Ω	V/A	$kg\text{-}m^2/A^2\text{-}s^3$
Conductance	Siemens	S	A/V	$A^2\text{-}s^3/kg\text{-}m^2$
Inductance	Henry	H		$kg\text{-}m^2/A^2\text{-}s^2$

Questions?

Resistors

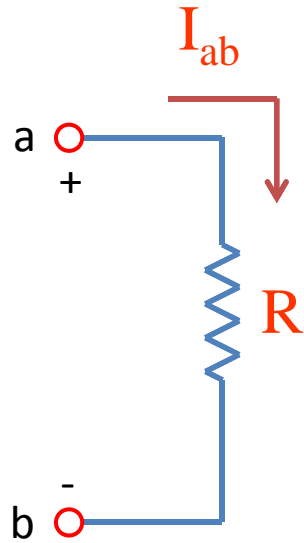


$$V_{ab} = I_{ab} \times R$$

Resistance units: Ohms [Ω]

Example circuit:
(Voltage source in series with resistor.)

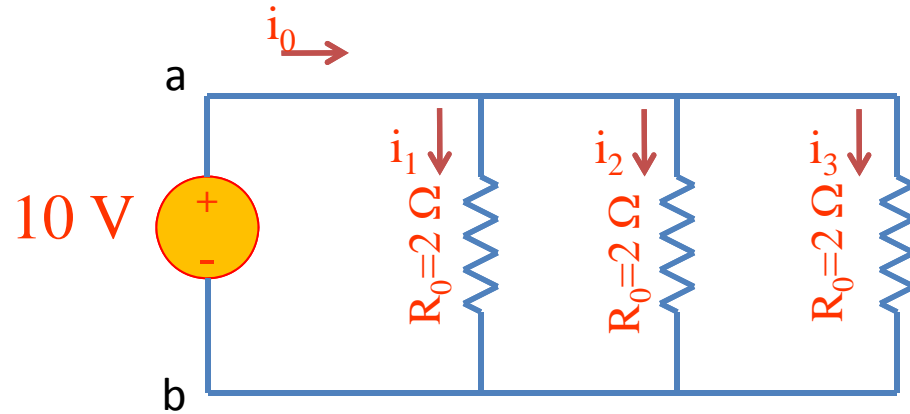
Example problem: Resistors in parallel.

Solve for all the currents and voltages in this circuit. (instructor).



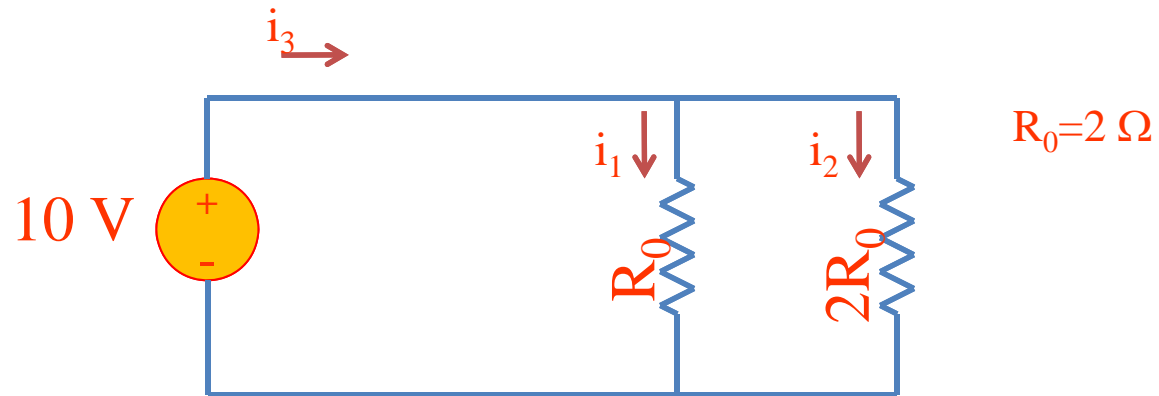Example problem: Resistors in parallel.

Solve for all the currents and voltages in this circuit. (students).



a) Find i_1


b) Find i_2

c) Find i_3

d) Find R_{eq}


Generalize: N resistors in parallel.

Solve for R_{eq} . (instructor).

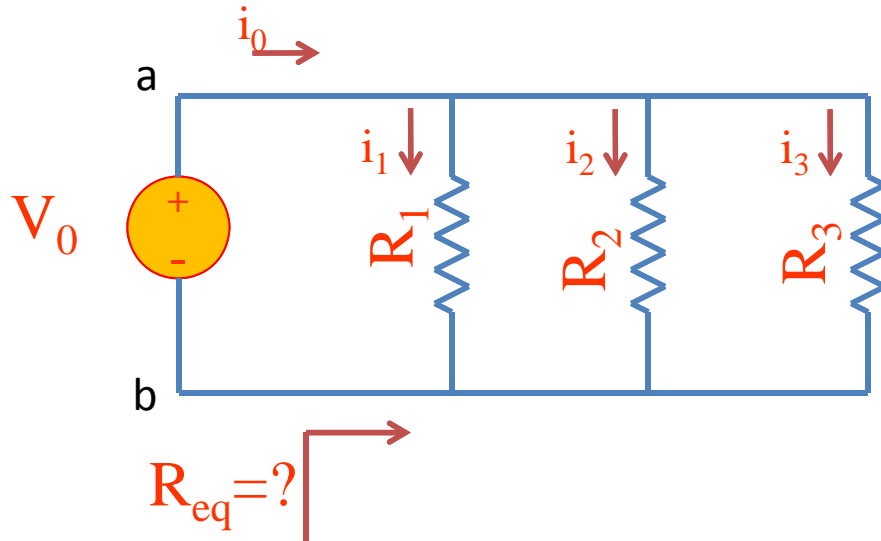


Example problem:

Solve for R_{eq} . (students).

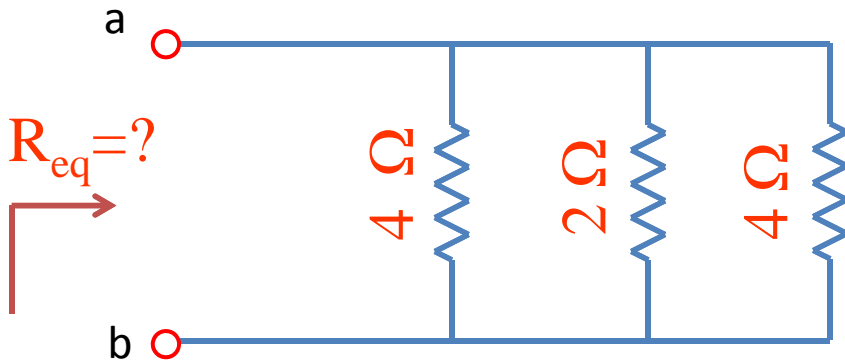


Important practical example:

Solve for R_{eq} . (instructor).

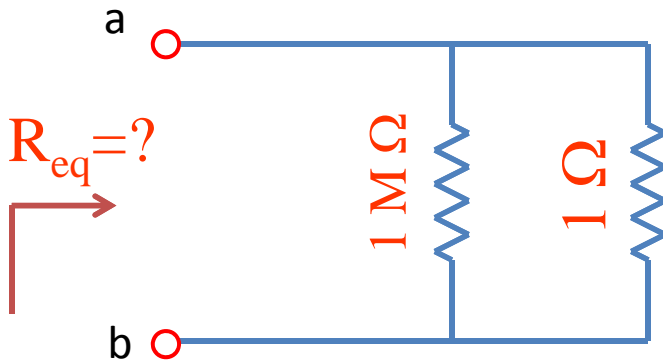

Questions?

Voltage addition in circuits

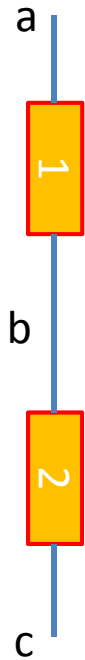


$$V_{ab} \equiv \int_a^b E dx$$

$$\Rightarrow V_{ac} \equiv \int_a^c E dx = \int_a^b E dx + \int_b^c E dx = V_{ab} + V_{bc}$$


$$V_{bc} \equiv \int_b^c E dx$$

$$V_{ac} = V_{ab} + V_{bc}$$

2 resistors in series

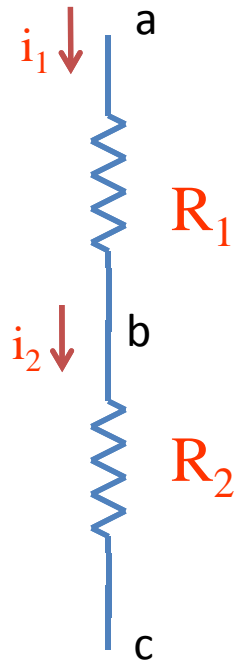


Generalize: N resistors in series

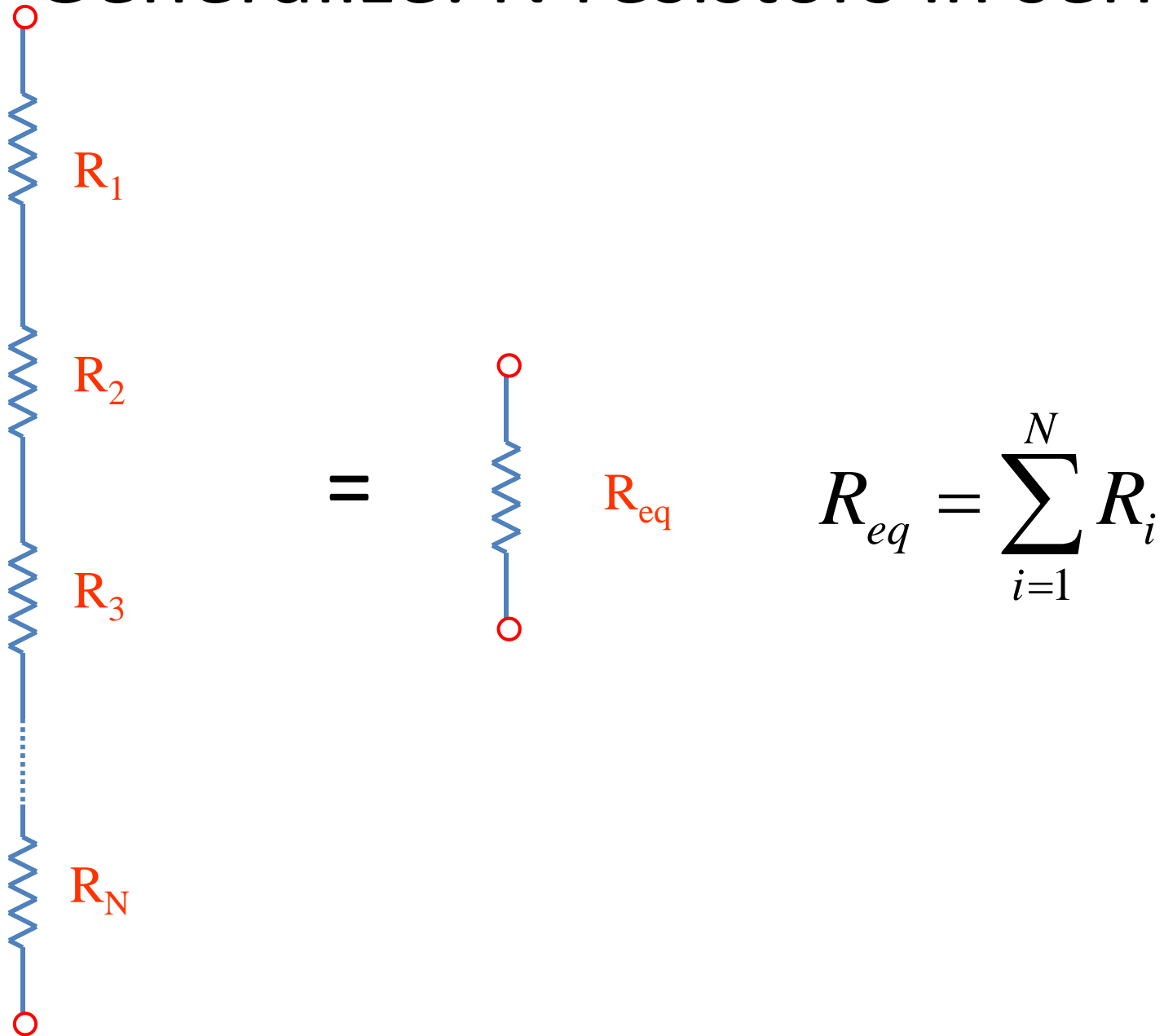


Example problems

Solve for R_{eq} . (instructor).

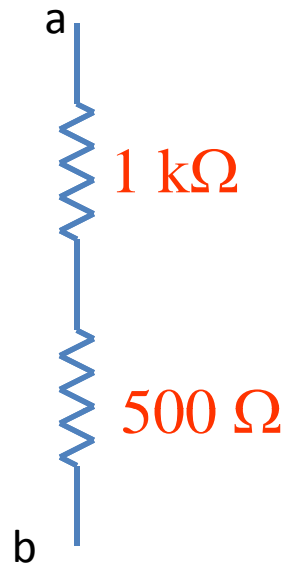


Solve for R_{eq} . (students).

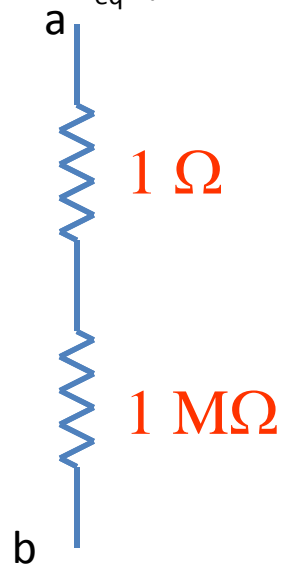

Questions?


Example problems

Solve for R_{eq} (instructor).

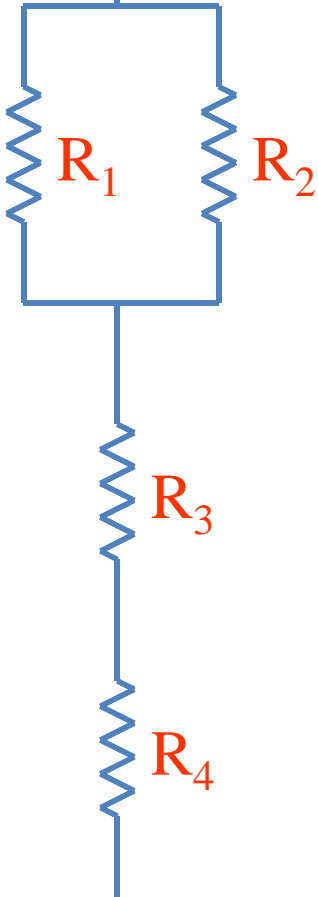


Example problems

Solve for R_{eq} . (students).

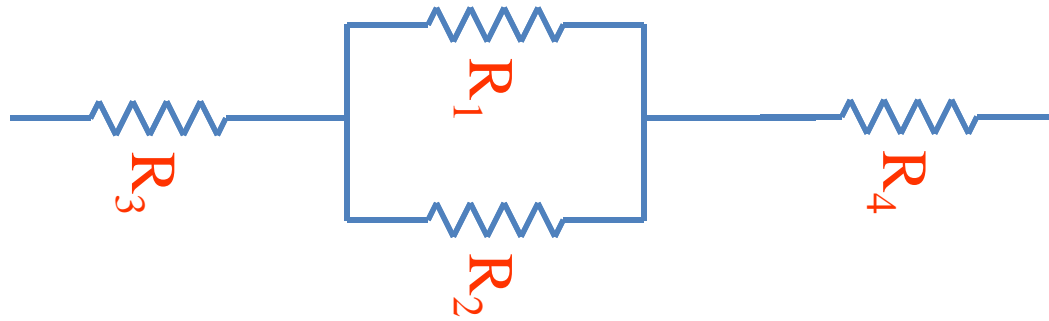


Example problems

Solve for R_{eq} . (instructor).

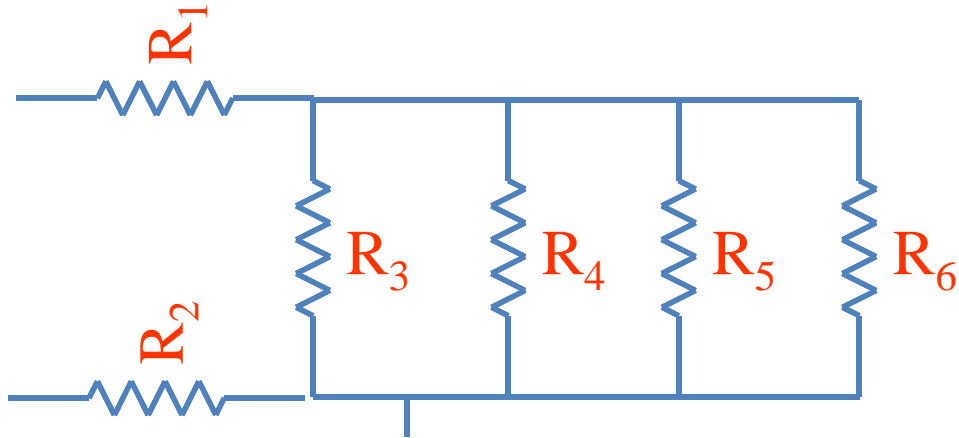

Example problems

Voltage divider



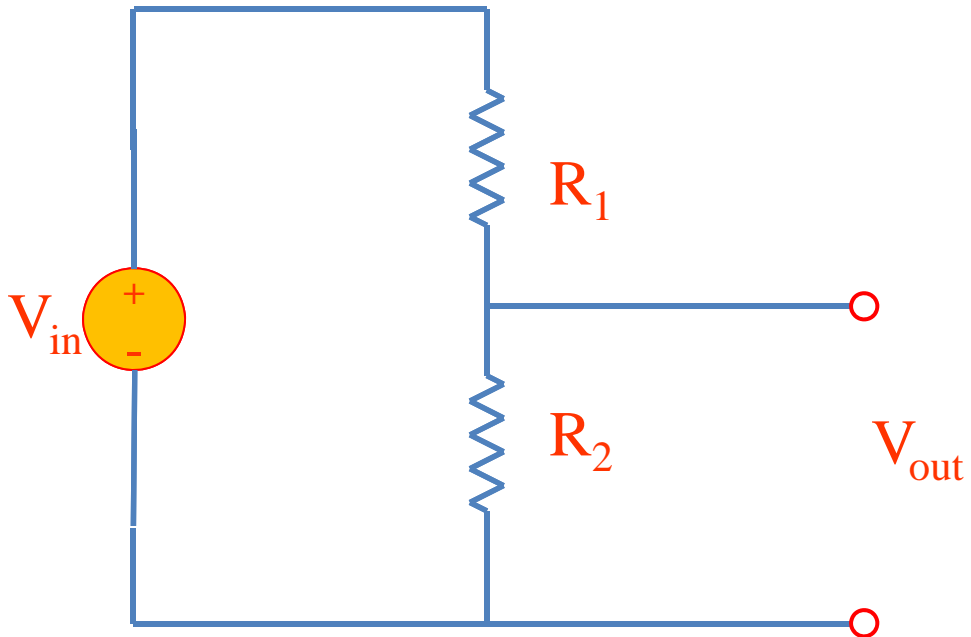


$$V_{out} = \frac{R_2}{R_1 + R_2} V_{in}$$

Why important?
Concept of source/load. (Thevenin...)

Source/load concept

Symbol library

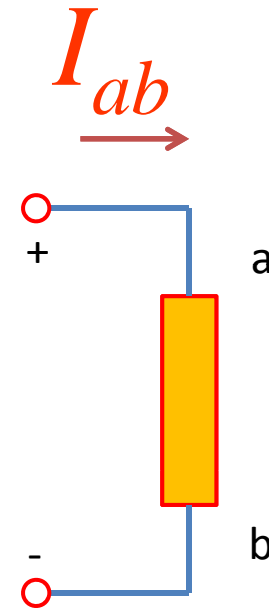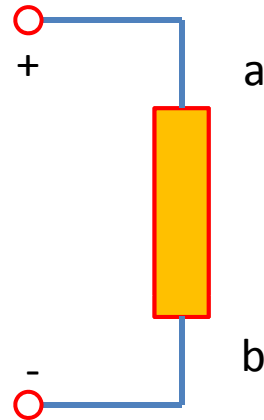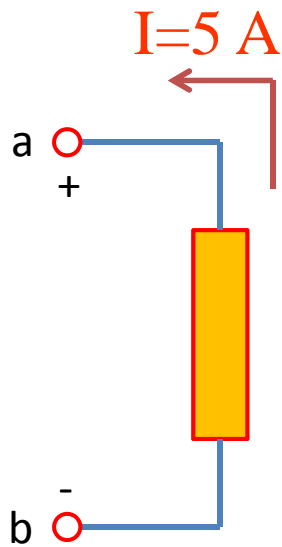

Symbol library

