

# EECS 70A: Network Analysis

## Lecture 2

# Announcements

- HW to be posted online- due Wed week 2 in disc.
- Quiz to be online eee- due Mon midnt. week 2
- Office hours posted online
- Lecture notes will be posted online
  - Skeleton before lecture
  - With annotation after lecture
- Please ask questions in lecture!
- Things will speed up...

# Review & agenda


Last lecture:

- Current
- Voltage
- Power

Today:

- Examples
  - Power (sink/source)
  - Current (positive/negative)
  - Dependent sources
- Resistors
  - Series
  - Parallel

# Power: Source vs. sink

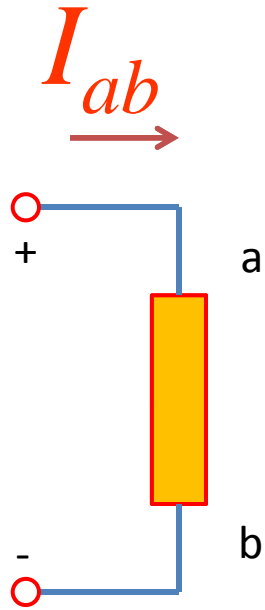

$$P = I_{ab} \times V_{ab}$$


$$P > 0$$

$\Rightarrow$  "sink": power delivered to element


$$P < 0$$

$\Rightarrow$  "source": power supplied by element


*“source”*

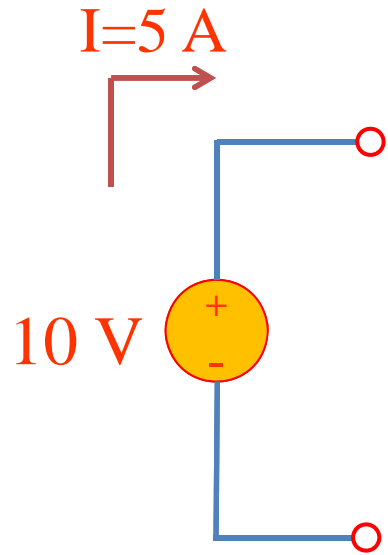

# “source”

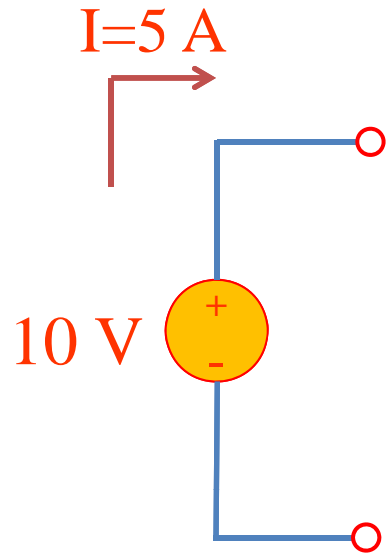


Draw or think of as:

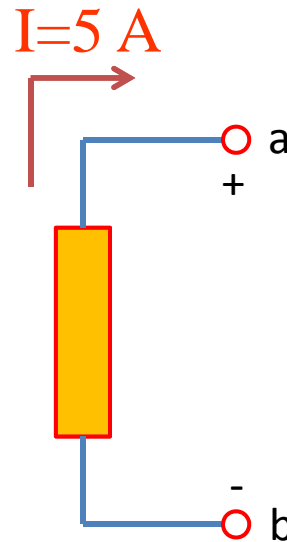

$$V_{ab} = 10\text{ V}$$

$$I_{ab} = -5\text{ A}$$

Same as:

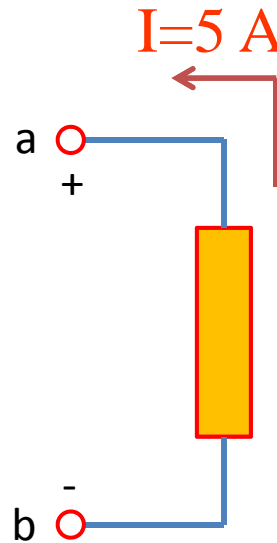


$$V_{ab} = 10\text{ V}$$

$$I_{ab} = -5\text{ A}$$

$$\begin{aligned} P &= I_{ab} \times V_{ab} \\ &= (-5\text{ A}) \times (10\text{ V}) \\ &= -50\text{ W} \end{aligned}$$
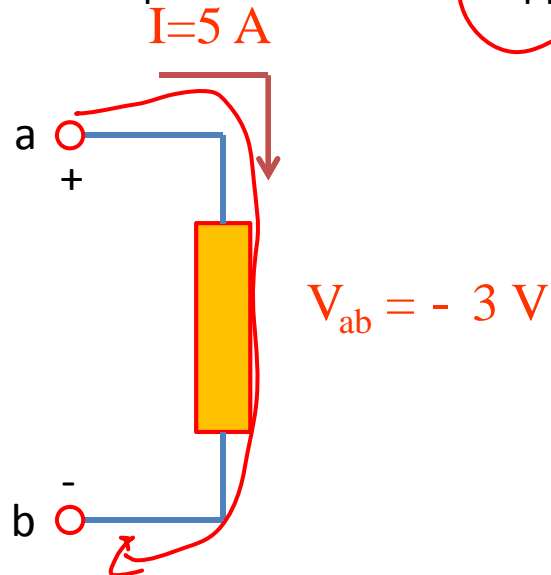
# Practice problems

Find the power absorbed or supplied by the element (instructor).




~~$V_{ab}$~~   $P = I_{ab} \times V_{ab}$

$$V_{ab} = -3V$$
$$I_{ab} = +5A$$
$$P = (-3V)(+5A) = -15W$$

Source

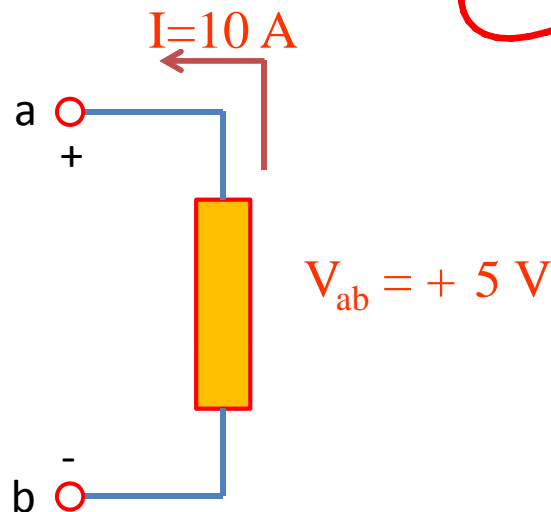Find the power absorbed or supplied by the element (instructor).




$$P = I_{ab} \times V_{ab}$$
$$I_{ab} = -10A$$
$$V_{ab} = +5V$$
$$P = (-10A) \times (+5V) = -50W$$

Source
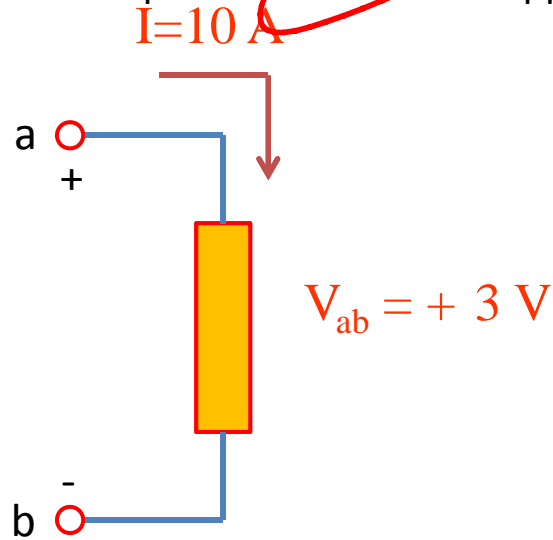
# Practice problems

Find the power absorbed or supplied by the element (student).




$$V_{ab} = + 3 \text{ V}$$

$$I_{ab} = + 10 \text{ A}$$

$$P = + 30 \text{ W}$$

sink

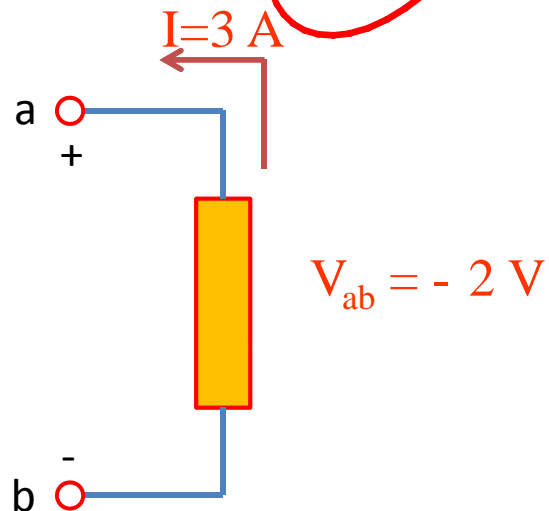Find the power absorbed or supplied by the element (student).



$$V_{ab} = - 2 \text{ V}$$



$$I_{ab} = - 3 \text{ A}$$

Sink

$$P = (- 3 \text{ A}) (- 2 \text{ V}) = 6 \text{ W}$$


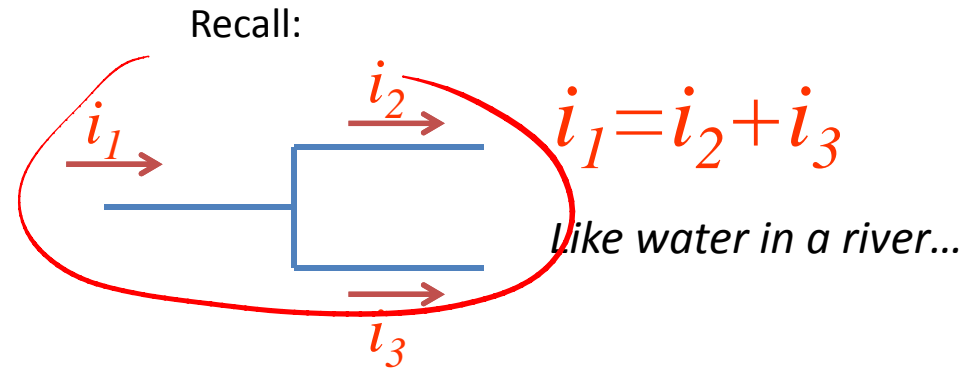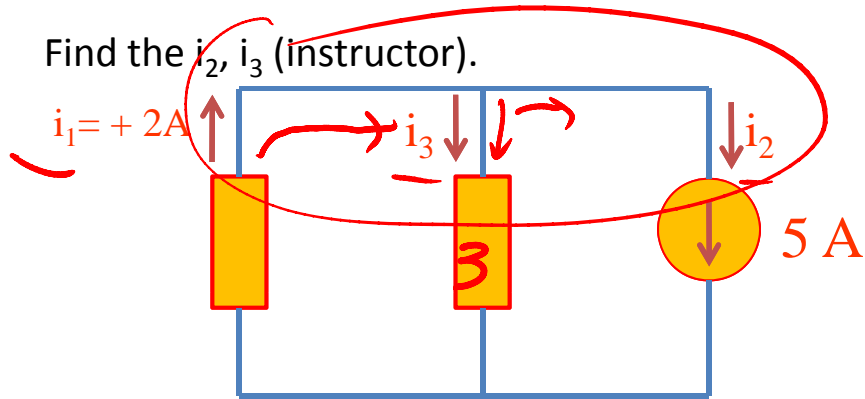
## Example problem: Current (positive/negative)




$$i_2 = +5A$$

$$i_1 = i_2 + i_3$$

$$i_3 = i_1 - i_2 = 2A - 5A = -3A$$

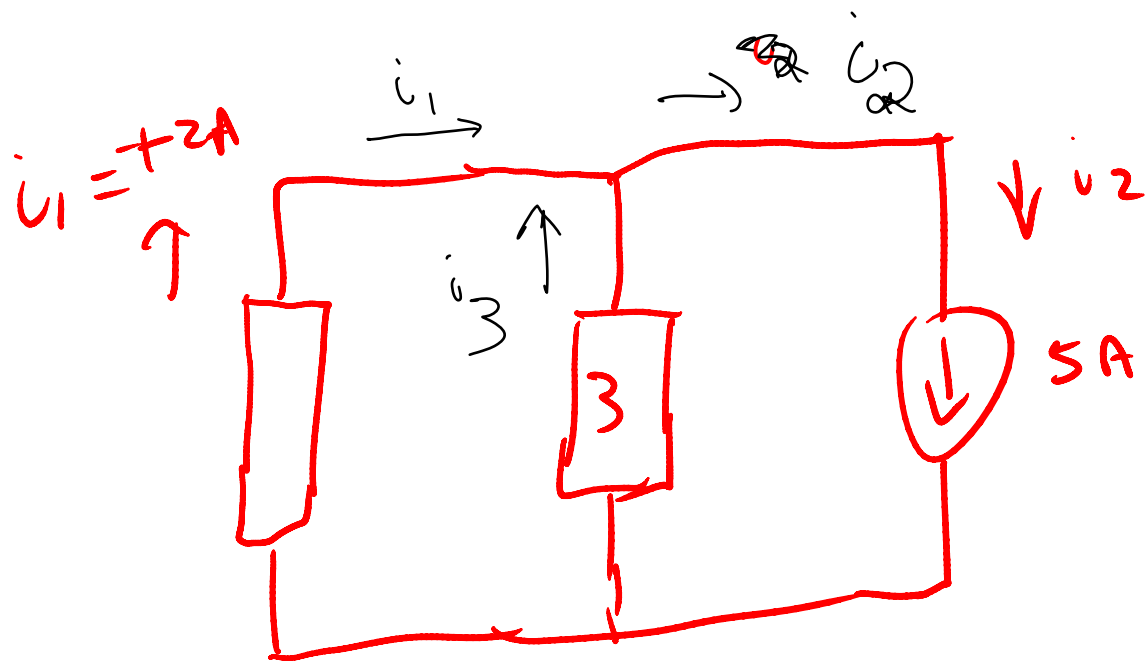$\Rightarrow$  Current thru element #3 is flowing opposite the direction of arrow.





P: Find current thru el. #3

$$i_1 + i_3 = i_2 \Rightarrow i_3 = i_2 - i_1 = 5A - 2A = 3A$$

# Example problem: Current

Find the  $i_2, i_3$  (instructor).

Recall:

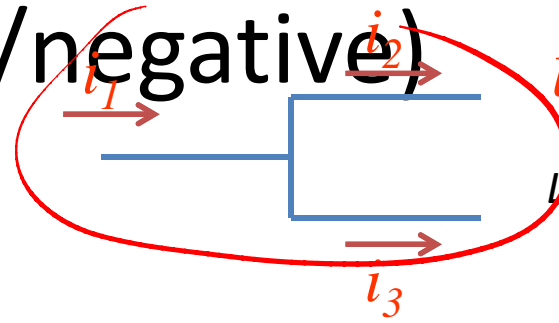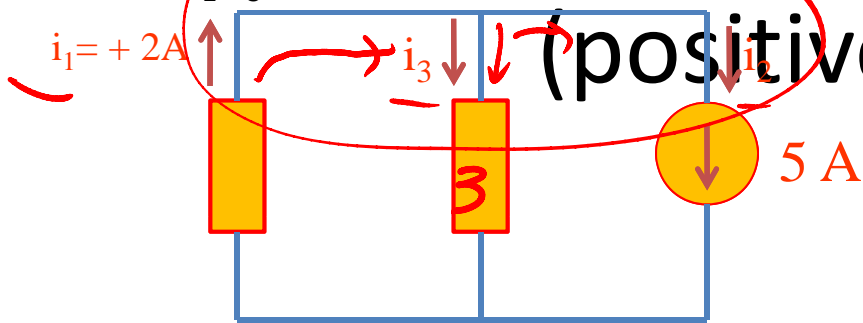

$$i_1 = i_2 + i_3$$

*like water in a river...*


$$i_2 = +5A$$

$$i_1 = i_2 + i_3$$


$$i_3 = i_1 - i_2 = 2A - 5A = -3A$$

$\Rightarrow$  current thru element #3 is flowing opposite the direction of arrow.

# Dependent sources

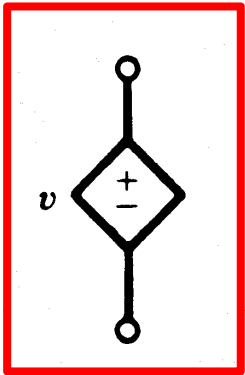

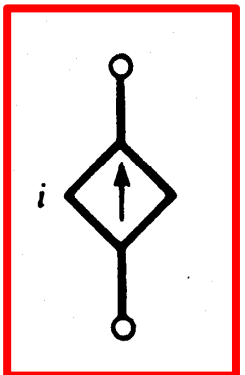
**VCVS: Voltage controlled voltage source**  
**CCVS: Current controlled voltage source**



**VCCS: Voltage controlled current source**  
**CCCS: Current controlled current source**
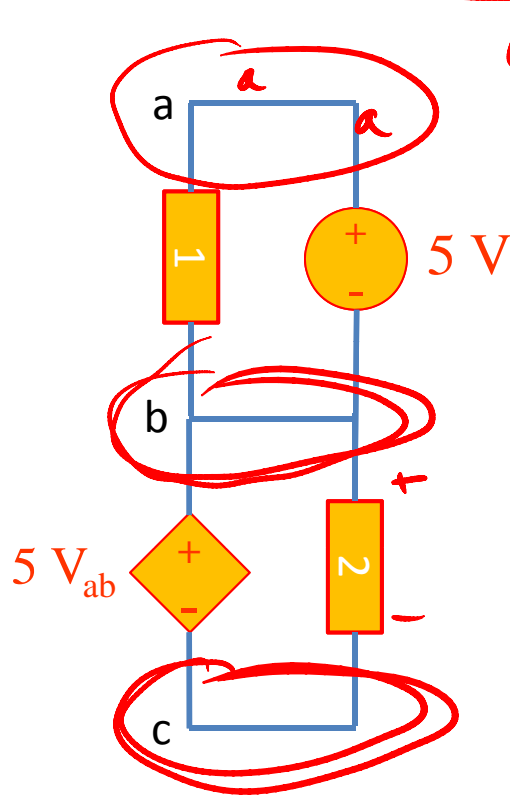
# Voltage controlled voltage source (VCVS)

Find the voltage drop across element 2 (instructor).



$$\hookrightarrow = V_{bc}$$

= voltage drop across  
dependent source


$$= 5 \times V_{ab}$$

$$= 5 \times (5V)$$

$$= 25V$$
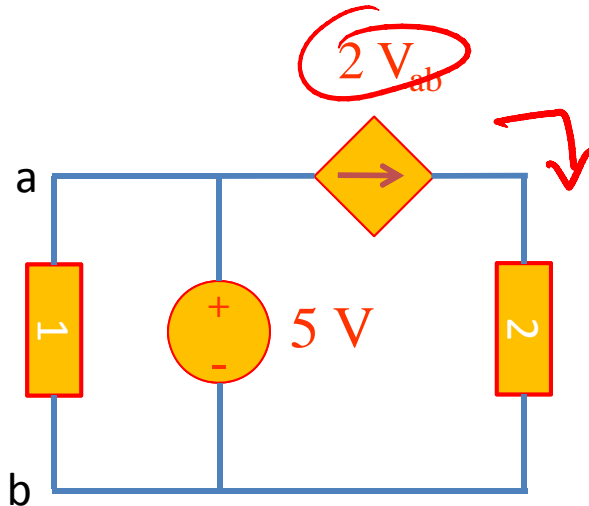
# Voltage controlled current source (VCCS)

Find the current through element 2 (student).



$$+10A$$


$$V_{ab} = +5V$$

$$\Rightarrow 2 \times V_{ab} = 10A$$

~~2~~


$$2 \left[ \frac{A}{V} \right] \times 5 [V] = 10A$$

$$2 \left[ \frac{A}{V} \right] V_{ab}$$

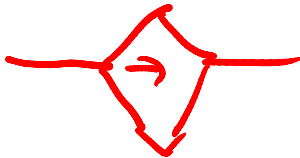

# Example problem.

Find the  $V_{bc}$  (instructor).

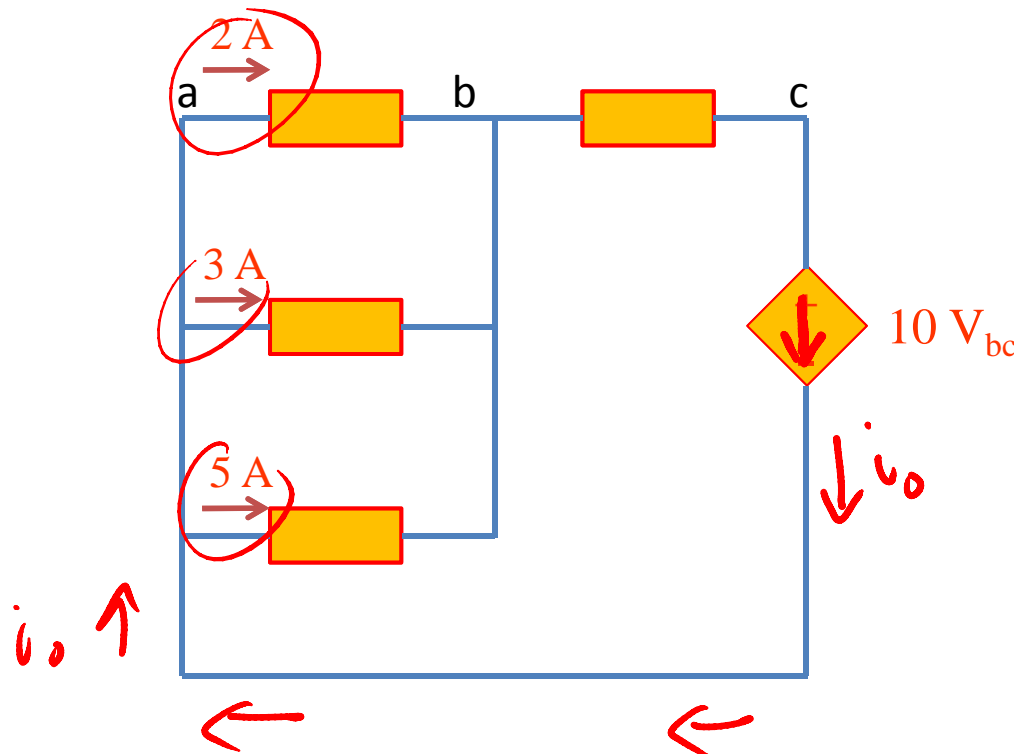


VCCS



$$i_0 = 10A$$

$$V_{bc} = 1V$$



$$10 \left[ \frac{A}{V} \right] V_{bc}$$

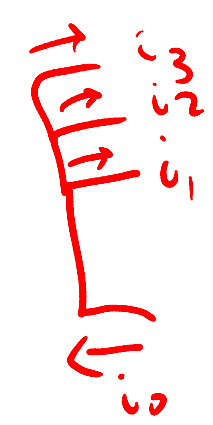

$$i_0 = i_1 + i_2 + i_3$$

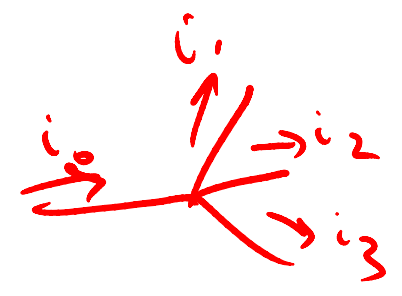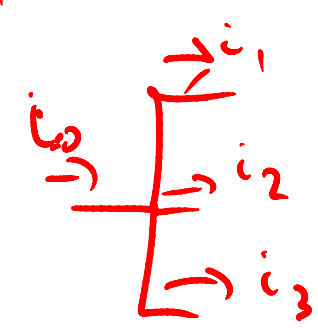

# Practical example (demo).

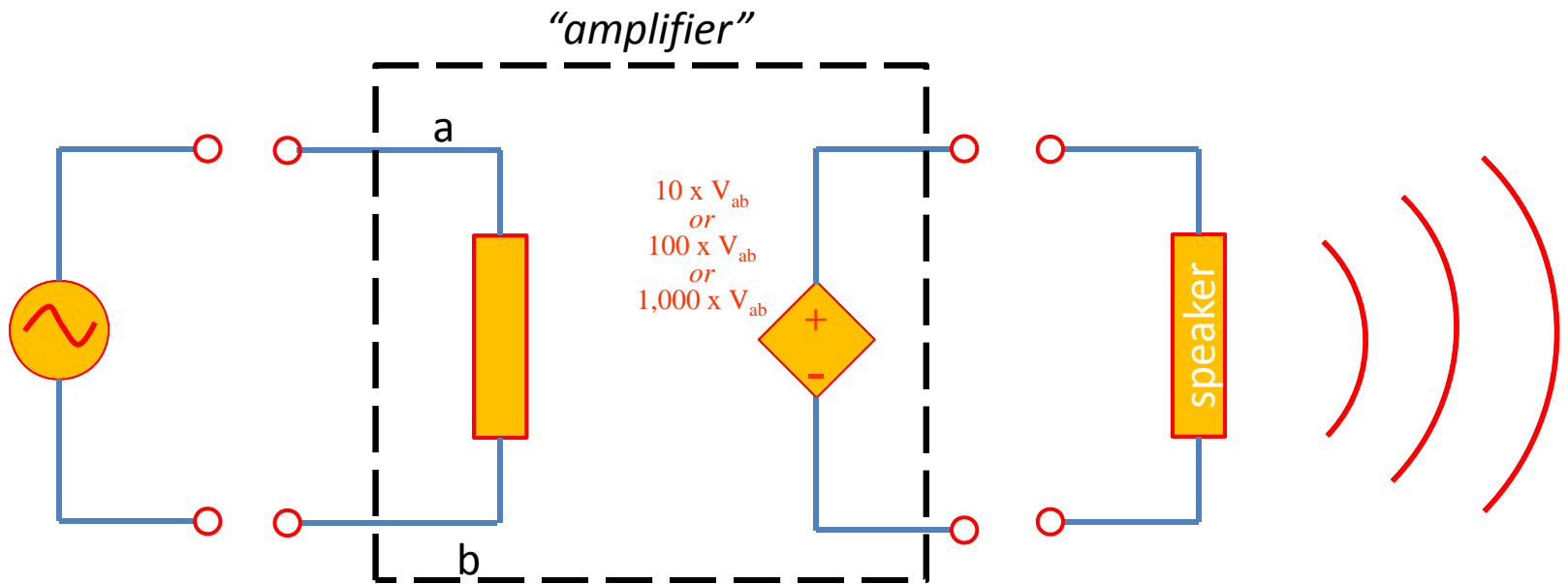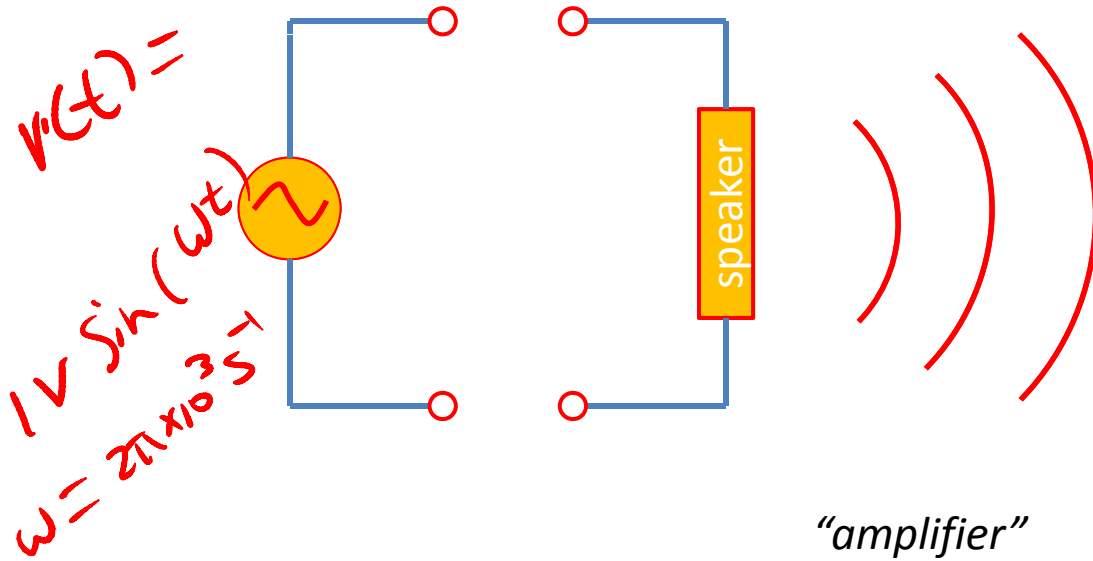




# MKSA units-cheat sheet

Quantity	Name	Symbol	Expression in terms of other units	Expression in terms of MKSA base units
Frequency	Hertz	Hz		$s^{-1}$
Force	Newton	N		$m\text{-kg}/s^2$
Pressure	Pascal	Pa	$N/m^2$	$kg/m\text{-}s^2$
Energy	Joule	J	$N\text{-}m$	$kg\text{-}m^2/s^2$
Power	Watt	W	$J/s$	$kg\text{-}m^2/s^3$
Charge	Coulomb	C		$A\text{-}s$
Voltage	Volt	V	$W/A$	$kg\text{-}m^2/A\text{-}s^3$
Capacitance	Farad	F	$C/V$	$A^2\text{-}s^4/kg\text{-}m^2$
Resistance	Ohm	$\Omega$	$V/A$	$kg\text{-}m^2/A^2\text{-}s^3$
Conductance	Siemens	S	$A/V$	$A^2\text{-}s^3/kg\text{-}m^2$
Inductance	Henry	H		$kg\text{-}m^2/A^2\text{-}s^2$

# Questions?


# Resistors

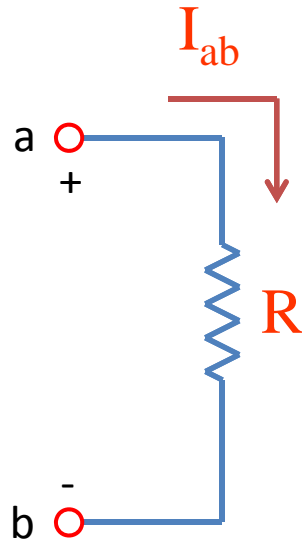

$$V_{ab} = I_{ab} \times R$$

Resistance units: Ohms [ $\Omega$ ]

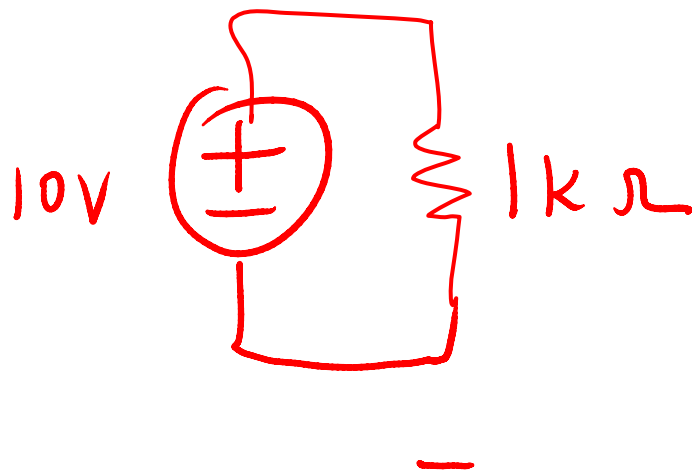
Example circuit:  
(Voltage source in series with resistor.)



$$\begin{aligned} V_{ab} &= 10V \\ R &= 1k\Omega \\ \Rightarrow I_{ab} &= \frac{10V}{1k\Omega} = 0.01 \frac{V}{\Omega} = 0.01A \end{aligned}$$
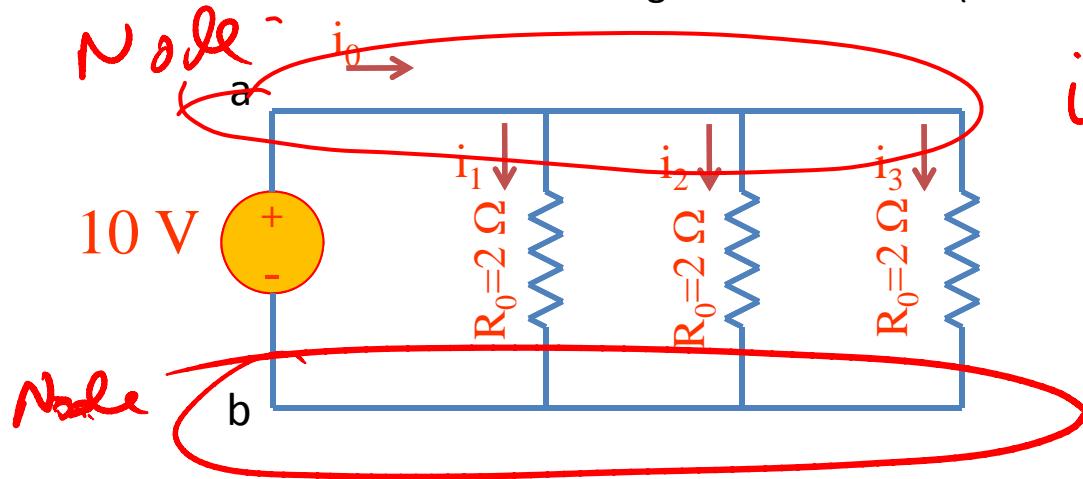
## Example problem: Resistors in parallel.

Solve for all the currents and voltages in this circuit. (instructor).



$$i_0 = i_1 + i_2 + i_3$$

$$i_1 = \frac{10V}{2\Omega} = 5A$$


$$i_2 = \frac{10V}{2\Omega} = 5A$$

$$i_3 = \frac{10V}{2\Omega} = 5A$$

$$i_0 = 15A$$


R:  $i_1 = i_2 = i_3$  "by symmetry"
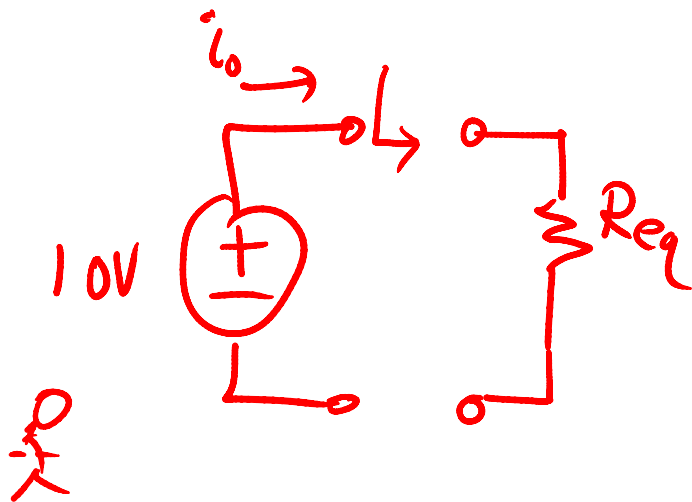
$$R_{eq} = \frac{10V}{i_0} = \frac{10V}{15A} = \frac{2}{3}\Omega$$


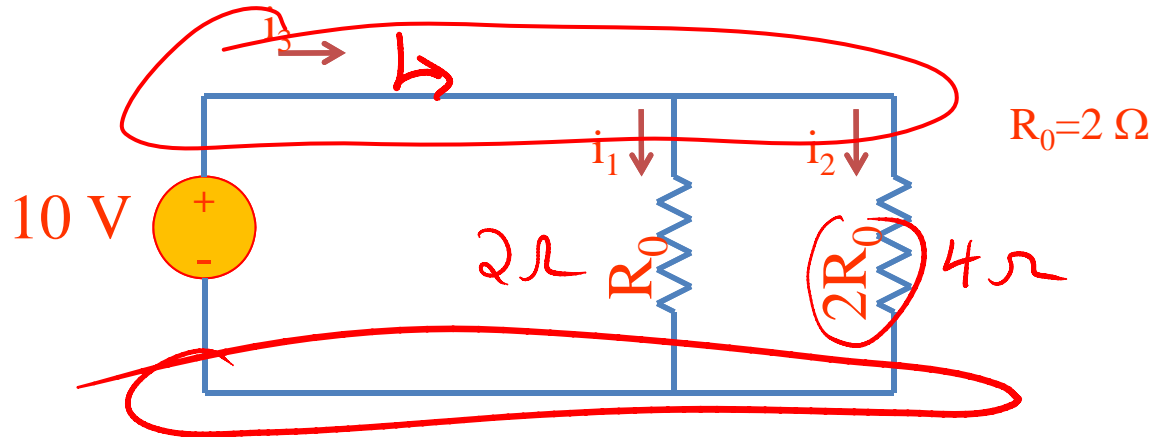
## Example problem: Resistors in parallel.

Solve for all the currents and voltages in this circuit. (students).



a) Find  $i_1 = \frac{10V}{2\Omega} = \dots 5A$


b) Find  $i_2 = \frac{10V}{4\Omega} = \frac{5}{2}A$

c) Find  $i_3 = \left(5 + \frac{5}{2}\right)A = 7.5A$

d) Find  $R_{eq} = \frac{10V}{7.5A} = \frac{10}{7.5}\Omega$

Generalize: N resistors in parallel.

Solve for  $R_{eq}$ . (instructor).

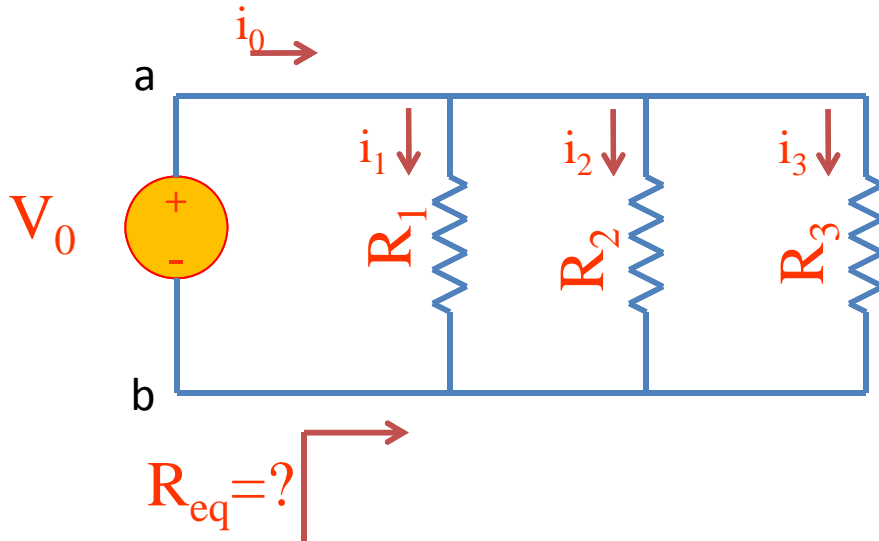

a)  $i_1 = v_0/R_1$

b)  $i_2 = v_0/R_2$

c)  $i_3 = v_0/R_3$

d)  $i_0 = \underline{i_1 + i_2 + i_3}$

e)  $\frac{v_0}{i_0} \equiv R_{eq}$



$$R_{eq} = \frac{V_0}{\frac{V_0}{R_1} + \frac{V_0}{R_2} + \frac{V_0}{R_3}} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots}$$

$R_1 \parallel R_2 \parallel R_3$   
Notation

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \rightarrow \sum_{i=1}^N \frac{1}{R_i}$$


Example problem:

Solve for  $R_{eq}$ . (students).

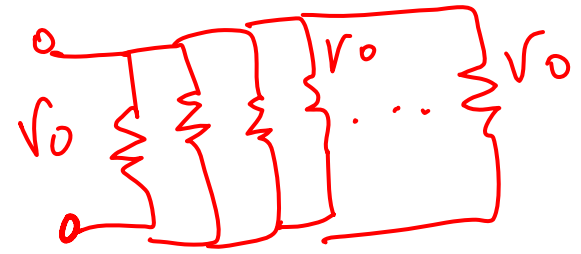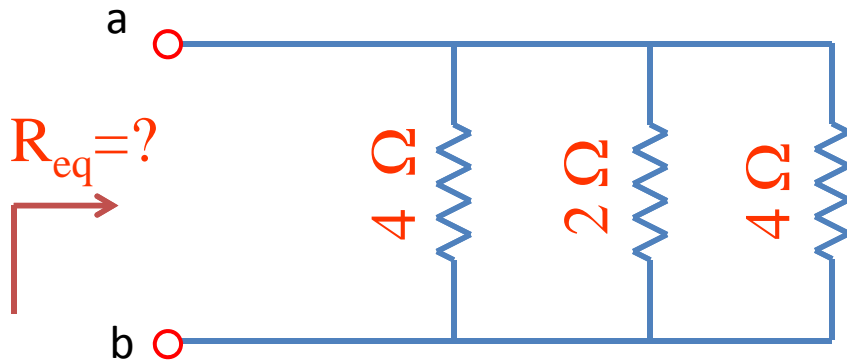


$1 \Omega$        $R_{eq} = \frac{v_0}{N}$
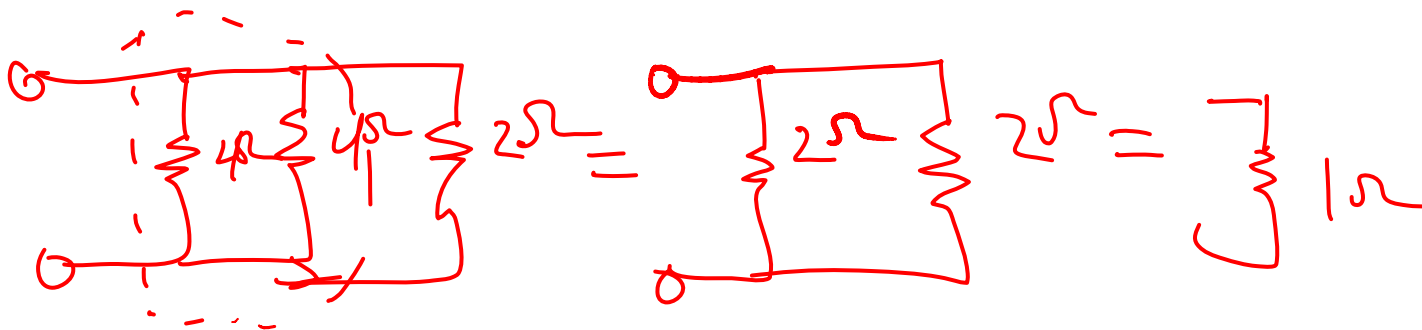
$$\frac{1}{R_{eq}} = \frac{1}{4} + \frac{1}{2} + \frac{1}{4} = 1 \Omega$$



## Important practical example:

Solve for  $R_{eq}$ . (instructor).

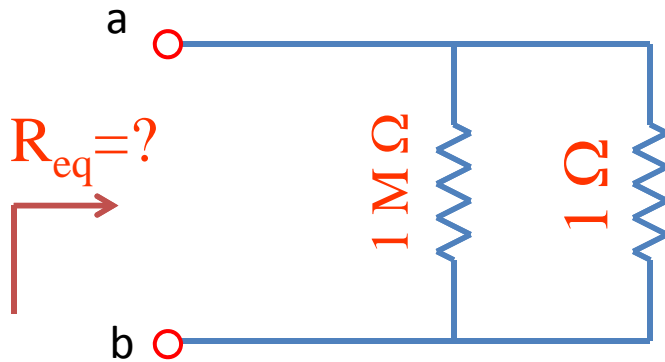

$1\Omega$

$\frac{R_1}{R_2}$  Small

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} \Rightarrow R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$$


$$= R_1 \frac{1}{1 + R_1/R_2} \rightarrow R_1 \frac{1}{1+x} = 1-x+\dots$$

$$\approx R_1 \left(1 - \frac{R_1}{R_2}\right) = 1\Omega \left(1 - \frac{1\Omega}{10^6\Omega}\right)$$



# Questions?

# Voltage addition in circuits

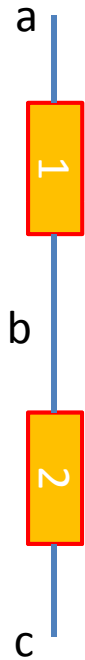


$$V_{ab} \equiv \int_a^b E dx$$

$$\Rightarrow V_{ac} \equiv \int_a^c E dx = \int_a^b E dx + \int_b^c E dx = V_{ab} + V_{bc}$$

$$V_{bc} \equiv \int_b^c E dx$$

$$V_{ac} = V_{ab} + V_{bc}$$

# 2 resistors in series

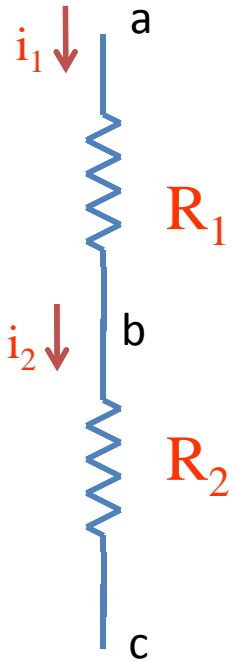

$$i_1 = i_2$$

$$i_1 = \frac{V_{ab}}{R_1}$$

$$i_2 = \frac{V_{bc}}{R_2}$$


$$\frac{V_{ab}}{R_1} = \frac{V_{bc}}{R_2} \Rightarrow V_{bc} = \frac{R_2}{R_1} V_{ab}$$

$$V_{ac} = V_{ab} + V_{bc} = V_{ab} \left( 1 + \frac{R_2}{R_1} \right)$$

$$= i R_1 \left( 1 + \frac{R_2}{R_1} \right) = \underline{i(R_1 + R_2) = V_{ac}}$$


$$R_{eq} = R_1 + R_2$$

# Generalize: N resistors in series

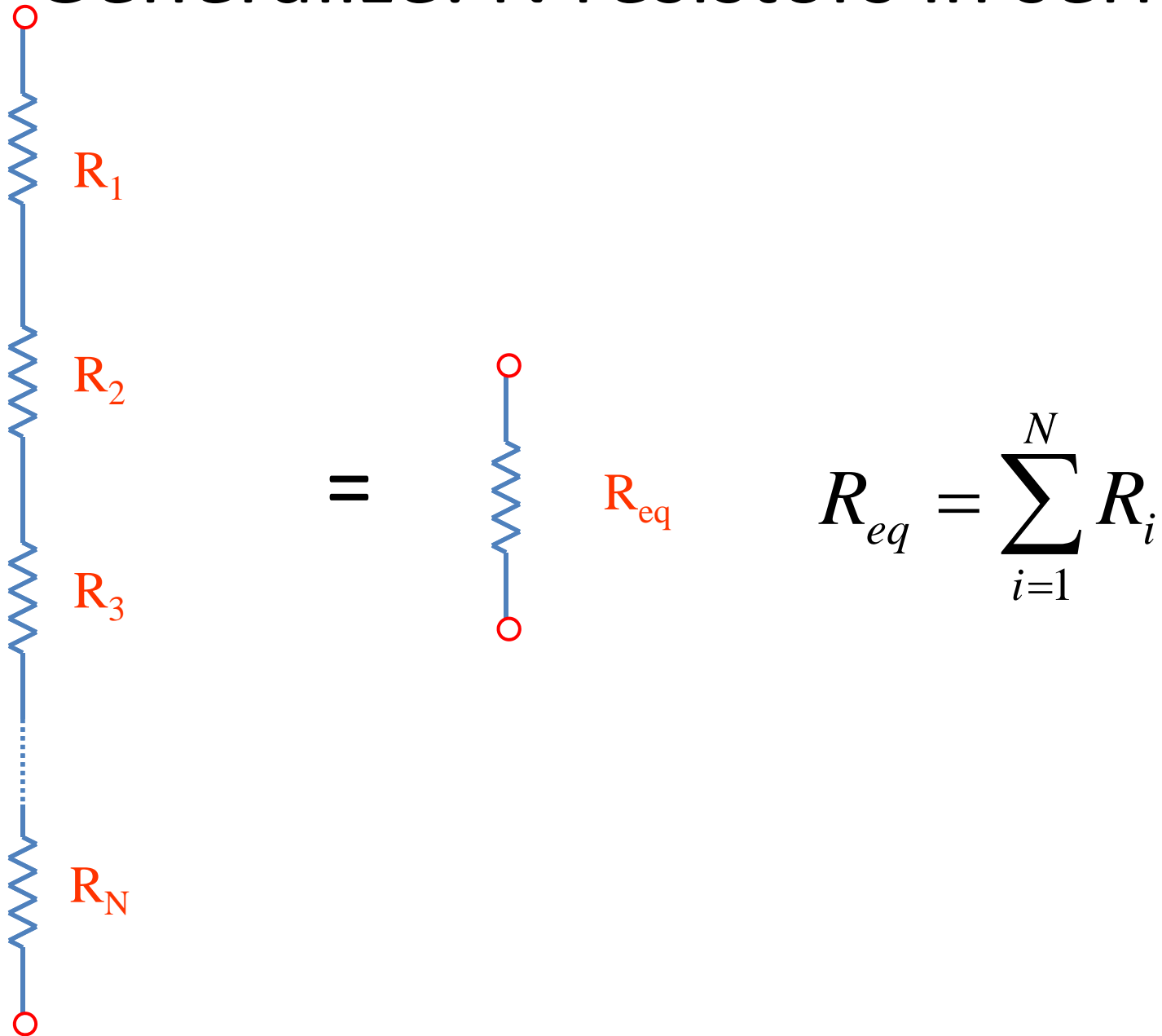


# Example problems

Solve for  $R_{eq}$ . (instructor).

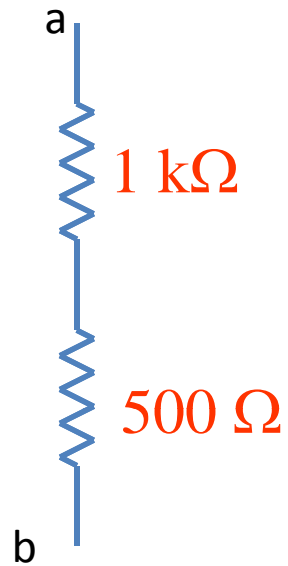


Solve for  $R_{eq}$ . (students).

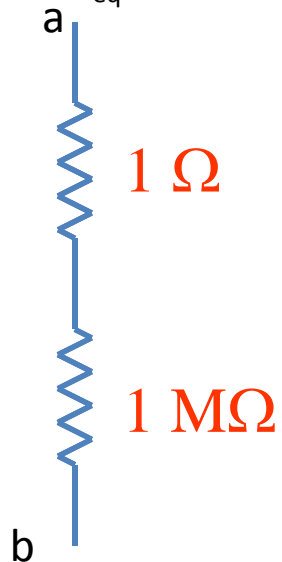

# Questions?


# Example problems

Solve for  $R_{eq}$  (instructor).

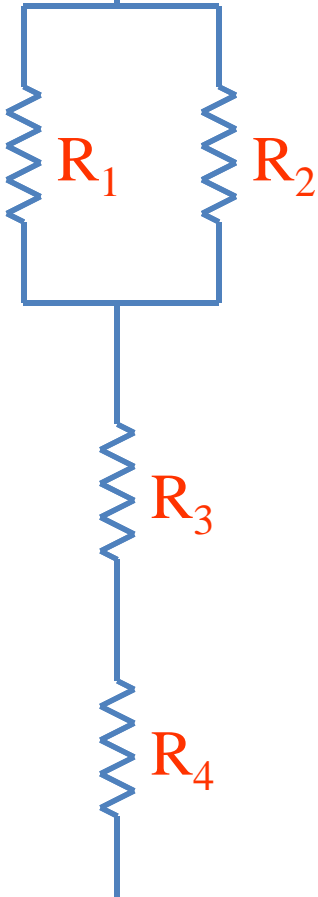

# Example problems


Solve for  $R_{eq}$ . (students).

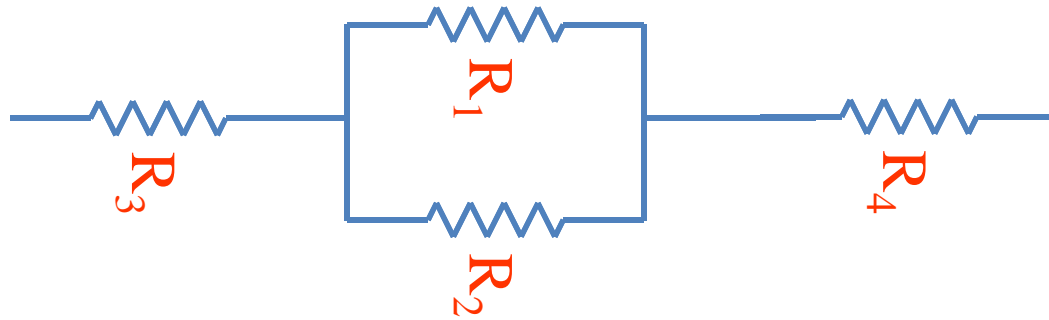




# Example problems

Solve for  $R_{eq}$ . (instructor).

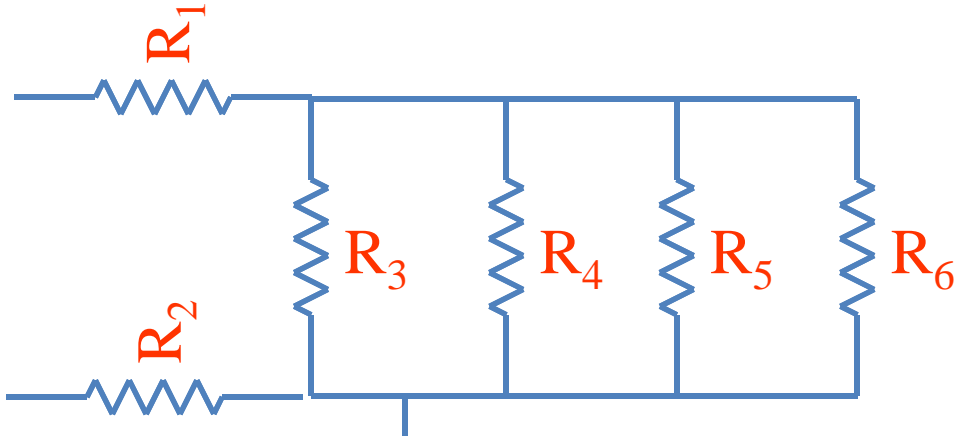

# Example problems

# Voltage divider



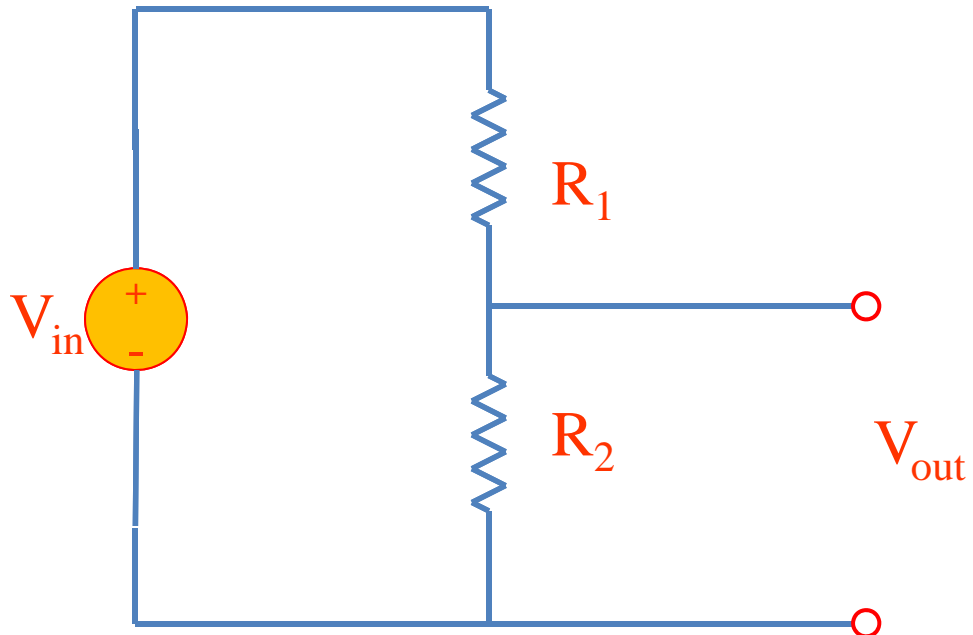


$$V_{out} = \frac{R_2}{R_1 + R_2} V_{in}$$

Why important?  
Concept of source/load. (Thevenin...)

# Source/load concept

# Symbol library

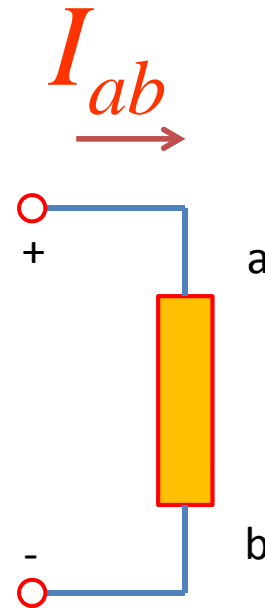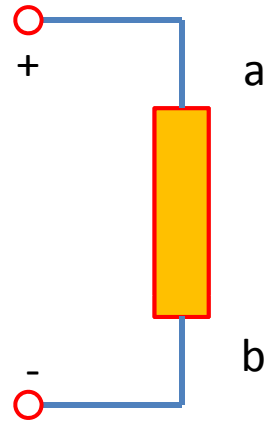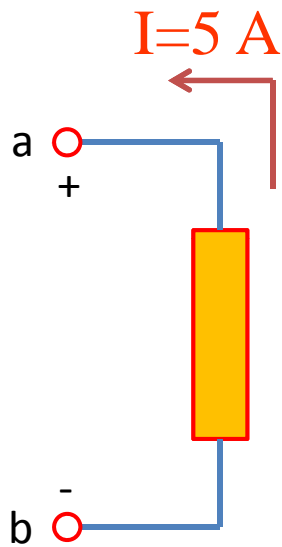

# Symbol library

