

EECS 70A: Network Analysis

Lecture 3

Announcements

- Quiz #1 results excellent
 - A few percent of students confused about sign
- HW 1 due tomorrow in discussion
- Midterm next Thursday (ch 1-2)
 - One more HW and quiz before then
- Recorded lectures to be posted online starting today

Review & agenda


Last lecture:

- Examples
 - Power (sink/source)
 - Current (positive/negative)
 - Dependent sources
- Resistors
 - Series
 - Parallel

Today

- Examples (resistor circuits)
- Kirchoff's laws
- Example applications of Kirchoff laws


Resistors

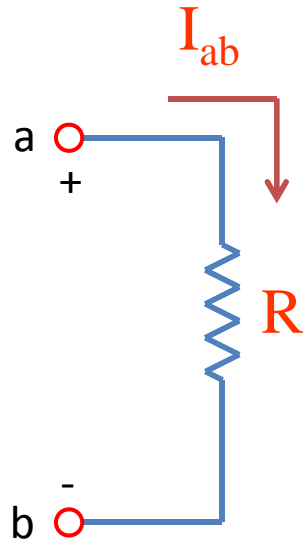

$$V_{ab} = I_{ab} \times R$$

Resistance units: Ohms [Ω]


Generalize: N resistors in parallel

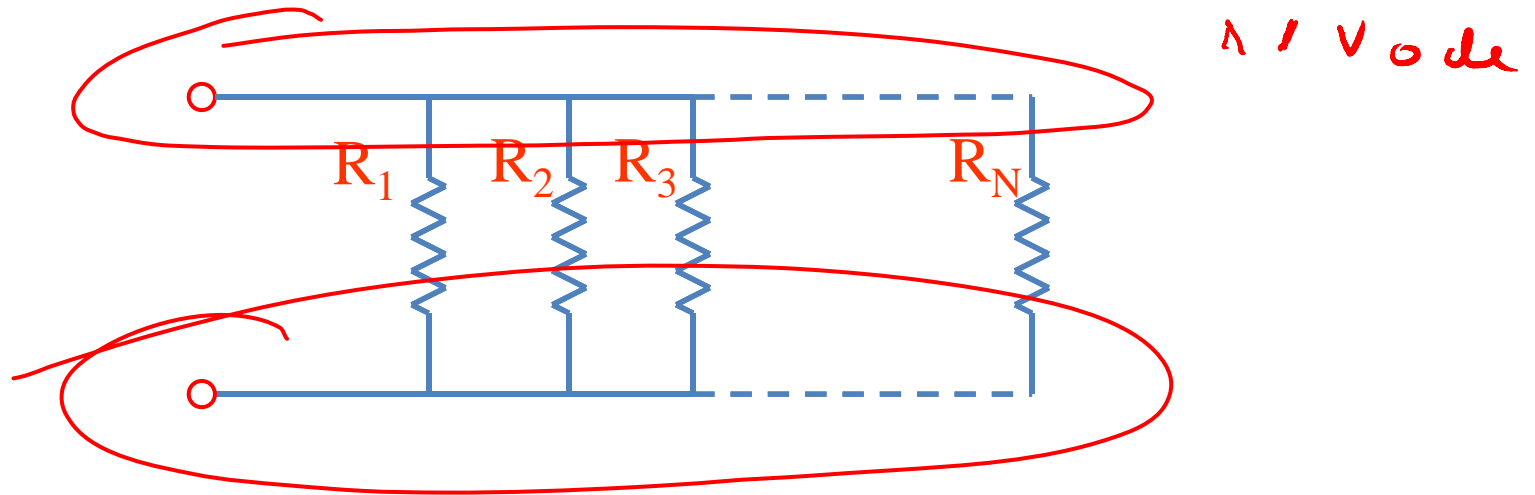


$$= \begin{array}{c} \circ \\ | \\ \text{---} \\ | \\ \text{---} \\ | \\ \circ \end{array} R_{eq} = \frac{1}{R_{eq}} = \sum_{i=1}^N \frac{1}{R_i}$$

$R_1 \parallel R_2$ is notation for " R_1 in parallel with R_2 "


Generalize: N resistors in series

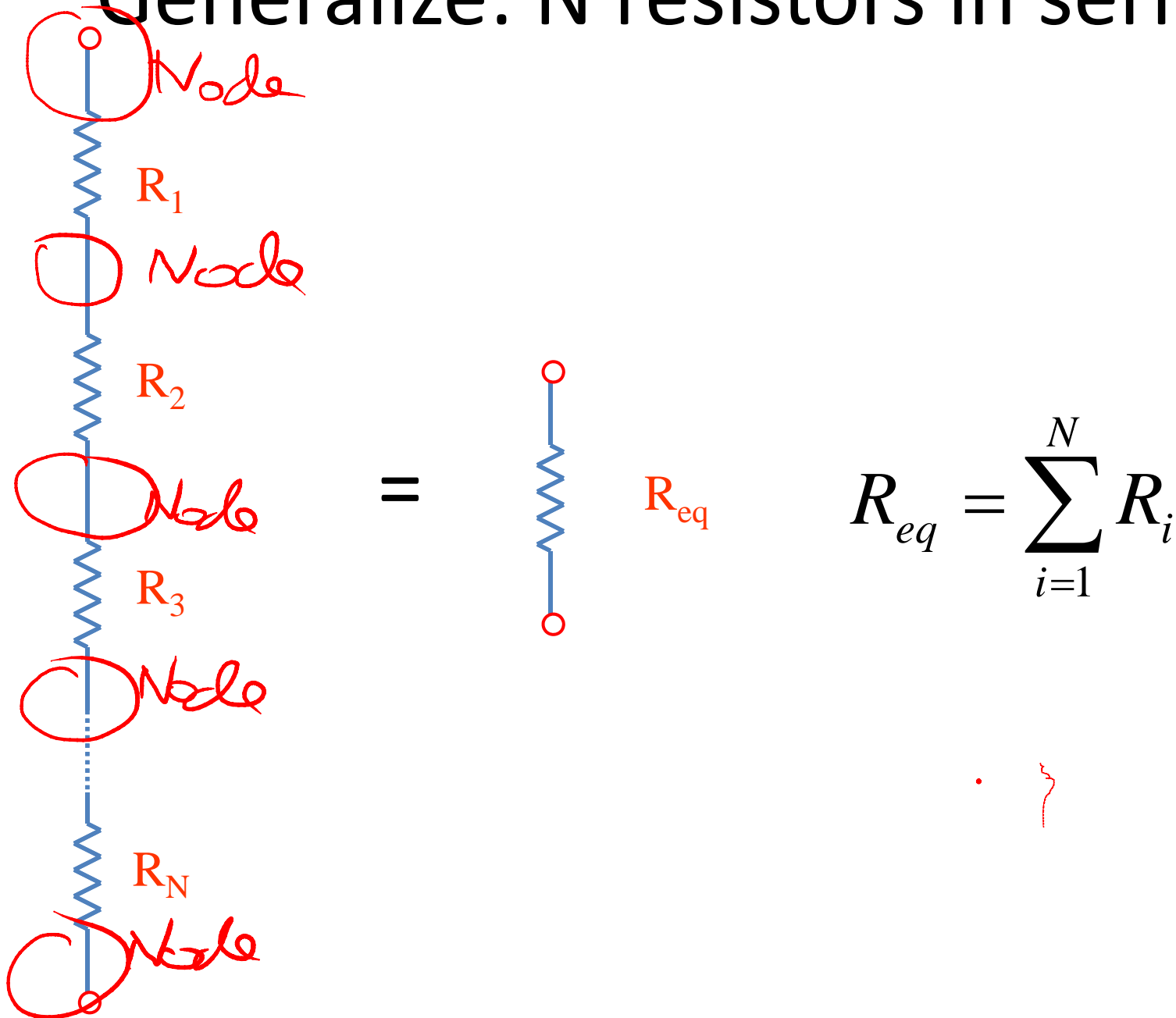

Node

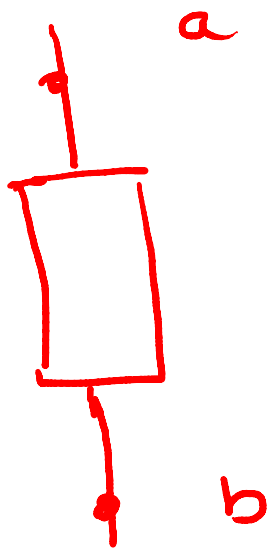
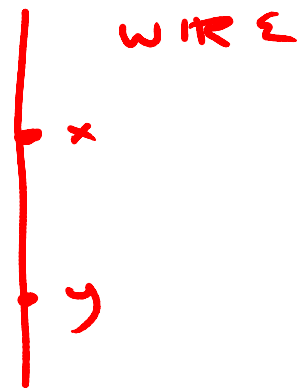
$$V_{ab} \equiv \int_a^b \vec{E} \cdot d\vec{x}$$




$$V_{xy} \equiv \int_x^y \vec{E} \cdot d\vec{x}$$

In ideal metal $\vec{E} = 0$



$$\Rightarrow V_{xy} = 0$$

Node:

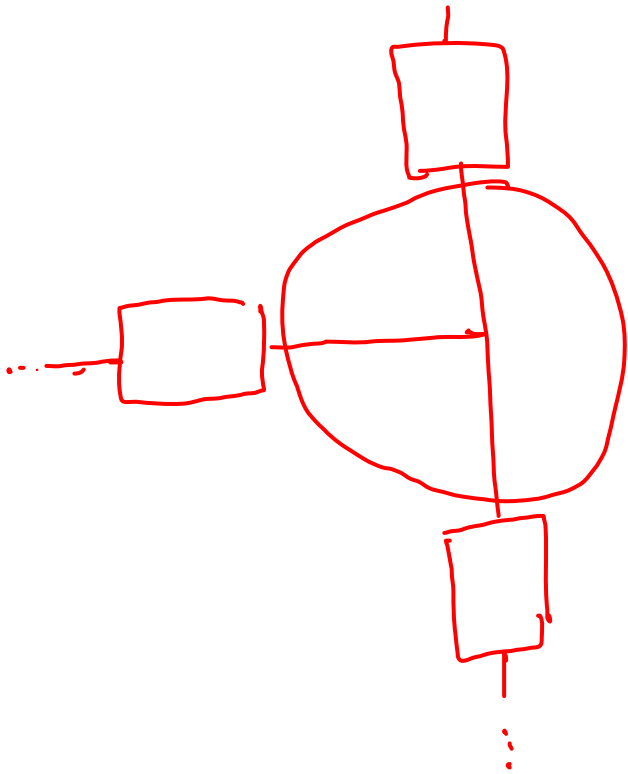

Example problems

Solve for R_{eq} (instructor).

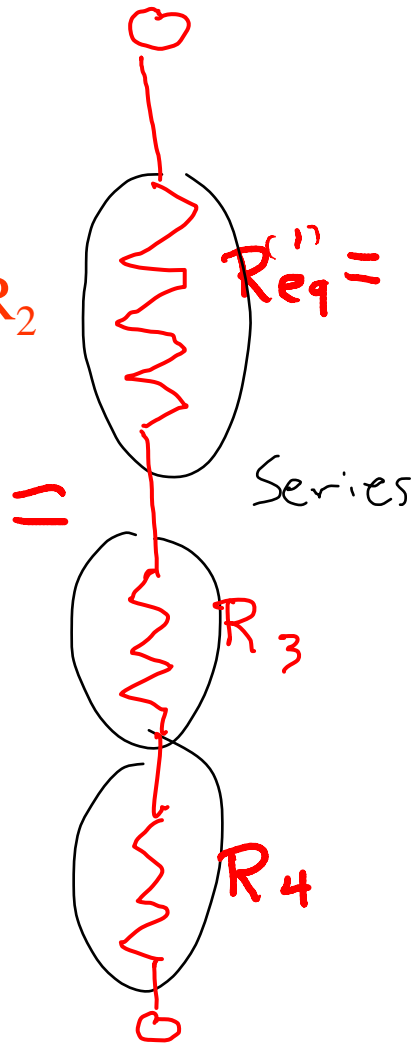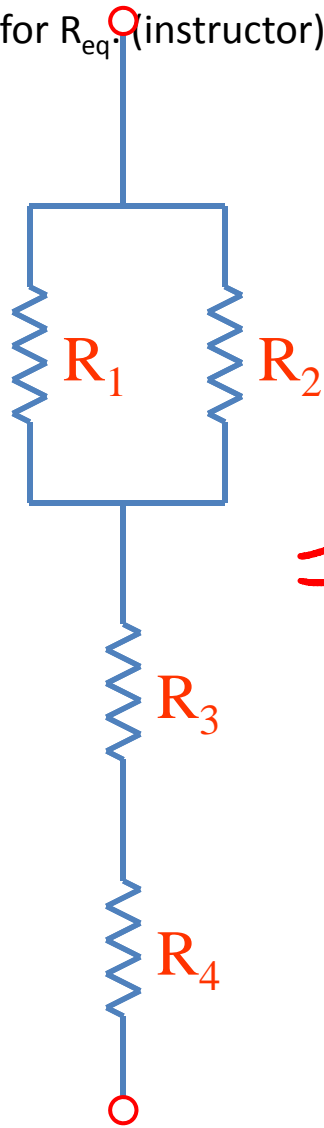

$$R_{eq}^{(1)} = R_1 || R_2$$


$$R_{eq} = (R_1 || R_2) + R_3 + R_4$$



Example problems


Solve for R_{eq} . (students).

pen
test


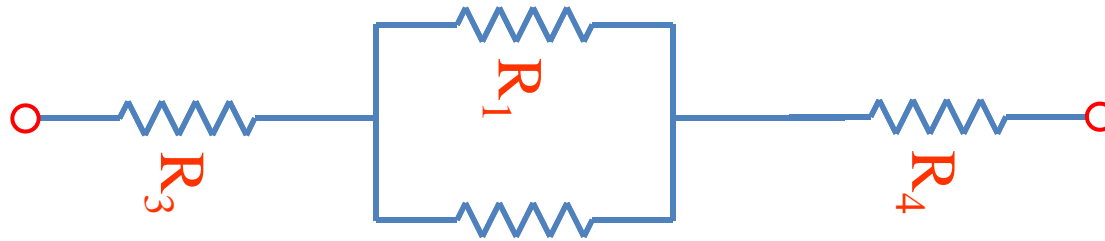


$$R_{eq} = R_3 + (R_1 \parallel R_2) + R_4$$

$$= (R_1 \parallel R_2) + R_3 + R_4$$

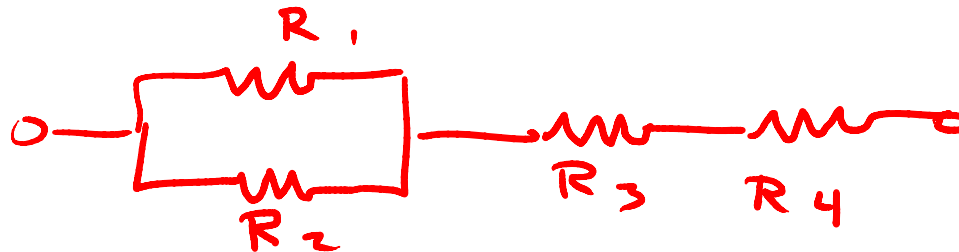

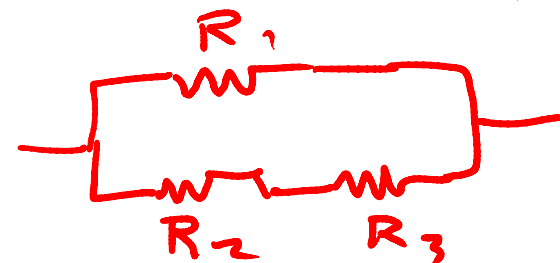
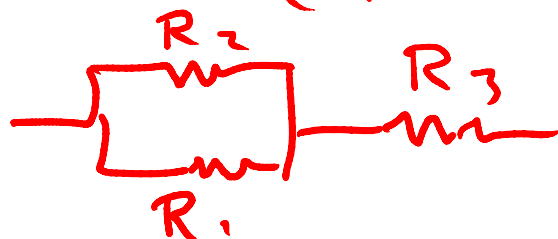
Careful $(R_1 \parallel R_2) + R_3 \neq R_1 \parallel (R_2 + R_3)$



Example problems

Solve for R_{eq} . (instructor).

How many nodes?

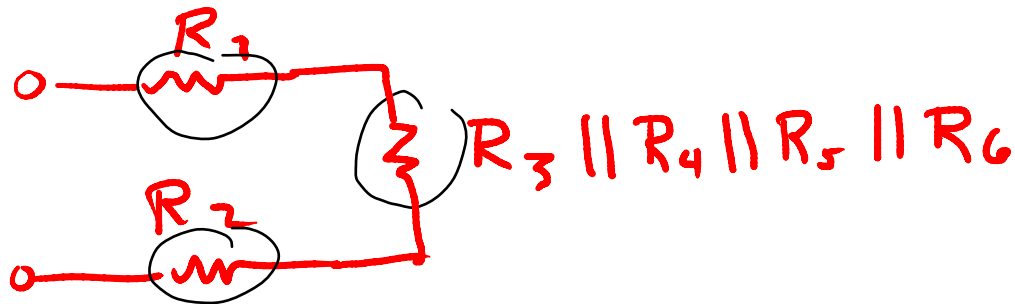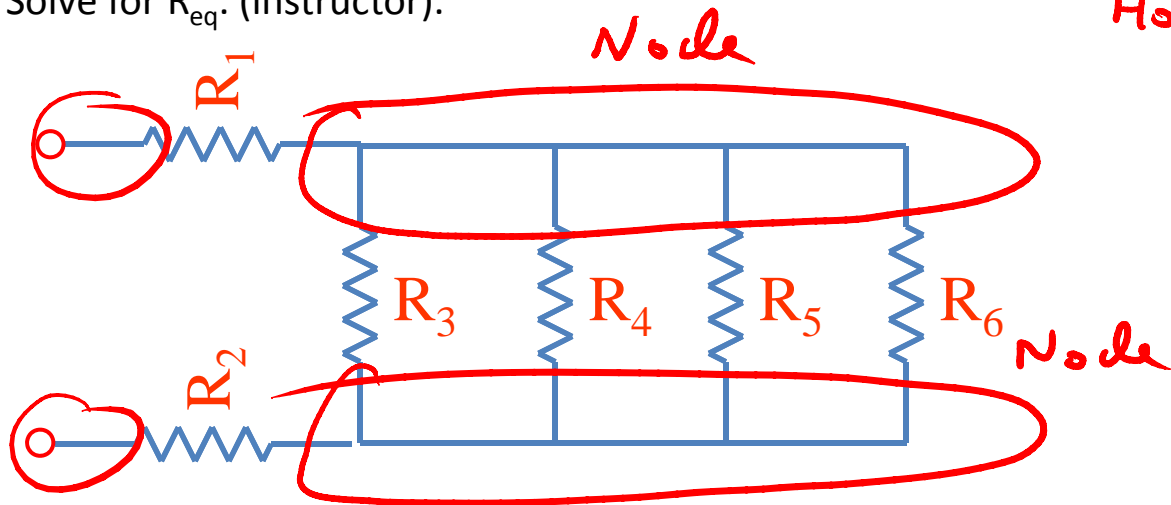

$$R_{eq} = R_1 + (R_3 \parallel R_4 \parallel R_5 \parallel R_6) + R_2$$

$$= R_1 + R_2 + \frac{1}{\frac{1}{R_3} + \frac{1}{R_4} + \frac{1}{R_5} + \frac{1}{R_6}}$$

$$R_3 - R_6 \quad ||$$



$$\frac{1}{R_{eq}^*} = \frac{1}{R_3} + \frac{1}{R_4} + \frac{1}{R_5} + \frac{1}{R_6}$$

$$R_{eq}^* = \frac{1}{\frac{1}{R_3} + \frac{1}{R_4} + \frac{1}{R_5} + \frac{1}{R_6}}$$

Example problems

Solve for R_{eq} . (instructor).

Emphasis: Nodes

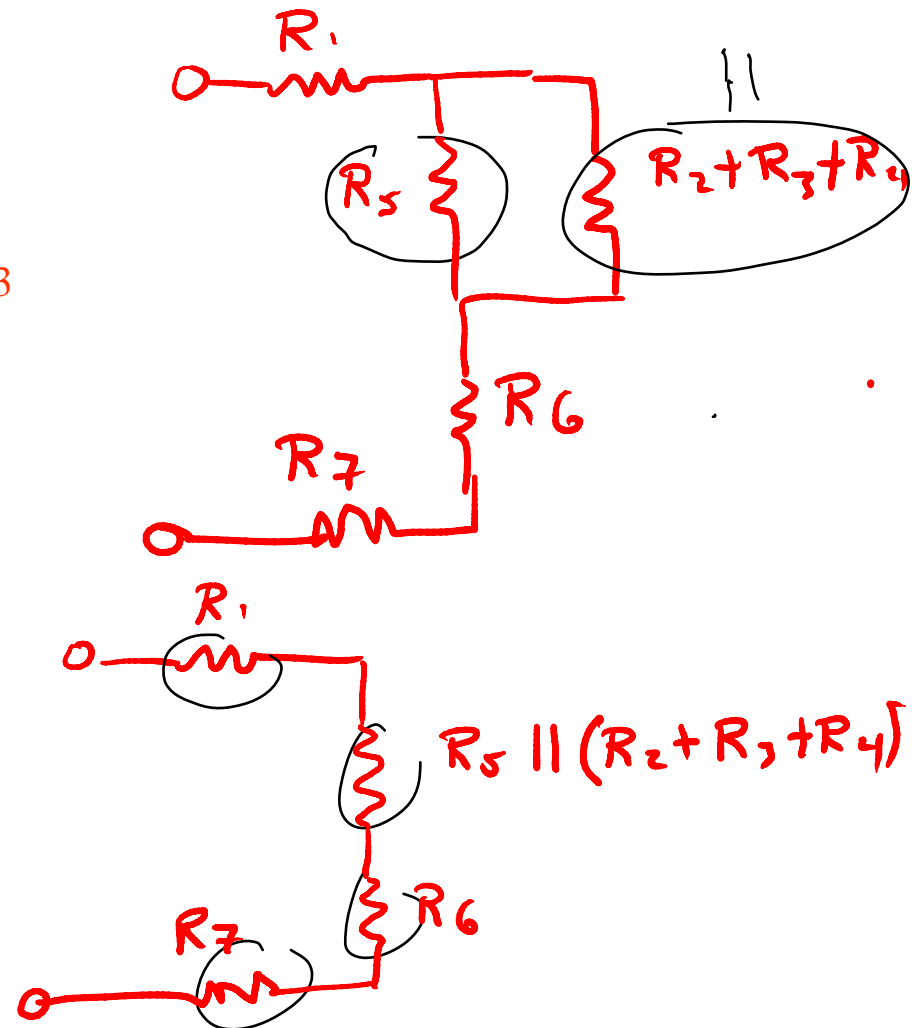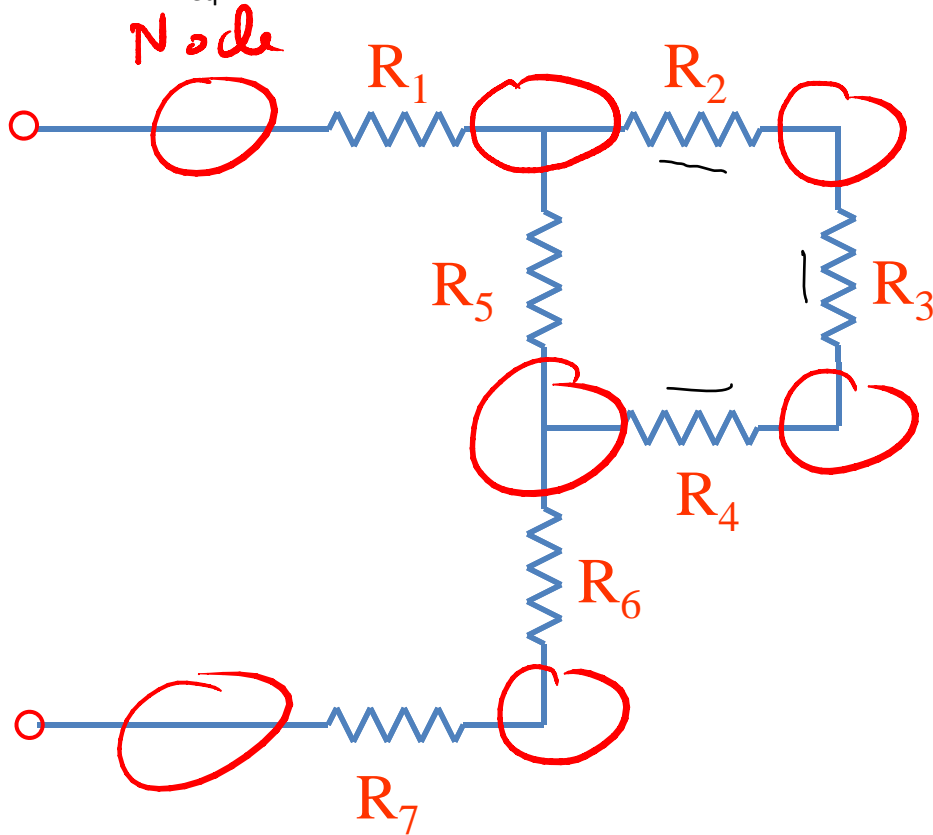


$$= \left\{ \begin{array}{l} R_{eq} = R_1 + R_6 + R_7 \\ + [R_5 \parallel (R_2 + R_3 + R_4)] \end{array} \right.$$

Example problems



Solve for R_{eq} . (instructor).

Emphasis: Nodes



3 nodes

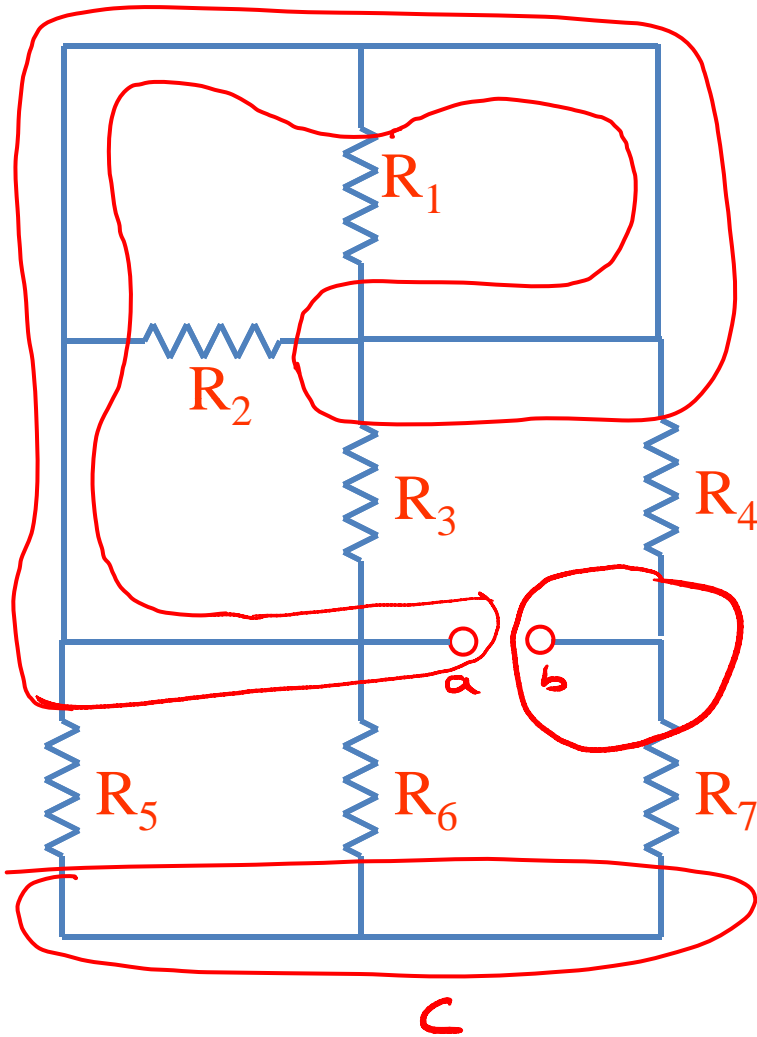


R_1 Shorted
 R_2 shorted
 R_3 shorted

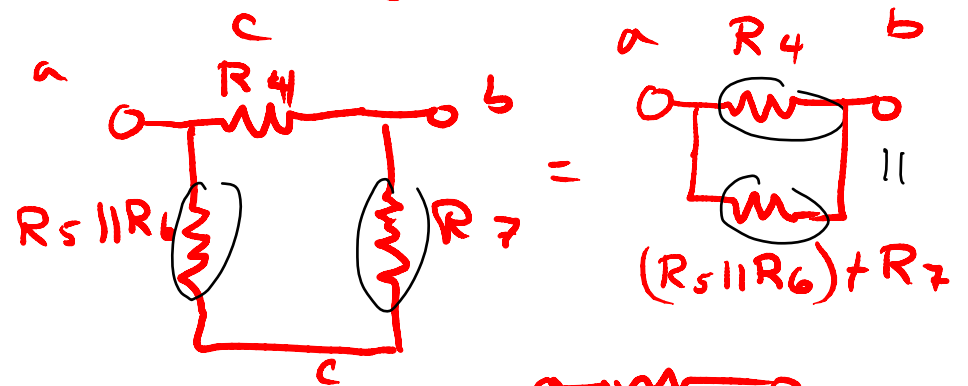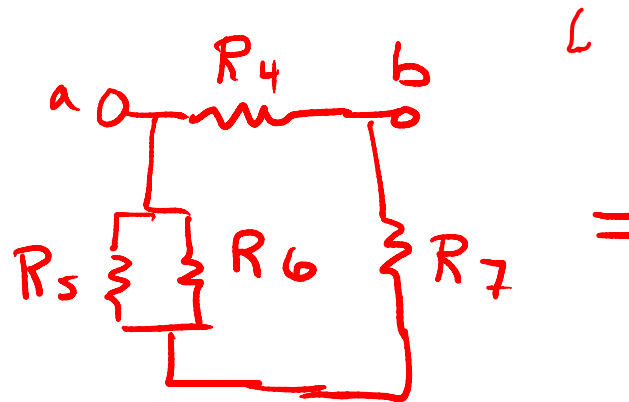

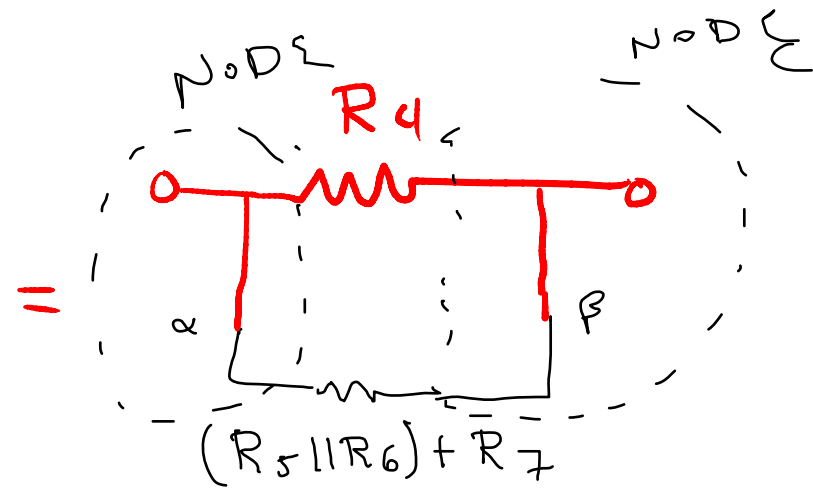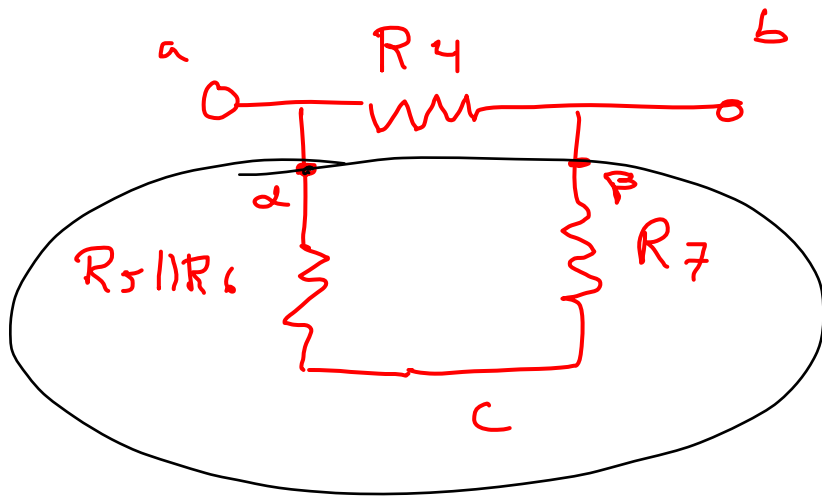
$$R_{eq} = R_4 \parallel \left[(R_5 \parallel R_6) + R_7 \right]$$



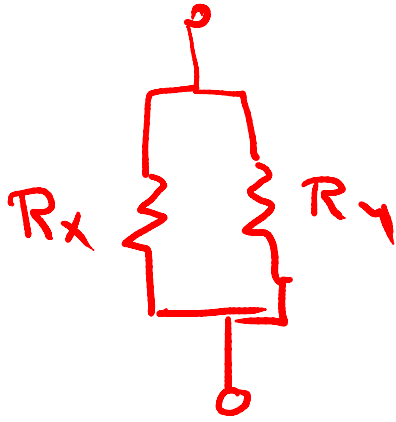

$$R_{eq} = R_x \parallel R_y$$
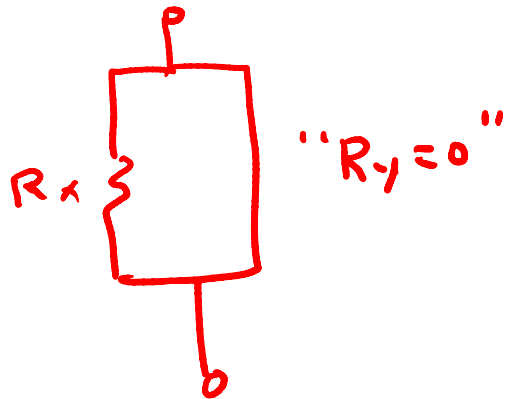
$$\frac{1}{R_{eq}} = \frac{1}{R_x} + \frac{1}{R_y}$$



$$\frac{1}{R_{eq}} = \frac{1}{R_x} + \frac{1}{0} =$$

$$\Rightarrow R_{eq} = 0$$



Voltage divider


Derivation:

$$i R_2 + i R_1 = V_{in}$$

$$i = \frac{V_{in}}{R_1 + R_2}$$

$$V_{out} = i R_2$$


$$= \frac{R_2}{R_1 + R_2} V_{in}$$

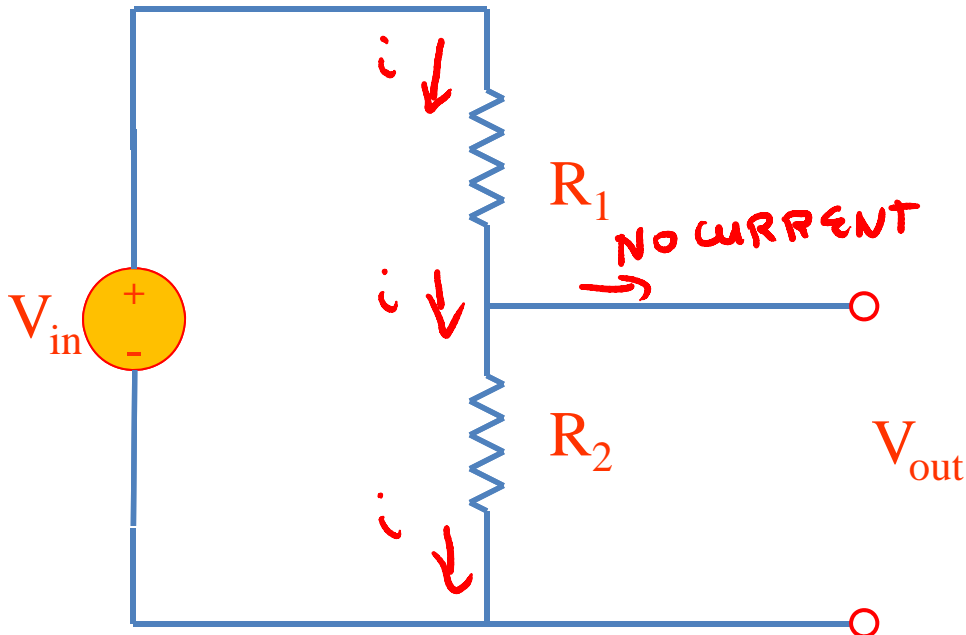

Why important?
Concept of source/load. (Thevenin...)

$$V_{out} = \frac{R_2}{R_1 + R_2} V_{in}$$

Source/load

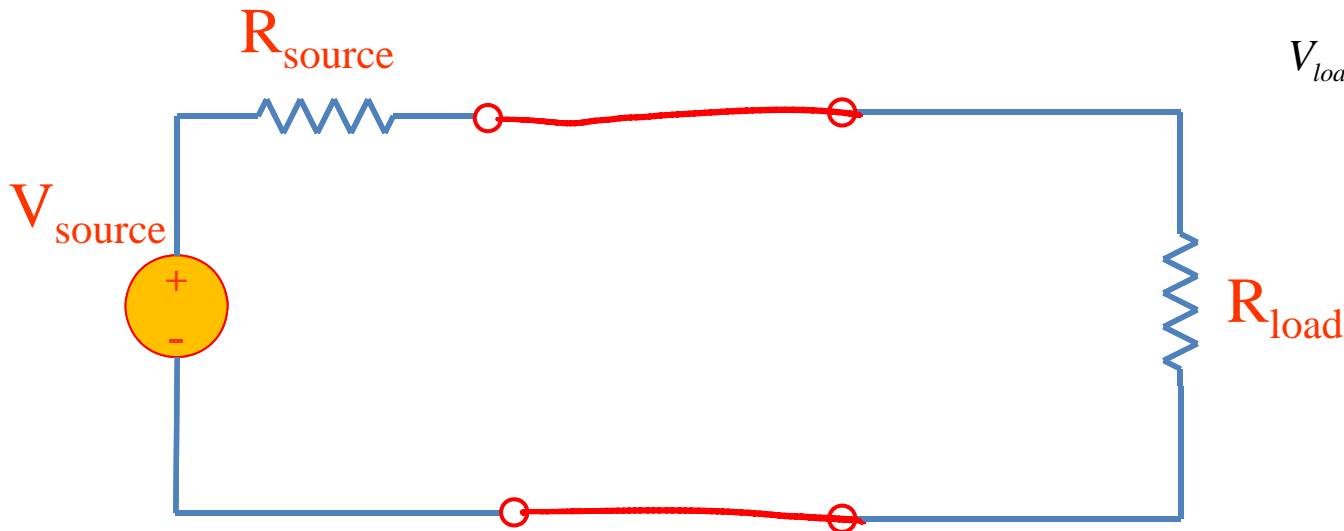

$$V_{load} = \frac{R_{load}}{R_{load} + R_{source}} V_{source}$$

Derivation:



Thevenin Thm:
Any circuit can be represented by this equivalent circuit.

Case 1:

$$R_{load} \gg R_{source}$$

$$\Rightarrow V_{load} \approx V_{source}$$



Case 2:

$$R_{source} \gg R_{load}$$

$$V_{load} \rightarrow 0$$
$$\approx \frac{R_{load}}{R_{source}} V_{source}$$

We say R_{load} "loads down" the source.

"Brownout"

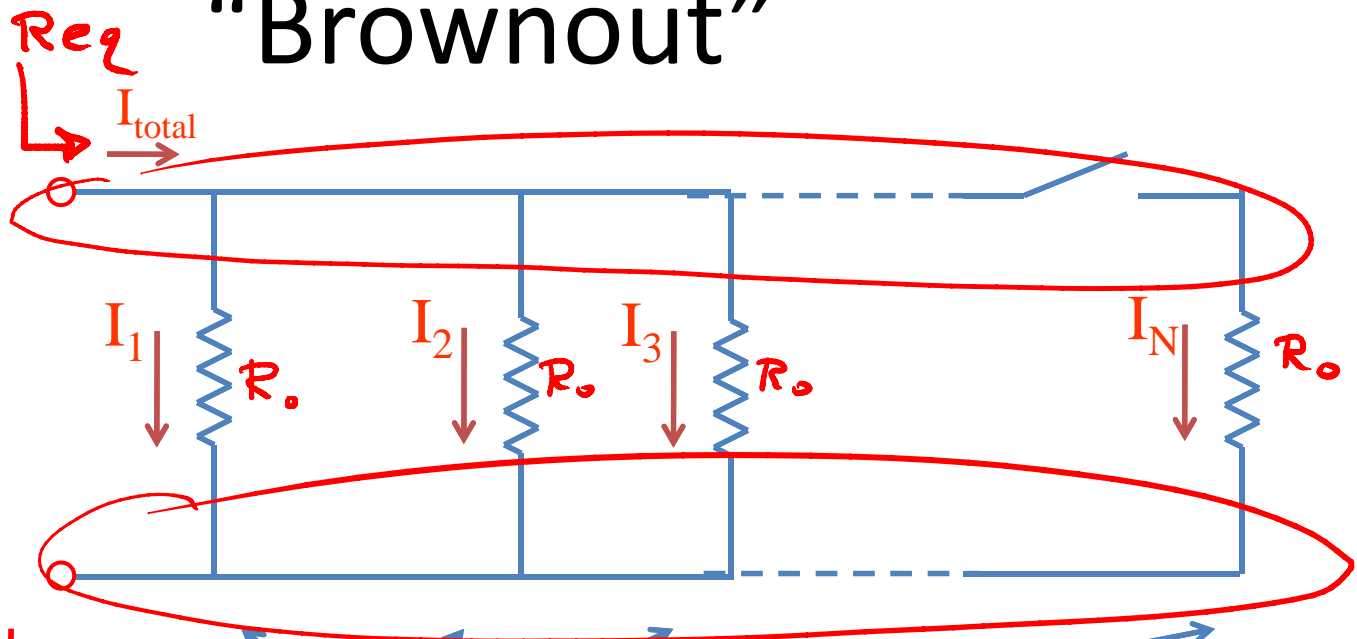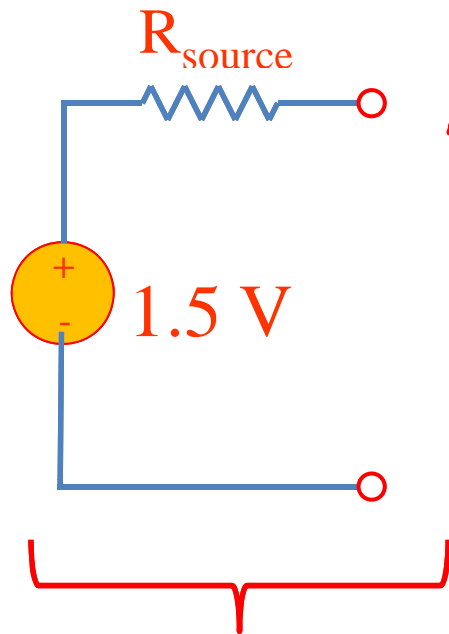

DEMO...


$$I_1 = I_2 = I_3 = \dots = I_N$$

Battery/light bulbs

“Fanout”

Questions?


Notation: one element

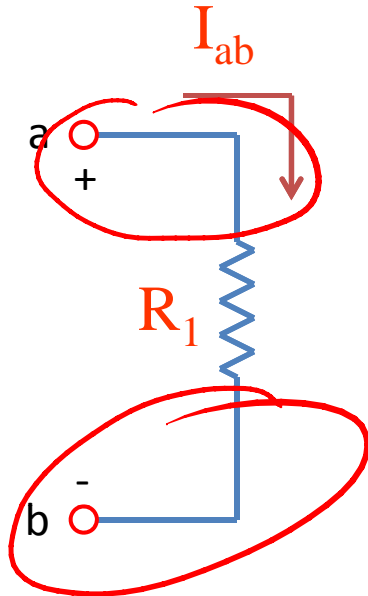

$$V_{ab} = I_{ab} R_1$$

V_{ab} is the voltage *drop* from a to b.

Textbook chapter 2 notation:

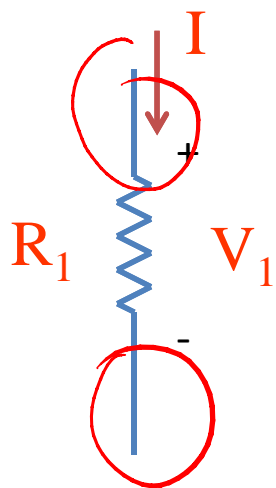


$$V_1 = I R_1$$

In chapter 2, text does not label each node.
 V_1 is voltage drop across resistor 1.

Notation: two elements in series


Textbook chapter 2 notation:

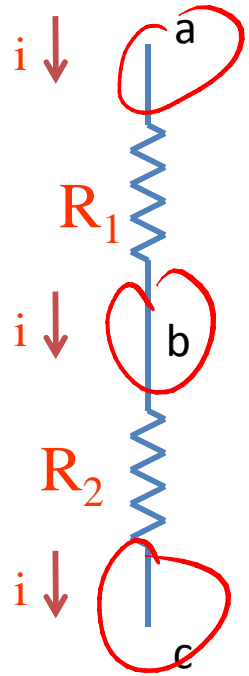

$$i = \frac{V_{ab}}{R_1}$$

$$i = \frac{V_{bc}}{R_2}$$

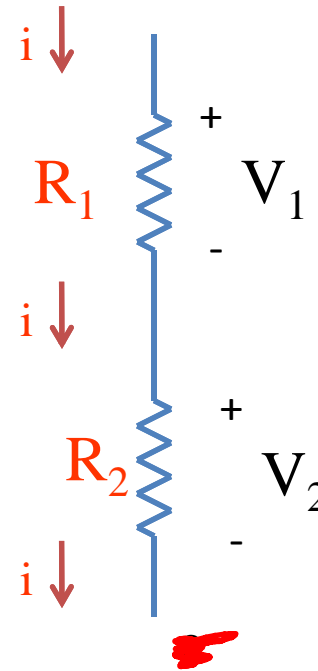V_{ab} is the voltage drop across resistor 1




$$i = \frac{V_1}{R_1}$$

$$i = \frac{V_2}{R_2}$$

V_1 is the voltage drop across resistor 1


Letters and numbers

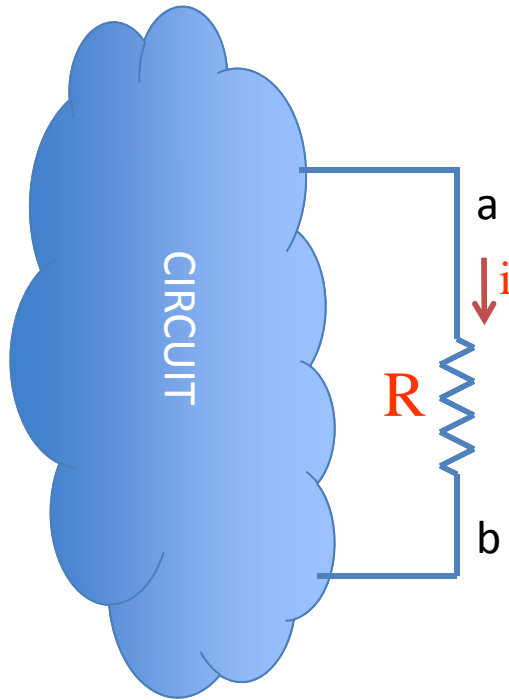Both can be used to label nodes, resistors, voltages, currents, etc.



$$i = \frac{V_{ab}}{R}$$

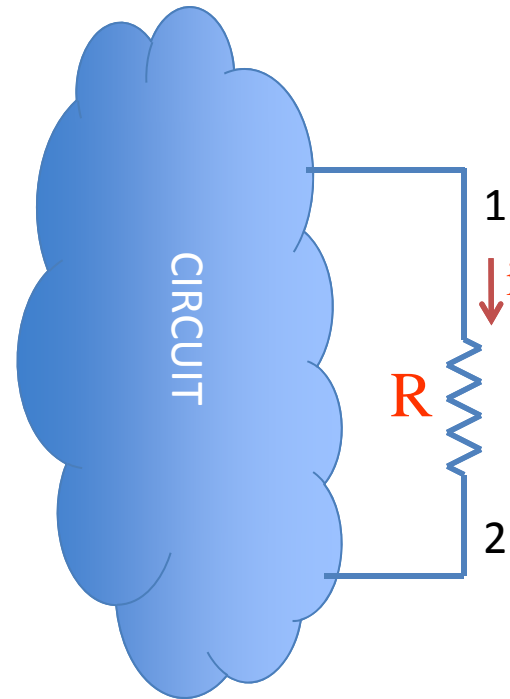V_{ab} is the voltage drop across resistor 1




$$i = \frac{V_{12}}{R}$$

V_{12} is the voltage drop across resistor 1


Chapter 2 notation

Textbook chapter 2 notation:

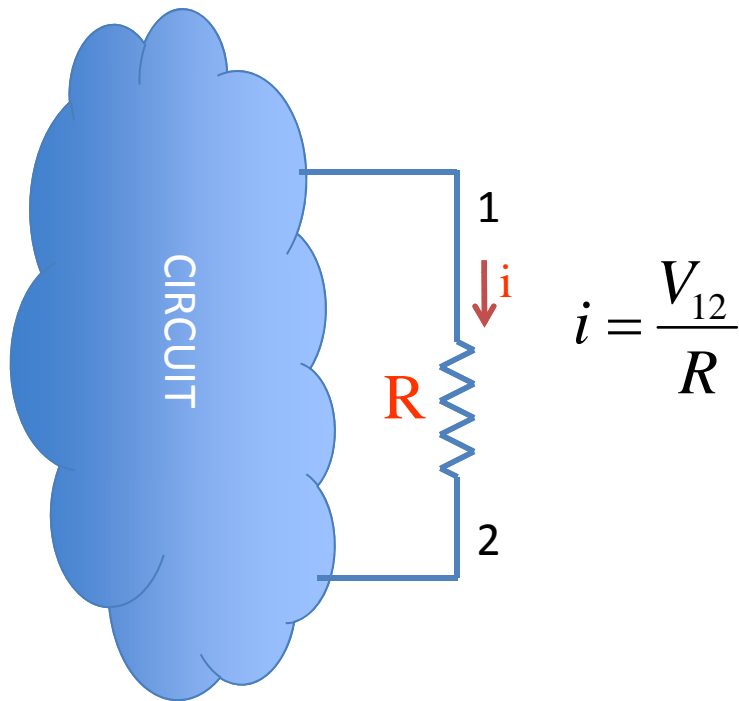

$$i = \frac{V_{12}}{R}$$

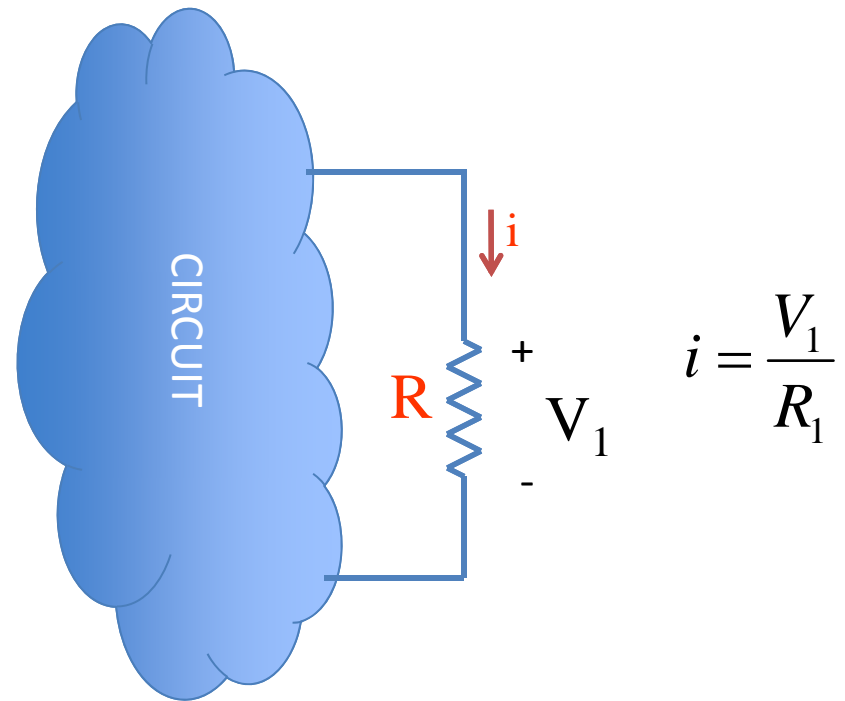V_{12} is the voltage drop
across resistor 1




$$i = \frac{V_1}{R_1}$$

V_1 is the voltage drop
across resistor 1

Questions?

Kirchoff's current law

You have already seen:

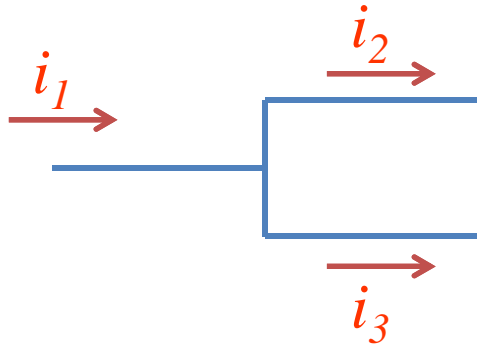

$$i_1 = i_2 + i_3$$

Like water in a river...

More generally:

Sum of currents *entering* node = sum of currents *leaving* node.


Stated as Kirchoff's current law (KCL):

$$\sum_{n=1}^N i_n = 0$$

Current *entering* a node: i_n positive
Current *leaving* a node: i_n negative

KCL examples

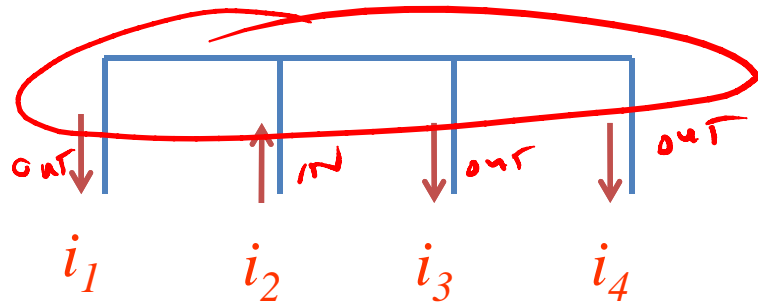Find a relationship among i_1, i_2, i_3, i_4 (instructor)




IN: i_2

OUT: $i_1 + i_3 + i_4$

KCL $\Rightarrow i_2 = i_1 + i_3 + i_4$

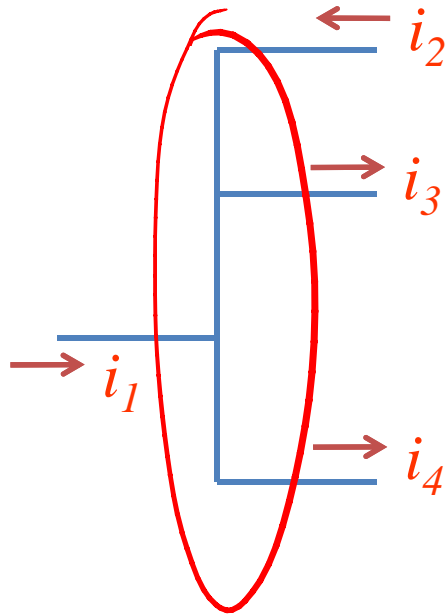Find a relationship among i_1, i_2, i_3, i_4 (students)




IN $i_1 + i_2$

OUT $i_3 + i_4$

KCL $\Rightarrow i_1 + i_2 = i_3 + i_4$


KCL examples

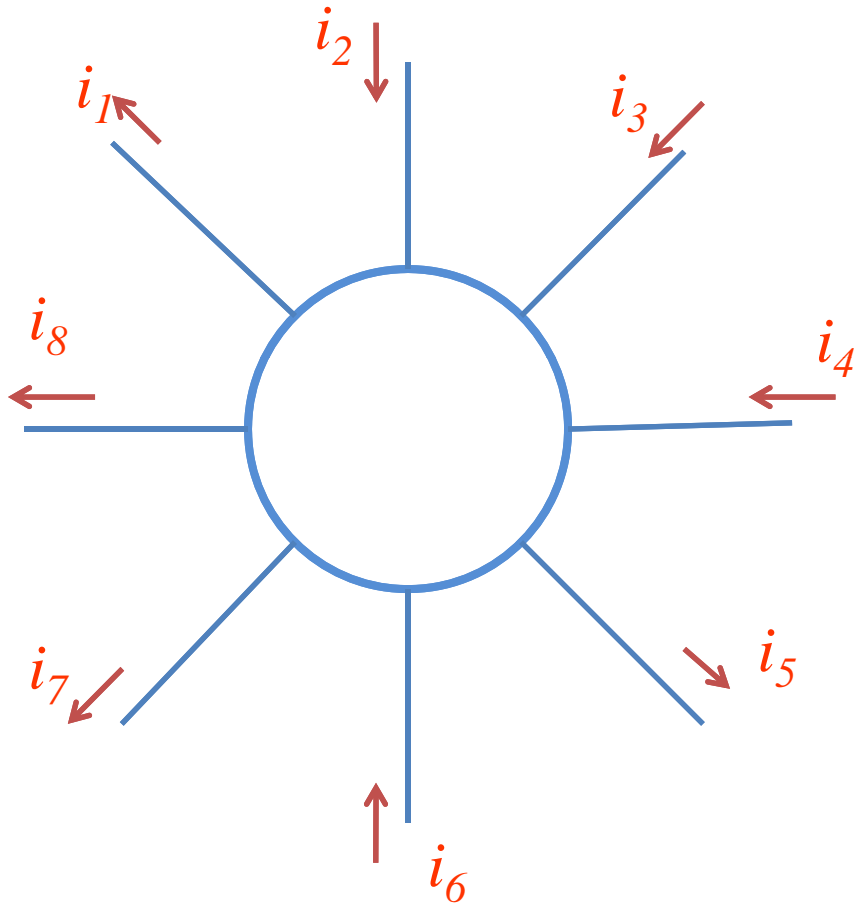Find a relationship among $i_1, i_2, i_3, i_4, \dots$ (instructor)




KCL examples

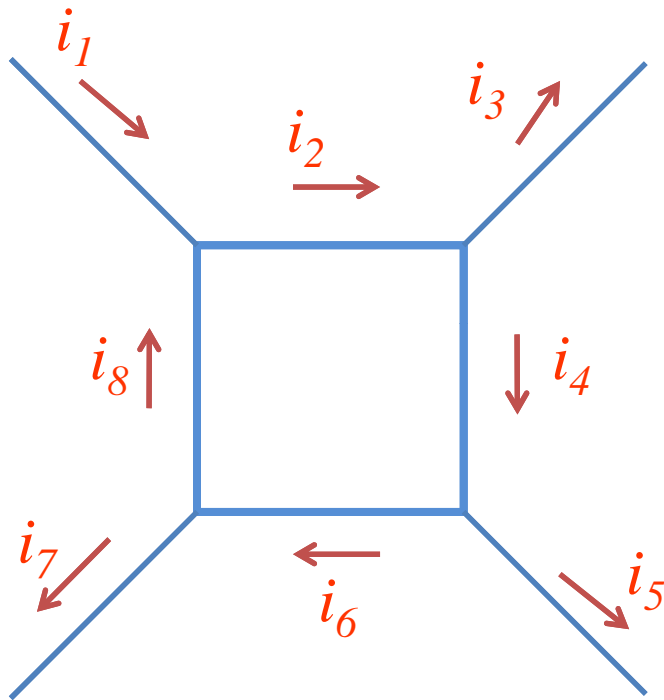Find a relationship among $i_1, i_2, i_3, i_4, \dots$ (instructor)




KCL examples

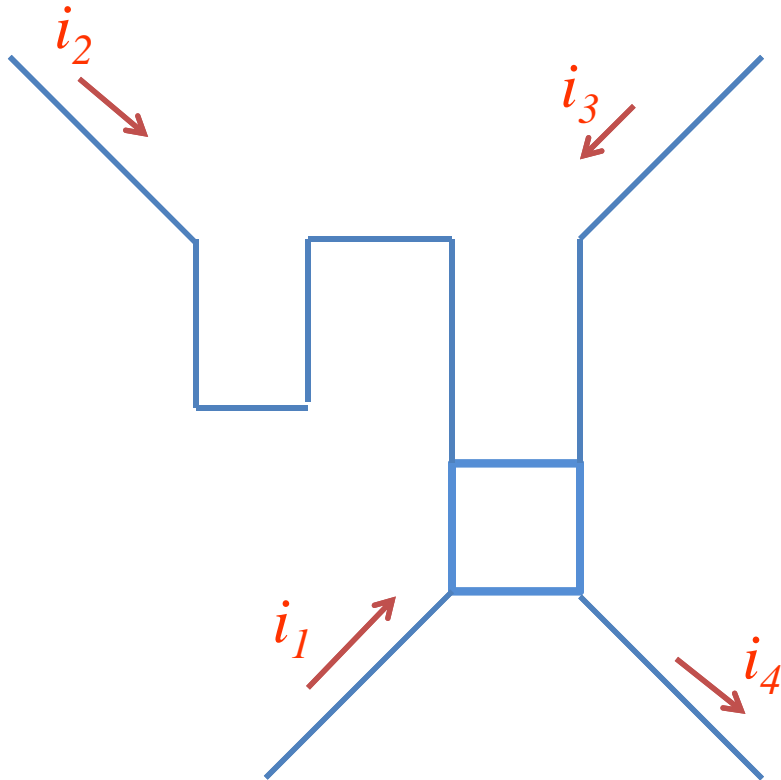Find a relationship among $i_1, i_2, i_3, i_4, \dots$ (students)




KCL examples

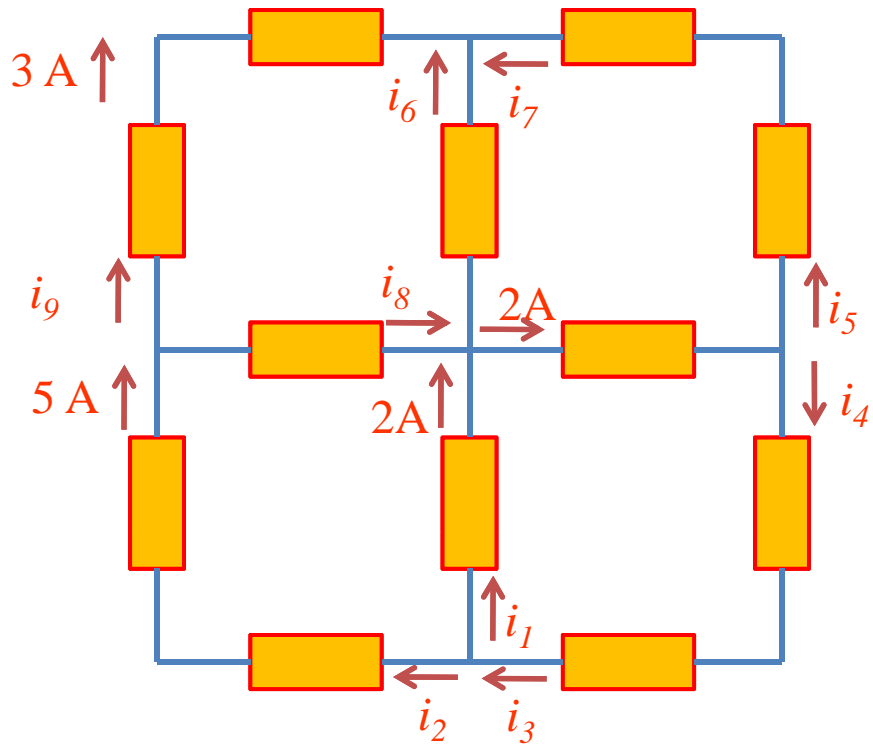- a) Find the # of nodes in this circuit. (Instructor)
b) Find i_1 thru i_9 in this circuit. (Instructor)
Hint: Apply KCL at each node.




KCL examples

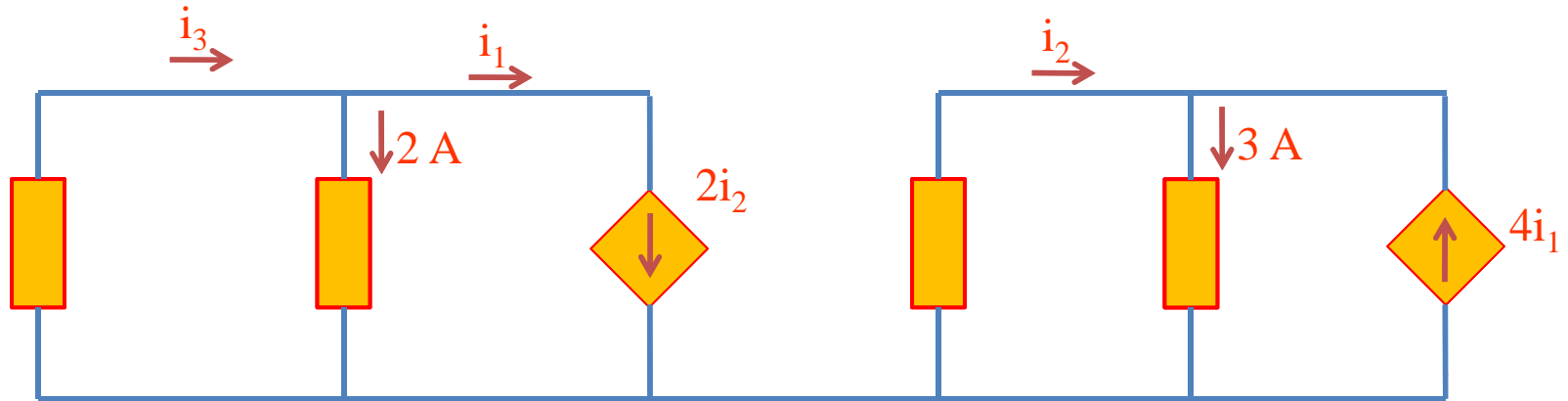- a) Find the # of nodes in this circuit. (Instructor)
b) Find i_1 , i_2 & i_3 in this circuit. (Instructor)
Hint: Apply KCL at each node.



KCL examples

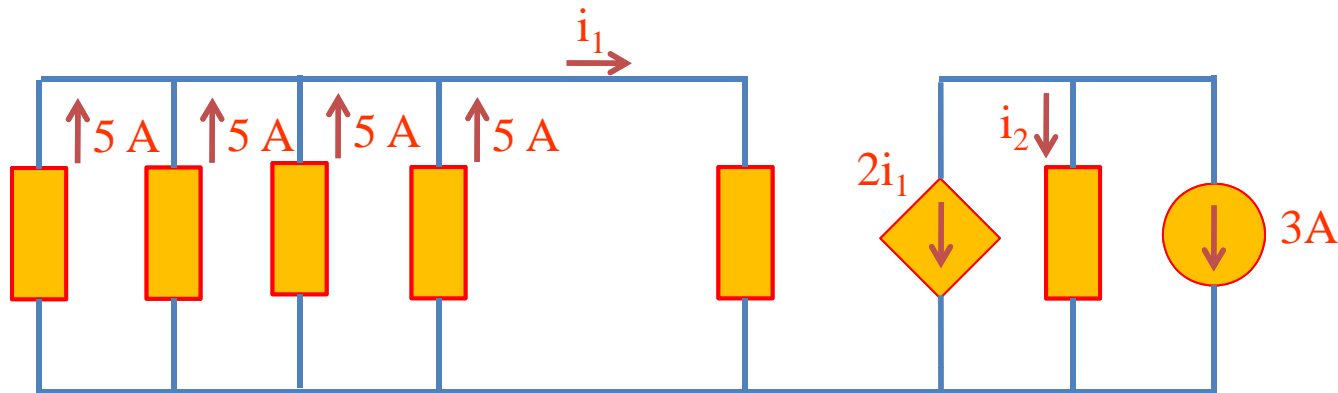
- a) Find the # of nodes in this circuit. (students)
b) Find i_1 & i_2 in this circuit. (students)
Hint: Apply KCL at each node.



Questions?

Voltage addition in circuits

From lecture #2:

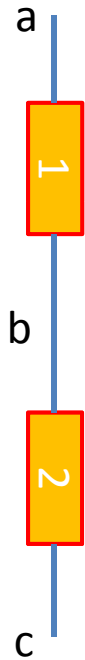

$$V_{ab} \equiv \int_a^b E dx$$

$$\Rightarrow V_{ac} \equiv \int_a^c E dx = \int_a^b E dx + \int_b^c E dx = V_{ab} + V_{bc}$$


$$V_{bc} \equiv \int_b^c E dx$$

$$V_{ac} = V_{ab} + V_{bc}$$

V_{ab} = “voltage drop” across element # 1

V_{bc} = “voltage drop” across element # 2

Closing the loop:

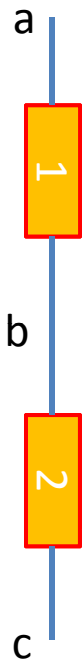


$$V_{ac} = V_{ab} + V_{bc}$$

V_{ab} = “voltage drop” across element # 1

V_{bc} = “voltage drop” across element # 2

Generalize loop to N-elements:

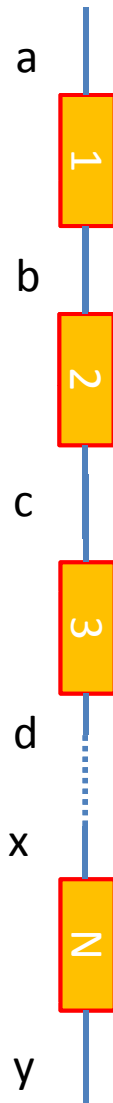

$$V_{ay} = V_{ab} + V_{bc} + V_{cd} + \dots + V_{xy}$$

V_{ab} = “voltage drop” across element # 1

V_{bc} = “voltage drop” across element # 2


V_{cd} = “voltage drop” across element # 3

V_{xy} = “voltage drop” across element # N

Kirchoff's voltage law

$$\sum_{n=1}^N v_n = 0$$




around *any* closed loop.

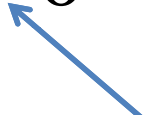


voltage *drops*

Questions?

Symbol library

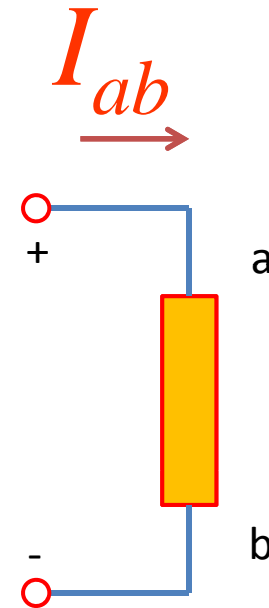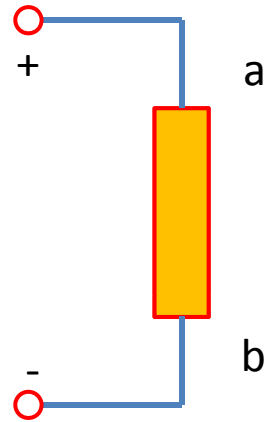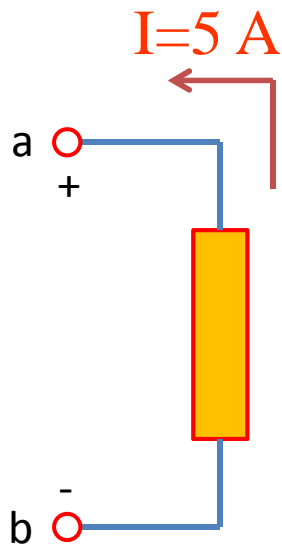

Symbol library

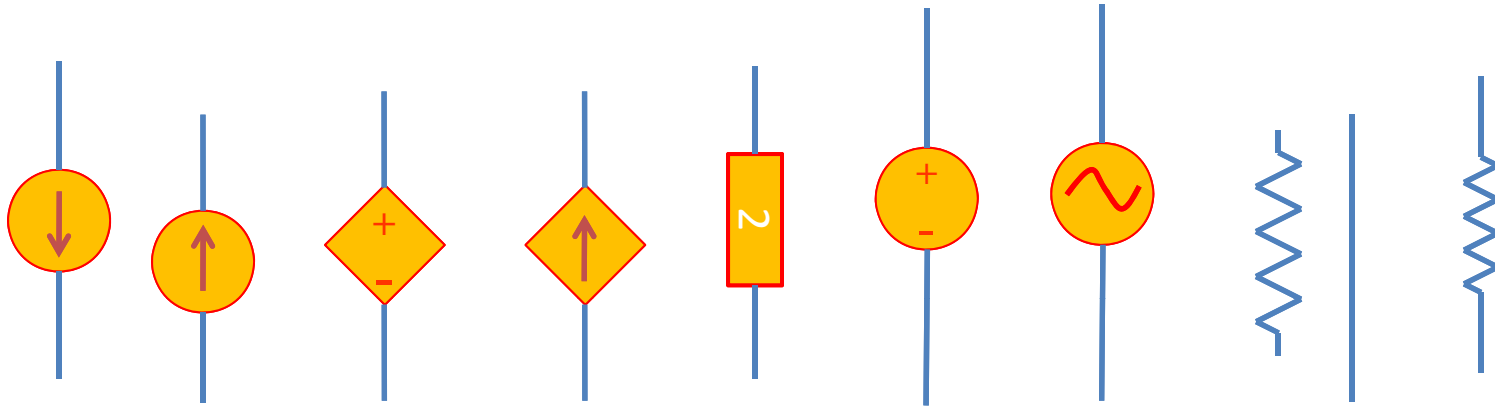

Symbol & circuit library

