

Announcements:

1. Announcements


EECS 70A: Network Analysis

Lecture 6

Today's Agenda

- Review of Nodal Analysis
- Mesh Analysis
 - Introduction
 - What is a Mesh?
 - Mesh Current
 - Method
- Mesh Analysis with Current Source

Node Voltage(review)

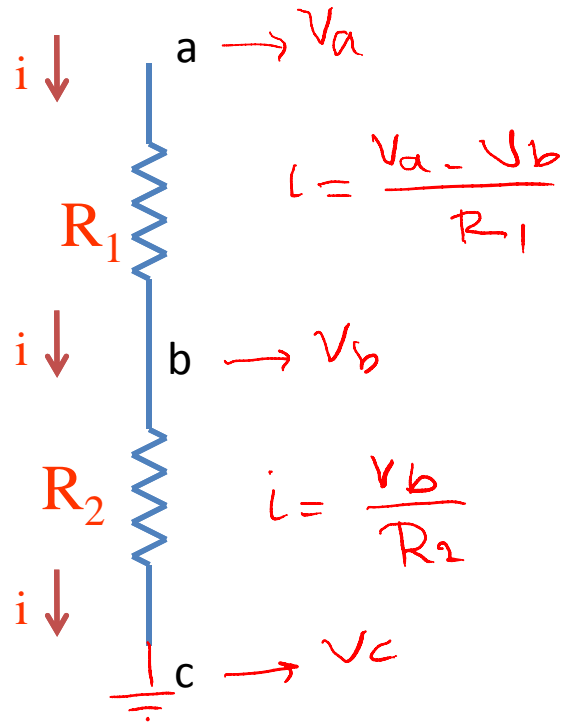


V_{ab} is the voltage drop
across resistor 1

Nodal Analysis(Review)

Based on KCL, Use node voltages as circuits variables.

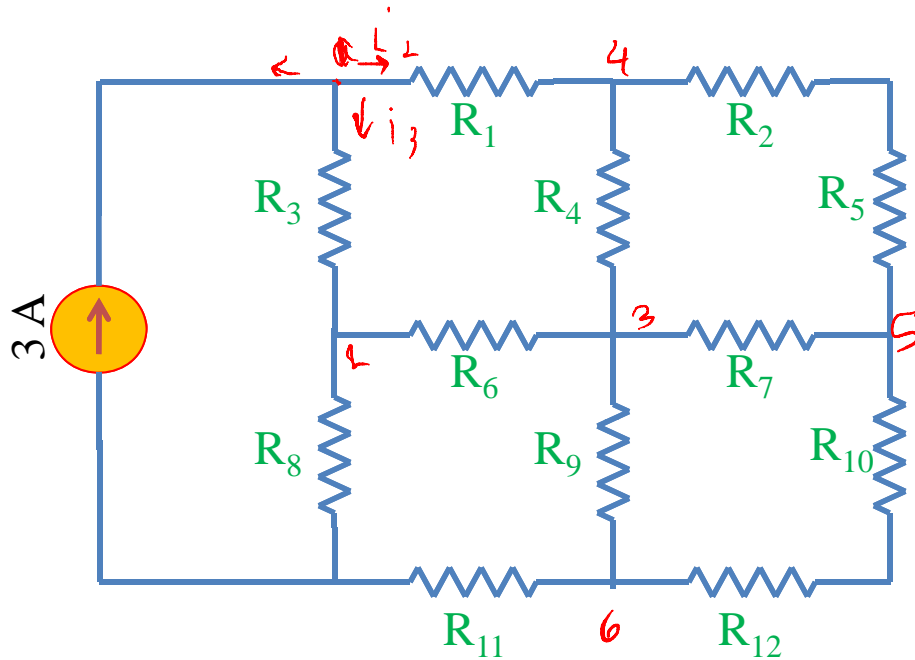1. Define a reference node.
2. Label remaining nodes. (n-1 nodes)
3. Apply KCL + ohm to all nodes and supernodes
 1. Express all I's in terms of v's
4. Apply KVL to loops with voltage source
5. Solve the n-1 simultaneous equations, to find V's
6. Use Ohm's law to find the currents.

Apply KCL + Ohm to All Nodes and Supernodes




$$i_3 = \frac{V_1 - V_2}{R_3}, \quad \frac{V_1 - V_4}{R_1} = i_2$$

KCL (1):

$$\frac{V_n - V_k}{R_{n,k}}$$

$$\frac{V_3 - V_4}{R_4} + \frac{V_3 - V_2}{R_6} + \frac{V_3 - V_5}{R_7} + \frac{V_3 - V_6}{R_9} = 0$$

Nodal Analysis-Example

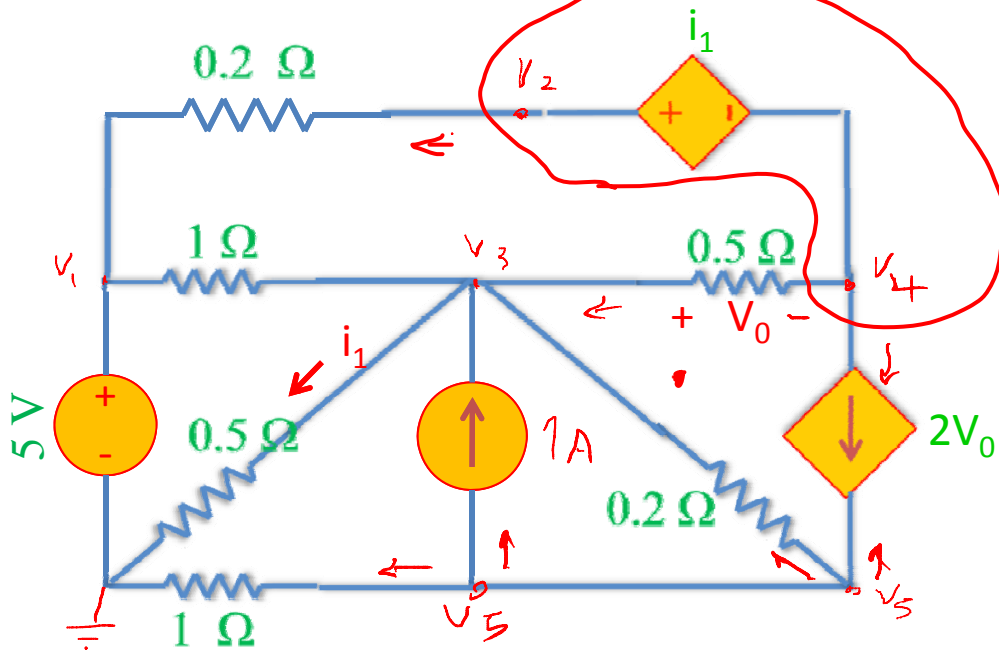

$$v_1 = 5V$$

$$\textcircled{3} \quad \frac{v_3 - v_1}{1} + 2v_3 + 5(v_3 - v_5) + 2(v_3 - v_4) - 1 = 0$$

$$-v_1 + 10v_3 - 5v_5 - 2v_4 = 1$$

$$10v_3 - 2v_4 - 5v_5 = 6 \quad (1)$$

(2)

$$\textcircled{5} \quad v_5 + 1 + 5(v_5 - v_3) - 2(v_3 - v_4) = 0$$


(3)

$$\textcircled{2} \ \& \ \textcircled{4} \quad 5(v_2 - v_1) + 2(v_3 - v_4) + 2(v_3 - v_4) = 0$$

$$\text{KVL: } \begin{cases} v_2 - v_4 = i_1 \\ v_2 - i_1 = v_4 \end{cases} \Rightarrow v_2 - v_4 = 2v_3 \quad (4)$$

Mesh Analysis-Introduction


What is a Mesh?

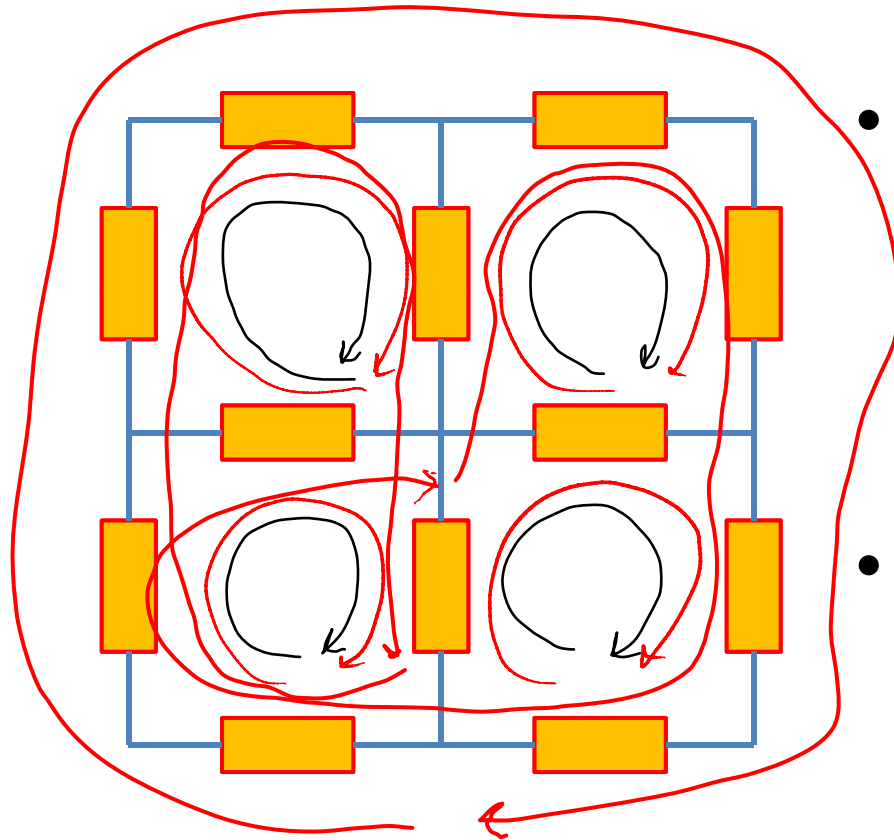

- A loop is a closed path with no node passed more than once.
- A mesh is a loop that does not contain any other loops within it.

Mesh Analysis-Introduction

Mesh Current vs. Element Current

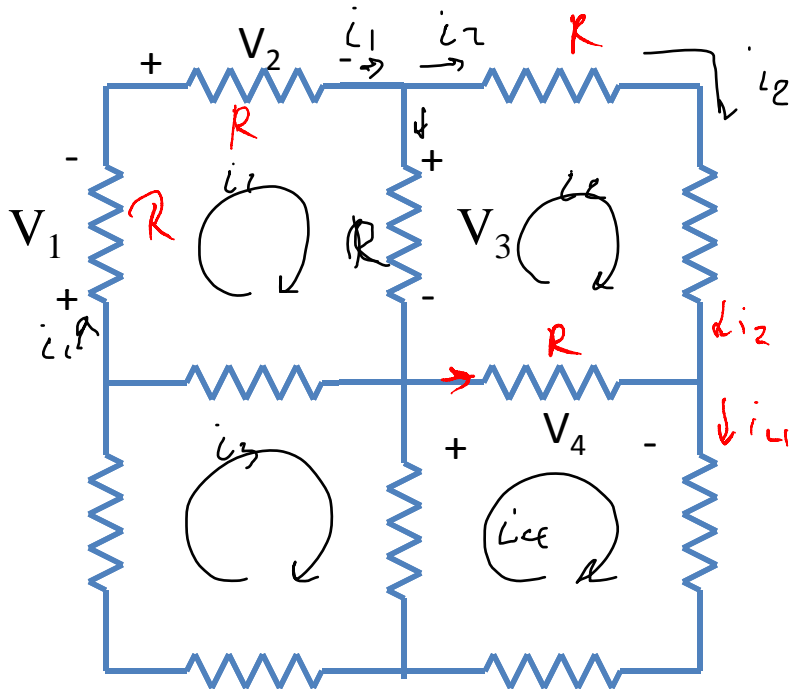

- The current through a mesh is known as mesh current.
- Direction of the mesh current is arbitrary-conventionally assumed to be clockwise.
- The current through an element can be the same as mesh current or the subtraction of two mesh currents.


$$V_3 = R \times (i_1 - i_2)$$

$$V_1 = i_1 \times R$$

$$V_4 = R \times (i_4 - i_2)$$

Mesh Analysis-Method

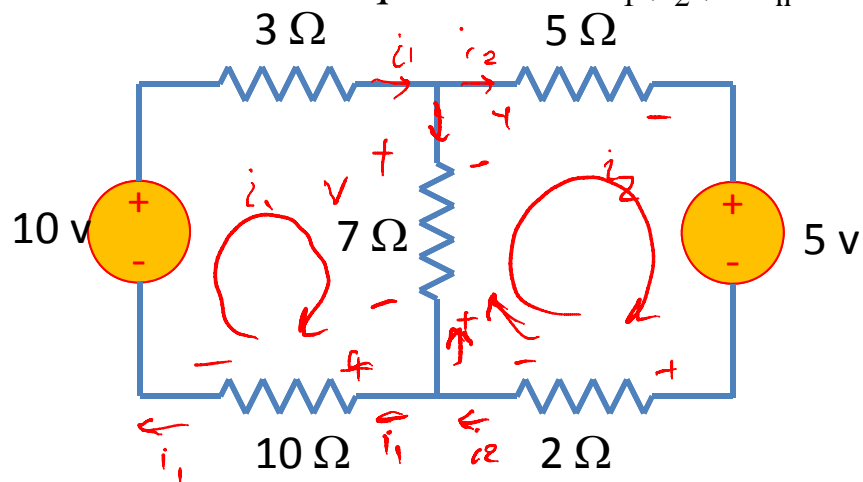- Assign mesh currents i_1, i_2, \dots, i_n
- Apply KVL+ Ohm's law to each mesh
- Solve the equations for i_1, i_2, \dots, i_n



13 vL
Mesh 1:

$$-10 + 3i_1 + 7(i_1 - i_2) + 10i_1 = 0$$


$$20i_1 - 7i_2 = 10 \quad (1)$$

Mesh 2:

$$7(i_2 - i_1) + 5i_2 + 5 + 2i_2 = 0$$

$$-7i_1 + 14i_2 = -5 \quad (2)$$

Apply KVL+ Ohm's Law to Each Mesh

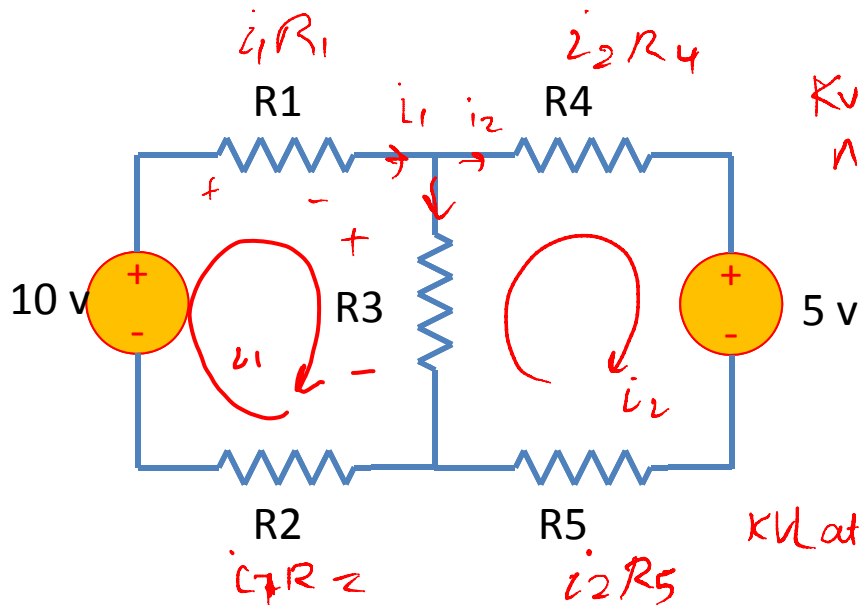


KVL $\sum V = R i_n$ (R only in mesh n)
n

$$V = R_3 (i_1 - i_2)$$

n $V = R (i_n - i_k)$ (R between mesh n & k)
n, k

KVL at k $V = R (i_k - i_n)$
n, k

Mesh Analysis - Example

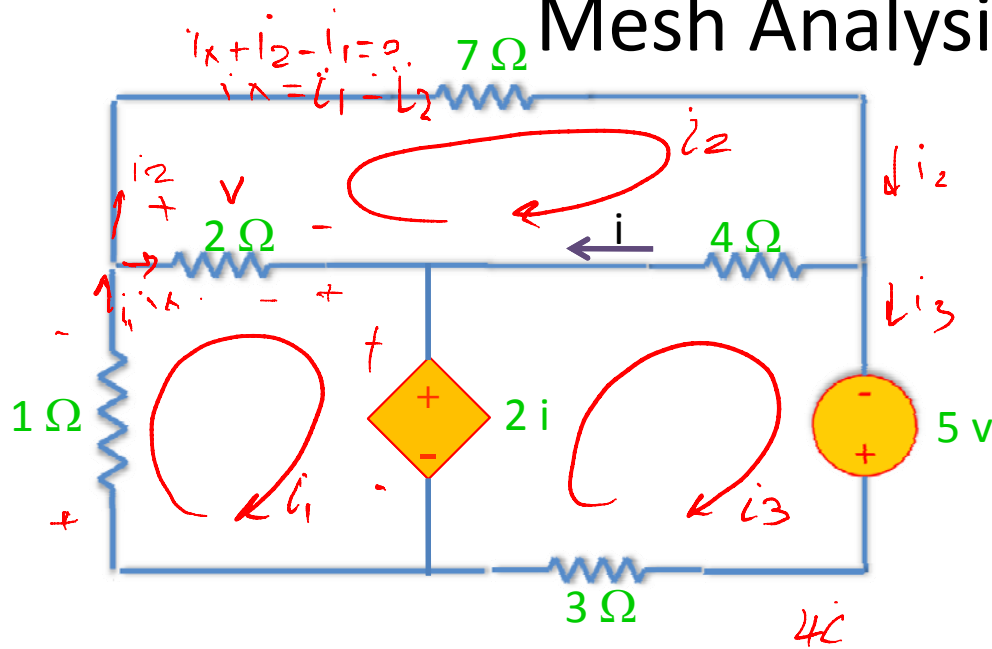

M1:

$$1 \times i_1 + 2(i_1 - i_2) + 2i = 0$$

\downarrow
 $(i_2 - i_3)$

$$i = i_2 - i_3$$

$$i_1(1 + 2) + i_2(-2 + 2) - 2i_3 = 0$$

$$3i_1 - 2i_3 = 0 \quad (1)$$

$$M_2: \quad 2(i_2 - i_1) + 7i_2 + 4(i_2 - i_3) = 0$$

$$-2i_1 + 13i_2 - 4i_3 = 0 \quad (2)$$

$$M_3: \quad -2(i_2 - i_3) + 4(i_3 - i_2) - 5 + 3i_3 = 0$$


$$-6i_2 + 9i_3 = 5 \quad (3)$$

Mesh Analysis with Current Sources

- CASE 1: current source only in one mesh.

already have the current for that mesh => no need to write

KVL for that mesh

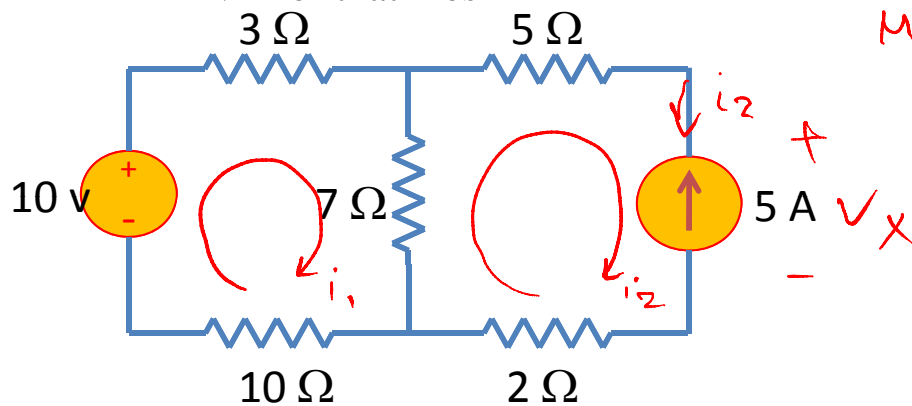

$$M_2: 7(i_2 - i_1) + 5i_2 + v_x + 2(i_2) = 0$$

$$i_2 = -5A$$

$$M_1: -10 + 3i_1 + 7(i_1 - i_2) + 10i_1 = 0$$

$$20i_1 - 7i_2 = 10$$

$$\downarrow$$

$$-5$$


$$20i_1 + 35 = 10$$

$$i_1 = \frac{-25}{20} = -1.25 A$$

Mesh Analysis with Current Sources

- CASE 2: current source exits between two meshes. => create a supermesh

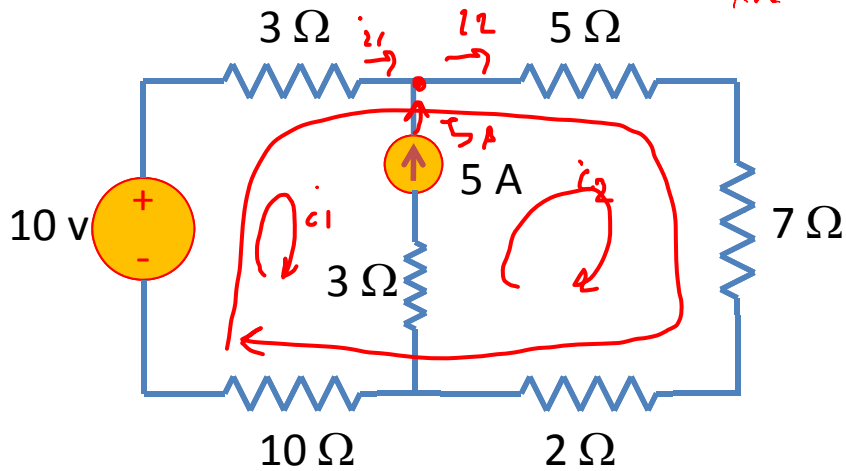- Apply KVL to the supermesh
- Apply KCL to the supermesh




KVL: $-10 + 3i_1 + 5i_2 + 7i_2 + 2i_2 + 10i_1 = 0$
 $13i_1 + 14i_2 = 10 \quad (1)$

KCL: $i_1 - 5A = i_2$
 $i_1 - i_2 = 5 \quad (2)$

$$\begin{cases} 13i_1 + 14i_2 = 10 \\ i_1 - i_2 = 5 \end{cases} \rightarrow i_1 \text{ \& } i_2$$

Mesh Analysis- Example

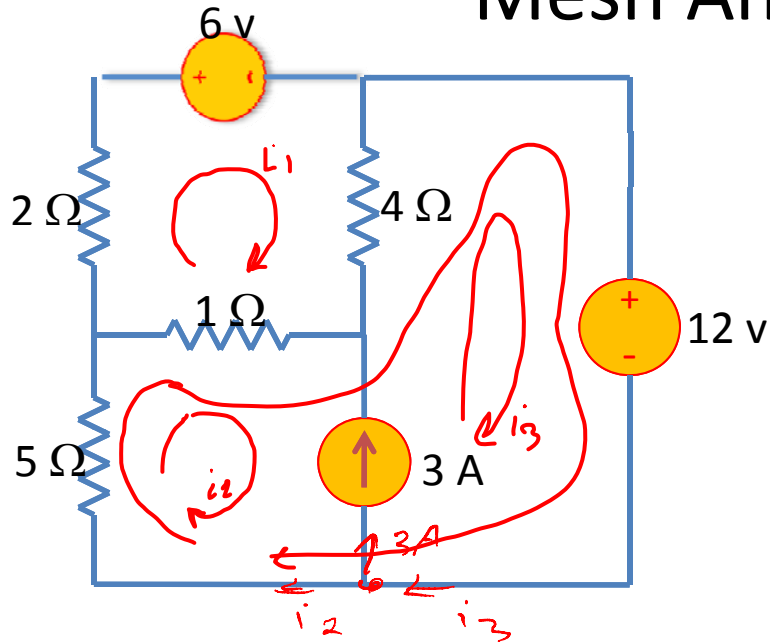

Mesh 1 :


$$2i_1 + 6 + 4(i_1 - i_3) + 1(i_1 - i_2) = 0 \quad (1)$$

(1) & (2) :

$$5i_2 + 1 \times (i_2 - 4) + 4(i_3 - i_1) + 12 = 0 \quad (2)$$




$$\text{KCL} \Rightarrow i_3 = 3 + i_2 \quad (3)$$

Mesh Analysis- Example



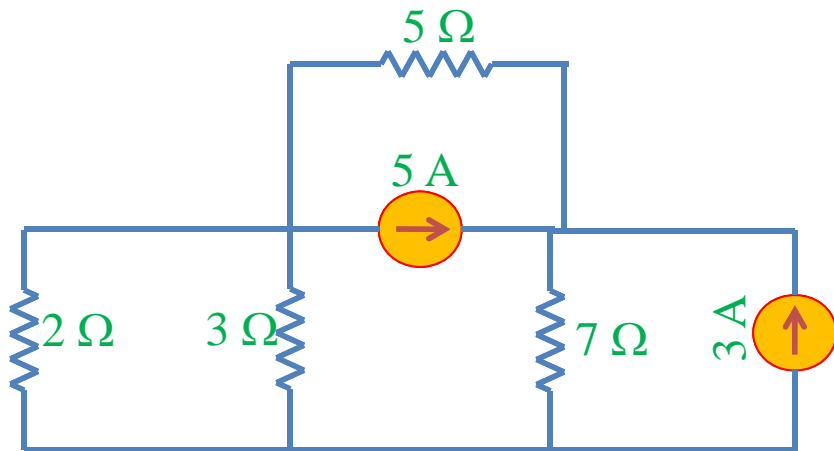


Nodal Versus Mesh Analysis

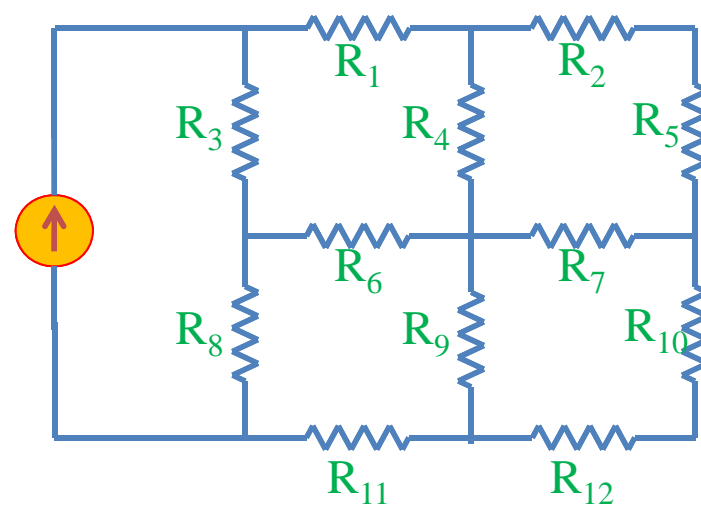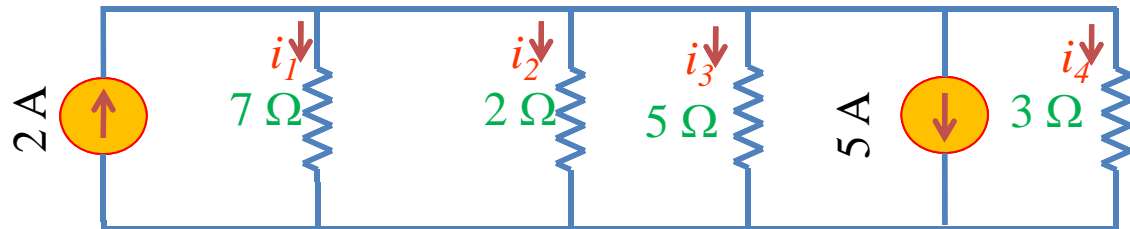
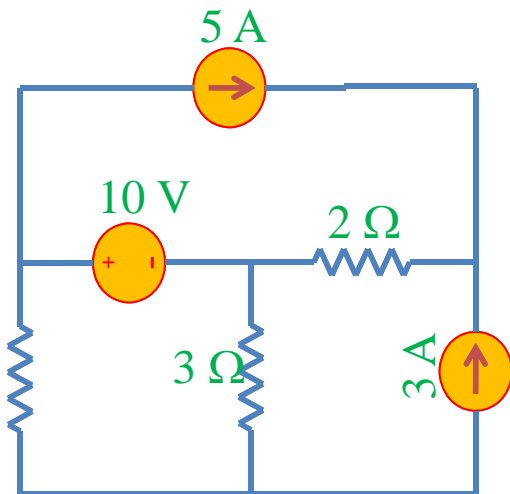
- The method that results in fewer number of equations is more suitable.
 - Mesh analysis for networks with many series connected elements
 - Nodal Analysis for networks with many parallel connected elements
- But also depends on the type of the sources.



Symbol library

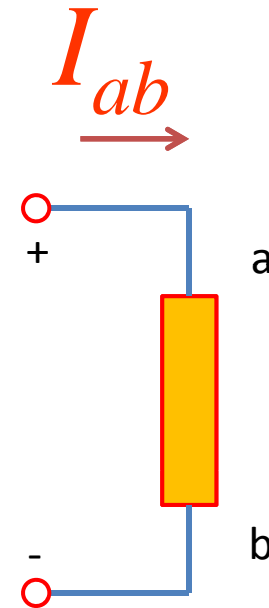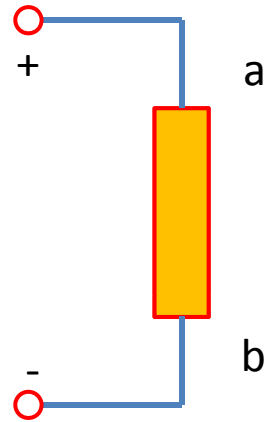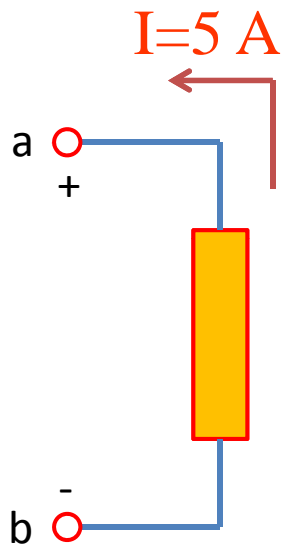

Symbol library

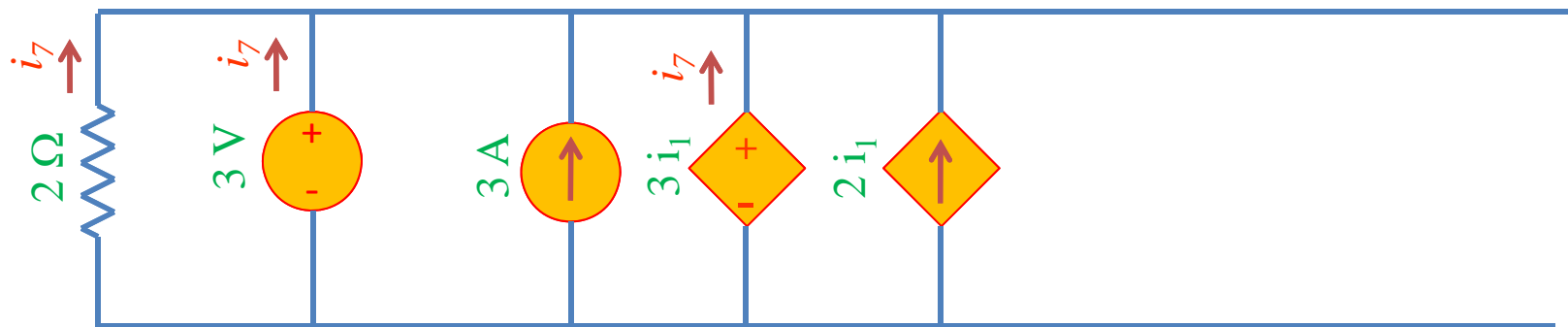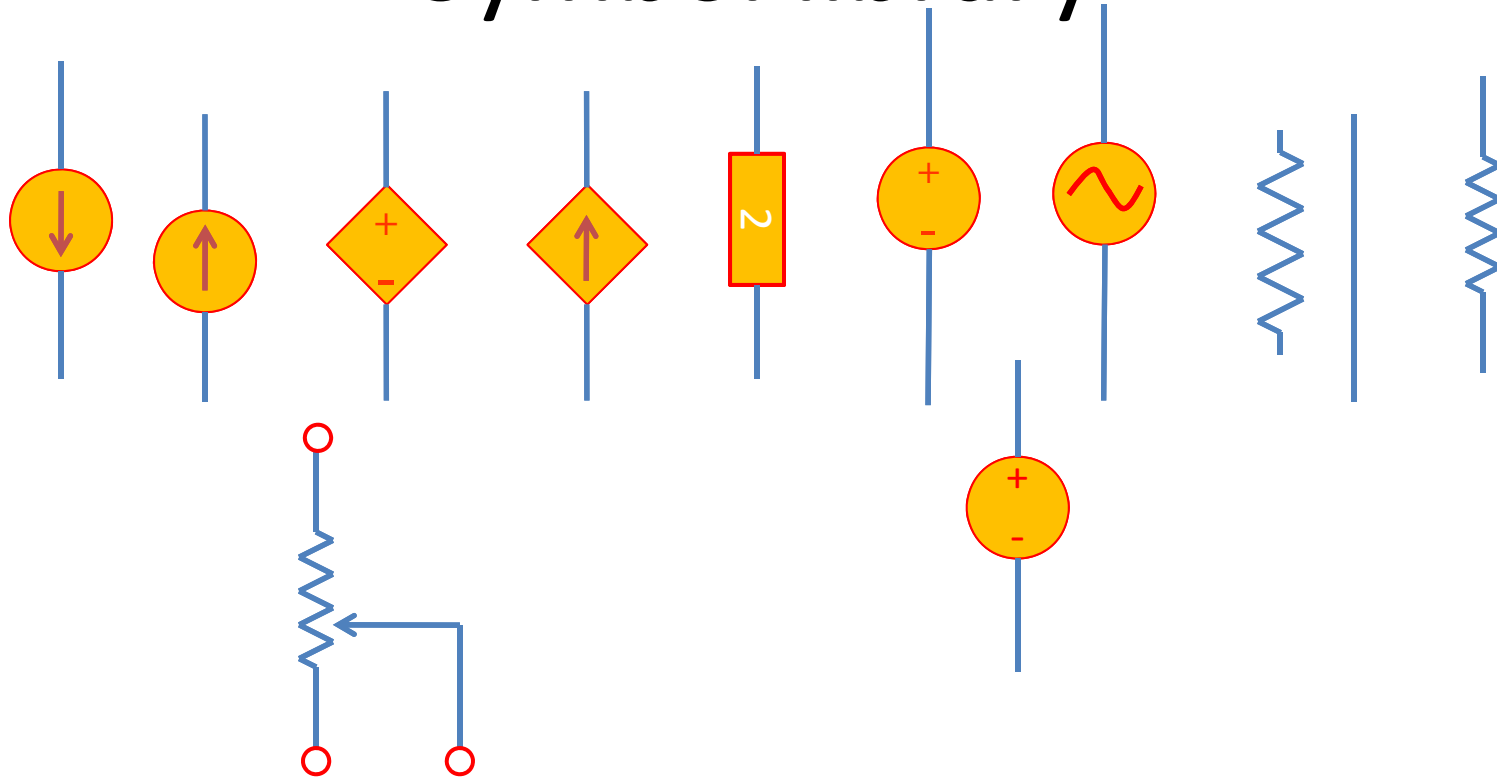

Symbol & circuit library

