

Announcements:

1. Next quiz will be due on Monday next week
2. Next HW will be due on Wednesday next week
3. Graded midterms are being scanned today;
available for pickup Wednesday from TAs

EECS 70A: Network Analysis

Lecture 7


Today's Agenda

- TLTC Midterm Student Feedback Survey
- Midterm 1 results
- Review of Nodal Analysis
- Review of Mesh Analysis
- Example problems using both techniques
- Thevinin/Norton theorem

TLTC Midterm Feedback Survey

- The good:
 - Recorded lectures
 - online notes/tablet pc
- To improve:
 - Need more complex examples in class
- To drop:
 - Demos

Midterm results

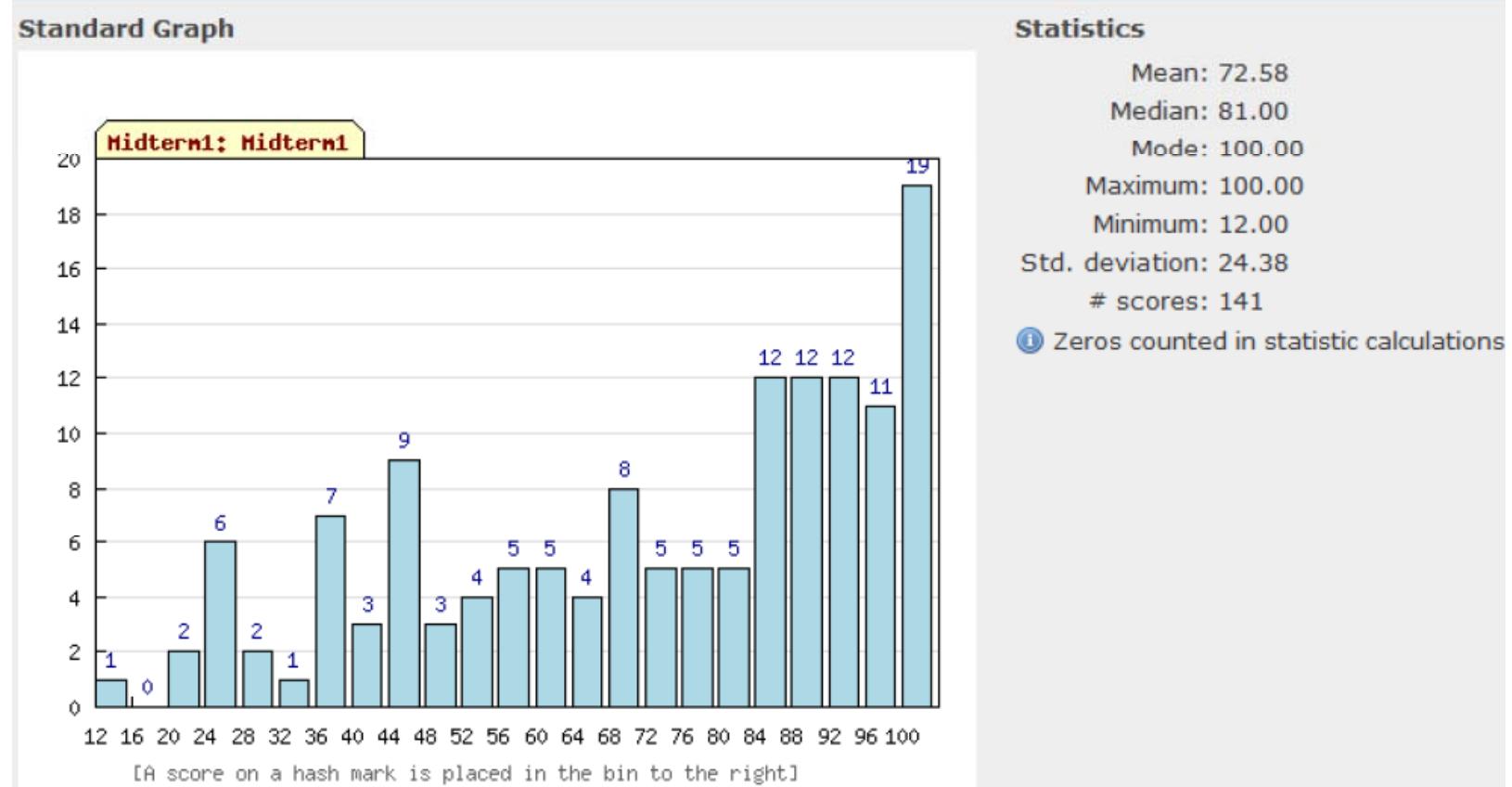

Detailed solutions posted online. Please make sure you understand them!


Nodal analysis summary

1. Define reference node
2. Label remaining nodes (e.g. V_1, V_2, V_3, \dots)
3. Apply KCL + Ohm's law
4. Solve for nodal voltages (e.g. using Kramer's rule)
5. Solve for currents

Nodal analysis example

$$G_1 = \frac{1}{R_1}, \quad G_2 = \frac{1}{R_2} \text{ etc}$$

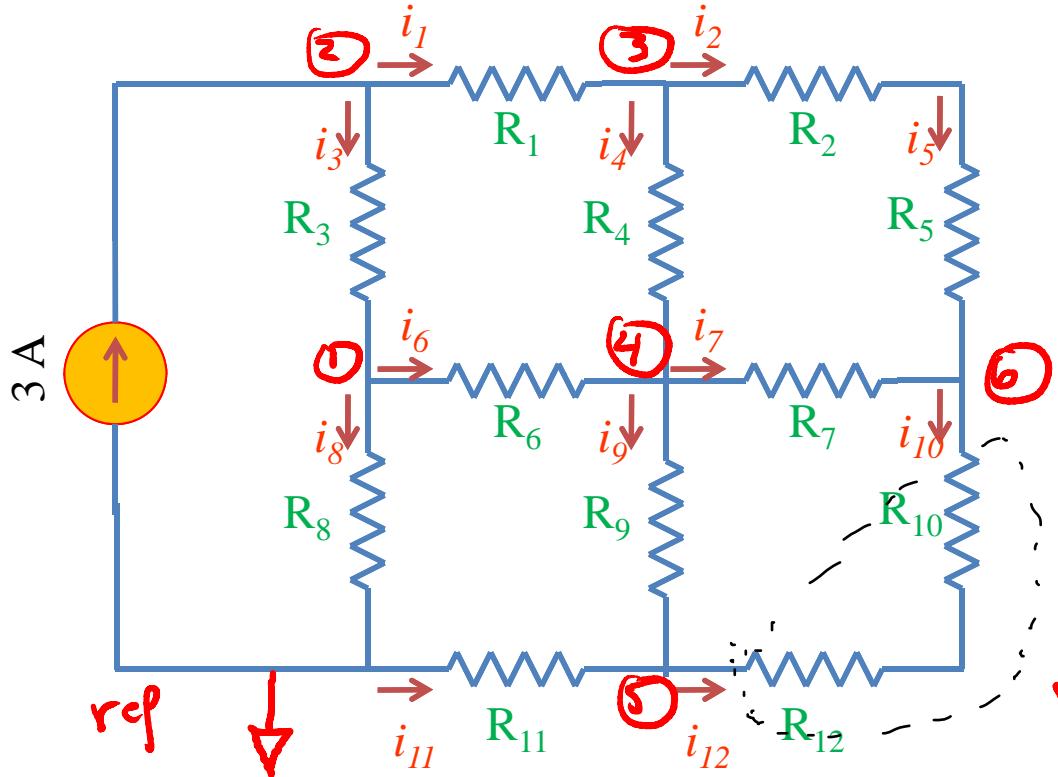1. Define a reference node.
2. Label remaining nodes.
3. Apply KCL + ohm.



Typical notation:

i_1 is current through R_1 . (Same as before)

V_1 is voltage of node 1 relative to reference node. (Different from before)

We will do this entire problem in class...

Using these techniques, you can attempt the "monster problem" as extra credit on HW3...

6 variables

$$V_1, V_2, V_3, V_4, V_5, V_6$$

Need 6 eqns.

$$i_{11} + i_9 = i_{12}$$

$$\frac{0 - V_S}{R_{11}} + \frac{V_4 - V_S}{R_9} = \frac{V_S - V_6}{R_{12} + R_{10}}$$

$$① i_3 = i_6 + i_7$$

$$i_8 + i_6 - i_3 = 0$$

$$\frac{V_1 - 0}{R_8 + R_6} + \frac{V_1 - V_4}{R_6} - \frac{V_2 - V_1}{R_3} = 0$$

$$② V_1 \left(\frac{1}{R_8} + \frac{1}{R_3} \right) + V_4 \left(-\frac{1}{R_6} \right) + V_2 \left(-\frac{1}{R_3} \right) = 0$$

$$V_1 (G_8 + G_3) + V_4 (-G_6) + V_2 (-G_3) = 0$$

$$\begin{aligned}
 & V_1 + (-G_2)V_2 + (G_3)V_3 + (-G_6)V_4 + (G_7)V_5 + (-G_8)V_6 = 0 \\
 & V_1 + \cancel{(-G_2)}V_2 + (-G_1)V_3 + (G_4)V_4 + (G_5)V_5 + (-G_6)V_6 = 0 \\
 & (G_6)V_1 + (G_4)V_2 + (G_3)V_3 + (-G_4)V_4 + (G_9)V_5 + (G_7)V_6 = 0 \\
 & (G_6)V_1 + (G_4)V_2 + (G_3)V_3 + (-G_4)V_4 + (G_9)V_5 + (G_7)V_6 = 0 \\
 & V_1 = \frac{|N_1|}{|D|} \quad V_2 = \frac{|N_2|}{|D|}
 \end{aligned}$$

$$V_1 = \frac{|N|}{|D|}$$

$$G_{21} \in \frac{G_2 + G_3}{G_2 G_3}$$

$$G_{12,10} \in \frac{G_{12} + G_{10}}{G_{10} G_{12}}$$

$$|N| = \begin{vmatrix} 0 & -G_2 & 0 & -G_6 & 0 & 0 \\ 0 & G_1 + G_3 & -G_1 & 0 & 0 & 0 \\ 0 & -G_1 & G_1 + G_9 & -G_9 & 0 & -G_5 \\ 0 & 0 & G_4 & -(***) & G_9 & G_7 \\ 0 & 0 & 0 & -G_9 & (***) & G_{10} G_{12} \\ 0 & 0 & G_{23} & G_7 & G_{12,10} & (*) \\ \end{vmatrix}$$

(∴ same)

$$D = \begin{vmatrix} G_0 + G_3 & . & . & . & . & . \\ G_6 & . & . & . & . & . \\ 0 & . & . & . & . & . \\ 0 & . & . & . & . & . \\ 0 & . & . & . & . & . \\ 0 & . & . & . & . & . \\ 0 & . & . & . & . & . \\ \end{vmatrix}$$

$$V_1 = \frac{|N|}{|D|}$$

$$G_{21} \in \frac{G_2 + G_3}{G_2 G_3}$$

$$G_{12,10} \in \frac{G_{12} + G_{10}}{G_{10} G_{12}}$$

$$|N| = \begin{vmatrix} 0 & -G_2 & 0 & -G_6 & 0 & 0 \\ 0 & G_1 + G_3 & -G_1 & 0 & 0 & 0 \\ 0 & -G_1 & G_1 + G_9 & -G_9 & 0 & -G_5 \\ 0 & 0 & G_4 & -(***) & G_9 & G_7 \\ 0 & 0 & 0 & -G_9 & (***) & G_{10} G_{12} \\ 0 & 0 & G_{23} & G_7 & G_{12,10} & (*) \\ \end{vmatrix}$$

(∴ same)

$$D = \begin{vmatrix} G_0 + G_3 & . & . & . & . & . \\ +G_6 & . & . & . & . & . \\ -G_3 & . & . & . & . & . \\ 0 & . & . & . & . & . \\ G_6 & . & . & . & . & . \\ 0 & . & . & . & . & . \\ 0 & . & . & . & . & . \end{vmatrix}$$

$$\left(\begin{array}{|c|c|c|c|c|} \hline & -G_2 & 0 & -G_6 & 0 & 0 \\ \hline 0 & G_1+G_3 & -G_1 & 0 & 0 & 0 \\ \hline 3 & -G_1 & G_1+G_9 & -G_9 & 0 & -G_5 \\ \hline 0 & 0 & G_4 & -(***) & G_9 & G_7 \\ \hline 0 & 0 & 0 & -G_9 & (****) & G_{10}G_{12} \\ \hline 0 & 0 & G_{23} & G_7 & G_{1210} & (*) \\ \hline 0 & 0 & 0 & 0 & 0 & 0 \\ \hline \end{array} \right) =$$

0 | -3 | m₃ | +0 | | φ 0 | | +0 | | -0 | |

$$= -3 \left| \begin{array}{ccccc} -G_2 & 0 & -G_6 & 0 & 0 \\ -G_1 & G_1+G_9 & & & \\ 0 & G_4 & \dots & \dots & \\ 0 & 0 & & & \\ 0 & G_{23} & & & \end{array} \right|$$

Mesh analysis summary


1. Assign mesh currents $i_1, i_2, \dots i_n$
2. Apply KVL to each mesh
3. Solve for mesh currents (e.g. using Kramer's rule)
4. Then solve for voltages

$$i_1 = I_1$$

$$i_2 = I_2$$

Assigning mesh currents

$$I_3 = i_1 - i_2$$

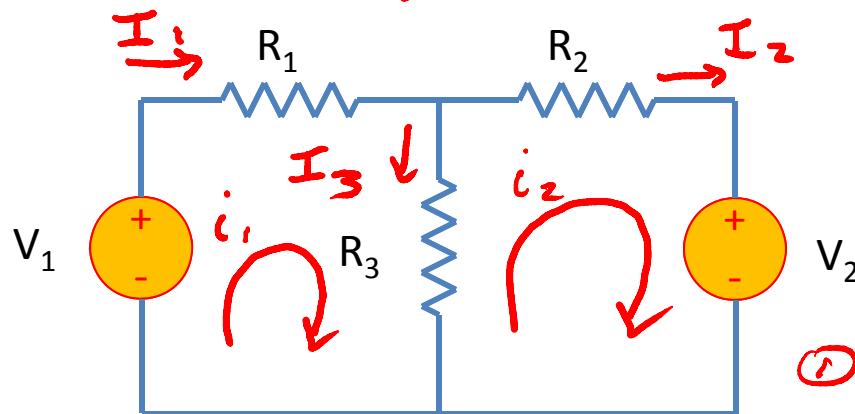

$$\textcircled{1} -V_1 + R_1 i_1 + R_3 (i_1 - i_2) = 0$$

$$\textcircled{2} -R_3 (i_1 - i_2) + R_2 i_2 + V_2 = 0$$

2eqns. 2 unk knowns

$$\textcircled{1} \frac{(R_1 + R_3)i_1 + (-R_3)i_2}{(R_1 + R_3)} = (V_1)$$

$$\textcircled{2} \frac{(-R_3)i_1 + (R_2 + R_3)i_2}{(R_2 + R_3)} = (-V_2)$$

Solve for i_1, i_2 :


$$i_1 = \frac{\begin{vmatrix} V_1 & -R_3 \\ -V_2 & R_2 + R_3 \end{vmatrix}}{\begin{vmatrix} R_1 + R_3 & -R_3 \\ -R_3 & R_2 + R_3 \end{vmatrix}} =$$

$$\frac{V_1(R_2 + R_3) - (-V_2)(-R_3)}{(R_1 + R_3)(R_2 + R_3) - (-R_3)(-R_3)}$$

$$i_2 = \frac{\begin{vmatrix} R_1 + R_3 & V_1 \\ -R_3 & -V_2 \end{vmatrix}}{\begin{vmatrix} R_1 + R_3 & -R_3 \\ -R_3 & R_2 + R_3 \end{vmatrix}} =$$

$$\frac{(R_1 + R_3)(-V_2) - (V_1)(-R_3)}{(R_1 + R_3)(R_2 + R_3) - (-R_3)(-R_3)}$$

Nodal vs. mesh analysis?

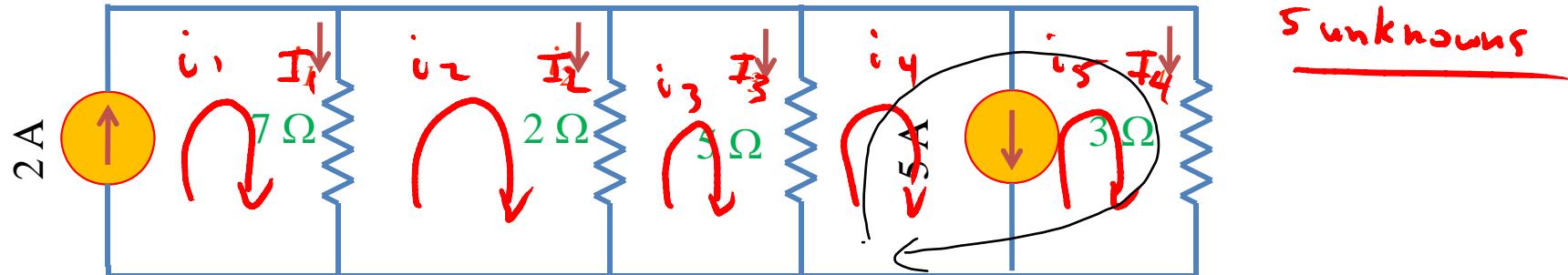

$$\textcircled{5} i_1 = 2A$$

$$\textcircled{1} -7(i_1 - i_2) + 2(i_2 - i_3) = 0$$

$$\textcircled{2} -2(i_2 - i_3) + 5(i_3 - i_4) = 0$$


KVL $\textcircled{3}$ supernode

$$\textcircled{3} -5\Omega(i_3 - i_4) + 3\Omega(i_5) = 0$$


KCL $\textcircled{4}$ Supernode

$$i_4 + 5A = i_5$$

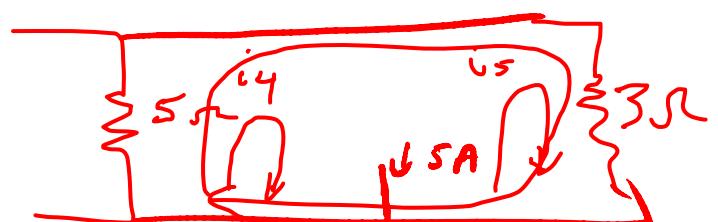5eqns. 5 unknowns i_1, i_2, i_3, i_4, i_5



Nodal analysis example

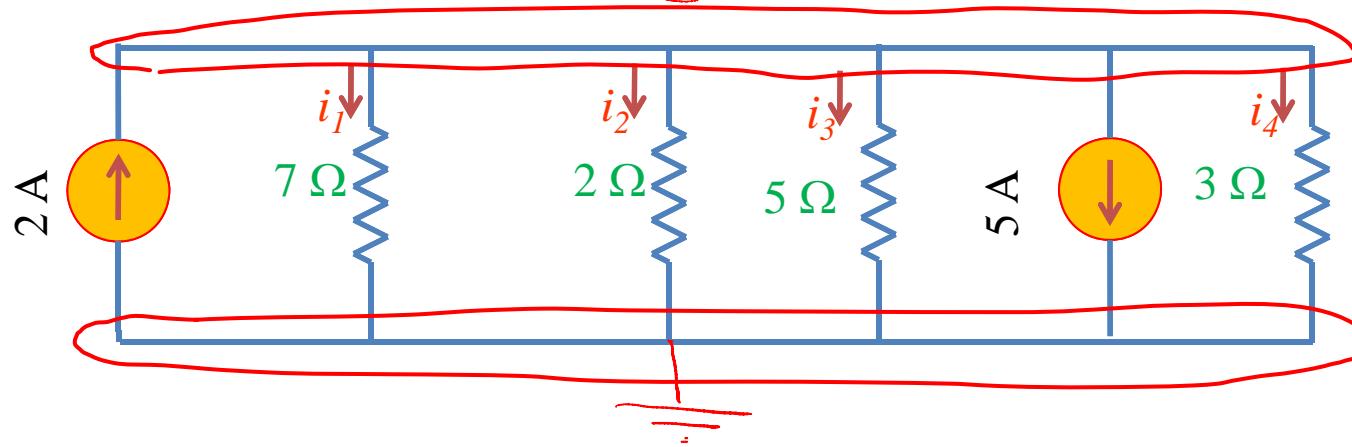


$$KCL : i_1 + i_2 + i_3 + i_4 + 5A - 2A = 0$$

$$\frac{V_1}{7} + \frac{V_1}{2} + \frac{V_1}{5} + \frac{V_1}{3} + 5 - 2 = 0$$

$$V_1 \left(\frac{1}{7} + \frac{1}{2} + \frac{1}{5} + \frac{1}{3} \right) = -3$$

$$V_1 = -2.5V$$

Nodal vs. Mesh Analysis

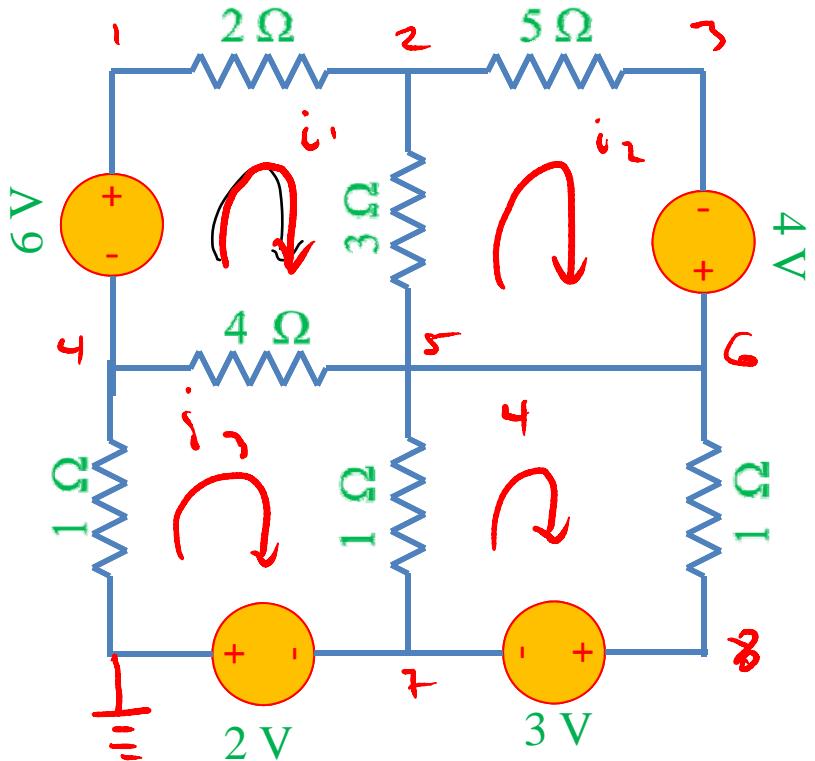


MESH


4 unknowns
4 eqns.


NODAL


$V_1 - V_8$ unknowns
8 eqns.


Nodal vs. Mesh Analysis

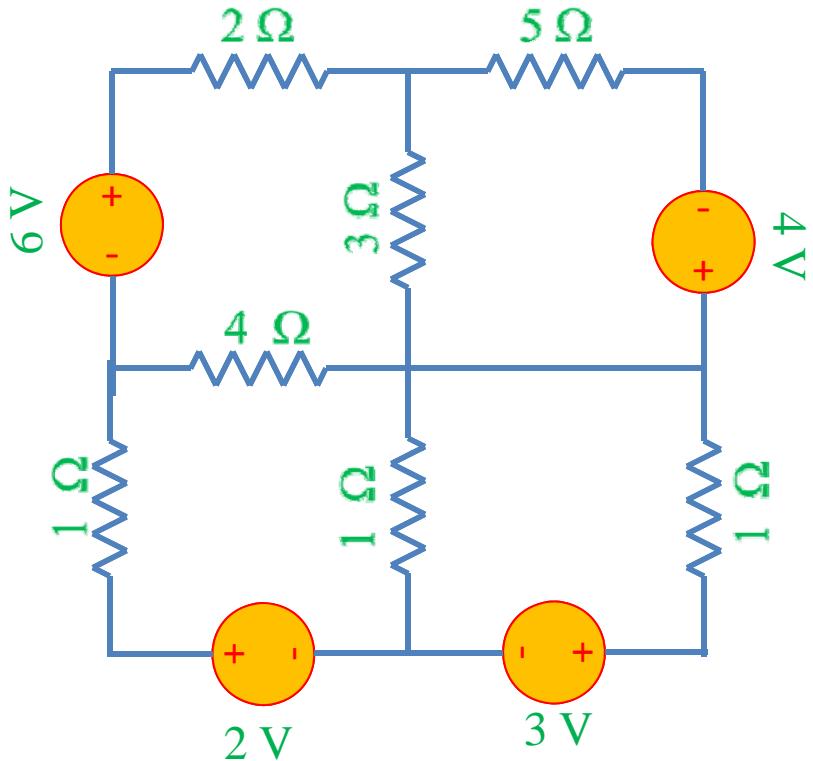


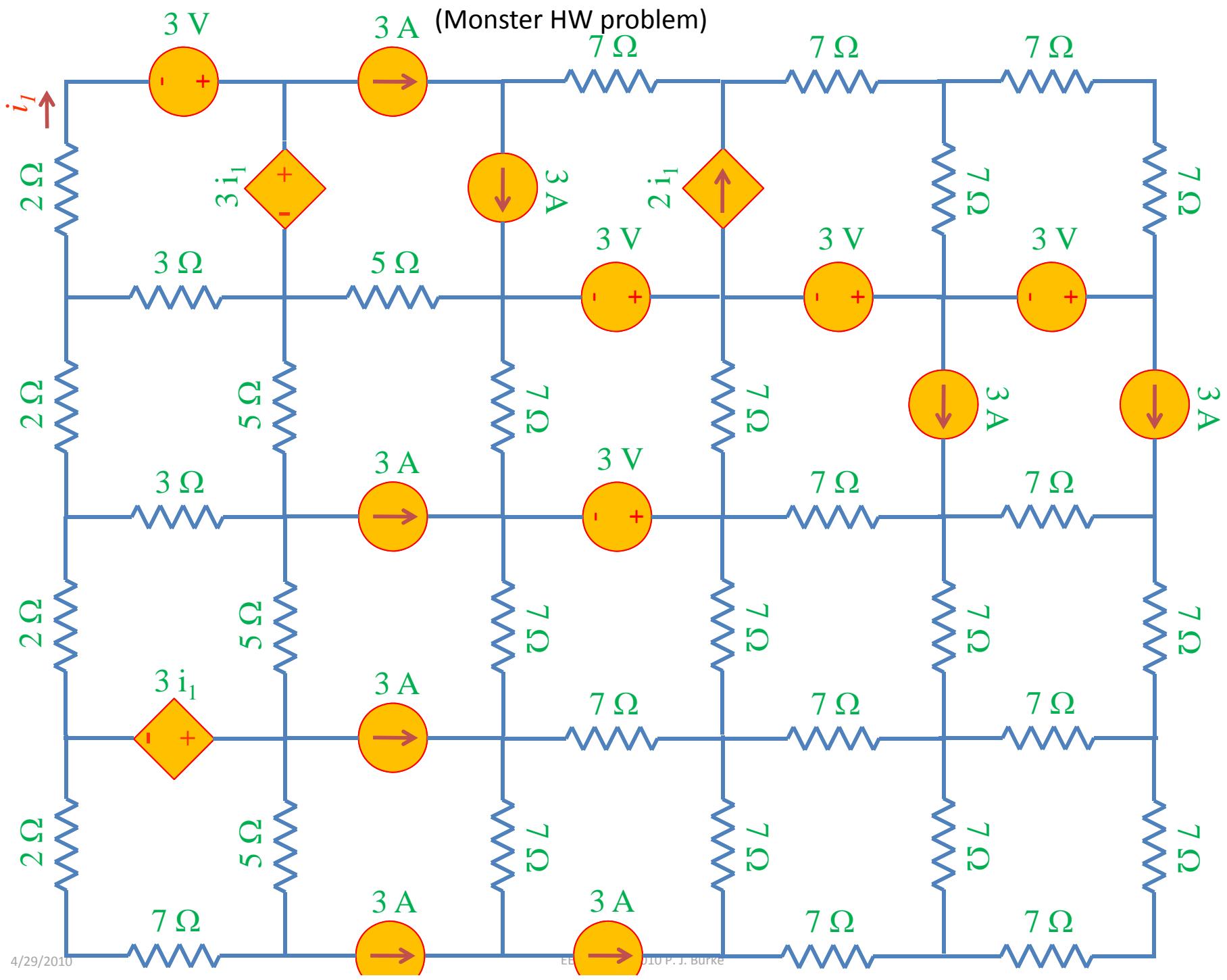


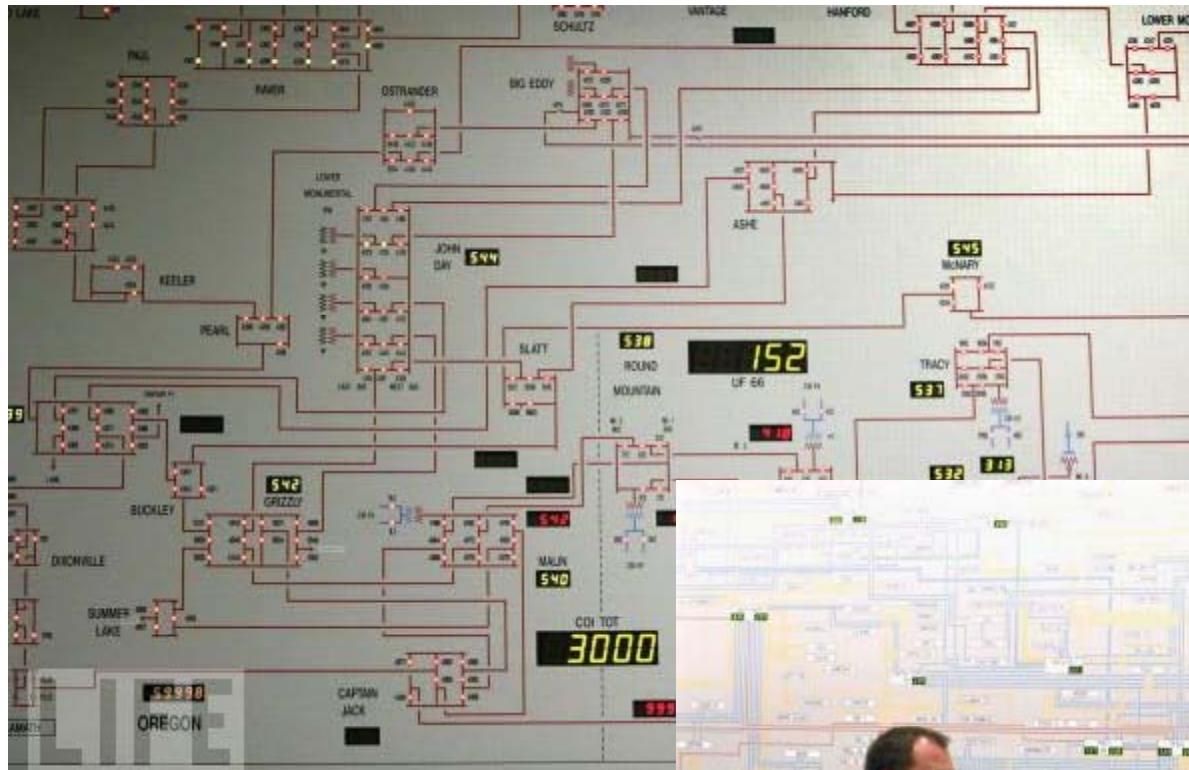

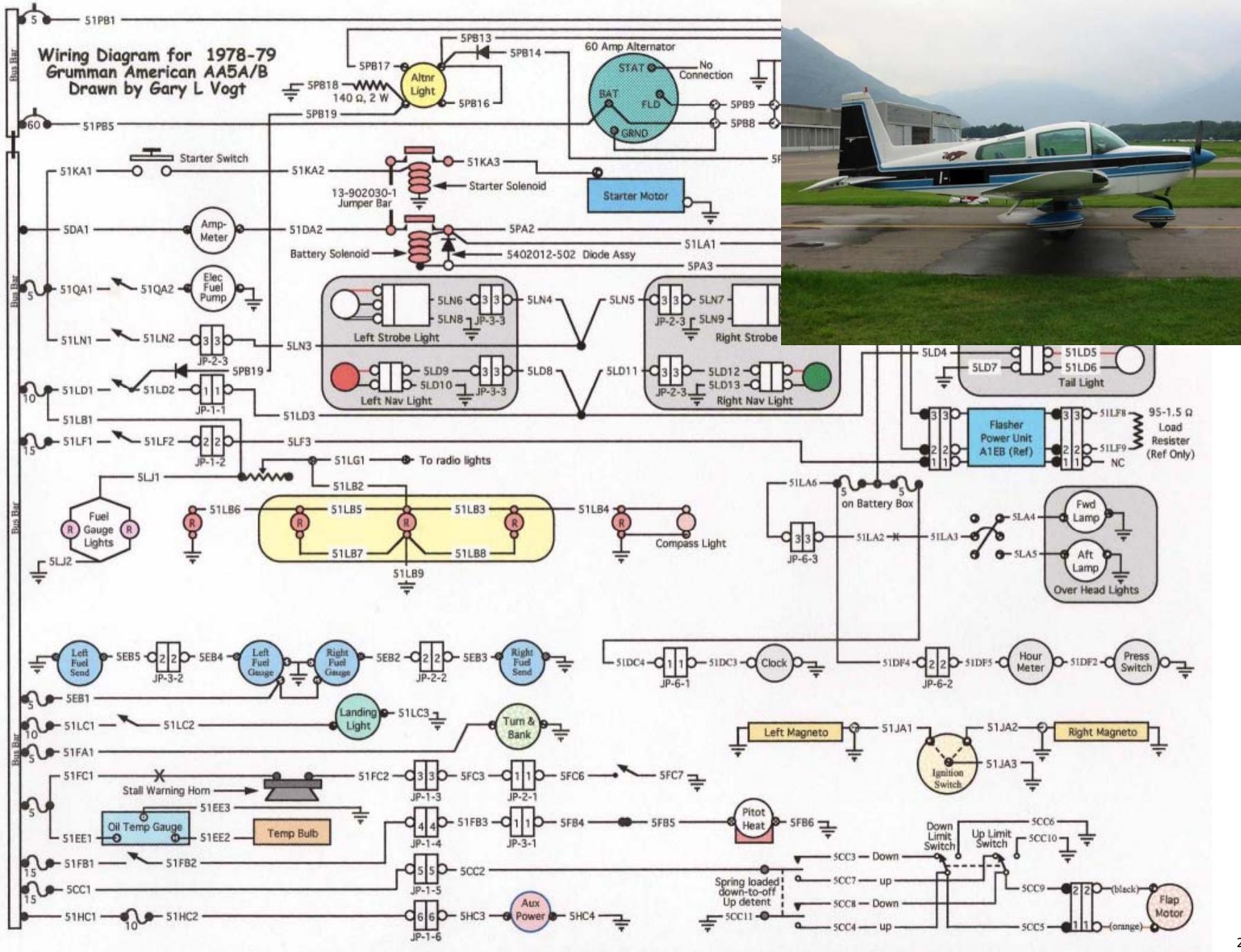


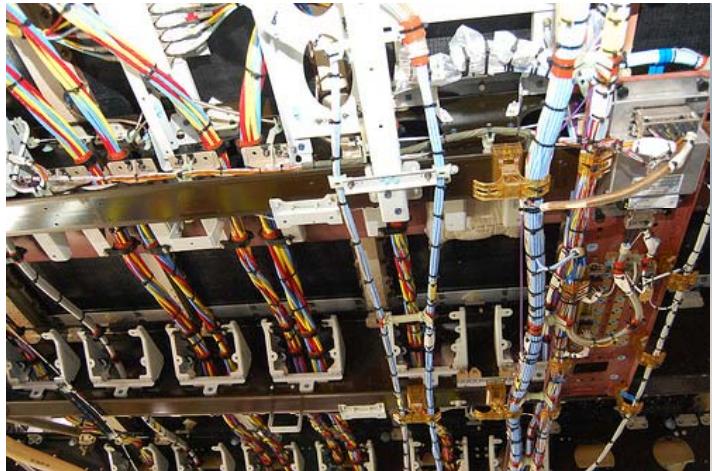

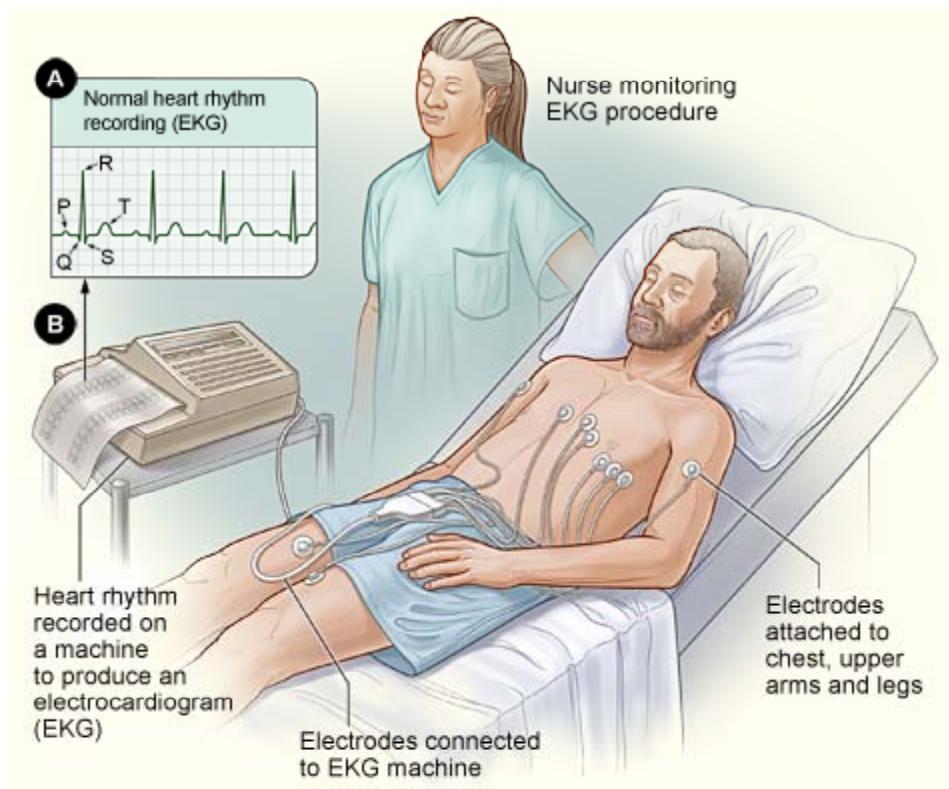

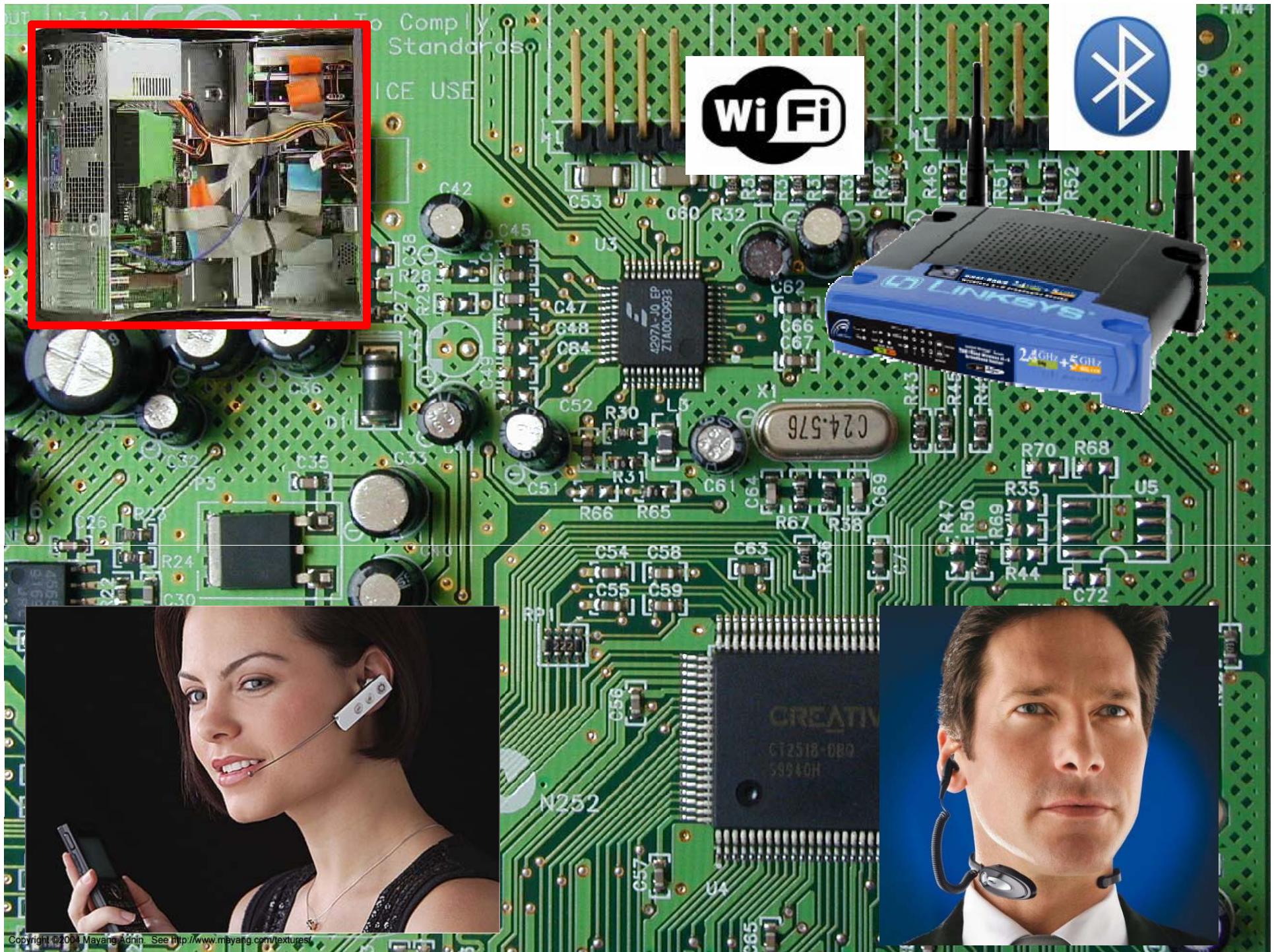


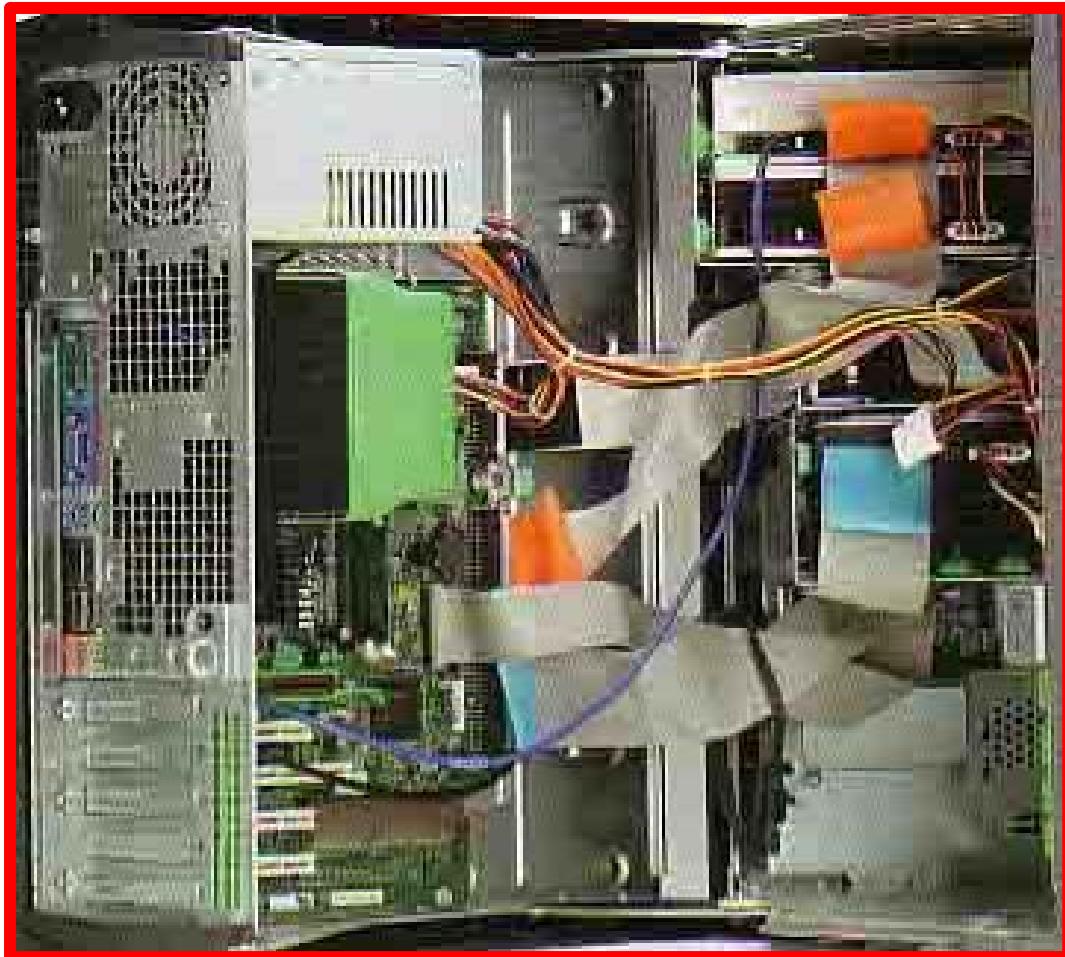Compartmentalization: Need for simplicity




Power brick image.
And ask class to show their own...
Demo: Computer?



Thevenin's Theorem

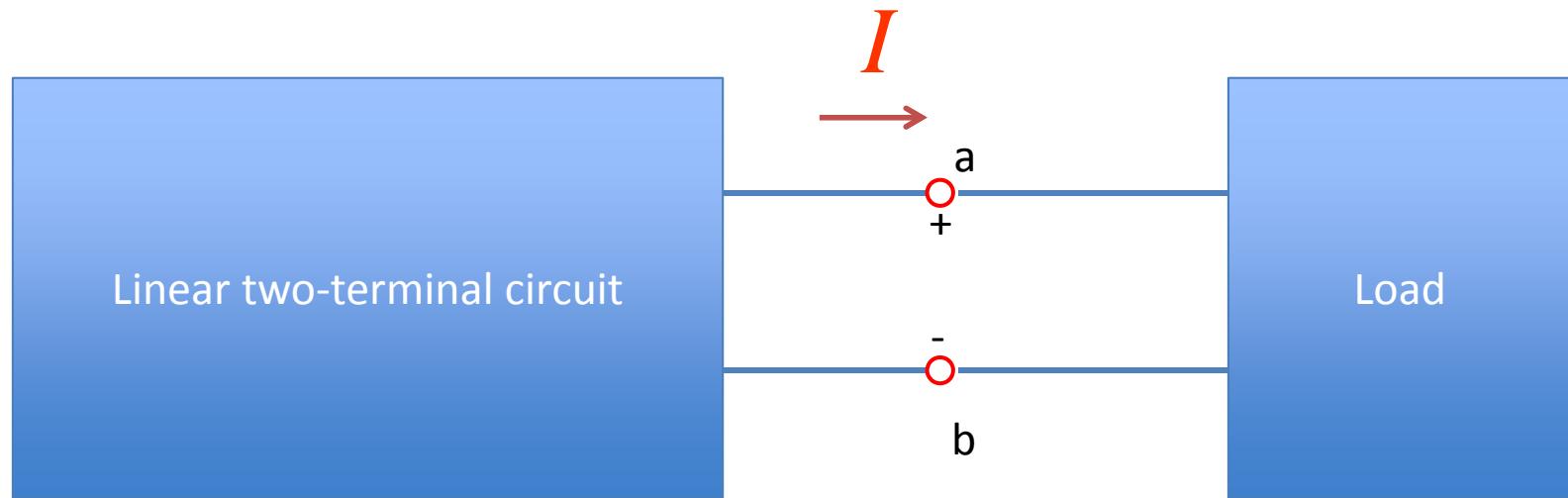

Equivalent to:

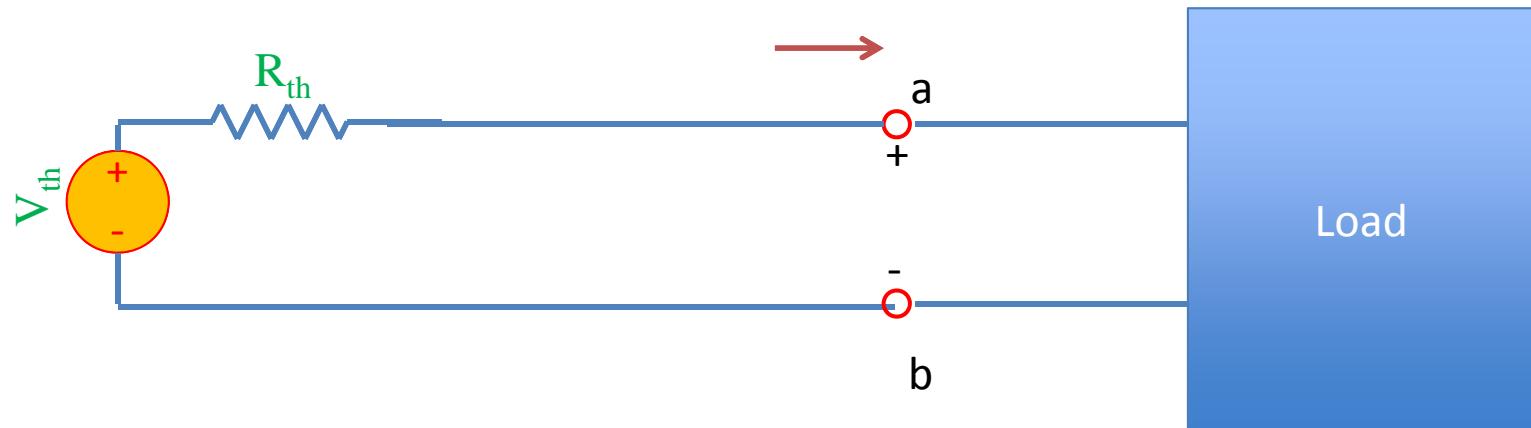

Finding V_{th} , R_{th}

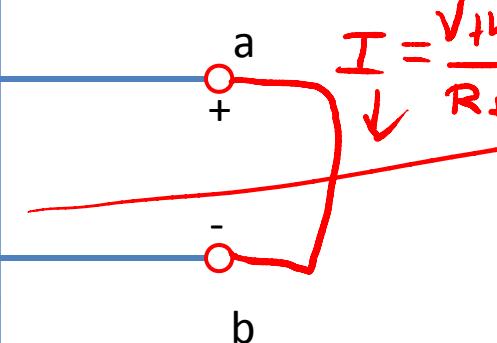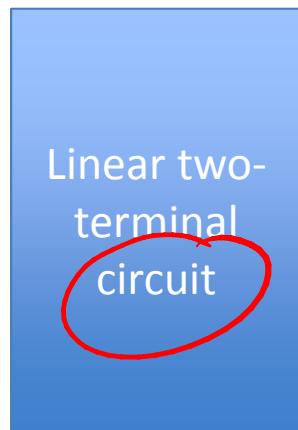

Goal: Find V_{th} , R_{th} :

Given: Circuit


1) Find V_{th} :

Calculate V_{ab} { when no external circuit connected }

Equivalent to:

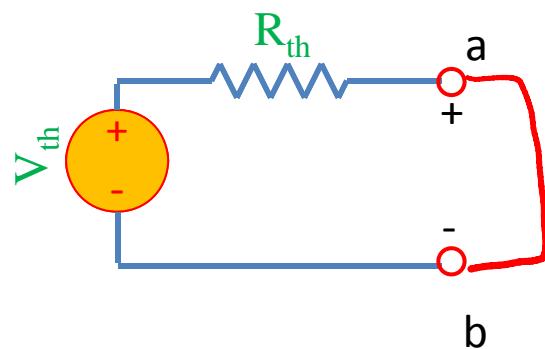2) Find $I_{short\ circuit}$


$$\text{Then } R_{th} = \frac{V_{th}}{I_{short\ circuit}}$$




$$I = \frac{V_{th}}{R_{th}}$$

$$\Leftrightarrow R_{th} = \frac{V_{th}}{I_{short\ circuit}}$$

Source/load

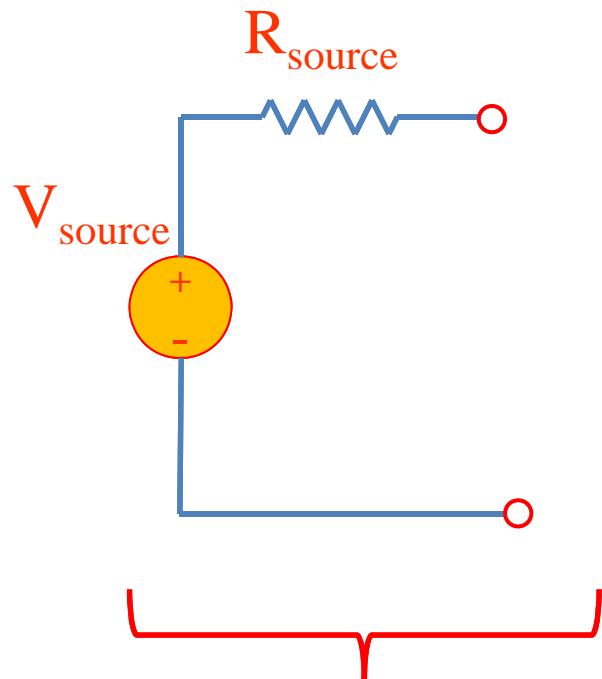

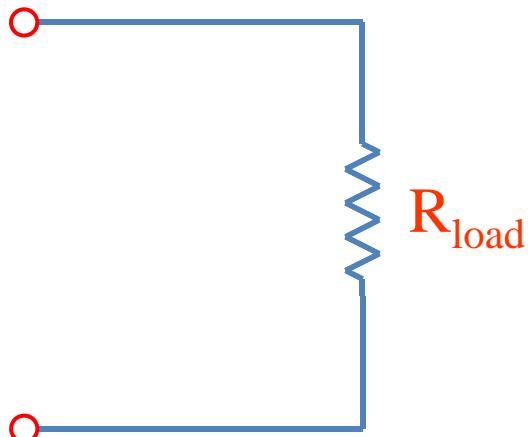Thevenin Thm:
Any circuit can be
represented by this
equivalent circuit.



$$V_{load} = \frac{R_{load}}{R_{load} + R_{source}} V_{source}$$

Derivation:

Case 1:


$$R_{load} \gg R_{source}$$

Case 2:

$$R_{source} \gg R_{load}$$

We say R_{load} “*loads down*” the source.

Source/load

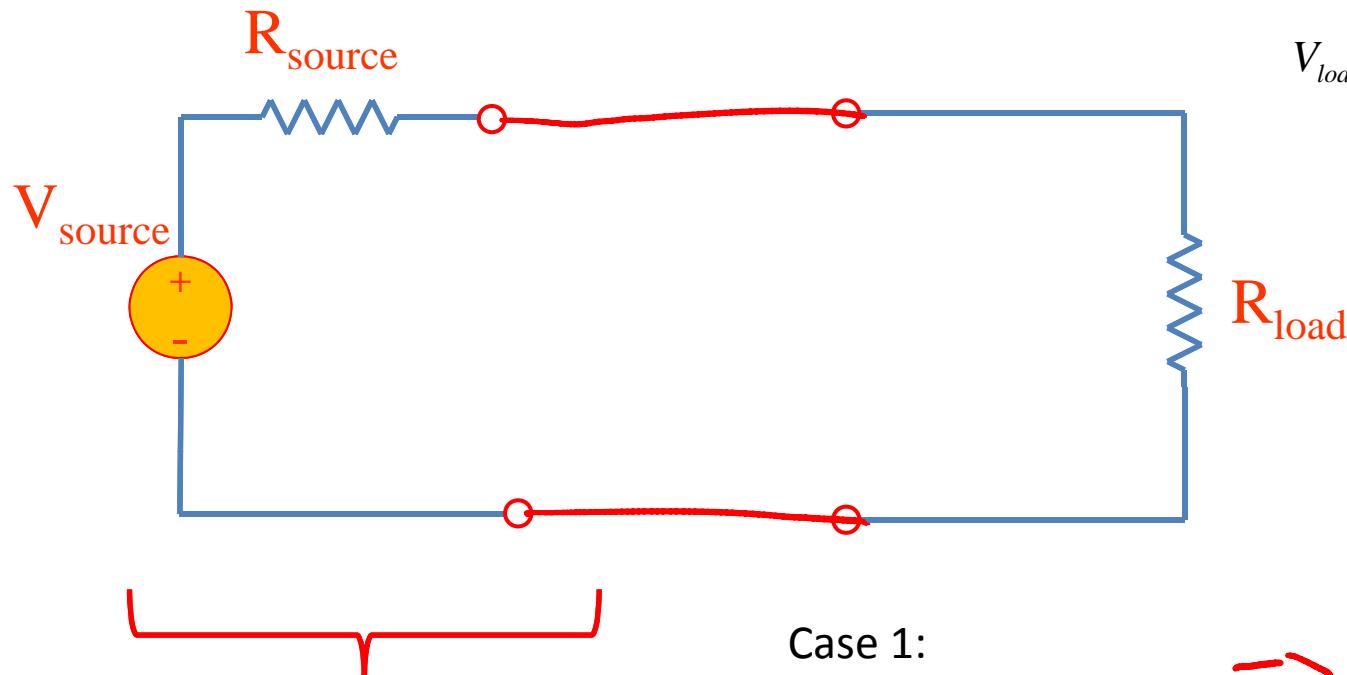

$$V_{load} = \frac{R_{load}}{R_{load} + R_{source}} V_{source}$$

Derivation:

Thevenin Thm:

Any circuit can be represented by this equivalent circuit.

Case 1:
 $R_{load} \gg R_{source}$

$$\Rightarrow V_{load} \approx V_{source}$$

Case 2:

$$R_{source} \gg R_{load}$$


$$V_{load} \rightarrow 0$$

$$\approx \frac{R_{load}}{R_{source}} V_{source}$$


We say R_{load} “loads down” the source.

Example


Find Thevenin equivalent circuit:

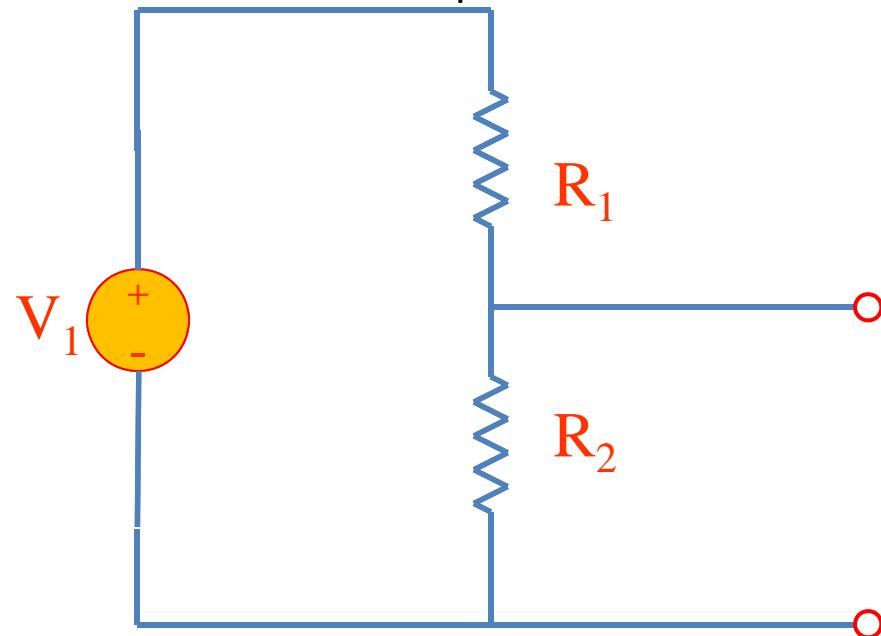


Norton's Theorem

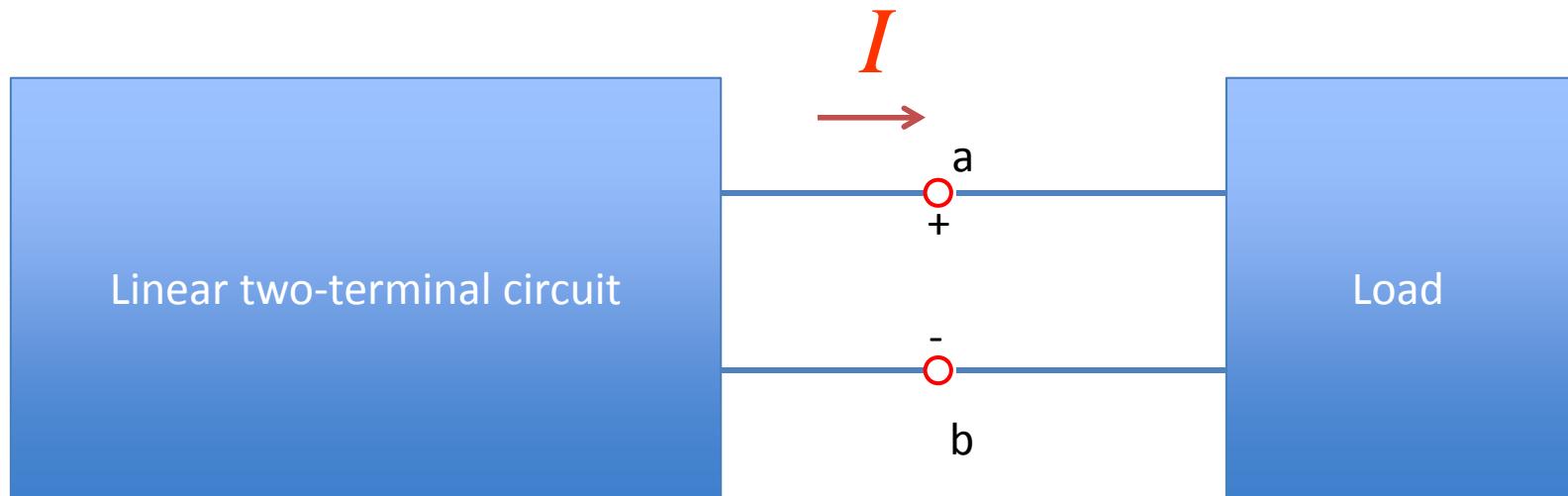


Equivalent to:

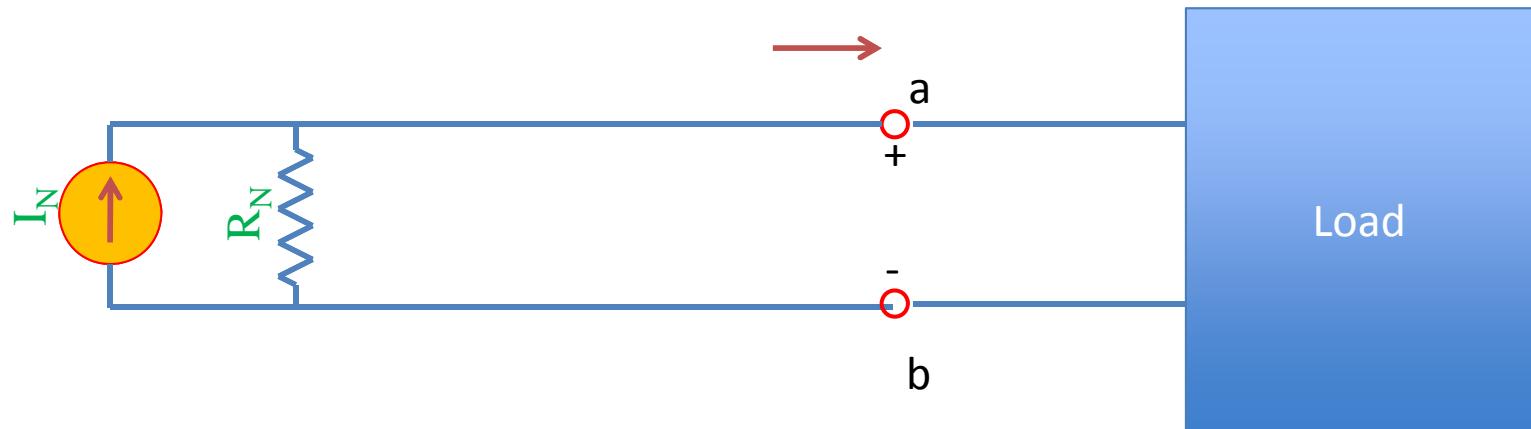


Finding V_{th} , R_{th}

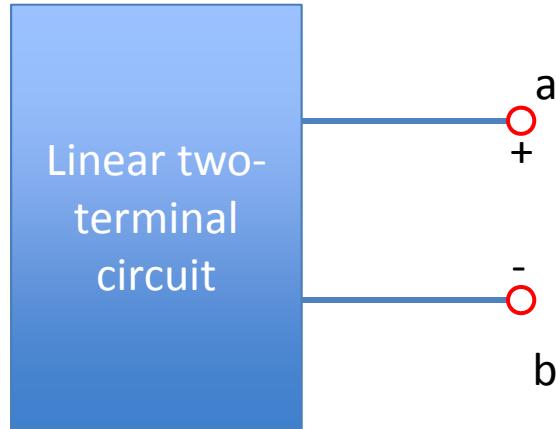

Equivalent to:

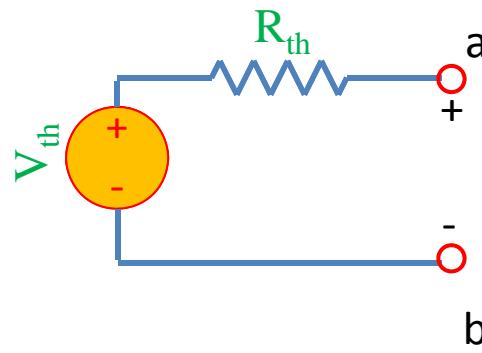


Equivalent to:

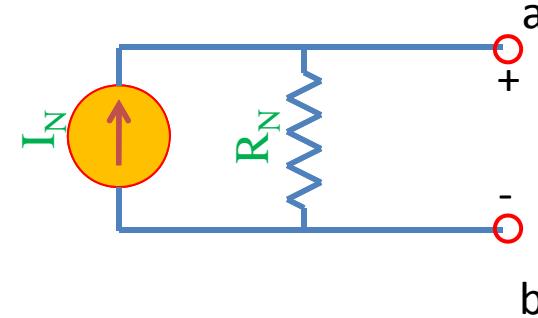


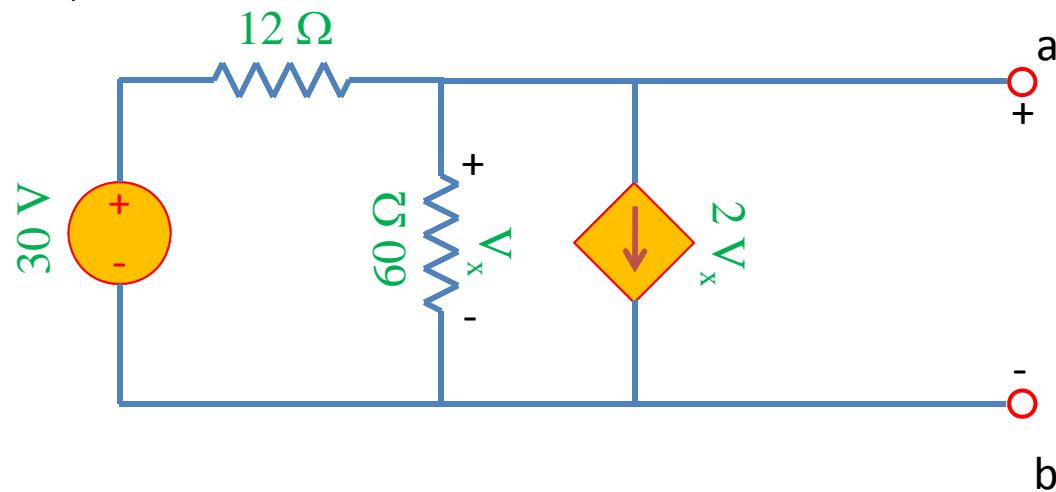Example


Find the Thevenin & Norton equivalent circuit of the circuit below with respect to terminals a and b:



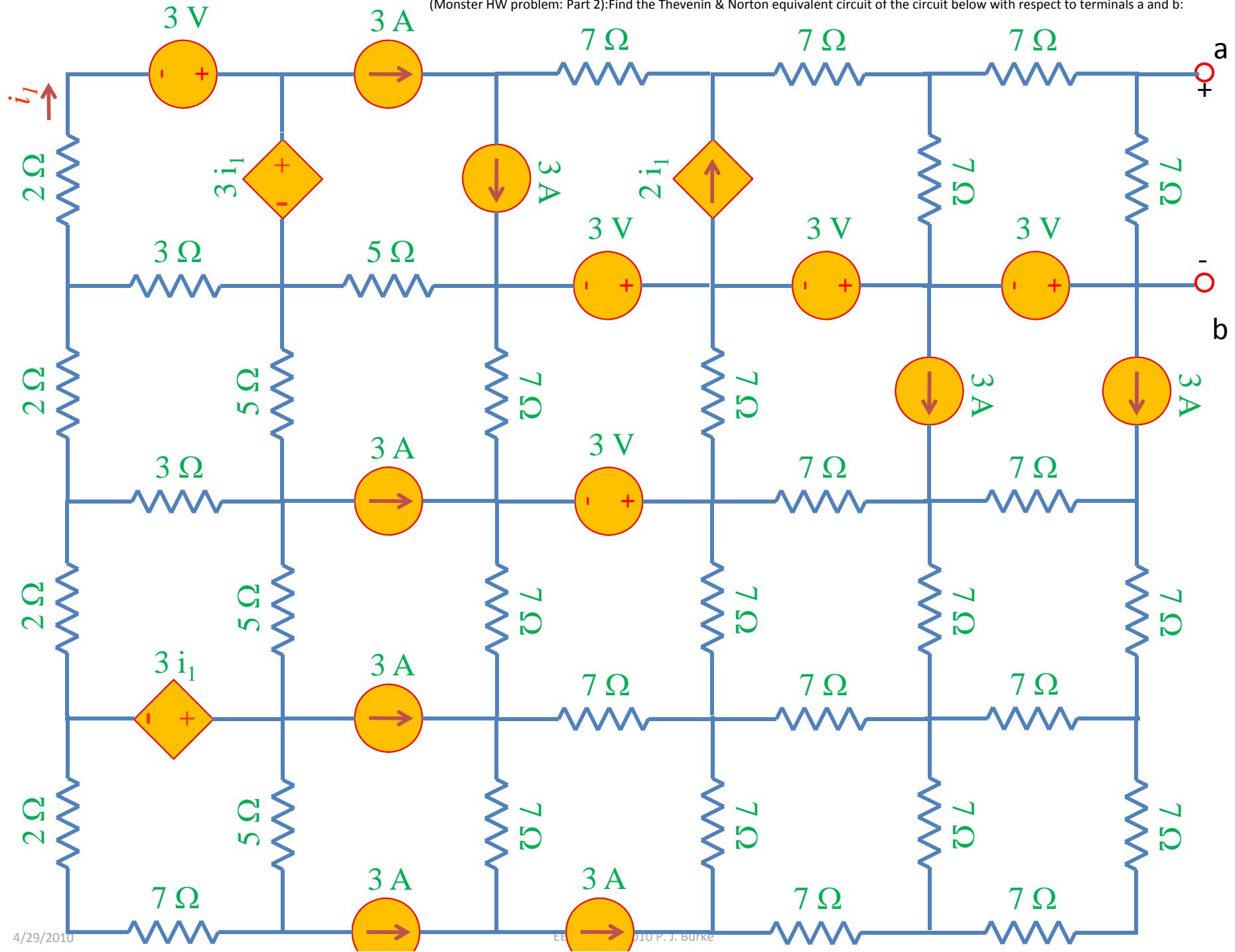(Monster HW problem: Part 2): Find the Thevenin & Norton equivalent circuit of the circuit below with respect to terminals a and b:



Power

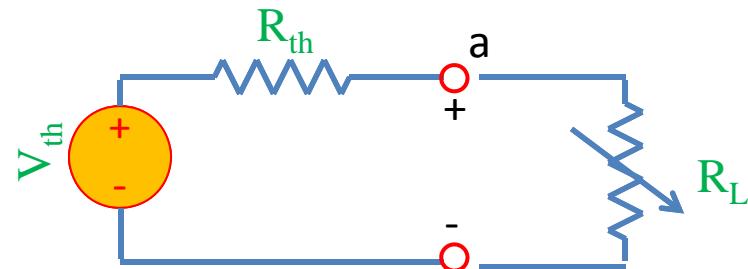

Arrow means R_L variable (e.g. by a knob)

Power delivered to load = ?




Questions?

Ground?




Ground
Reference
Earth

Symbol library

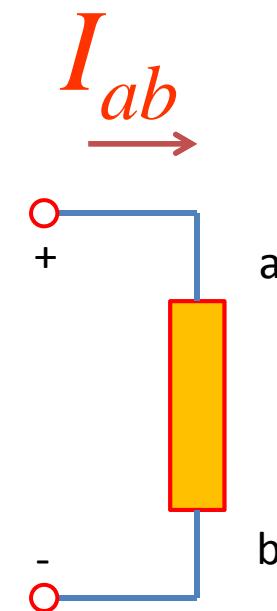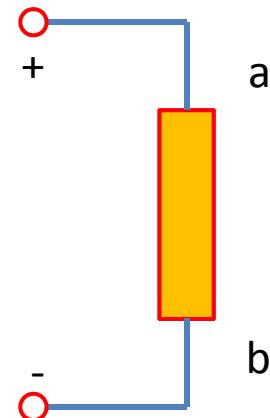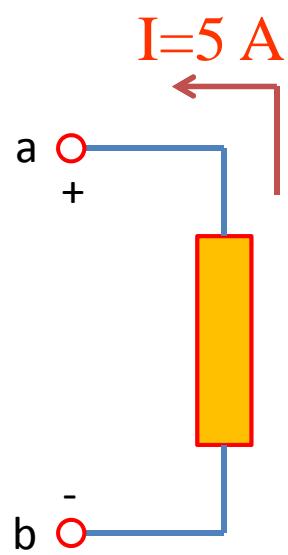

Symbol library

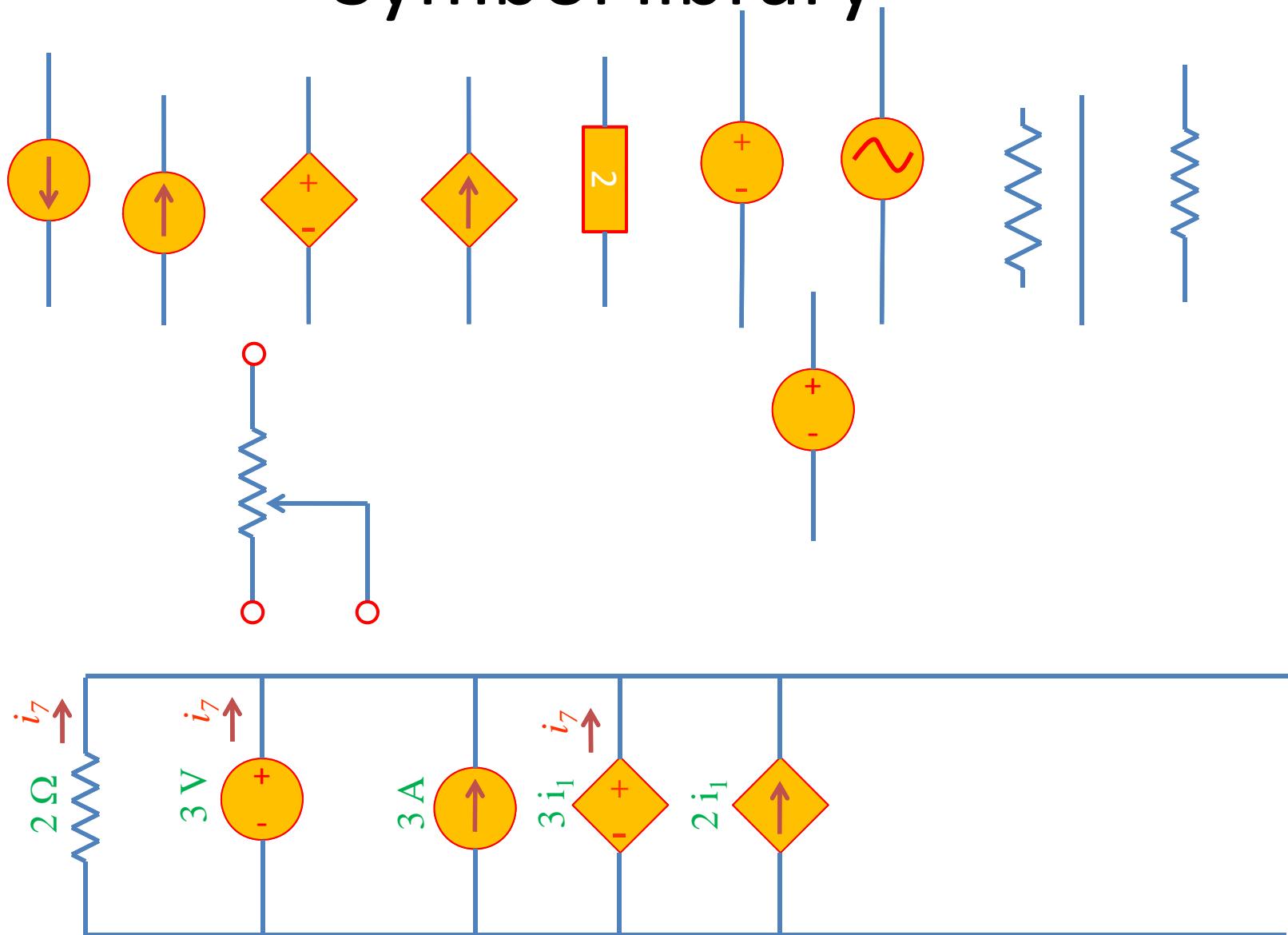

Symbol & circuit library

