

Announcements:

1. HW will be due on Wednesday this week  
(check website for new version)
2. Graded midterms are for pickup from TAs


# EECS 70A: Network Analysis

## Lecture 9

# Today's Agenda


- Thevinin/Norton theorem
- Power transfer
- Capacitors
- Inductors
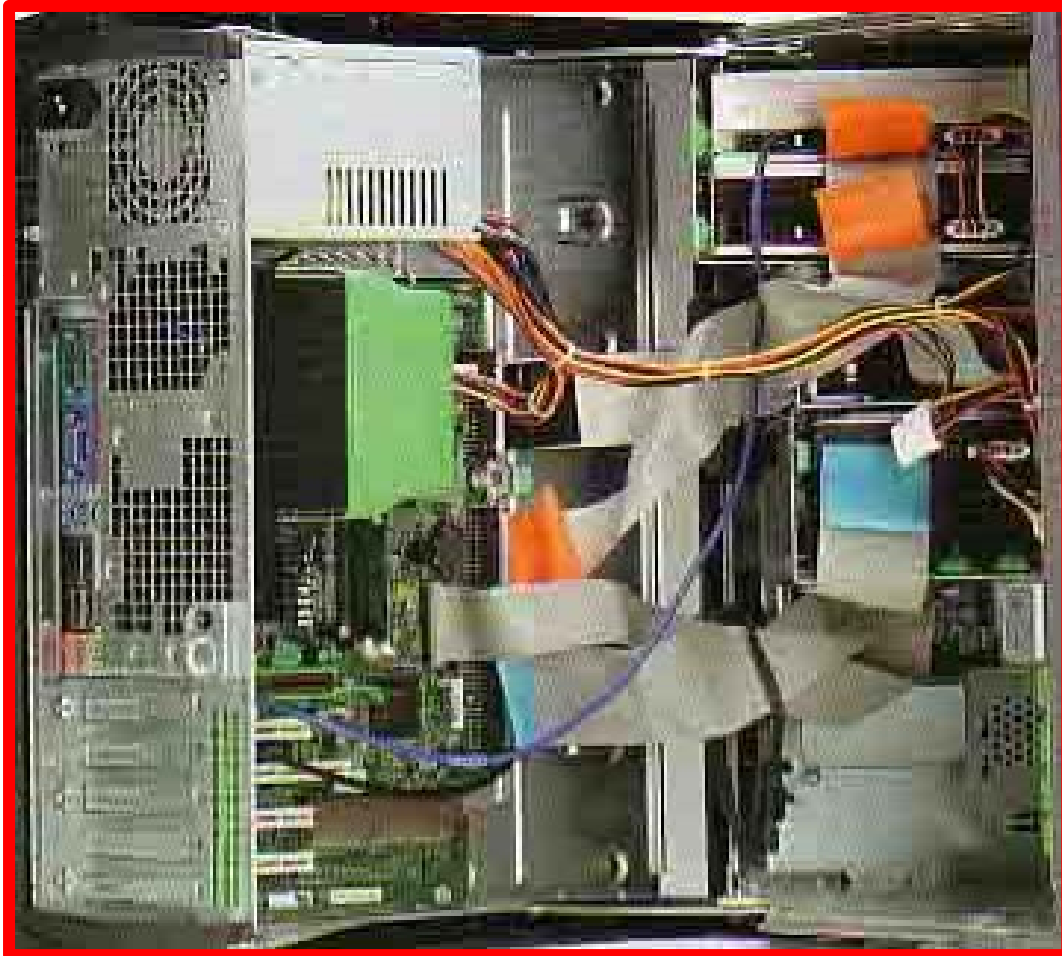
# Compartmentalization: Need for simplicity




Power brick image.  
And ask class to show their own...  
Demo: Computer?


# Thevenin's Theorem

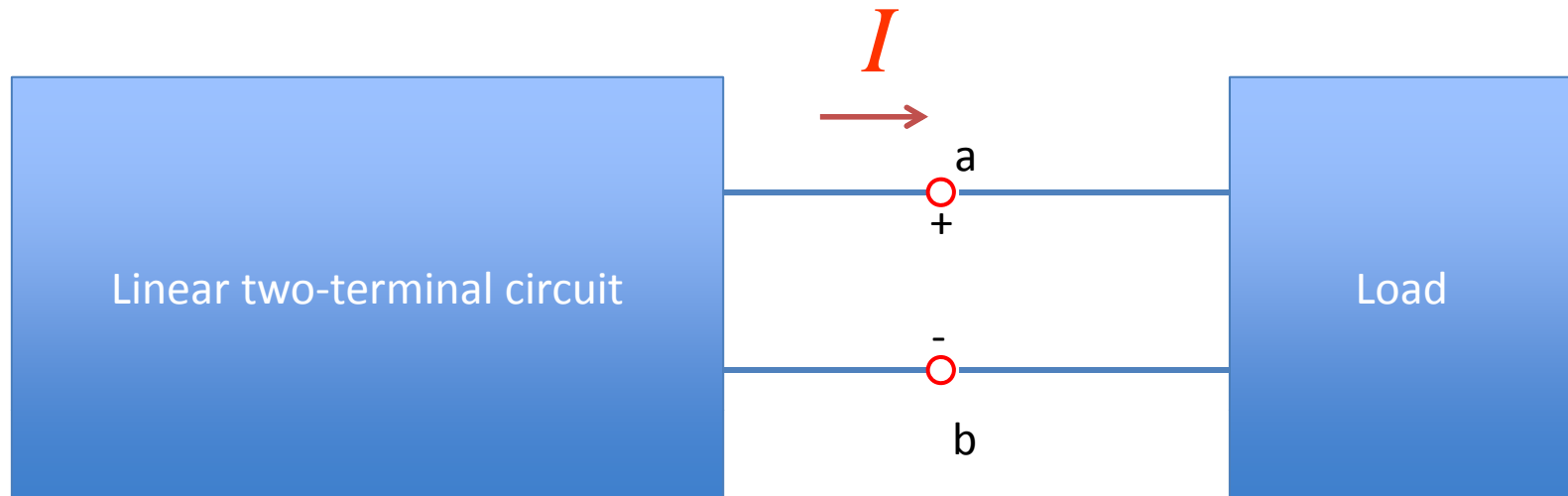

Equivalent to:

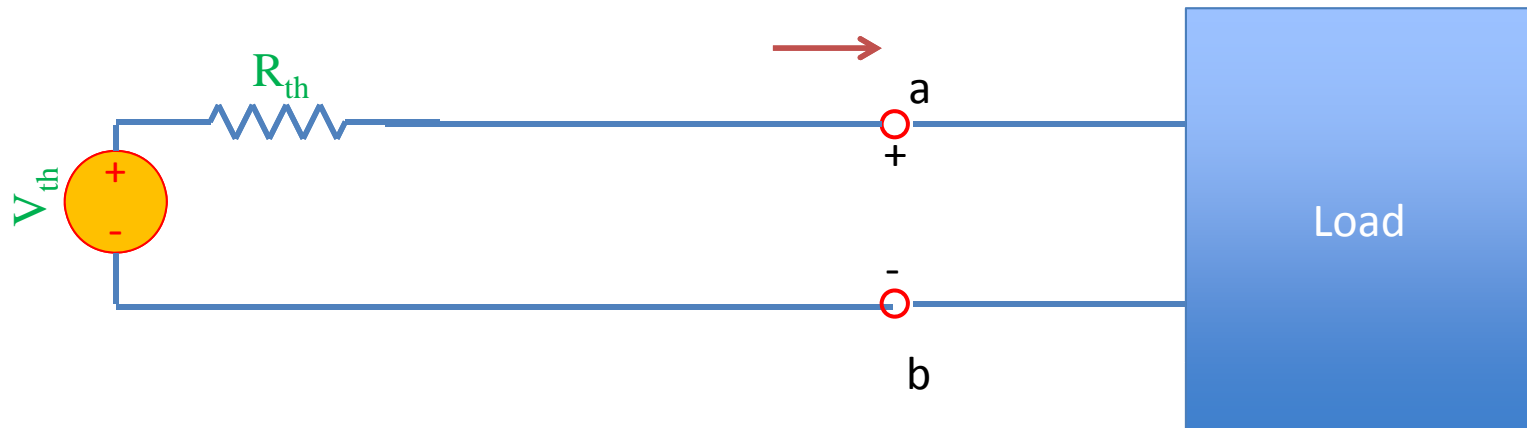

# Finding $V_{th}$ , $R_{th}$

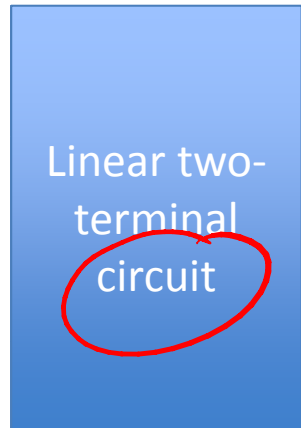

Goal: Find  $V_{th}$ ,  $R_{th}$ :


Given: circuit

$$I = \frac{V_{th}}{R_{th}}$$

1) Find  $V_{th}$ :

Calculate  $V_{ab}$  (when no external circuit connected)

Equivalent to:

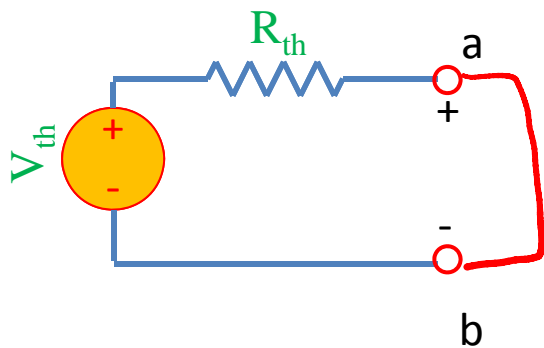

2) Find  $I_{short}$  circuit


$$\text{Then } R_{th} = \frac{V_{th}}{I_{short \text{ circuit}}}$$

$$I = \frac{V_{th}}{R_{th}}$$

$$\Leftrightarrow R_{th} = \frac{V_{th}}{I_{short \text{ circuit}}}$$
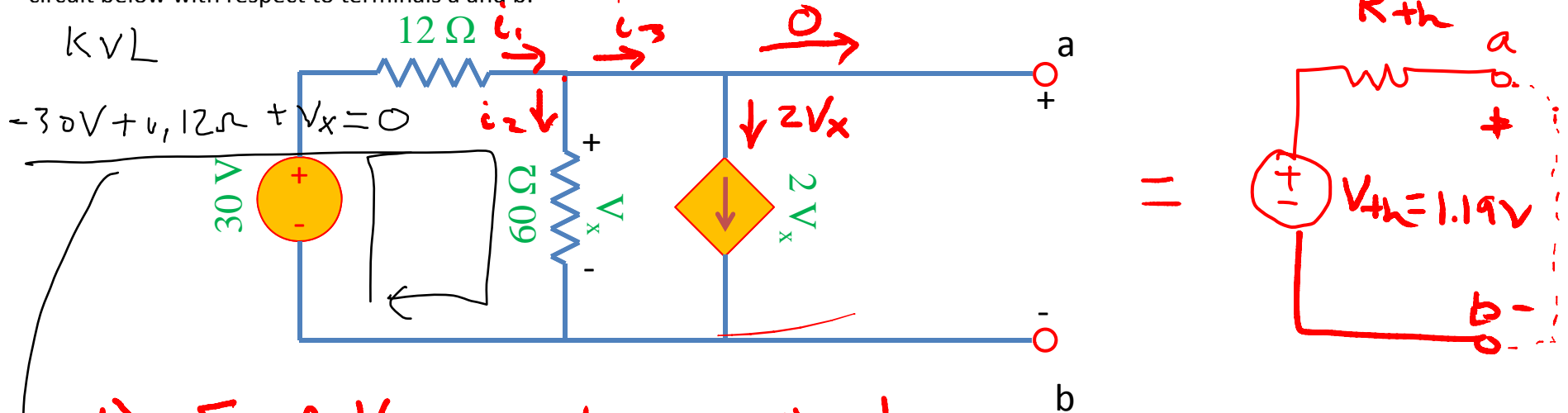
# Example

Find the Thevenin & Norton equivalent circuit of the circuit below with respect to terminals a and b:



1) Find  $V_{ab}$  complex circuit w/ nothing connected to a, b.

$$V_{ab} = V_x \quad KCL \Rightarrow i_1 = i_2 + i_3 \quad (*)$$

$$i_1 = \frac{30V - V_x}{12\Omega} \quad i_2 = \frac{V_x}{60} \quad i_3 = 2V_x$$

$$(*) \Rightarrow \frac{30V - V_x}{12\Omega} = \frac{V_x}{60} + 2V_x \Rightarrow V_x = 1.19V \quad \checkmark$$


$= V_{th}$

→ 2) Find  $I_{short}$  circuit


$$= \frac{30V}{12\Omega} = 2.5A \Rightarrow I_{short \text{ circuit}} = \frac{V_{th}}{R_{th}}$$

$$\Rightarrow R_{th} = \frac{1.19V}{2.5A} = 0.476\Omega$$

# Alternate method to find $R_{th}$ :

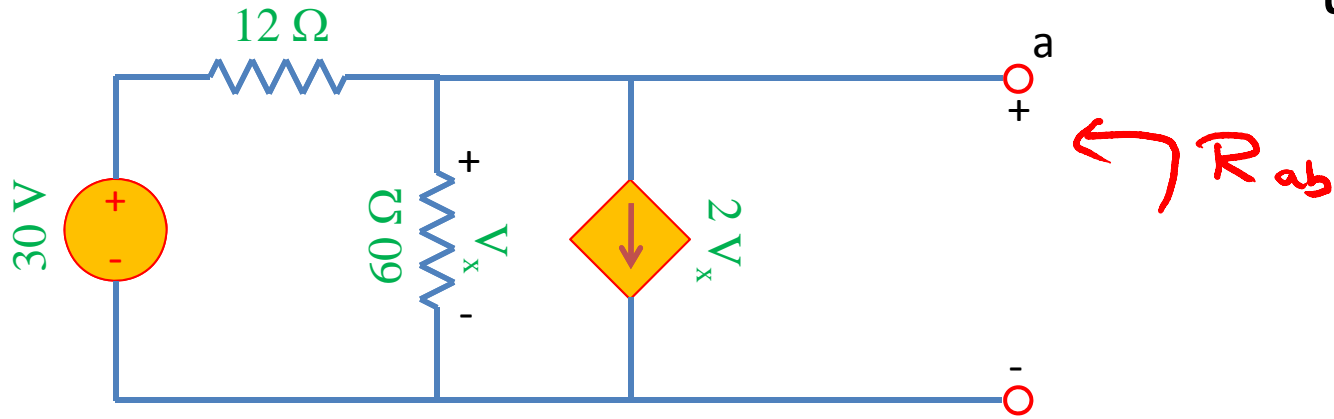

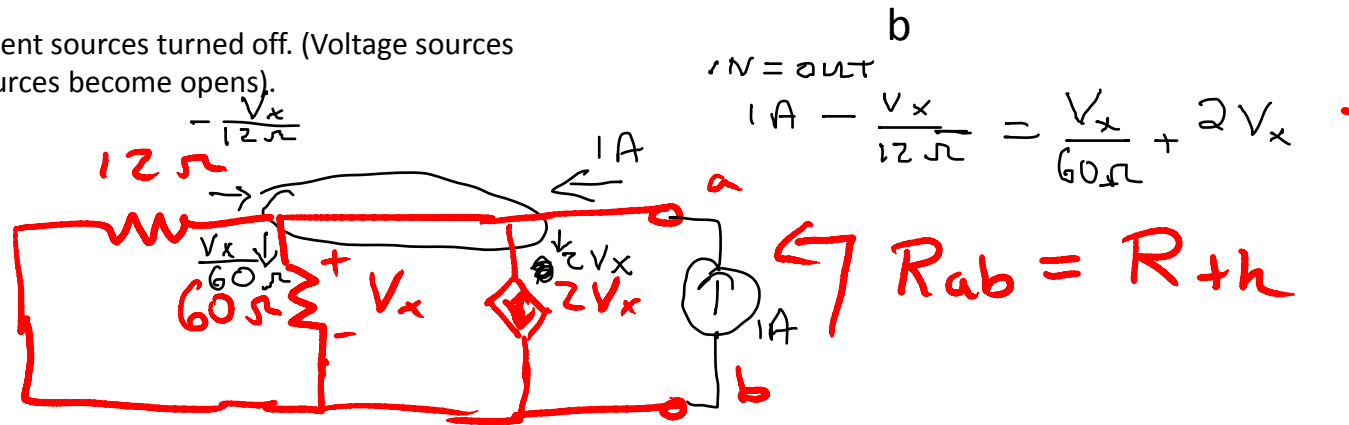Find  $R_{ab}$  when all independent sources turned off. (Voltage sources become shorts, current sources become opens).




TRICK: APPLY 1A CURRENT SOURCE TO a-b  
 FIND  $V_{ab}$  UNDER THAT CONDITION.


EQUATE  $R_{ab} = \frac{V_{ab}}{1 \text{ A}}$

KCL  $1 \text{ A} = 2V_x + \frac{V_x}{60 \Omega} + \frac{V_x}{12 \Omega} \Rightarrow V_x = 0.476 \text{ V} = V_{ab}$   
 $R_{ab} = \frac{0.476 \text{ V}}{1 \text{ A}} = 0.476 \Omega = R_{th}$

# Norton's Theorem

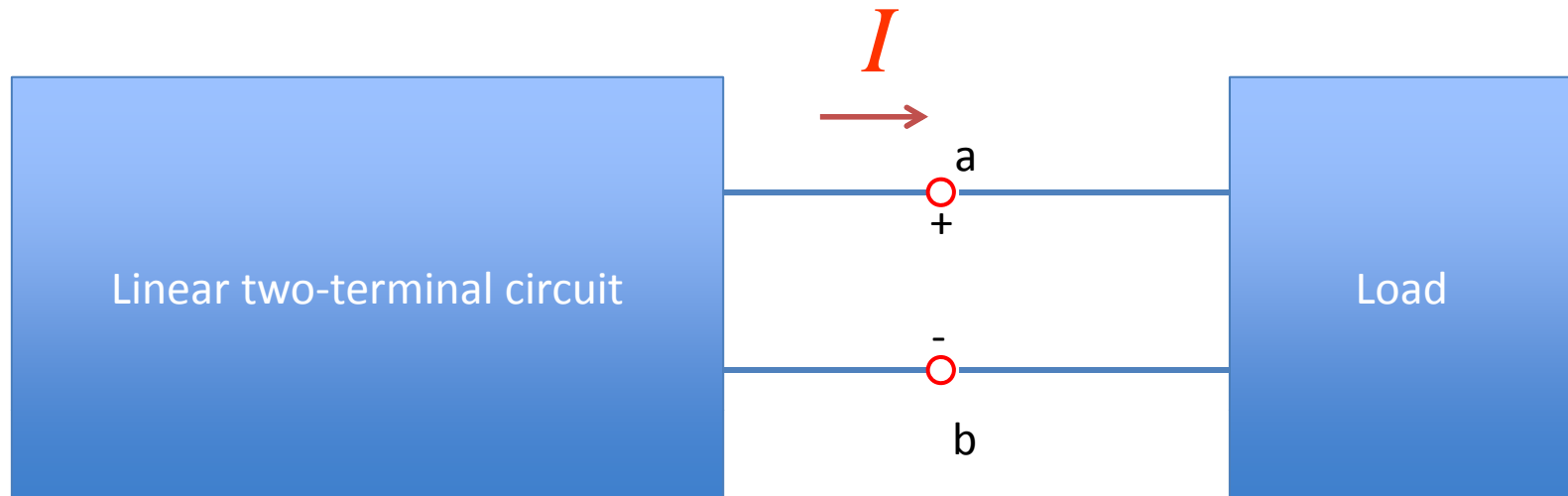

Equivalent to:

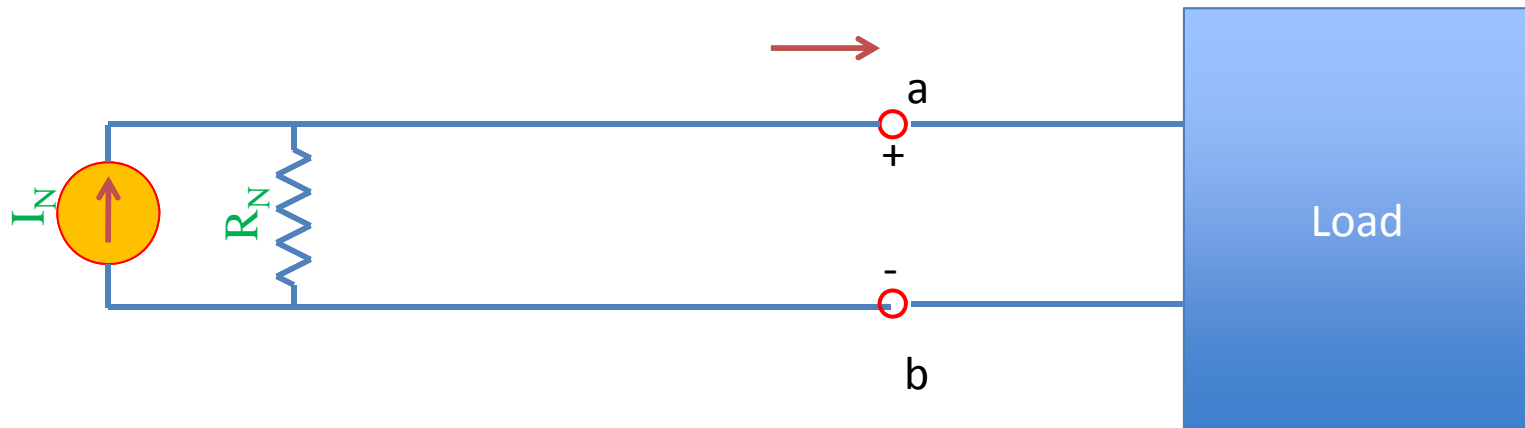



# Finding $V_{th}$ , $R_{th}$


Once you Find  $R_{th}$ ,  $V_{th}$ ,  
easy to find  $I_N$ ,  $R_N$

Open (means: nothing connected to a,b)


$$V_{ab} = V_{th} = I_N R_N (*)$$

Short (means: short a to b)

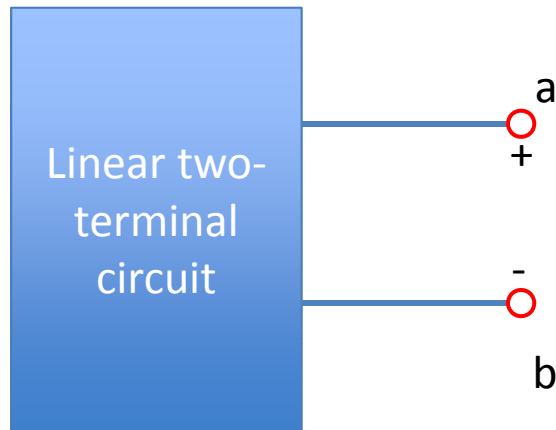
$$I_{short\ circuit} = \frac{V_{th}}{R_{th}} = I_N (**)$$



Equivalent to:



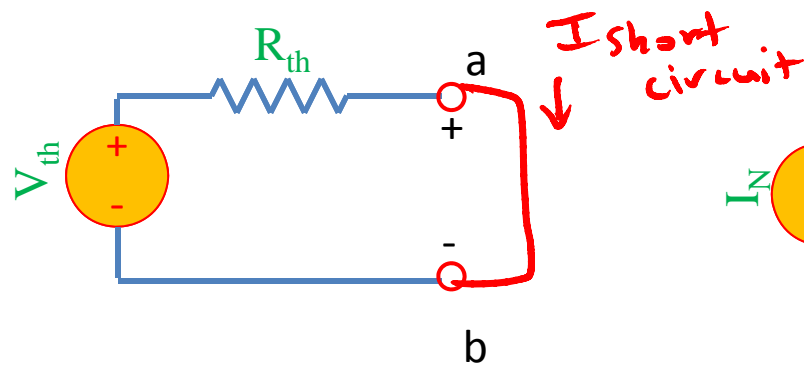


Equivalent to:

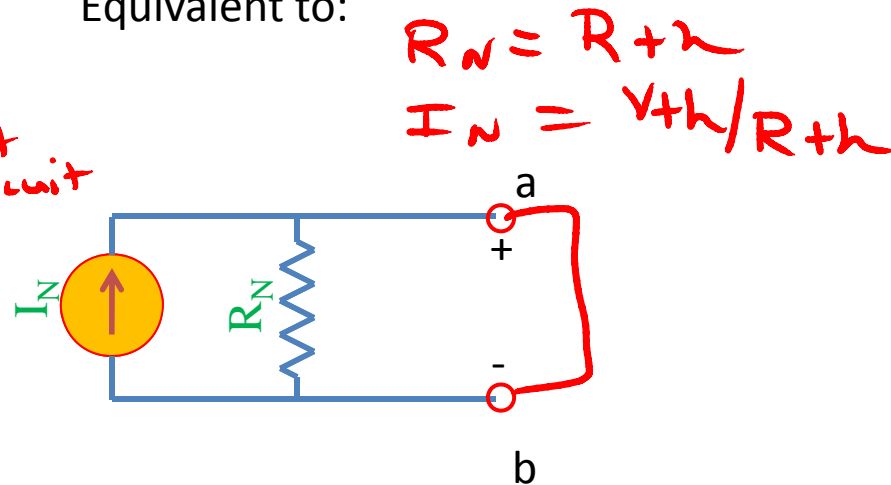

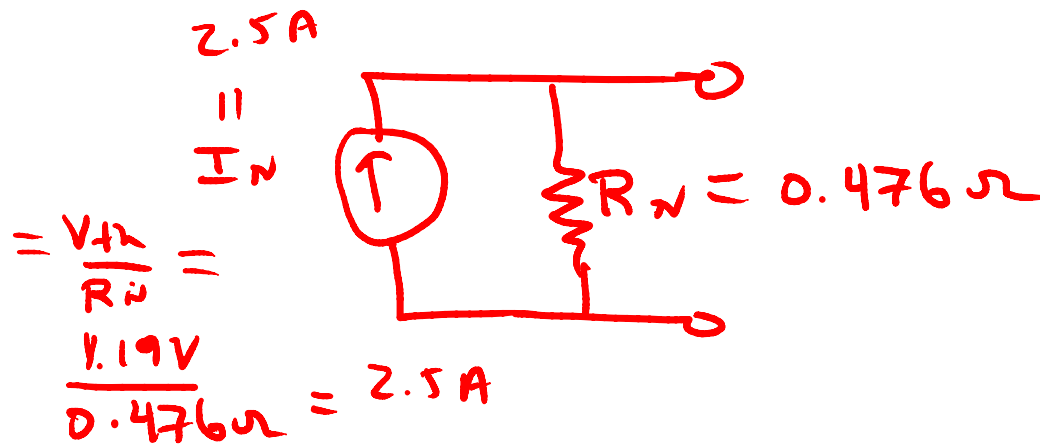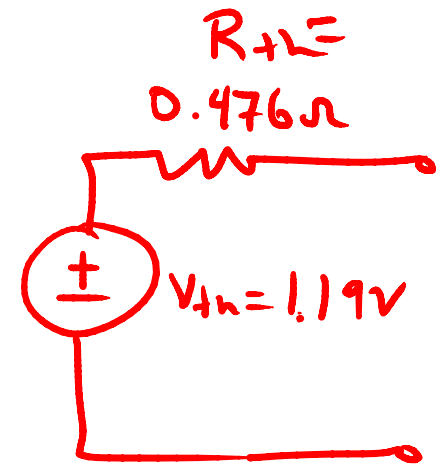
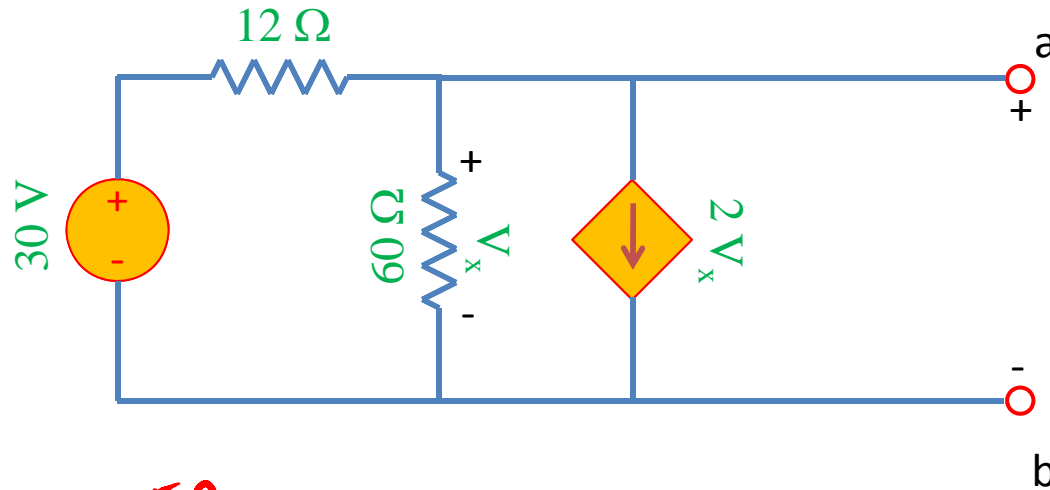
# Example

Find the Thevenin & Norton equivalent circuit of the circuit below with respect to terminals a and b:


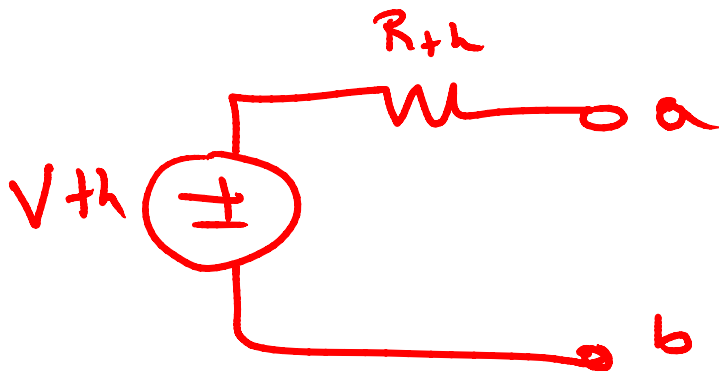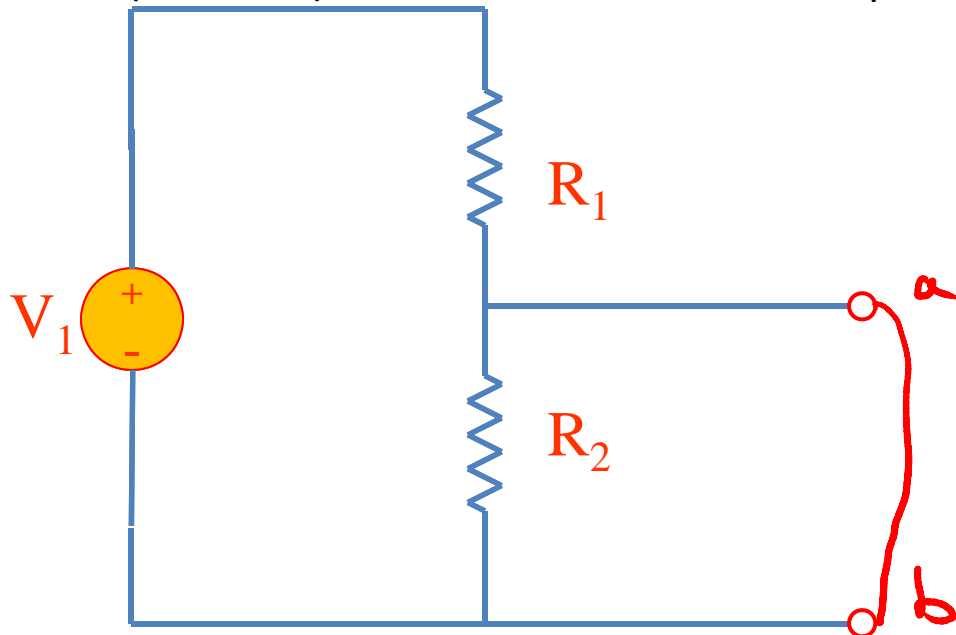
# IMPORTANT Example

(Students): Find Thevenin & Norton equivalent circuit:



- in terms of  $V_1, R_1, R_2$
- 1) Find  $V_{ab}$  (open)
  - 2) Find  $I_{\text{short circuit}} = \frac{V_1}{R_1}$


$$V_{ab} = \frac{R_2 V_1}{R_1 + R_2} = V_{th}$$

$$R_{th} = \frac{V_{th}}{I_{\text{short circuit}}} =$$

$$\frac{\frac{R_2 V_1}{R_1 + R_2}}{\frac{V_1}{R_1}}$$


$$= \frac{R_1 R_2}{R_1 + R_2} = R_1 \parallel R_2 = R_{th}$$

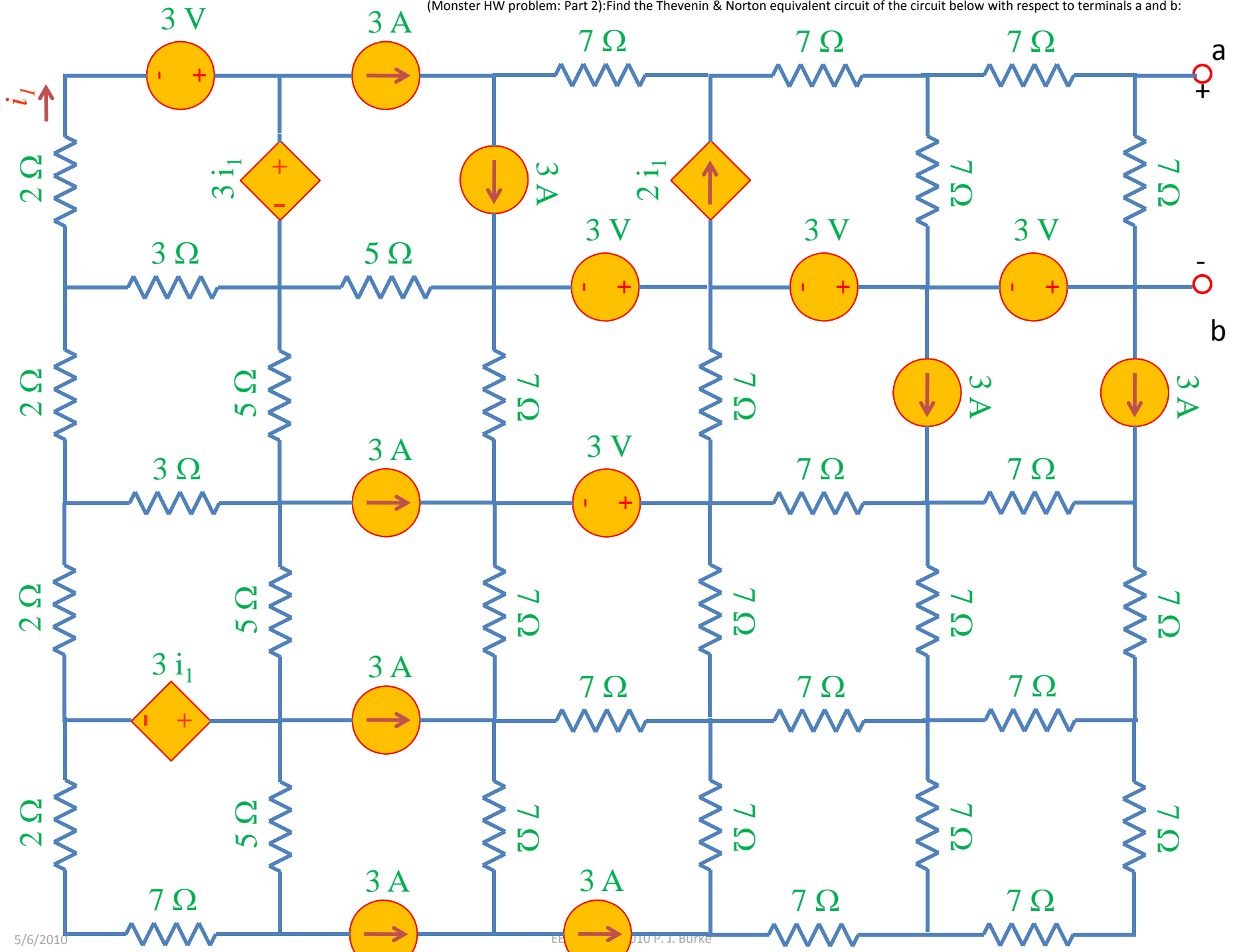(Monster HW problem: Part 2): Find the Thevenin & Norton equivalent circuit of the circuit below with respect to terminals a and b:



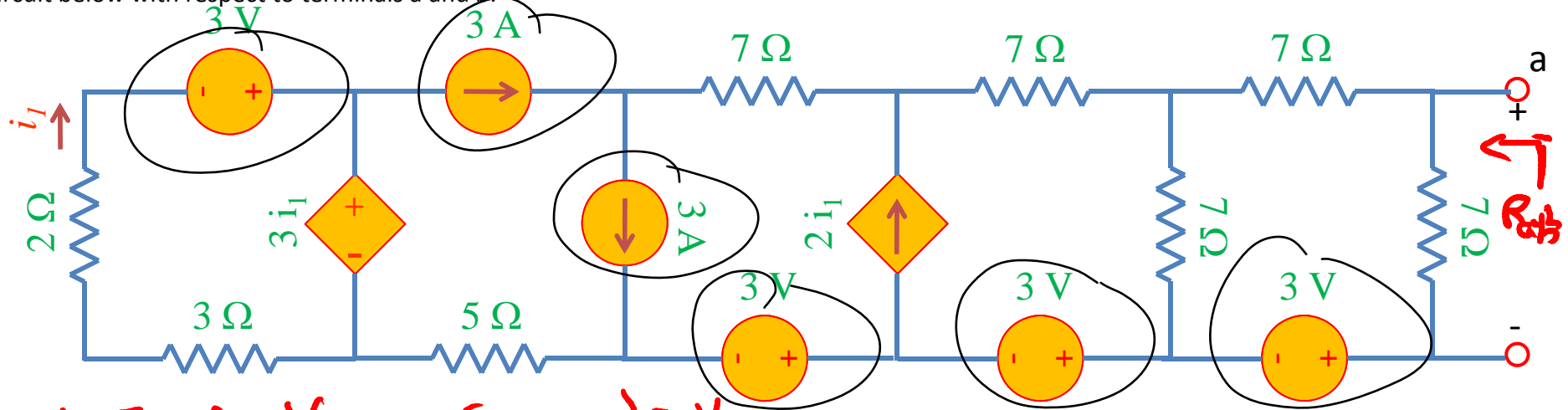
# "Baby" monster problem

Find the Thevenin & Norton equivalent circuit of the circuit below with respect to terminals a and b:




1) Find  $V_{ab}$  (open) =  $V_{th}$

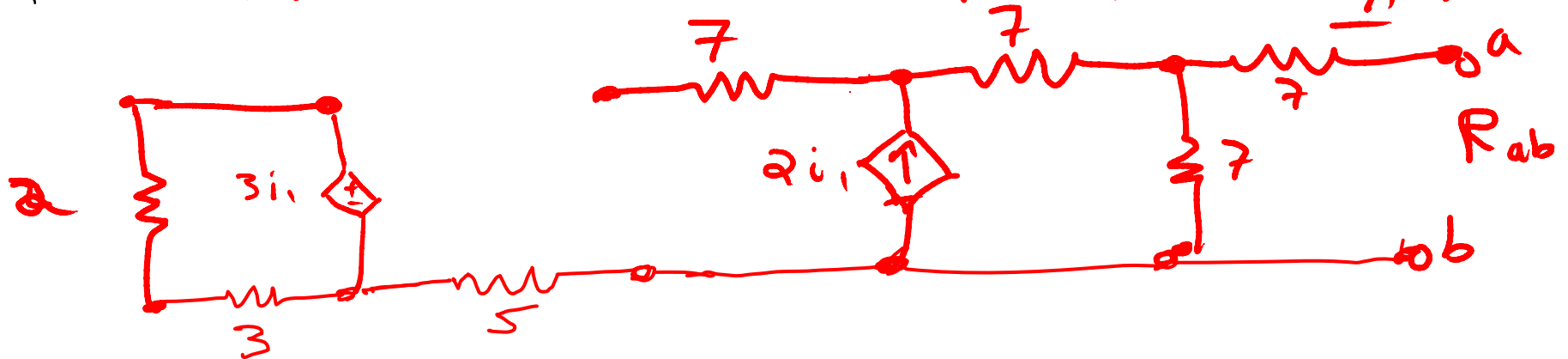
2) Find  $I_{short-circuit}$   $R_{th} = \frac{V_{th}}{I_{short-circuit}}$   
 OR Find  $R_{ab}$  when all independent sources off.



# Source/load

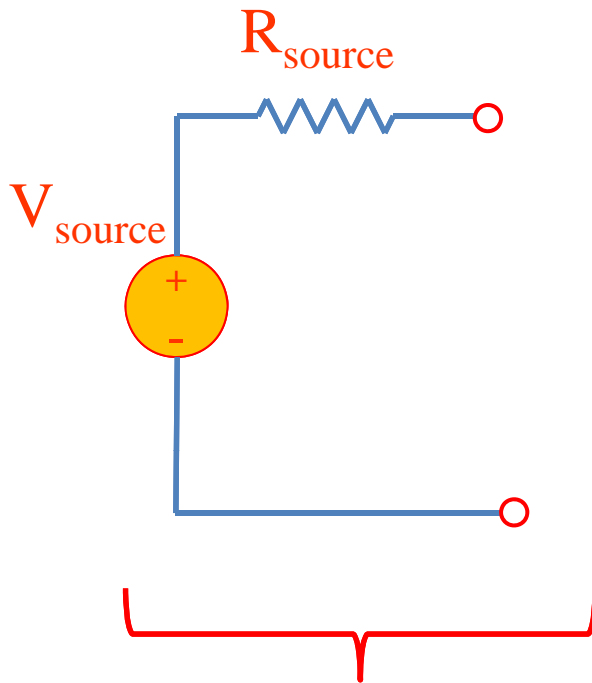

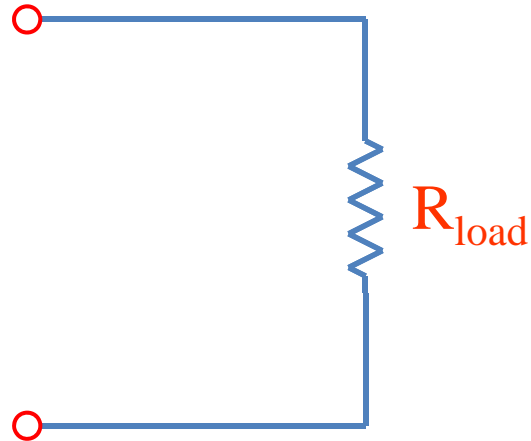Thevenin Thm:  
Any circuit can be  
represented by this  
equivalent circuit.



$$V_{load} = \frac{R_{load}}{R_{load} + R_{source}} V_{source}$$

Derivation:

Case 1:


$$R_{load} \gg R_{source}$$

Case 2:

$$R_{source} \gg R_{load}$$

We say  $R_{load}$  “loads down” the source.

# Source/load

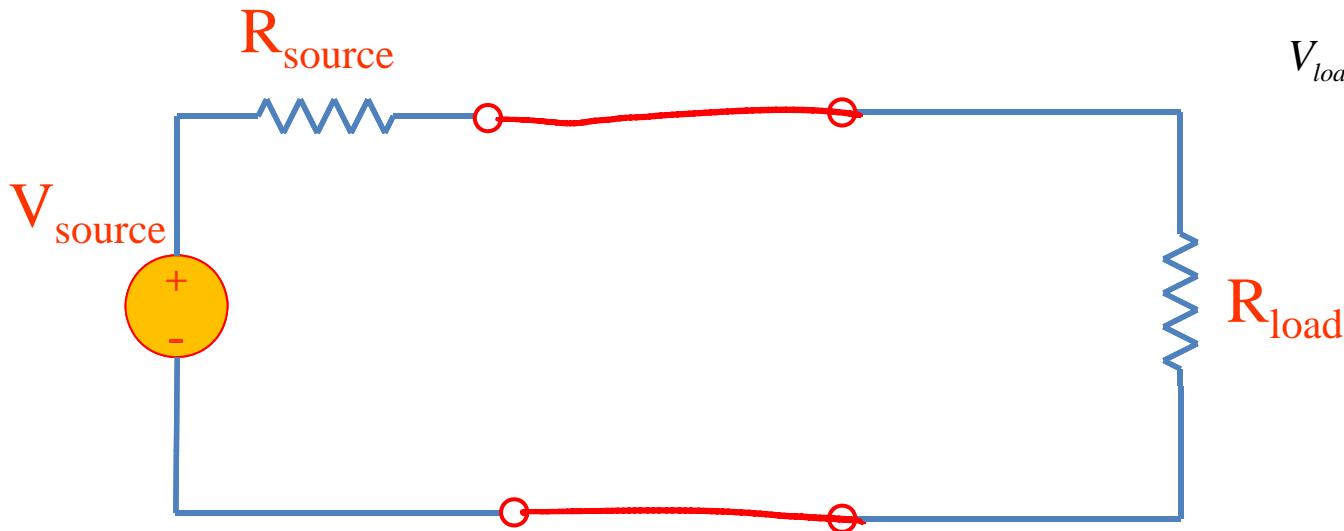

$$V_{load} = \frac{R_{load}}{R_{load} + R_{source}} V_{source}$$

Derivation:



Thevenin Thm:  
Any circuit can be represented by this equivalent circuit.

Case 1:

$$R_{load} \gg R_{source}$$

$$\Rightarrow V_{load} \approx V_{source}$$

Case 2:


$$R_{source} \gg R_{load}$$

$$V_{load} \rightarrow 0$$

$$\approx \frac{R_{load}}{R_{source}} V_{source}$$

We say  $R_{load}$  "loads down" the source.

# Power

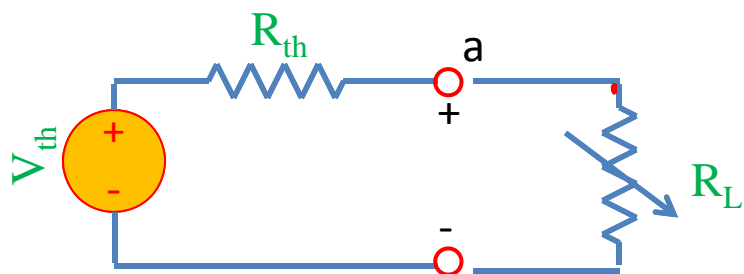


Arrow means  $R_L$  variable (e.g. by a knob)

Power delivered to load = ?

$$\frac{R_L}{R_{th} + R_L} V_{th} = \text{voltage across } R_L$$

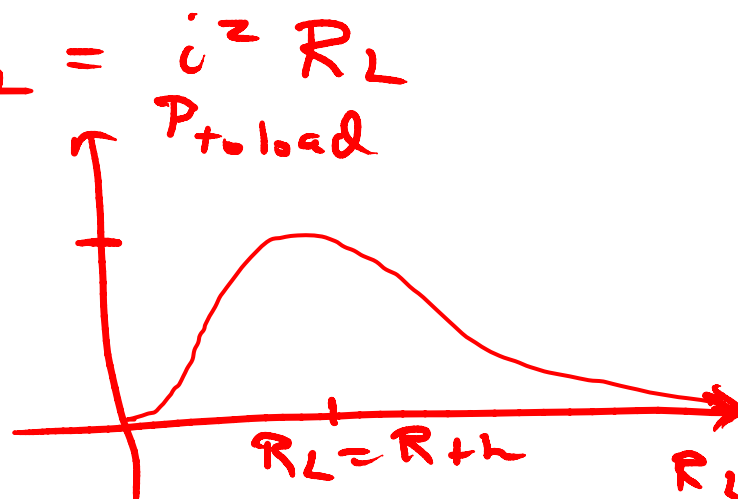
$$\begin{aligned} \text{Power delivered to } R_L &= i^2 R_L \\ &= \left( \frac{V_{th}}{R_{th} + R_L} \right)^2 R_L \end{aligned}$$





# Questions?

# Capacitors

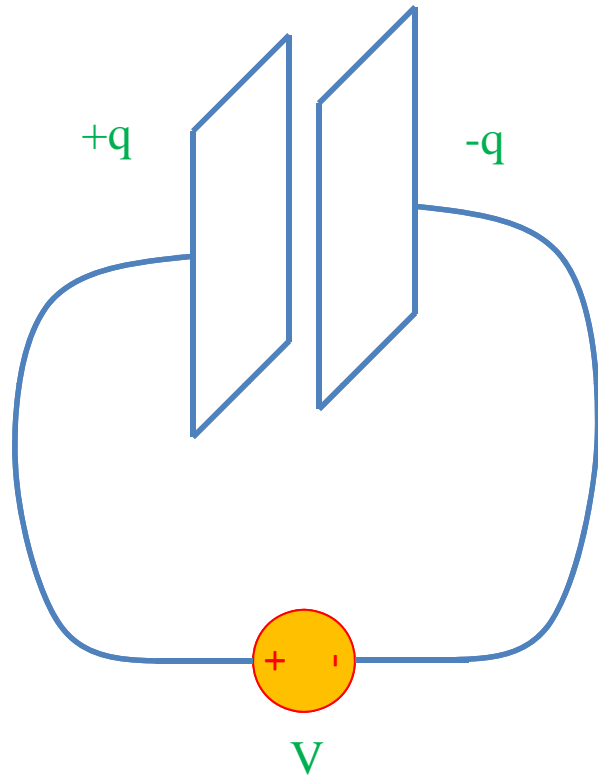

$$q = CV$$

$$C = \frac{\epsilon A}{d}$$

A=area  
d=plate separation

Farads[F] = Coulombs/Volt [C]/[V]


$$\epsilon_0 = 8.85 \times 10^{-12} \text{ F / m}$$

$$\epsilon = K\epsilon_0$$

Dielectric constant:


$$K = 3.9 \text{ SiO}_2$$

$$K = 25 \text{ HfO}_2$$

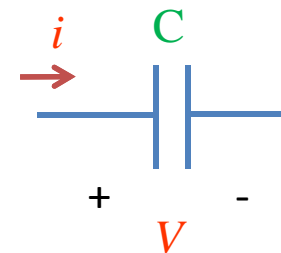
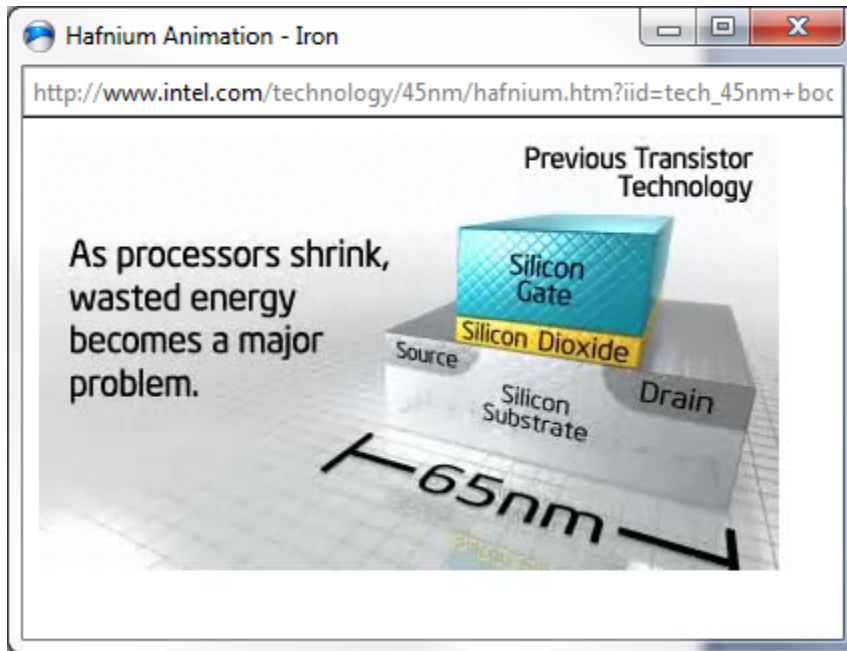
# “High-K Dielectric”

[http://www.intel.com/technology/45nm/hafnium.htm?iid=tech\\_45nm+body\\_animation\\_hafnium](http://www.intel.com/technology/45nm/hafnium.htm?iid=tech_45nm+body_animation_hafnium)



# Time dependence

$$q = CV \quad i = \frac{dq}{dt} = C \frac{dV}{dt}$$

*q, V, i can depend on time !*

Implicit:


$$q(t) = CV(t) \quad i(t) = \frac{dq(t)}{dt} = C \frac{dV(t)}{dt}$$

Will not always write (t), but it is assumed from now on.



$$i(t) = C \frac{dV(t)}{dt} \Rightarrow V(t) = \frac{1}{C} \int i(t) dt$$
$$\Rightarrow q(t) = \int i(t) dt$$

# Example Capacitor Problem

Find  $V(t)$ ,  $q(t)$

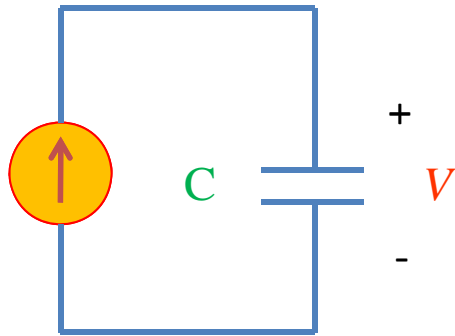


# One-bit memory

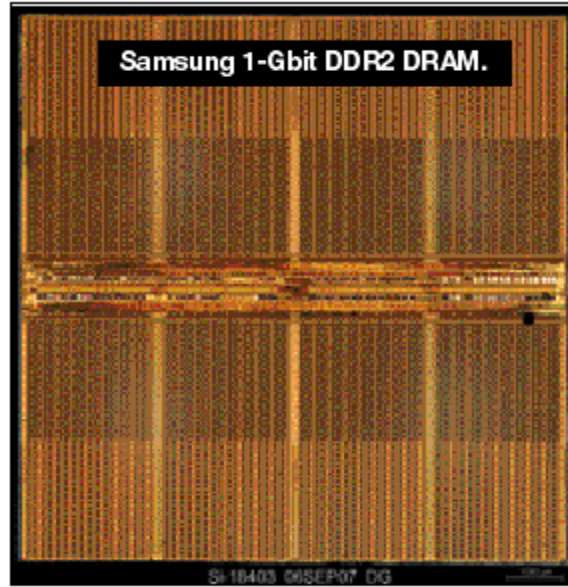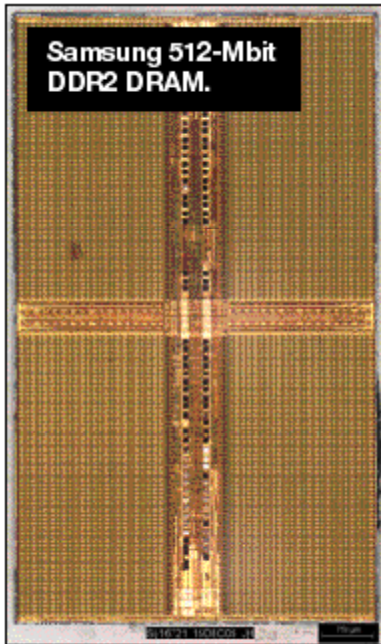

Typical dimensions:  
0.1 micron x 0.1 micron area  
10 nm thickness.  
What is C?



[http://i.cmpnet.com/eet/news/07/11/DC1502\\_UTH\\_samsung.gif](http://i.cmpnet.com/eet/news/07/11/DC1502_UTH_samsung.gif)

# 1 Bit Read/Write

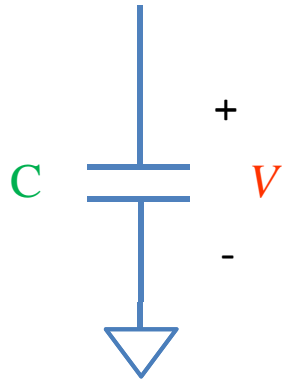

# Example Problem #2


(Students): Find  $i(t)$ ,  $q(t)$

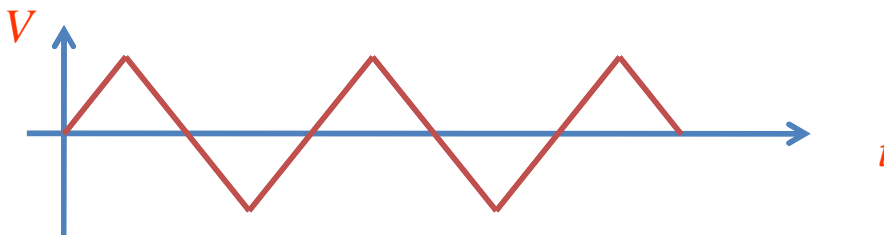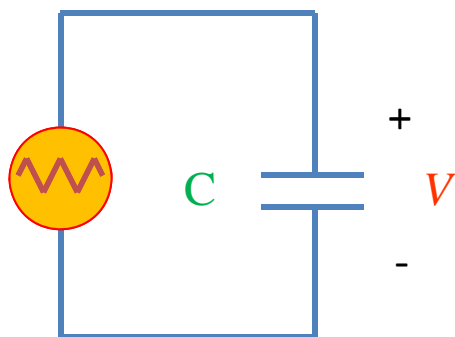



# RC circuit


Find  $V(t)$ ,  $q(t)$ ,  $i(t)$

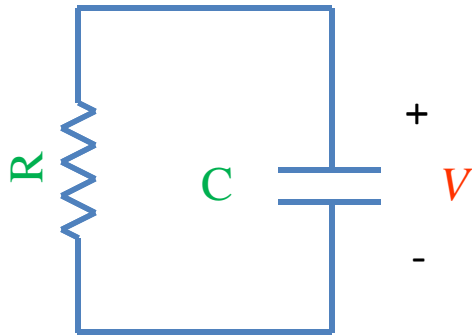


# DRAM vs. SRAM

# Example Capacitor Problem #2


Find  $V(t)$ ,  $q(t)$

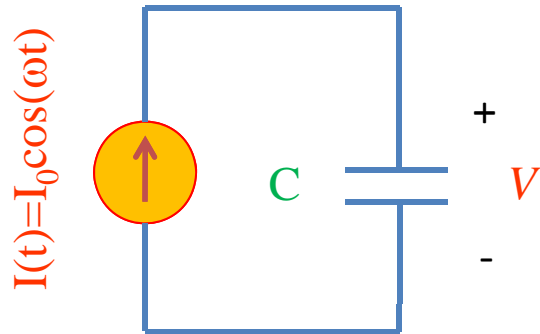

# Parallel Capacitors

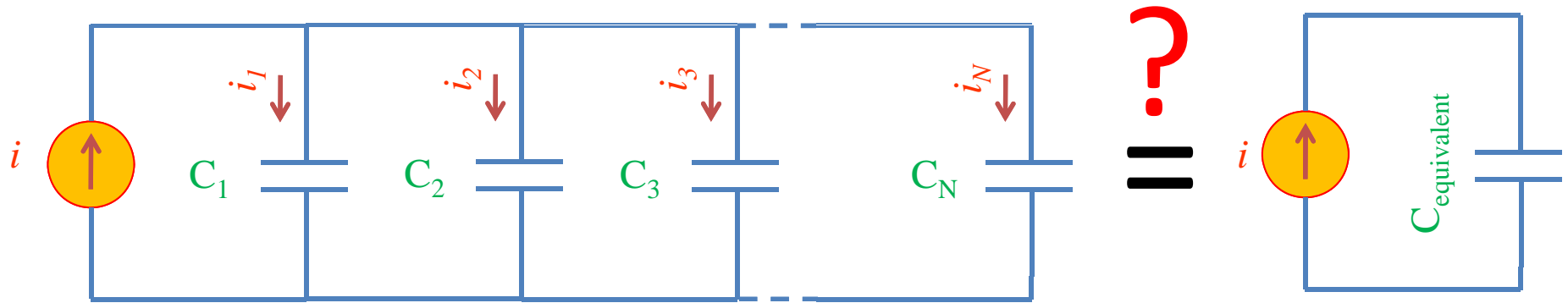


# Series Capacitors

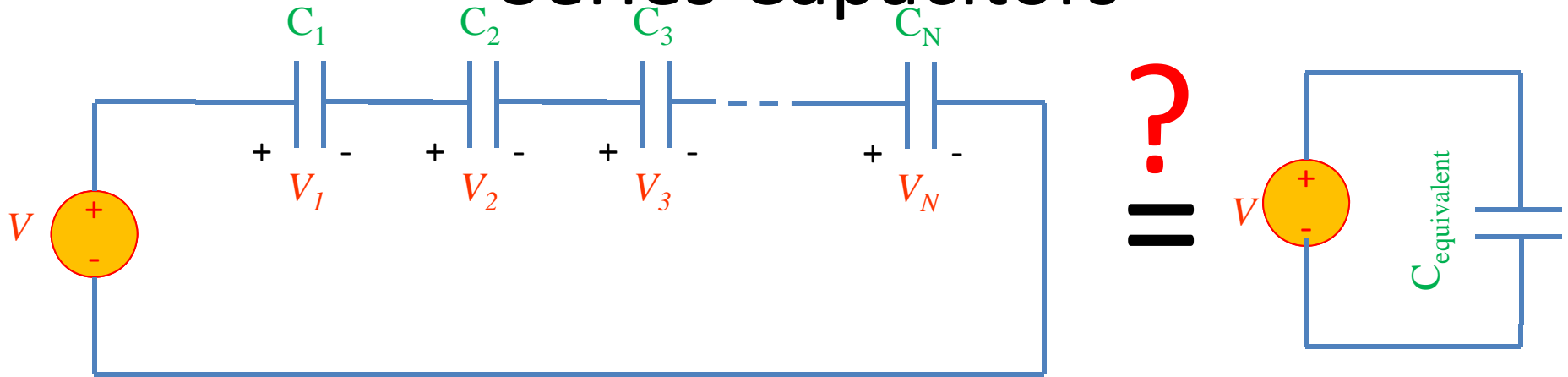

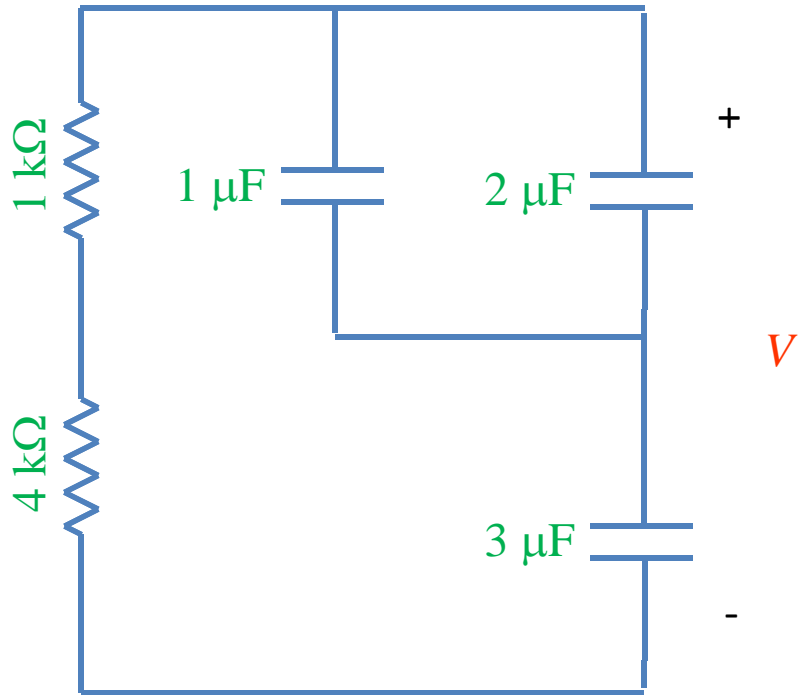
# Example problem #4

(Students) Find  $V(t)$ , given that  $V(t=0) = 5$  Volts



# Inductors

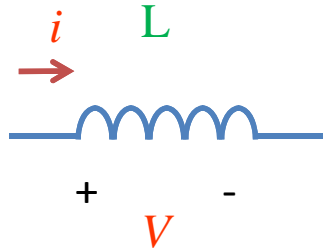

$$L = \frac{N^2 \mu A}{l}$$

A=area

l=wire length

N = # of turns



$\mu = 4 \pi 10^{-6}$  H/m

$$V = L \frac{di}{dt}$$

Henry[H]


$$V = L \frac{di}{dt} \Rightarrow i(t) = \frac{1}{L} \int V(t) dt$$

# Series Inductors

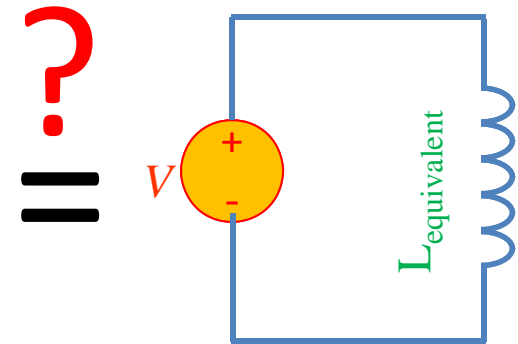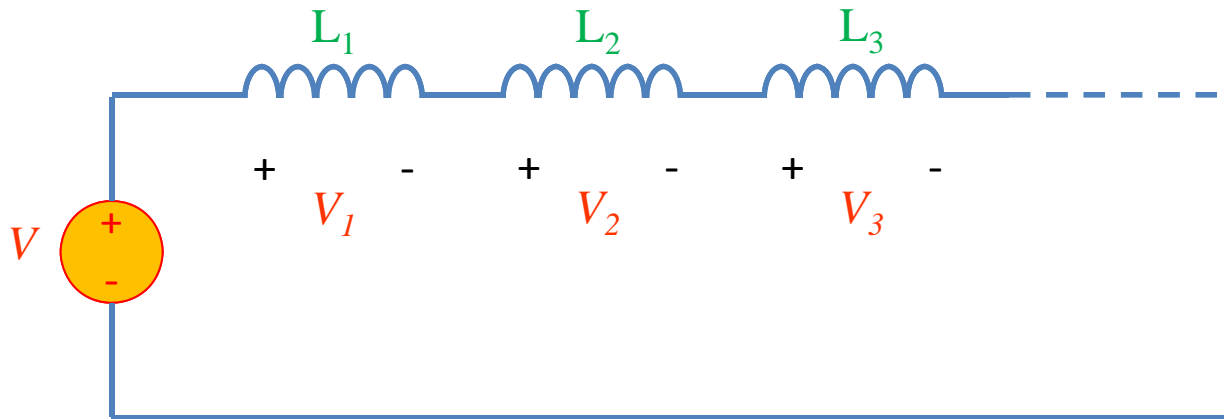




# Parallel Inductors

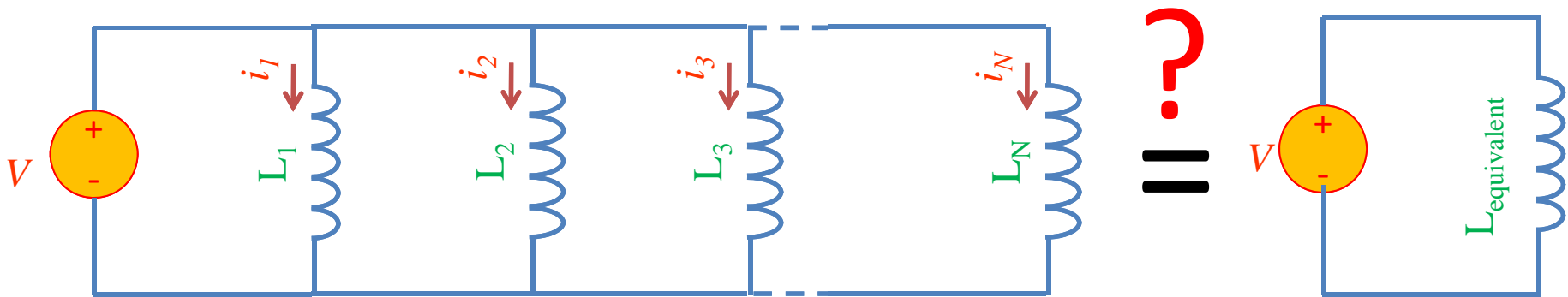



# Example Inductor Problem

(Students): Find  $V(t)$ .

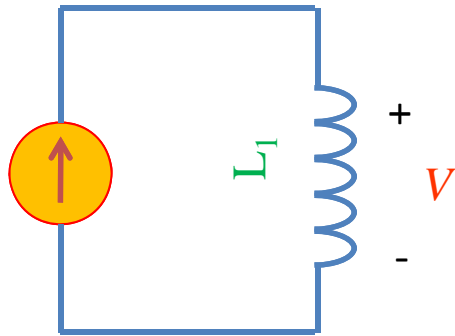


# Example Inductor Problem #2

(Students): Find  $i(t)$

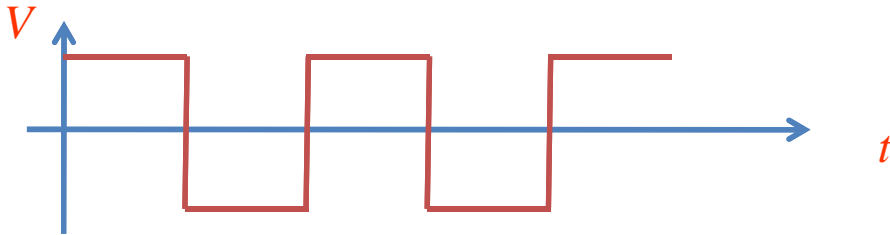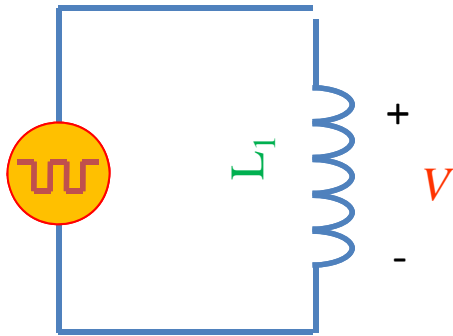


# Example Inductor Problem #3

Find  $V(t)$

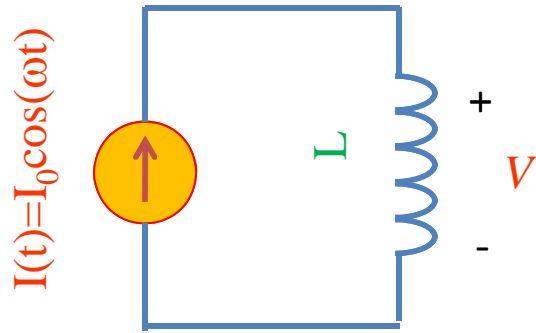


# LR circuit

Find  $V(t)$ ,  $i(t)$

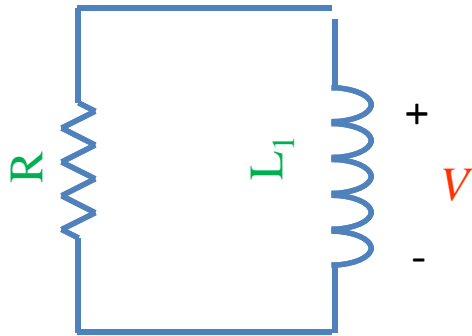

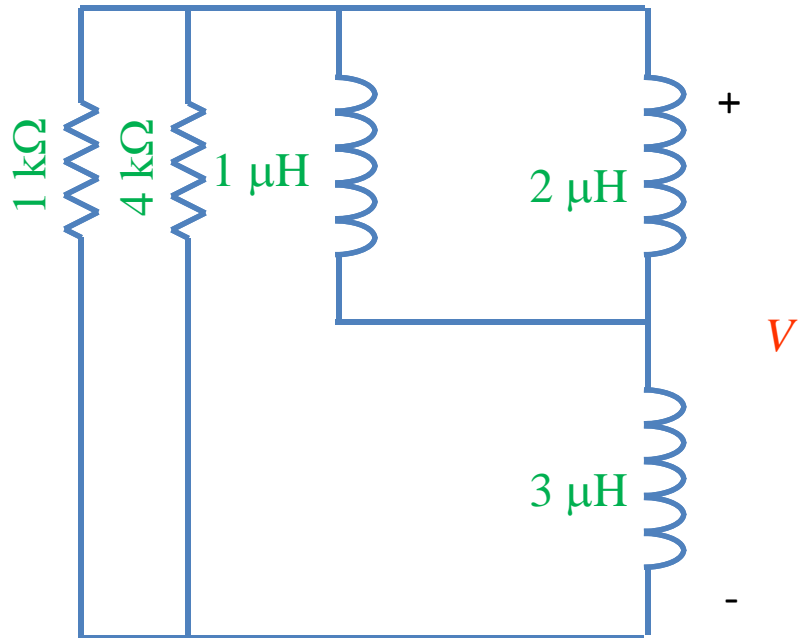
# Example LR problem

(Students) Find  $V(t)$ , given that  $V(t=0) = 5$  Volts



# Power

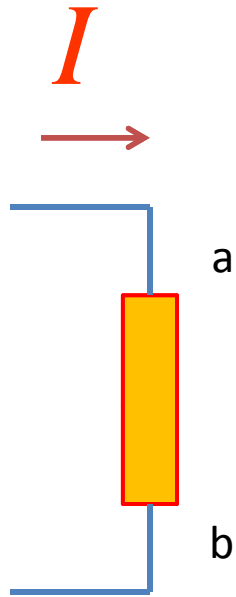

$$I \times V_{ab} = \text{power}$$


Watts [W] = Volt Amp [V-A]

Note: MKSA unit system:  
*Meters Kilogram Second Amp*

Resistor:  
Energy lost to heat...

Inductor or capacitor:  
Energy **STORED** and can be recovered...

# Energy stored

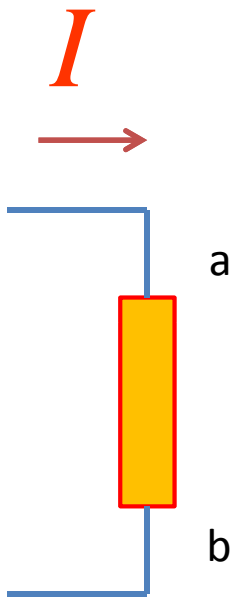

$$I \times V_{ab} = \text{power}$$

Energy:

$$W = \int P dt = \int I \cdot V dt$$

Capacitor stored energy:




$$\int I \cdot V dt = \int C \frac{dV}{dt} \cdot V dt = \frac{1}{2} CV^2 = \frac{Q^2}{2C}$$

Inductor stored energy:

$$\int I \cdot V dt = \int I \cdot L \frac{dI}{dt} dt = \frac{1}{2} LI^2$$



# Symbol library

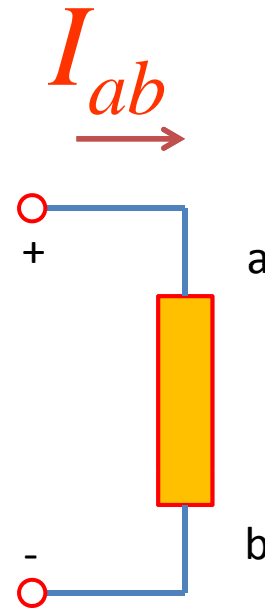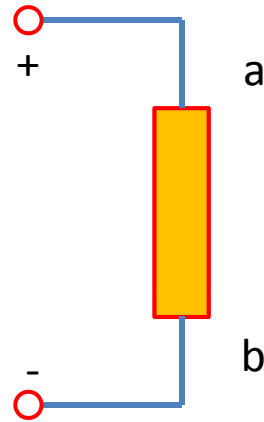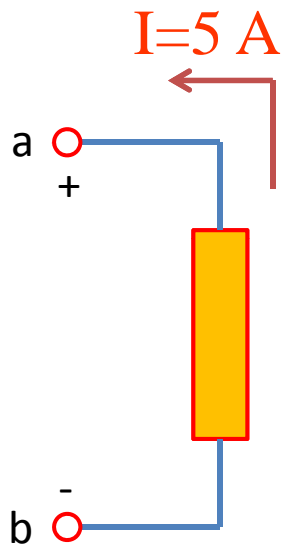

# Symbol library

