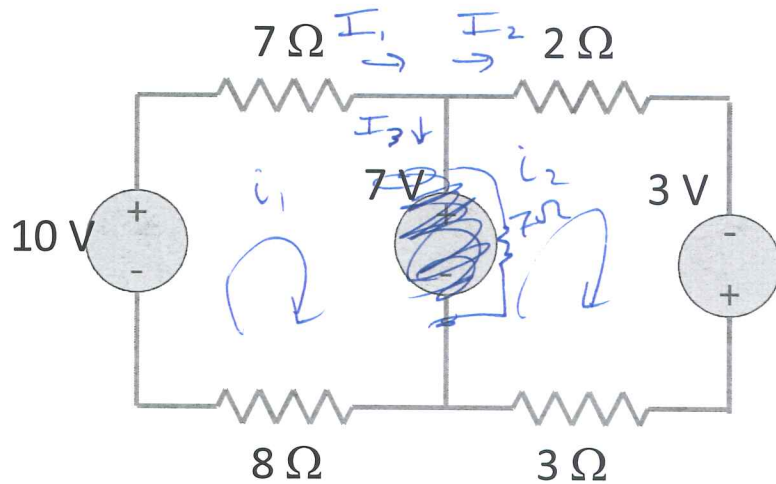


Mesh Analysis Example 1



Note: I changed example to be a 7Ω resistor in the center.

KVL

$$-10V + i_1 7\Omega + (i_1 - i_2) 7\Omega + i_1 8\Omega = 0$$

$$-(i_1 - i_2) 7\Omega + i_2 2\Omega - 3V + i_2 3\Omega = 0$$

Solve i_1, i_2

then I_1, I_2, I_3


then voltages.

$$I_1 = i_1$$

$$I_2 = i_2$$

$$I_3 = i_1 - i_2$$

Mesh Analysis Example 2

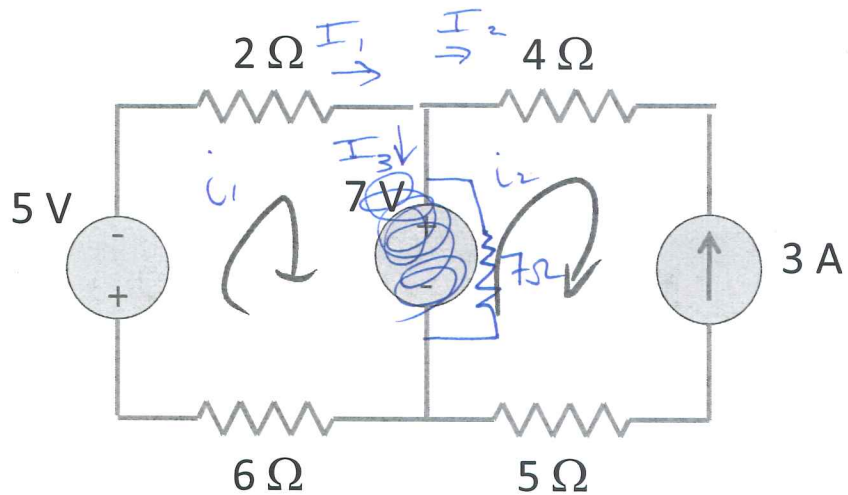

$$I_1 = i_1$$

$$I_2 = i_2$$

$$I_3 = i_1 - i_2$$

Also change 7V to resistor.

no SM

$$5V + i_1 2\Omega + (i_1 - i_2) 7\Omega = 0$$

$$i_2 = -3A$$


Solve i_1, i_2

then I_1, I_2, I_3

then Voltages

Thevenin/Norton example 1

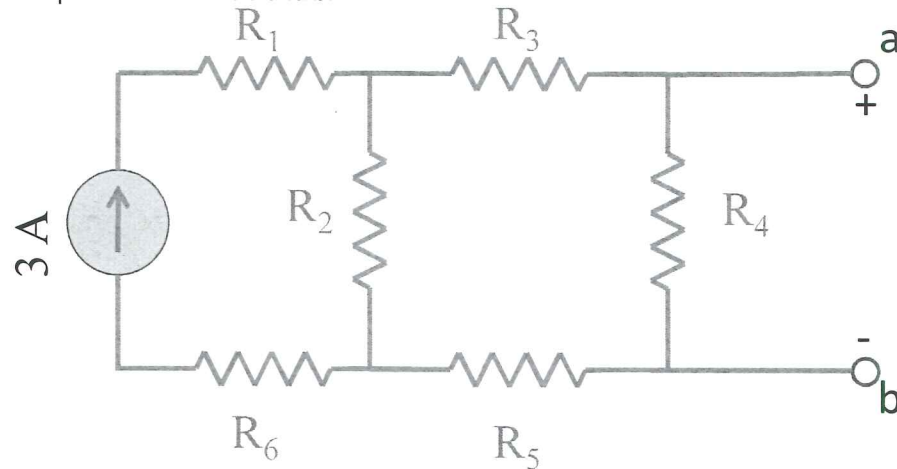Find the Thevenin & Norton equivalent circuit of the circuit below with respect to terminals a and b:




Step one V_{th}

Calc. V_{ab} w/ nothing connected.

Hint: find current thru


R_4 then $V_{ab} = R_4 \times \text{current thru } R_4$

Use knowledge of current divider:

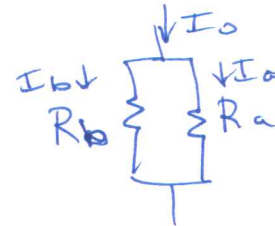

$$I_a = \left(\frac{R_b}{R_a + R_b} \right) I_0$$


then

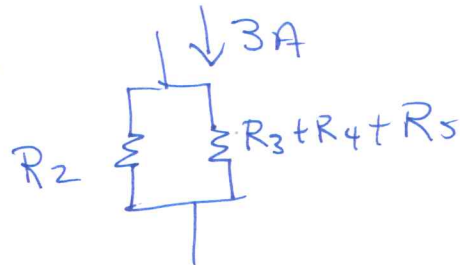

$$\text{curr thru } R_4 = 3A \frac{R_2}{R_2 + R_3 + R_4 + R_5}$$

$$\Rightarrow V_{th} = \frac{R_2 R_4}{R_2 + R_3 + R_4 + R_5} 3A$$

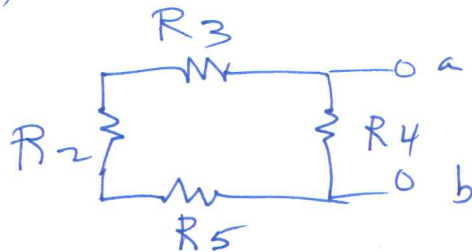
For R_{th} , find R_{ab} when ind. sources off:



$$R_{th} = R_4 \parallel (R_2 + R_3 + R_5)$$

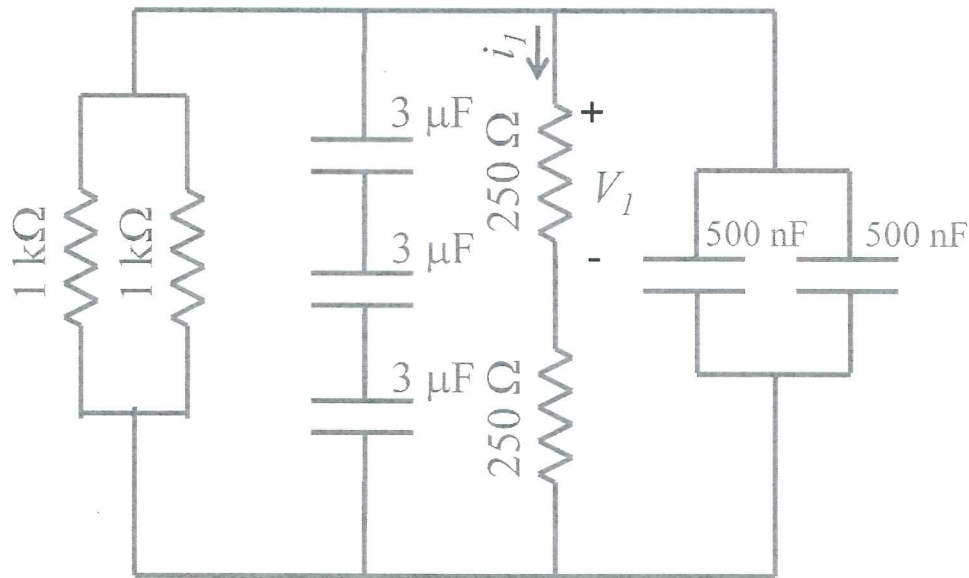Example RC problem 1

Find $i_1(t)$, given that $V_1(t=0) = 3$ Volts



$$V(t) = V(t=0) e^{-t/\tau_{\text{Req}}}$$



$$R_{\text{eq}} = (1\text{ k}\Omega \parallel 1\text{ k}\Omega) \parallel (250\Omega + 250\Omega)$$

$$= 500\Omega \parallel 500\Omega = 250\Omega$$

$$C_{\text{eq}} = (500\text{ nF} \parallel 500\text{ nF}) \parallel \text{series with } 1\mu\text{F}$$

\uparrow
 $= 3\mu\text{F}$ in series with
 $3\mu\text{F}$ in series with
 $3\mu\text{F}$

$$= 1\mu\text{F} \parallel 1\mu\text{F}$$

$$= 2\mu\text{F}$$

$$\tau_{\text{Req}} C_{\text{eq}} = 500\mu\text{s} = 0.5\text{ms}$$

$$(\tau = 2\mu\text{F} \times 250\Omega)$$

$$V_1(t) = \frac{1}{2} V(t) \Rightarrow V_1(t=0) = \frac{1}{2} V(t=0)$$

$$\Rightarrow V(t=0) = 6\text{V}$$

$$i_1(t) = \frac{V_1(t)}{250\Omega} = \frac{1}{500\Omega} V(t)$$


$$= \frac{6\text{V}}{500\Omega} e^{-t/0.5\text{ms}}$$

$$= \frac{6}{500} \text{ A } e^{-t/0.5\text{ms}} = i_1(t)$$

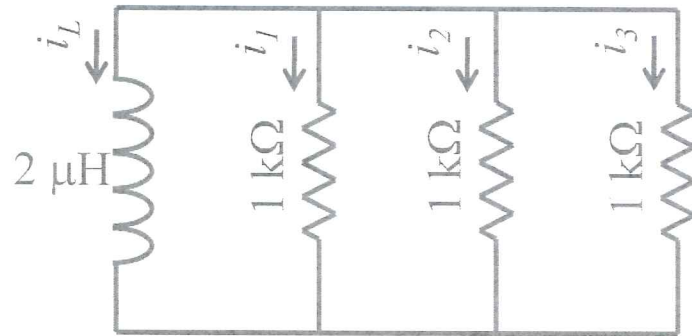Example LR problem #1

(Students) Find $i_1(t)$ given $i_L(t=0) = 5$ A.


Hint: $i_1 + i_2 + i_3 = -i_L$. How are i_1, i_2, i_3 related?



$$i_1 = i_2 = i_3$$

$$i_1 = -\frac{1}{3} i_L$$
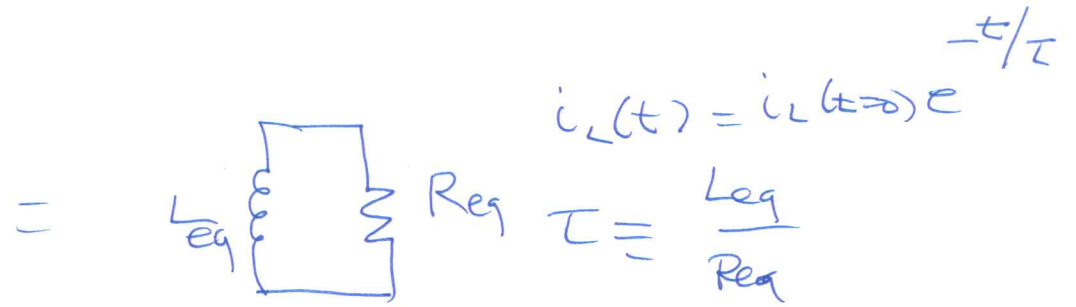
$$i_1(t) = -\frac{5}{3} \text{ A } e^{-\frac{t}{\frac{2}{3} \text{ ms}}}$$





$$L_{eq} = 2 \mu\text{H}$$

$$R_{eq} = (1 \text{ k}\Omega) \parallel (1 \text{ k}\Omega) \parallel (1 \text{ k}\Omega) = \frac{1}{3} \text{ k}\Omega$$

$$\Rightarrow \tau = \frac{2}{3} \text{ ms}$$

Example Impedance Problem

Find Z_{eq} for this circuit: (students)

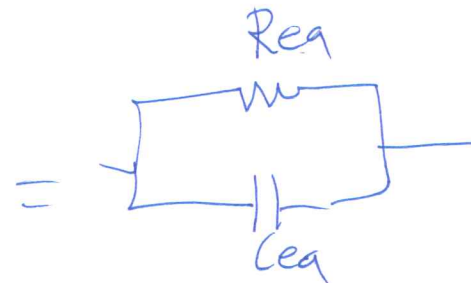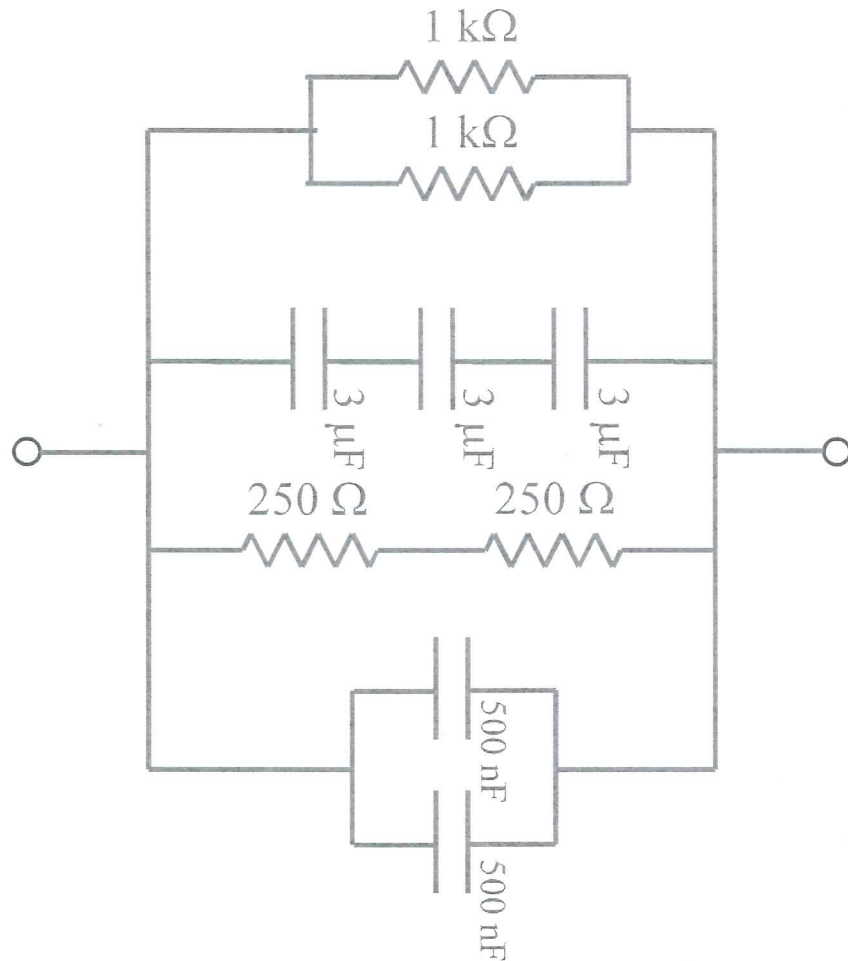

See slide #30

$$R_{eq} = 250\Omega$$

$$C_{eq} = 2\text{ nF}$$

$$\frac{1}{Z_{eq}} = \frac{1}{R_{eq}} + \frac{1}{1/j\omega C_{eq}}$$

$$\Rightarrow Z_{eq} = \frac{R_{eq} \cdot \frac{1}{j\omega C_{eq}}}{R_{eq} + \frac{1}{j\omega C_{eq}}} = \frac{R_{eq}}{1 + j\omega C_{eq} R_{eq}}$$