
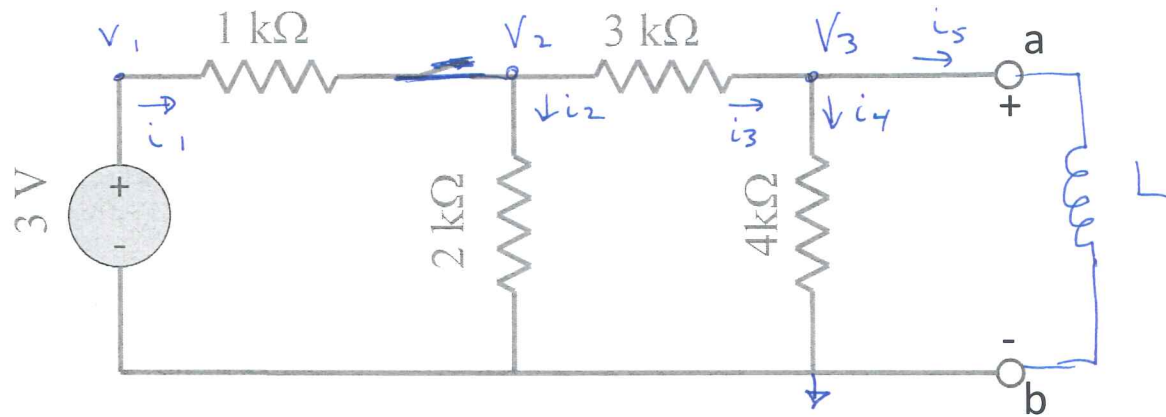


Comprehensive Example

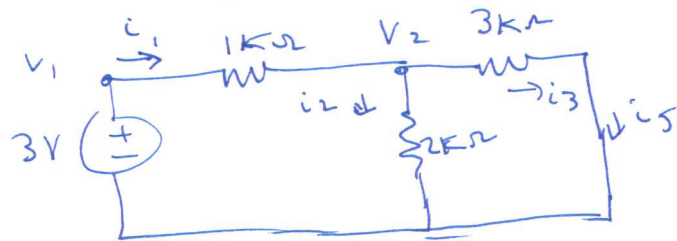

A) At DC, inductor is a short circuit. So we need to solve:



Note $V_3 = 0$
 $i_4 = 0$
 $i_3 = i_5$

$$i_1 = \frac{3V}{1k\Omega + (2k\Omega \parallel 3k\Omega)} = \frac{3}{1 + \frac{2 \cdot 3}{2+3}} \text{ mA} = \frac{3}{1 + \frac{6}{5}} \text{ mA} = \frac{3}{\frac{11}{5}} \text{ mA} = \frac{15}{11} \text{ mA}$$


$$i_2 = i_1 \frac{3}{2+3} = \frac{15}{11} \frac{3}{5} = \frac{9}{11} \text{ mA}$$

$$i_3 = i_1 \frac{2}{2+3} = \frac{15}{11} \frac{2}{5} \text{ mA} = \frac{6}{11} \text{ mA}$$


$$V_1 = 3V$$

$$V_2 = 3V - \frac{i_1 \cdot 1k\Omega}{1} = 3V - \frac{15}{11} V = \frac{33-15}{11} V = \frac{18}{11} V$$


Comprehensive Example

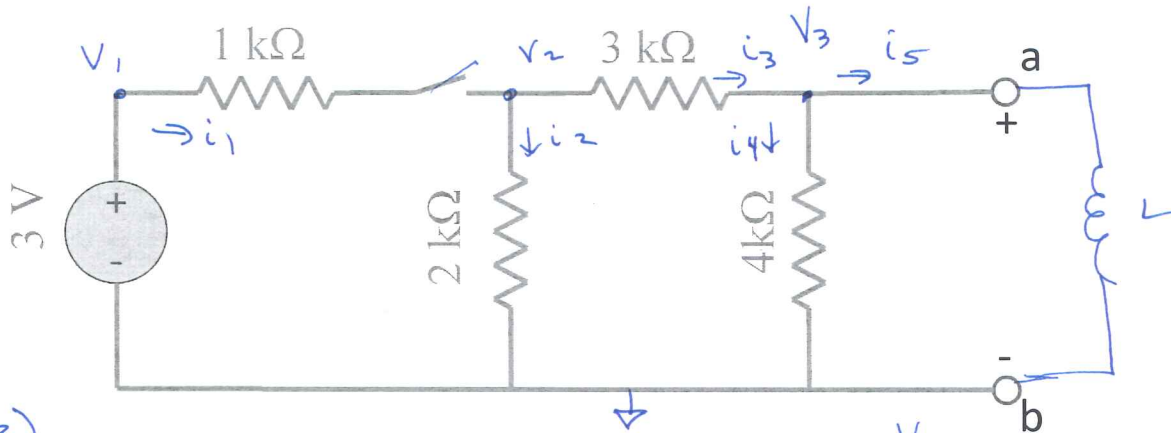

B)

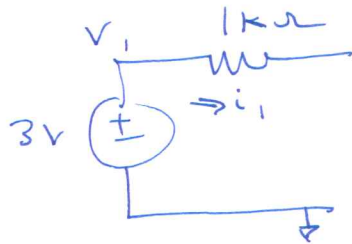

$$V_1 = 3V \quad i_1 = 0$$

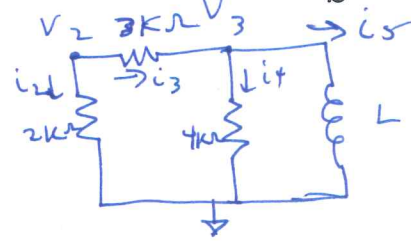

$$-t/\tau$$

$$\begin{aligned} \tau &= \frac{L}{R_{eq}} = \frac{L}{4 \parallel (2+3) k\Omega} \\ &= \frac{L}{\frac{4.5}{4+5} k\Omega} \\ &= \frac{9L}{20 k\Omega} \end{aligned}$$

$$i_5 = i_L(t) = i_L(t=0) e^{-t/\tau}$$

$$i_L(t=0) = \frac{6}{11} \text{ mA from last slide.} \Rightarrow i_5(t) = \frac{6}{11} \text{ mA} e^{-t/\tau}$$

$$+i_3 = i_5 \frac{4}{4 + (2+3)} \Rightarrow i_3(t) = \frac{4 \times 6}{9 \times 11} e^{-t/\tau} \text{ mA} = \frac{24}{99} e^{-t/\tau} \text{ mA}$$

$$i_2(t) = -i_3(t)$$

$$i_4(t) = -i_5(t) \frac{2+3}{4+2+3} = -\frac{5}{7} \times \frac{6}{11} e^{-t/\tau} \text{ mA} = -\frac{30}{77} e^{-t/\tau} \text{ mA}$$

$$V_2(t) = i_2(t) 2k\Omega = -\frac{24}{99} \times 2 e^{-t/\tau} \text{ V} = -\frac{48}{99} e^{-t/\tau} \text{ V}$$

$$V_3(t) = 4k\Omega i_4(t) = -\frac{120}{77} e^{-t/\tau} \text{ V}$$