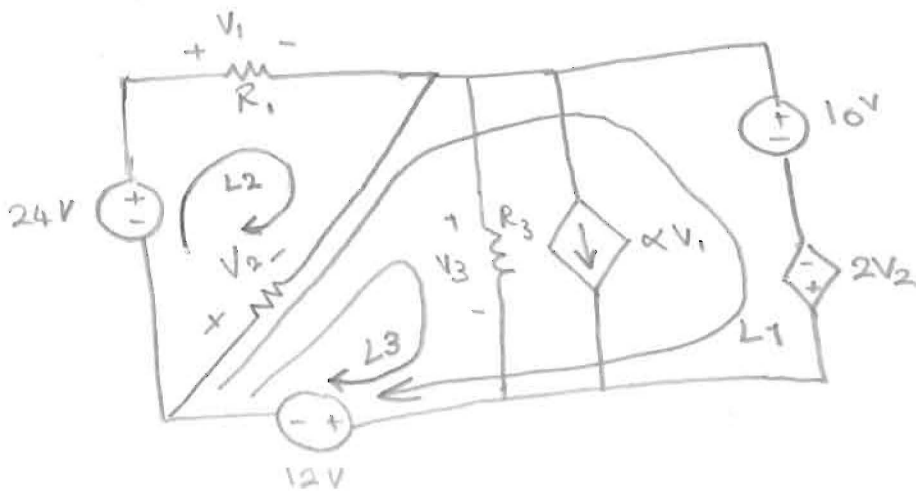


example 1

find $V_1 - V_3$



KVL

$$L_1: V_2 + 10V - 2V_2 + 12V = 0 \Rightarrow V_2 = 22V$$

$$L_2: -24V + V_1 - V_2 = 0$$

$$-24V + V_1 - 22V = 0 \Rightarrow V_1 = 46V$$


$$L_3: V_2 + V_3 + 12V = 0$$

$$22V + V_3 + 12V = 0 \Rightarrow V_3 = -34V$$

Example 2 :

- Find i_1 , i_3 and v_1 , v_3

- Show that $\sum P = 0$

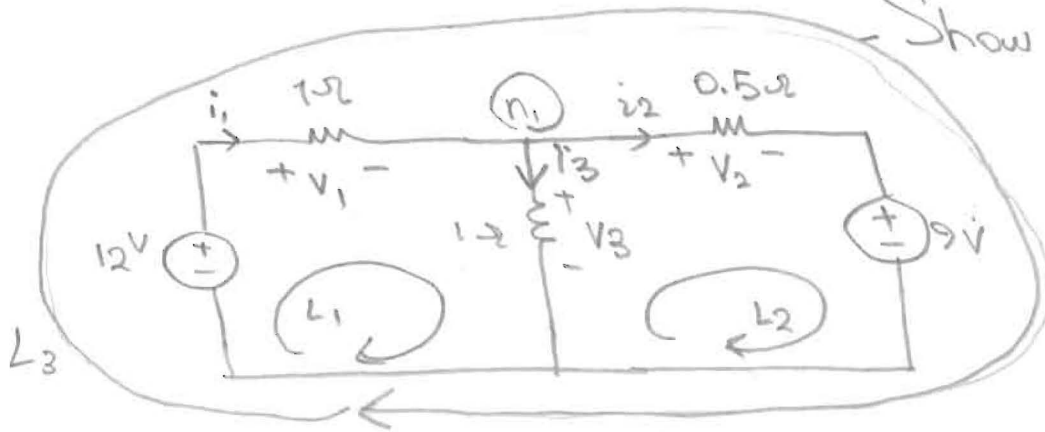

$$\text{KVL} = \begin{cases} L_1 : & -12V + V_1 + V_3 = 0 & (1) \\ L_2 : & -V_3 + V_2 + 9V = 0 & (2) \end{cases}$$

$L_3 : -12V + V_1 + V_2 + 9V = 0 \Rightarrow$ This is the sum of (1) & (2) \Rightarrow not an independent equation.

$$\text{KCL } (n_1) : \begin{matrix} i_3 + i_2 - i_1 = 0 \\ \downarrow \quad \downarrow \quad \downarrow \\ \frac{V_3}{R_3} + \frac{V_2}{R_2} - \frac{V_1}{R_1} = 0 \end{matrix} \Rightarrow \frac{V_3}{1\Omega} + \frac{V_2}{0.5\Omega} - \frac{V_1}{1\Omega} = 0$$

$$V_3 + 2V_2 - V_1 = 0 \quad (3)$$

$$\begin{cases} V_1 + V_3 = 12V & (1) \\ V_2 - V_3 = -9V & (2) \\ V_3 + 2V_2 - V_1 = 0 & (3) \end{cases} \Rightarrow \begin{cases} V_1 = 4.5V \\ V_2 = -1.5V \\ V_3 = 7.5V \end{cases}$$

$$* \sum P :$$

$$\left\{ \begin{array}{l} V_1 = 4.5 \text{ v} \\ i_1 = \frac{4.5 \text{ v}}{1 \Omega} = 4.5 \text{ A} \end{array} \right. \Rightarrow P_1 = V_1 \cdot i_1 = 20.25 \text{ w Sink}$$

$$\left\{ \begin{array}{l} V_2 = -1.5 \text{ v} \\ i_2 = \frac{V_2}{R_2} = \frac{-1.5 \text{ v}}{0.5 \Omega} = -3 \text{ A} \end{array} \right. \Rightarrow P_2 = V_2 \cdot i_2 = 4.5 \text{ w Sink}$$

$$\left\{ \begin{array}{l} V_3 = 7.5 \text{ v} \\ i_3 = \frac{V_3}{R_3} = \frac{7.5 \text{ v}}{1 \Omega} = 7.5 \text{ A} \end{array} \right. \Rightarrow P_3 = i_3 \cdot V_3 = 56.25 \text{ w Sink}$$



$$12 \text{ v Source} : P_5 = V_5 \cdot i_5 = 12 \text{ v} \times (-4.5 \text{ A}) = -54 \text{ w Source}$$

$$9 \text{ v Source} : P_6 = V_6 \cdot i_2 = 9 \text{ v} \times (-3 \text{ A}) = -27 \text{ w Source}$$

$$\sum P = 20.25 \text{ w} + 4.5 \text{ w} + 56.25 \text{ w} - 54 - 27 = 0$$

Example 3 :

— find i_1 A

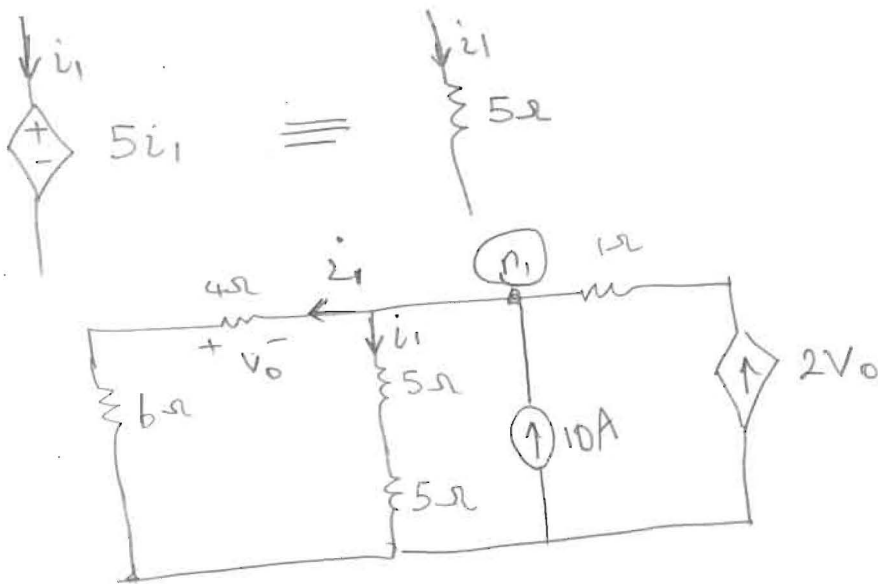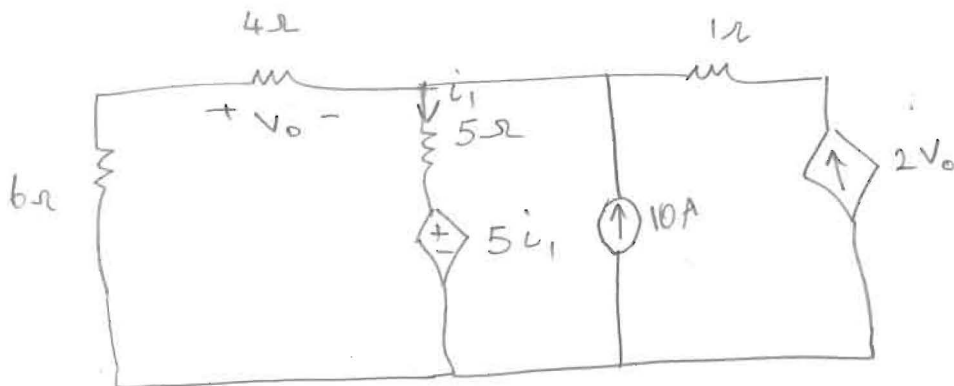

KCL at (n_1) :


$$i_1 + i_1 - 10A - 2V_o = 0 \Rightarrow 2i_1 - 2V_o = 10A$$

$$V_o = -i_1 \times 4\Omega = -4i_1$$

$$2i_1 - 2 \times (-4i_1) = 10A \Rightarrow 2i_1 + 8i_1 = 10A \Rightarrow \underline{i_1 = 1A}$$

Example 4 : $+ V_x -$

- find V_x

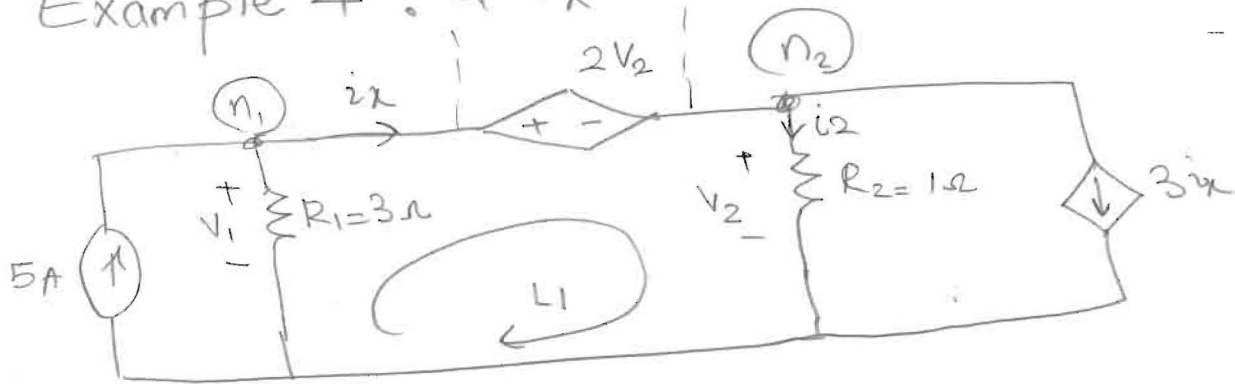

KCL

$$\left. \begin{array}{l} n_1: \quad i_x + i_1 = 5A \quad (1) \\ n_2: \quad 3i_x + i_2 = i_x \quad (2) \end{array} \right\}$$

KVL @ L_1 : $-V_1 + 2V_2 + V_2 = 0$

$$V_1 = 3V_2$$

↓ ↓

$$R_1 i_1 = 3 \times R_2 i_2$$

$$3\Omega \times i_1 = 3 \times 1\Omega \times i_2 \Rightarrow i_1 = i_2$$


$$(1) \quad i_x + i_1 = 5A \rightsquigarrow \begin{cases} i_x + i_2 = 5A \\ (2) \quad i_2 - 2i_x = 0 \end{cases} \Rightarrow \begin{cases} i_2 = \frac{10}{3} A \\ i_1 = \frac{10}{3} A \end{cases}$$

$$R_2 = i_2 \cdot R_2 = \frac{10}{3} A \times 1\Omega = \frac{10}{3} V$$

$$V_x = 2V_2 = 2 \times \frac{10}{3} V = \frac{20}{3} V$$

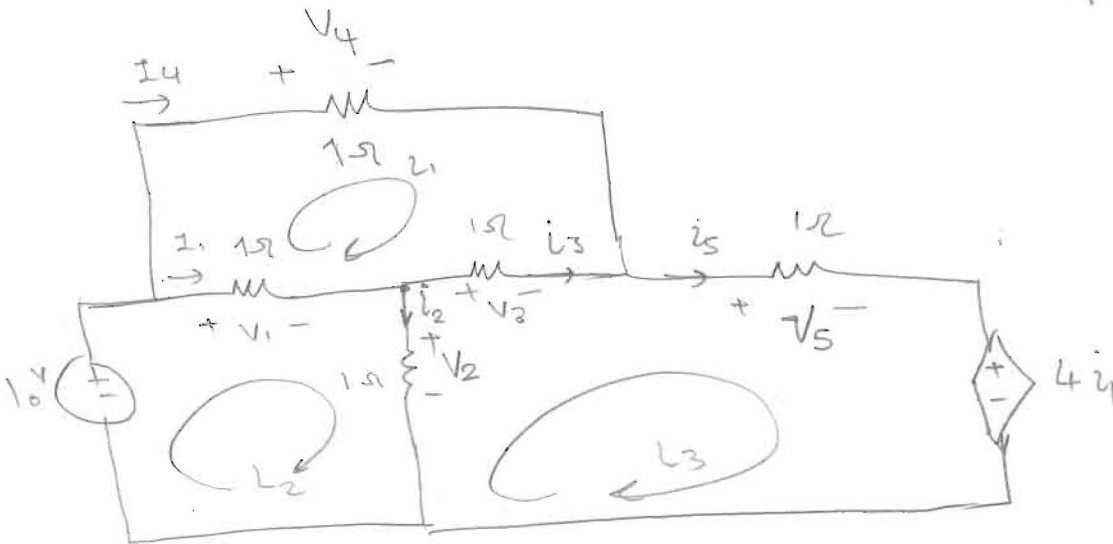Example 5 :

Find 5 independent equations for $V_1 - V_5$



$$\begin{cases} i_2 + i_3 - i_1 = 0 & (1) \\ i_5 - i_3 - i_4 = 0 & (2) \end{cases}$$

$$L_1: V_4 - V_3 - V_1 = 0 \quad (3)$$

$$L_2: -10V + V_1 + V_2 = 0 \quad (4)$$

$$L_3: -V_2 + V_3 + V_5 + 4i_1 = 0 \quad (5)$$

$$i_1 = \frac{V_1}{1\Omega}, \quad i_2 = \frac{V_2}{1\Omega}, \quad i_3 = \frac{V_3}{1\Omega}, \quad i_4 = \frac{V_4}{1\Omega}, \quad i_5 = \frac{V_5}{1\Omega}$$

$$\begin{array}{l} (1) \rightarrow \\ (2) \rightarrow \\ (3) \rightarrow \\ (4) \rightarrow \\ (5) \rightarrow \end{array} \left\{ \begin{array}{l} V_2 + V_3 - V_1 = 0 \\ V_5 - V_3 - V_4 = 0 \\ V_4 - V_3 - V_1 = 0 \\ V_1 + V_2 = 10V \\ 4V_1 + V_3 + V_5 - V_2 = 0 \end{array} \right.$$