

Given  $u = \frac{A + jB}{C + jD}$  and  $A, B, C, D$  are all real. ①

1) Express  $u$  in the form  $x + jy$   
 $re^{j\phi}$   
 $r < \phi$

2) Find  $\operatorname{Re}(u)$   
 $\operatorname{Im}(u)$

3) Find  $\operatorname{Re}(ue^{j\omega t})$

Trick: Whenever denominator has complex #, multiply entire expression by the complex conjugate over itself. (2)

$$u = \frac{A + jB}{C + jD} \cdot \frac{C - jD}{C - jD} = \frac{(A + jB)(C - jD)}{C^2 + \cancel{jCD} - \cancel{jCD} + (jD)(-jD)}$$

$$= \frac{(A + jB)(C - jD)}{C^2 + D^2} = \frac{AC + jBC - jAD + (jB)(-jD)}{C^2 + D^2}$$

$$= \frac{AC + BD}{C^2 + D^2} + j \frac{BC - AD}{C^2 + D^2} \quad \checkmark \text{ form is } x + jy$$

$$r = \sqrt{x^2 + y^2} = \sqrt{\left(\frac{AC + BD}{C^2 + D^2}\right)^2 + \left(\frac{BC - AD}{C^2 + D^2}\right)^2}$$

$$\phi = \tan^{-1} \frac{y}{x} = \tan^{-1} \frac{BC - AD}{C^2 + D^2}$$

$$u = \sqrt{\left(\frac{AC + BD}{C^2 + D^2}\right)^2 + \left(\frac{BC - AD}{C^2 + D^2}\right)^2} e^{j \tan^{-1} \left(\frac{BC - AD}{C^2 + D^2}\right)} \quad \checkmark \text{ form } r e^{j\phi}$$

$$u = \sqrt{\left(\frac{AC + BD}{C^2 + D^2}\right)^2 + \left(\frac{BC - AD}{C^2 + D^2}\right)^2} \angle \tan^{-1} \left(\frac{BC - AD}{C^2 + D^2}\right) \quad \checkmark \text{ form } r \angle \phi$$

$$\operatorname{Re}(u) = \frac{AC+BD}{C^2+D^2} \quad \checkmark$$

$$\operatorname{Im}(u) = \frac{BC-AD}{C^2+D^2} \quad \checkmark$$


$$\operatorname{Re}[ue^{j\omega t}] = \operatorname{Re}[re^{j\phi}e^{j\omega t}] = r \operatorname{Re}[e^{j(\phi+\omega t)}]$$

$$\stackrel{\text{Euler}}{=} r \operatorname{Re}[\cos(\omega t + \phi) + j \sin(\omega t + \phi)] = r \cos(\omega t + \phi)$$


$$= \sqrt{\left(\frac{AC+BD}{C^2+D^2}\right)^2 + \left(\frac{BC-AD}{C^2+D^2}\right)^2} \cos\left[\omega t + \tan^{-1}\left(\frac{BC-AD}{AC+BD}\right)\right] \quad \checkmark$$

Find all currents, voltages in this circuit

$$v(t) = V_0 \cos(\omega t + 45^\circ)$$

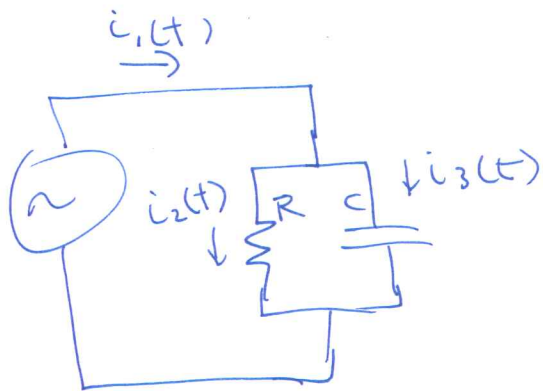

=

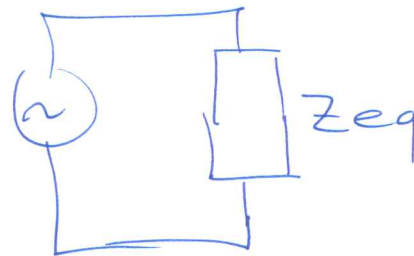

Soln: All voltages same. For  $i_1(t)$ :

$$Z_{eq}^{-1} = Z_1^{-1} + Z_2^{-1} = \frac{1}{R} + j\omega C = \frac{1 + j\omega RC}{R}$$

$$= \frac{1 + j\omega \tau}{R}$$

$$i_1(t) \Rightarrow V(t) \rightarrow V \rightarrow \underline{I} = \frac{V}{Z_{eq}} \rightarrow i_1(t) \Rightarrow Z_{eq} = \frac{R}{1 + j\omega \tau}$$

$$V = V_0 e^{j45^\circ} = V_0 e^{j\frac{\pi}{4}}$$

$$\underline{I} = \frac{V_0 e^{j\frac{\pi}{4}}}{R / (1 + j\omega \tau)} = \frac{V_0}{R} e^{j\frac{\pi}{4}} (1 + j\omega \tau)$$

$$i_1(t) = \text{Re}[\underline{I} e^{j\omega t}] = \text{Re}\left[\frac{V_0}{R} e^{j\frac{\pi}{4}} (1 + j\omega \tau) e^{j\omega t}\right] = \frac{V_0}{R} \text{Re}\left[e^{j\frac{\pi}{4}} (1 + j\omega \tau) e^{j\omega t}\right]$$

||

$$\begin{aligned} &= \frac{V_0}{R} \operatorname{Re} \left[ e^{j\left(\frac{\pi}{4} + \omega t\right)} (1 + j\omega\tau) \right] \quad \underline{\text{Euler}} \\ &= \frac{V_0}{R} \operatorname{Re} \left[ \cos\left(\frac{\pi}{4} + \omega t\right) + j \sin\left(\frac{\pi}{4} + \omega t\right) \right] [1 + j\omega\tau] \\ &= \frac{V_0}{R} \left[ \cos\left(\frac{\pi}{4} + \omega t\right) - \omega\tau \sin\left(\frac{\pi}{4} + \omega t\right) \right] = i_1(t) \end{aligned}$$