

1	2	3	4	5	6	Total
/10	/10	/10	/25	/20	/25	/100

**DO NOT BEGIN THE EXAM
UNTIL YOU ARE TOLD TO
DO SO.**

PROBLEM ONE: (20 points)

The differential equation that describes the voltage in an *RLC* network is

$$\frac{d^2v}{dt^2} + 5\frac{dv}{dt} + 4v = 0$$

Given that $v(0) = 0$, $dv(0)/dt = 10$ obtain $v(t)$.

Use the mathematical tools you learned for analyzing linear RLC circuits: First, find $s_{1,2}$ for the general solution, then decide whether it is under damped or overdamped, then find the constants and hence $v(t)$ from the initial values.

PROBLEM TWO:

State and describe Thevenin's Theorem.

State and describe Norton's Theorem.


PROBLEM THREE:

Describe the concept of transient response and of linear RLC circuits.

Describe the concept of steady state response and of linear RLC circuits.

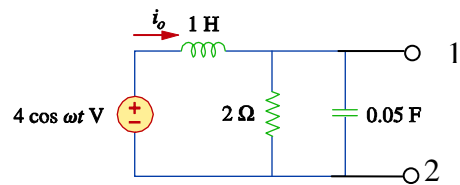
PROBLEM FOUR:

Using Phasors, find the Thevenin equivalent voltage V_{Th} and impedance Z_{Th} at terminals 1-2 of the circuits shown below. (You need not simplify your result.)



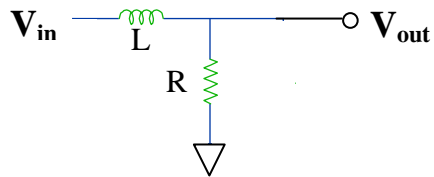PROBLEM FIVE:

Using Phasors, find $V_{\text{out}}/V_{\text{in}}$ for the circuit below. Sketch the magnitude of $V_{\text{out}}/V_{\text{in}}$ vs. frequency.



PROBLEM SIX:

Determine $i(t)$ for $t > 0$ in the circuit below.

