

1	2	3	4	5	Total
/20	/20	/20	/20	/20	/100


**DO NOT BEGIN THE EXAM
UNTIL YOU ARE TOLD TO
DO SO.**

PROBLEM ONE: (20 points)

In a certain application, the circuit in the figure below must be designed to meet these two criteria:

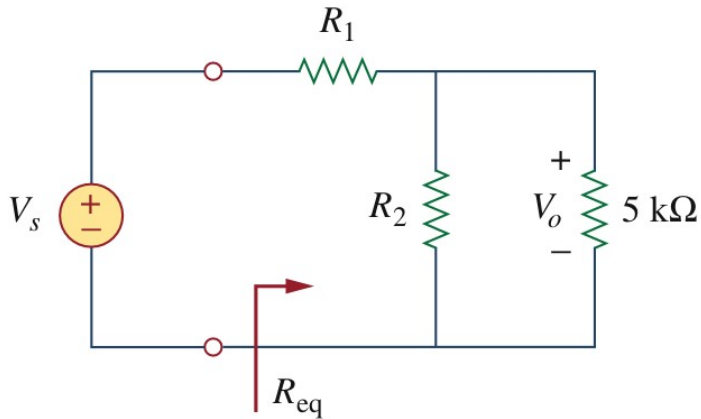(a) $V_o / V_s = 0.05$ (b) $R_{eq} = 40 \text{ k}\Omega$

If the load resistor $5 \text{ k}\Omega$ is fixed, find R_1 and R_2 to meet the criteria.




PROBLEM TWO:

A load is connected to a network. At the terminals to which the load is connected, $R_{Th} = 10 \Omega$ and $V_{Th} = 40 \text{ V}$. Find the maximum possible power supplied to the load.

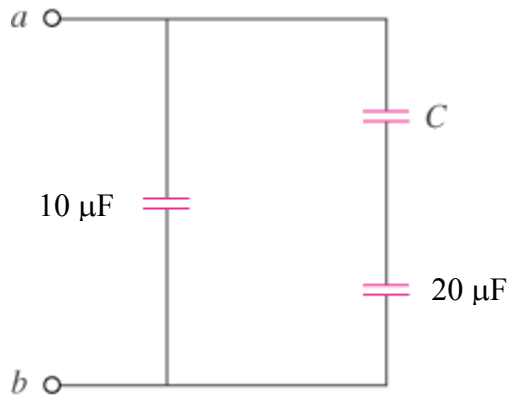
PROBLEM THREE:

The equivalent capacitance at terminals a - b in the circuit in the figure below is $20 \mu\text{F}$. Calculate the value of C .



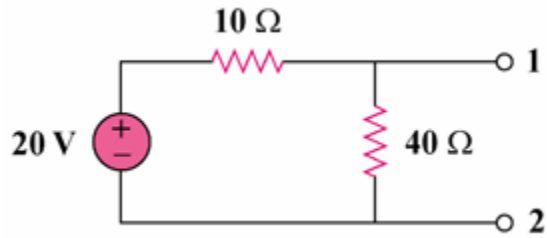
PROBLEM FOUR:

Determine R_{Th} and V_{Th} at terminals 1-2 of the circuits shown below.



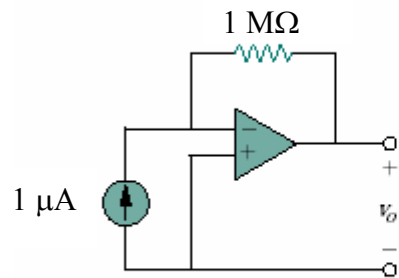PROBLEM FIVE:

Obtain v_o for the op amp circuit shown below.



EECS70A / CSE 70A Network Analysis I
Prof. Peter Burke

Midterm II solution

Grading criteria: for all questions, no credits for answers without units and -5pts for each wrong unit.

Problem 1:

Criteria: (a) $V_o / V_s = 0.05$ and (b) $R_{eq} = 40 \text{ k}\Omega$

From the circuit, $R_{eq} = R_1 + R_2 \parallel 5 \text{ k}\Omega = 40 \text{ k}\Omega$

Using voltage divider: $V_o = V_s \cdot (R_2 \parallel 5 \text{ k}\Omega) / (R_1 + R_2 \parallel 5 \text{ k}\Omega)$

$$V_o / V_s = (R_2 \parallel 5 \text{ k}\Omega) / (R_1 + R_2 \parallel 5 \text{ k}\Omega) = 0.05$$

$$(R_2 \parallel 5 \text{ k}\Omega) = 0.05 \times 40 \text{ k}\Omega = 2 \text{ k}\Omega$$

$$(R_2 \times 5 \text{ k}\Omega) / (R_2 + 5 \text{ k}\Omega) = 2 \text{ k}\Omega$$

$$R_2 = 0.4 R_2 + 2 \text{ k}\Omega$$

$$\therefore R_2 = 3.3 \text{ k}\Omega$$

$$\therefore R_1 = 40 \text{ k}\Omega - R_2 \parallel 5 \text{ k}\Omega = 38 \text{ k}\Omega$$

Grading criteria: -5pts for every incorrect equation
-2pts for each wrong substitution
-2pts for wrong final answers

Problem 2:

To have maximum possible power supplied to the load, $R_{Th} = R_L = 10\Omega$

$$W_{max} = V_{Th}^2 / 4R_{Th} = (40)^2 / (4 \times 10) = 40 \text{ W}$$

Grading criteria: -5pts for incorrect equation
-5pts for wrong R_L
-5pts for wrong substitutions
-2pts for wrong final answer

Problem 3:

$$10 \text{ F} + 1 / (1/C + 1/20 \text{ F}) = 20 \text{ F}$$

$$1/C + 1/20 \text{ F} = 1/10\mu\text{F}$$

EECS70A / CSE 70A Network Analysis I
Prof. Peter Burke

Midterm II solution

Grading criteria: for all questions, no credits for answers without units and -5pts for each wrong unit.

Problem 1:

Criteria: (a) $V_o / V_s = 0.05$ and (b) $R_{eq} = 40 \text{ k}\Omega$

From the circuit, $R_{eq} = R_1 + R_2 \parallel 5 \text{ k}\Omega = 40 \text{ k}\Omega$

Using voltage divider: $V_o = V_s \cdot (R_2 \parallel 5 \text{ k}\Omega) / (R_1 + R_2 \parallel 5 \text{ k}\Omega)$

$$V_o / V_s = (R_2 \parallel 5 \text{ k}\Omega) / (R_1 + R_2 \parallel 5 \text{ k}\Omega) = 0.05$$

$$(R_2 \parallel 5 \text{ k}\Omega) = 0.05 \times 40 \text{ k}\Omega = 2 \text{ k}\Omega$$

$$(R_2 \times 5 \text{ k}\Omega) / (R_2 + 5 \text{ k}\Omega) = 2 \text{ k}\Omega$$

$$R_2 = 0.4 R_2 + 2 \text{ k}\Omega$$

$$\therefore R_2 = 3.3 \text{ k}\Omega$$

$$\therefore R_1 = 40 \text{ k}\Omega - R_2 \parallel 5 \text{ k}\Omega = 38 \text{ k}\Omega$$

Grading criteria: -5pts for every incorrect equation
-2pts for each wrong substitution
-2pts for wrong final answers

Problem 2:

To have maximum possible power supplied to the load, $R_{Th} = R_L = 10\Omega$

$$W_{max} = V_{Th}^2 / 4R_{Th} = (40)^2 / (4 \times 10) = 40 \text{ W}$$

Grading criteria: -5pts for incorrect equation
-5pts for wrong R_L
-5pts for wrong substitutions
-2pts for wrong final answer

Problem 3:

$$10 \text{ F} + 1 / (1/C + 1/20 \text{ F}) = 20 \text{ F}$$

$$1/C + 1/20 \text{ F} = 1/10\mu\text{F}$$