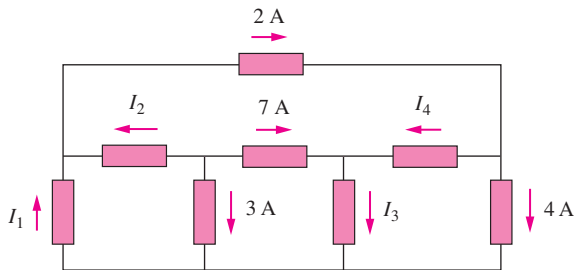


1	2	3	4	5	5	Total
/20	/20	/10	/10	/20	/20	/100

**DO NOT BEGIN THE EXAM
UNTIL YOU ARE TOLD TO
DO SO.**


PROBLEM ONE: (20 points)

For the circuit in below, use KCL to find the branch currents I_1 to I_4 .



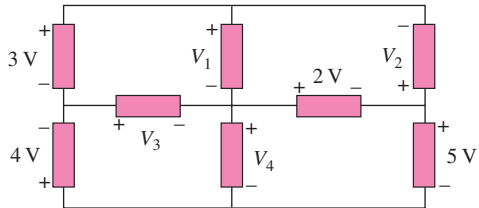
PROBLEM TWO(20 points):


Given the circuit below, use KVL to find the branch voltages V_1 to V_4 .



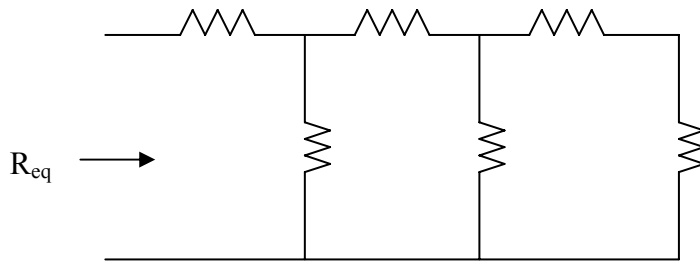PROBLEM THREE(10 points):

All resistors in the figure below are $1\ \Omega$ each. Find R_{eq} .



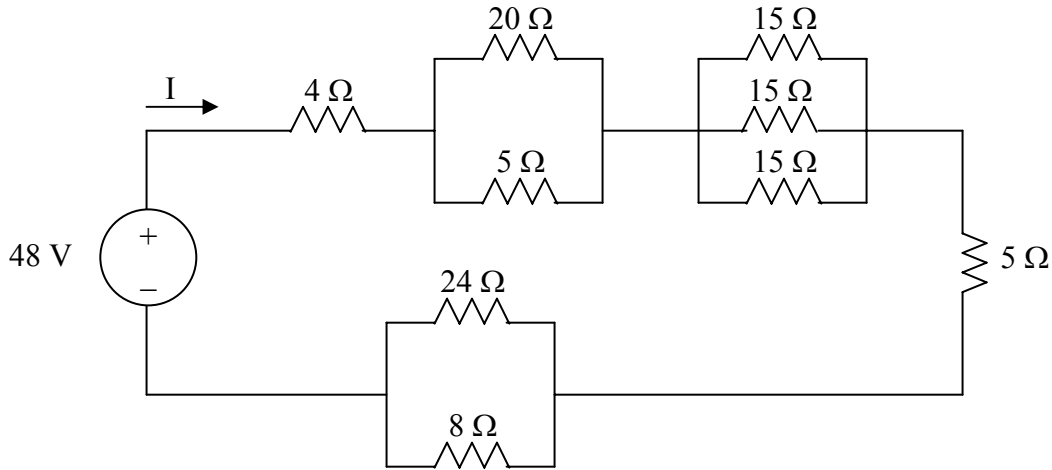
PROBLEM FOUR(10 points):Find I in the circuit of the figure below.

PROBLEM FIVE (20 points):

In a certain application, the circuit in the figure below must be designed to meet these two criteria:

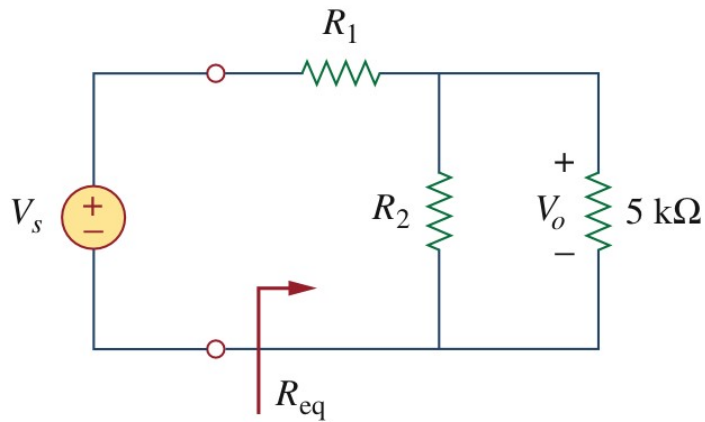- (a) $V_o / V_s = 0.05$ (b) $R_{eq} = 40 \text{ k}\Omega$


If the load resistor $5 \text{ k}\Omega$ is fixed, find R_1 and R_2 to meet the criteria.



PROBLEM SIX(20 points):


(Brain teaser).

Find R_{ab} for the circuit below.

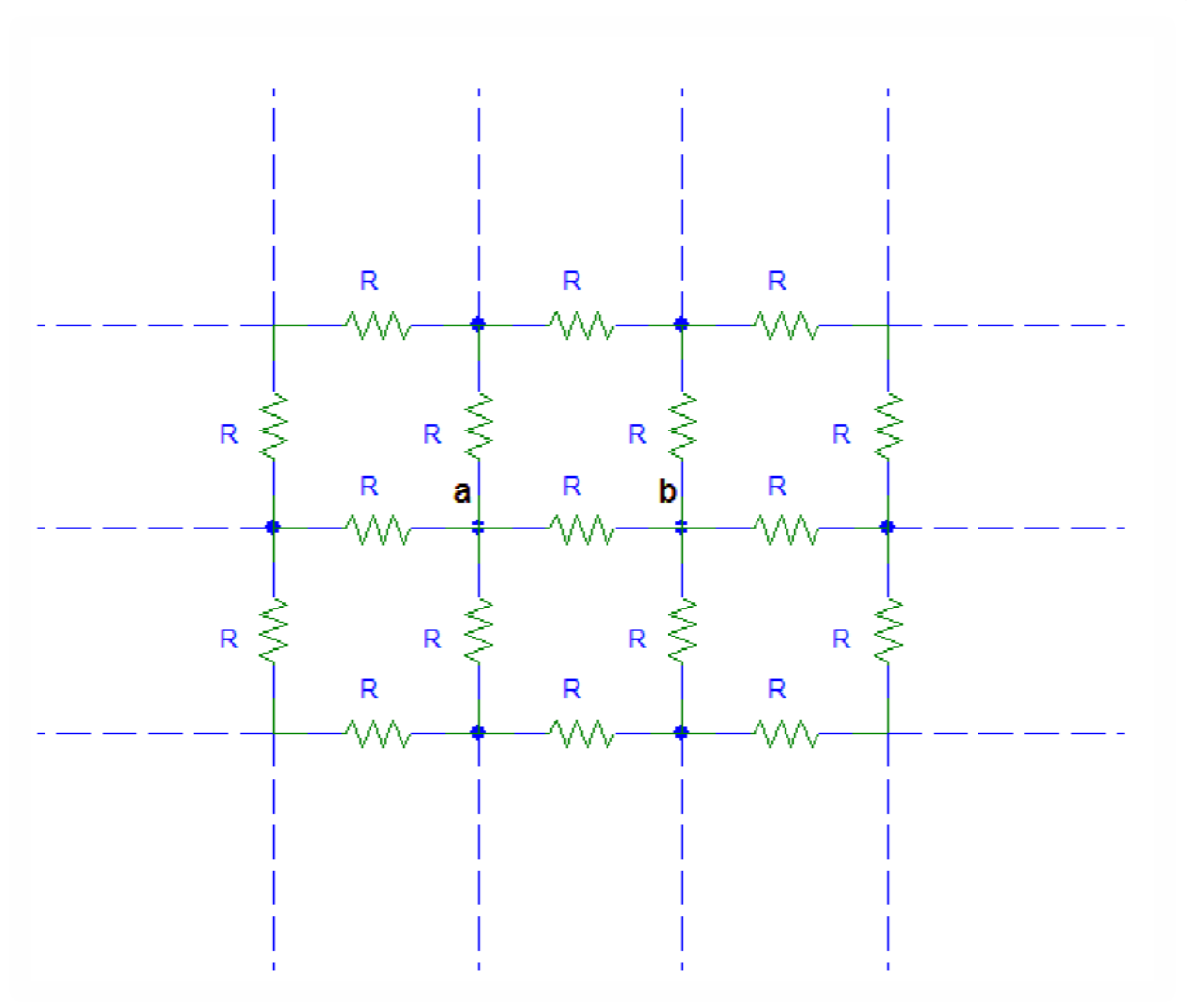

Midterm 1 Solutions

1.

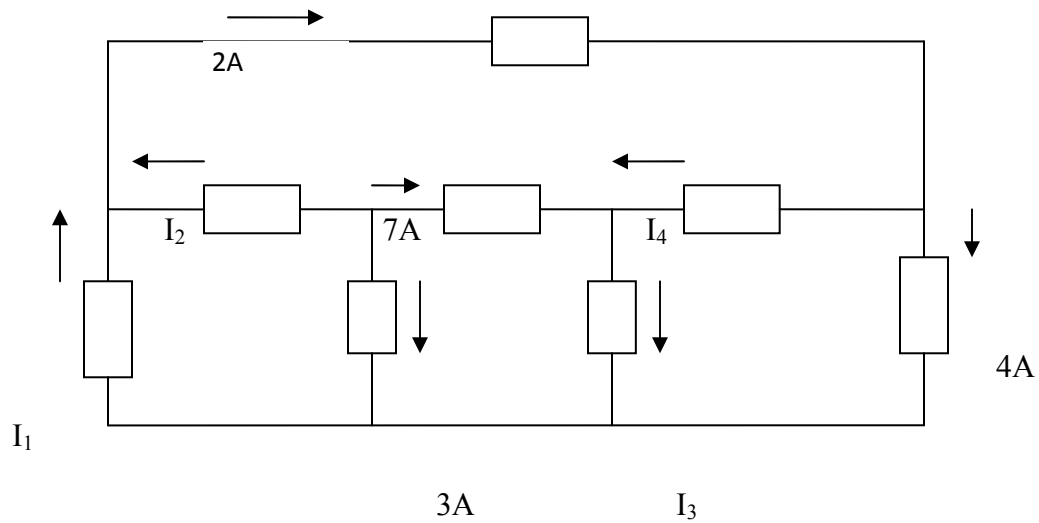

At node 2,

$$3 + 7 + I_2 = 0 \quad \longrightarrow \quad I_2 = -10A$$

At node 1,

$$I_1 + I_2 = 2 \quad \longrightarrow \quad I_1 = 2 - I_2 = 12A$$

At node 4,

$$2 = I_4 + 4 \quad \longrightarrow \quad I_4 = 2 - 4 = -2A$$

At node 3,

$$7 + I_4 = I_3 \quad \longrightarrow \quad I_3 = 7 - 2 = 5A$$


Hence,

$$\underline{I_1 = 12A, \quad I_2 = -10A, \quad I_3 = 5A, \quad I_4 = -2A}$$

Grading : “5” points for each node.

a. “1” point each sign/value of the current in each node.

2.

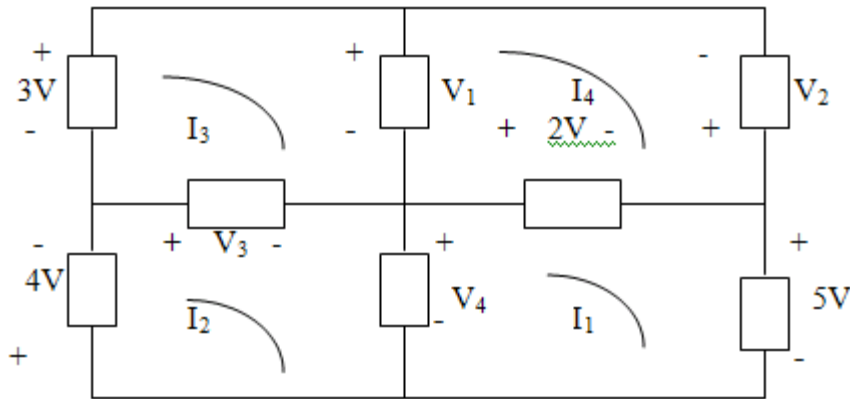

For mesh 1,

$$-V_4 + 2 + 5 = 0 \longrightarrow V_4 = 7V$$

For mesh 2,

$$+4 + V_3 + V_4 = 0 \longrightarrow V_3 = -4 - 7 = -11V$$

For mesh 3,

$$-3 + V_1 - V_3 = 0 \longrightarrow V_1 = V_3 + 3 = -8V$$

For mesh 4,

$$-V_1 - V_2 - 2 = 0 \longrightarrow V_2 = -V_1 - 2 = 6V$$

Thus,

$$\underline{V_1 = -8V, \quad V_2 = 6V, \quad V_3 = -11V, \quad V_4 = 7V}$$

Grading : “5” points for each mesh.

a. “1” point each sign/value of the voltage in each mesh.

3.

Starting from far right side of the network:

1. 1 & 1 in series resulting in 2 ohms.
2. 2 & 1 are in parallel resulting in $2/3$ ohm.
3. $2/3$ and 1 in series resulting in $5/3$ ohm.
4. $5/3$ and 1 in parallel resulting in $5/8$ ohm.
5. $5/8$ and 1 in series resulting in Req as:


$$R_{eq} = 1 + 1/(1 + 1/2) = 1 + 1/(1 + 2/3) = 1 + 1/5/3 = \underline{\underline{1.625 \Omega}}$$

Grading: “2” points each part.


If you did Delta-Y:

“2” points for each part in the picture below.

$Y \rightarrow \Delta$:

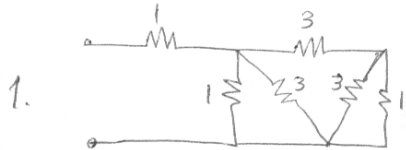


$$1 \parallel 3 = \frac{3}{4} \Omega$$

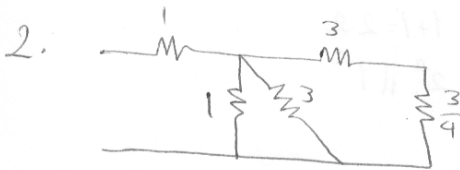


$$3 + \frac{3}{4} = \frac{15}{4} \Omega$$
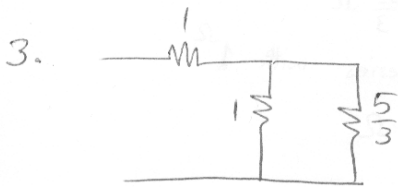
$$\frac{15}{4} \parallel 3 = \frac{5}{3} \Omega$$


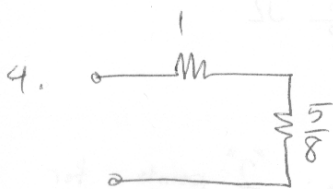
$$\frac{5}{3} \parallel 1 = \frac{5}{8} \Omega$$



Grading: $\frac{5}{8}$ points each part.

5. $R_{eq} = 1 + \frac{5}{8} = \frac{13}{8} \Omega$

4.

1. 5 in parallel with 20 resulting in 4 ohms.
2. 15 & 15 & 15 are all in parallel resulting in 5 ohms all together.
3. 24 and 8 in parallel resulting in 6 ohms.
4. All the above are in series with the 4ohms and 5ohms also resulting in Req as:

$$R_{eq} = 4 + 5 // 20 + \frac{1}{3} \times 15 + 5 + 24 // 8 = 4 + 4 + 5 + 5 + 6 = 24$$

5. $I = 48/24 = \underline{\underline{2 \text{ A}}}$

Grading: "2" points each part.

5.

Let R_1 and R_2 be in $k\Omega$.

$$R_{eq} = R_1 + R_2 \parallel 5 \quad (1)$$

$$\frac{V_o}{V_s} = \frac{5 \parallel R_2}{5 \parallel R_2 + R_1} \quad (2)$$

From (1) and (2), $0.05 = \frac{5 \parallel R_1}{40} \longrightarrow 2 = 5 \parallel R_2 = \frac{5R_2}{5 + R_2}$ or $R_2 = 3.333 k\Omega$

From (1), $40 = R_1 + 2 \longrightarrow R_1 = 38 k\Omega$

Thus **$R_1 = 38 k\Omega$, $R_2 = 3.333 k\Omega$**

Grading: “7” points for equation (1).

“5” points for coming up with the equation 2.

“3” points for equation in the third line above ending with $2 = 5 \parallel R_2$.

“5” points calculating R_2 and R_1 finally.

If you go with KVL:

“7” points again for equation (1).

“3” points for writing down the correct KVL.

“5” points to end up with the equation (2) after the KVL or something like that to use the V_o/V_s ratio.

“5” points to calculate both R_1 and R_2 finally.

6.

As it can be seen from the network, the equivalent resistance between node “a” and “b” is the combination of one resistor “R” (which connects node “a” to “b”) in parallel with the rest of the network. Therefore, the result for R_{ab} should be less than or equal to R.

Grading: “20” point for anything between “0” and “R”.

“10” points for any effort that leads to R_{ab} greater than “R”.

No point for blank paper!