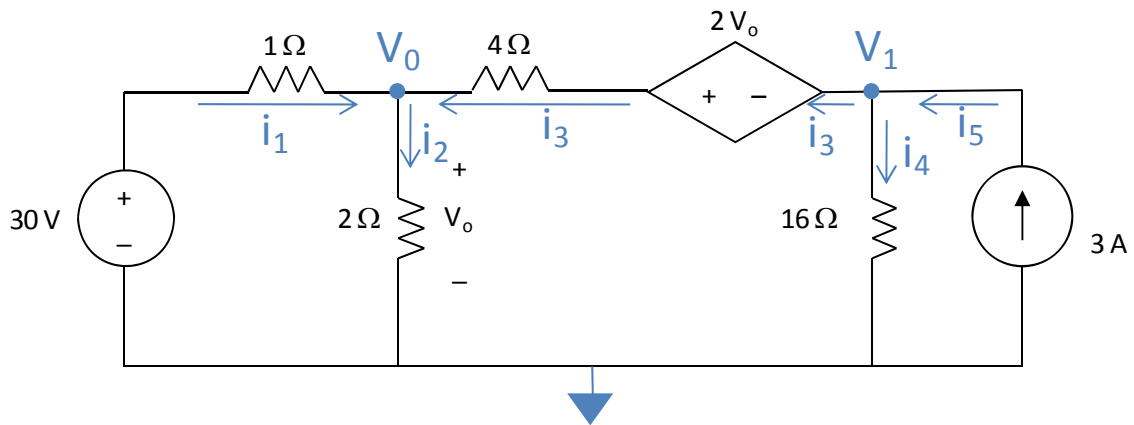


SOLUTIONS: Midterm #2

PROBLEM ONE: (40 points)

Use nodal analysis to find all the currents and voltages in this circuit.
Label your current and voltage definitions clearly!!!



At node 1 we get the equation,

$$i_1 + i_3 = i_2 \quad (1)$$

$$\left(\frac{30V - V_0}{1\Omega}\right) + \left(\frac{(V_1 + 2V_0) - V_0}{4\Omega}\right) = \left(\frac{V_0}{2\Omega}\right)$$

$$\left(\frac{30V}{1\Omega}\right) + \left(\frac{V_1}{4\Omega}\right) = \left(\frac{5V_0}{4\Omega}\right) \quad (2)$$

At node 2 we get the equation,

$$i_4 + i_3 = i_5 \quad (3)$$

$$\left(\frac{V_1}{16\Omega}\right) + \left(\frac{(V_1 + 2V_0) - V_0}{4\Omega}\right) = 3A$$

$$\left(\frac{5V_1}{16\Omega}\right) + \left(\frac{V_0}{4\Omega}\right) = 3A \quad (4) \quad (2)$$

With two equations, (1) and (2), and two variables, V_0 and V_1 , we can solve for their values and get $V_0 = 648/29 = 22.3V$ and $V_1 = -240/29 = -8.28V$. Solving for the currents we get

$$i_1 = \left(\frac{30V - V_0}{1\Omega} \right) = \frac{222}{29} = 7.655A$$

$$i_2 = \left(\frac{V_0}{2\Omega} \right) = \frac{324}{29} = 11.15A$$

$$i_3 = \left(\frac{(V_1 + 2V_0) - V_0}{4\Omega} \right) = \frac{102}{29} = 3.45A$$

$$i_4 = \left(\frac{V_1}{16\Omega} \right) = -\frac{15}{29} = -0.53A$$

$$i_5 = 3A$$

(3)

Problem 1 : Grading Criteria:

Maximum points:

6pts for correctly setting up the node equation (1)

6pts for correctly setting up the node equation (3)

4pts for i_1 (full credit if $7.0 < i_1 < 8.1$)4pts for i_2 (full credit if $10.0 < i_2 < 12.2$)4pts for i_3 (full credit if $3.1 < i_3 < 3.8$)4pts for i_4 (full credit if $-0.58 < i_4 < -0.48$)4pts for i_5 *Partial Credit for i 's above*

3pts partial credit for correct equation but wrong numerical answer

1pts partial credit for a mistake in the equation

4pts for V_0 (full credit if $20 < V_0 < 24$ and correct equation)

2pts partial credit fair attempt at solving

4pts for V_1 (full credit if $7.5 < V_1 < 9.1$ and correct equation)

2pts partial credit fair attempt at solving


PROBLEM ONE SPACE FOR WORK:**PROBLEM TWO (30 points):**

An attenuator is an interface circuit that reduces the voltage level without changing the output resistance.

- (a) By specifying R_s and R_p of the interface circuit in the figure below, design an attenuator that will meet the following requirements:


$$\frac{V_o}{V_g} = 0.125, \quad R_{eq} = R_{Th} = R_g = 100\Omega. \quad (\text{Note: } 0.125 = 1/8).$$

- (b) Using the interface designed in part (a), calculate the current through a load of $R_L = 50\Omega$ when $V_g = 12\text{ V}$.
- (c) What value of R_L achieves maximum power delivered to the load? Express your answer in Ω . In this case, what is the power (in Watts) delivered to the load?

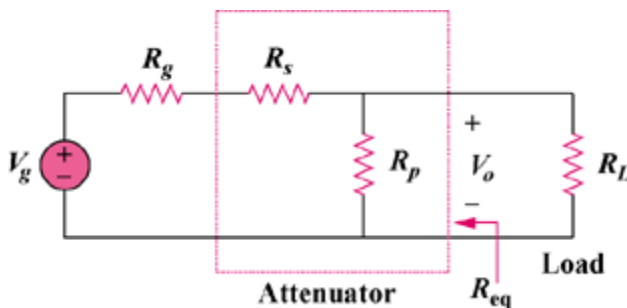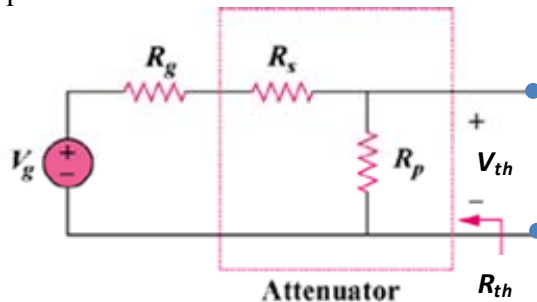**Solution:**

(a)

Finding the Thevenin equivalent of this circuit.



The equation for R_{th} is the equivalent resistance seen looking into the load-port when the voltage source, V_g , is set to zero. Also, it is given that $R_{th}=100\Omega$ thus giving

$$R_{th} = \frac{(R_g + R_s)R_p}{(R_g + R_s) + R_p} = \frac{(100\Omega + R_s)R_p}{(100\Omega + R_s) + R_p} = 100\Omega \quad (1)$$


The Thevenin equivalent voltage can be shown to be a voltage divider

$$V_{th} = V_g \frac{R_p}{(R_g + R_s) + R_p} = V_g \frac{R_p}{(100\Omega + R_s) + R_p}$$

$$\frac{V_{th}}{V_g} = 0.125 = \frac{R_p}{(100\Omega + R_s) + R_p} \quad (2)$$

Now we have two equations, (1) and (2), and two unknown variables, R_s and R_p which we can solve for to get $R_p=800/7=114.28\Omega$ and $R_s=700\Omega$.

(b)

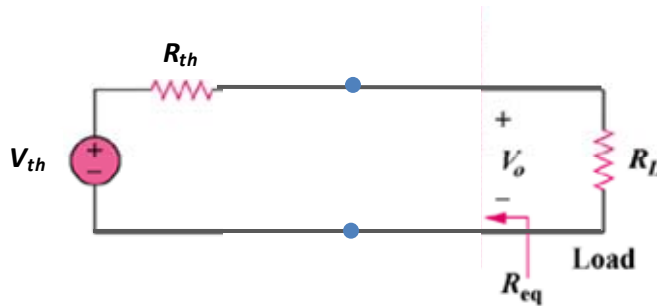

As given, $R_L=50$, $V_g=12V$, and $V_{th}=0.125V_g$, $R_{th}=100\Omega$ we get

$$i = \frac{V_{th}}{R_{th} + R_L} = \frac{0.125(12V)}{100\Omega + 50\Omega} = 0.01A \quad (3)$$

(c)

For maximum power delivery to the load resistor, $R_{L,max}=R_{th}=100\Omega$, (see pg 151 in textbook) and the corresponding power delivered to the load is



$$P_{max} = \frac{V_{th}^2}{4R_{th}} = \frac{(0.125(12V))^2}{4(100\Omega)} = 0.005625W \quad (4)$$

Problem 2: Grading Criteria:

- a) 16pts: 5pts for eq (1) R_{th} , 5pts for eq (2) V_{th} , 3pts for R_s (full credit if $630 < R_s < 770$), and 3pts for R_p (full credit if $103 < R_p < 125$).
 - a. 2pts credit for fair attempt at R_{th} , V_{th}
 - b. 1pt partial credit for fair attempt at R_s and R_p
- b) 6pts for the correct current through the load (full credit if $0.009 < i < 0.011$)
 - a. 2pts-3pts partial credit for fair attempt at load current
- c) 8pts: 4pts for correct $R_{L,max}$ and 4pts for correct P_{max} (full credit if $0.0051 < P_{max} < 0.0061$)
 - a. 2pts partial credit for fair attempt at P_{max}
 - b. 2pts partial credit for describing how to find $R_{L,max}$ for max power using derivatives.

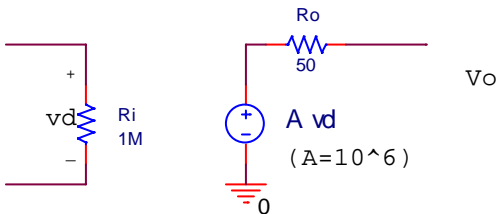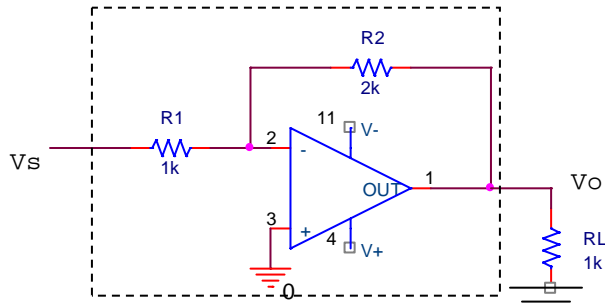PROBLEM THREE (30 points):

Consider the following inverting Op Amp circuit. The circuit model for the non-ideal Op Amp is also included below. The boxed region is to be represented using Thevenin equivalent circuit. Find an algebraic expression for V_{th} and R_{th} in terms of A , V_s , R_1 , R_2 , R_i , R_o . Then find numerical result for V_{th} and R_{th} in terms of V_s . Hint: Replace the op-amp by its equivalent model, and then analyze the resultant circuit. Show your result becomes the value we had in class for the limit of an ideal op-amp. (What does ideal op-amp mean?)



($R_i = 1 \text{ M}\Omega$, $R_o = 50 \Omega$)

Solution:

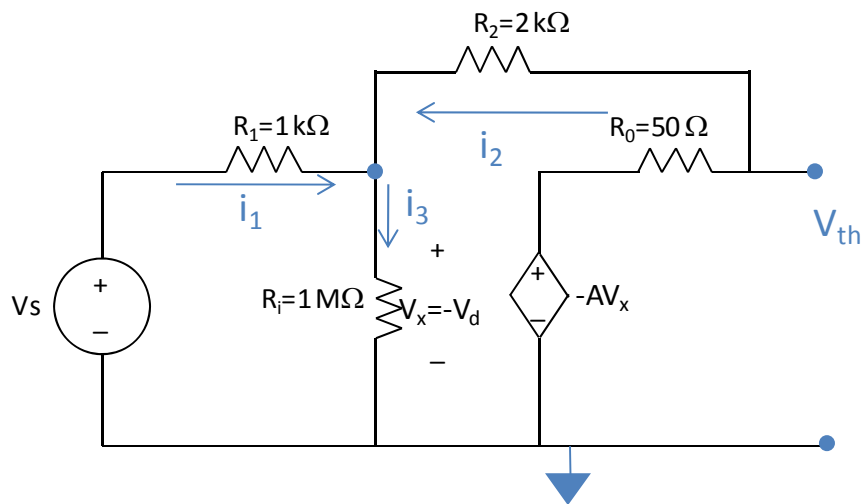


Figure 1: Circuit diagram for solving V_{th}

First, find V_{th}

$$\begin{aligned}
 i_1 + i_2 &= i_3 \\
 \left(\frac{v_s - V_x}{R_1}\right) + \frac{((-AV_x) - V_x)}{R_0 + R_2} &= \frac{V_x}{R_i} \\
 \frac{V_s}{R_1} &= V_x \left(\frac{1}{R_1} + \frac{A + 1}{R_0 + R_2} + \frac{1}{R_i}\right) \\
 \rightarrow V_x &= \left(\frac{V_s}{\left(1 + \frac{R_1(A + 1)}{R_0 + R_2} + \frac{R_1}{R_i}\right)}\right) \tag{1}
 \end{aligned}$$

And we can write the equation,

$$\begin{aligned}
 V_{th} &= -AV_x - i_2 R_0 \\
 V_{th} &= -AV_x - AV_x - V_x R_0 + R_2 R_0 \\
 V_{th} &= V_x \left(-A + \left(\frac{A + 1}{R_0 + R_2}\right) R_0\right) \\
 V_{th} &= \left(\frac{V_s}{\left(1 + \frac{R_1(A + 1)}{R_0 + R_2} + \frac{R_1}{R_i}\right)}\right) \left(-A + \left(\frac{A + 1}{R_0 + R_2}\right) R_0\right) \\
 V_{th} &= V_s \left(\frac{\left(-A + \left(\frac{A + 1}{R_0 + R_2}\right) R_0\right)}{\left(1 + \frac{R_1(A + 1)}{R_0 + R_2} + \frac{R_1}{R_i}\right)}\right) \\
 V_{th} &\approx -\frac{R_2}{R_1} V_s = -2V_s \tag{2}
 \end{aligned}$$

Finding R_{th} , since we have a dependent voltage source we apply an external voltage, v_o , and remove the independent voltage source to get $R_{th} = v_o / i_o$.

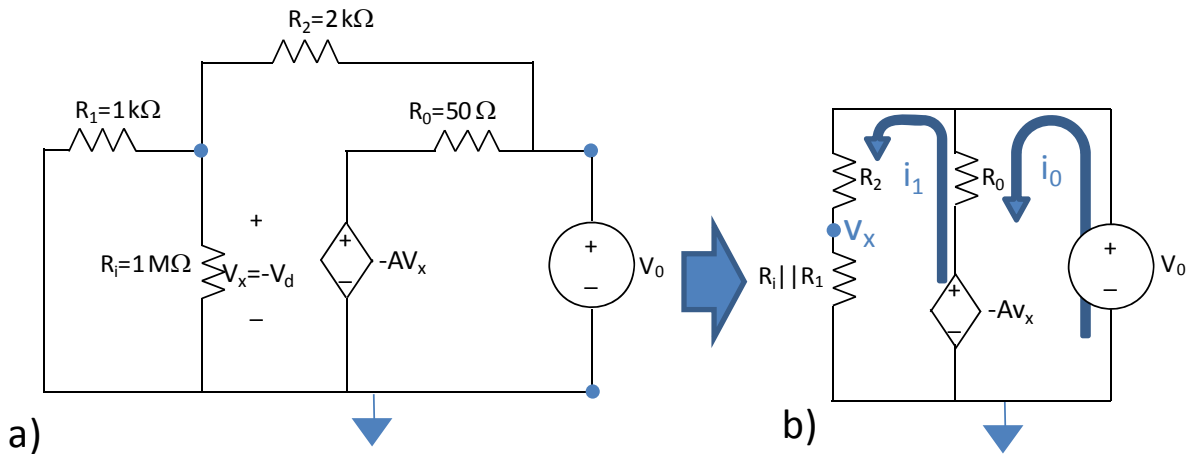


Figure 2 : Circuit diagram for solving for R_{th} using meth analysis. From a) to b) we have redrawn the circuit to improve the visualization of it.

First looking at loop i_0 and use $v_x = i_1(R_i \parallel R_1)$ to get,

$$\begin{aligned} v_0 - (i_0 - i_1)R_0 &= -v_x A \\ v_0 - (i_0 - i_1)R_0 &= -i_1(R_i \parallel R_1)A \\ \Rightarrow v_0 &= i_0 R_0 - i_1(R_0 + (R_i \parallel R_1)A) \end{aligned} \quad (3)$$

And for loop i_1 and again using $v_x = i_1(R_i \parallel R_1)$ we get,

$$\begin{aligned} -v_x A - (i_1 - i_0)R_0 - i_1 R_2 - i_1(R_i \parallel R_1) &= 0 \\ -v_x A + i_0(R_0) - i_1(R_0 + R_2 + R_i \parallel R_1) &= 0 \\ -(i_1(R_i \parallel R_1))A + i_0(R_0) - i_1(R_0 + R_2 + R_i \parallel R_1) &= 0 \\ i_0(R_0) - i_1(R_0 + R_2 + R_i \parallel R_1(1 + A)) &= 0 \end{aligned} \quad (4)$$


Using (4) to eliminate i_1 in (3) we get,

$$v_0 = i_0 R_0 - \left(\frac{i_0(R_0)}{(R_0 + R_2 + R_i \parallel R_1(1 + A))} \right) (R_0 + (R_i \parallel R_1)A) \quad (5)$$

Thus, $R_{th} = v_0/i_0$,

$$\begin{aligned} R_{th} &= \frac{v_0}{i_0} = R_0 \left(1 - \left(\frac{(R_0 + (R_i \parallel R_1)A)}{(R_0 + R_2 + R_i \parallel R_1(1 + A))} \right) \right) \\ R_{th} &= R_0 \left(\frac{R_2 + (R_i \parallel R_1)}{(R_0 + R_2 + R_i \parallel R_1(1 + A))} \right) \approx \frac{R_0}{A} \\ \Rightarrow R_{th} &= 0.00015\Omega \end{aligned} \quad (6)$$

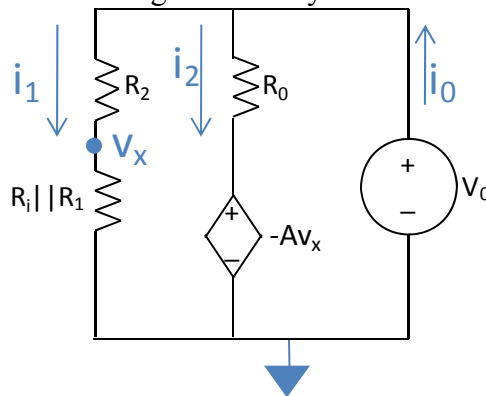Alternatively, R_{th} can also be solved using nodal analysis




Using

$$\begin{aligned} i_0 &= i_1 + i_2 \\ i_0 &= \frac{v_0}{R_2 + R_1 \parallel R_i} + \frac{v_0 - (-Av_x)}{R_0} \\ i_0 &= v_0 \left(\frac{1}{R_2 + R_1 \parallel R_i} + \frac{1}{R_0} \right) + \frac{A}{R_0} \left(v_0 \frac{R_1 \parallel R_i}{R_1 \parallel R_i + R_2} \right) \\ i_0 &= v_0 \left(\frac{1}{R_2 + R_1 \parallel R_i} + \frac{1}{R_0} + \frac{A}{R_0} \frac{R_1 \parallel R_i}{R_1 \parallel R_i + R_2} \right) \\ \Rightarrow \frac{i_0}{v_0} &= \left(\frac{R_0 + R_2 + R_1 \parallel R_i(1 + A)}{R_0(R_1 \parallel R_i + R_2)} \right) \end{aligned}$$

$$\Rightarrow R_{th} = \frac{v_0}{i_0} = R_0 \left(\frac{(R_1 \parallel R_i + R_2)}{R_0 + R_2 + R_1 \parallel R_i(1 + A)} \right) \approx \frac{R_0}{A}$$

$$\Rightarrow R_{th} = 0.00015\Omega$$

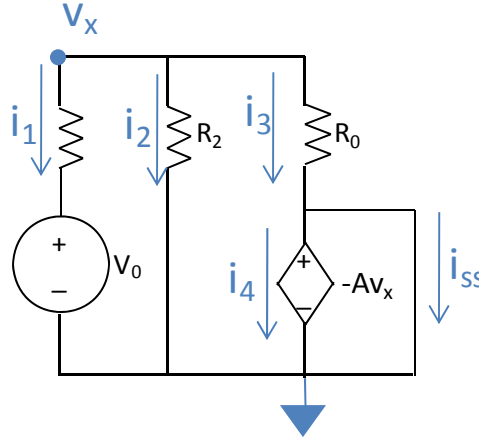

Alternatively, you can short the load and find i_{short} and get $R_{th} = V_{th}/i_{short}$

$$i_1 + i_2 + i_3 = 0$$

$$\frac{v_x - v_s}{R_1} + \frac{v_x}{R_i} + \frac{v_x}{R_2} = 0$$

$$v_x \left(\frac{1}{R_1} + \frac{1}{R_i} + \frac{1}{R_2} \right) - \frac{v_s}{R_1} = 0$$

$$\Rightarrow v_x = \frac{v_s}{1 + \frac{R_1}{R_i} + \frac{R_1}{R_2}}$$

At the other node the current equation is,

$$i_4 + i_{ss} = i_3$$

$$\frac{0 - Av_x}{R_0} + i_{ss} = \frac{v_x}{R_2}$$

$$\Rightarrow i_{ss} = v_x \left(\frac{1}{R_2} + \frac{A}{R_0} \right)$$

$$\Rightarrow i_{ss} = \frac{v_s}{1 + \frac{R_1}{R_i} + \frac{R_1}{R_2}} \left(\frac{1}{R_2} + \frac{A}{R_0} \right)$$

Since $R_{th} = V_{th}/i_{ss}$ we get,

$$\Rightarrow R_{th} = \frac{v_{th}}{i_{ss}} = \frac{\left(\frac{(-A + \frac{A+1}{R_0 + R_2}) R_0}{\left(1 + \frac{R_1(A-1)}{R_0 + R_2} + \frac{R_1}{R_i} \right)} \right)}{\frac{\left(\frac{1}{R_2} + \frac{A}{R_0} \right)}{1 + \frac{R_1}{R_i} + \frac{R_1}{R_2}}} \approx \frac{R_0}{A}$$

$$\Rightarrow R_{th} = 0.00015\Omega$$

Assuming an ideal op-amp we get $V_{th} = -(R_2/R_1)V_s = -2V_s$ and $R_{th} = 0\Omega$ which is approximately what was derived above. Other characteristics of an ideal op-amp are $R_0 = 0$, $R_i = \infty$, $A = \infty$.

Problem 3: Grading Criteria:

6pts for drawing the circuit diagram

8pts for R_{th} :

- . 4pts partial credit for fair attempt at R_{th} and is given as a function of R_1 , R_2 , R_i , R_0
OR
- . 2pts partial credit for fair attempt at R_{th} and is given as a function of R_1 , R_2

8pts for V_{th} :

- . 4pts partial credit for fair attempt at V_{th} and is given as a function of R_1 , R_2 , R_i , R_0 , A , V_s
OR
- . 2pts partial credit for fair attempt at V_{th} and is given as a function of R_1 , R_2 , V_s

5pts for comparing to ideal op-amp, $V_0 = -R_2/R_1 V_s = -2V_s$.

- 3pts if you write $V_0 = 2V_s$

3pts for saying $R_0 = 0$, $R_i = \infty$, $A = \infty$.