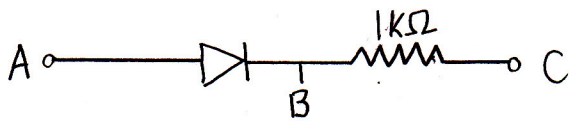


①



$$V_{AC} = R I_{AC} + V_d$$

$$① I_{AC} = \frac{V_{AC} - V_d}{R}$$

$$② I_{AC} = I_0 (e^{\frac{qV_d}{kT}} - 1)$$

Equate ①, ②:

$$\ln \left[\frac{I_{AC}}{I_0} + 1 \right] = \frac{qV_d}{kT}$$

$$\ln \left[\frac{I_{AC}}{I_0} + 1 \right] = \frac{qV_d}{kT}$$

$$V_d = \frac{kT}{q} \ln \left[\frac{I_{AC}}{I_0} + 1 \right]$$


$$③ V_{BC} = R I_{AC}$$

$$④ V_d = \frac{kT}{q} \ln \left[\frac{\frac{V_{AC} - V_d}{R}}{I_0} + 1 \right]$$

← Solve with iteration process.
(Assume diode is on).

V_{AC}	V_d	V_{BC}
-10	0	0
-7.5	0	0
-5	0	0
0	0	0
5	0.756V	4.244V
7.5	0.768V	6.732V
10	0.776V	9.234V

↑ diode off
↓ diode on

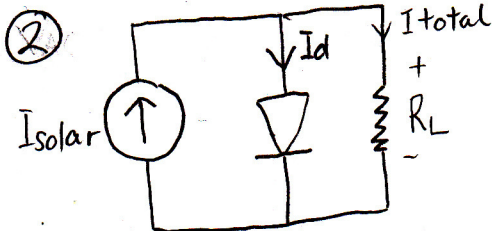

$$I_{total} = I_{solar} - I_d$$

$$I_{total} = I_{solar} - I_0 (e^{\frac{qV_d}{kT}} - 1)$$


$$I_{solar} = I_{total} + I_0 e^{\frac{qV_d}{kT}} - I_0$$

$$= \frac{V_D}{R_L} + I_0 e^{\frac{qV_d}{kT}} - I_0$$

$$= \frac{0.7}{1000} + 10^{-15} e^{\frac{0.7}{0.0259}} - 10^{-15}$$

with a V_d turn-on voltage 0.7V

$$I_{solar} = 1.247 \text{ mA}$$

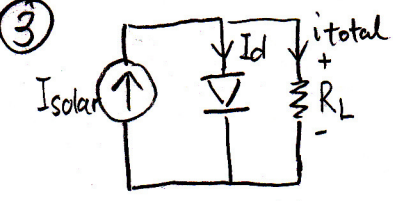


$$\begin{aligned}
 I_{total} &= I_{solar} - I_0 \\
 &= I_{solar} - I_0 \left(e^{\frac{qV_d}{kT}} - 1 \right) \\
 &= 1.247 \text{ mA} - 0.547 \text{ mA} \\
 &= 0.7 \text{ mA}
 \end{aligned}$$

$$\begin{aligned}
 P &= IV = I^2 \cdot R = (0.7 \text{ mA})^2 \cdot R_L \\
 &= (0.7 \text{ mA})^2 \cdot 1000 \Omega \\
 P &= 0.4 \text{ mW}
 \end{aligned}$$

④ $N_A = 10^{18} \text{ cm}^{-3}$ $N_D = 10^{14} \text{ cm}^{-3}$

a) 0 Applied Voltage

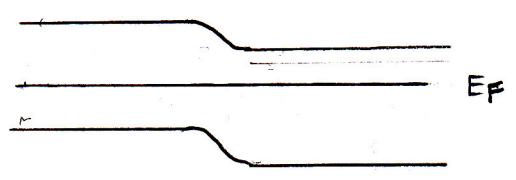


b) $V_{bi} = \frac{kT}{q} \ln \left(\frac{N_A \cdot N_D}{n_i^2} \right)$

$$\begin{aligned}
 &= 0.0259 \ln \left(\frac{10^{32}}{10^{20}} \right) \\
 &= 0.0259 (27.631) \\
 &= 0.718 \text{ V}
 \end{aligned}$$


$V_A = 0.1 \text{ V}$
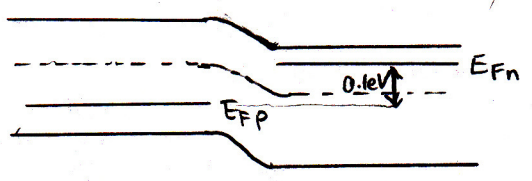
$$\begin{aligned}
 E_{Fp} - E_{Fn} &= -q \cdot V_A \\
 E_{Fn} - E_{Fp} &= 0.1 \text{ eV}
 \end{aligned}$$



$V_A = -1 \text{ V}$

$$E_{Fp} - E_{Fn} = 1 \text{ eV}$$

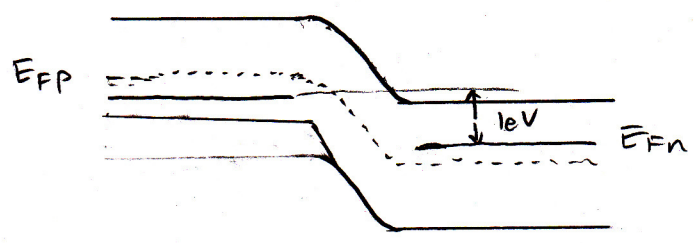

$V_A = -10 \text{ V}$

$$E_{Fp} - E_{Fn} = 10 \text{ eV}$$

