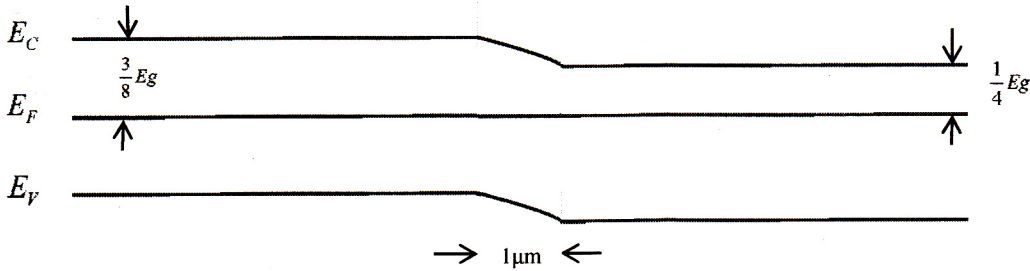


PROBLEM ONE: (30 points)





- a) Sketch and find $n(x)$ and $p(x)$ on both sides.
- b) Sketch $J_{ndiff}(x)$, $J_{ndrift}(x)$, $J_{pdiff}(x)$, $J_{pdrift}(x)$
- c) Sketch E-field $\mathcal{E}(x)$
- d) Find $N_D(x)$ on both sides assuming $N_A(x) = 0$.

a) $n(x)_L = N_C e^{-(E_C - E_F)/kT}$
 $= 3.2 \times 10^{19} \cdot e^{-0.42/0.0259}$
 $= 2.9 \times 10^{12} \text{ cm}^{-3}$ on left


$p(x)_L = N_V e^{-(E_F - E_V)/kT}$
 $= 1.9 \times 10^{19} e^{-(0.7)/0.0259}$
 $= 3.476 \times 10^7 \text{ cm}^{-3}$ on left

$p(x)_R = 1.9 \times 10^{19} e^{-.84/0.0259}$
 $= 1.56 \times 10^5 \text{ cm}^{-3}$ on right

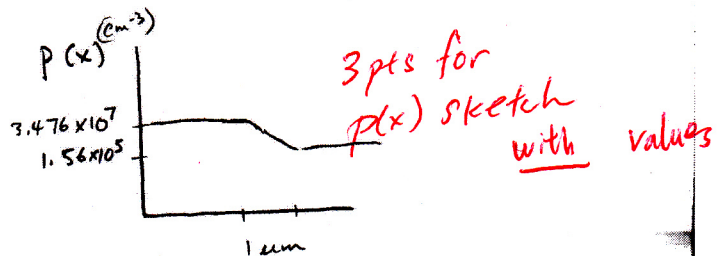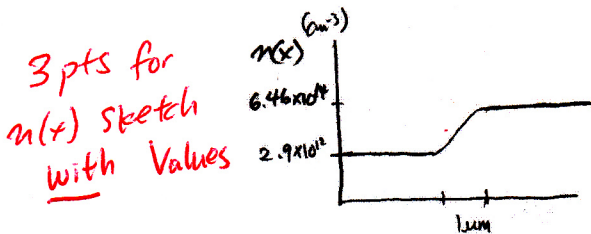
2pts for $n(x)$ calculation
 $n(x)_R = 3.2 \times 10^{19} \cdot e^{-0.28/0.0259}$
 $= 6.46 \times 10^{14} \text{ cm}^{-3}$ on right




5pts for J_n

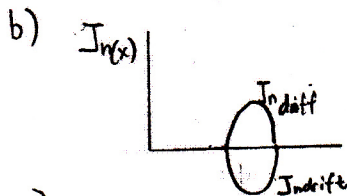

5pts for J_p

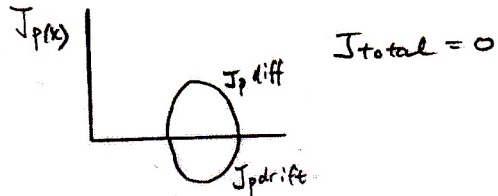

6pts for $\mathcal{E}(x)$

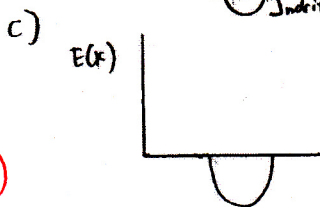

d) $N_D(x)$ left = $n(x)$ left = $2.9 \times 10^{12} \text{ cm}^{-3}$
 $N_D(x)$ right = $n(x)$ right = $6.46 \times 10^{14} \text{ cm}^{-3}$

4pts for d):

2pt for left side.
 2pt for right side.

PROBLEM TWO(25 points):

- a) For a Given Silicon pn diode at room temperature, $N_A = 10^{17} \text{ cm}^{-3}$ and $N_D = 10^{17} \text{ cm}^{-3}$. Find V_{bi} .

$$V_{bi} = \frac{kT}{q} \ln\left(\frac{N_A * N_D}{n_i^2}\right)$$


$$V_{bi} = 0.0259 \ln\left(\frac{10^{34}}{10^{20}}\right)$$

$$V_{bi} = 0.835V$$

3 pts for correct setup

2 pts for answer

- b) For the circuit below, find the approximate current I_1 , V_1 , V_2 , and V_3 .

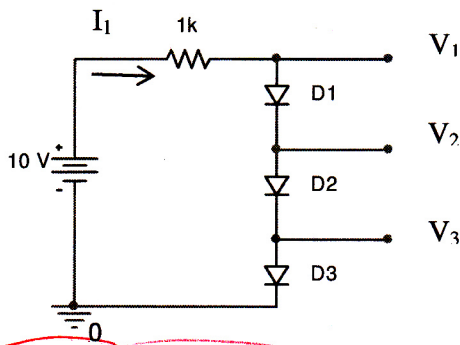

For 0.6V assumption:

$$KVL: 10 = I_1 R + 3V_d$$

$$I_1 = \frac{10 - 3V_d}{R} = \frac{10 - 3(0.6)}{1000} = 8.2 \text{ mA}$$

$$V_1 = 10 - I_1 R = 10 - (8.2)(1000) = 1.8V$$

$$V_2 = 1.8V - 0.6V = 1.2V$$

$$V_3 = 1.2V - 0.6V = 0.6V$$

← 2 pts for Diode turn on voltage assumption.

← 2 pts for I_1

← 2 pts for V_1

← 2 pts for V_2

← 2 pts for V_3

For 0.7V assumption:

$$KVL: 10 = I_1 R + 3V_d$$

$$I_1 = \frac{10 - 3V_d}{R} = \frac{10 - 3(0.7)}{1000} = 7.9 \text{ mA}$$


$$V_1 = 10 - I_1 R = 10 - (7.9)(1000) = 2.1V$$

$$V_2 = 2.1V - 0.7V = 1.4V$$

$$V_3 = 1.4V - 0.7V = 0.7V$$

Same as above

- c) For the circuit below, find the approximate current for
- I_1
- ,
- I_2
- ,
- I_3
- .

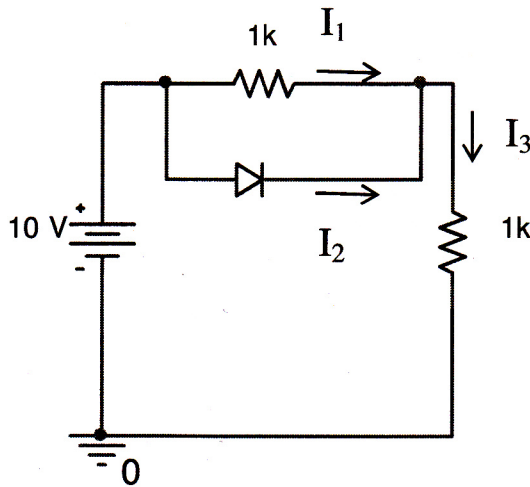**For 0.6V assumption:**Set node between the two resistors to be V_x .

$$V_x = 10 - 0.6 = 9.4V$$

$$I_3 = V_x / 1000 = 9.4mA$$

$$I_1 = \frac{10 - V_x}{1000} = 0.6mA$$

$$I_2 = I_3 - I_1 = 9.4 - 0.6 = 8.8mA$$

← 1pts for Diode turn on voltage assumption

← 3pts for I_3 ← 3pts for I_1 ← 3pts for I_2 **For 0.7V assumption:**Set node between the two resistors to be V_x .

$$V_x = 10 - 0.7 = 9.3V$$

$$I_3 = V_x / 1000 = 9.3mA$$

$$I_1 = \frac{10 - V_x}{1000} = 0.7mA$$

$$I_2 = I_3 - I_1 = 9.3 - 0.7 = 8.6mA$$

Same as Above.

PROBLEM THREE(45 points):

For the amplifier circuit below at room temperature, $\beta = 100$ and the turn-on voltage for V_{BE} is 0.7V.

a) 22.5 pts
b) 22.5 pts

- a) Find the AC voltage gain.
b) If the 100K Ω resistor becomes 50K Ω , find the AC voltage gain.

- a) Find the AC voltage gain.
b) If the 100K Ω resistor becomes 50K Ω , find the AC voltage gain.

b) same as (a)

a) $i_B = 2$ pts

$i_C = 2$ pts


$V_C = 2$ pts

Forward Active mode verification: 2 pt


Hybrid- π Model correct drawing: 3 pts

$g_m = 3$ pts

$r_{\pi} = 3$ pts

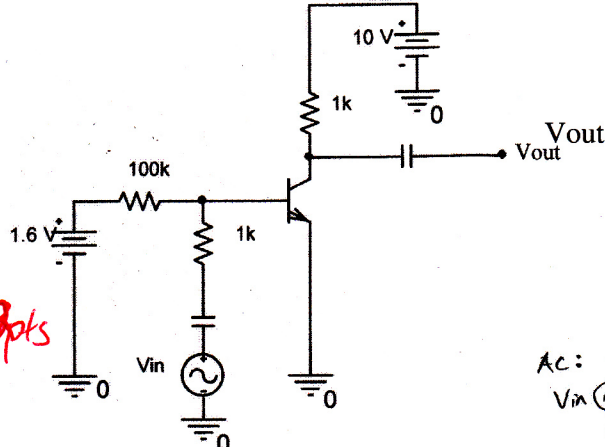

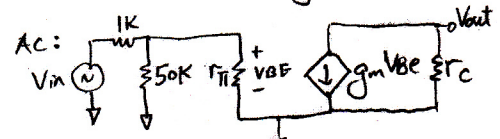b) DC op point: Assume F.A
 $1.6 = 50k i_B + 0.7$
 $i_B = 18 \mu A$
 $i_C = 100 i_B = 1.8 mA$ F.A
 $V_C = 10 - i_C R_C = 8.2 V$
 $g_m = \frac{I_C}{V_T} = \frac{1.8 mA}{0.0259} = 0.695 S$
 $r_{\pi} = \frac{\beta}{g_m} = 1439 \Omega$




$V_{BE} = V_{in} \left(\frac{r_{\pi} // 50k}{r_{\pi} // 50k + 1k} \right)$

$\frac{V_{out}}{1k} = -g_m V_{BE}$

$\frac{V_{out}}{V_{in}} = \left(\frac{r_{\pi} // 50k}{r_{\pi} // 50k + 1k} \right) (-g_m R_C) = -40.5$

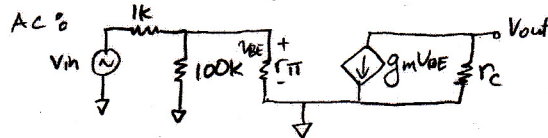a) DC op point: Assume F.A
 KVL: $1.6 = 100k i_B + 0.7$
 $i_B = \frac{0.9 mA}{100k} = 9 \mu A$
 $i_C = \beta i_B = 0.9 mA$
 $V_C = 10 - i_C R_C = 10 - (0.9)(1000) = 9.1 V$ ← F.A.V



$g_m = \frac{I_C}{V_T} = \frac{0.9 mA}{0.0259} = 0.03475 S$

$r_{\pi} = \frac{\beta}{g_m} = \frac{100}{0.03475} = 2877.7 \Omega$

$V_{Be} = V_{in} \left(\frac{r_{\pi} // 100k}{r_{\pi} // 100k + 1k} \right)$

KCL: $\frac{V_{out}}{1k} = -g_m V_{BE} \rightarrow \frac{V_{out}}{V_{in}} = \left(\frac{r_{\pi} // 100k}{r_{\pi} // 100k + 1k} \right) (-g_m R_C) = -25.6$

Correct $\frac{V_{out}}{V_{in}}$ expression: 5 pts

Correct Final answer: 2.5 pts.