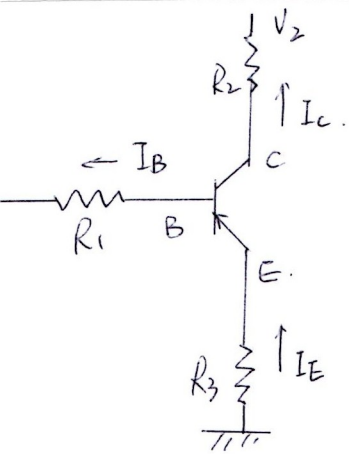


Homework 6. Solution.



D. Since $V_{BE} = 0.6V$, the transistor is not in forward active mode.

Assuming the transistor is in forward active mode:

$$V_{EB} = 0.6V \quad I_C = \beta I_B = 100 I_B \quad I_E = I_B + I_C = 101 I_B$$

$$\text{KVL: } -V_E + V_{EB} + V_{R1} = -V_1 \quad (*)$$

$$\begin{cases} V_E = -R_3 I_E \\ V_{R1} = I_B R_1 \\ V_{EB} = 0.6V \end{cases}$$

$$(*) \Rightarrow R_3 I_E + 0.6 + R_1 I_B = -V_1$$

$$\left(\frac{R_1}{101} + R_3\right) I_E = -(V_1 + 0.6)$$

$$\Rightarrow I_E = \frac{-101(V_1 + 0.6)}{R_1 + 101R_3}$$

$$I_B = \frac{I_E}{101} = \frac{-(V_1 + 0.6)}{R_1 + 101R_3}$$

$$I_C = 100 I_B = \frac{-100(V_1 + 0.6)}{R_1 + 101R_3}$$

$$V_E = -I_E R_3 = \frac{-101 R_3 (V_1 + 0.6)}{R_1 + 101 R_3}$$

$$V_B = V_{BE} + V_E = V_E - 0.6 = \frac{-0.6 R_1 + 101 R_3 V_1}{R_1 + 101 R_3}$$

$$V_C = V_2 + R_2 I_C = V_2 - \frac{100 R_2 (0.6 + V_1)}{R_1 + 101 R_3}$$


$$V_{BE} = -0.6V$$

$$V_{CE} = V_2 + R_2 I_C + R_3 I_E = V_2 - \frac{100 R_2 (0.6 + V_1)}{R_1 + 101 R_3} - \frac{101 R_3 (V_1 + 0.6)}{R_1 + 101 R_3}$$

$$V_{BC} = V_B - V_C = -I_E R_3 - 0.6 - V_2 - R_2 I_C$$

$$= \frac{(101 R_3 + 100 R_2) V_1 - (R_1 + 101 R_3) V_2 + (100 R_2 - R_1) \cdot 0.6}{R_1 + 101 R_3}$$

2. Hybrid Pi Model AC:

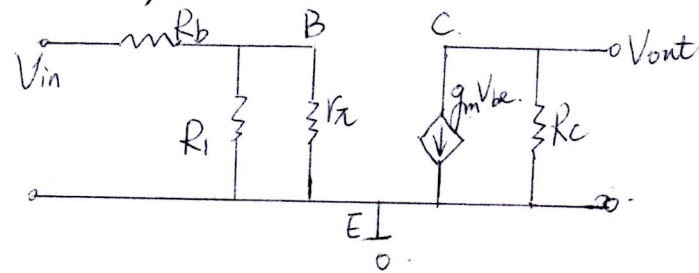

$$R_i \parallel r_\pi = \frac{R_i \beta / g_m}{R_i + \beta / g_m} = \frac{R_i \beta}{R_i g_m + \beta}$$

$$\Rightarrow \text{gain} = \frac{-g_m R_c R_i \beta}{R_b (g_m R_i + \beta) + R_i \beta} \quad (*)$$

$$V_{out} = -g_m V_{be} R_c$$

$$V_{in} = \frac{R_b + R_i \parallel r_\pi}{R_i \parallel r_\pi} V_{be}$$

$$\text{gain} = \frac{V_{out}}{V_{in}} = \frac{-g_m V_{be} R_c}{\frac{R_b + R_i \parallel r_\pi}{R_i \parallel r_\pi} V_{be}}$$

* $g_m = \frac{I_c}{V_T}$ $I_c = \beta I_B$ $2 - R_i I_B = V_{BE} = 0.6 \text{ V}$

$$I_B = \frac{2 - 0.6}{R_i} = \frac{1.4}{R_i} \Rightarrow I_c = \frac{140}{R_i} \quad V_T = \frac{kT}{q}$$


$$\Rightarrow \text{gain} = \frac{-140 R_c}{1.4 R_b + V_T + R_i V_T}$$

3 From (*), $\Rightarrow \lim_{g_m \rightarrow \infty} \text{gain} = -\frac{g_m R_c R_i \beta}{R_b (g_m R_i)} = -\beta \frac{R_c}{R_b}$

When $g_m \rightarrow \infty \Rightarrow \frac{kT}{q} \rightarrow 0 \Rightarrow T \rightarrow 0 \text{ K}$

$$\text{Gain} = -\beta \frac{R_c}{R_b}$$


4 AC:

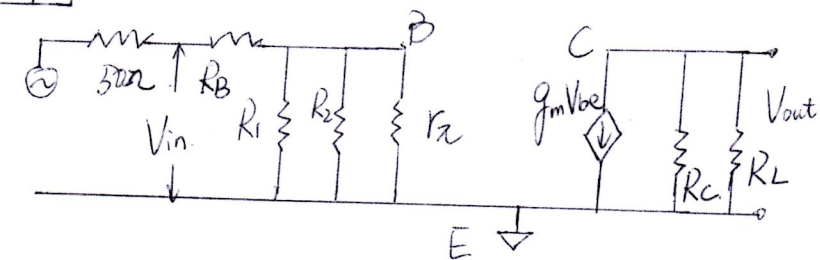

$$V_{out} = -g_m V_{be} \cdot R_c \parallel R_L$$

$$V_{in} = \frac{R_B + R_i \parallel R_2 \parallel r_\pi}{R_i \parallel R_2 \parallel r_\pi} V_{be}$$
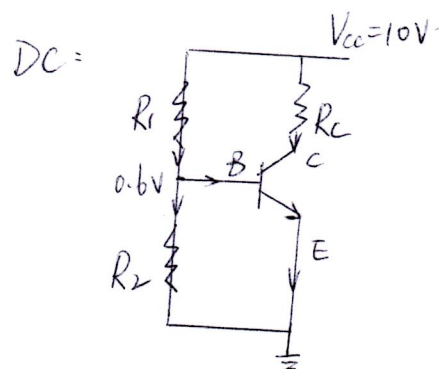
$$\text{Gain} = \frac{V_{out}}{V_{in}} = \frac{-g_m R_c \parallel R_L}{(R_B + R_i \parallel R_2 \parallel r_\pi) / R_i \parallel R_2 \parallel r_\pi} \quad (*)$$



$$\text{KCL} = I_B = I_{R_1} - I_{R_2} = \frac{10 - 0.6}{R_1} - \frac{0.6}{R_2}$$

$$I_c = \beta I_B = \beta \left(\frac{9.4}{R_1} - \frac{0.6}{R_2} \right)$$

$$g_m = \frac{I_c}{V_T} = \frac{\beta}{V_T} \left(\frac{9.4}{R_1} - \frac{0.6}{R_2} \right)$$

$$r_\pi = \beta / g_m$$

$$\text{Gain} = -g_m \frac{R_c R_L}{R_c + R_L} \left(\frac{R_1 R_2 r_z}{R_1 R_2 + R_1 r_z + R_2 r_z} \right) \left(\frac{R_1 R_2 r_z}{R_B + \frac{R_1 R_2 r_z}{R_1 R_2 + R_1 r_z + R_2 r_z}} \right)$$

$$= \frac{-\beta}{V_T} \frac{R_c R_L}{R_c + R_L} \left(\frac{r_z}{R_1} - \frac{0.6}{R_2} \right) \left(\frac{R_1 R_2 r_z}{R_1 R_2 + R_1 r_z + R_2 r_z} \right) \left(\frac{R_1 R_2 r_z}{R_B + \frac{R_1 R_2 r_z}{R_1 R_2 + R_1 r_z + R_2 r_z}} \right) \cdot \text{which } r_z = \beta / g_m$$

$$\lim_{\substack{V_T \rightarrow 0 \\ R_L \rightarrow \infty}} \text{Gain} = \lim_{R_L \rightarrow \infty} -\beta \frac{R_L R_c}{R_B (R_L + R_c)} = -\beta \frac{R_c}{R_B}$$

The condition we find = $\boxed{V_T \rightarrow 0, T \rightarrow 0 \text{ K}, R_L \rightarrow +\infty}$