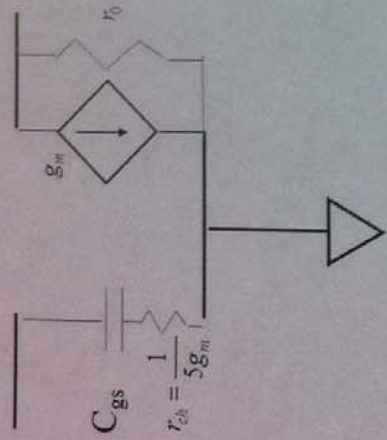


3) For the circuit below, find the y-matrix. Next, find terms of the circuit elements. Find  $f_T$  and  $f_{MAX}$ .



CORRECTION

$$U = \frac{g_m V_0}{20 \omega^2 C_{gs}^2} (25 g_m^2 + \omega^2 C_{gs}^2)$$

$$U|_{f_{MAX}} = 1$$

$$1 = \frac{g_m V_0}{20 C_{gs}^2 \omega_{MAX}^2} (25 g_m^2 + \omega_{MAX}^2 C_{gs}^2)$$

$$1 - \frac{g_m V_0}{20} = \frac{25}{20} \frac{g_m V_0}{C_{gs}^2 \omega_{MAX}^2}$$

$$\omega_{MAX}^2 = \frac{25}{20} \frac{g_m V_0}{C_{gs}^2 \omega_{MAX}^2} / \left( 1 - \frac{g_m V_0}{20} \right)$$

$$\omega_{MAX} = 5 \frac{g_m}{C_{gs}} \sqrt{\frac{g_m V_0}{20 - g_m V_0}} = 2\pi f_{MAX}$$

$$U = \frac{|y_{21} - y_{12}|^2}{4 \operatorname{Re}(y_{11}) \operatorname{Re}(y_{22}) - \operatorname{Re}(y_{12}) \operatorname{Re}(y_{21})}$$

$$= \frac{g_m^2}{4 \frac{1}{r_0} \operatorname{Re} \left[ \frac{j \omega C_{gs} 5 g_m}{(5 g_m + j \omega C_{gs})} \right]}$$

$$= \frac{g_m^2 r_0 / 4}{\operatorname{Re} \left( \frac{j \omega C_{gs} 5 g_m (5 g_m - j \omega C_{gs})}{(5 g_m + j \omega C_{gs}) (5 g_m - j \omega C_{gs})} \right)}$$

$$= \frac{g_m^2 r_0 / 4}{\operatorname{Re} \left( \frac{5 g_m^2 + \omega^2 C_{gs}^2}{(5 g_m)^2 + (\omega C_{gs})^2} \right)}$$

$$= \frac{g_m^2 r_0 / 4}{(5 g_m)^2 + (\omega C_{gs})^2} \text{ pts}$$

$$U = \frac{g_m^2 r_0}{20 \omega^2 C_{gs}^2} (25 g_m^2 + \omega^2 C_{gs}^2)$$