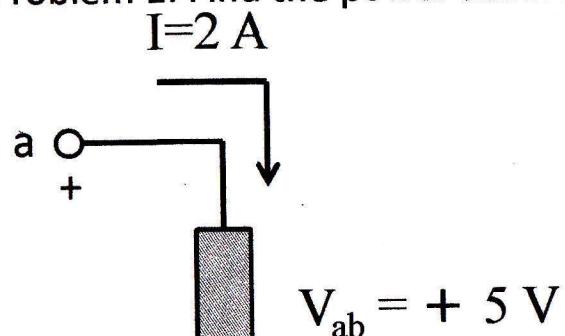


Problem 1: Find the power absorbed or supplied by the element.




Solution:  $P = V_{ab} \cdot I_{ab}$

$$\begin{aligned} &= 5 \times 2 \\ &= \boxed{10 \text{ W}} \end{aligned}$$

$P > 0$  power absorbed

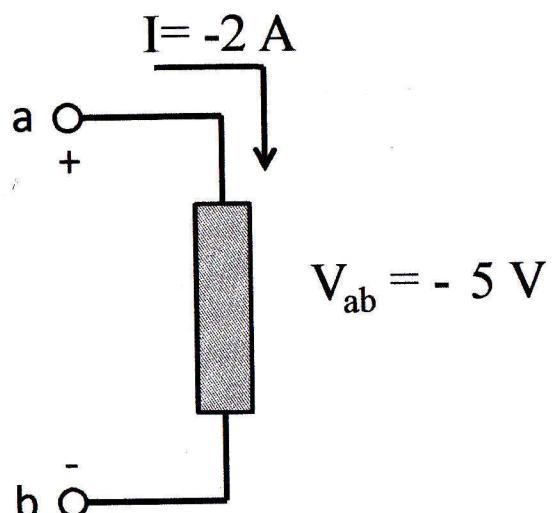Problem 2: Find the power absorbed or supplied by the element.




Solution:

$$\begin{aligned} P &= V \cdot I \\ &= V_{ab} \cdot I_{ab} \\ &= (-5) \times (-2) \\ &= \boxed{10 \text{ W}} \end{aligned}$$

$P > 0$  power absorbed

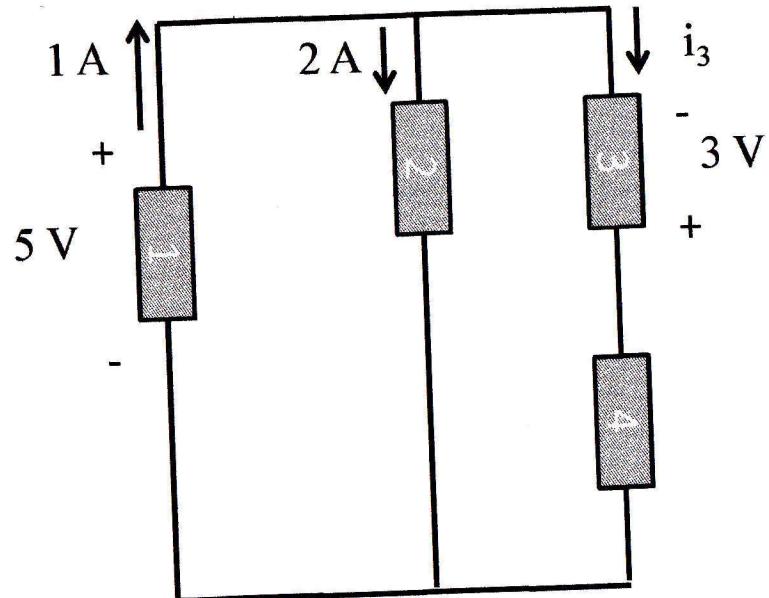Problem 3:

- Find  $i_3$ .
- Find the power absorbed or supplied by element 3.
- Is element 3 a source or a sink?



Solution: Kirchhoff's current law

a) the total current flowing into a node  
= the total current leaving a node

$$\text{So } 1A = 2A + i_3 \\ i_3 = \boxed{-1A}$$

$$\begin{aligned} b) P &= V \cdot I \\ &= (-3) \cdot i_3 \\ &= (-3) \times (-1) = \boxed{3W.} \end{aligned}$$

c)  $P > 0$  power absorbed, sink.

Problem 4: (Power balance)

Assume  $P_1 = 10 \text{ W}$ ,  $P_2 = 30 \text{ W}$ ,  $P_3 = -5 \text{ W}$ .

Find the power absorbed or supplied by element 4. Is it a source or a sink?

Solution: power conservation

$$\sum P = 0$$


$$P_1 + P_2 + P_3 + P_4 = 0$$

$$P_4 = -(P_1 + P_2 + P_3)$$

$$= -(10 + 30 - 5)$$

$$= \boxed{-35 \text{ W}}$$


$P_4 < 0$  it is a source.

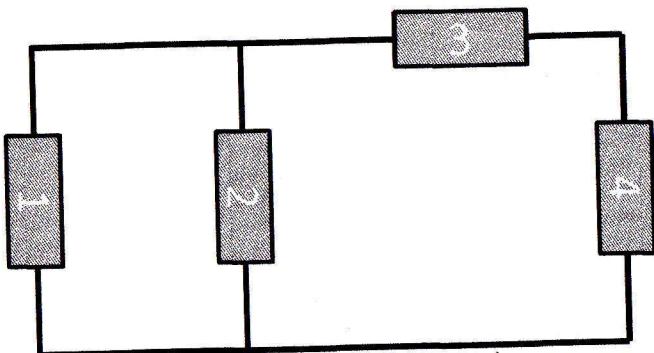

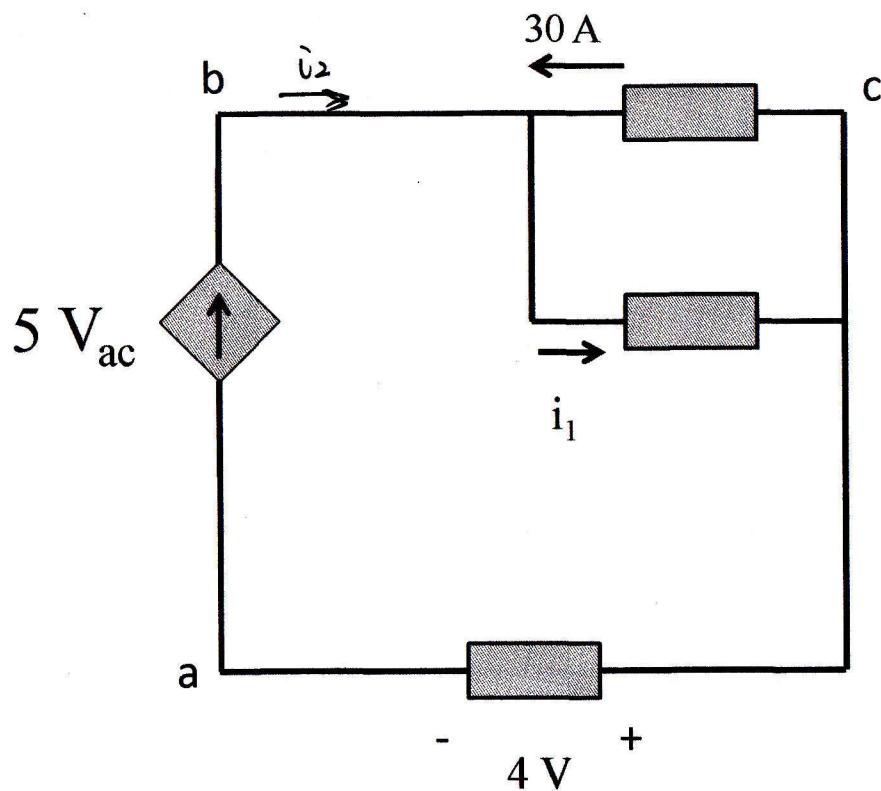Problem 5: (VCCS)

Find  $i_1$ .

Is current flowing from b to c or from c to b?



Solution : kirchhoff's current law.

$$5V_{ac} + 30A = i_1$$

$$V_{ac} = -4V$$

$$-20 + 30 = i_1$$

$$i_1 = \boxed{10 A}$$

$$i_2 = 5V_{ac} = -20 A$$


it's negative, therefore the direction  
is from c to b

Problem 6: (CCVS)

Find  $i_1, i_2$ .

Find  $V_{bc}$ .

Solution: kirchhoff's current law

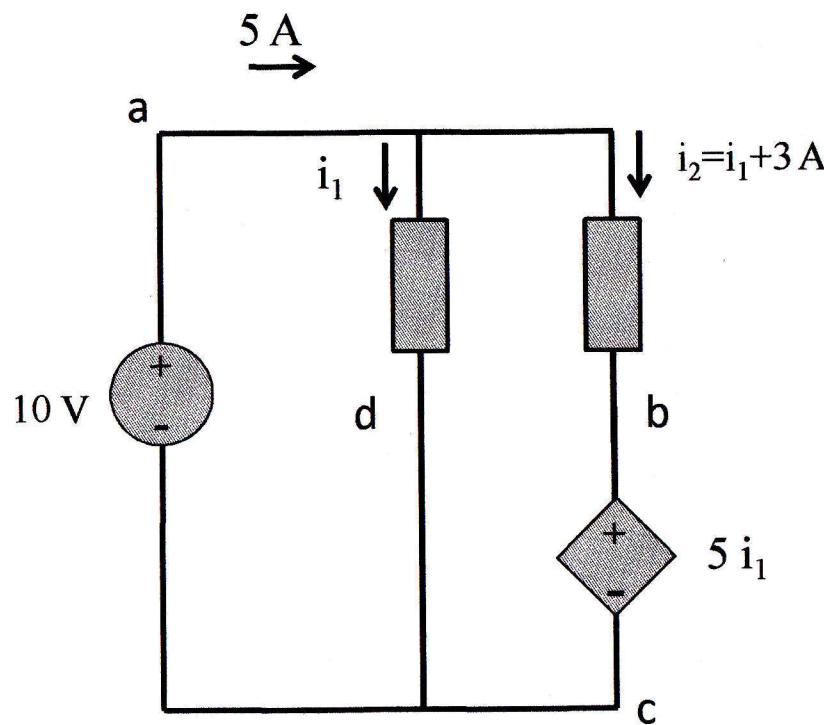

$$5 = i_1 + i_2$$

$$= i_1 + i_1 + 3$$

$$= 2i_1 + 3$$

$$i_1 = \boxed{1 \text{ A}}$$

$$i_2 = \boxed{4 \text{ A}}$$

$$V_{bc} = 5i_1 = \boxed{5 \text{ V}}$$


Problem 7: (VCVS)

Find  $V_{ac}$ .

Solution :  $V_{ac} = 2V_{bc}$

$$= 2 \times 5$$

$$= \boxed{10\text{ V}}$$

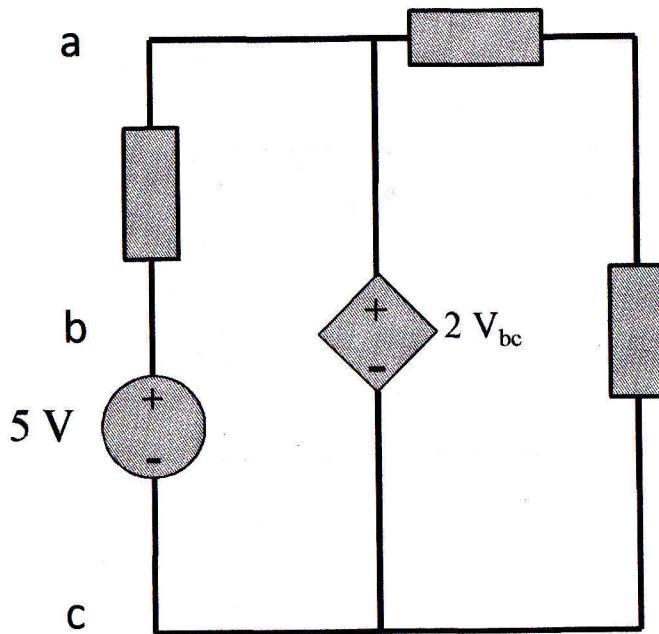

Problem 8: (CCCS)

Find  $i_1$ .

Solution: Kirchhoff's current law

$$5 + i_1 + i_1 + 1 = 8i_1$$

$$6i_1 = 6$$
$$i_1 = \boxed{1 \text{ A}}$$

