

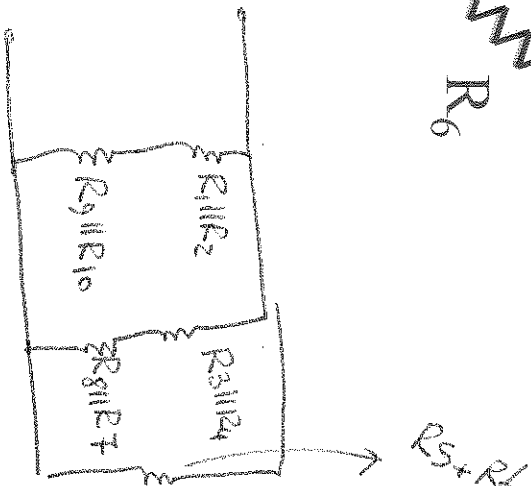
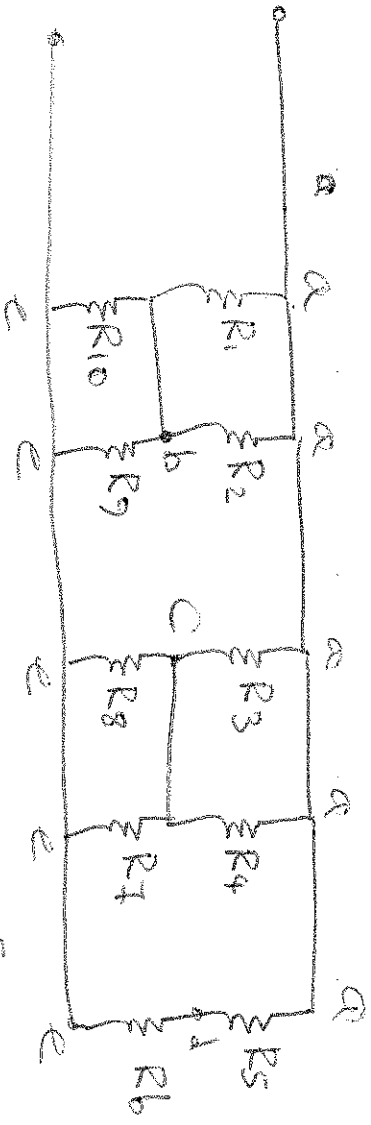
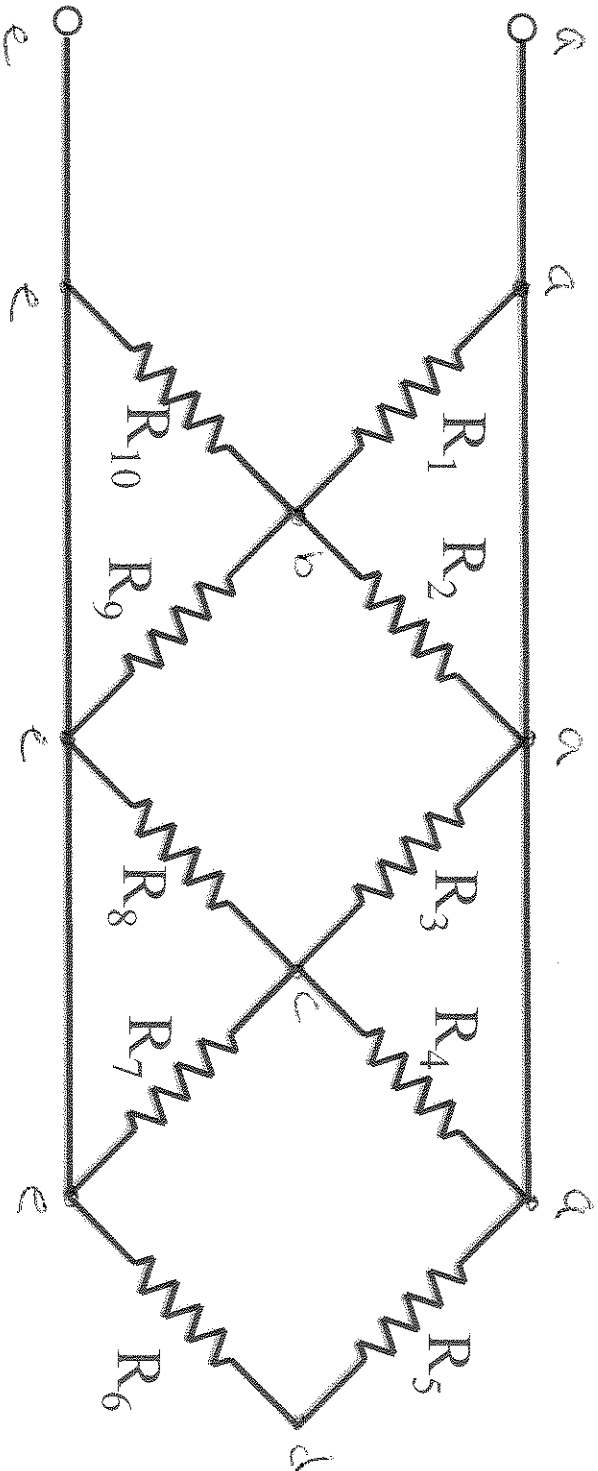


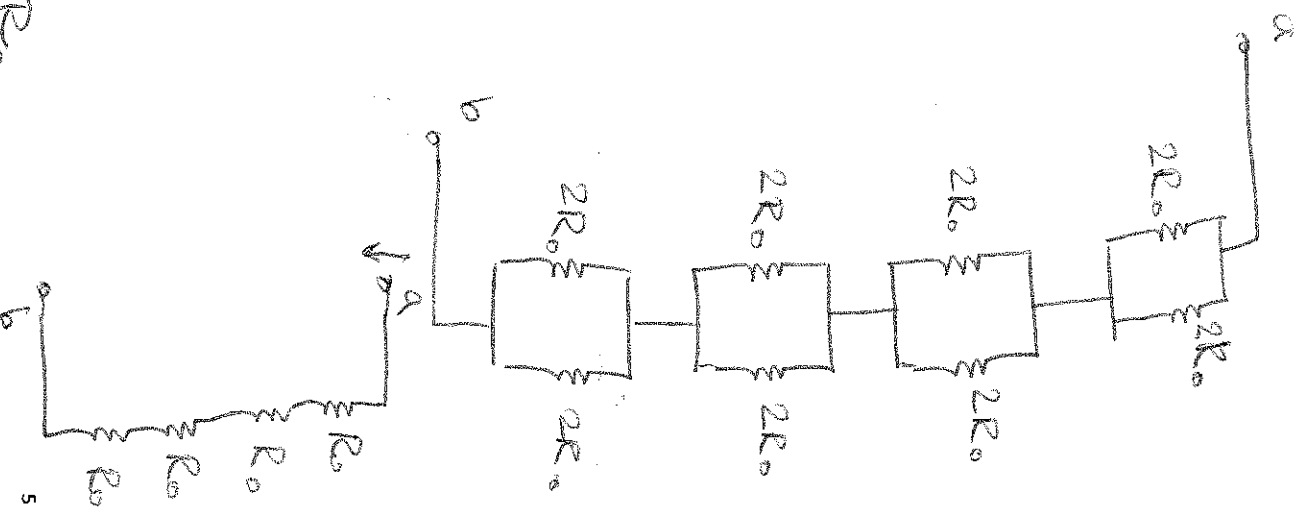Problem 2: Solve for R_{eq} . You may use the parallel notation discussed in class.



$$R_{eq} = (R_5 + R_6) \parallel \left[(R_1 \parallel R_2) + (R_3 \parallel R_4) + (R_7 \parallel R_8) + (R_9 \parallel R_{10}) \right]$$

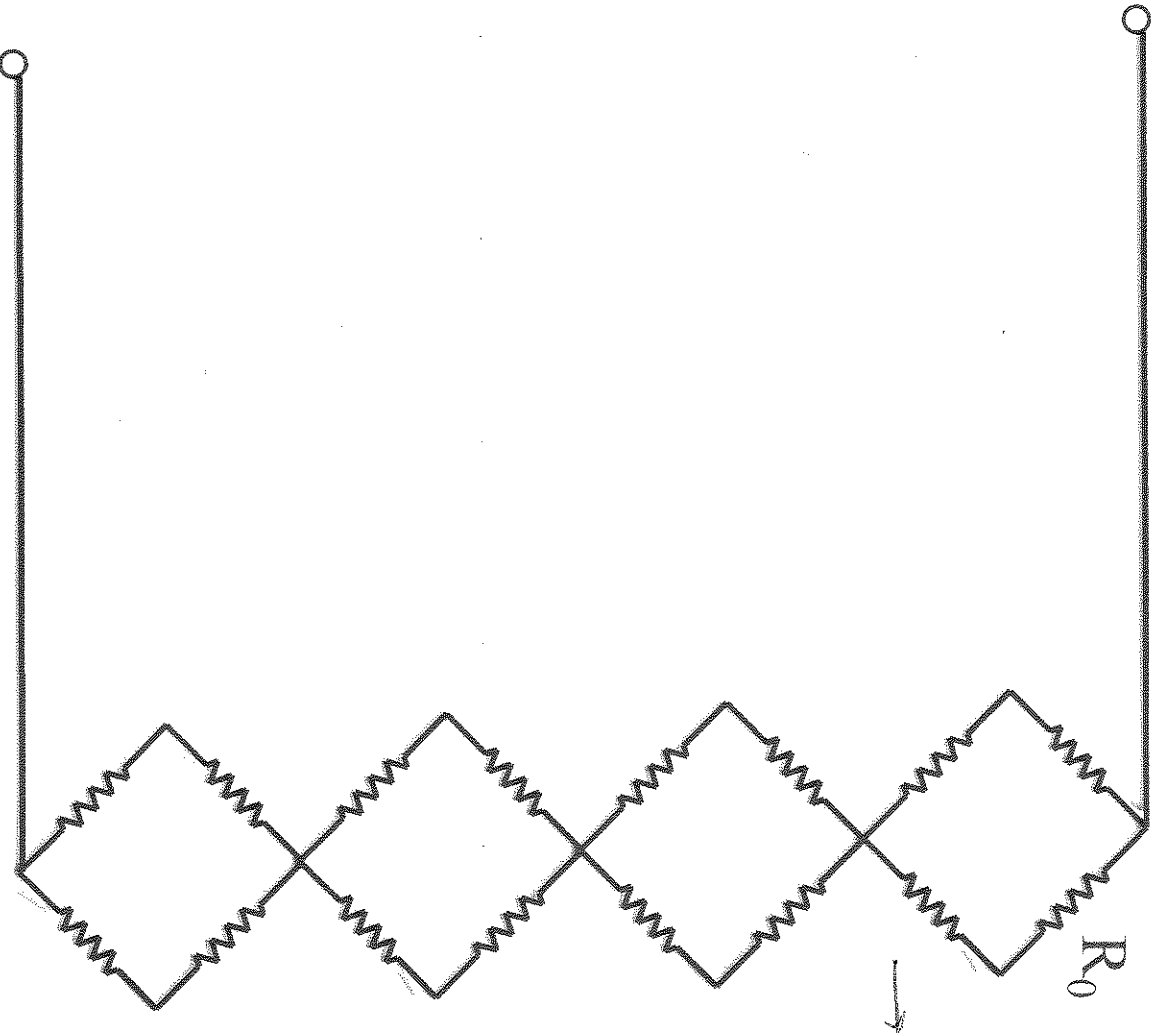
Problem 3: Solve for R_{eq} . All resistors have the same value R_0 .



$\Rightarrow R_{eq} = 4R_0$

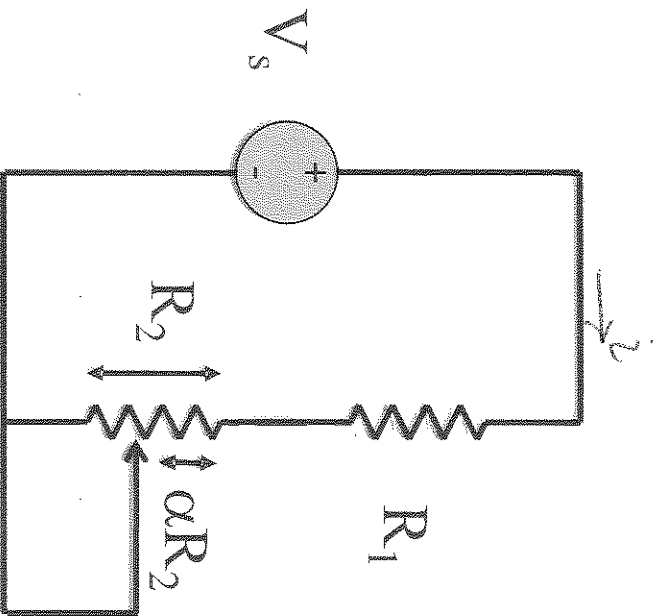Problem 4: Potentiometer.

In the circuit below, the wiper divides the potentiometer resistance between αR_2 and $(1-\alpha)R_2$, where $0 < \alpha < 1$. Find the ratio of the power dissipated in R_1 to the power supplied by the voltage source (P_1/P_s) as a function of α .



$$i_1 = \frac{V_s}{R_1 + \alpha R_2}$$


$$P_1 = i_1^2 R_1 = \frac{V_s^2 R_1}{(R_1 + \alpha R_2)^2}$$

$$P_s = V_s \cdot i_1 = \frac{V_s^2}{R_1 + \alpha R_2}$$

$$\frac{P_1}{P_s} = \frac{\frac{V_s^2 R_1}{(R_1 + \alpha R_2)^2}}{\frac{V_s^2}{R_1 + \alpha R_2}} = \frac{R_1}{R_1 + \alpha R_2}$$

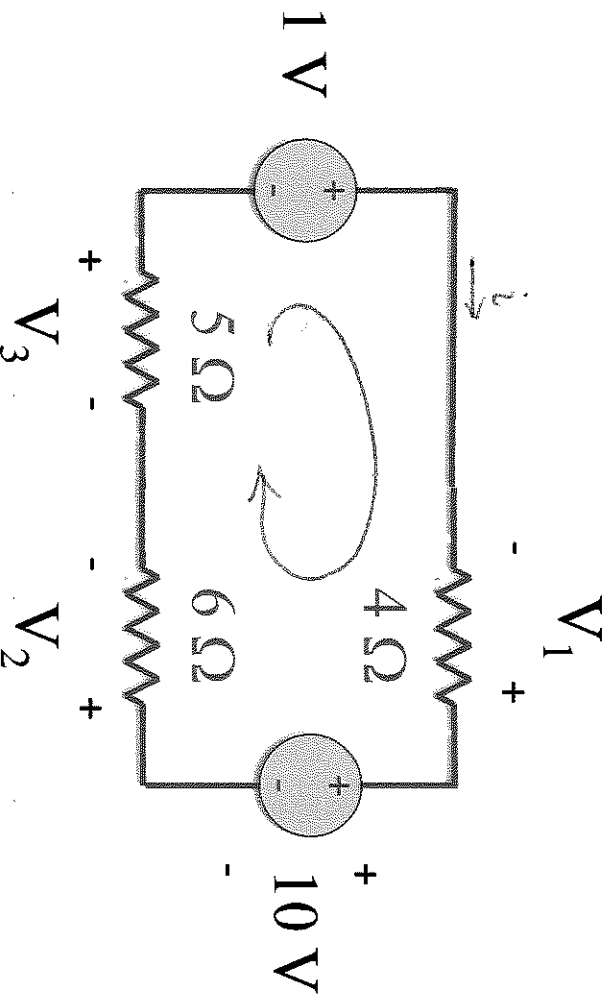Problem 5: KVL & Ohm

Find V_1 through V_3 and the current flowing in the circuit below.



~~KVL: $-1 + V_1$~~

KVL: $-1 - V_1 + 10 + V_2 - V_3 = 0$

$\Rightarrow V_2 - V_1 - V_3 = -9$ *

Ohm's Law:

$$\begin{cases} V_2 = iR_2 = 4i \\ V_1 = -iR_1 = -4i \\ V_3 = -iR_3 = -5i \end{cases}$$


* $6i + 4i + 5i = -9 \Rightarrow i = -0.6 \text{ A}$

$V_2 = -8.6 \text{ V}$

$V_1 = 2.4 \text{ V}$

$V_3 = 3 \text{ V}$

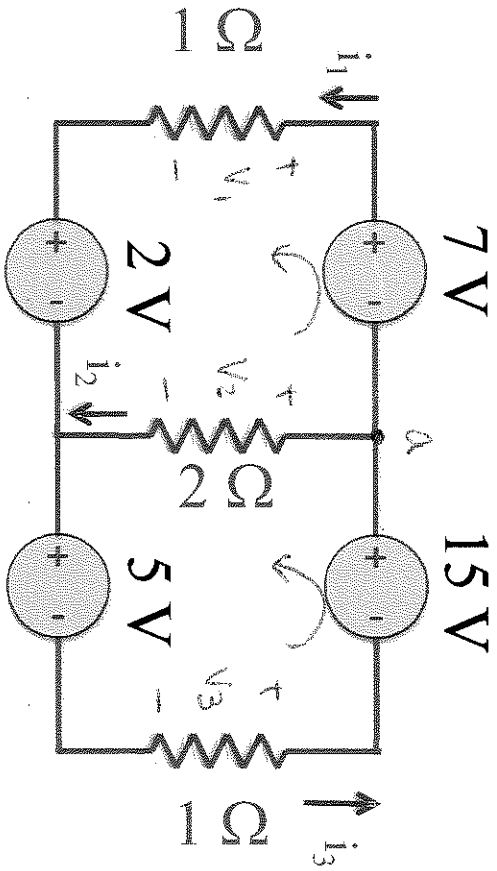Problem 6: KVL, KCL & Ohm
 Find i_1 through i_3 in the circuit below.



KVL

$$\begin{cases} V_1 + 2 - V_2 - 7 = 0 \\ V_2 + 5 - V_3 - 15 = 0 \end{cases}$$

$$\Rightarrow \begin{cases} i_1 - 2i_2 = 5 \\ 2i_2 + i_1 = 10 \end{cases}$$

replace with i

$$\Rightarrow \begin{cases} i_1 = 4 \text{ A} \\ i_2 = 1 \text{ A} \end{cases}$$

$$\begin{cases} i_1 - 2i_2 = 5 \\ 2i_2 + i_3 = 10 \end{cases}$$

$$\Rightarrow i_3 = 8 \text{ A}$$

replace i_3
 from KCL

$$\begin{cases} i_1 - 2i_2 = 5 \\ 2i_2 + (i_1 + i_2) = 10 \end{cases}$$


KCL at node a:

$$i_3 = i_2 + i_1$$

Ohm's Law:

$$\begin{aligned} V_1 &= i_1 \times 1\Omega = i_1 \\ V_2 &= i_2 \times 2\Omega = 2i_2 \\ V_3 &= -i_3 \times 1\Omega = -i_3 \end{aligned}$$

Problem 7: Find V_1 through V_4 and i_1 through i_3 in the circuit below.

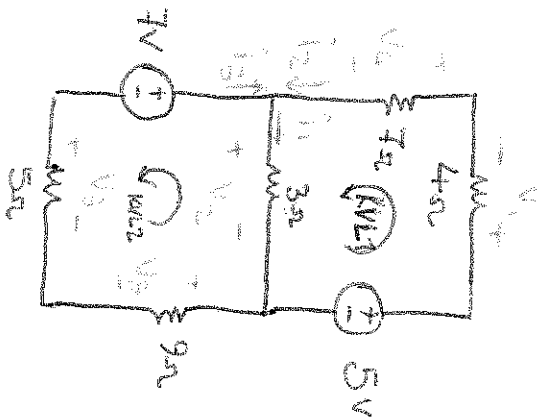

KVL1: $V_1 + V_4 + V_2 - 5 = 0$
 KVL2: $7 + V_3 - V_5 - V_2 = 0$

replace with currents

$$\begin{cases} 4i_2 + 7i_2 + 3i_1 = 5 \\ 7 - 5i_3 - 9i_3 - 3i_1 = 0 \end{cases}$$

$$\begin{cases} 11i_2 + 3i_1 = 5 \\ 3i_1 + 14i_3 = 7 \end{cases}$$

replace ~~with~~ i_1 with $i_2 + i_3$

$$\begin{cases} 11i_2 + 3(i_2 + i_3) = 5 \\ 3(i_2 + i_3) + 14i_3 = 7 \end{cases}$$

$$\begin{cases} 14i_2 + 3i_3 = 5 \\ 3i_2 + 17i_3 = 7 \end{cases}$$

$$\begin{cases} 238i_2 + 51i_3 = 85 \\ 9i_2 + 51i_3 = 21 \end{cases}$$

\Rightarrow

$$\begin{aligned} i_2 &= 0.28 \text{ A} \\ i_3 &= 0.36 \text{ A} \\ i_1 &= 0.28 + 0.36 = 0.64 \text{ A} \end{aligned}$$

\Rightarrow

$$\begin{aligned} V_1 &= 1.12 \text{ V} \\ V_2 &= 1.92 \text{ V} \\ V_3 &= -1.8 \text{ V} \\ V_4 &= 1.96 \text{ V} \\ V_5 &= 3.24 \text{ V} \end{aligned}$$

Ohm's Law

$$\begin{aligned} V_1 &= 4i_2 \\ V_2 &= 3i_1 \\ V_3 &= -5i_3 \\ V_4 &= 7i_2 \\ V_5 &= 9i_3 \end{aligned}$$

KCL: $i_1 = i_2 + i_3$