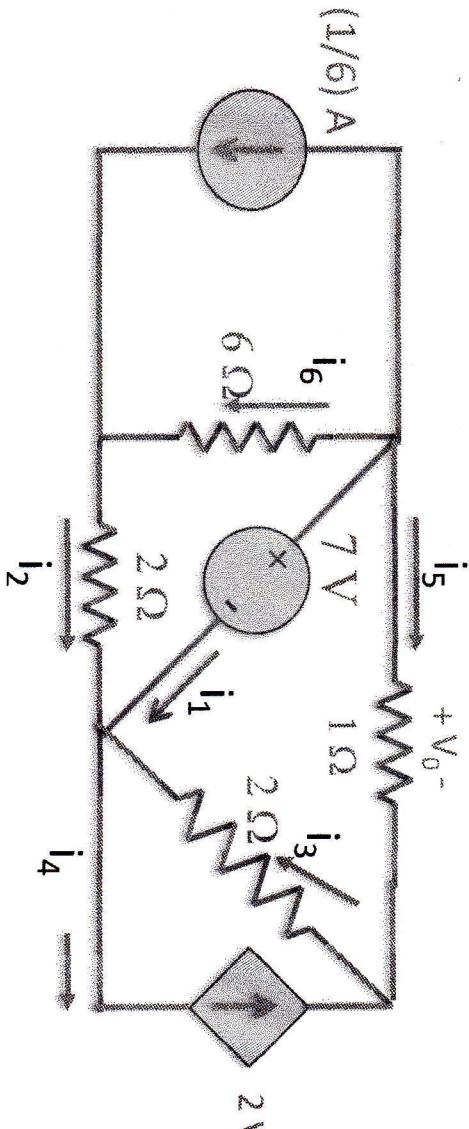


Problem 1:


- Use nodal analysis to find all node voltages.
- Find all the currents.

$$\text{At node } 1 : V_1 = 7V$$

$$\text{kcl at node } 2 : \left\{ \begin{array}{l} \frac{V_2 - V_1}{1\Omega} + \frac{V_2}{2\Omega} - 2V_0 = 0 \\ V_0 = V_1 - V_2 \end{array} \right.$$



Solution:

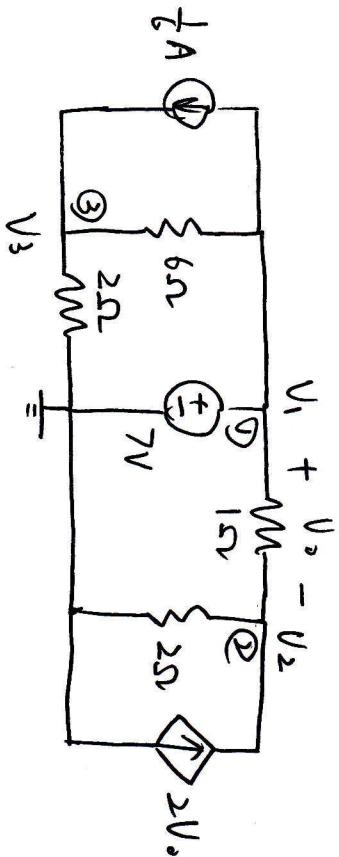

Let's set the cathode of the voltage source as the reference ground.

$$i_1 = -(i_5 + i_6) = -\frac{11}{6}A \text{ not right}$$

$$i_5 = \frac{V_1 - V_3}{1\Omega} = 1A$$

$$i_6 = \frac{V_1 - V_3}{6\Omega} = \frac{5}{6}A$$

$$i_4 = 2(V_1 - V_2) = 2A$$

For the currents

$$i_2 = \frac{V_3}{2\Omega} = 1A$$

$$i_3 = \frac{V_1 - V_2}{1\Omega} + 2(V_1 - V_2) = 3A$$

$$\text{Solve for node } 2 : V_2 = 6V$$

$$\text{Solve for node } 3 : V_3 = 2V$$

$$\text{Therefore } V_1 = 7V, V_2 = 6V, V_3 = 2V$$

Problem 2: Use nodal analysis to find all the node voltages and currents

KCL @ node 3:

$$\frac{V_3 - V_2}{2\Omega} + \frac{V_3 - V_1}{12\Omega} + \frac{V_3 - V_4}{12\Omega} = 0 \quad (1)$$

KCL @ node 4:

$$\frac{V_4 - V_2}{2\Omega} + \frac{V_4 - V_3}{12\Omega} + \frac{V_4 - V_1}{12\Omega} = 0 \quad (2)$$

$$\begin{cases} V_2 - V_1 = 9V \\ V_1 = 3V_0 \\ \cancel{V_0 = \frac{V_2}{3}} \\ \text{VO = V4} \end{cases}$$

Substitute V_1, V_2 into Eq.(1)

$$\frac{V_3 - (3V_4 + 9)}{2} + \frac{(V_3 - 3V_4)}{12} + \frac{V_3 - V_4}{12} = 0$$

$$\Rightarrow 8V_3 - 22V_4 - 54 = 0 \quad (3)$$


Substitute V_1, V_2 into Eq.(2)

$$\frac{V_4}{2} + \frac{V_4 - V_3}{12} + \frac{V_4 - 3V_4}{12} = 0$$


$$\Rightarrow 5V_4 - V_3 = 0 \quad (4)$$

substitute $\bar{E}_g(4)$ into $\bar{E}_g(3)$
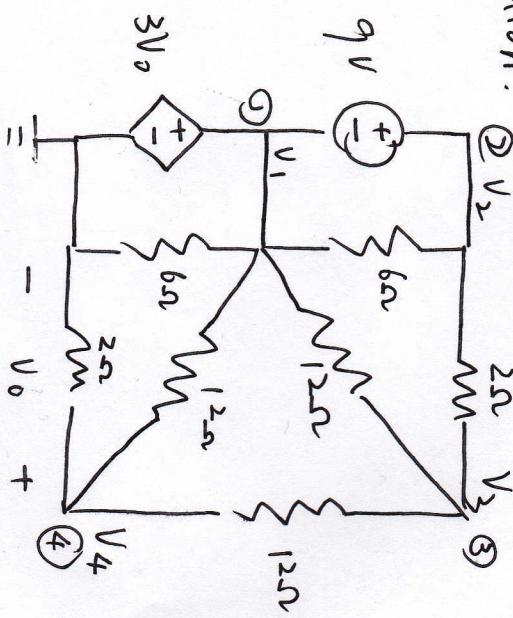
$$\Rightarrow \begin{cases} V_4 = 3V \\ V_3 = 15V \end{cases}$$



Solution:

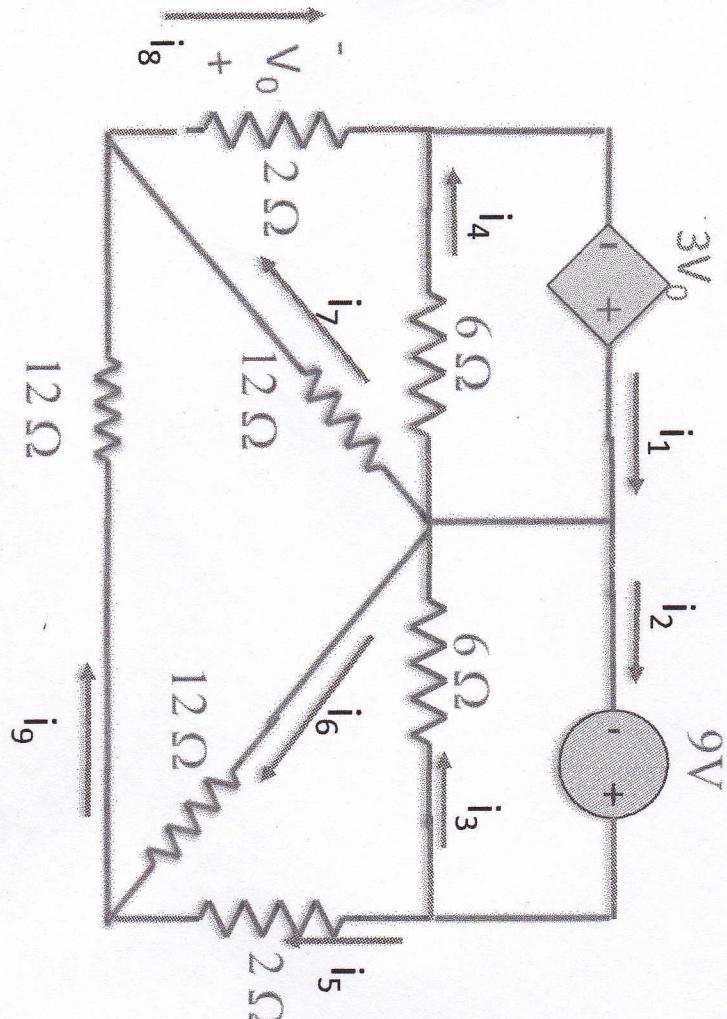

$$S_D \quad V_1 = 9V$$

$$V_2 = 18V$$

$$V_3 = 15V$$

$$V_4 = 3V$$

•

For the currents:

$$i_3 = \frac{V_2 - V_1}{6\Omega} = \frac{18 - 9}{6} = \frac{3}{2} A$$

$$i_4 = \frac{V_1}{6\Omega} = \frac{3}{2} A$$

$$i_5 = \frac{V_2 - V_3}{2\Omega} = \frac{18 - 15}{2} = \frac{3}{2} A$$

$$i_6 = \frac{V_1 - V_3}{12\Omega} = \frac{9 - 15}{12} = -\frac{1}{2} A$$

$$i_7 = \frac{V_1 - V_4}{12\Omega} = \frac{9 - 3}{12} = \frac{1}{2} A$$

$$i_8 = \frac{V_4}{2\Omega} = \frac{3}{2} = 1.5 A$$

$$i_9 = \frac{V_3 - V_4}{12\Omega} = \frac{15 - 3}{12} = 1 A$$

$$i_1 = i_4 + i_8 = 3 A$$

$$i_2 = i_3 + i_5 = 3 A$$

Problem 3: Write all the node voltage equations and put them in the matrix form. You don't need to solve

Supernode

$$\text{@ node } 6: \frac{V_7 - V_6}{R_9} - \frac{V_6 - V_3}{R_7} - \frac{V_6 - V_2}{R_{11}} = 0 \quad (4)$$

$$\text{@ node } 8: \frac{V_7 - V_8}{R_{10}} = \frac{V_8 - V_4}{R_8} \quad (5)$$

@ Supernode

$$\frac{V_6 - V_7}{R_9} + \frac{V_8 - V_2}{R_{10}} + \frac{V_3 - V_5}{R_5} + \frac{V_4 - V_5}{R_6} + \frac{V_2}{R_2} + \frac{V_1}{R_1} = 0 \quad (6)$$

$$\Rightarrow \frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_5} + \frac{V_4}{R_6} - \left(\frac{1}{R_5} + \frac{1}{R_6} \right) V_5 + \frac{V_6}{R_9} - \left(\frac{1}{R_9} + \frac{1}{R_{10}} \right) V_7 + \frac{V_8}{R_{10}} = 0 \quad (6)$$

In addition:

$$V_7 - V_5 = V_2 \quad (7)$$

$$V_5 = V_X \equiv V_6 - V_2 \quad \text{we have eight equations}$$

for eight unknown numbers.

@ node ②:

$$\frac{V_3 - V_2}{R_3} + \frac{V_6 - V_2}{R_{11}} - \frac{V_2}{R_2} = 0 \Rightarrow -\left(\frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_{11}}\right)V_2 + \frac{1}{R_3}V_3 + \frac{1}{R_{11}}V_6 = 0 \quad (1)$$


@ node ③:

$$\frac{V_6 - V_3}{R_7} + \frac{V_5 - V_3}{R_5} - \frac{V_3 - V_2}{R_2} = 0 \Rightarrow \frac{1}{R_3}V_2 - \left(\frac{1}{R_2} + \frac{1}{R_5} + \frac{1}{R_7}\right)V_3 + \frac{1}{R_5}V_5 + \frac{1}{R_7}V_6 = 0 \quad (2)$$

@ node ④:

$$\frac{V_8 - V_4}{R_8} + \frac{V_5 - V_4}{R_5} - \frac{V_4 - V_1}{R_1} = 0 \Rightarrow \frac{1}{R_4}V_1 - \left(\frac{1}{R_1} + \frac{1}{R_5} + \frac{1}{R_8}\right)V_4 + \frac{1}{R_6}V_5 + \frac{1}{R_8}V_8 = 0 \quad (3)$$

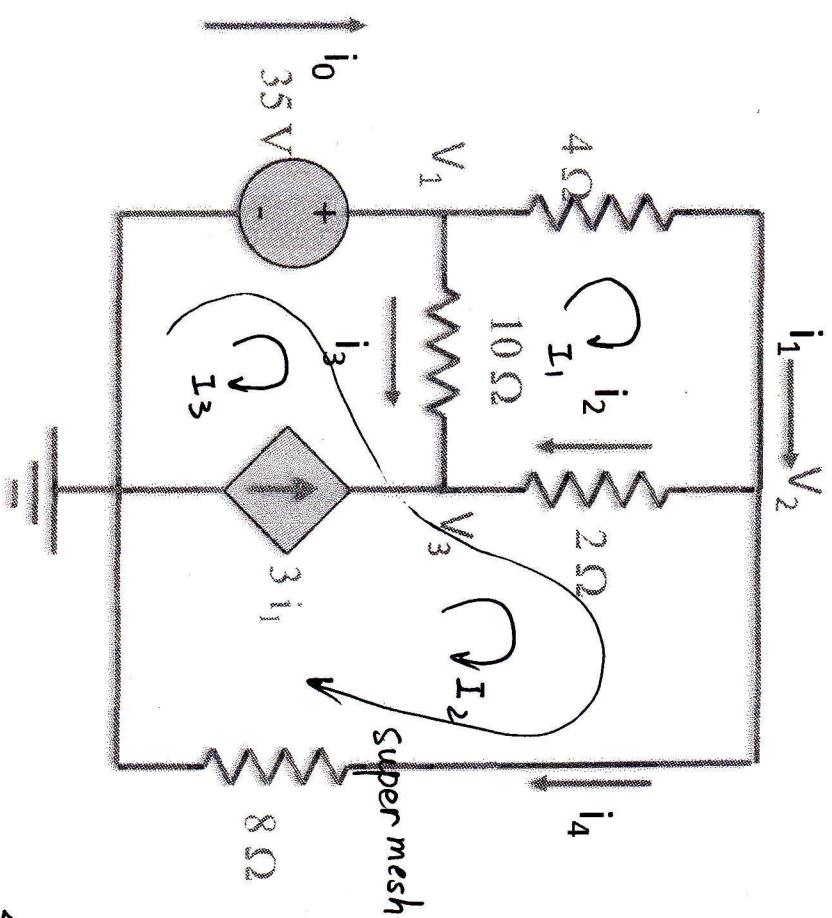Problem 4: use mesh analysis to find all the currents and node voltages.



KVL @ mesh I_2 & mesh $I_3 \rightarrow$ supermesh

$$-35 + (I_3 - I_1) \times 10 + (I_2 - I_1) \times 2 + I_2 \times 8 = 0 \\ \Rightarrow -12I_1 + 10I_2 + 10I_3 = 35 \quad (1)$$

$$I_2 - I_3 = 3i_1 = 3I_1 \Rightarrow 3I_1 - I_2 + I_3 = 0 \quad (2)$$

matrix form :

$$\begin{bmatrix} -8 & -1 & -5 \\ -12 & 10 & 10 \\ 3 & -1 & 1 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 0 \\ 35 \\ 0 \end{bmatrix}$$

$$\Delta = \begin{vmatrix} 8 & -1 & -5 \\ -12 & 10 & 10 \\ 3 & -1 & 1 \end{vmatrix} = 208 \quad \Delta_3 = \begin{vmatrix} 8 & -1 & 0 \\ -12 & 10 & 35 \\ 3 & 1 & 0 \end{vmatrix} = 175$$

$$\Delta_1 = \begin{vmatrix} 0 & -1 & -5 \\ 35 & 10 & 10 \\ 0 & -1 & 1 \end{vmatrix} = 210 \quad I_1 = \frac{\Delta_1}{\Delta} = 1.0096 \text{ A}$$

$$I_2 = \frac{\Delta_2}{\Delta} = \frac{805}{208} = 3.8702 \text{ A}$$

Solution:

KVL @ mesh I_1

$$4I_1 + 2(I_1 - I_2) + 10(I_1 - I_3) = 0 \\ \Rightarrow 8I_1 - I_2 - 5I_3 = 0 \quad (1)$$

$$\Delta_2 = \begin{vmatrix} 8 & 0 & -5 \\ -12 & 35 & 10 \\ 3 & 0 & 1 \end{vmatrix} = 805$$

$$I_3 = \frac{\Delta_3}{\Delta} = 0.8413 \text{ A}$$

$$i_1 = I_1 = 1.0096 A$$

$$i_4 = I_2 = 3.8702 A$$

$$i_2 = I_1 - I_2 = -2.8606 A$$

$$i_3 = I_3 - I_1 = 0.8413 - 1.0096 = -0.1683 A$$

For the node voltages:

$$V_1 = 35 V$$

$$V_2 = V_1 - 4i_1 = 30.9616 V$$

$$V_3 = V_1 - 10i_3 = 35 - 10 \times (-0.1683) = 36.683 V$$

Problem 5:

- Use mesh analysis to find resistor currents and the all node voltages

Solution:

$$\text{kVL @ mesh } I_1 \\ -I_2 + 8I_1 + 4(I_4 + I_3) + 2(I_1 - I_2) = 0 \\ \Rightarrow 7I_1 - I_2 + 2I_3 = 6 \quad (1)$$

$$\text{kVL @ mesh } I_2 \\ \left\{ \begin{array}{l} 2(I_2 - I_1) + 8(I_2 + I_3) + 4(I_2 + I_5) = 0 \\ I_5 = 5A \end{array} \right.$$

$$\Rightarrow I_1 - 7I_2 - 4I_3 = 10 \quad (2)$$


$$\text{kVL @ mesh } I_3 \\ 4(4I_3 + 8(I_2 + I_3) + 2(I_3 - I_4)) = 0$$

$$I_4 = 3A$$

$$\Rightarrow 2I_1 + 4I_2 + 7I_3 = 3 \quad (3)$$

matrix form
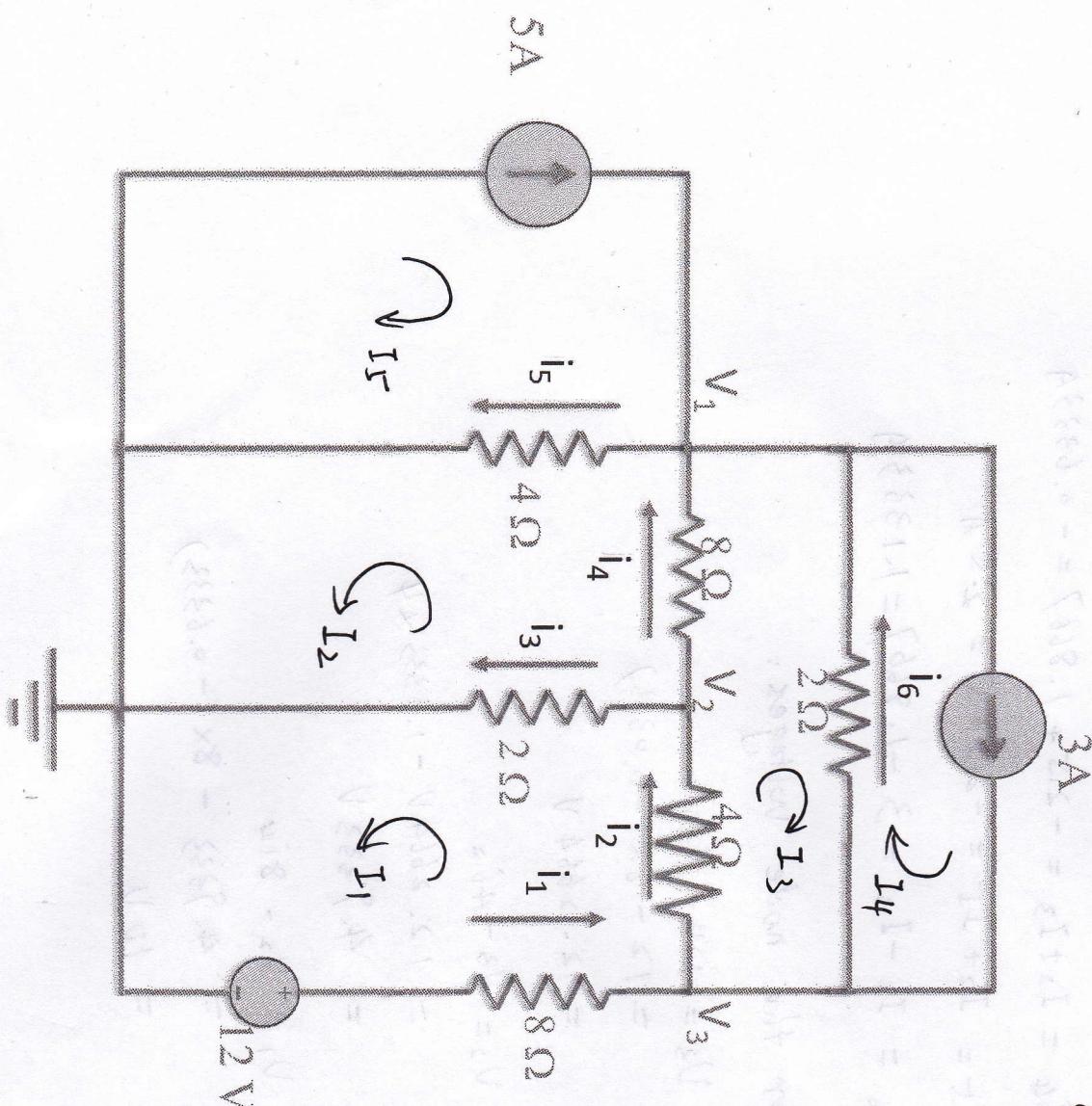
$$\begin{bmatrix} 7 & -1 & 2 \\ 1 & -7 & -4 \\ 2 & 4 & 7 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 6 \\ 10 \\ 3 \end{bmatrix}$$



$$\Delta = \begin{vmatrix} 7 & -1 & 2 \\ 1 & -7 & -4 \\ 2 & 4 & 7 \end{vmatrix} = -180$$

$$i_1 = I_1 = -0.0333 A$$

$$i_2 = I_1 + I_3 = -0.0333 + 1.8667 = 1.8334 A$$

$$i_3 = I_1 - I_2 = -0.0333 + 2.5 = 2.4667 A$$

$$i_4 = I_2 + I_3 = -2.5 + 1.8667 = -0.6333 A$$

$$i_5 = I_2 + I_5 = -2.5 + 5 = 2.5 A$$

$$i_6 = I_4 - I_3 = 3 - 1.8667 = 1.1333 A$$

$$\Delta 2 = \begin{vmatrix} 7 & 6 & 2 \\ 1 & 10 & -4 \\ 2 & 3 & 7 \end{vmatrix} = 450$$

For the node voltages:

$$V_3 = 12V - 8i_1 \\ = 12 - 8 \times (-0.0333) \\ = 12.2664 V$$

$$\Delta 3 = \begin{vmatrix} 7 & -1 & 6 \\ 1 & -7 & 10 \\ 2 & 4 & 3 \end{vmatrix} = -338$$

$$V_2 = V_3 - 4i_2 \\ = 12.2664 V - 1.8333 \times 4 \\ = 4.9333 V$$

$$I_1 = \frac{\Delta 1}{\Delta} = -0.0333 A$$

$$I_2 = \frac{\Delta 2}{\Delta} = -2.5 A$$

$$I_3 = \frac{\Delta 3}{\Delta} = 1.8667 A$$

$$V_1 = V_2 - 8i_4 \\ = 4.9333 - 8 \times (-0.6333) \\ = 10 V$$

Problem 6: Write all the mesh current equations and put them in the matrix form. You don't need to solve

Solution:

kVL @ supermesh I :

$$3k\Omega I_1 + (I_1 - I_3) \times 1k\Omega + (I_2 - I_4) 4k\Omega = 0 \quad (1)$$

kVL @ supermesh II :

$$6k\Omega (I_3 - I_5) + 8k\Omega (I_4 - I_5) + 8k\Omega I_4 + 4k\Omega (I_4 - I_2) + 1k\Omega (I_3 - I_1) = 0 \quad (2)$$

kVL @ mesh 5 :

$$2k\Omega I_5 + 8k\Omega (I_5 - I_4) + 6k\Omega (I_5 - I_3) = 0 \quad (3)$$

$$2k\Omega - I_3 + I_4 = 2mA \quad (4)$$

$$I_1 - I_2 + 2I_5 = 0 \quad (5)$$

Suppose all the current are in the order of mA range.
We can remove kΩ to simplify the equations, because

$$1k\Omega \times 1mA = 1\Omega \times 1A = 1V.$$


Eg. 1) :

$$4I_1 + 4I_2 - I_3 - 4I_4 = 0$$

$$\bar{E}_6^{(2)} : -I_1 - 4I_2 + 7I_3 + 20I_4 - 14I_5 = 0$$

$$\bar{E}_6^{(3)} : -6I_3 - 8I_4 + 16I_5 = 0$$

$$\bar{E}_6^{(4)} : -I_3 + I_4 = 2$$

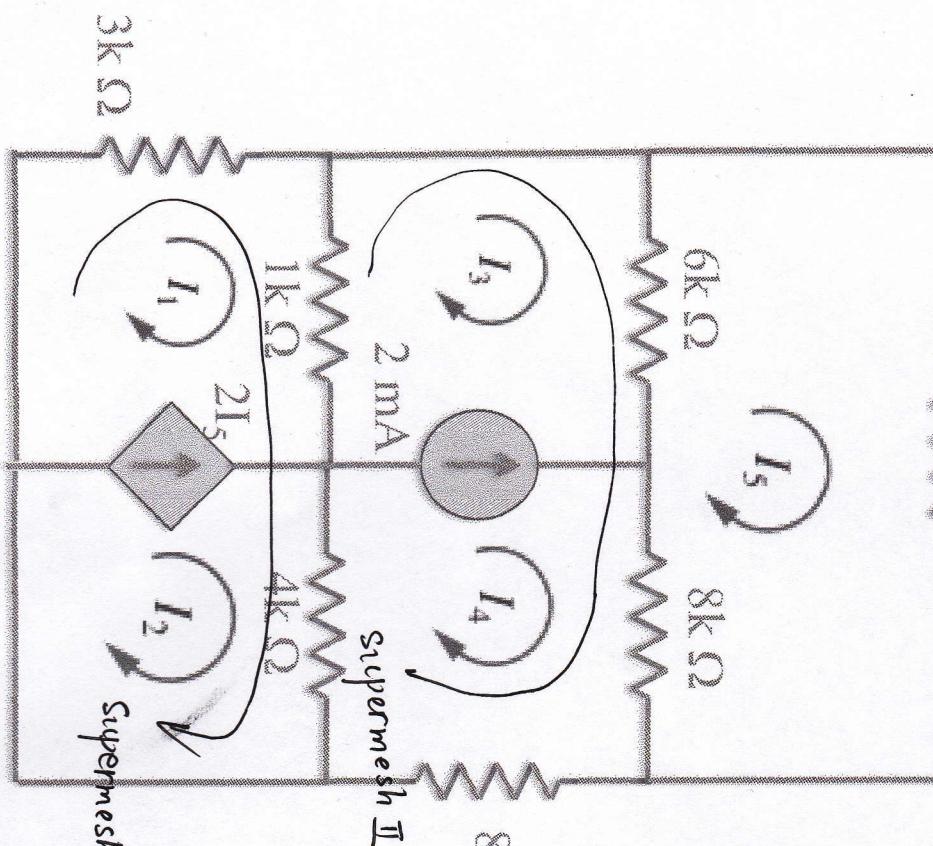


matrix form:

$$\begin{bmatrix} -4 & 4 & -1 & 4 & 0 \\ -1 & -4 & 7 & 20 & -14 \\ 0 & 0 & -6 & -8 & 16 \\ 0 & 0 & -1 & 1 & 0 \\ 1 & -1 & 0 & 0 & 2 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \\ I_4 \\ I_5 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 0 \\ 0 \\ 2 \end{bmatrix}$$

$I_1, I_2 \dots I_6$ should have units of mA.

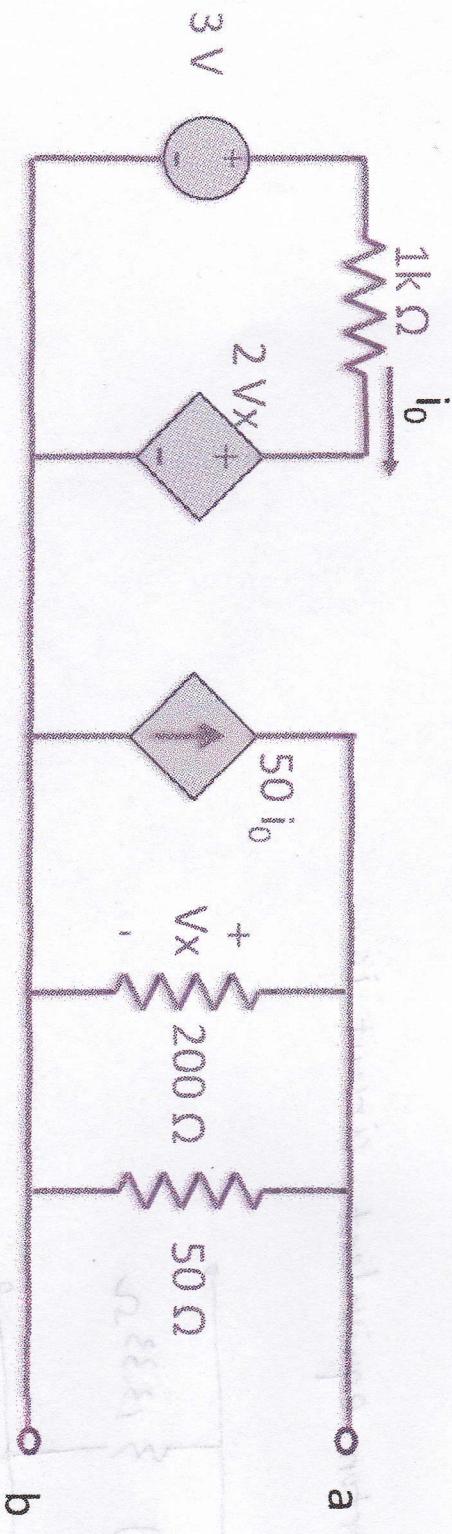Problem 7: Obtain the Thevenin and Norton equivalent as seen from a-b terminals:



So Solution :

$$i_0 = \frac{3V - 2Vx}{1k\Omega}$$

$$3600i_0 = 3 \\ i_0 = 10^{-3}A \quad i_0 = 6 \times 10^{-4} A$$

$$Vx = 50i_0 \times (200\Omega // 50\Omega)$$

$$= 40 \times 10^{-3}$$

$$i_0 = \frac{3 - 2000i_0}{1000} \quad 4000i_0$$

$$= 2V \quad Vx = 1.2V$$

$$\therefore V_{ab} = 2V \quad V_{ab} = 1.2V$$

$$R_{th} = \frac{V_{ab}}{I_{ab}} = \frac{2V}{150mA} = 13.33\Omega$$

$$R_{th} = 1.2 / 0.15 = 8 \text{ ohm}$$

Now let's short a-b ports with a wire, then $Vx = 0$


$$\therefore i_0 = \frac{3V}{1k\Omega} = 3mA$$

$$I_{ab} = 10i_0 = 150mA$$


$$R_{th} = \frac{V_{ab}}{I_{ab}} = \frac{2V}{150mA} = 13.33\Omega$$

$$R_{th} = 1.2 / 0.15 = 8 \text{ ohm}$$

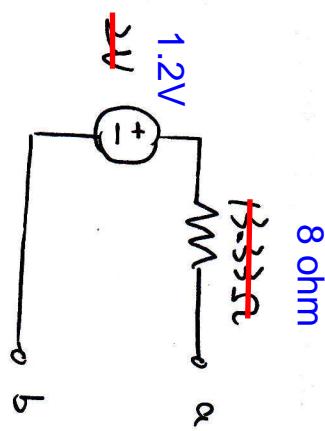
Therefore, the Thevenin equivalent circuit is



The Norton equivalent circuit is

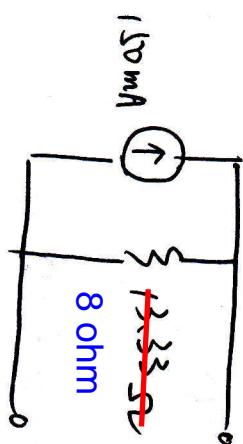

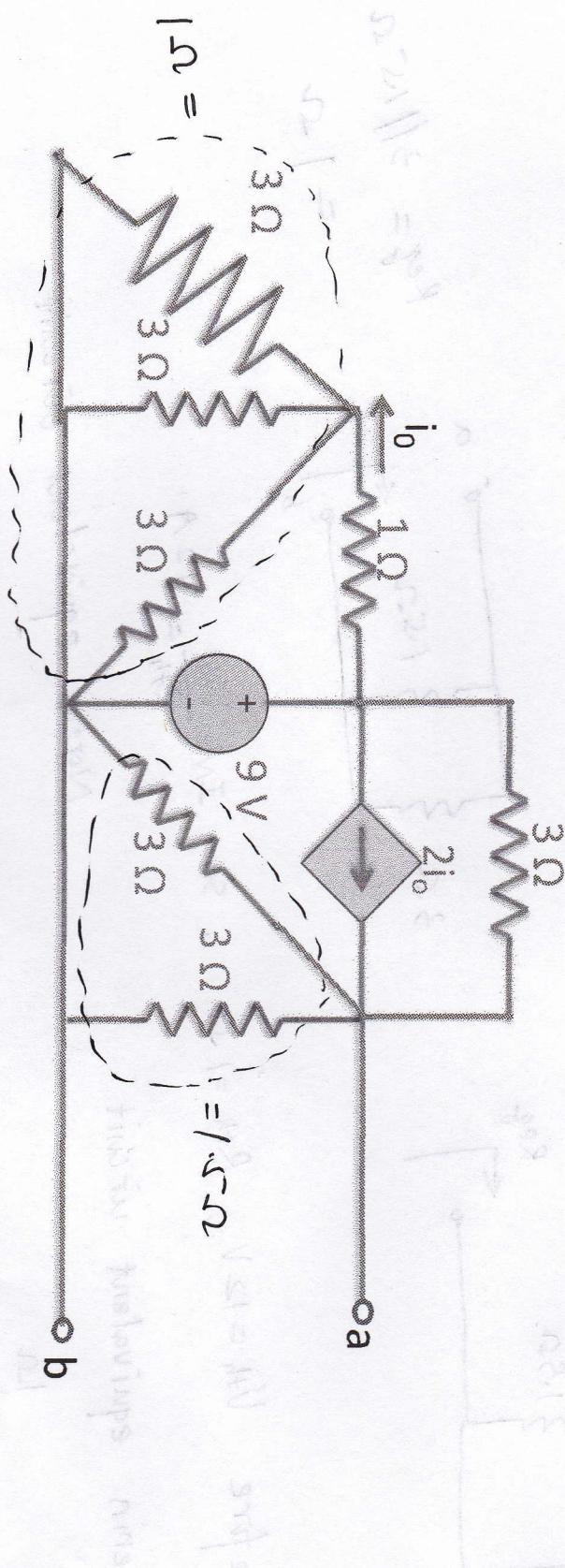Problem 8: Obtain the Thevenin and Norton equivalent as seen from a-b terminals:




Solution: The above circuit can be simplified as the following equivalent circuit


$$i_o = \frac{9V}{2\Omega} = 4.5A$$

$$KCL @ \text{node 1: } 2i_o + \frac{9 - V_1}{3\Omega} - \frac{V_1}{1.5\Omega} = 0$$


$$\Rightarrow V_{oc} = 12V$$

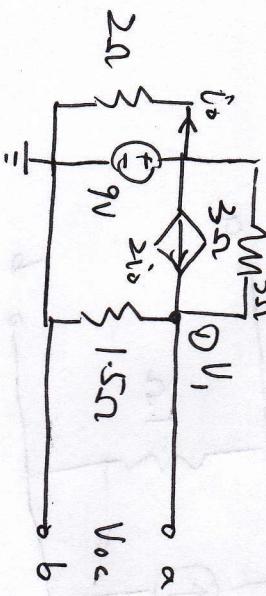

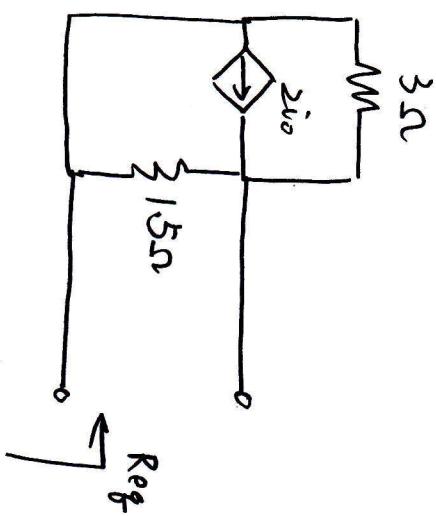To obtain Thevenin equivalent resistance, we short circuit the independent voltage source, the equivalent circuit is as follows:




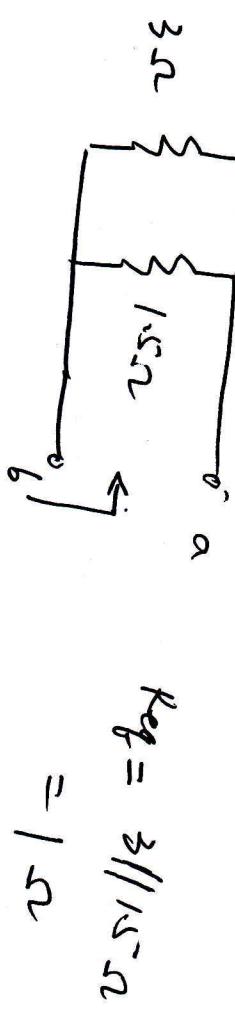Since $i_o = 0$, therefore the CCCS can be viewed as open circuit
the circuit can be simplified further:



Therefore $V_{th} = 12V$, $R_{th} = 1\Omega$, so $I_{in} = \frac{V_{th}}{R_{th}} = 12A$

Thevenin equivalent circuit

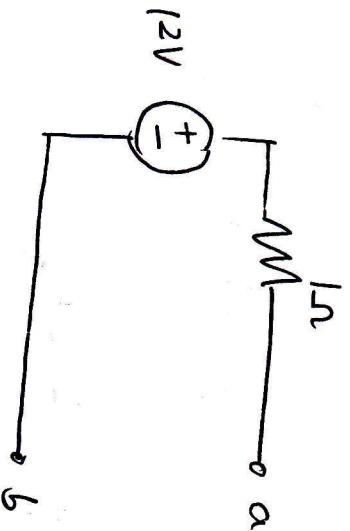

Norton equivalent circuit

