

# EECS 70A: Network Analysis

## Homework #4


- The homework is due Thursday 5/29/2014 at 5:30pm.
- You can choose either way to turn in your homework.
  - 1) Turn it in during discussions (Highly recommended)
  - 2) Turn it in during TA or Grader's office hour
  - 3) Slide it under TA's lab office door (Any time before deadline @EH5109)
- Note: lab location is different from office hour location.

Problem 1:

- A) Given  $v(t) = 8 \cos(\omega t + \pi/4)$  find the phasor  $\mathbf{V}$  that represents  $v(t)$ .  
Express  $\mathbf{V}$  as  $x+jy$  and as  $re^{i\phi}$ .
- B) Given  $i(t) = 4 \sin(\omega t + \pi/4)$  find the phasor  $\mathbf{I}$  that represents  $i(t)$ .  
Express  $\mathbf{I}$  as  $x+jy$  and as  $re^{i\phi}$ .
- C) Given  $\mathbf{V} = 8 + j6$  find  $v(t)$ .
- D) Given  $\mathbf{I} = 2 + 2j$ , find  $i(t)$ .

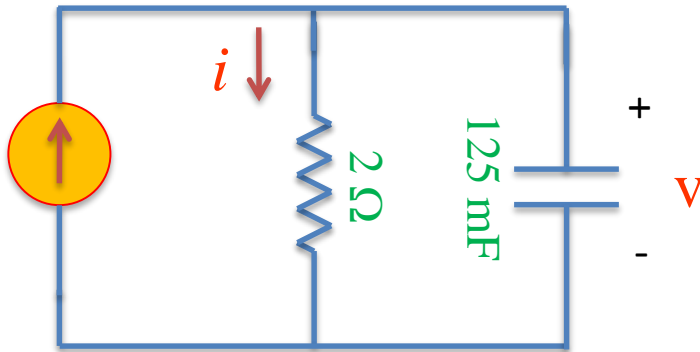
Problem 2:

$$I_s(t) = 3 \cos(4t + 45^\circ) \text{ A}$$




Find  $i(t)$  and  $v(t)$ . Hint: convert the current source into a phasor, then find the current and voltage phasors for the whole circuit, then convert back to the time dependent  $i(t)$ ,  $v(t)$ .

Problem 3:

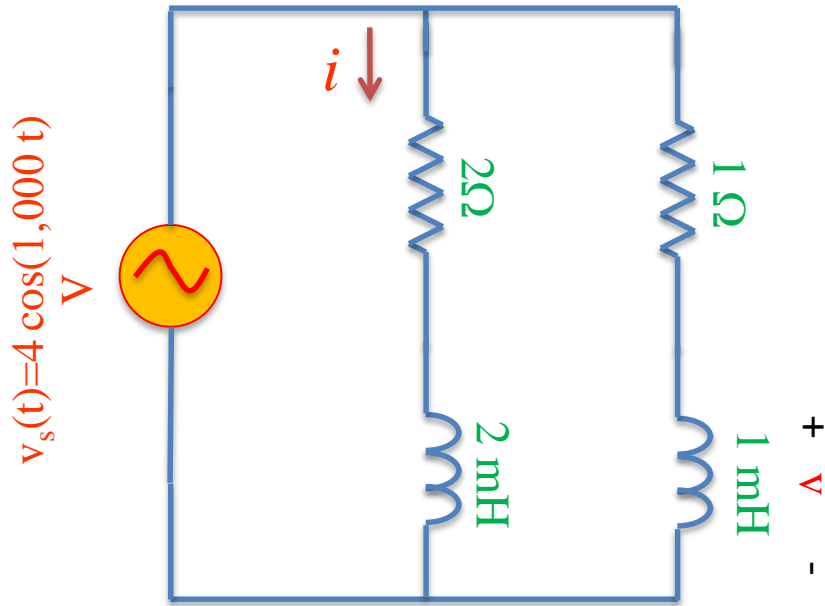

Find  $i(t)$  and  $v(t)$ . Hint: convert the voltage source into a phasor, then find the current and voltage phasors for the whole circuit, then convert back to the time dependent  $i(t)$ ,  $v(t)$ .

Problem 4: Find  $v(t)$ .

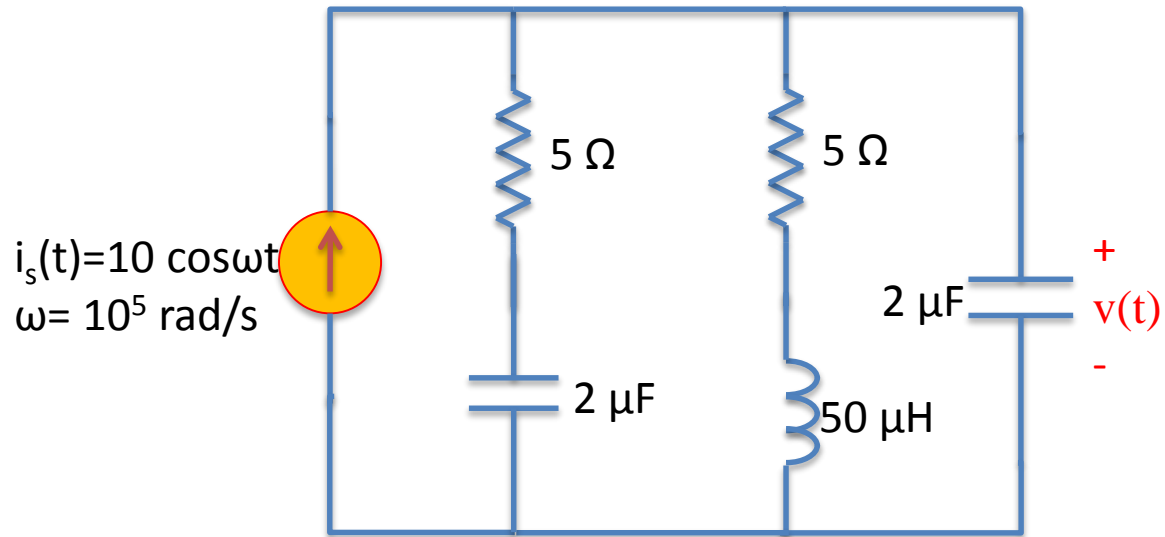

Problem 5: Suppose the following circuit has been run for enough long time.(Initial conditions are ignored.)

Find  $i(t)$ ,  $V_1(t)$ ,  $V_2(t)$  for this circuit. In class, we used phasors. For the HW, I want you to do it WITHOUT phasors!

