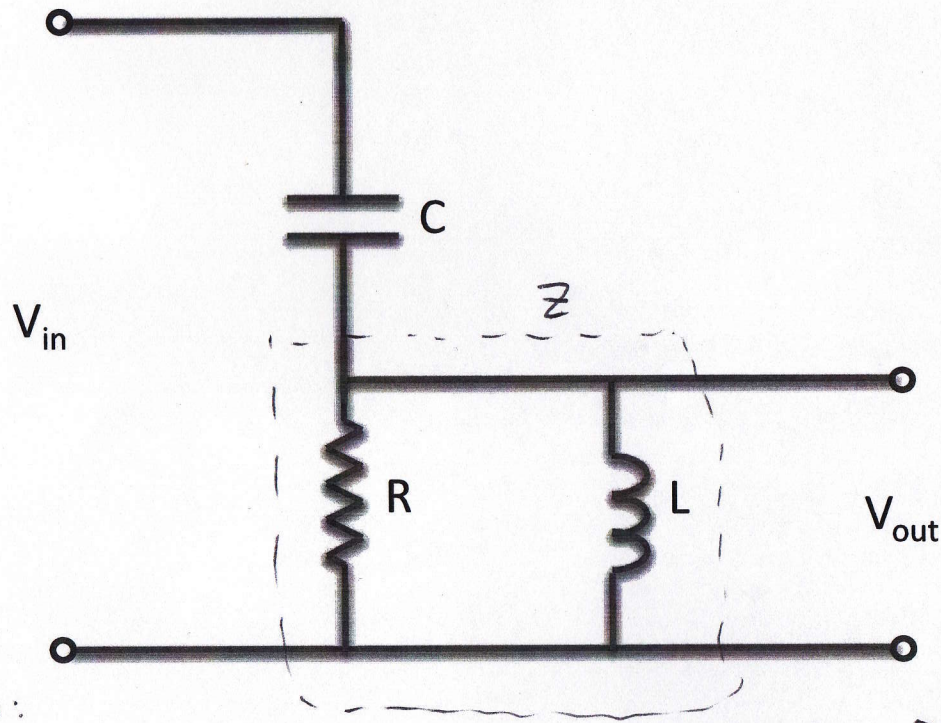


Problem 1: Find the transfer function of the circuit.



Solution:

$$H(\omega) = \frac{V_{out}}{V_{in}} = \frac{Z}{Z + \frac{1}{j\omega C}}$$

$$Z = R \parallel j\omega L = \frac{R \cdot j\omega L}{R + j\omega L}$$

$$\therefore H(\omega) = \frac{\frac{R \cdot j\omega L}{R + j\omega L}}{\frac{R \cdot j\omega L}{R + j\omega L} + \frac{1}{j\omega C}}$$

$$H(\omega) = \frac{R \cdot j\omega L}{R \cdot j\omega L + \frac{1}{j\omega C} (R + j\omega L)}$$

$$= \frac{R \cdot j\omega L \cdot j\omega C}{R \cdot j\omega L \cdot j\omega C + R + j\omega L}$$

$$= \frac{-\omega^2 RLC}{-\omega^2 RLC + R + j\omega L}$$

Problem 2: Given $H(\omega) = \frac{1}{1+j\omega\tau_1} \cdot \frac{j\omega\tau_2}{1+j\omega\tau_2}$, where $\tau_2 > \tau_1$, please draw the Bode plot (only magnitude) of the transfer function.

Extra credit: Try to design a circuit having such a transfer function.

Solution:


$$H(\omega) = \frac{1}{1+j\omega\tau_1} \cdot \frac{j\omega\tau_2}{1+j\omega\tau_2}$$

poles at $\begin{cases} \omega_{p1}\tau_1 = 1 \Rightarrow \omega_{p1} = \frac{1}{\tau_1} \\ \omega_{p2}\tau_2 = 1 \Rightarrow \omega_{p2} = \frac{1}{\tau_2} \end{cases}$


zero at $\omega_z \cdot \tau_2 = 0 \Rightarrow \omega_z = 0$.

The zero is located at the origin.

and $|H(0)| = 0$, if the unit is dB, then $|H(0)|$ is negative infinity.

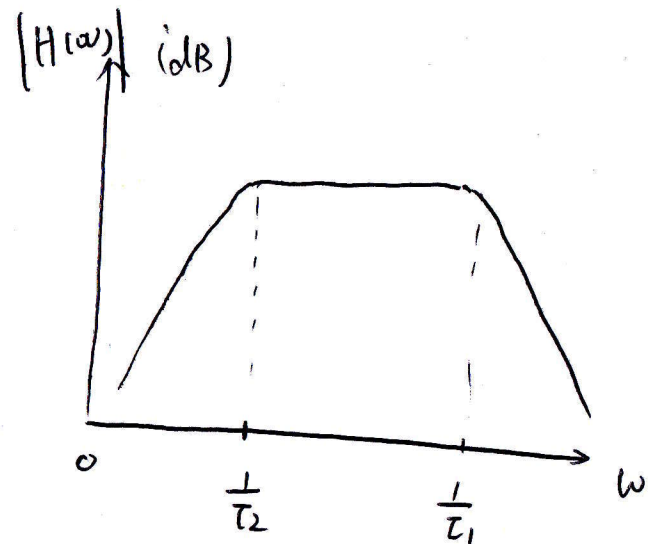

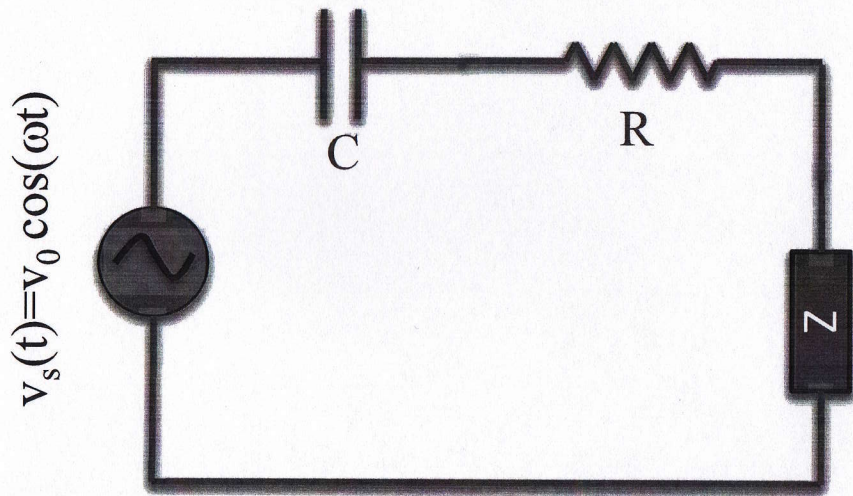Problem 3: Given $R = 5 \Omega$, $C = 2 \text{ mF}$, $\omega = 100 \text{ rad/s}$. Find the impedance of Z so as to maximize the power transfer.




The Thevenin equivalent impedance is

$$Z_{th} = R + \frac{1}{j\omega C} = 5 + \frac{1}{j \times 2 \times 10^{-3} \times 100} = 5 - 5j$$

When the load matches the conjugate of Z_{th} , the load gets the maximum power.

$$Z = Z_{th}^* = 5 + 5j$$

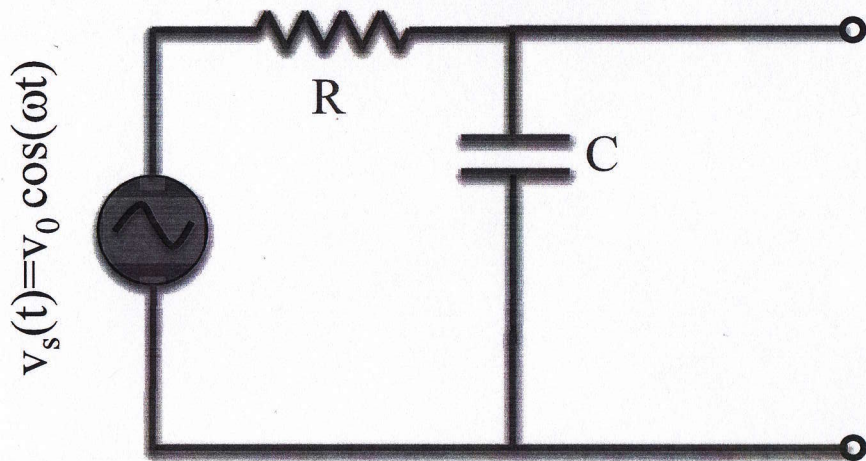
Problem 4: Find V_{th} and R_{th} , and draw the Thevenin equivalent circuit for the following circuit.



$$\begin{aligned} \underline{V_{th}} &= \underline{V_{oc}} = \frac{\frac{1}{j\omega C}}{\frac{1}{j\omega C} + R} \cdot \underline{V_s} \\ &= \frac{1}{1 + j\omega RC} \cdot \underline{V_s} \\ &= \frac{V_0}{1 + j\omega RC} \end{aligned}$$

Solution:


$\underline{Z_{th}}$:

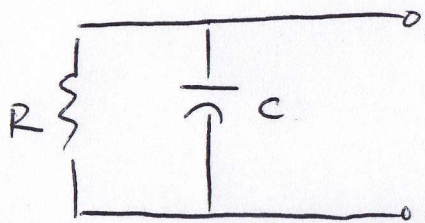

$$\underline{Z_{th}} = R \parallel \frac{1}{j\omega C} = \frac{R \cdot \frac{1}{j\omega C}}{R + \frac{1}{j\omega C}}$$

$$= \frac{R}{1 + j\omega RC}$$

Thevenin equivalent circuit

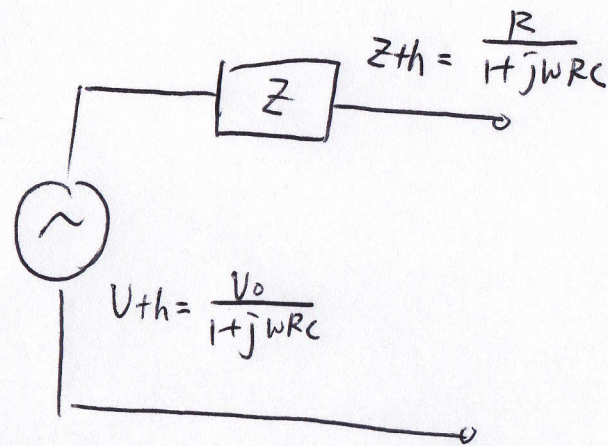

Problem 5: Given the transfer function $H(\omega)$ of a system,

if the input is $V_{in}(t) = \text{Re}\left(\sum_n a_n e^{j\omega_n t}\right)$

then the output can be expressed as $V_{out}(t) = \text{Re}\left[\sum_n a_n H(\omega_n) e^{j\omega_n t}\right]$

where $H(\omega) = |H(\omega)| e^{j\phi(\omega)}$

Now, for a system, the Bode plot of its transfer function is illustrated in the next page, and $\omega_0 \tau = 1$

If the input voltage is $V_{in}(t) = \text{Re}(1V \cdot e^{j\omega_1 t} + 1V \cdot e^{j\omega_2 t})$

Find the output voltage for the following cases:

a) $\omega_1 = 0.1\tau^{-1}$ $\omega_2 = 10\tau^{-1}$

b) $\omega_1 = 0.01\tau^{-1}$ $\omega_2 = 100\tau^{-1}$

$\angle H(\omega_1) = 0$

$\angle H(\omega_2) = -90^\circ = -\frac{\pi}{2}$

Solution $\omega_0 \tau = 1 \Rightarrow \omega_0 = \frac{1}{\tau}$

a) $\omega_1 = 0.1 \tau^{-1} = 0.1 \omega_0$

$\omega_2 = 10 \tau^{-1} = 10 \omega_0$

from Bode plot, $|H(\omega_1)| = 0 \text{ dB}$

$|H(\omega_2)| = -20 \text{ dB}$



$\therefore |H(\omega_1)| = 1$

$|H(\omega_2)| = \frac{1}{10}$

$V_{out}(t) = \text{Re}\left[1V \cdot H(\omega_1) \cdot e^{j\omega_1 t} + 1V \cdot H(\omega_2) \cdot e^{j\omega_2 t}\right]$

$= \text{Re}\left[1 \cdot e^{j\omega_1 t} + \frac{1}{10} e^{-j\frac{\pi}{2}} \cdot e^{j\omega_2 t}\right]$

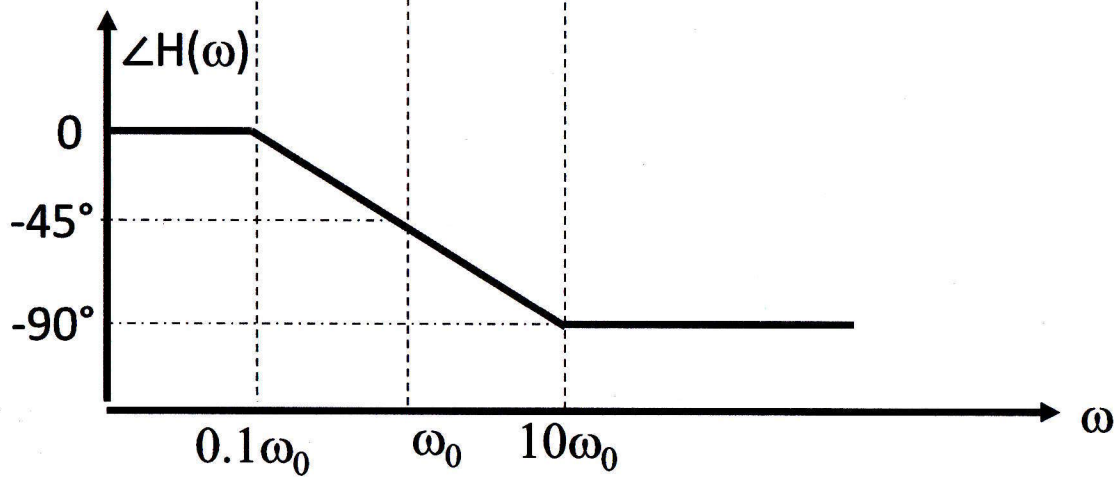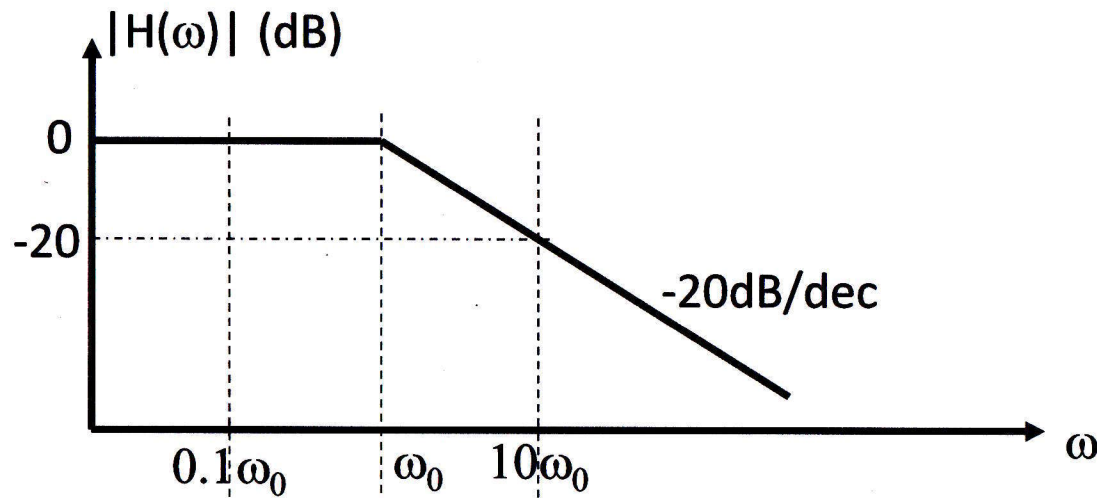$= \cos \omega_1 t + \frac{1}{10} \cos(\omega_2 t - \frac{\pi}{2})$



b). $\omega_1 = 0.01 \tau^{-1} = 0.01 \omega_0$

$\omega_2 = 100 \tau^{-1} = 100 \omega_0$

from Bode plot

$|H(\omega_1)| = 1 \quad \angle H(\omega_1) = 0$

$|H(\omega_2)| = -40 \text{ dB} = \frac{1}{100}, \quad \angle H(\omega_2) = -90^\circ$

$V_{out}(t) = \text{Re} [1 \cdot H(\omega_1) e^{j\omega_1 t} + \frac{1}{100} \cdot H(\omega_2) e^{j\omega_2 t}]$

$= \text{Re} [e^{j\omega_1 t} + \frac{1}{100} e^{-j\frac{\pi}{2}} e^{j\omega_2 t}]$

$= \cos \omega_1 t + \frac{1}{100} \cos(\omega_2 t - \frac{\pi}{2})$