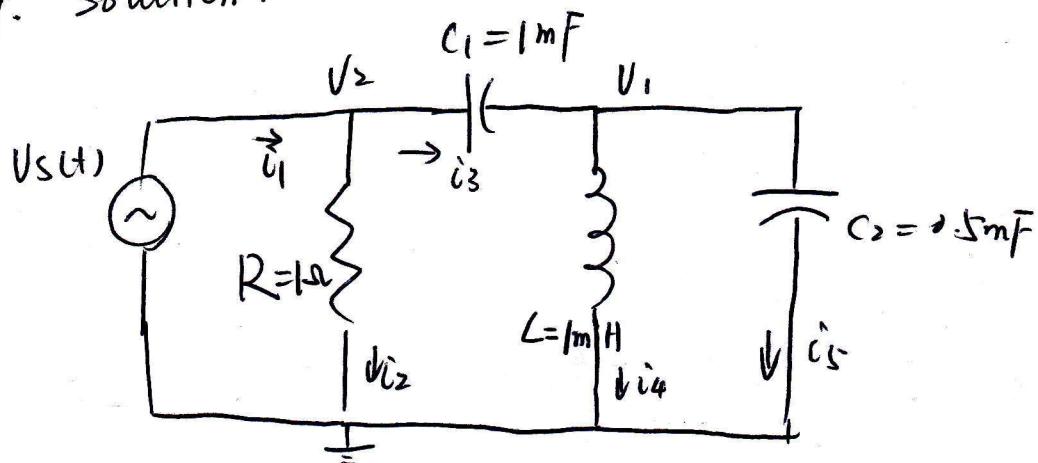


1. Solution:



and currents

use nodal analysis to find the node voltages in phasor

$$U_S = 1 \text{ V} \quad \omega = 1000 \text{ rad/s}$$

$$\frac{1}{j\omega C_1} = -j \Omega, \quad \frac{1}{j\omega C_2} = -2j \Omega, \quad j\omega L = j \Omega$$

$$\left\{ \begin{array}{l} U_2 = 1 \\ \frac{U_2 - U_1}{\frac{1}{j\omega C_1}} = \frac{U_1}{j\omega L} + \frac{U_1}{\frac{1}{j\omega C_2}} \end{array} \Rightarrow \frac{1 - U_1}{-j} = \frac{U_1}{j} + \frac{U_1}{-2j} \right.$$

$$U_1 - 1 = U_1 - \frac{U_1}{2} \Rightarrow U_1 = 2$$

$$i_2 = \frac{U_2}{R} = \frac{1}{1} = 1 \text{ A}$$

$$i_3 = \frac{U_2 - U_1}{-j} = \frac{1 - 2}{-j} = -j \text{ A}$$

$$i_4 = \frac{U_1}{j\omega L} = \frac{2}{j} = -2j \text{ A}$$

$$i_5 = \frac{U_1}{\frac{1}{j\omega C_2}} = \frac{2}{-2j} = j \text{ A}$$

$$i_1 = i_2 + i_3 = 1 - j \text{ A}$$

in time domain

$$V_2(t) = \operatorname{Re}[V_2 e^{j\omega t}] \\ = \cos(\omega t) = \cos(100\pi t) \cdot V.$$

$$V_1(t) = \operatorname{Re}[V_1 e^{j\omega t}] = 2 \cos(100\pi t) V.$$

$$i_1(t) = \operatorname{Re}[i_1 e^{j\omega t}] = \operatorname{Re}[\sqrt{2} e^{-j\frac{\pi}{4}} e^{j\omega t}] = \sqrt{2} \cos(\omega t - \frac{\pi}{4}) A$$


$$i_2(t) = \operatorname{Re}[i_2 e^{j\omega t}] = \cos(100\pi t) A$$

$$i_3(t) = \operatorname{Re}[i_3 e^{j\omega t}] = \operatorname{Re}[e^{-j\frac{\pi}{2}} e^{j\omega t}] = \cos(\omega t - \frac{\pi}{2}) A$$

$$i_4(t) = \operatorname{Re}[i_4 e^{j\omega t}] = \operatorname{Re}[2 e^{-j\frac{\pi}{2}} e^{j\omega t}] = 2 \cos(\omega t - \frac{\pi}{2}) A$$

$$i_5(t) = \operatorname{Re}[i_5 e^{j\omega t}] = \operatorname{Re}[e^{j\frac{\pi}{2}} e^{j\omega t}] = \cos(\omega t + \frac{\pi}{2}) A$$

2. Solution:

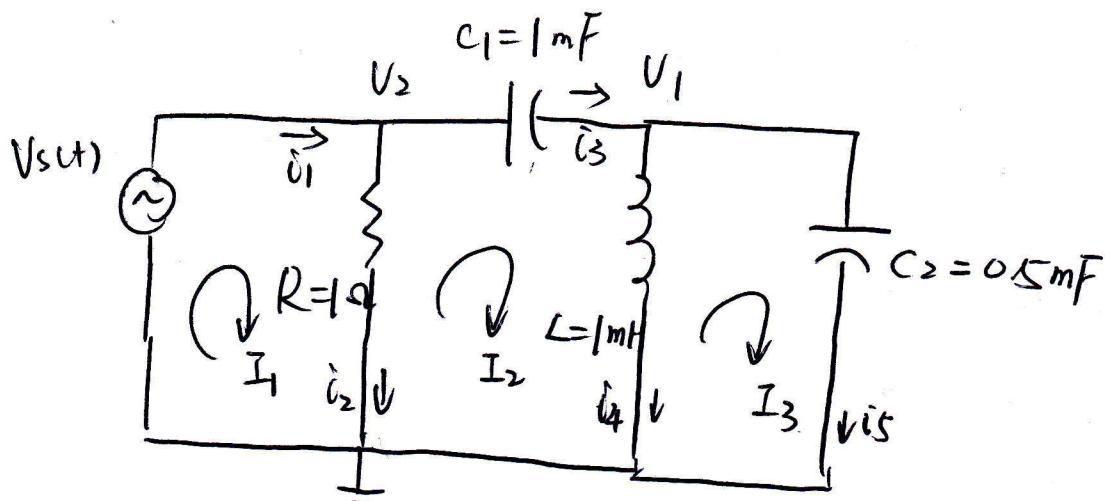

use mesh analysis to find the node voltages and currents in phasor, and then change them into time domain.

Loop I:

$$I = I_R (\underline{I}_1 - \underline{I}_2) \quad (1)$$

Loop II:

$$I_R (\underline{I}_2 - \underline{I}_1) + \underline{I}_2 (-j) + (\underline{I}_2 - \underline{I}_3) \cdot j = 0 \quad (2)$$

Loop III:

$$(\underline{I}_3 - \underline{I}_2) \cdot j + \underline{I}_3 (-j) = 0 \quad (3)$$

Substitute (1) into (2)

$$-j \underline{I}_2 + j \cdot \underline{I}_2 - \underline{I}_3 \cdot j - 1 = 0$$

$$\underline{I}_3 = \frac{-1}{j} = j \text{ A} \quad (4)$$

Substitute (4) into (3)

$$\underline{I}_3 \cdot j - 2j \underline{I}_3 - j \underline{I}_2 = 0$$

$$-j \underline{I}_2 = j \underline{I}_3$$

$$\underline{I_2} = -\underline{I_3} = -j \text{ A} \quad (5)$$

Substitute (5) into (1)

$$\underline{I_1} = 1 + \underline{I_2} = 1 - j \text{ A}$$

$$\underline{V_1} = \underline{I_1} = 1 - j \text{ A}$$

$$\underline{i_2} = I_1 - I_2 = 1 \text{ A}$$

$$\underline{v_3} = I_2 = -j \text{ A}$$

$$\underline{i_4} = I_2 - I_3 = -2j \text{ A}$$

$$\underline{i_5} = \underline{I_3} = j$$

$$\underline{V_2} = \underline{V_S} = 1 \text{ V}$$

$$\underline{V_1} = \underline{i_4} \cdot jwL = -2j \cdot j = 2 \text{ V}$$

in time domain:

$$V_1(t) = 2 \cos 1000t \text{ V}$$

$$V_2(t) = \cos 1000t \text{ V}$$

$$i_1(t) = \sqrt{2} \cos(1000t - \frac{\pi}{4}) \text{ A}$$

$$i_2(t) = \cos(1000t) \text{ A}$$

$$i_3(t) = \cos(1000t - \frac{\pi}{2}) \text{ A}$$

$$i_4(t) = -2 \cos(1000t - \frac{\pi}{2}) \text{ A}$$

$$i_5(t) = \cos(1000t + \frac{\pi}{2}) \text{ A}$$

3. Solution :

A).  $|H(f_1)| = 0 \text{ dB} \Rightarrow |H(f_1)| = 1$

$$V_{\text{out}}(t) = 4 \cos(2\pi f_1 t + \varphi_1) \quad , \quad \varphi_1 \text{ is unknown.}$$

B)  $|H(f_2)| = 0 \text{ dB} \Rightarrow |H(f_2)| = 1$

$$V_{\text{out}}(t) = 3 \cos(2\pi f_2 t + \varphi_2) \quad , \quad \varphi_2 \text{ is unknown.}$$

C)  $|H(f_3)| = -10 \text{ dB} \Rightarrow |H(f_3)| = 10^{-\frac{10}{20}} = 10^{-0.5} = \frac{1}{\sqrt{10}}$

$$V_{\text{out}}(t) = \frac{5}{\sqrt{10}} \cos(2\pi f_3 t + \varphi_3) \quad , \quad \varphi_3 \text{ is unknown.}$$


D)  $|H(f_4)| = -20 \text{ dB} \Rightarrow |H(f_4)| = 10^{-1} = 0.1$

$$\begin{aligned} V_{\text{out}}(t) &= \frac{1}{10} \cdot 10 \cos(2\pi f_4 t + \varphi_4) \\ &= 0.1 \cos(2\pi f_4 t + \varphi_4) \quad , \quad \varphi_4 \text{ is unknown} \end{aligned}$$

E)  $|H(f_5)| = -40 \text{ dB} \Rightarrow |H(f_5)| = 10^{-2} = 0.01$

$$\begin{aligned} V_{\text{out}}(t) &= 0.01 \times 10 \cos(2\pi f_5 t + \varphi_5) \\ &= 0.1 \cos(2\pi f_5 t + \varphi_5) \quad , \quad \varphi_5 \text{ is unknown.} \end{aligned}$$

4. Solution.

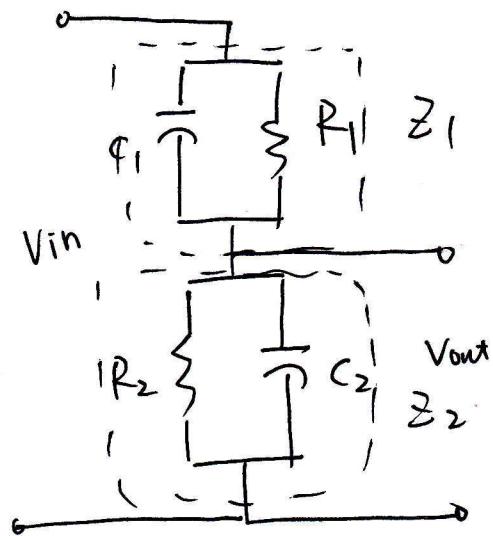

$$Z_1 = R_1 \parallel \frac{1}{j\omega C_1} = \frac{R_1 \cdot \frac{1}{j\omega C_1}}{R_1 + \frac{1}{j\omega C_1}} = \frac{R_1}{1 + j\omega R_1 C_1}$$

$$Z_2 = R_2 \parallel \frac{1}{j\omega C_2} = \frac{R_2 \cdot \frac{1}{j\omega C_2}}{R_2 + \frac{1}{j\omega C_2}} = \frac{R_2}{1 + j\omega R_2 C_2}$$

$$H(\omega) = \frac{Z_2}{Z_1 + Z_2}$$


$$= \frac{\frac{R_2}{1 + j\omega R_2 C_2}}{\frac{R_2}{1 + j\omega R_2 C_2} + \frac{R_1}{1 + j\omega R_1 C_1}}$$

$$H(\omega) = \frac{R_2}{R_2 + \frac{1 + j\omega R_2 C_2}{1 + j\omega R_1 C_1} \cdot R_1}$$

$$= \frac{1}{1 + \frac{1 + j\omega R_2 C_2}{1 + j\omega R_1 C_1} \cdot \frac{R_1}{R_2}}$$


Two extreme cases:

$$|H(0)| = \frac{1}{1 + \frac{R_1}{R_2}} = \frac{R_2}{R_1 + R_2}$$

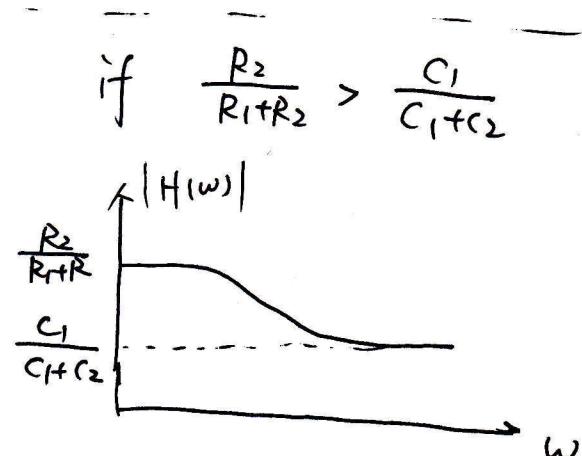


$$|H(\infty)| = \frac{1}{1 + \frac{R_2}{R_1} \cdot \frac{R_2 C_2}{R_1 C_1} \cdot \frac{R_1}{R_2}}$$
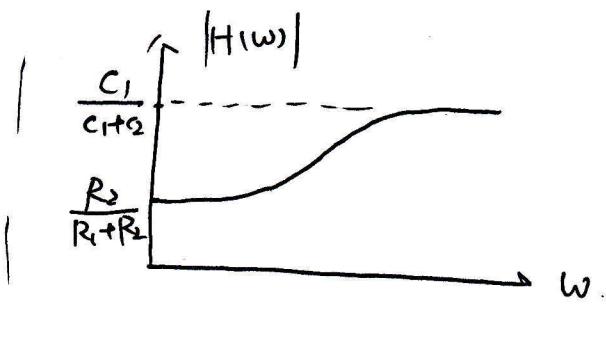
$$= \frac{1}{1 + \frac{C_2}{C_1}} = \frac{C_1}{C_1 + C_2}$$




5. Solution:

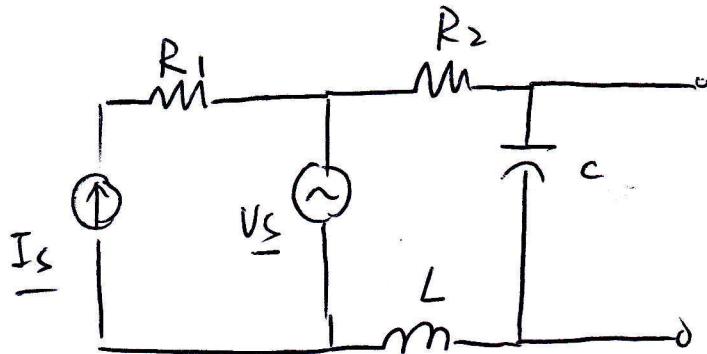

$$\omega = 1000 \text{ rad/s}$$

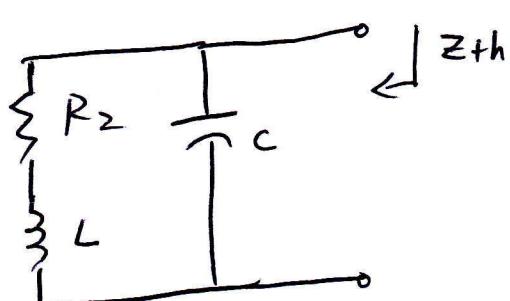To find  $Z_{th}$ , leave the current source as open circuit, leave the voltage source as short circuit.



$$\begin{aligned} Z_{th} &= (R_2 + j\omega L) // \frac{1}{j\omega C} \\ &= (2 + 2j) // -2j \\ &= \frac{(2+2j) \cdot (-2j)}{2+2j-2j} \\ &= 2-2j \Omega \end{aligned}$$

$V_{th} = V_{oc}$ , the current source won't contribute anything to the open circuit voltage, because it is fixed by  $V_S$ .

$$V_{oc} = \frac{\frac{1}{j\omega C}}{R_2 + \frac{1}{j\omega C} + j\omega L} \cdot V_S = \frac{-2j \times 10}{2-2j+2j} = -j10$$

$$\therefore V_{th} = -10j \text{ V}$$

When  $Z = Z_{th}$ , the load gets maximum transfer power

$$\begin{aligned} \therefore Z &= Z_{th} = 2+2j \\ \text{and, } P_{max} &= \frac{|V_{th}|^2}{8R_{th}} = \frac{|10|^2}{8 \times 2} = 6.25 \text{ W}, \text{ where } R_{th} = \operatorname{Re}[Z_{th}] \end{aligned}$$