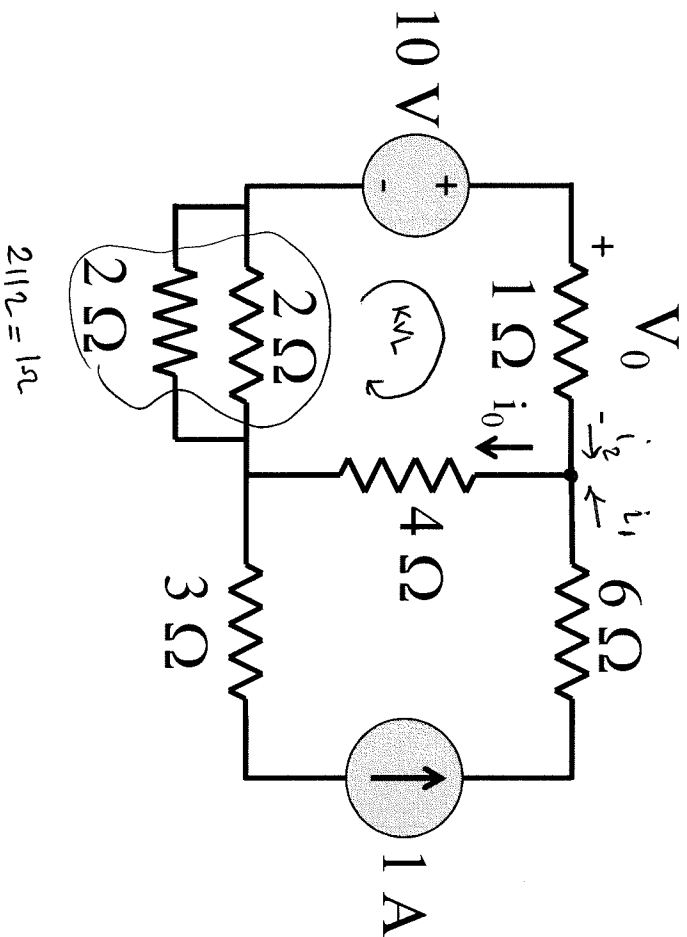




Problem 2: Find  $V_0$  and  $i_0$  in the circuit below.



$$\text{KVL: } -10 + V_0 + 4i_0 + 1 \times i_2 = 0$$

$$\Rightarrow 4i_0 + 2i_2 = 10 \text{ V}$$

$$\text{KCL: } i_0 = i_2 + i_1 \Rightarrow i_0 \neq i_2 + 1$$

$$i_1 = 1 \text{ A}$$

$$4i_0 + 2(i_0 - 1) = 10 \text{ V}$$


$$6i_0 - 2 = 10 \text{ V}$$

$$i_0 = \frac{12}{6} = 2 \text{ A}$$

$$i_2 = i_0 - 1 = 1 \text{ A}$$

$$V_0 = 1 \text{ V} \times 1 \text{ A} = 1 \text{ V}$$

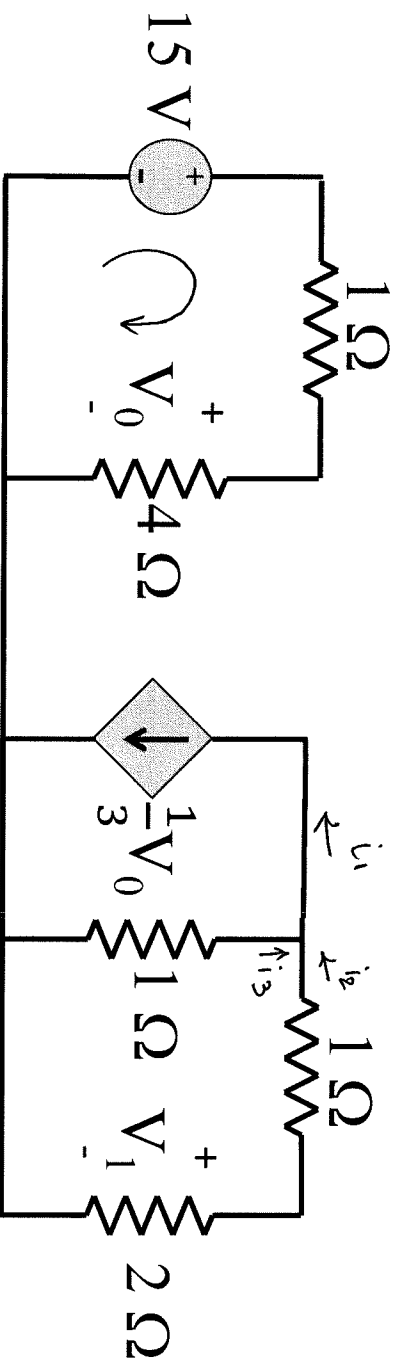Problem 3: Find  $V_1$  in the circuit below.




$$V_0 = \frac{4}{4+1} \times 15 = \frac{4 \times 15}{5} = 12V$$

$$i_1 = \frac{1}{3} \times V_0 = 4A$$

$$i_2 = i_1 \times \frac{1\Omega}{1\Omega + 3\Omega} = 4 \times \frac{1}{4} = 1A$$

$$V_1 = -i_2 \times 2\Omega = -2V$$

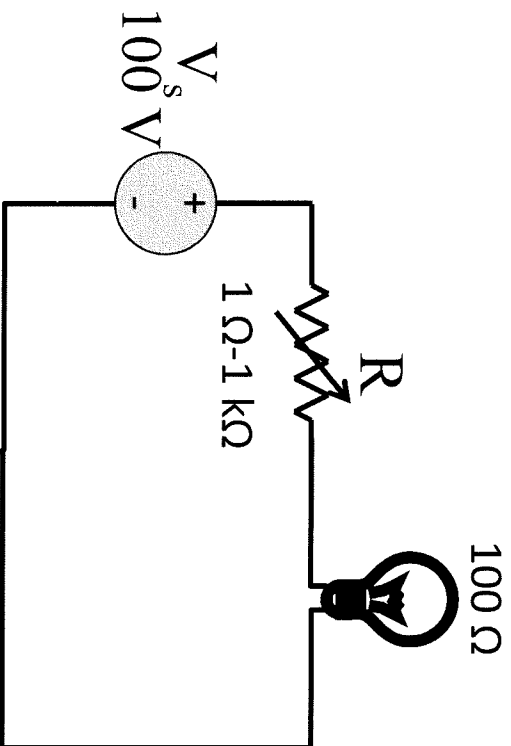Problem 4: Dimmer circuit: the variable resistor can be changed from  $1\Omega$  to  $1\text{ k}\Omega$  to adjust the power delivered to the bulb. Find the power supplied or absorbed by each circuit element for the resistor set to minimum and maximum values. At which limit is the bulb brighter? (note: you can round up the numbers to simplify the calculations)



$$\text{at } R = 1\Omega \quad i = \frac{100\text{ V}}{101\Omega} \approx 1\text{ A}$$

$$P_R = i^2 R = 1 \times 1 = 1\text{ W}$$

$$P_{\text{bulb}} = 1^2 \times 100 = 100\text{ W}$$

$$P_{\text{source}} = i \times V = 1\text{ A} \times 100\text{ V} = 100\text{ W}$$

$$\text{at } R = 1\text{ k}\Omega \quad i = \frac{100\text{ V}}{1100\Omega} \approx 0.1\text{ A}$$

$$P_R = (0.1)^2 \times 1000 = 10\text{ W}$$

$$P_{\text{bulb}} = (0.1)^2 \times 100 = 1\text{ W}$$

$$P_{\text{source}} = 100 \times 0.1 = 10\text{ W}$$

	$P_{\text{bulb}}$	$P_{\text{resistor}}$	$P_{\text{source}}$
$R = 1\Omega$	100 W	1 W	100 W
$R = 1\text{ k}\Omega$	1 W	10 W	100 W