

Announcements:


1. Etc etc etc

Note: Video did not get recorded on replay because of technical error.

EECS 70A: Network Analysis

Lecture 10

Capacitors

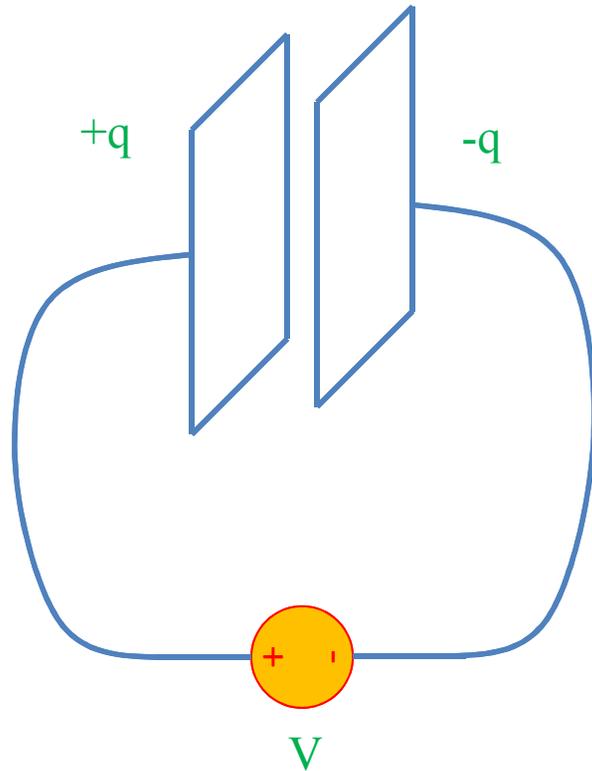

$$q = CV$$

$$C = \frac{\epsilon A}{d}$$

A=area
d=plate separation

Farads[F] = Coulombs/Volt [C]/[V]


$$\epsilon_0 = 8.85 \times 10^{-12} \text{ F / m}$$

$$\epsilon = K\epsilon_0$$

Dielectric constant:

$$K = 3.9 \text{ SiO}_2$$

$$K = 25 \text{ HfO}_2$$

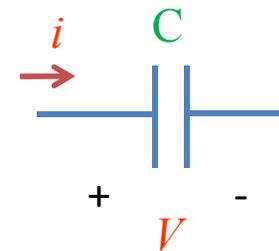

Time dependence

$$q = CV \quad i = \frac{dq}{dt} = C \frac{dV}{dt}$$

q, V, i can depend on time !

Implicit:



$$q(t) = CV(t) \quad i(t) = \frac{dq(t)}{dt} = C \frac{dV(t)}{dt}$$

Will not always write (t), but it is assumed from now on.

$$i(t) = C \frac{dV(t)}{dt} \Rightarrow V(t) = \frac{1}{C} \int i(t) dt$$
$$\Rightarrow q(t) = \int i(t) dt$$

Example Problem #2

(Students): Find $i(t)$, $q(t)$

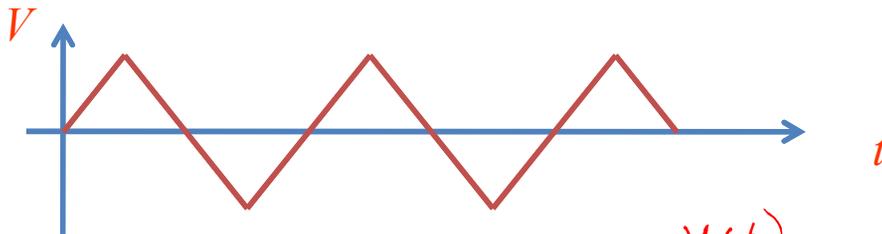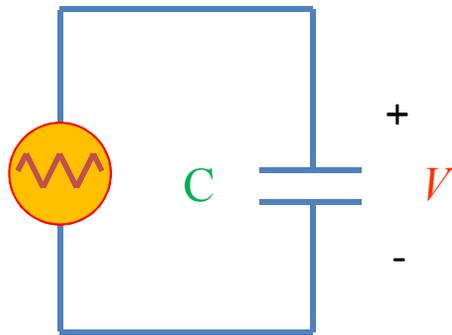

$$q = cV$$

$$i = \frac{dq}{dt} = c \frac{dV}{dt}$$


$$V = \frac{1}{c} \int i dt$$



Example Capacitor Problem #2

$q = CV$
 $i = C \frac{dV}{dt}$
 $V =$

Find $V(t)$, $q(t)$

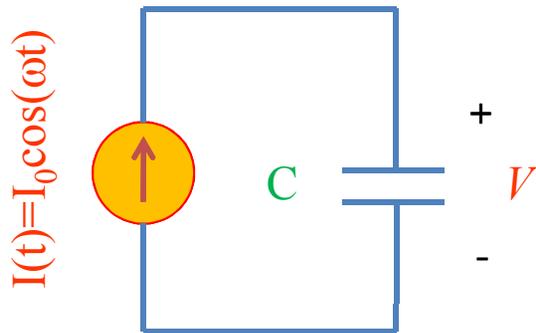

$$V = \frac{1}{C} \int i(t) dt$$

$$= \frac{1}{C} \int I_0 \cos(\omega t) dt = \frac{I_0}{C} \int \cos(\omega t) dt$$

$u = \omega t \quad du = \omega dt$
 $dt = \frac{1}{\omega} du$

$$= \frac{I_0}{C} \int \cos(u) du \frac{1}{\omega}$$

$$= \frac{I_0}{\omega C} \sin u = \frac{I_0}{\omega C} \sin(\omega t) = V(t)$$

blue V
red i

$$I(t) = \text{Re}[I_0 e^{j\omega t}]$$

claim

why?

$$z = x + jy \quad \text{Re}[z] = x$$

$$\text{Re}[I_0 e^{j\omega t}] = \text{Re}[I_0 (\cos(\omega t) + j \sin(\omega t))] = I_0 \cos(\omega t)$$


Euler $e^{j\theta} = \cos \theta + j \sin \theta$
"phasor"

$$V(t) = \frac{1}{C} \int I(t) dt = \frac{1}{C} \int \text{Re}[I_0 e^{j\omega t}] dt = \frac{1}{C} I_0 \int \text{Re}[e^{j\omega t}] dt =$$

$$\frac{1}{C} I_0 \text{Re} \left[\int e^{j\omega t} dt \right] = \frac{1}{C} I_0 \text{Re} \left[\frac{1}{j\omega} e^{j\omega t} \right] = \text{Re} \left[\frac{I_0}{j\omega C} e^{j\omega t} \right] = V(t)$$

$$\text{Re} \left[I_0 e^{j\omega t} \right] = I(t)$$

CAP.

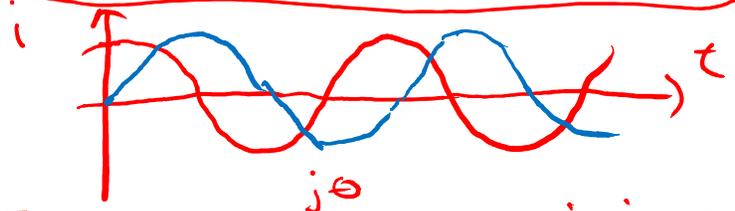

$$\int e^{j\omega t} dt = \int e^u \frac{du}{j\omega} = \frac{1}{j\omega} \int e^u du$$

$$u = j\omega t$$

$$du = j\omega dt$$

$$dt = \frac{1}{j\omega} du$$

$$= \frac{1}{j\omega} e^u = \frac{1}{j\omega} e^{j\omega t}$$

↪
back

Phasors

$$I(t) = \text{Re} \left[\underbrace{I_0 e^{j\omega t}}_{\text{CURRENT PHASOR}} \right]$$


$$V(t) = \text{Re} \left[\underbrace{\frac{1}{j\omega C} I_0 e^{j\omega t}}_{\text{VOLTAGE PHASOR}} \right]$$

Voltage phasor \vec{V}

Current phasor \vec{I}

For a capacitor we have $\vec{V} = \vec{I} \underbrace{\frac{1}{j\omega C}}_{\text{"impedance"}}$

Parallel Capacitors

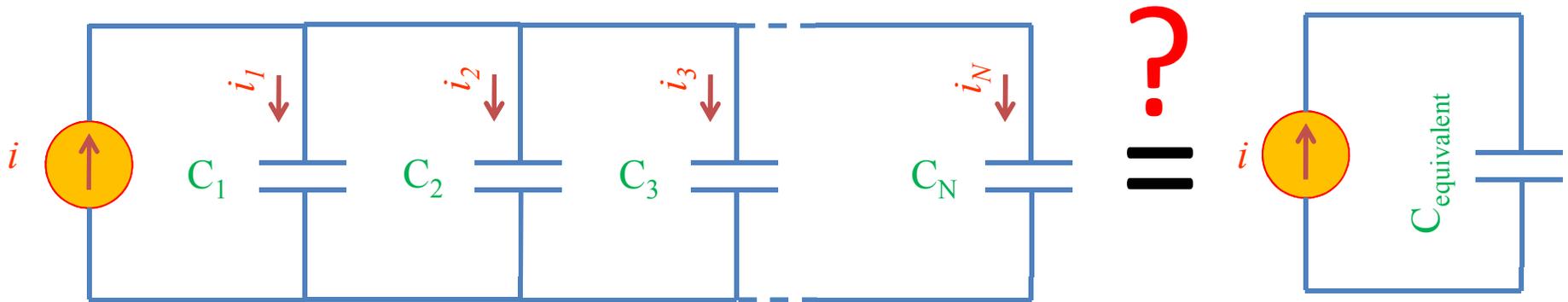

KCL $i = i_1 + i_2 + i_3 + \dots + i_N$

$$i_1 = C_1 \frac{dV}{dt} \quad i_2 = C_2 \frac{dV}{dt} \quad \dots \quad i_N = C_N \frac{dV}{dt}$$



$$i = C_1 \frac{dV}{dt} + C_2 \frac{dV}{dt} + \dots + C_N \frac{dV}{dt}$$

$$= \frac{dV}{dt} (C_1 + C_2 + \dots + C_N) = \frac{dV}{dt} \left[\sum_{k=1}^N C_k \right]$$

$$i = [C_{\text{eq}}] \frac{dV}{dt}$$

$$C_{\text{eq}} = \sum_{k=1}^N C_k$$

Series Capacitors

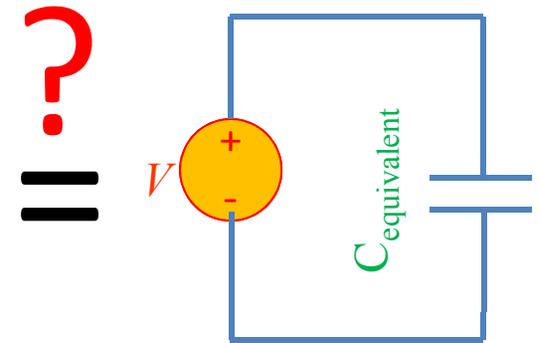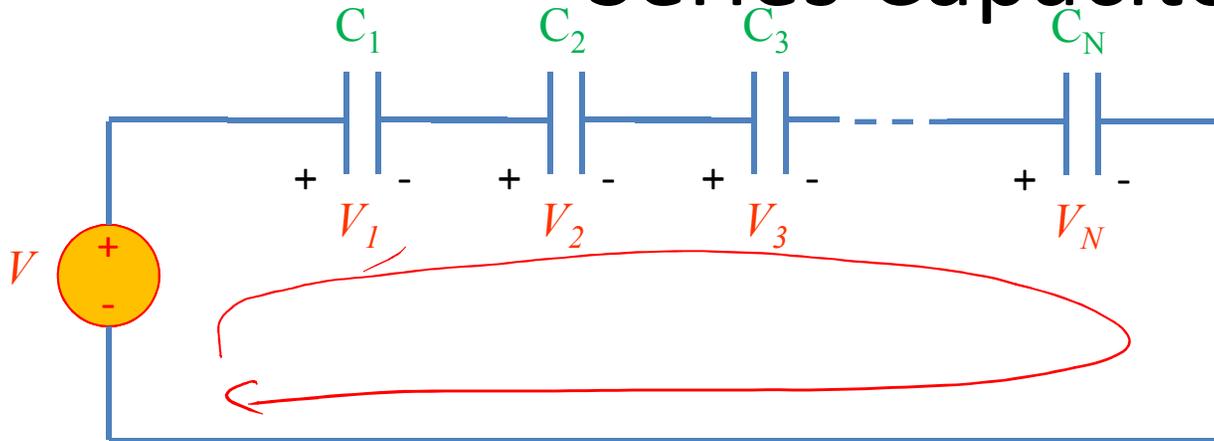

$$V = V_1 + V_2 + \dots + V_N$$

$$\Rightarrow V_1 = \frac{1}{C_1} \int i dt \quad V_2 = \frac{1}{C_2} \int i dt$$

$$i_1 = i_2 = i_3 = \dots = i$$

$$= \frac{1}{C_1} \int i dt + \frac{1}{C_2} \int i dt + \dots + \frac{1}{C_N} \int i dt$$


$$= \int i dt \left(\frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_N} \right)$$

C_{eq}^{-1}

$$\frac{1}{C_{\text{eq}}} = \frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_N}$$

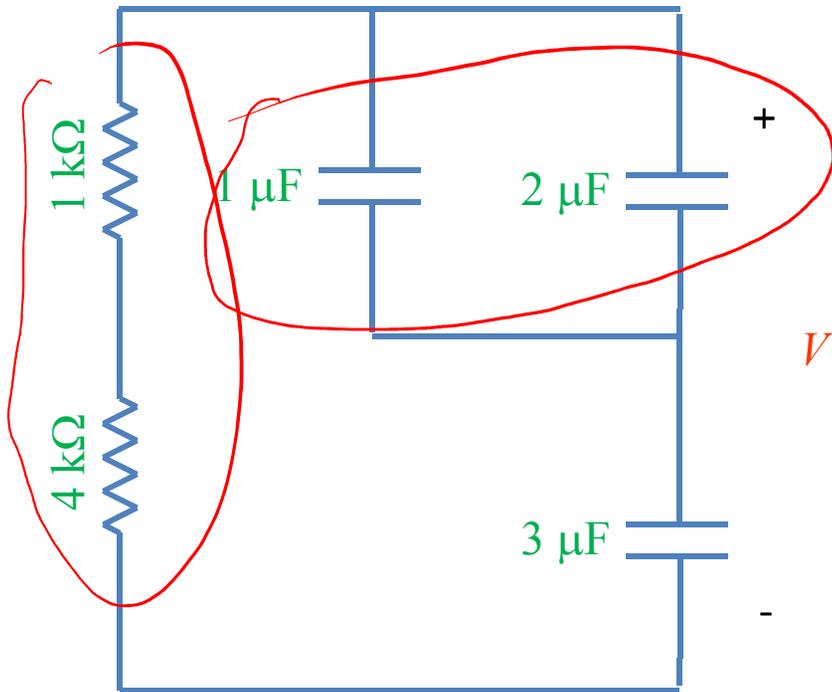
Example problem #4

(Students) Find $V(t)$, given that $V(t=0) = 5$ Volts



$$K = 10^3$$


$$\mu = 10^{-6}$$

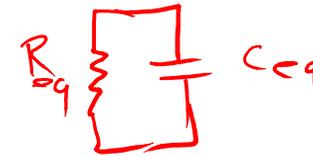

$$R_{eq} = 5 \text{ k}\Omega$$

$$V(t) = V(t=0) e^{-t/RC}$$

V

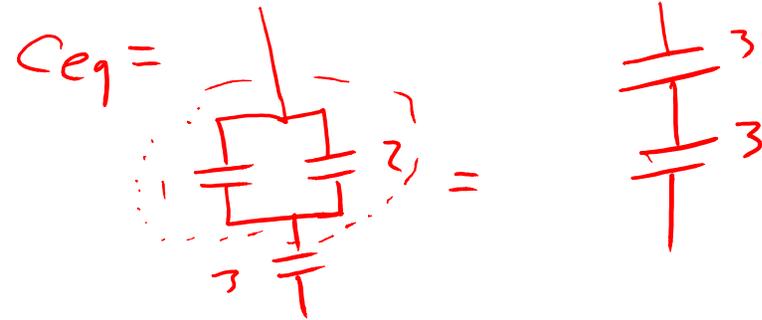

$$= \frac{1}{\frac{1}{3} + \frac{1}{3}} = \frac{3}{2} \mu\text{F}$$

$-t/\tau$


$$V(t) = 5 \text{ V } e^{-t/\tau}$$

$$\tau = R_{eq} C_{eq} = 5 \text{ k}\Omega \cdot \frac{3}{2} \mu\text{F} = 7.5 \cdot 10^3 \Omega \cdot 10^{-6} \text{ F}$$

$$= 7.5 \cdot 10^{-3} \text{ s} = \underline{\underline{7.5 \text{ ms}}}$$

Inductors

$$I(t) = I_0 \cos(\omega t)$$

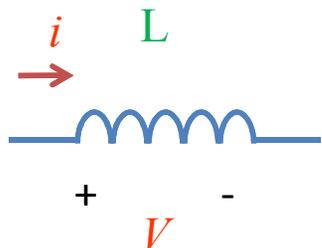

$$L = \frac{N^2 \mu A}{l}$$

A=area

l=wire length

N = # of turns

$\mu = 4 \pi 10^{-6} \text{ H/m}$

$$V = L \frac{di}{dt}$$

compare cap.


$$i = C \frac{dV}{dt}$$

Henry[H]


$$\Rightarrow i = \frac{1}{L} \int v dt$$

Blue v

Red i

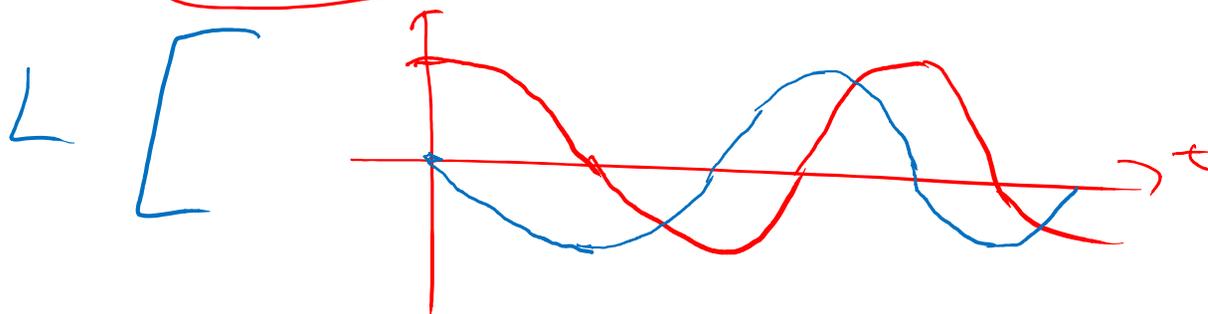

Series Inductors

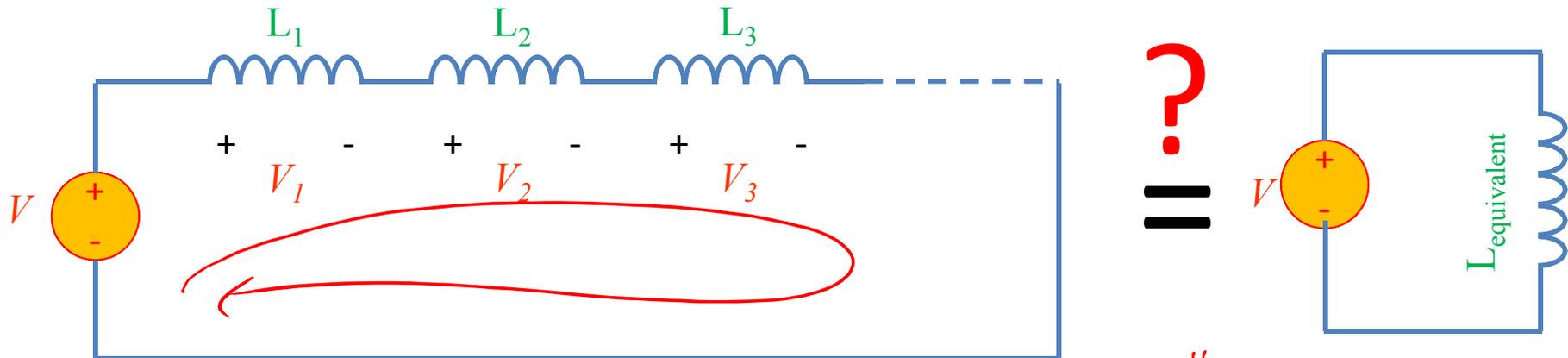


KVL $V = V_1 + V_2 + \dots + V_N$ $i_1 = i_2 = \dots = i_N = i$

$$V_1 = L_1 \frac{di}{dt} \quad V_2 = L_2 \frac{di}{dt} \quad \dots \quad V_N = L_N \frac{di}{dt}$$

$$V = L_1 \frac{di}{dt} + L_2 \frac{di}{dt} + \dots + L_N \frac{di}{dt} = \frac{di}{dt} (L_1 + L_2 + \dots + L_N)$$

$$L_{\text{eq}} = L_1 + L_2 + \dots + L_N = \sum_{i=1}^N L_N$$

Parallel Inductors

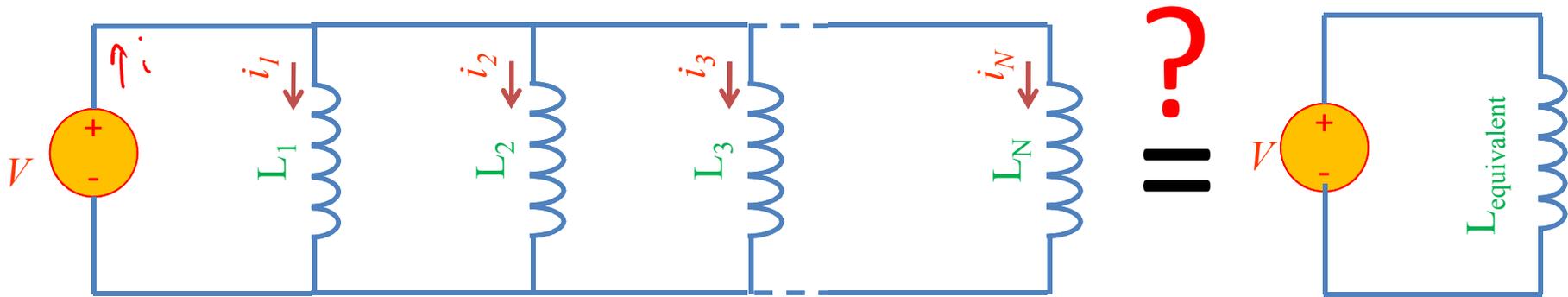

KCL $i = i_1 + i_2 + \dots + i_N$ $v_1 = v_2 = \dots = v_N = "v"$

$$i_1 = \frac{1}{L_1} \int v dt \quad i_2 = \frac{1}{L_2} \int v dt \quad \dots$$


$$i = \frac{1}{L_1} \int v dt + \frac{1}{L_2} \int v dt + \dots + \frac{1}{L_N} \int v dt$$

$$= \left(\frac{1}{L_1} + \frac{1}{L_2} + \dots + \frac{1}{L_N} \right) \int v dt$$


$$\frac{1}{L_{\text{eq}}} = \frac{1}{L_1} + \frac{1}{L_2} + \dots + \frac{1}{L_N}$$

Example Inductor Problem

(Students): Find $V(t)$.

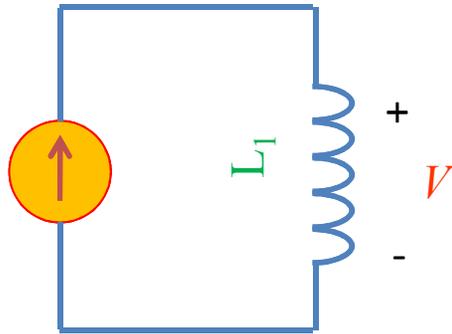




$$V = L \frac{di}{dt}$$

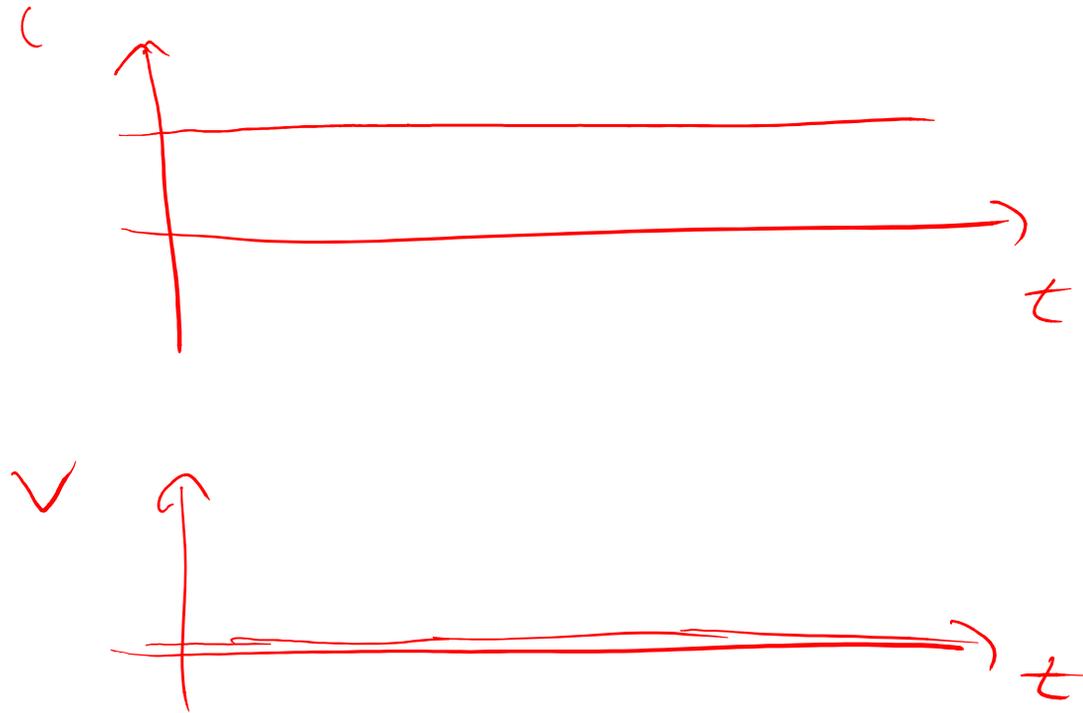

DC: cap looks like "open"
ind looks like "short"

Example Inductor Problem #2

(Students): Find $i(t)$

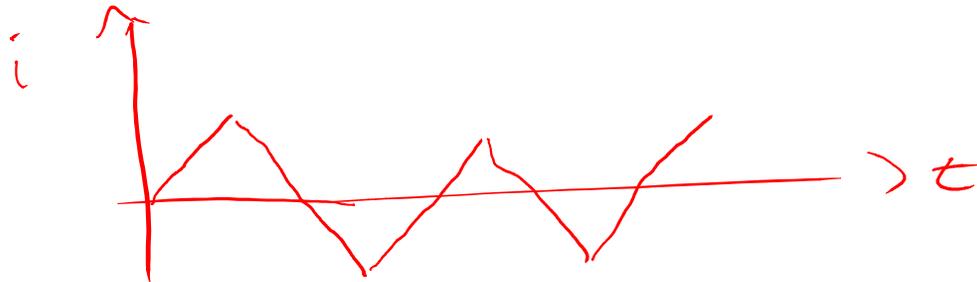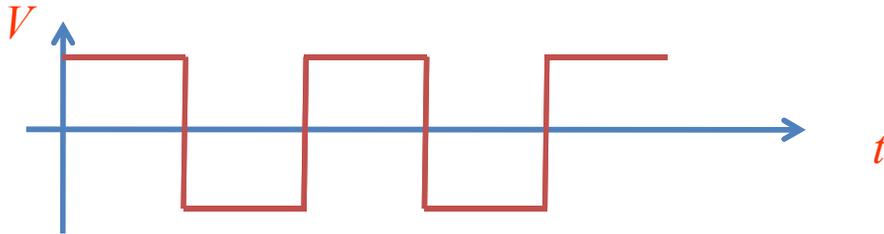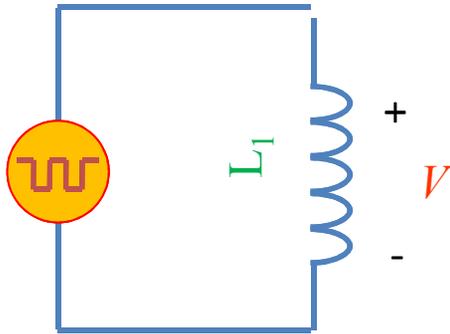


$$v = L \frac{di}{dt}$$

$$i = \frac{1}{L} \int v dt$$

Example Inductor Problem #3

Find $V(t)$

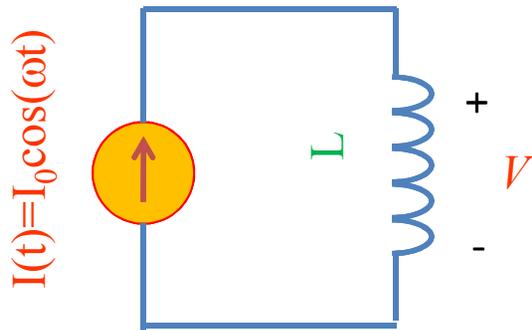

$$V(t) = L \frac{d}{dt} [I_0 \cos(\omega t)]$$

$$= -I_0 \omega L [\sin(\omega t)] \quad \checkmark$$

current phasor

$$I(t) = \text{Re}[I_0 e^{j\omega t}] = \text{Re}[\underline{I} e^{j\omega t}]$$

$$V(t) = L \frac{d}{dt} [\text{Re} I_0 e^{j\omega t}] = \text{Re} \left[L I_0 \frac{d}{dt} e^{j\omega t} \right]$$

$$= \text{Re} [L I_0 j\omega e^{j\omega t}] = \text{Re} \left[\underbrace{I_0 j\omega L}_{\text{voltage phasor } \underline{V}} e^{j\omega t} \right]$$

Inductor

$$\underline{V} = \underbrace{j\omega L}_{\text{"impedance"}} \underline{I}$$

Impedance = Z



R



$\frac{1}{j\omega C}$




$j\omega L$

$$\overline{V} = Z \overline{I}$$

KVL, KCL, Node / Mesh, Thev. Norton

LR circuit

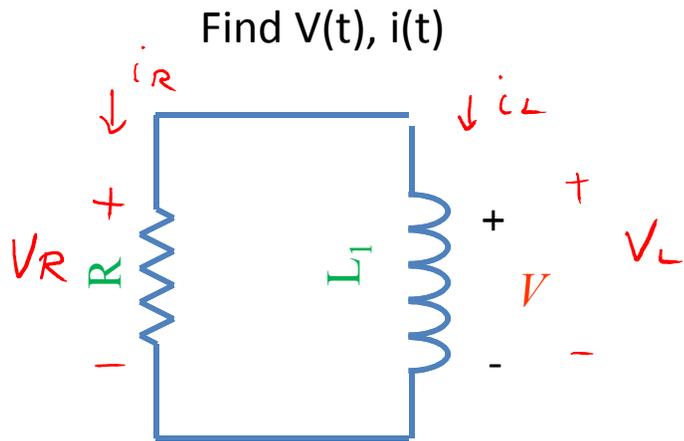

$$\left| \frac{dF(x)}{dx} = aF(x) \right.$$

$$f(x) = ce^{ax}$$

$$c \frac{d}{dx} e^{ax} = ace^{ax} = aF(x)$$

$$KVL \Rightarrow V_L = V_R$$

$$KCL \Rightarrow i_R = -i_L$$

$$L \frac{di_L}{dt} = V_L = V_R = +i_R R = -i_L R$$

$$-i_L R = L \frac{di_L}{dt}$$


$$\frac{di_L}{dt} = -\frac{1}{L/R} i_L$$

$$i_L(t) = i_L(t=0) e^{-t/\tau}$$


$$\tau = \frac{L}{R}$$

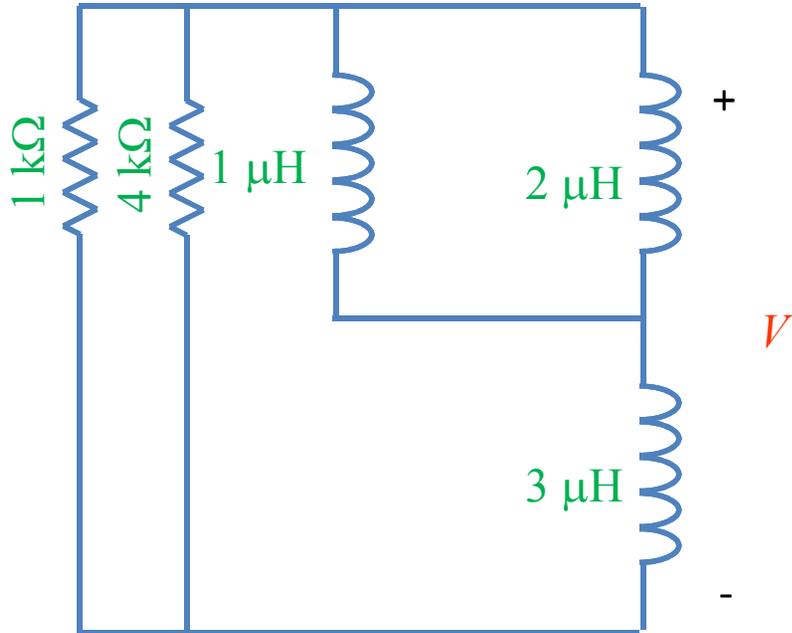Example LR problem

(Students) Find $V(t)$, given that $V(t=0) = 5$ Volts



Power

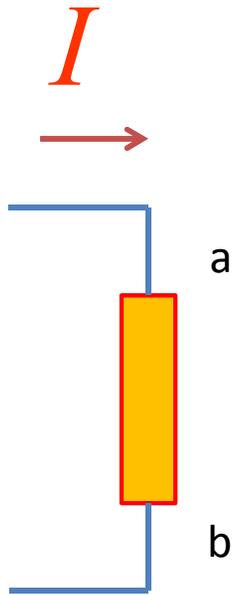

$$I \times V_{ab} = \text{power}$$


Watts [W] = Volt Amp [V-A]

Note: MKSA unit system:
Meters Kilogram Second Amp

Resistor:
Energy lost to heat...

Inductor or capacitor:
Energy **STORED** and can be recovered...

Energy stored

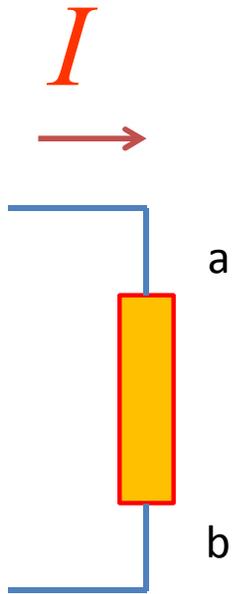

$$I \times V_{ab} = \text{power}$$

Energy:

$$W = \int P dt = \int I \cdot V dt$$




Capacitor stored energy:

$$\int I \cdot V dt = \int C \frac{dV}{dt} \cdot V dt = \frac{1}{2} CV^2 = \frac{Q^2}{2C}$$

Inductor stored energy:

$$\int I \cdot V dt = \int I \cdot L \frac{dI}{dt} dt = \frac{1}{2} LI^2$$

Symbol library

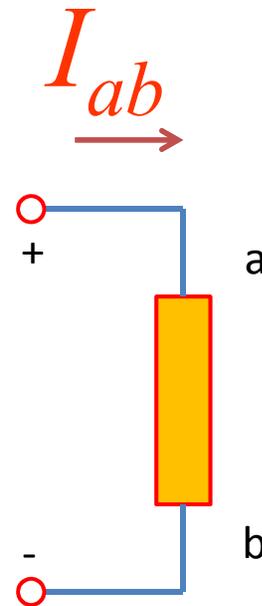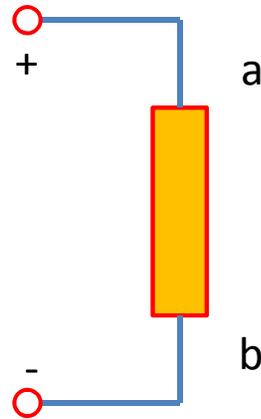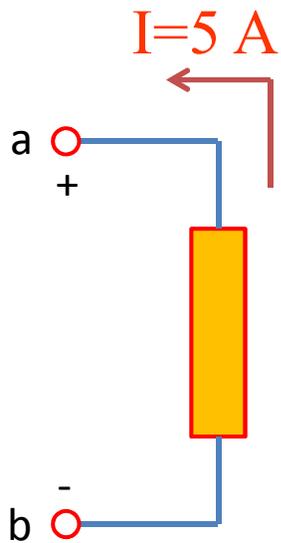

Symbol library

