

EECS 70A: Network Analysis

June 5, 2014

Comprehensive review

Topics covered

- KCL, KVL
- Nodal analysis
- Mesh analysis
- Thevenin/Norton theorem
- RL, RC circuits (time dependence)
- R,L,C circuits
 - Phasors
 - Impedances
 - Transfer function/Bode
 - Power

Nodal Analysis(Review)

Based on KCL, use node voltages as circuits variables.


1. Define a reference node.
2. Label remaining nodes. (n-1 nodes)
3. Apply KCL + ohm to all nodes and supernodes (e.g. V_1, V_2, V_3, \dots)
Express all i's in terms of v's
4. Apply KVL to the voltage source
If one end of voltage source connected to ground, don't need to
5. Solve the n-1 simultaneous equations, to find V's
6. Use Ohm's law to find the currents.

Mesh analysis summary


Based on KVL, use mesh currents as circuit variables.

1. Assign mesh currents i_1, i_2, \dots, i_n
2. Apply KVL + Ohm's law to each mesh
3. Supermesh (if there is a current source present):
 - CASE 1: current source only in one mesh.
 - Already have the current for that mesh => no need to write KVL for that mesh
 - CASE 2: current source exists between two meshes. => create a supermesh
 - Apply KVL to the supermesh
 - Apply KCL to a node in the branch where two meshes intersect
1. Solve the equations for i_1, i_2, \dots, i_n
(e.g. using Kramer's rule)
2. Then solve for voltages using Ohm's law


Thevenin, Norton Theorems:

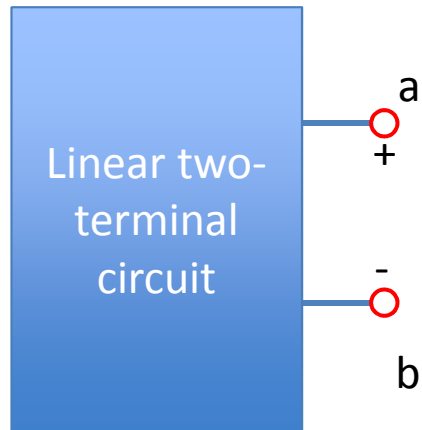

Equivalent to:

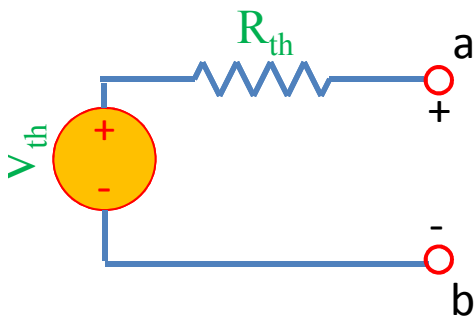

Equivalent to:

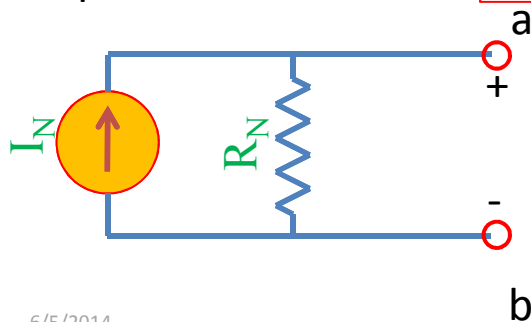

Thevenin:

1. Calculating V_{th} :

Connect nothing to a-b. Calculate voltage. This is V_{th} .

2. Calculating R_{th} :

Method 1:

Connect terminal a to b (short).

Calculate the current from a to b. This is call $I_{short\ circuit}$.

$$R_{th} = V_{th} / I_{short\ circuit}$$

Method 2:

Find the input resistance looking into terminals a-b after all the independent sources have been turned off.

(Voltage sources become shorts, current sources become opens.)

Trick (if dependent sources present):

Apply a 1 A current source to terminals a-b, find V_{ab}

$$R_{th} = V_{ab} / 1A.$$

Norton:

1. Calculating R_N :

$$R_N = R_{th}$$

2. Calculating I_N :

$$I_N = V_{th} / R_{th}$$

Conversion procedures

$$i(t) \rightarrow \mathbf{I}$$

$$i(t) = I_m \cos(\omega t + \phi) \Rightarrow \mathbf{I} = I_m e^{j\phi}$$

$$v(t) \rightarrow \mathbf{V}$$

$$v(t) = V_m \cos(\omega t + \phi) \Rightarrow \mathbf{V} = V_m e^{j\phi}$$

$$\mathbf{I} \rightarrow i(t)$$


$$i(t) = \operatorname{Re}(\mathbf{I} e^{j\omega t})$$

$$\mathbf{V} \rightarrow v(t)$$

$$v(t) = \operatorname{Re}(\mathbf{V} e^{j\omega t})$$

For the exam, you should know how to carry out these procedures.

Circuits

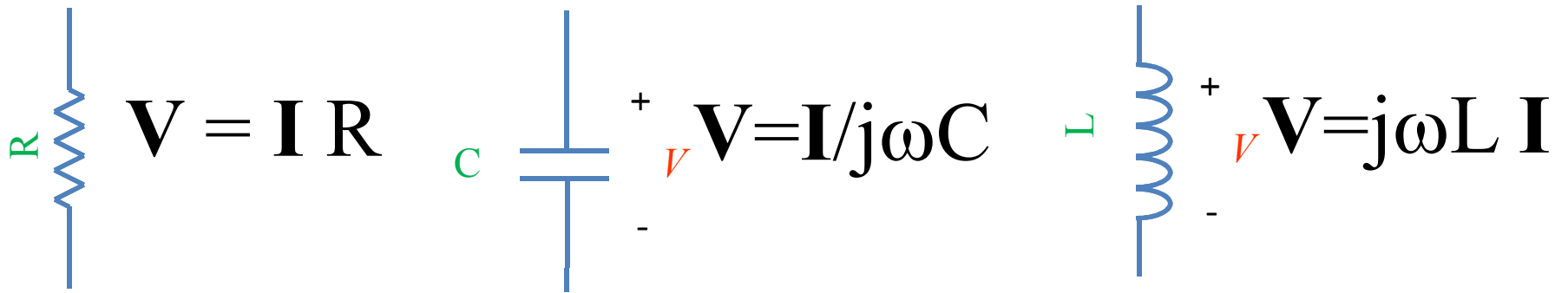

“Impedance”

$$Z = R$$

$$Z = 1 / j\omega C$$

$$Z = j\omega L$$

KCL, KVL hold for relationship
between V , I .

Series/Parallel Impedances




$$Z_{eq} = Z_1 + Z_2 + Z_3$$



$$Z_{eq}^{-1} = Z_1^{-1} + Z_2^{-1} + Z_3^{-1}$$

Conversion procedures

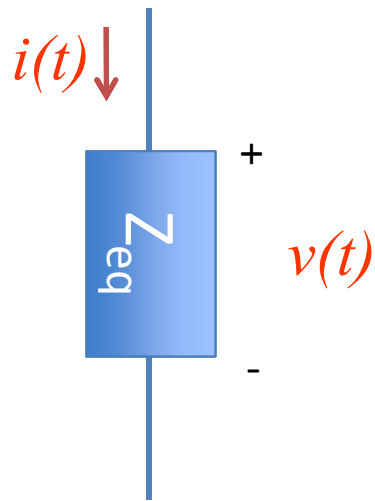

Given $i(t)$ find $v(t)$:

$$i(t) \rightarrow \mathbf{I} \rightarrow \mathbf{V} = \mathbf{I} Z_{eq} \rightarrow v(t)$$

Given $v(t)$ find $i(t)$:

$$v(t) \rightarrow \mathbf{V} \rightarrow \mathbf{I} = \mathbf{V} / Z_{eq} \rightarrow i(t)$$



For the exam, you should know how to carry out these procedures.

“Transfer Function”




$$H(\omega) = \mathbf{V}_{\text{out}} / \mathbf{V}_{\text{in}}$$

Example Transfer function

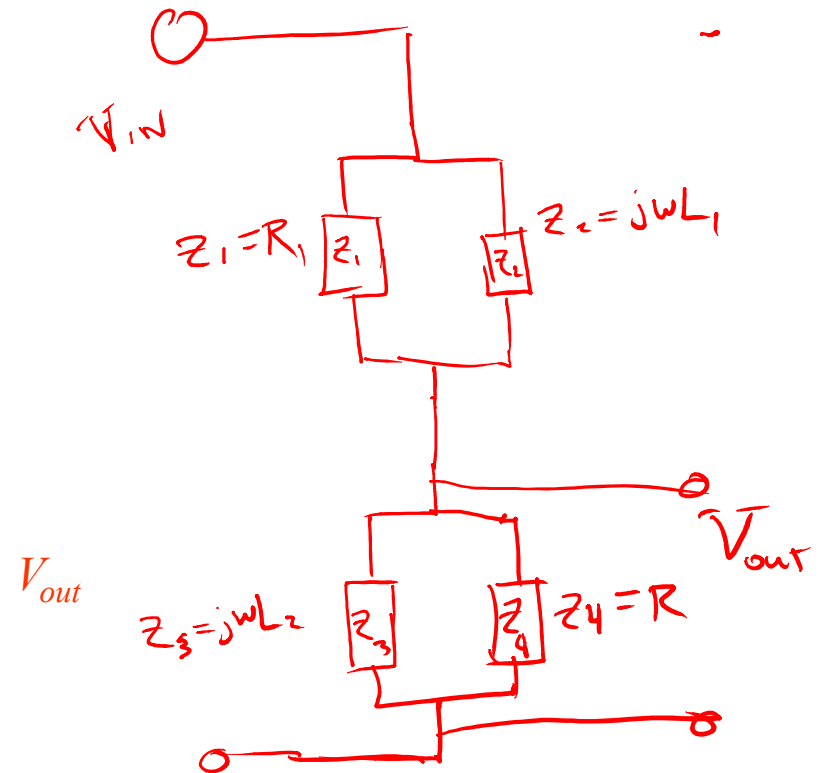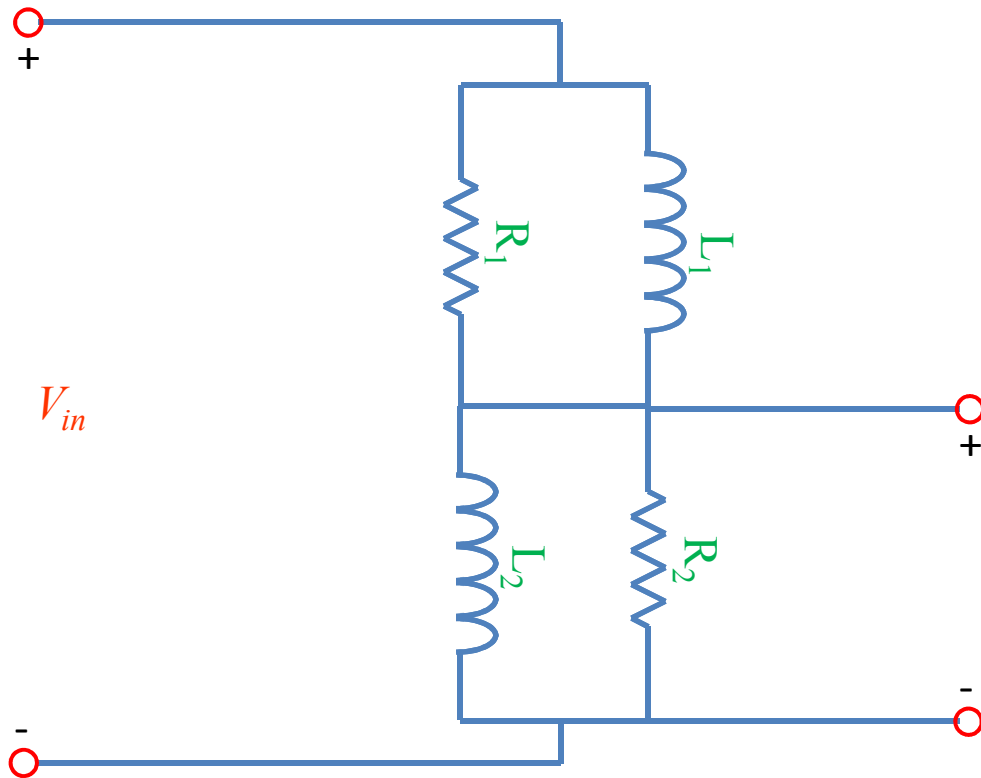


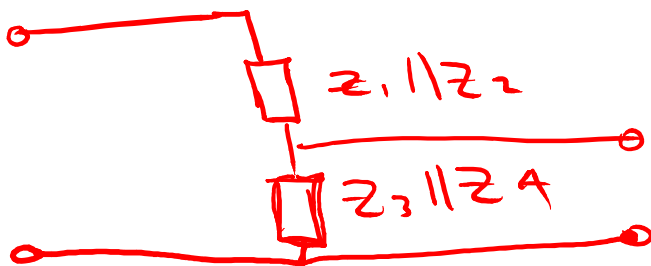Calculate $H(\omega)$ for this circuit. Sketch the magnitude of $H(\omega)$ vs. ω .



$$\frac{V_{out}}{V_{in}} = \frac{(z_3 || z_4)}{(z_3 || z_4) + (z_1 || z_2)} = H(\omega)$$


Bode example

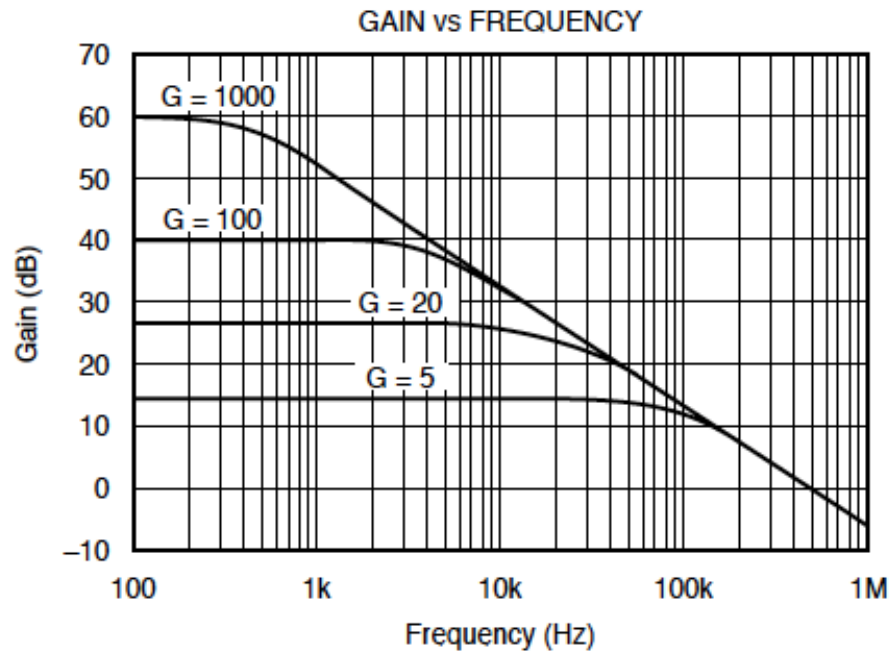

Find $V_{out}(t)$ given:

$$V_{in}(t) = 1 \text{ mV} \cos(2\pi \cdot 1\text{kHz} \cdot t)$$

Comprehensive Example

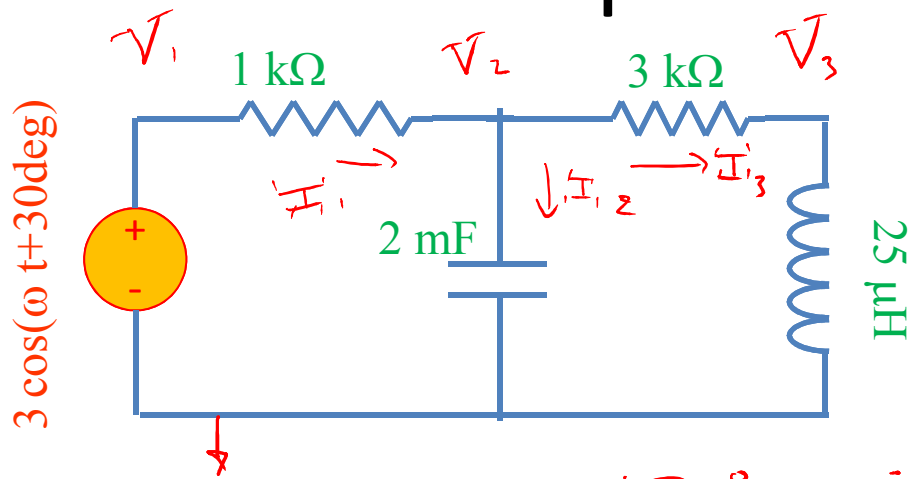

Solve all currents, voltages using Nodal. Do again using mesh.

$$i_1(t) = \text{Re}[I_1 e^{j\omega t}]$$

(N1) $V_1 = 3e^{j30^\circ} = 3e^{j\pi/6}$

(N2) $I_1 = I_2 + I_3$

$$\frac{V_1 - V_2}{1 \text{ k}\Omega} = \frac{V_2 - 0}{j\omega 2 \text{ mF}} + \frac{V_2 - V_3}{3 \text{ k}\Omega}$$

(N3) $I_3 = I_3 \Rightarrow \frac{V_2 - V_3}{3 \text{ k}\Omega} = \frac{V_3 - 0}{j\omega 25 \mu\text{H}}$


$$I_1 = \frac{V_1 - V_2}{1 \text{ k}\Omega}$$

$$I_2 = \frac{V_2}{j\omega 2 \text{ mF}}$$

$$I_3 = \frac{V_3}{j\omega 25 \mu\text{H}}$$

2 eq. 2 unknowns Find V_2, V_3 .

Comprehensive Example

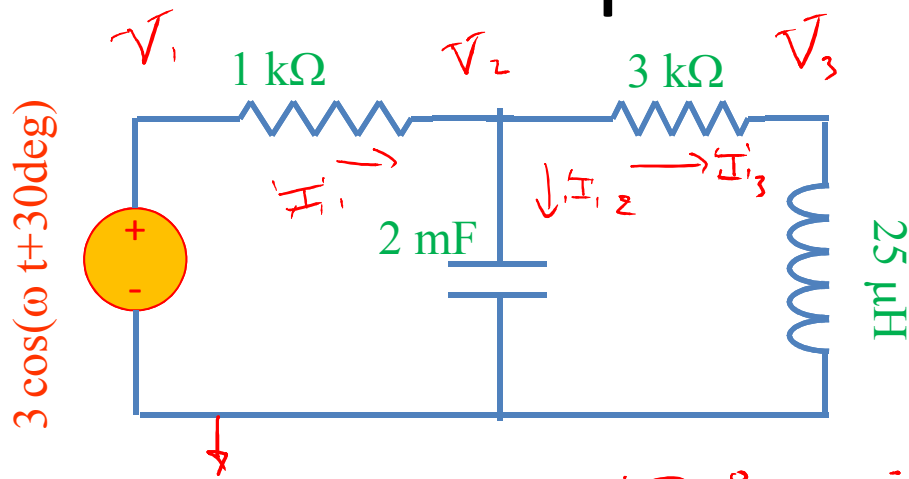

Solve all currents, voltages using Nodal. Do again using mesh.

$$i_1(t) = \text{Re}[I_1 e^{j\omega t}]$$

(N1) $\bar{V}_1 = 3e^{j30^\circ} = 3e^{j\pi/6}$

(N2) $\bar{I}_1 = \bar{I}_2 + \bar{I}_3$

$$\frac{\bar{V}_1 - \bar{V}_2}{1 \text{ k}\Omega} = \frac{\bar{V}_2 - 0}{j\omega 2 \text{ mF}} + \frac{\bar{V}_2 - \bar{V}_3}{3 \text{ k}\Omega}$$


(N3) $\bar{I}_3 = \bar{I}_3 \Rightarrow \frac{\bar{V}_2 - \bar{V}_3}{3 \text{ k}\Omega} = \frac{\bar{V}_3 - 0}{j\omega 25 \mu\text{H}}$

$$\bar{I}_1 = \frac{\bar{V}_1 - \bar{V}_2}{1 \text{ k}\Omega}$$

$$\bar{I}_2 = \frac{\bar{V}_2}{j\omega 2 \text{ mF}}$$

$$\bar{I}_3 = \frac{\bar{V}_3}{j\omega 25 \mu\text{H}}$$

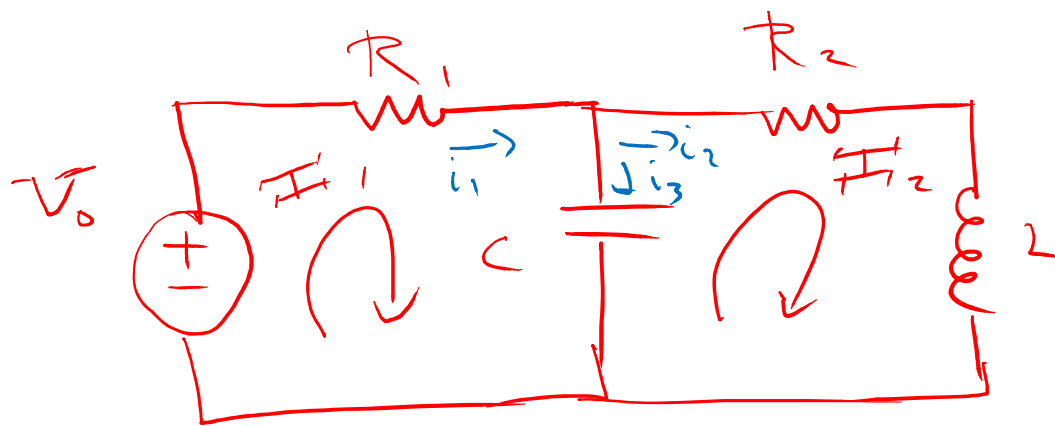2 eq. 2 unknowns Find \bar{V}_2, \bar{V}_3 .



$$i_1(t) = \text{Re}[\tilde{I}'_1 e^{j\omega t}]$$

$$i_3(t) = \text{Re}[(\tilde{I}'_1 - \tilde{I}'_2) e^{j\omega t}]$$


$$i_2(t) = \text{Re}[\tilde{I}'_2 e^{j\omega t}]$$

$$(m1) \quad V_0 + \tilde{I}'_1 R_1 + (\tilde{I}'_1 - \tilde{I}'_2) \frac{1}{j\omega C} = 0$$


$$(m2) \quad (\tilde{I}'_2 - \tilde{I}'_1) \frac{1}{j\omega C} + \tilde{I}'_2 R_2 + \tilde{I}'_2 j\omega L = 0$$

Solve $\tilde{I}'_1, \tilde{I}'_2$

Phasor Example 2

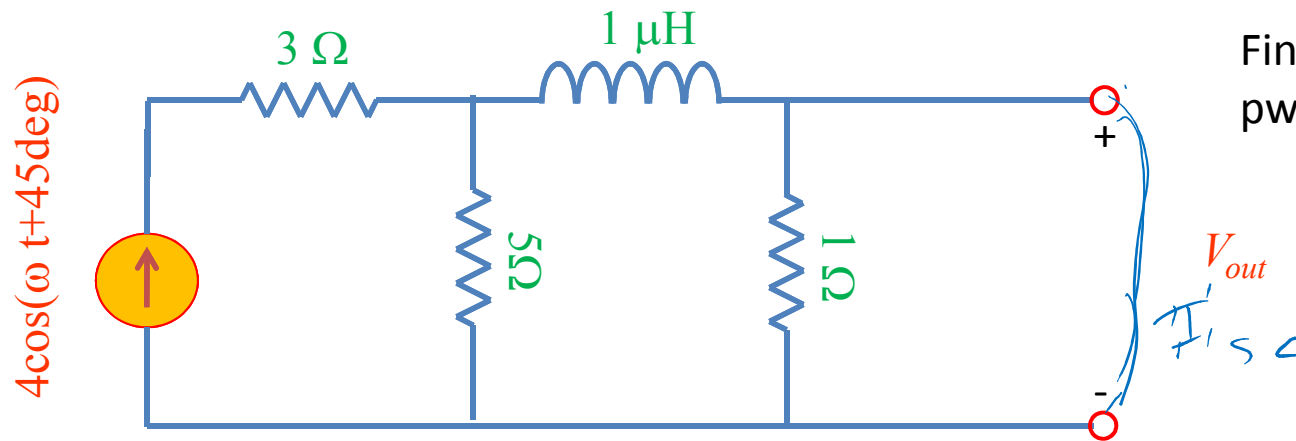

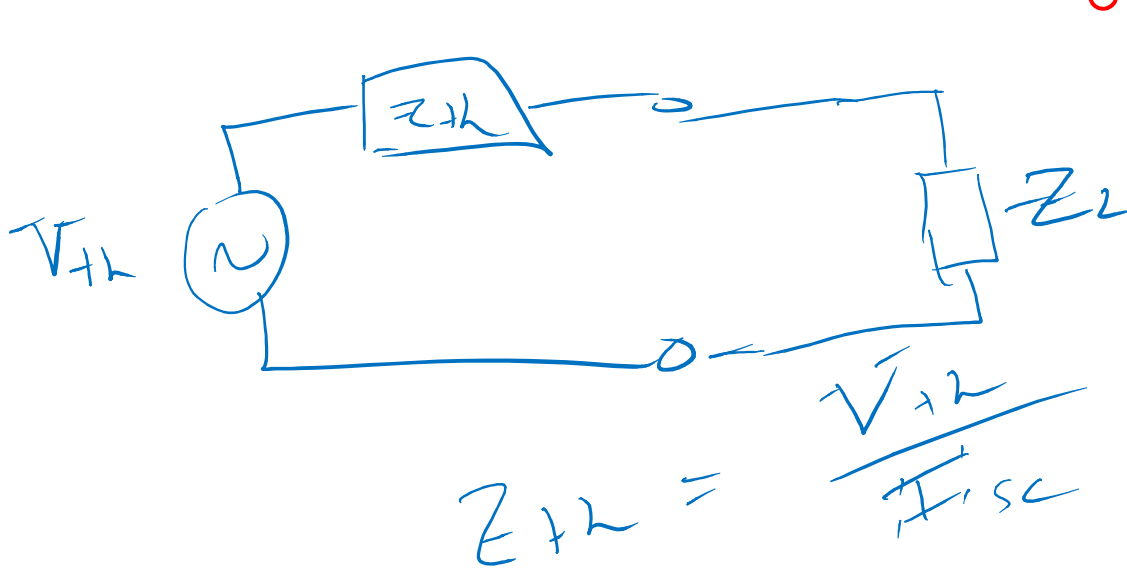
Find Thev Eq Circ + max
pwr txfr load impedance.





$$Z_L = Z_{th}^*$$

Phasor Example 1

Find $v(t)$.

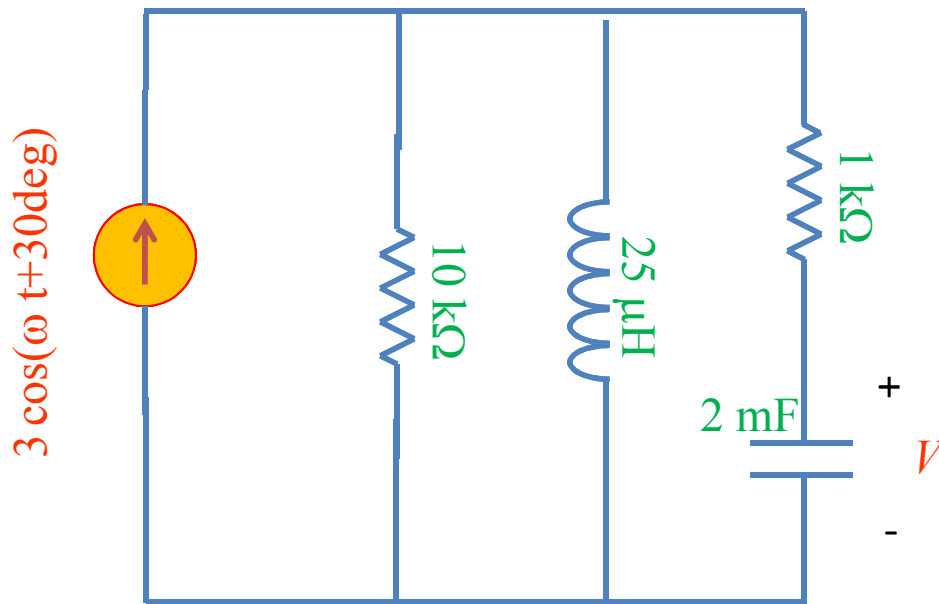

Symbol library

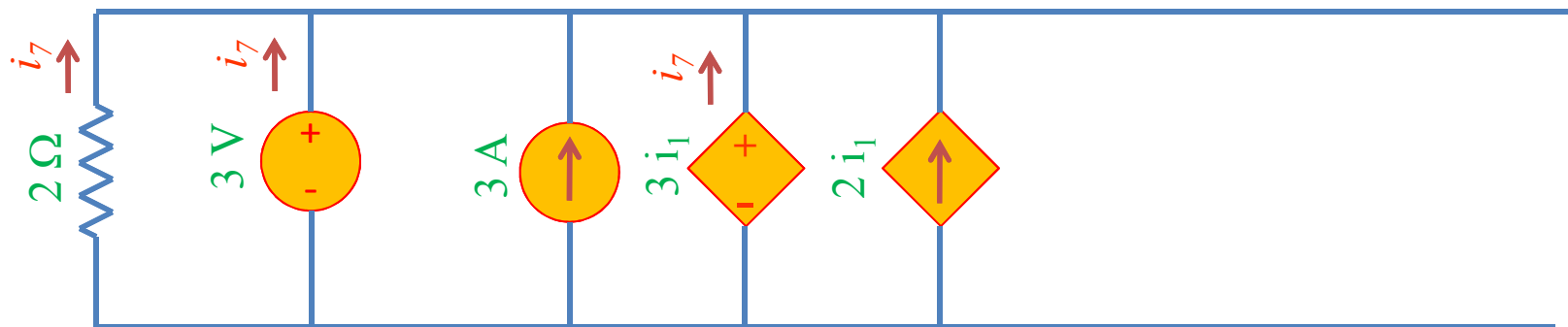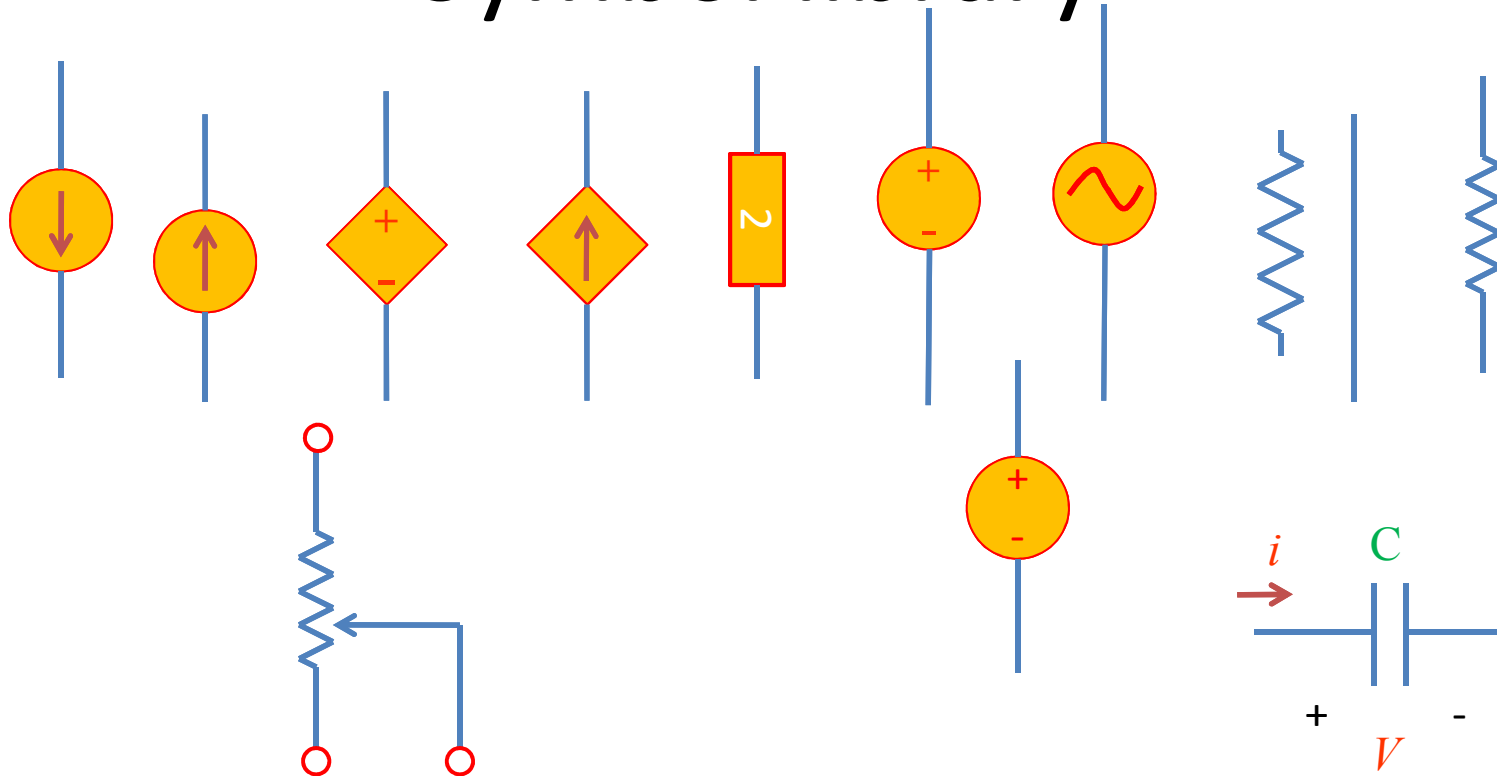

Exam cheat sheet

This will be provided with the exam.

radians :	0	$\frac{\pi}{6}$	$\frac{\pi}{4}$	$\frac{\pi}{3}$	$\frac{\pi}{2}$	π
sin	$\frac{\sqrt{0}}{2}$	$\frac{\sqrt{1}}{2}$	$\frac{\sqrt{2}}{2}$	$\frac{\sqrt{3}}{2}$	$\frac{\sqrt{4}}{2}$	0
cos	$\frac{\sqrt{4}}{2}$	$\frac{\sqrt{3}}{2}$	$\frac{\sqrt{2}}{2}$	$\frac{\sqrt{1}}{2}$	$\frac{\sqrt{0}}{2}$	-1
tan	$\frac{\sqrt{0}}{\sqrt{4}}$	$\frac{\sqrt{1}}{\sqrt{3}}$	$\frac{\sqrt{2}}{\sqrt{2}}$	$\frac{\sqrt{3}}{\sqrt{1}}$	DNE	0

where $\sqrt{\cdot}$ always denotes the positive square root, and DNE means does not exist.