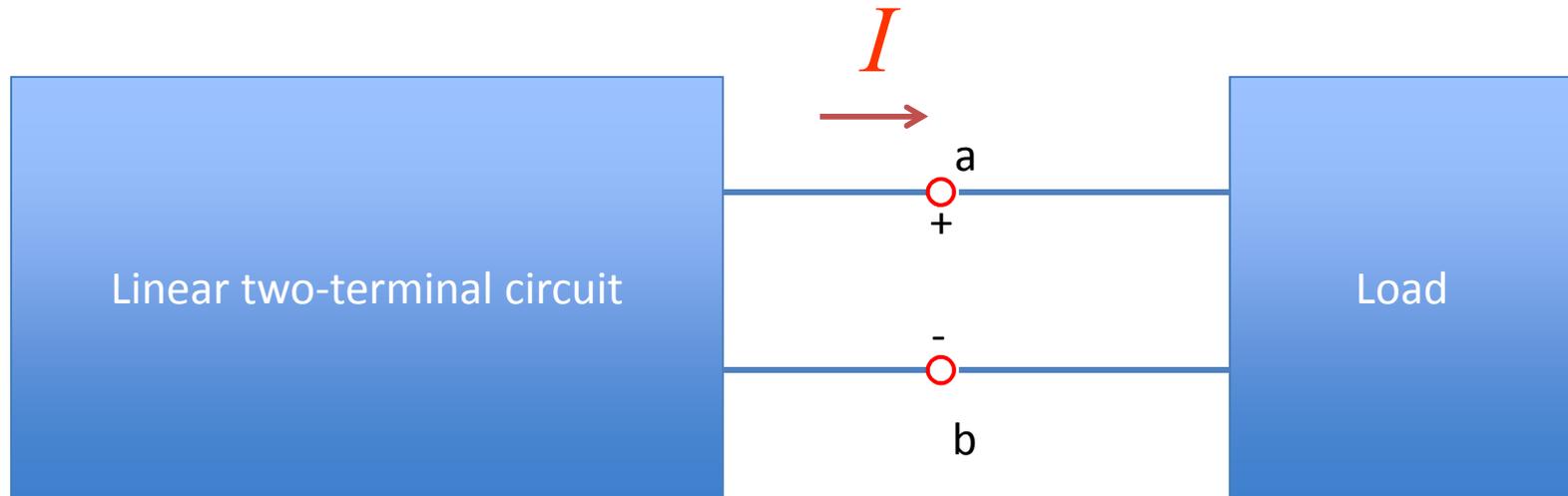


Announcements:


1. Announcements

EECS 70A: Network Analysis

Thevenin's Theorem



Equivalent to:

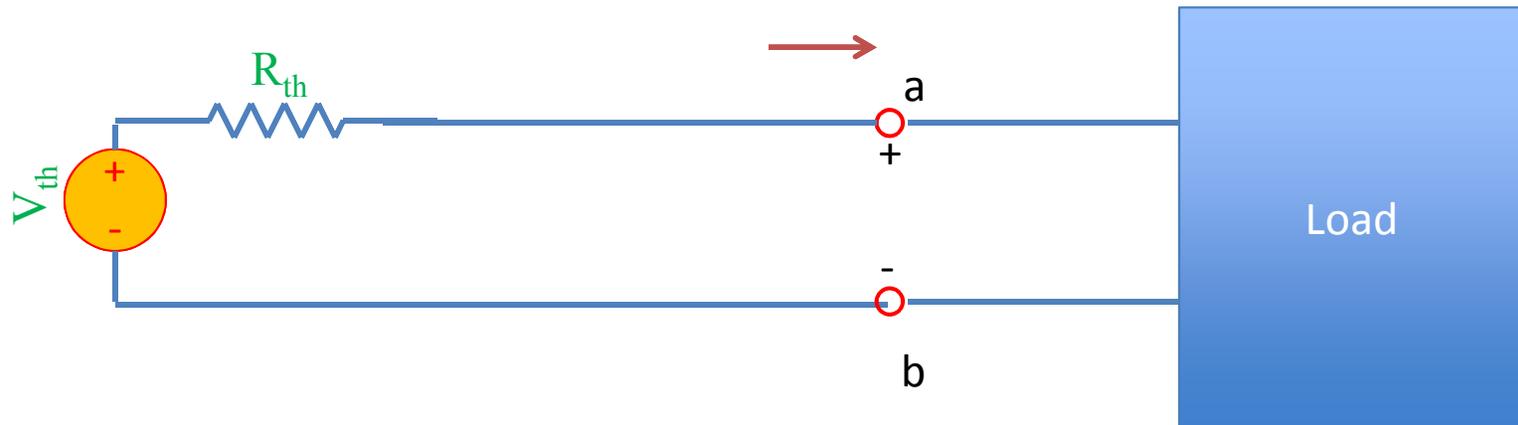


Finding V_{th} , R_{th}

Goal: Find V_{th} , R_{th}


Given: Circuit

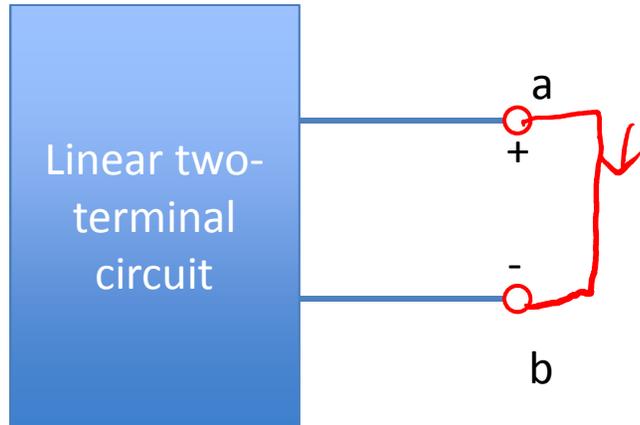1) Find V_{th}

Calculate V_{ab} (when no external circuit connected)



Equivalent to:

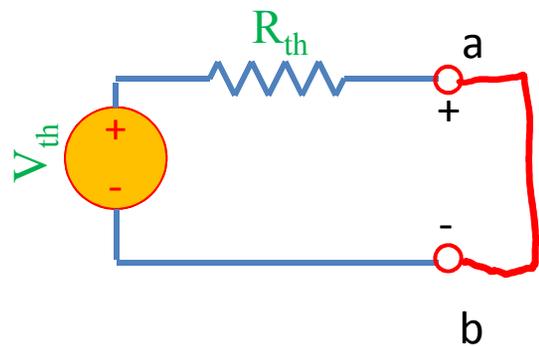


$$I = \frac{V_{th}}{R_{th}}$$


2) Find R_{th}

$$R_{th} = \frac{V_{th}}{I_{short\ circuit}}$$

Source/load

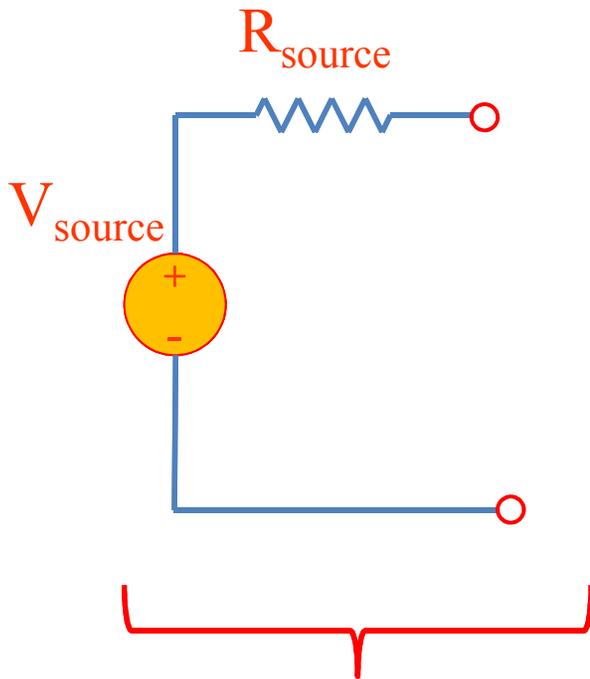

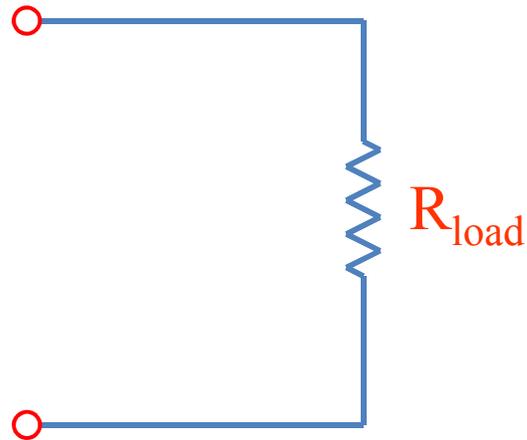Thevenin Thm:
Any circuit can be
represented by this
equivalent circuit.



$$V_{load} = \frac{R_{load}}{R_{load} + R_{source}} V_{source}$$

Derivation:

Case 1:


$$R_{load} \gg R_{source}$$

Case 2:


$$R_{source} \gg R_{load}$$

We say R_{load} “loads down” the source.

Source/load

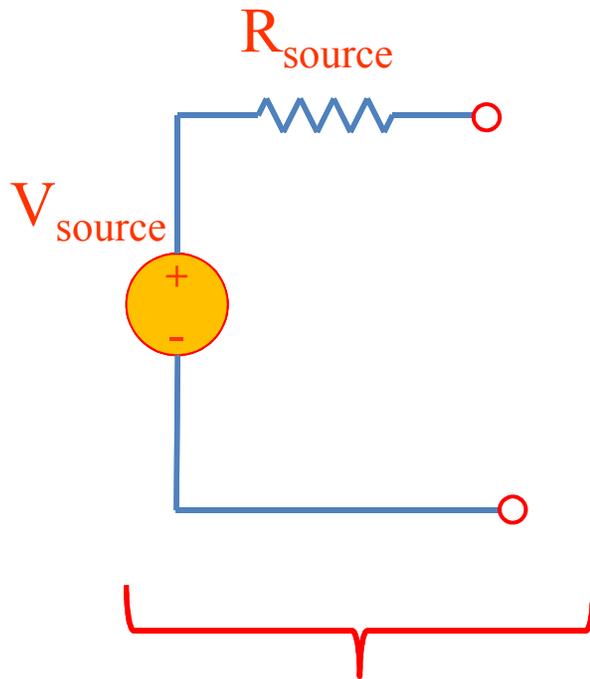

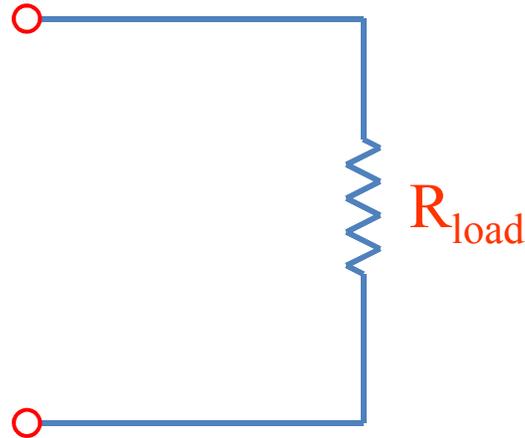Thevenin Thm:
Any circuit can be
represented by this
equivalent circuit.



$$V_{load} = \frac{R_{load}}{R_{load} + R_{source}} V_{source}$$

Derivation:

Case 1:

$$R_{load} \gg R_{source}$$

Case 2:


$$R_{source} \gg R_{load}$$

We say R_{load} “loads down” the source.

IMPORTANT!

Example

Find Thevenin equivalent circuit:


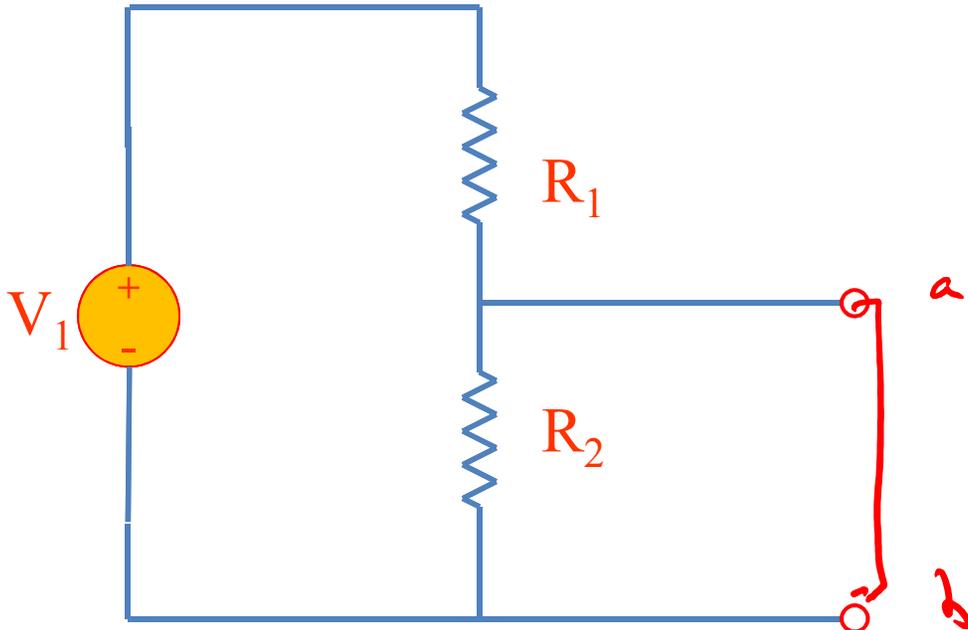


$$1) V_{th} = V_{ab} \text{ (open)}$$
$$= V_1 \frac{R_2}{R_1 + R_2}$$

$$2) R_{th} = \frac{V_{th}}{I_{\text{short circuit}}}$$


$$= \frac{V_1 \frac{R_2}{R_1 + R_2}}{I_{\text{short circuit}}}$$

$I_{\text{short circuit}}$

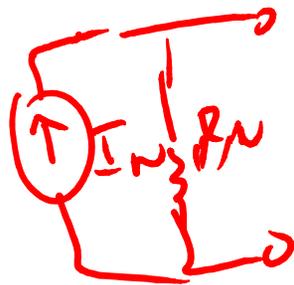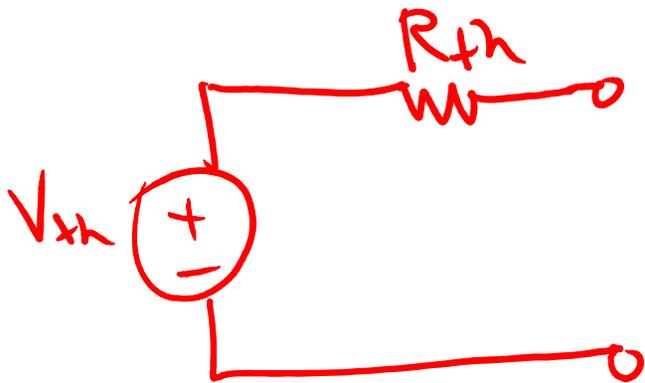

$$= \frac{\frac{V_1 R_2}{R_1 + R_2}}{\frac{V_1}{R_1}} = \frac{R_1 R_2}{R_1 + R_2} = R_1 \parallel R_2$$


EX PART 2 FIND NORTON EQ CIR.

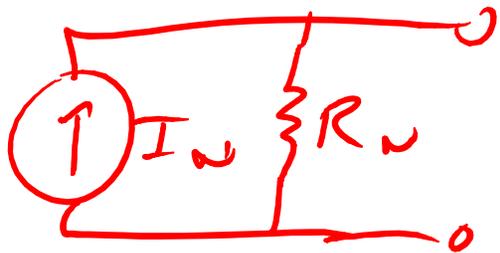


$$R_n = R_1 \parallel R_2 \quad (= R_{th})$$

$$I_n = \frac{V_{th}}{R_n} = \frac{V_1 \frac{R_2}{R_1 + R_2}}{\frac{R_1 R_2}{R_1 + R_2}} = \frac{V_1}{R_1}$$

Norton's Theorem

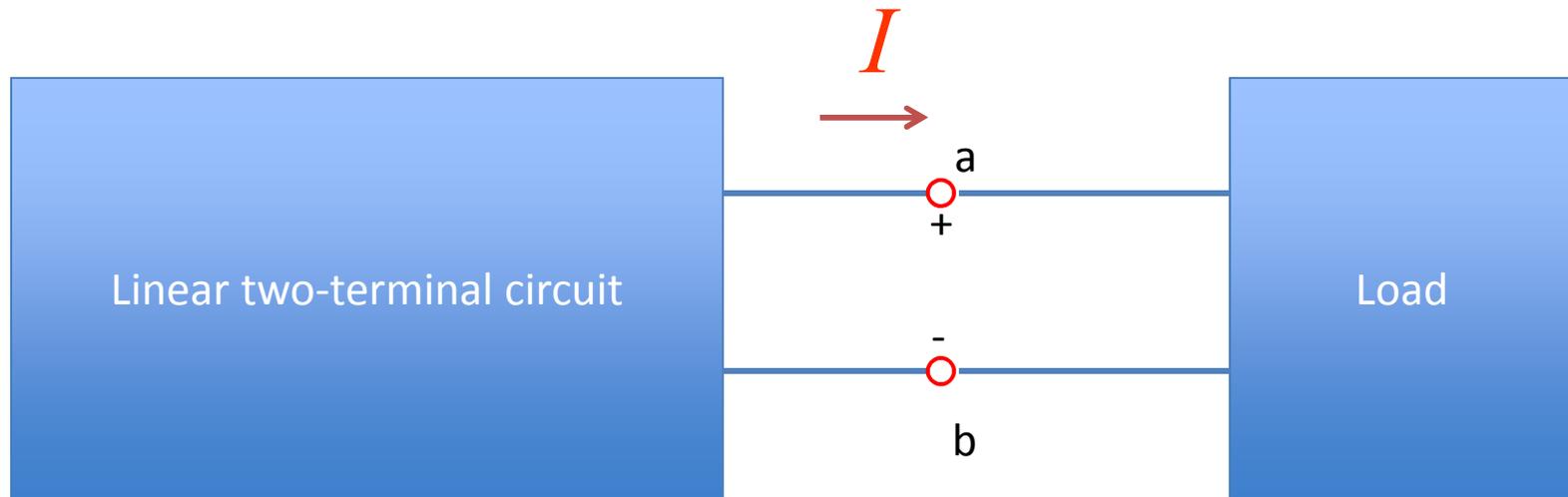


Equivalent to:

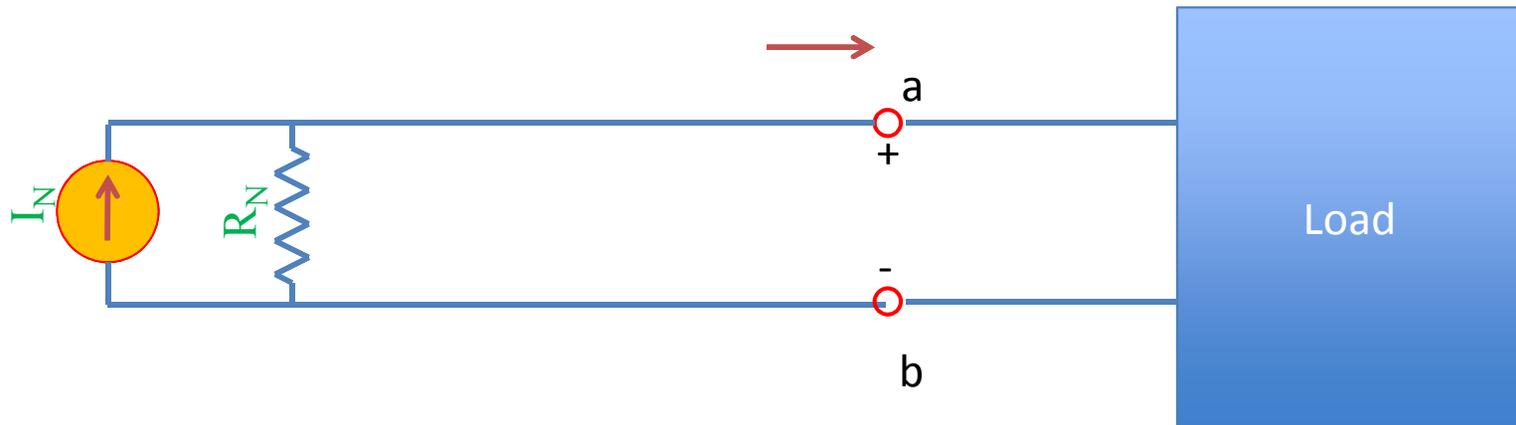

Finding V_{th} , R_{th}

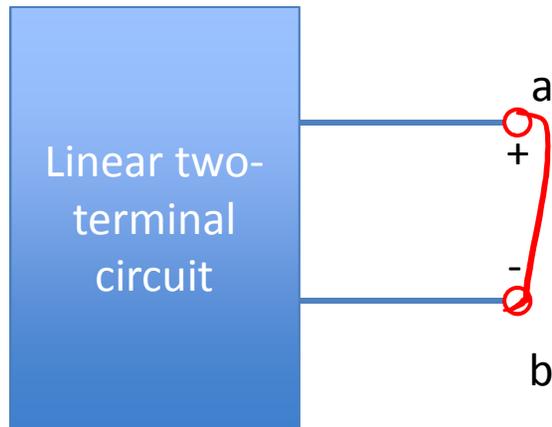Once you find R_{th} , V_{th}
easy to find I_N , V_N
 Open (i.e. nothing connected
 to a, b)





$$V_{a-b} = V_{th} = I_N R_N \quad (*)$$

Equivalent to:

(Equivalent to:)

consider a short to b

$$I_{short\ circuit} = \quad (**)$$

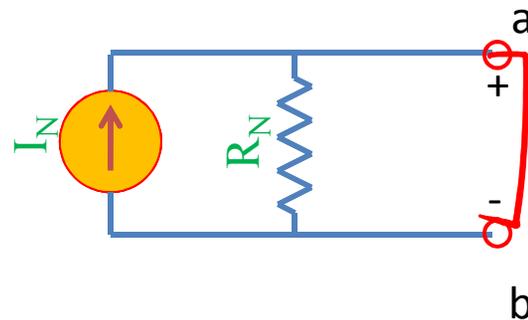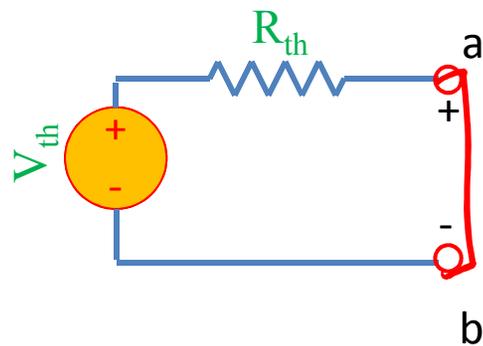


$$\frac{V_{th}}{R_{th}} = I_N$$

$$R_N = R_{th}$$

$$I_N = V_{th} / R_{th}$$

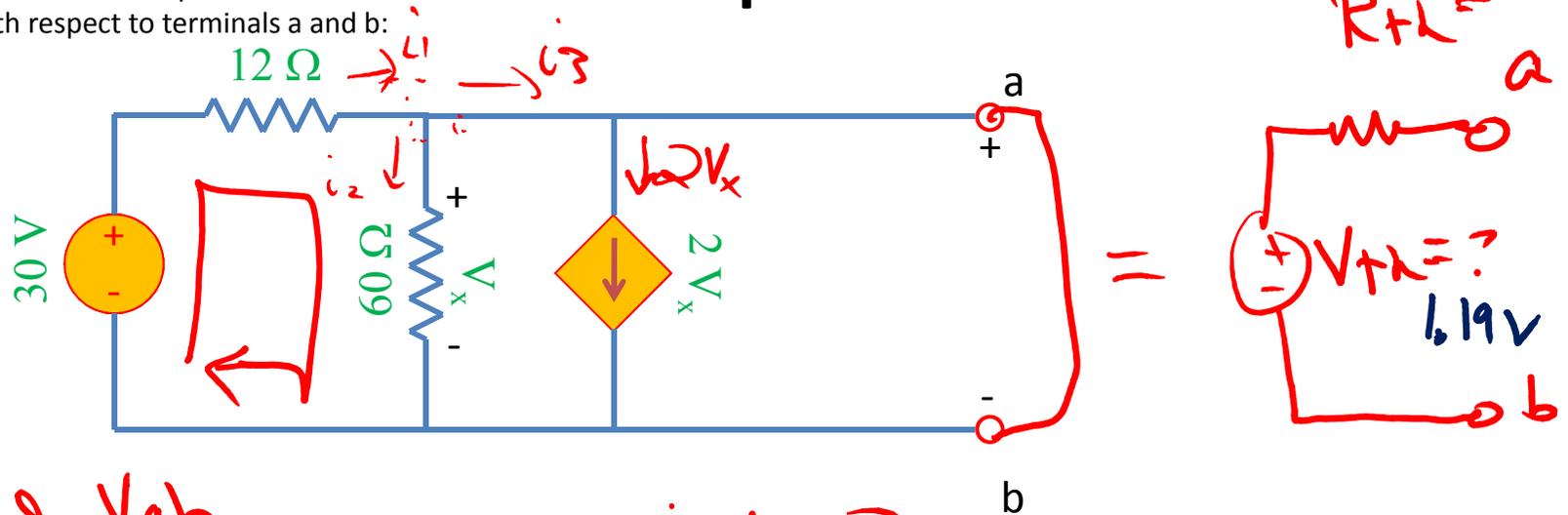Example

Find the Thevenin & Norton equivalent circuit of the circuit below with respect to terminals a and b:



1) Find V_{ab}

$$V_{ab} = V_x$$

$$\text{KCL } i_1 = i_2 + i_3 \quad (*)$$

$$\text{KVL } -30 + i_1 \cdot 12 + V_x = 0 \Rightarrow i_1 = \frac{30 - V_x}{12}$$

$$i_2 = \frac{V_x}{60}$$

$$i_3 = 2V_x$$

$$R_{th} = \frac{V_{th}}{I_{sc}} = \frac{1.19V}{2.5A} = 0.476 \Omega$$


$$\frac{30 - V_x}{12} = \frac{V_x}{60} + 2V_x$$

$$V_x = 1.19V = V_{th} = 0.476 \Omega$$

2) Find I_{short} if circuit = $\frac{30V}{12\Omega} = 2.5A$

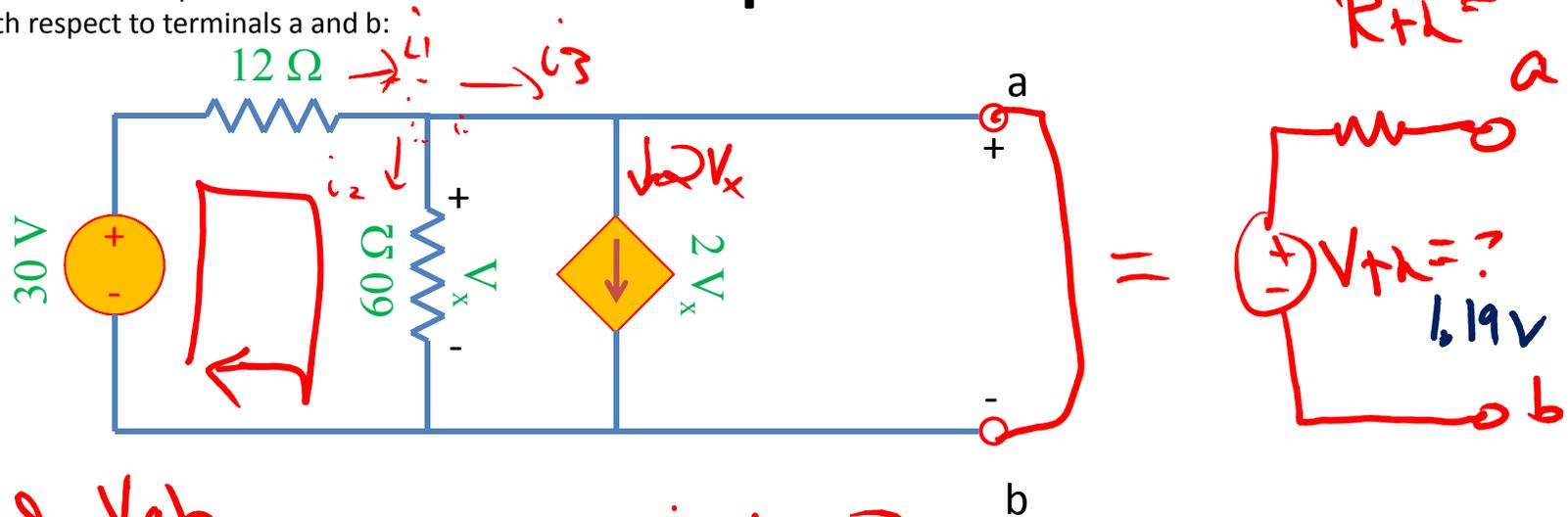Example

Find the Thevenin & Norton equivalent circuit of the circuit below with respect to terminals a and b:



1) Find V_{ab}

$$V_{ab} = V_x$$

KCL $i_1 = i_2 + i_3$ (*)

KVL $-30 + i_1 \cdot 12 + V_x = 0 \Rightarrow i_1 = \frac{30 - V_x}{12}$

$$i_2 = \frac{V_x}{60}$$



$$i_3 = 2V_x$$

$$R_{th} = \frac{V_{th}}{I_{sc}} = \frac{1.19V}{2.5A} = 0.476 \Omega$$

$$\frac{30 - V_x}{12} = \frac{V_x}{60} + 2V_x$$

$$V_x = 1.19V = V_{th} = 0.476 \Omega$$

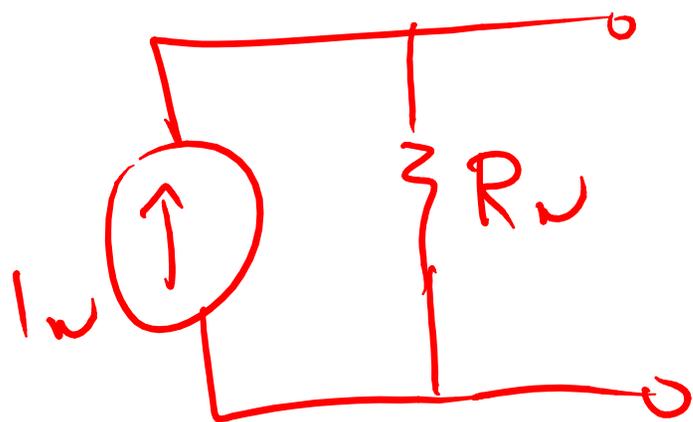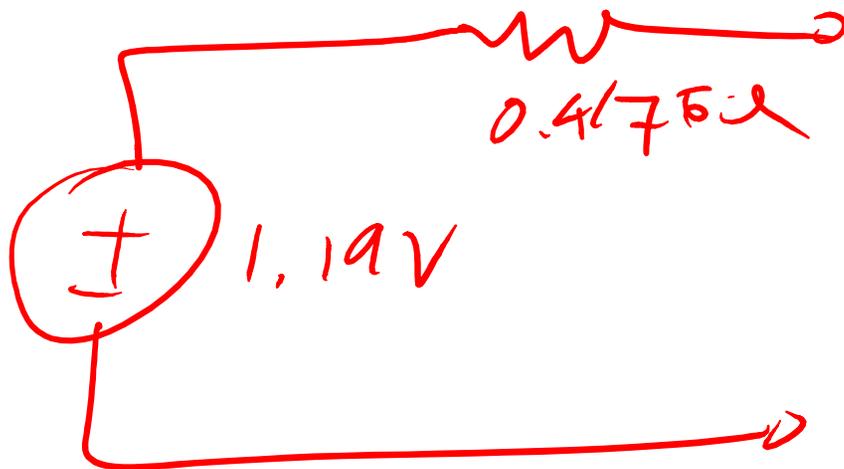
2) Find I_{short} of circuit $= \frac{30V}{12\Omega} = 2.5A$




$$R_N = 0.476 \Omega$$

$$I_N = \frac{V_{th}}{R_N}$$

$$= \frac{1.19V}{0.476 \Omega} = 2.5A$$

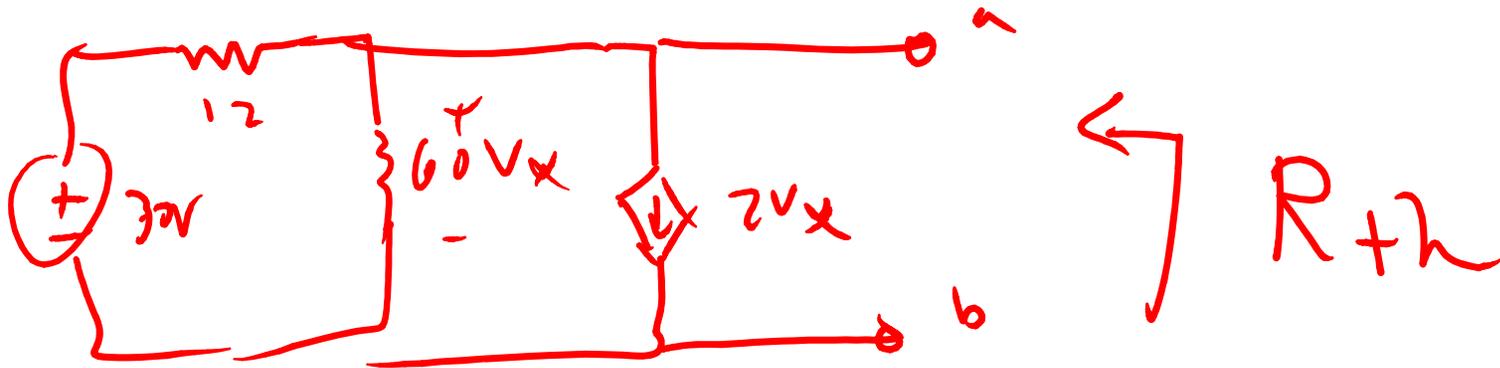

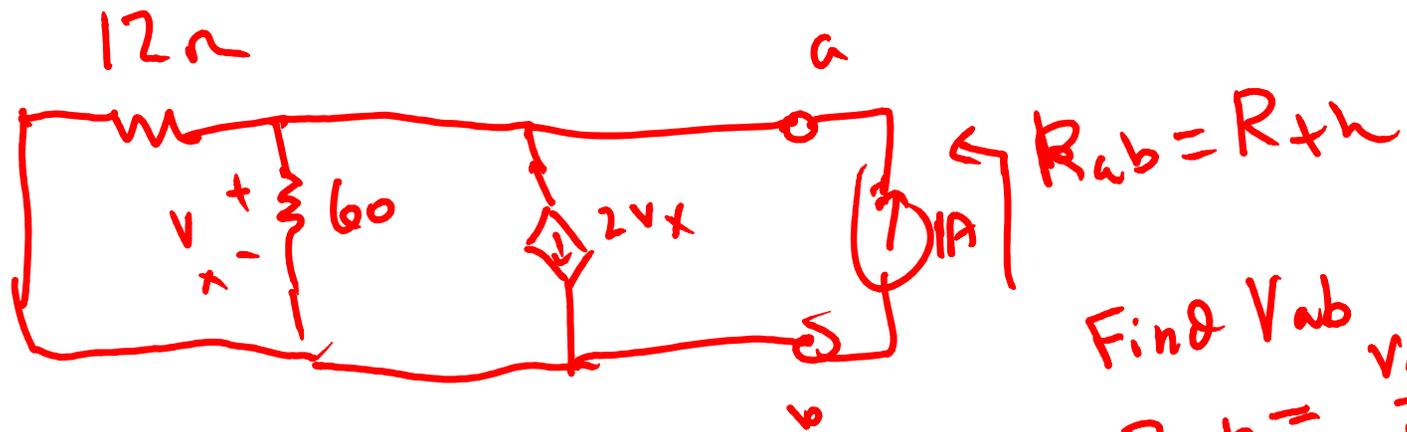Find R_{ab} when all indep. source, turned off
 Volt source \rightarrow short,
 Curr source \rightarrow open





Find V_{ab}
 $R_{ab} = \frac{V_{ab}}{1A}$

2


“Baby” monster problem

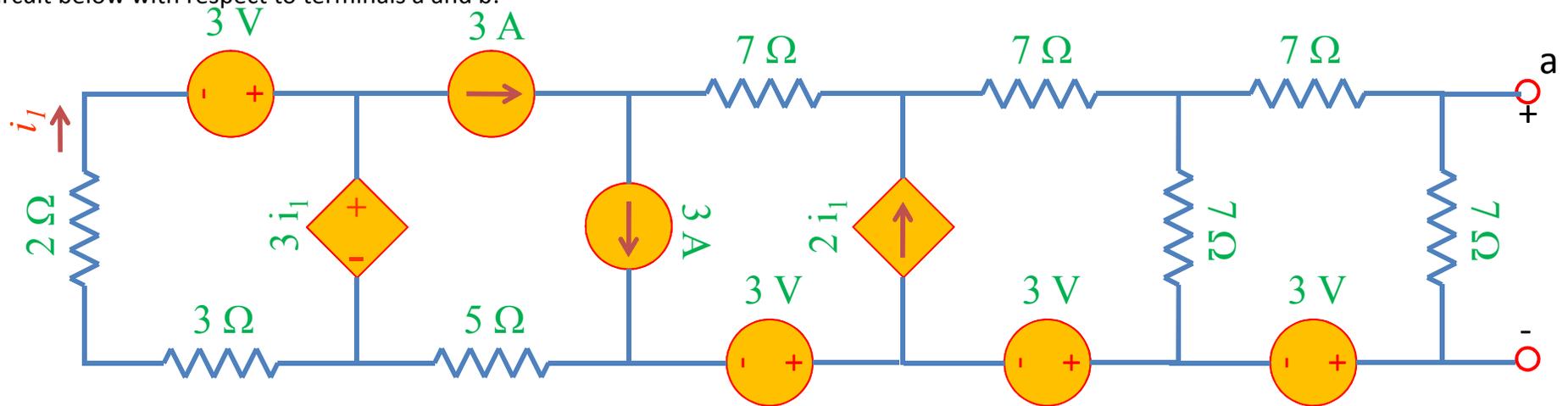Find the Thevenin & Norton equivalent circuit of the circuit below with respect to terminals a and b:




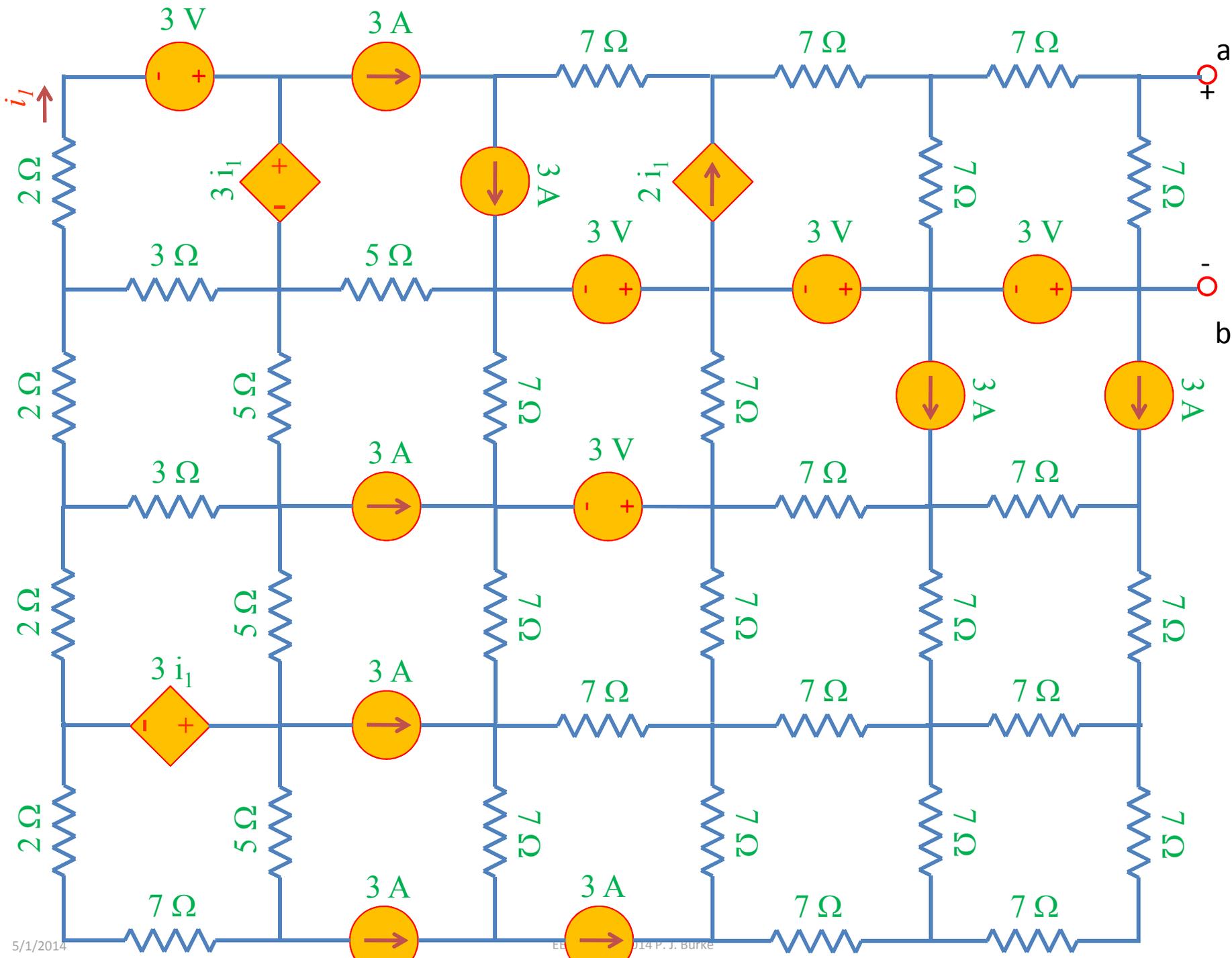

Power

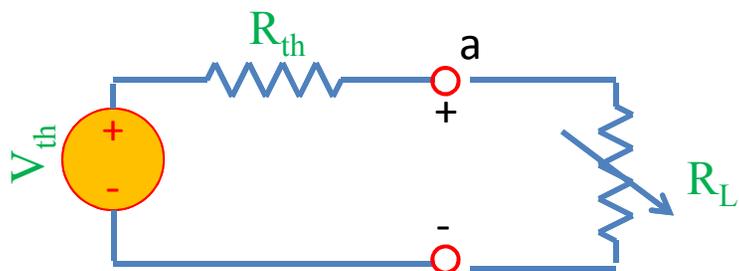

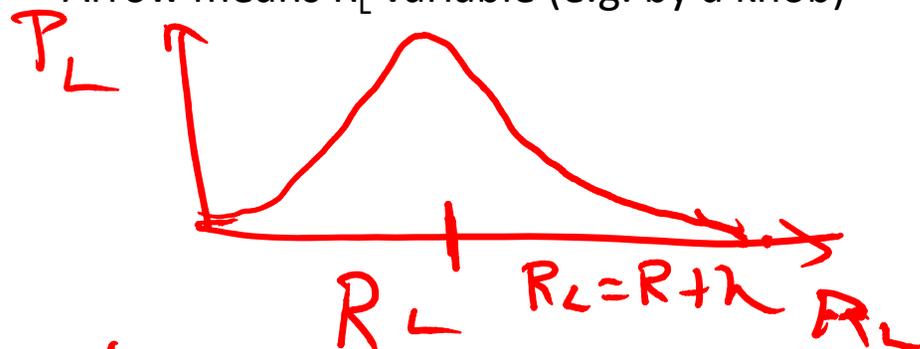
Arrow means R_L variable (e.g. by a knob)



Power delivered to load = ?

$$\text{Voltage across } R_L = V_{th} \frac{R_L}{R_L + R_{th}}$$
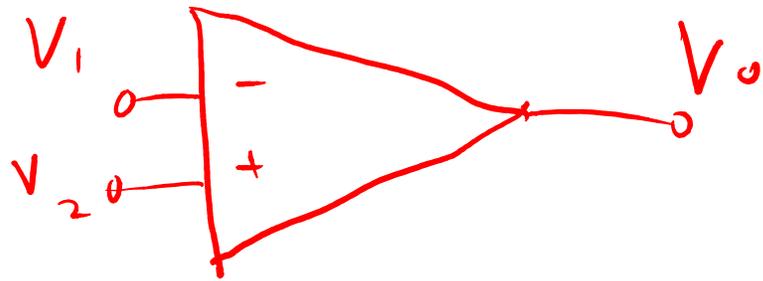
$$\begin{aligned} \text{Power delivered to load} &= P_L = V_L \times I_L \\ &= V_{th} \frac{R_L}{R_L + R_{th}} \frac{V_{th}}{R_L + R_{th}} = \frac{V_{th}^2 R_L}{(R_{th} + R_L)^2} \end{aligned}$$



OPAMP

IDEAL

REAL

$$R_i = \infty$$


$$10^6 - 10^{12} \Omega$$

$$R_o = 0$$

$$1 - 100 \Omega$$


$$A = \infty$$

$$10^4 - 10^6$$

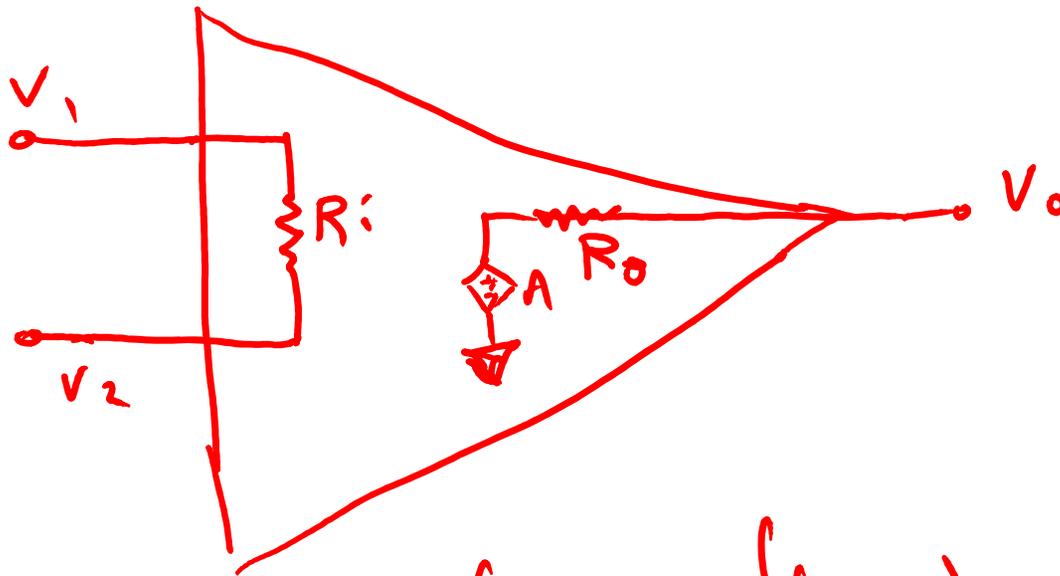

$$V_0 = A (V_2 - V_1)$$

Voltage Follower

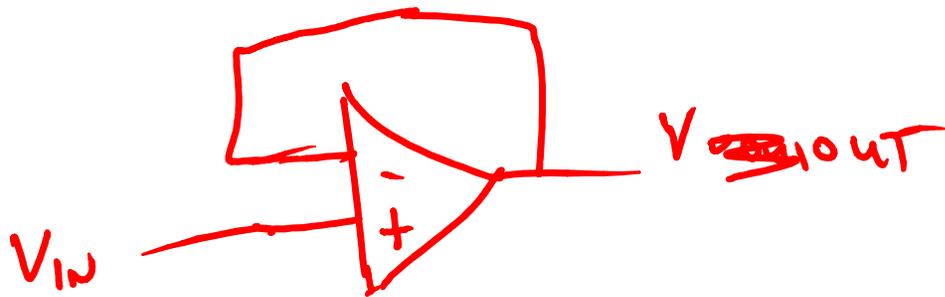

IDEAL

$$V_{OUT} = V_{IN}$$

