

Announcements:  
1. Announcements


# EECS 70A: Network Analysis

## Lecture 6

# Nodal Analysis(Review)

Based on KCL, Use node voltages as circuits variables.

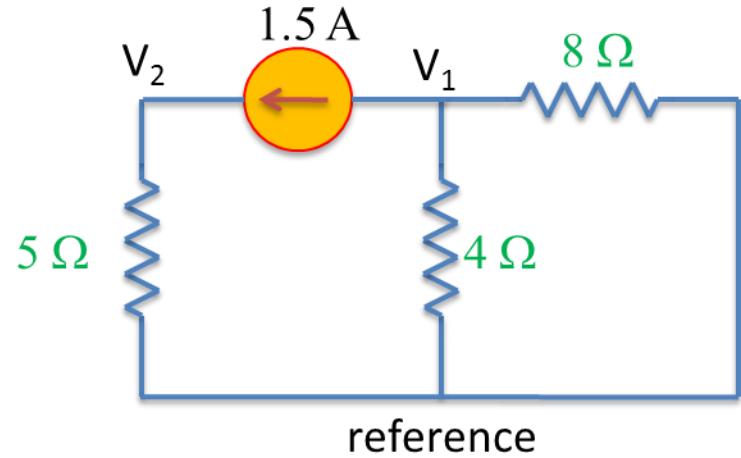1. Define a reference node.
2. Label remaining nodes. ( $n-1$  nodes)
3. Apply KCL + ohm to all nodes and supernodes
  1. Express all I's in terms of v's
4. Apply KVL to loops with voltage source
5. Solve the  $n-1$  simultaneous equations, to find V's
6. Use Ohm's law to find the currents.




$$V_1 = \frac{\begin{vmatrix} 3 & \frac{1}{5} \\ -\frac{3}{2} & 0 \\ 0 & \frac{1}{5} \\ \frac{3}{8} & 0 \end{vmatrix}}{\begin{vmatrix} 2 & 0 \\ 0 & 0 \end{vmatrix}} = -4 \text{ V}$$

$$\begin{vmatrix} a & b \\ c & d \end{vmatrix} = ad - bc$$


$$V_1 = \frac{\frac{3}{2} \times 0 - \left(-\frac{3}{2}\right) \left(\frac{1}{5}\right)}{0 \times 0 - \left(\frac{1}{5}\right) \left(\frac{3}{8}\right)} = -4 \checkmark$$
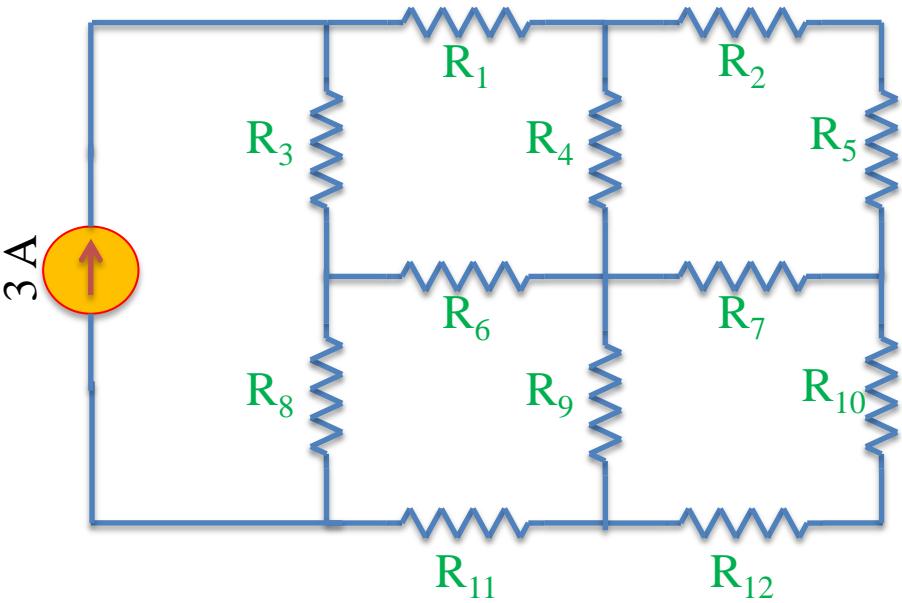
# Example Nodal Problem (detailed solution)



# Same circuit: Nodal analysis

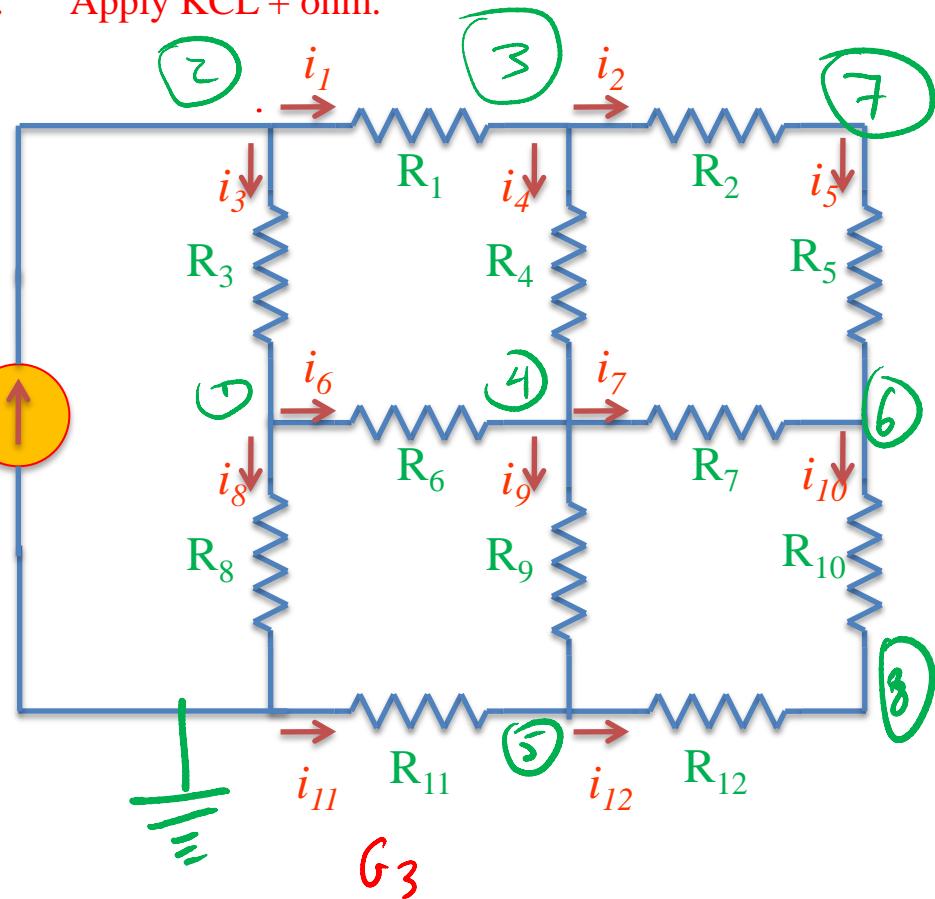1. Define a reference node.
2. Label remaining nodes.
3. Apply KCL + ohm.



$$\textcircled{1} \quad i_N = 0 \text{ at } v_3 = i_6 + i_8$$

$$\frac{v_2 - v_1}{R_3} = \frac{v_1 - v_4}{R_6} + \frac{v_1 - 0}{R_8}$$

$$G_3 = \frac{1}{R_3}, \quad G_6 = \frac{1}{R_6}, \text{ etc}$$

$$(G_3 + G_6 + G_8)v_1 + (0)v_2 + (0)v_3 + (G_6)v_4 + (0)v_5 + (0)v_6 \\ 3.68 + (0)v_7 + (0)v_8 = (0)$$

$$-(G_3 + G_6 + G_9)V_1 + G_3V_2 + 0V_3 + G_6V_4 + 0V_5 + 0V_6 + 0V_7 + 0V_8 = 0$$

$$-G_3 V_1 + (G_1 + G_3)V_2 + (G_1) V_3 + 0V_4 + 0V_5 + 0V_6 + 0V_7 + 0V_8 = 0$$

$$0V_1 + G_1V_2 + (-G_1 - G_2)V_3 + (G_2 + G_4)V_4 + 0V_5 + 0V_6 + 0V_7 + 0V_8 = 0$$

$$G_1V_1 + 0V_2 + G_4V_3 + -(G_6 + G_4 + G_9 + G_7)V_4 + G_4V_5 + 0V_6 + 0V_7 + 0V_8 = 0$$

$$0V_1 + 0V_2 + 0V_3 + (-G_9)V_4 + (G_9 + G_{12})V_5 + 0V_6 + 0V_7 + (G_{12})V_8 = 0$$

$$0V_1 + 0V_2 + 0V_3 + G_7V_4 + 0V_5 + \left( \frac{(-G_5 + G_7)}{-G_{10}} \right) V_6 + G_5V_7 + G_{10}V_8 = 0$$

$$0V_1 + 0V_2 + G_2V_3 + 0V_4 + 0V_5 + G_5V_6 + (G_2 - G_5)V_7 + 0V_8 = 0$$

$$0V_1 + 0V_2 + 0V_3 + 0V_4 + G_{12}V_5 + G_{10}V_6 + (G_{12} - G_{10})V_8 = 0$$

$$V_1 = \frac{\dots \dots \dots \dots \dots \dots}{\dots \dots \dots \dots \dots \dots}$$

LHS 10 coeffs.

$$-(G_3 + G_6 + G_9)V_1 + G_3V_2 + 0V_3 + G_6V_4 + 0V_5 + 0V_6 + 0V_7 + 0V_8 = 0$$

$$-G_3 V_1 + (G_1 + G_3)V_2 + (G_1)N_3 + 0V_4 + 0V_5 + 0V_6 + 0V_7 + 0V_8 = 0$$

$$0V_1 + G_1V_2 + (-G_1 - G_2)V_3 + (G_2 + G_4)V_4 + 0V_5 + 0V_6 + 0V_7 + 0V_8 = 0$$

$$G_1V_1 + 0V_2 + G_4V_3 + -(G_6 + G_4 + G_9 + G_7)V_4 + G_4V_5 + 0V_6 + 0V_7 + 0V_8 = 0$$

$$0V_1 + 0V_2 + 0V_3 + (-G_9)V_4 + (G_9 + G_{12})V_5 + 0V_6 + 0V_7 + (G_{12})V_8 = 0$$

$$0V_1 + 0V_2 + 0V_3 + G_7V_4 + 0V_5 + \left( \frac{(-G_5 + G_7)}{-G_{10}} \right) V_6 + G_5V_7 + G_{10}V_8 = 0$$

$$0V_1 + 0V_2 + G_2V_3 + 0V_4 + 0V_5 + G_5V_6 + (G_2 - G_5)V_7 + 0V_8 = 0$$


$$0V_1 + 0V_2 + 0V_3 + 0V_4 + G_{12}V_5 + G_{10}V_6 + (G_{12} - G_{10})V_8 = 0$$

$$V_1 = \frac{\dots \dots \dots \dots \dots \dots \dots}{\dots \dots \dots \dots \dots \dots \dots}$$

N

D


LHS 10eqns.

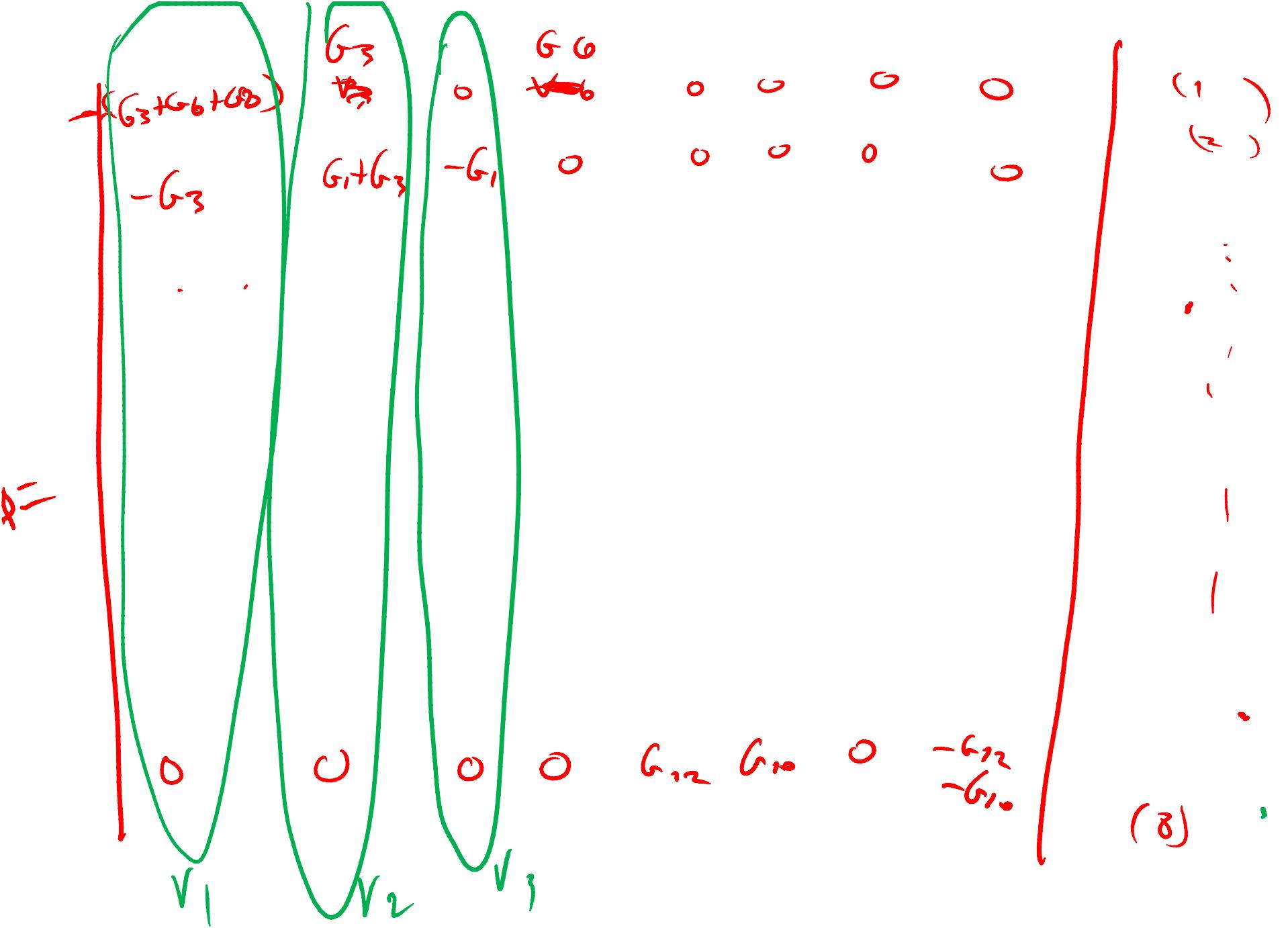

$$\begin{vmatrix} 0 & 1 & 2 \\ +0 & -0 \\ 6 & 3 & 4 \end{vmatrix} = 1 \begin{vmatrix} 1^2 \\ 34 \\ +0 \end{vmatrix} \begin{vmatrix} -\cancel{0} \end{vmatrix} \\ = -(4-6) = +2$$

$$\begin{vmatrix} abc \\ def \\ ghi \end{vmatrix} = a \begin{vmatrix} e f \\ e h \end{vmatrix} - b \begin{vmatrix} d f \\ g h \end{vmatrix} + c \begin{vmatrix} d e \\ g e \end{vmatrix} \\ \begin{vmatrix} abc \\ def \\ ger \\ a \end{vmatrix} = d \begin{vmatrix} b c \\ c h \end{vmatrix} + e \begin{vmatrix} a c \\ g h \end{vmatrix} - f \begin{vmatrix} a b \\ \cancel{f g} \end{vmatrix}$$

# Nodal Analysis-Example

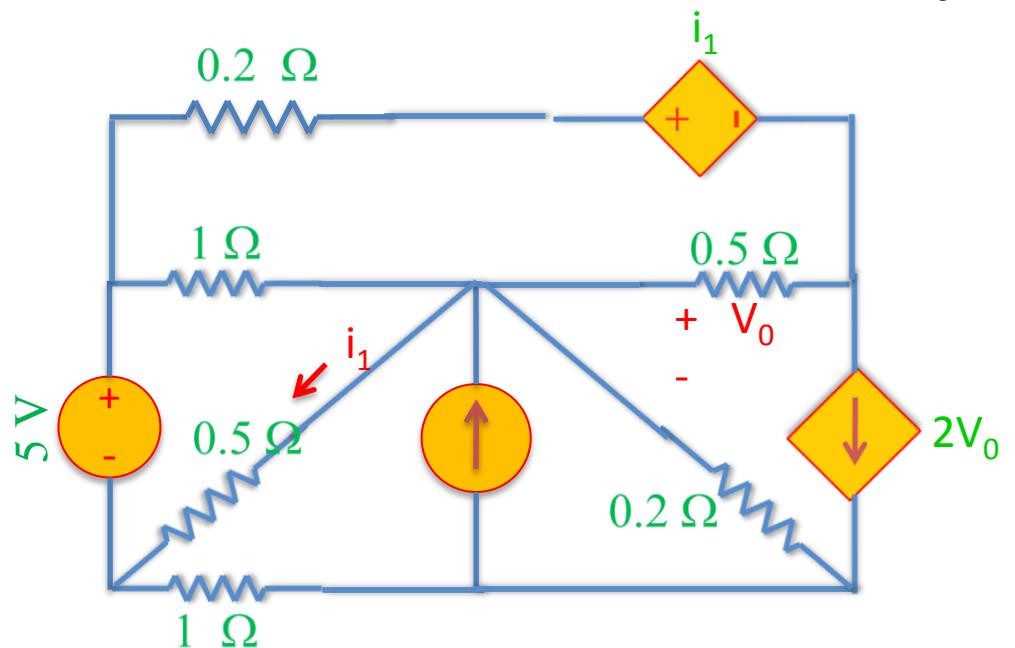


# Mesh Analysis(Review)

Based on KVL, use mesh currents as circuits variables.

1. Assign mesh currents  $i_1, i_2, \dots, i_n$ 
  - A. Create supermesh if current source
2. Apply KVL+ Ohm's law to each mesh *KCL w/ curr. source*
3. Solve the equations for mesh currents  $i_1, i_2, \dots, i_n$
4. Find voltage drops

## Mesh Analysis- Example

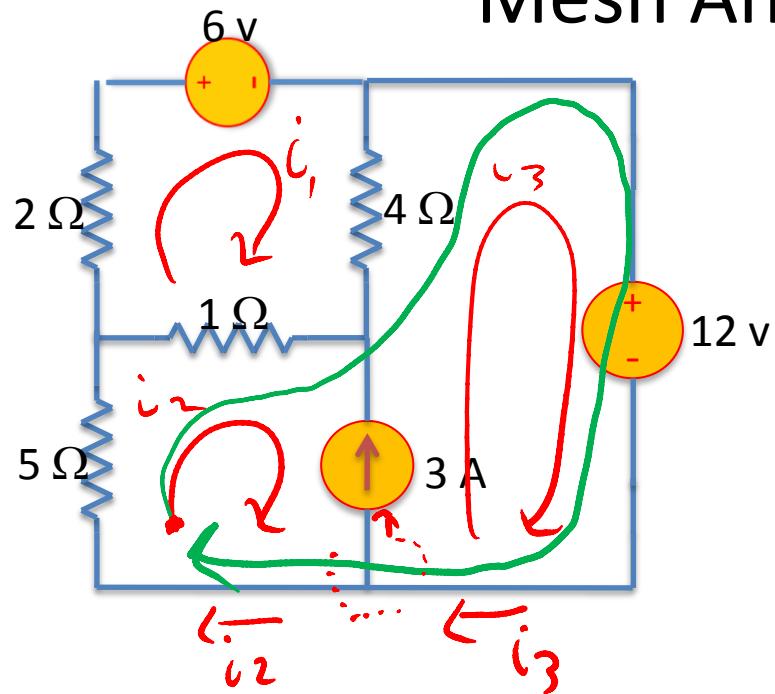

KVL MESH 1

$$2i_1 + 6 + (i_1 - i_3)4 + (i_1 - i_2)1 = 0$$

KVL SUPER MESH

$$(i_2)5 + (i_2 - i_1)1 + (i_3 + i_1)4 + 12 = 0$$




~~$$i_2 = 3 + i_3$$~~

$$i_3 = 3A + i_2$$

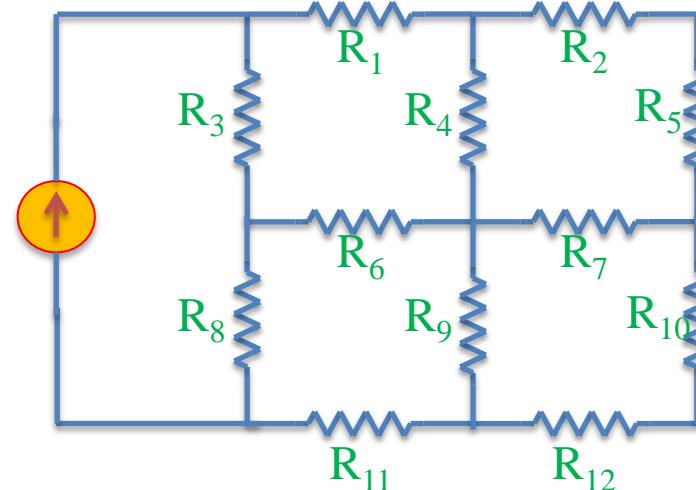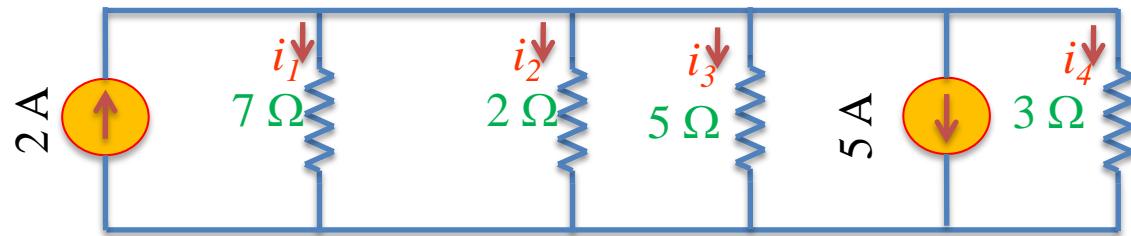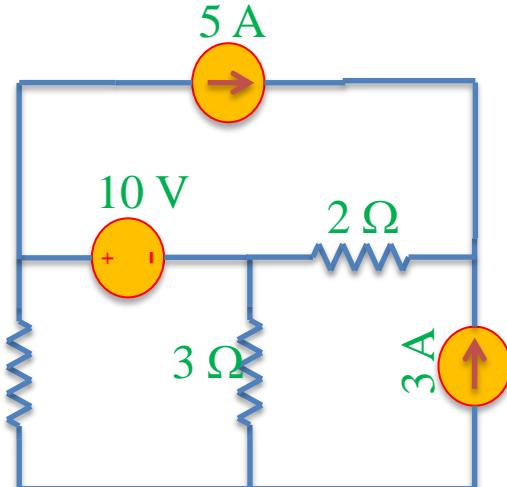
# Nodal Versus Mesh Analysis

- The method that results in fewer number of equations is more suitable.
  - Mesh analysis for networks with many series connected elements
  - Nodal Analysis for networks with many parallel connected elements

But also depends on the type of the sources.



# Nodal vs. mesh analysis?

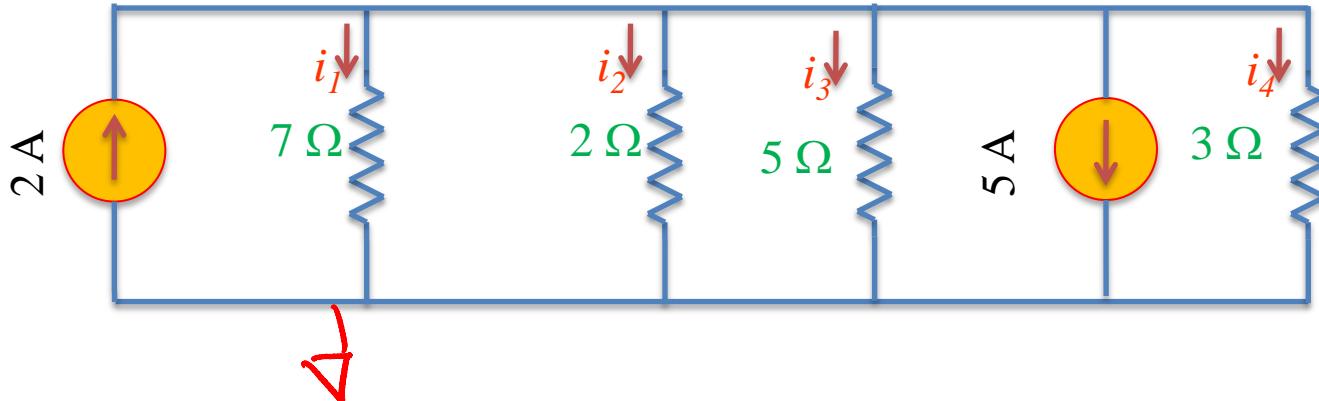

$V_N = \text{out}$  @ NODE 1


$$2 = i_1 + i_2 + i_3 + 5 + i_4$$

$$2 = \frac{V_1}{7} + \frac{V_1}{2} + \frac{V_1}{5} + 5 + \frac{V_1}{3}$$

$$V_1 = -2.5 V$$

$$i_1 = -\frac{2.5}{7} A \quad i_2 = -\frac{2.5}{2} A \quad i_3 = -\frac{2.5}{5} A \quad i_4 = -\frac{2.5}{3} A$$

# Nodal vs. mesh analysis?

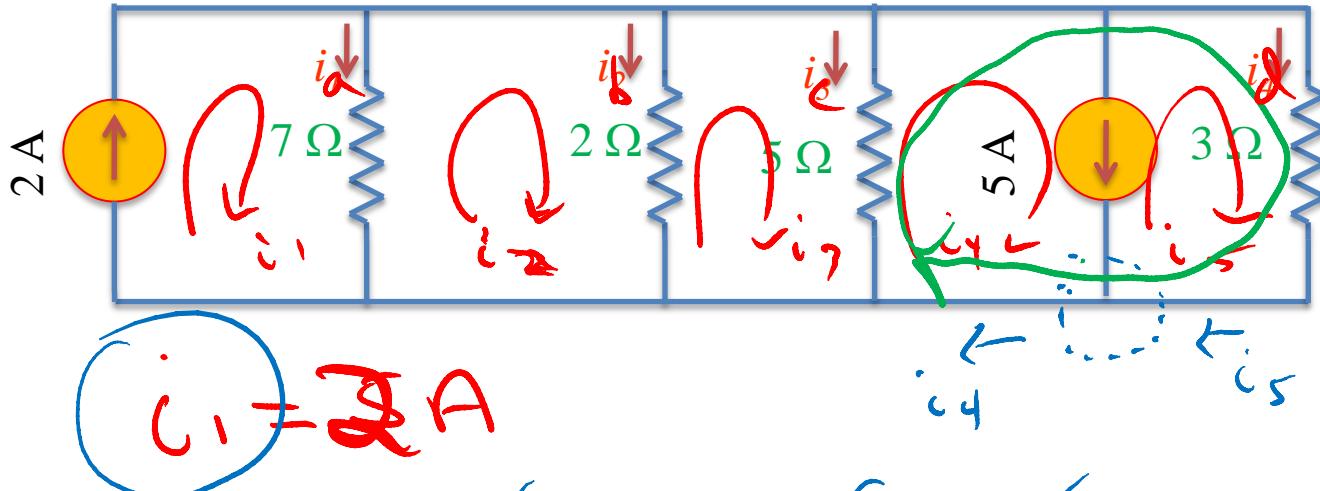

$$i_1 = 2A$$

$$\begin{aligned} i_a &= i_1 - i_2 \\ i_b &= i_2 - i_3 \\ i_c &= i_3 - i_4 \\ i_d &= i_4 \end{aligned}$$

$$\begin{aligned} ① \quad 7(i_2 - i_1) + 2(i_2 - i_3) &= 0 \\ ② \quad 2(i_3 - i_2) + 5(i_3 - i_4) &= 0 \\ ③ \quad 5(i_4 - i_3) + 3(i_5) &= 0 \end{aligned}$$


KCL

$$IN = 0 \text{ at } 5A$$

$$5A + i_5 = i_4$$

5eq 5 unknowns. Solve!

# Nodal vs. Mesh Analysis

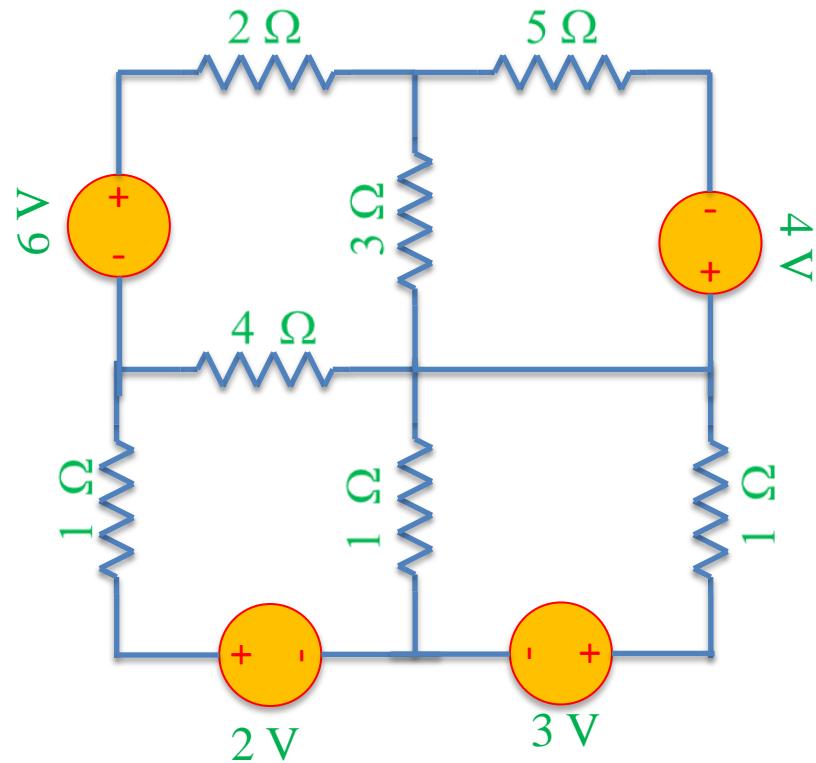

MESH

4 unknowns

4 eqns.


NO DAL

9 Nodes


8 eqn. 8 unknowns

/

# Nodal vs. Mesh Analysis

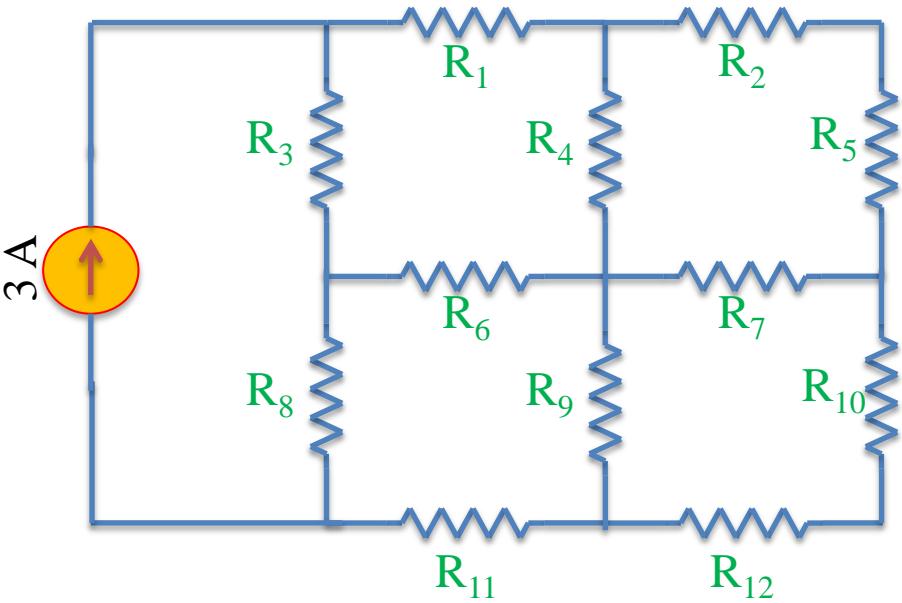

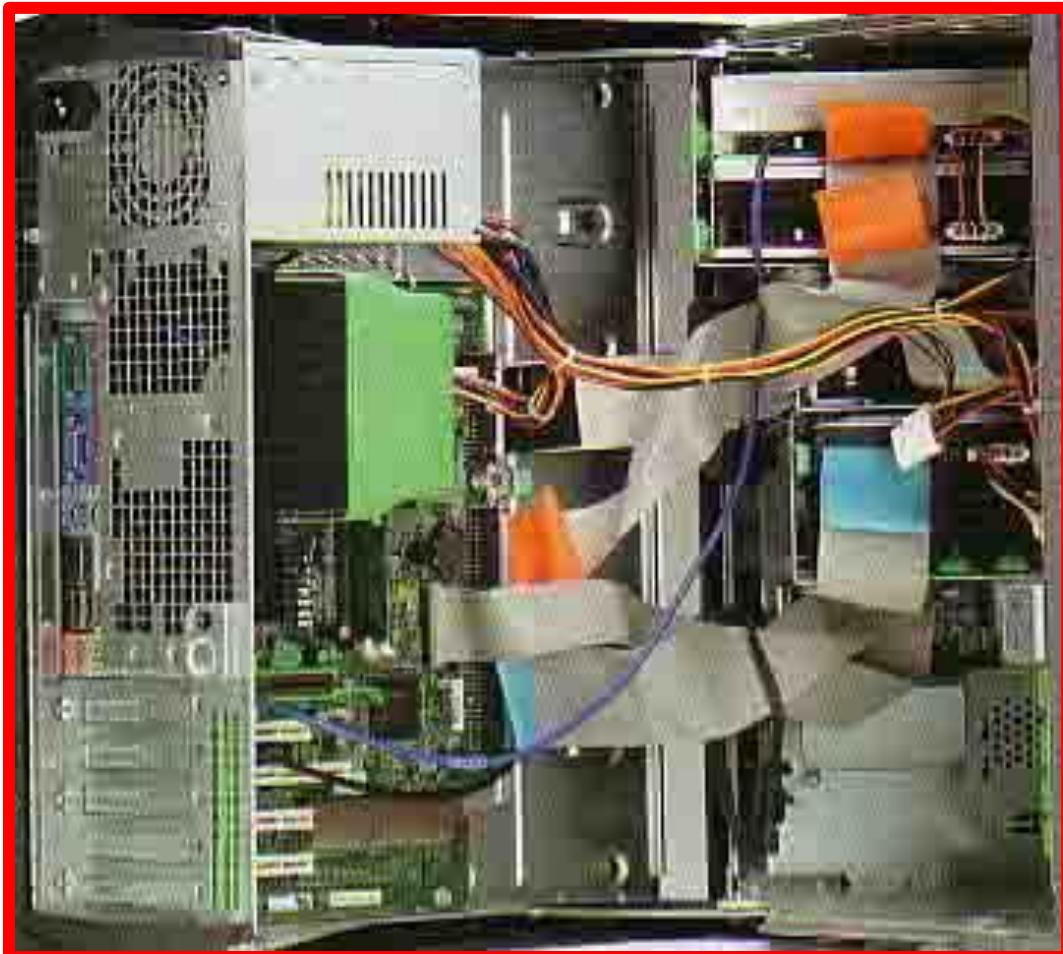
# Compartmentalization: Need for simplicity




Power brick image.  
And ask class to show their own...  
Demo: Computer?


# Thevenin's Theorem

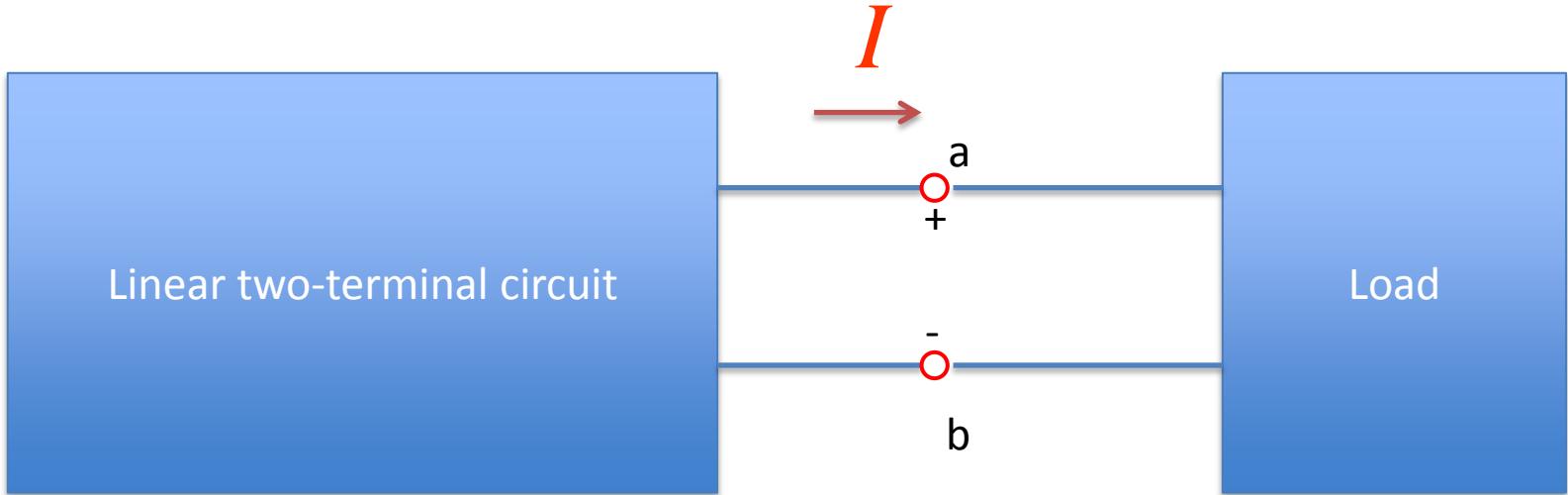


Equivalent to:

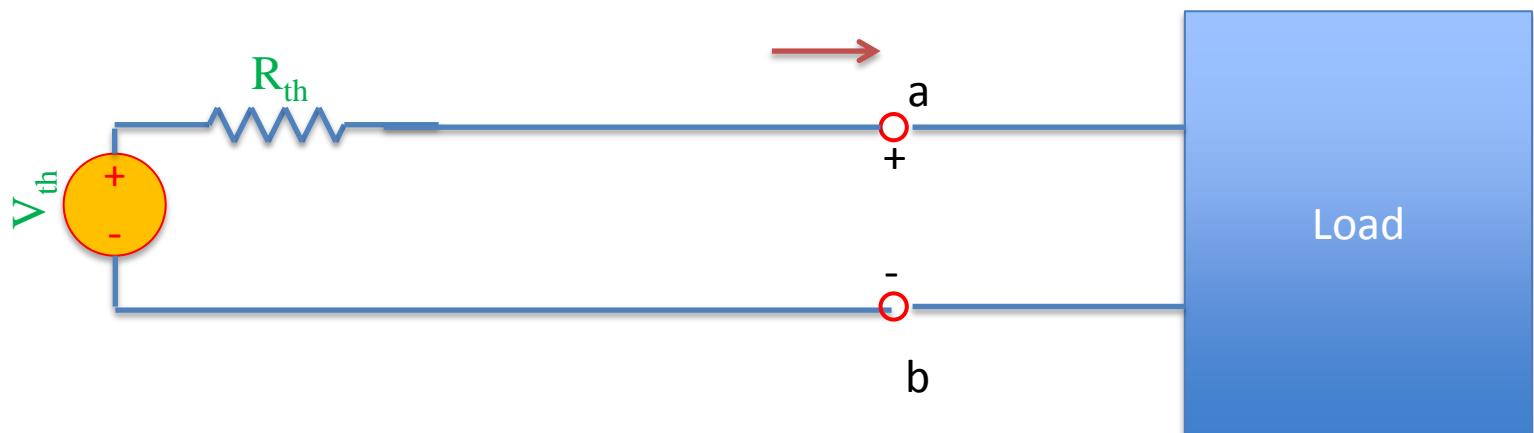


# Finding $V_{th}$ , $R_{th}$

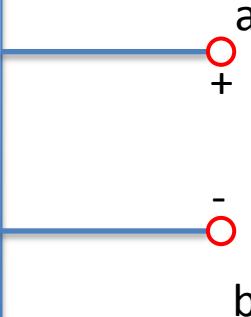


Equivalent to:

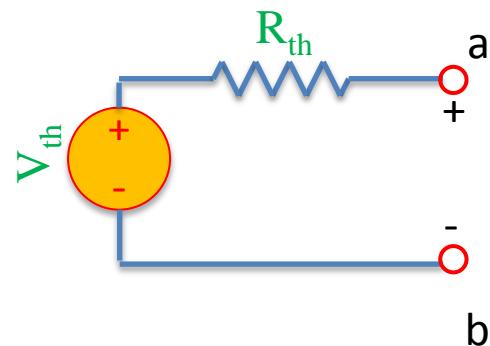

# Source/load

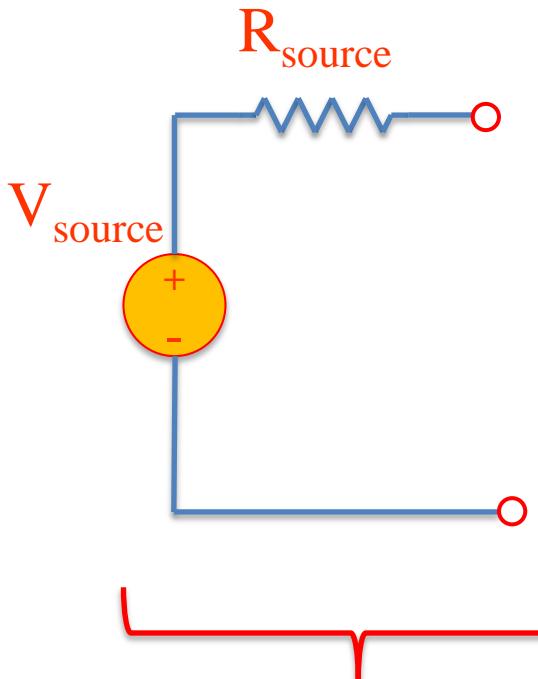

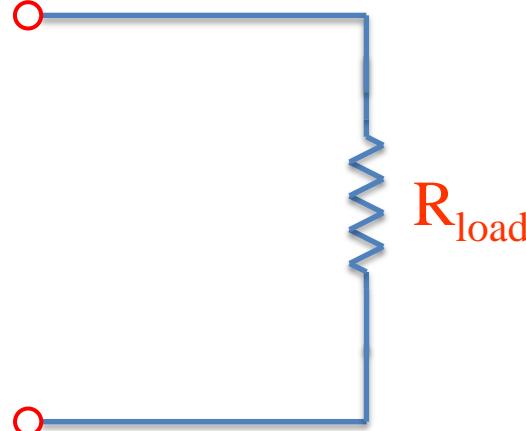Thevenin Thm:  
Any circuit can be  
represented by this  
equivalent circuit.



$$V_{load} = \frac{R_{load}}{R_{load} + R_{source}} V_{source}$$

*Derivation:*

Case 1:


$$R_{load} \gg R_{source}$$

Case 2:


$$R_{source} \gg R_{load}$$

We say  $R_{load}$  “*loads down*” the source.

# Source/load

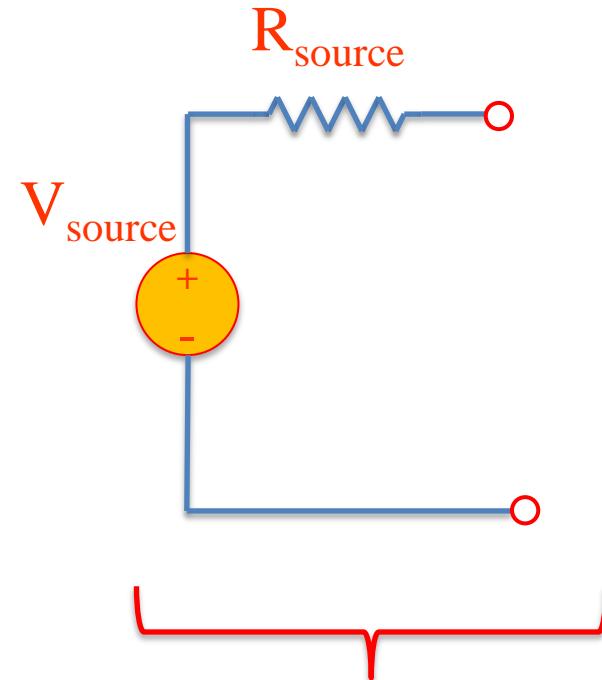

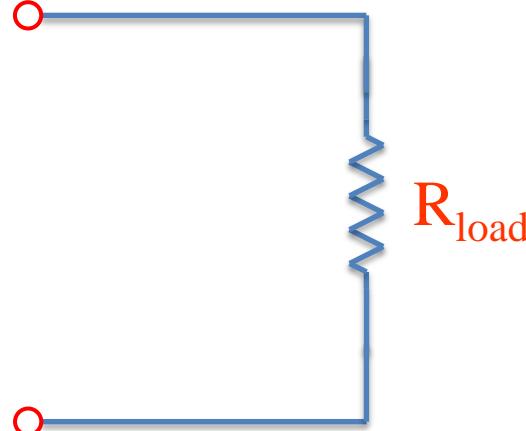Thevenin Thm:  
Any circuit can be  
represented by this  
equivalent circuit.



$$V_{load} = \frac{R_{load}}{R_{load} + R_{source}} V_{source}$$

*Derivation:*

Case 1:

$$R_{load} \gg R_{source}$$


Case 2:

$$R_{source} \gg R_{load}$$


We say  $R_{load}$  “*loads down*” the source.

# Example


Find Thevenin equivalent circuit:

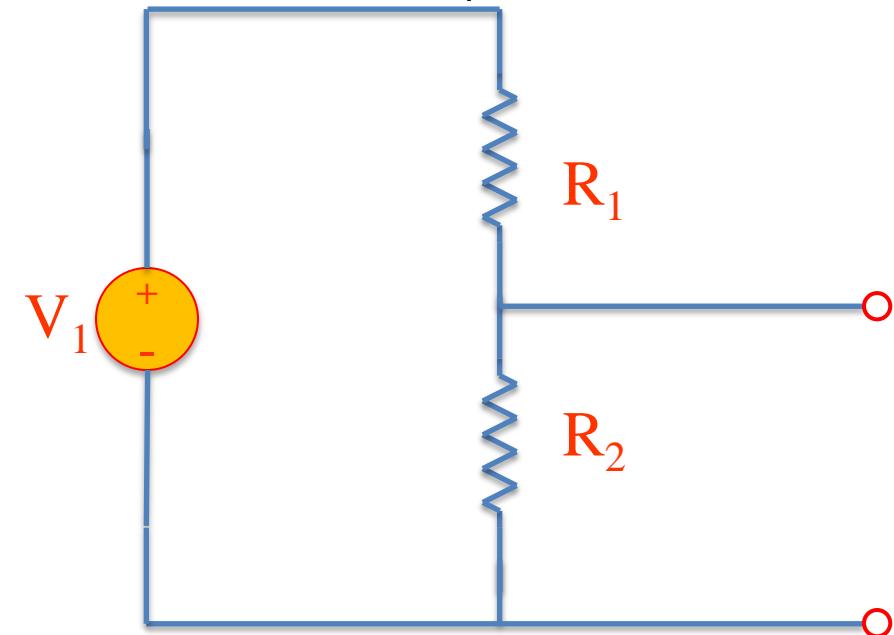

# Norton's Theorem

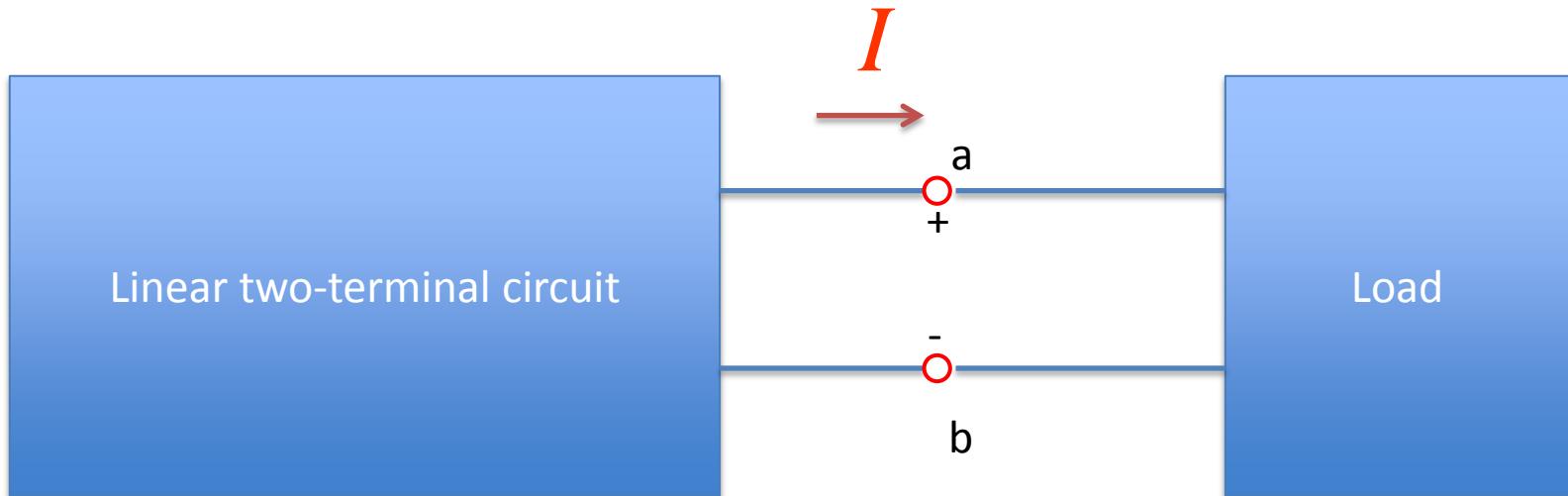


Equivalent to:

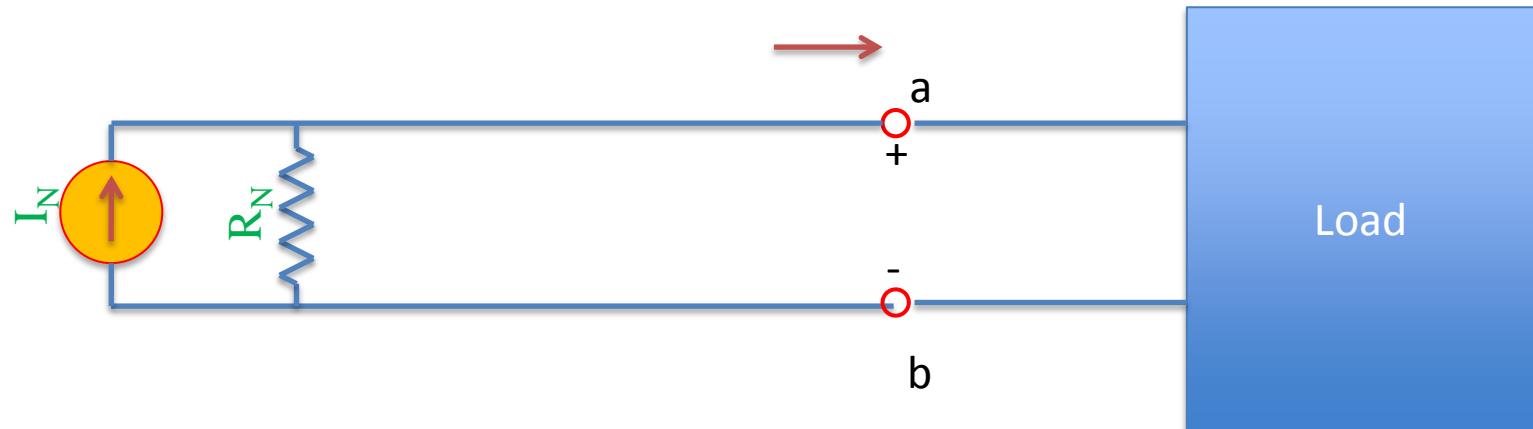


# Finding $V_{th}$ , $R_{th}$


Linear two-terminal circuit

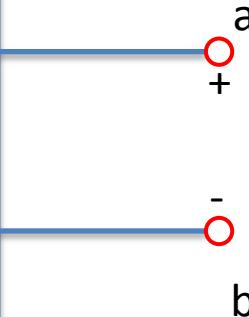

Equivalent to:

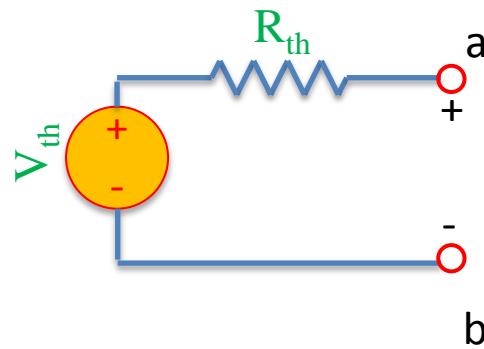


Equivalent to:

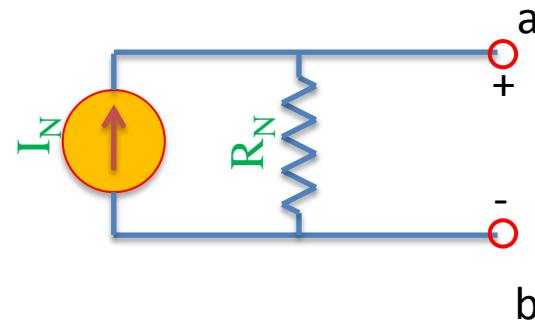
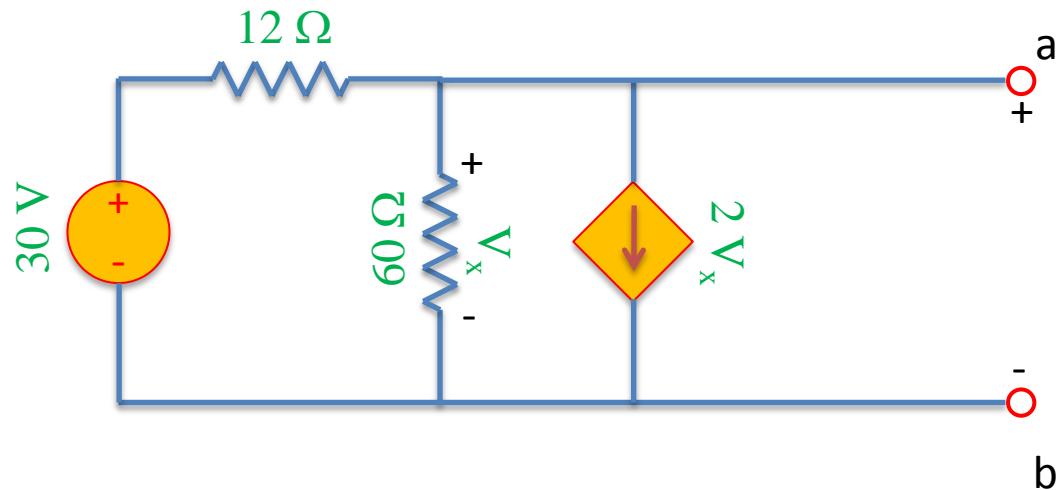
# Example

Find the Thevenin & Norton equivalent circuit of the circuit below with respect to terminals a and b:



# “Baby” monster problem

Find the Thevenin & Norton equivalent circuit of the circuit below with respect to terminals a and b:

