

Announcements:

1. HW
2. etc

EECS 70A: Network Analysis

Phasors

$$v(t) = \operatorname{Re}(\underbrace{\mathbf{V}}_{\substack{\text{voltage} \\ \text{phasor}}} e^{j\omega t})$$

$$i(t) = \operatorname{Re}(\underbrace{\mathbf{I}}_{\substack{\text{current} \\ \text{phasor}}} e^{j\omega t})$$


$$\mathbf{V} = \mathbf{I} \mathbf{Z}$$

Fourier

$$F(t) = \operatorname{Re} \left[\sum_n a_n e^{j\omega_n t} \right]$$

$\rightarrow \int a(\omega) d\omega e^{j\omega t}$

Conversion procedures

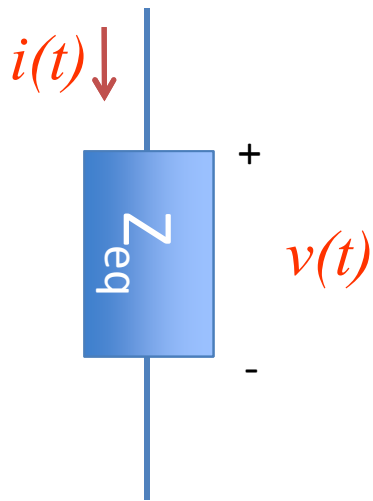

Given $i(t)$ find $v(t)$:

$$i(t) \rightarrow \mathbf{I} \rightarrow \mathbf{V} = \mathbf{I} Z_{eq} \rightarrow v(t)$$

Given $v(t)$ find $i(t)$:

$$v(t) \rightarrow \mathbf{V} \rightarrow \mathbf{I} = \mathbf{V} / Z_{eq} \rightarrow i(t)$$

Conversion procedures

$$i(t) \rightarrow \mathbf{I}$$

$$i(t) = I_m \cos(\omega t + \phi) \Rightarrow \mathbf{I} = I_m e^{j\phi}$$

$$v(t) \rightarrow \mathbf{V}$$


$$v(t) = V_m \cos(\omega t + \phi) \Rightarrow \mathbf{V} = V_m e^{j\phi}$$

$$\mathbf{I} \rightarrow i(t)$$

$$i(t) = \operatorname{Re}(\mathbf{I} e^{j\omega t})$$

$$\mathbf{V} \rightarrow v(t)$$
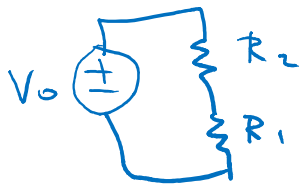
$$v(t) = \operatorname{Re}(\mathbf{V} e^{j\omega t})$$





$$V_{R_1} = V_0 \frac{R_1}{R_1 + R_2}$$

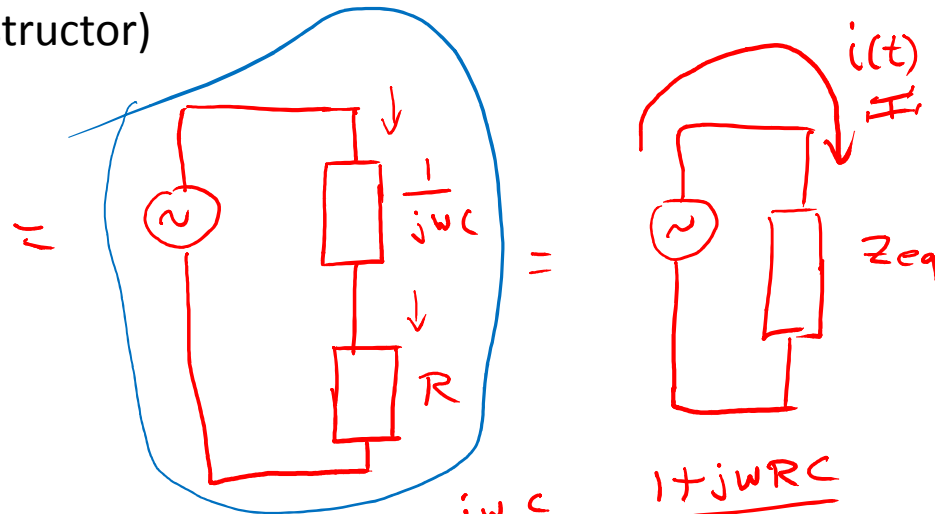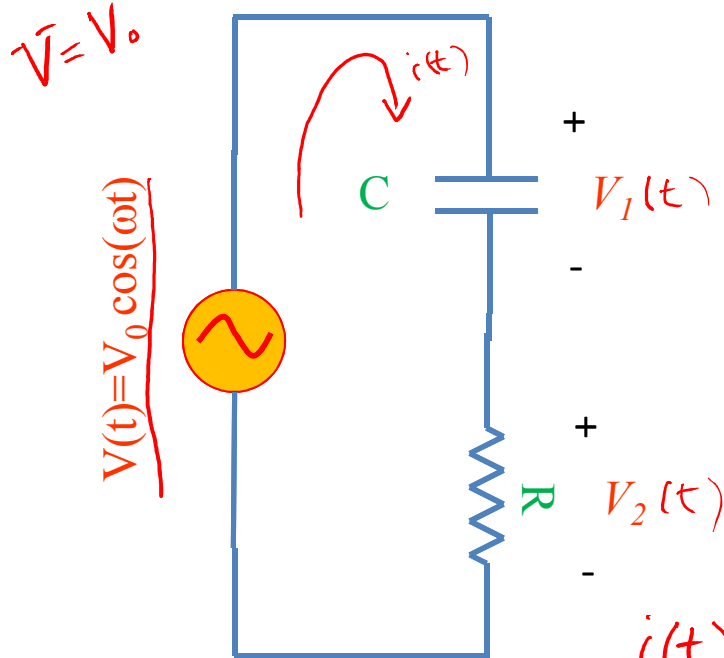Example problem #3

t time
 $\tau = RC$

Find $i(t)$, $V_1(t)$, $V_2(t)$ for this circuit: (instructor)



$$Z_{eq} = \left(R + \frac{1}{j\omega C} \right) \frac{j\omega C}{j\omega C} = \frac{1 + j\omega RC}{j\omega C}$$

$$\bar{V} = Z_{eq} \bar{I} \Rightarrow \bar{I} = \frac{\bar{V}}{Z_{eq}} = \frac{V_0}{R + \frac{1}{j\omega C}}$$

$$i(t) = \text{Re} \left[\bar{I} e^{j\omega t} \right] = \text{Re} \left[\frac{V_0}{R + \frac{1}{j\omega C}} e^{j\omega t} \right]$$

$$i(t) = \text{Re} \left[V_0 \frac{R}{R} \frac{j\omega C}{1 + j\omega RC} e^{j\omega t} \right] = \text{Re} \left[\frac{V_0}{R} \frac{j\omega RC}{1 + j\omega RC} e^{j\omega t} \right]$$

$$= \frac{V_0}{R} \frac{\omega \tau}{\sqrt{1 + (\omega \tau)^2}} \cos \left(\omega t + \tan^{-1} \left(\frac{1}{\omega \tau} \right) \right)$$

$$i(t) = \text{Re} \left[\frac{V_0}{R} \frac{j\omega RC}{1+j\omega RC} e^{j\omega t} \right] = \frac{V_0}{R} \text{Re} \left[\frac{j\omega \tau}{1+j\omega \tau} e^{j\omega t} \right]$$

$$\frac{j\omega \tau}{1+j\omega \tau} = r e^{j\phi}$$

$$\frac{j\omega \tau}{1+j\omega \tau} \frac{1-j\omega \tau}{1-j\omega \tau} = \frac{j\omega \tau + (\omega \tau)^2}{1 + (\omega \tau)^2}$$

$$= \omega \tau \frac{j + \omega \tau}{1 + (\omega \tau)^2} = \frac{\omega \tau}{1 + (\omega \tau)^2} (j + \omega \tau)$$

$$i(t) = \frac{V_0}{R} \text{Re} \left[\frac{\omega \tau}{1 + (\omega \tau)^2} (j + \omega \tau) e^{j\omega t} \right] =$$

$$= \frac{V_0}{R} \frac{\omega \tau}{1 + (\omega \tau)^2} \text{Re} \left[(j + \omega \tau) e^{j\omega t} \right]$$

$$= \frac{V_0}{R} \frac{\omega \tau}{1 + (\omega \tau)^2} \text{Re} \left[(?) e^{j(?)\omega t} \right]$$

$$= \frac{V_0}{R} \frac{\omega \tau}{1 + (\omega \tau)^2} \text{Re} \left[\sqrt{1 + (\omega \tau)^2} e^{j \tan^{-1} \frac{1}{\omega \tau}} e^{j\omega t} \right]$$

$$= \frac{V_0}{R} \frac{\omega \tau}{\sqrt{1 + (\omega \tau)^2}} \text{Re} \left[e^{j \tan^{-1} \frac{1}{\omega \tau}} e^{j\omega t} \right]$$


$$= \frac{V_0}{R} \text{Re} \left[r e^{j\phi} e^{j\omega t} \right]$$

$$= \frac{V_0}{R} \text{Re} \left[r e^{j(\omega t + \phi)} \right]$$

$$= \frac{V_0}{R} r \cos(\omega t + \phi)$$

$$e^{u} e^{v} = e^{u+v}$$

$$u \equiv w\tau + j = (?) e^{j(?)}$$

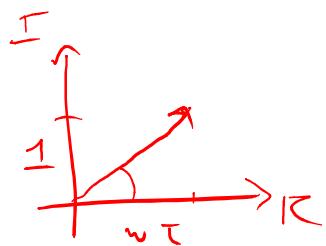

$$= \sqrt{\text{Re}(u)^2 + \text{Im}(u)^2} e^{j \tan^{-1} \frac{\text{Im}(u)}{\text{Re}(u)}}$$

$$= \sqrt{1 + (w\tau)^2} e^{j \tan^{-1} \frac{1}{w\tau}}$$

DISCUSSION

$$u = \frac{a + jb}{c + jd}$$

a b c d real

Re(u)

Also:
write

a + jb

as


—

e

jφ


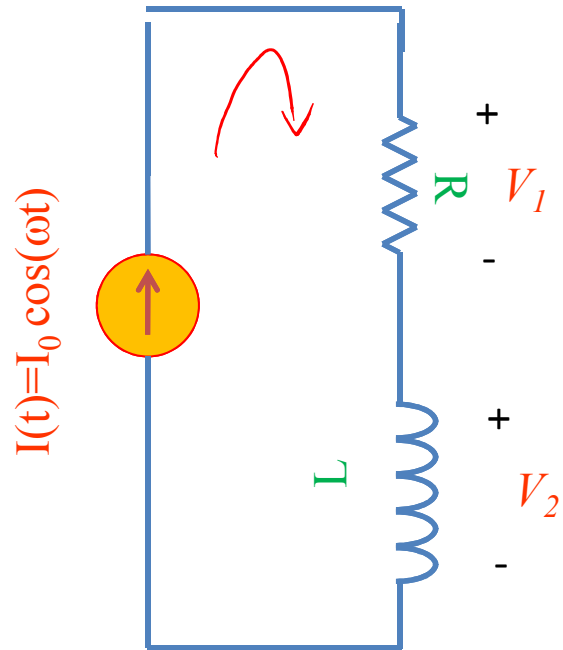
Example problem #4

Find $i(t)$, $V_1(t)$, $V_2(t)$ for this circuit: (students)



$$\begin{aligned}V_1(t) &= R i(t) = R I_0 \cos(\omega t) \\V_2(t) &= \text{Re} [V_2 e^{j\omega t}] \\&= \text{Re} [\cancel{I_0} j\omega L e^{j\omega t}] \\&= \text{Re} [I_0 j\omega L e^{j\omega t}] \\&= I_0 \omega L \text{Re} [j e^{j\omega t}] \\&= I_0 \omega L \\&= -I_0 \omega L \sin(\omega t)\end{aligned}$$


High pass filter

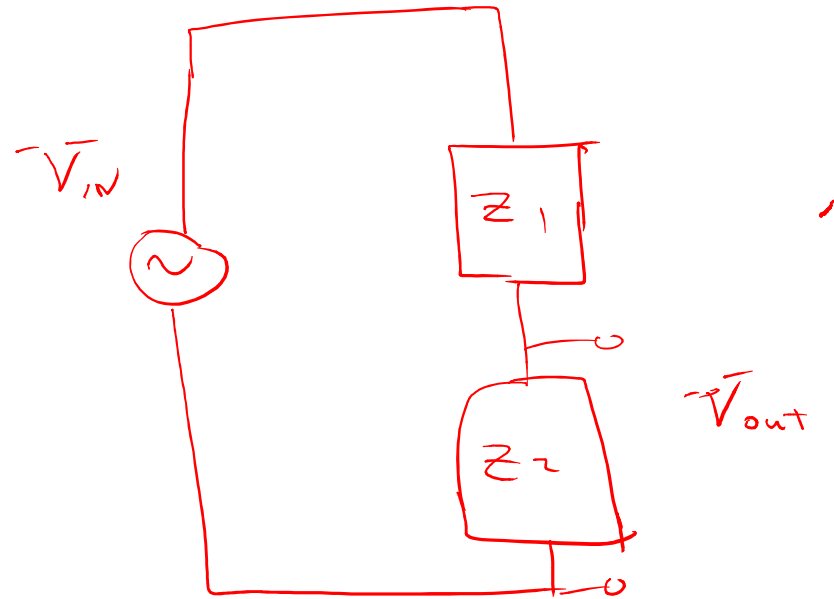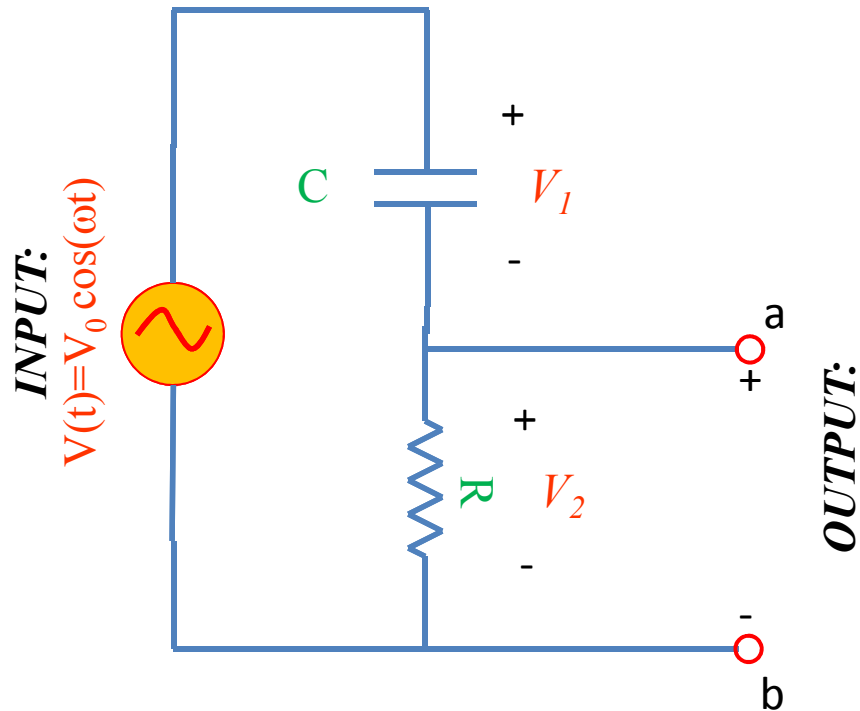

$$\begin{aligned} \bar{V}_{out} &= \bar{V}_{in} \frac{Z_2}{Z_1 + Z_2} = \bar{V}_{in} \frac{R}{R + \left(\frac{1}{j\omega C}\right)} \\ &= \bar{V}_{in} \frac{j\omega CR}{1 + j\omega RC} = \bar{V}_{in} \frac{j\omega \tau}{1 + j\omega \tau} \end{aligned}$$

As $\omega \rightarrow \infty$
 $\omega \rightarrow 0$ $\bar{V}_{out} = \bar{V}_{in} \Rightarrow V_{out}(t) = V_{in}(t)$

Low pass filter

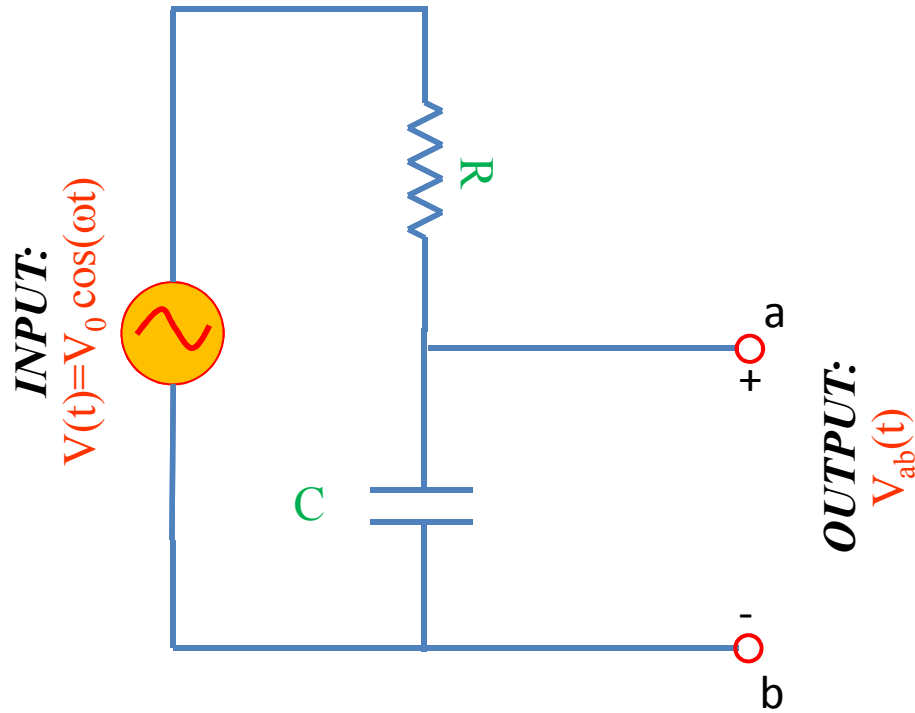

$$V_c = I_c \frac{1}{j\omega C}$$

Complex numbers

Euler's relationship:

$$e^{j\phi} = \cos \phi + j \sin \phi$$

Memorize

Need to be able to manipulate complex numbers, e.g. given:

$$u = \frac{A + jB}{C + jD} \quad (A, B, C, D \text{ all real})$$

- Find $\text{Re}(u)$, $\text{Im}(u)$
- Express u as $x + jy$, $re^{i\phi}$
- Find $\text{Re}(u e^{j\omega t})$

Did some of this in office hours..