

- Announcements:
1. Announcement


EECS 70A: Network Analysis

29 May 2014





<http://www.peachparts.com/shopforum/showthread.php?t=256624>

“Transfer function”

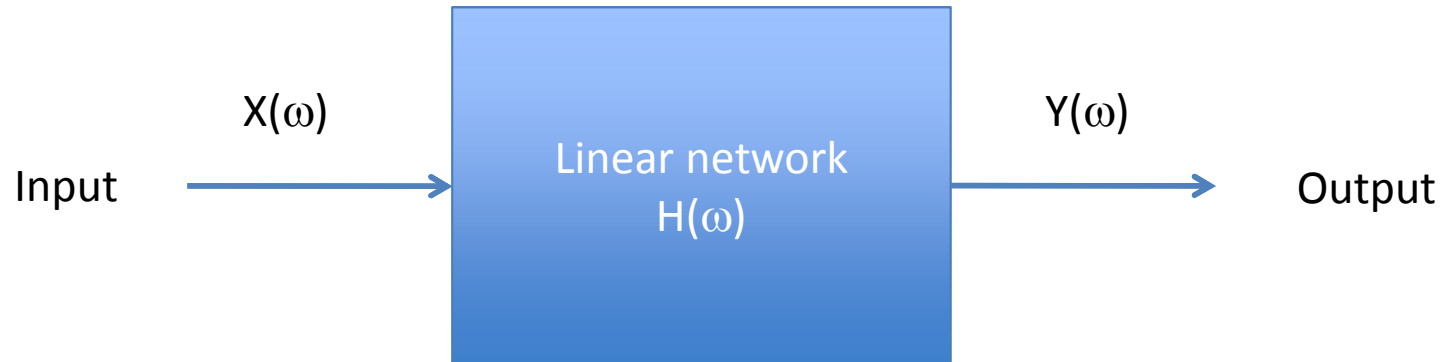

Band pass filter (RLC)

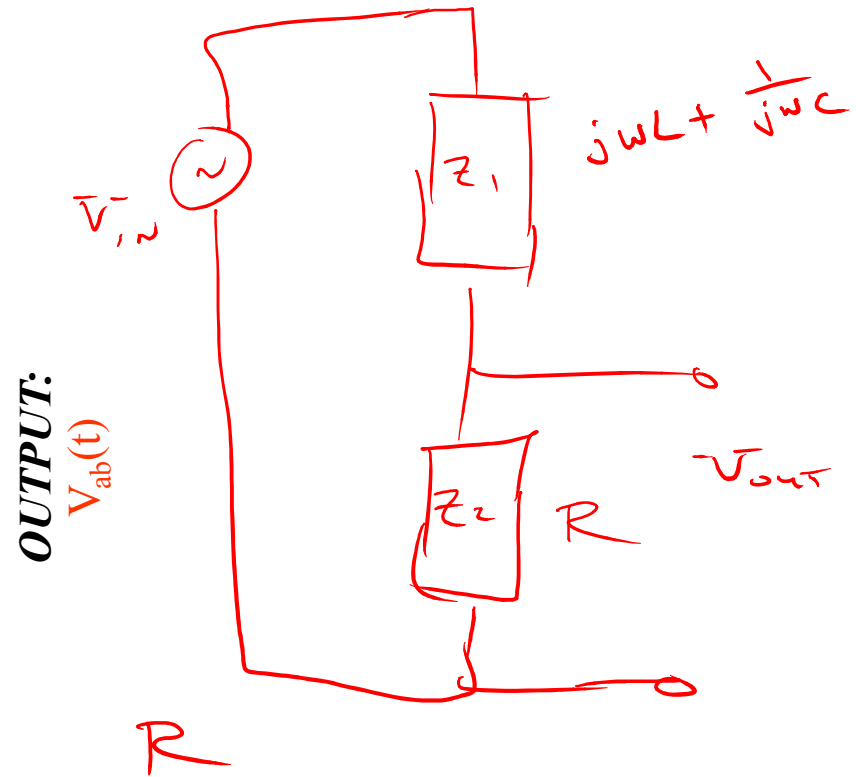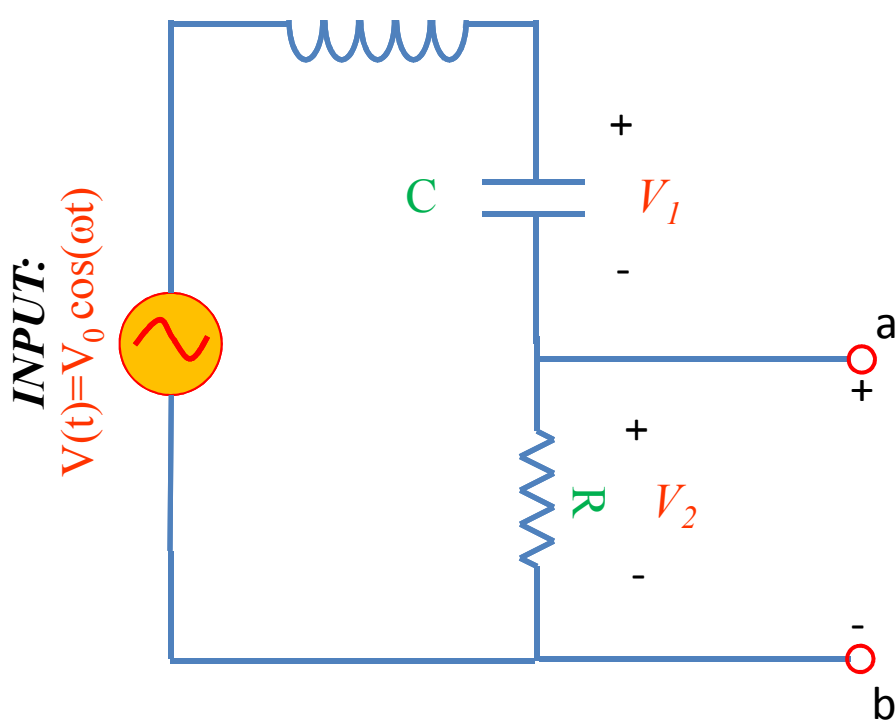

$$H(\omega) = \frac{Z_2}{Z_1 + Z_2} = \frac{R}{R + j(\omega L - \frac{1}{\omega C})}$$

$$= \frac{R}{R + j(\omega L - \frac{1}{\omega C})}$$

$$\omega^2 L - \frac{1}{C} = 0$$

$$\omega_R = \sqrt{\frac{1}{LC}}$$

$$H(\omega) = \frac{R}{R + j(\omega L - \frac{1}{\omega C})}$$



Bandwidth

"3dB" BW

$$H(\omega) = \frac{R}{R + j(\omega L - \frac{1}{\omega C})} \frac{R - j(\omega L - \frac{1}{\omega C})}{R - j(\omega L - \frac{1}{\omega C})}$$

$$= \frac{R}{R^2 + (\omega L - \frac{1}{\omega C})^2} \left[R - j(\omega L - \frac{1}{\omega C}) \right]$$

$$|H(\omega)| = \sqrt{(\operatorname{Re}[H(\omega)])^2 + (\operatorname{Im}[H(\omega)])^2} = \frac{R}{R^2 + (\omega L - \frac{1}{\omega C})^2} \sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}$$

$$= \frac{R}{\sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}}$$


$$\omega_0 \equiv \frac{1}{\sqrt{LC}}$$

$$0.7 = \frac{1}{\sqrt{2}}$$

$\frac{\omega_0}{B} \equiv Q$ "quality factor"


$$= \omega_0 \frac{L}{R} = \frac{1}{\omega_0 RC}$$

VERY IMPORTANT

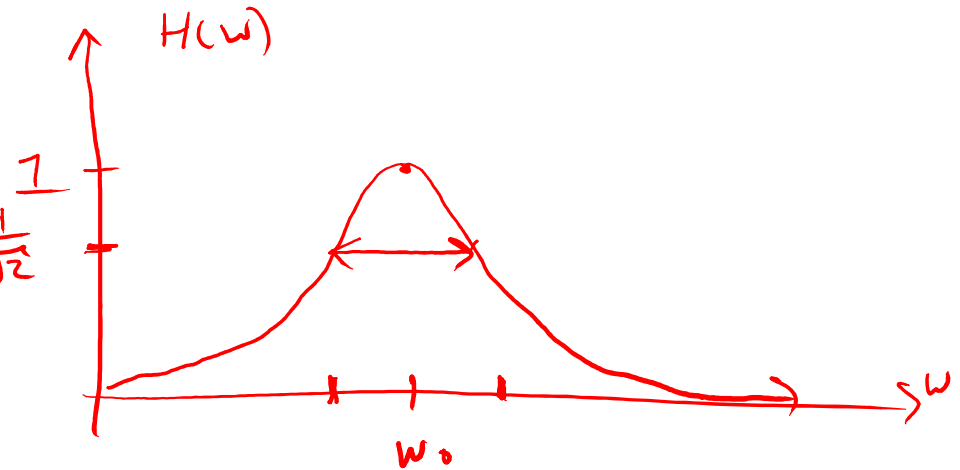



$$B = \frac{R}{L}$$

Bode of RLC

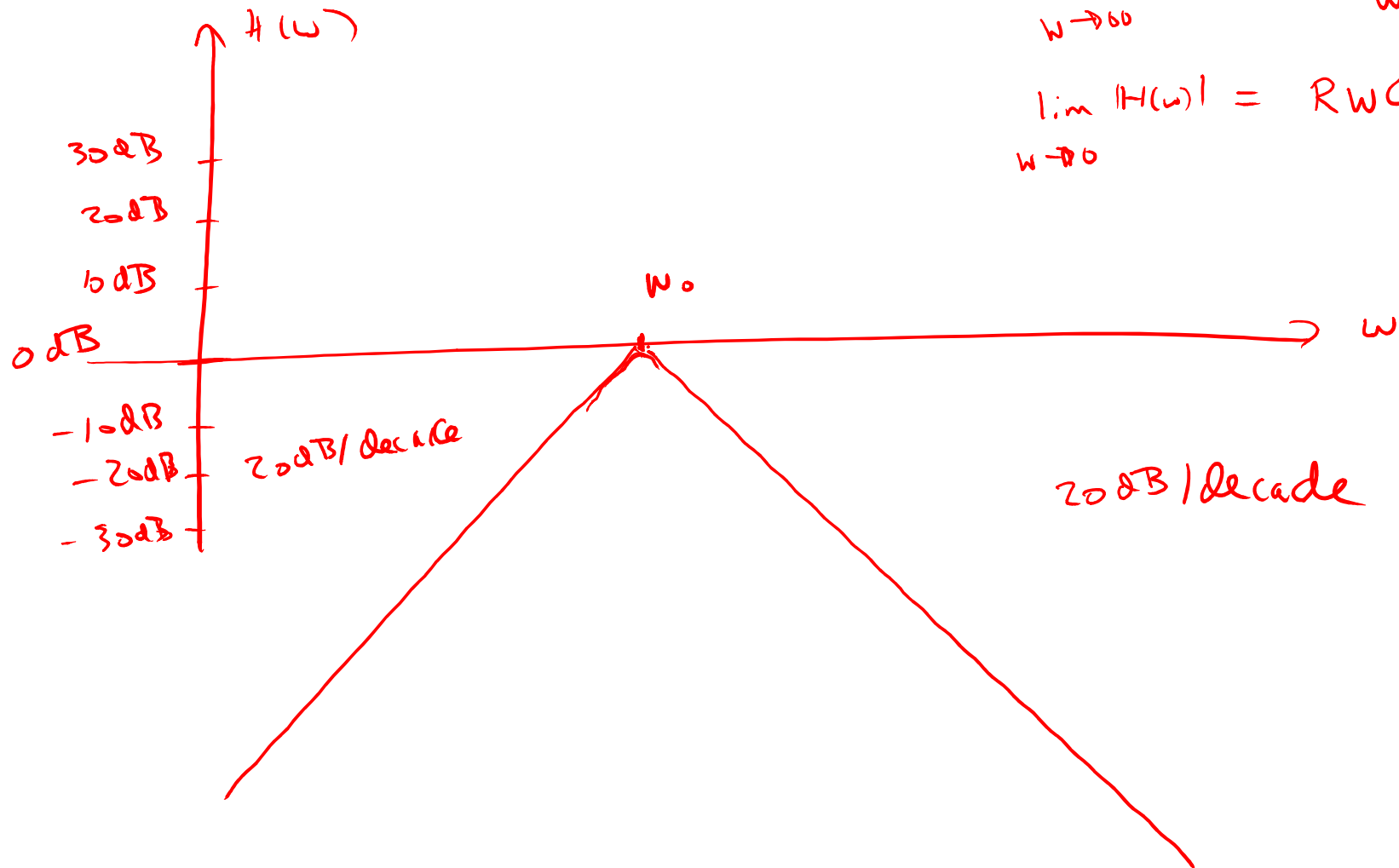

$$\lim_{\omega \rightarrow \infty} |H(\omega)| = \frac{R}{\omega L}$$

$$\lim_{\omega \rightarrow 0} |H(\omega)| = R\omega C$$

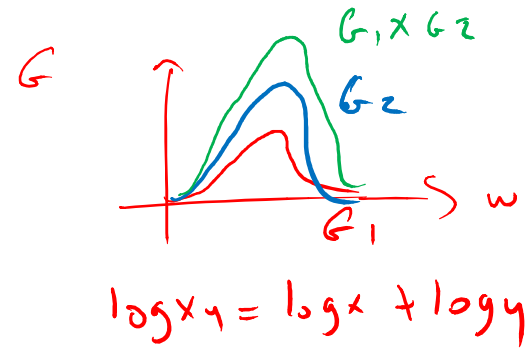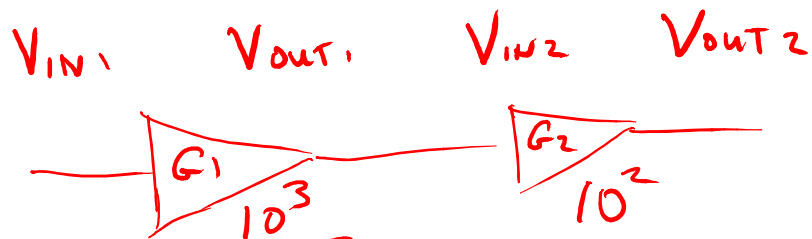

$$\frac{V_{OUT1}}{V_{IN1}} = G_1$$

$$\frac{V_{OUT2}}{V_{IN2}} = G_2$$

$$\frac{V_{OUT2}}{V_{IN1}} = \frac{V_{IN2}}{V_{IN1}} G_2 = \frac{V_{OUT1}}{V_{IN1}} G_2 = G_1 G_2 = 10^2 10^3 = 10^5$$

$$G_1 (\text{dB}) = 20 \log \frac{V_{OUT1}}{V_{IN1}} = 20 \log 10^3 = 20 \cdot 3 \log 10 = 60 \text{ dB}$$

$$G_2 (\text{dB}) = 40 \text{ dB}$$

$$\begin{aligned} G_{\text{TOTAL}} (\text{dB}) &= 20 \log \frac{V_{OUT2}}{V_{IN1}} = 20 \log (G_1 G_2) \\ &= 20 \log G_1 + 20 \log G_2 = G_1 (\text{dB}) + G_2 (\text{dB}) \\ &= 60 \text{ dB} + 40 \text{ dB} = 100 \text{ dB} \end{aligned}$$

Fourier

$$F(t) = \text{Re} \left[\sum_n a_n e^{j\omega_n t} \right]$$




$$V_{in}(t) = \text{Re} \left[\sum_n a_n e^{j\omega_n t} \right]$$

$$V_{out} = \text{Re} \left[\sum_n a_n H(\omega_n) e^{j\omega_n t} \right]$$

EX. $V_{in}(t) = 1 \text{ V} \sin[(97.1 \text{ MHz} \cdot 2\pi)t] + 3 \text{ V} \sin[(100.3 \text{ MHz} \cdot 2\pi)t]$


EECS 70A

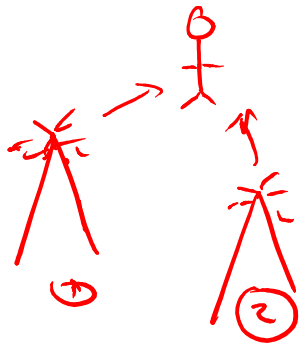

$$E = E_1 + E_2$$

X = EECS 70 STUDENT

$$2\pi F = \omega$$



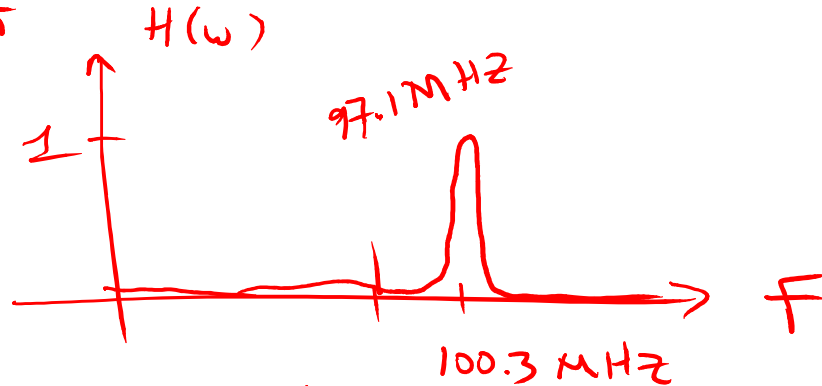


(t)

$$V_{out} = 1 \text{ V} H(\omega) \Big|_{\omega = 97.1 \text{ MHz} \cdot 2\pi} \sin(97.1 \text{ MHz} \cdot 2\pi t) + 3 \text{ V} H(\omega) \Big|_{\omega = 100.3 \text{ MHz}} \sin(100.3 \text{ MHz} \cdot 2\pi t)$$

$$= 3 \text{ V} \sin(100.3 \text{ MHz} \cdot 2\pi t)$$

Modulation Schemes

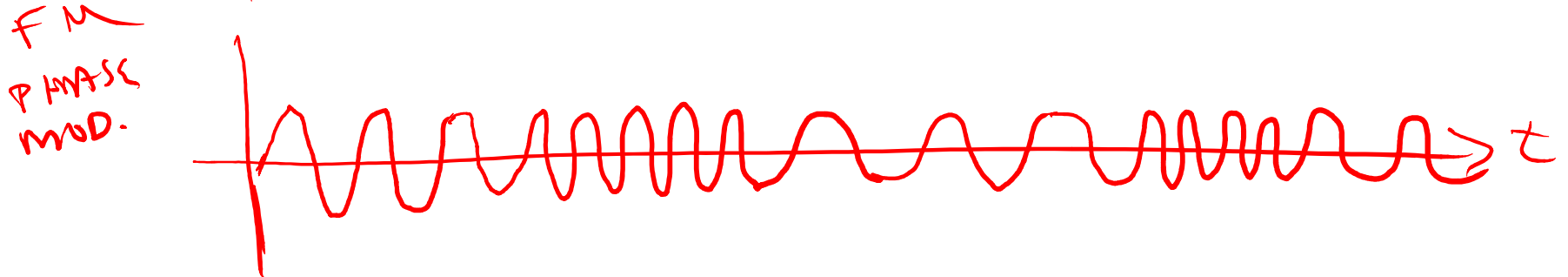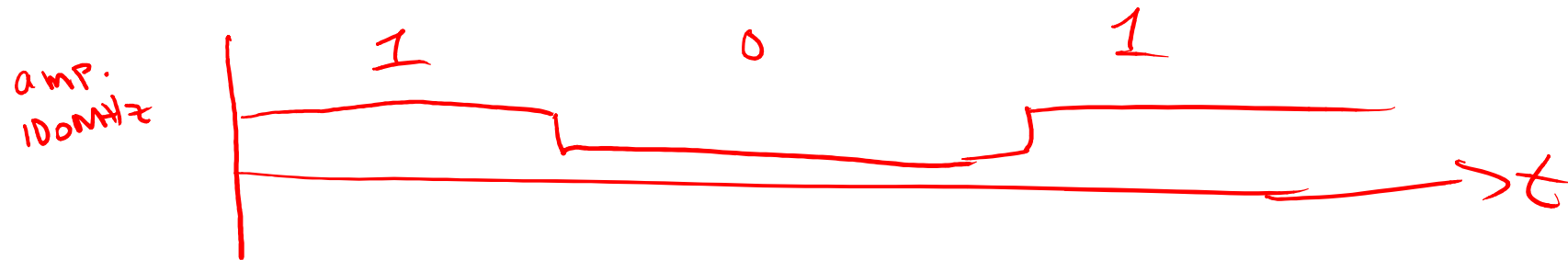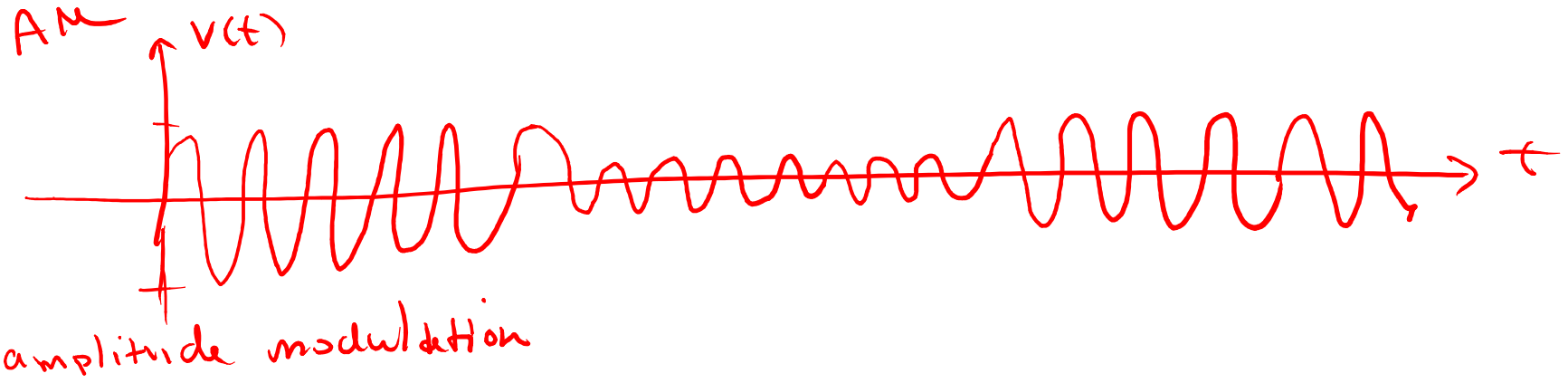


Sidebands

$$V(t) = (1V \sin(1\text{kHz} 2\pi t)) \sin(1\text{MHz} 2\pi t)$$

$$\text{Fourier} = \text{Re} \left[\sum a_n e^{j\omega_n t} \right]$$
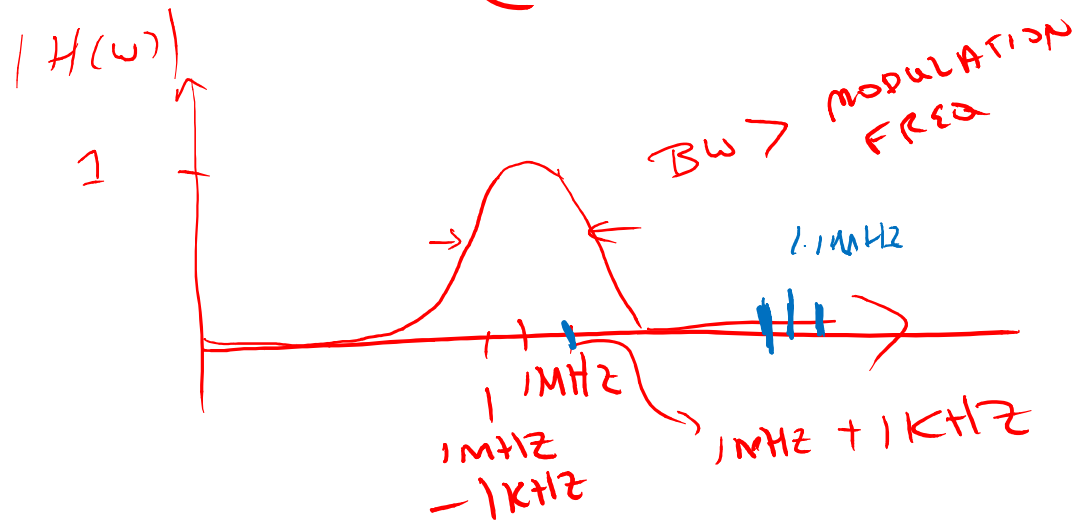
$$= (1V) e^{j(1\text{MHz} + 1\text{kHz}) 2\pi t} + (1V) e^{j(1\text{MHz} - 1\text{kHz}) 2\pi t}$$



Demo

