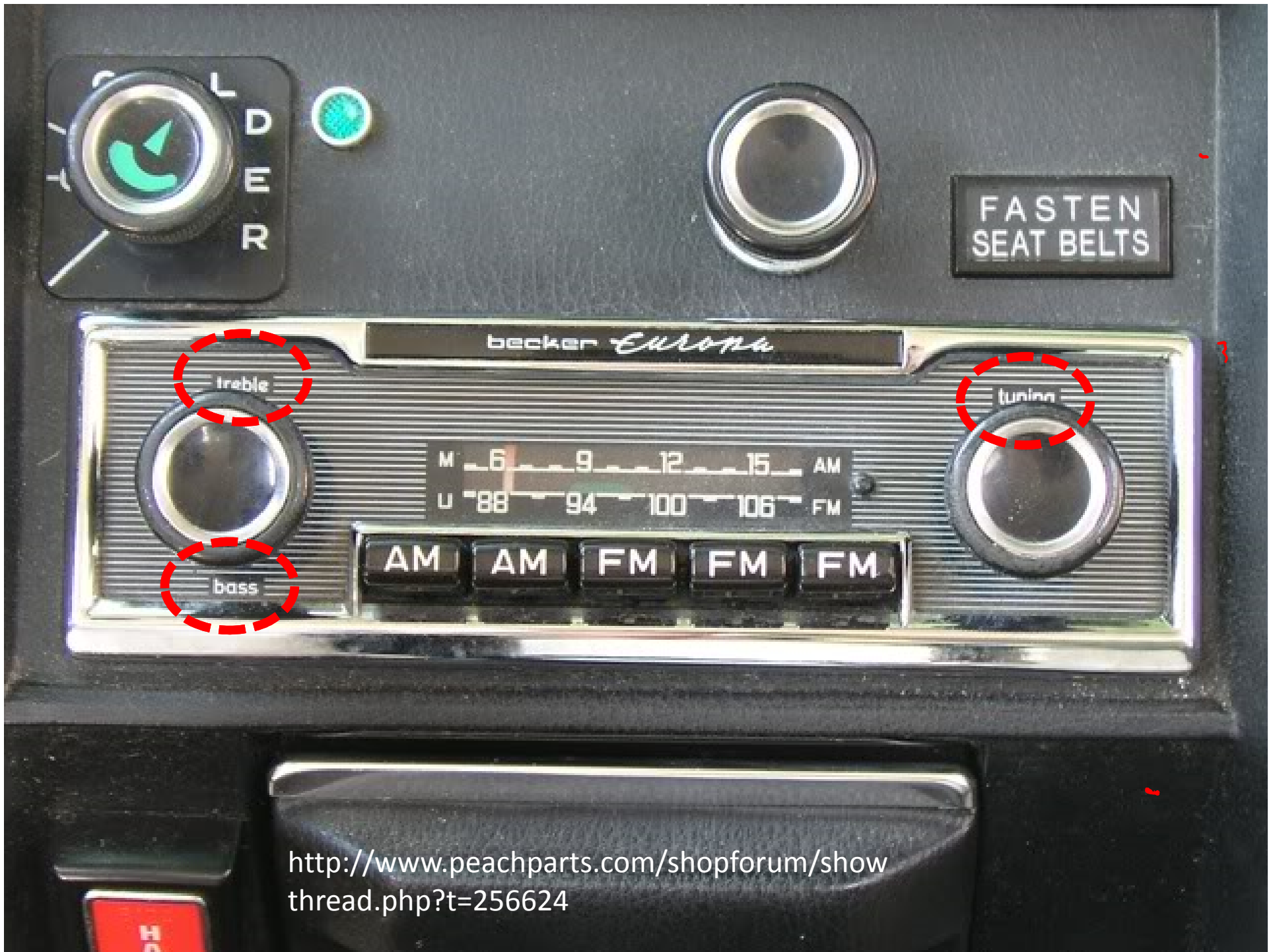


- Announcements:
1. Announcement





EECS 70A: Network Analysis

3 June 2014




<http://www.peachparts.com/shopforum/showthread.php?t=256624>


Rectification

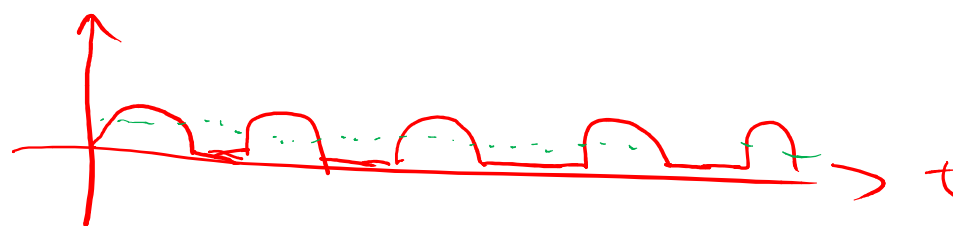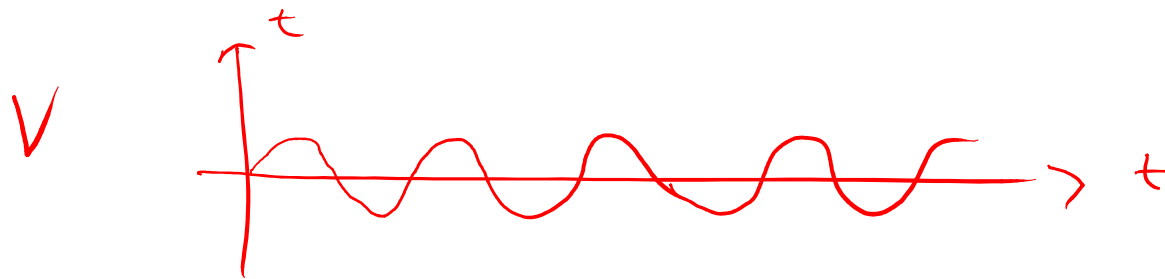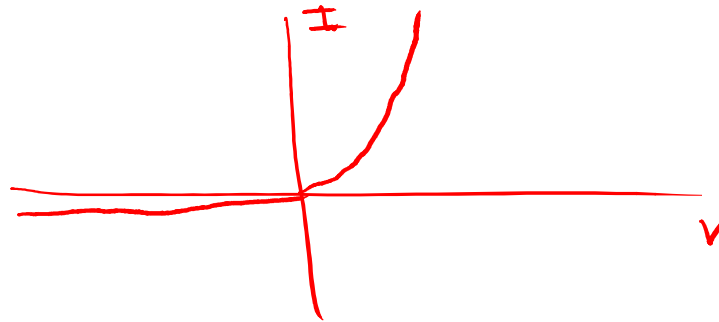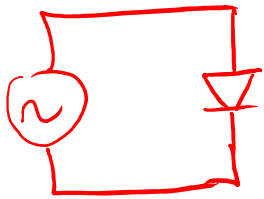
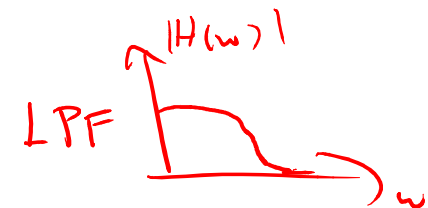
$$i(t) = i_{dc} + i_{ac} \cos(2\omega t) + \dots$$



$$I(V) = I(V_0) + \left. \frac{dI}{dV} \right|_{V_0} (V - V_0) + \left. \frac{d^2 I}{dV^2} \right|_{V_0} (V - V_0)^2 + \dots$$

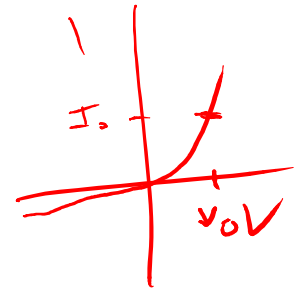

$$V(t) = \underset{\text{DC}}{V_0} + V_{ac} \cos(\omega t)$$



$$I = \underbrace{I(V_0)}_{\text{DC}} + \underbrace{\left. \frac{dI}{dV} \right|_{V_0}}_{\omega} (V_{ac} \cos \omega t) + \underbrace{\left. \frac{d^2 I}{dV^2} \right|_{V_0}}_{\omega^2} (V_{ac} \cos \omega t)^2 + \dots$$

$$\frac{1}{2} \left. \frac{d^2 I}{dV^2} \right|_{V_0} V_{ac}^2$$



$$\cos^2 \theta = \frac{1}{2} (1 + \cos 2\theta)$$

$$+ \frac{1}{2} V_{ac}^2 \left. \frac{d^2 I}{dV^2} \right|_{V_0} \cos(2\omega t)$$

AM Radio Schematic

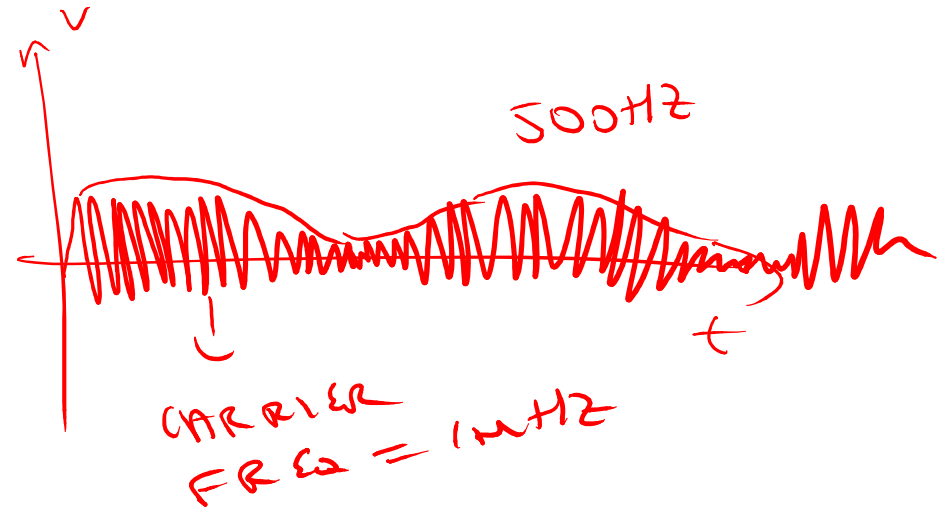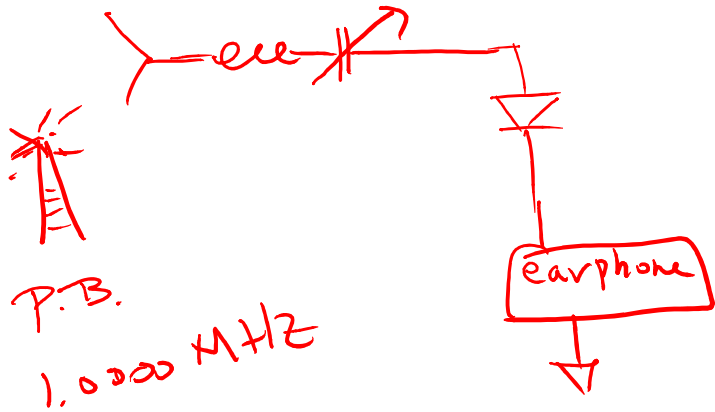

PIVDC BRIDGE

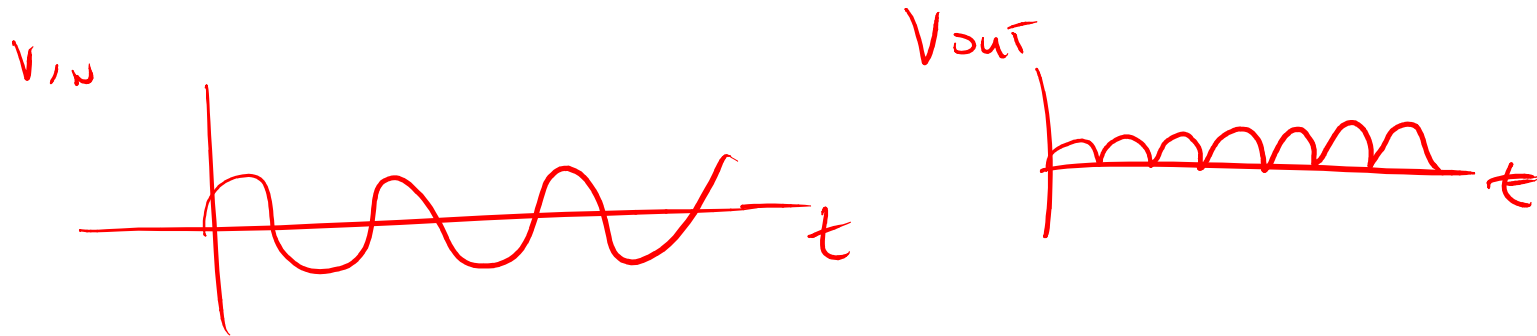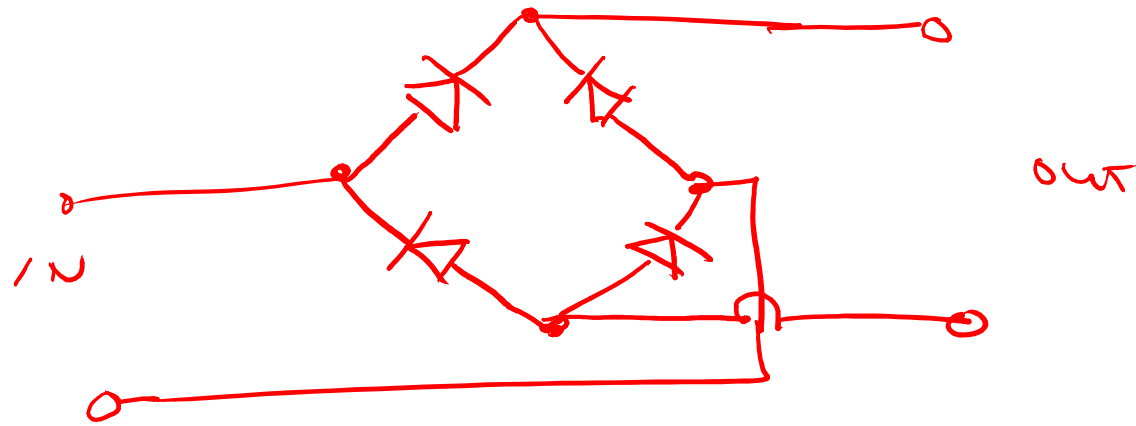


Power

$$P(t) = i(t) v(t)$$

$$v(t) = V_m \cos(\omega t + \theta_v)$$

$$i(t) = i_m \cos(\omega t + \theta_i)$$

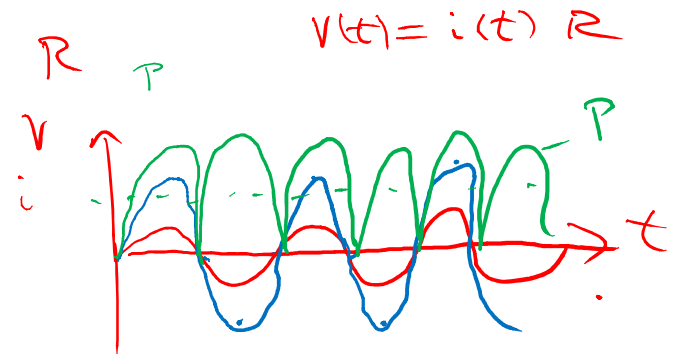

$$\begin{aligned} P(t) = i(t)v(t) &= V_m i_m \cos(\omega t + \theta_v) \cos(\omega t + \theta_i) \\ &= \frac{1}{2} V_m i_m \cos(\theta_v - \theta_i) \leftarrow \\ &\quad + \frac{1}{2} V_m i_m \cos(2\omega t + \theta_v + \theta_i) \end{aligned}$$

$$\langle P \rangle = \frac{1}{T} \int_0^T P(t) dt = \frac{1}{2} V_m i_m \cos(\theta_v - \theta_i)$$

$$\frac{1}{2} \bar{V} \bar{I}^* = \frac{1}{2} V_m i_m e^{j(\theta_v - \theta_i)}$$

$$\begin{aligned} \bar{V} &= V_m e^{j\theta_v} \\ \bar{I} &= i_m e^{j\theta_i} \end{aligned}$$

$$\begin{aligned} \operatorname{Re} \left[\frac{1}{2} \bar{V} \bar{I}^* \right] &= \frac{1}{2} V_m i_m \cos(\theta_v - \theta_i) \\ &= \langle P \rangle \end{aligned}$$

Case 1: Resistor

$$\vec{V} = \vec{I} z = \vec{I} R$$

$$\langle P \rangle = \frac{1}{2} \operatorname{Re} \left[\vec{I} R \vec{I}^* \right] = \frac{1}{2} R \operatorname{Re} \left[\vec{I} \vec{I}^* \right] \\ = \frac{1}{2} R |\vec{I}|^2$$

$$u = a + jb \quad u^* = a - jb \\ u u^* = a^2 + b^2 = |u|^2$$

$$\langle P \rangle = \frac{1}{T} \int_0^T v_m \cos(\omega t + \theta_v) \cos(\omega t + \theta_i) dt \\ = \frac{1}{T} v_m i_m \underbrace{\int_0^T \cos^2(\omega t) dt}_{\frac{1}{2}} \\ = \frac{1}{2} v_m i_m$$

Case 2: Capacitor

$$\mathbf{I} \mathbf{I}^* = |\mathbf{I}|^2$$

$$\mathbf{V} = \mathbf{I} z = \mathbf{I} \frac{1}{j\omega c}$$

$$\langle P \rangle = \frac{1}{2} \operatorname{Re}[\mathbf{V} \mathbf{I}^*] = \frac{1}{2} \operatorname{Re}\left[\mathbf{I} \frac{1}{j\omega c} \mathbf{I}^*\right]$$


$$= \frac{1}{2} \operatorname{Re}\left[|\mathbf{I}|^2 \frac{1}{j\omega c}\right] = \frac{1}{2} |\mathbf{I}|^2 \operatorname{Re}\left[\frac{1}{j\omega c}\right] = 0$$

$$\frac{1}{j\omega c} = -j \frac{1}{\omega c} = 0 + \left(-\frac{1}{\omega c}\right)j$$

$$\mathbf{V} = \mathbf{I} j\omega L$$

$$\langle P \rangle = \frac{1}{2} \operatorname{Re}\left[\mathbf{I} j\omega L \mathbf{I}^*\right] = \frac{1}{2} |\mathbf{I}|^2 \operatorname{Re}[j\omega L] = 0$$

Maximum Power Transfer

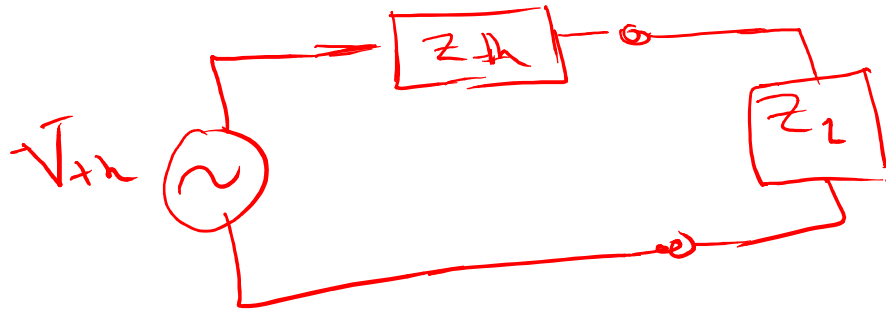

$$Z_{th} = R_{th} + jX_{th}$$

$$Z_L = R_L + jX_L$$

$$P = \frac{1}{2} \operatorname{Re} [V_L \dot{I}_L^*] =$$

$$V_L = \frac{Z_L}{Z_{th} + Z_L} V_{th}$$

$$\dot{I}_L = \frac{V_{th}}{Z_{th} + Z_L}$$

$$P = \frac{1}{2} |V_{th}|^2 \frac{R_L}{(R_{th} + R_L)^2 + (X_{th} + X_L)^2}$$


max $X_{th} = -X_L \quad R_{th} = R_L$

$$Z_L = Z_{th}^*$$

Digital Circuits

0 1

pMOS

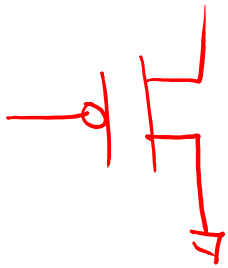

nMOS



AND
NOR
NOT
INVERTER


$V_g = 0$ SHORT

$V_g = V_{dd}$ OPEN


$V_g = 0$ OPEN

$V_g = V_{dd}$ SHORT


CMOS inverter

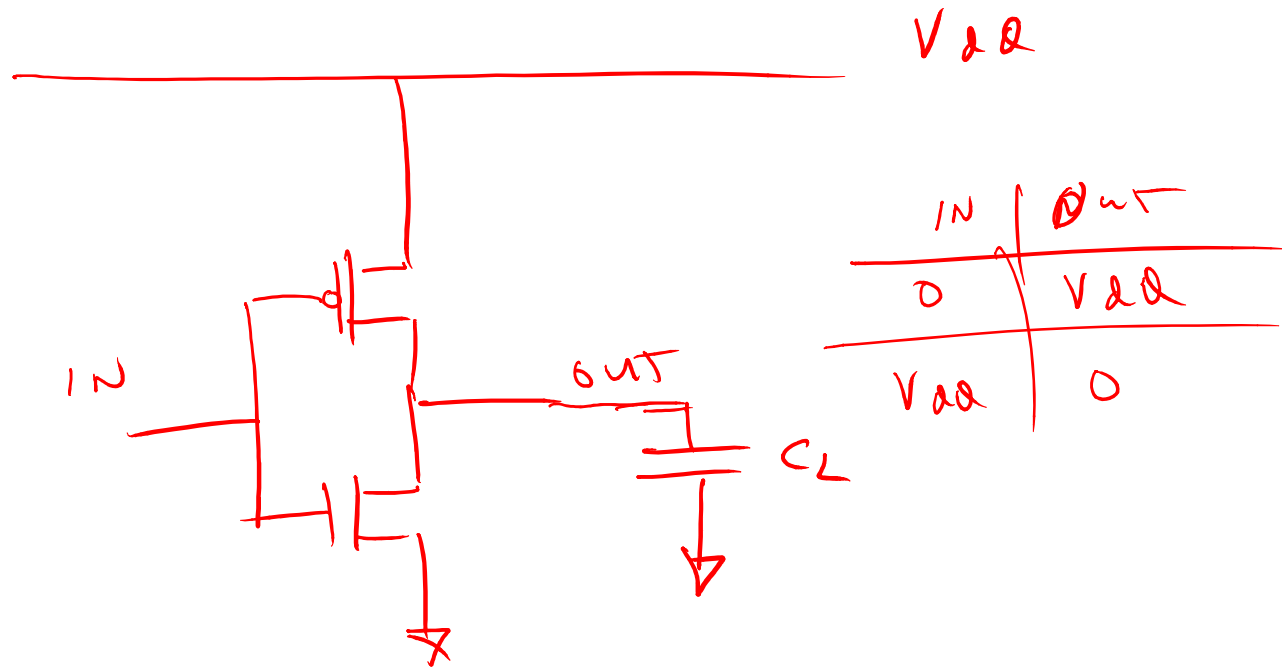

Dynamic power

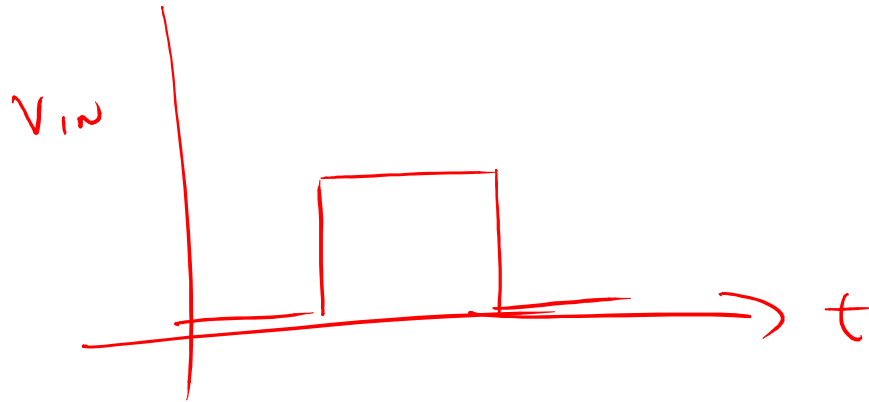
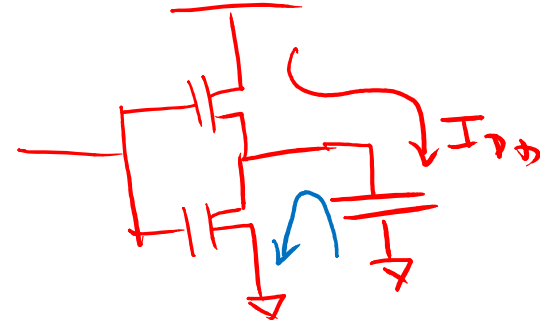
$$P_{DYN} = \frac{1}{2} C V_{DD}^2 F_{clk}$$



$$\frac{1}{2} C_{Load} V_{DD}^2$$

ENERGY COST
TO FLIP BIT