

EECS 70A: Network Analysis

Midterm review



Topics covered

- KCL, KVL
- Nodal analysis
- Mesh analysis
- Thevenin/Norton theorem


Nodal Analysis(Review)

Based on KCL, use node voltages as circuits variables.

1. Define a reference node.
2. Label remaining nodes. (n-1 nodes)
3. Apply KCL + ohm to all nodes and supernodes (e.g. V_1, V_2, V_3, \dots)
Express all i's in terms of v's
4. Apply KVL to the voltage source
If one end of voltage source connected to ground, don't need to
5. Solve the n-1 simultaneous equations, to find V's
6. Use Ohm's law to find the currents.

“Supernode”

A node with a voltage source in it...

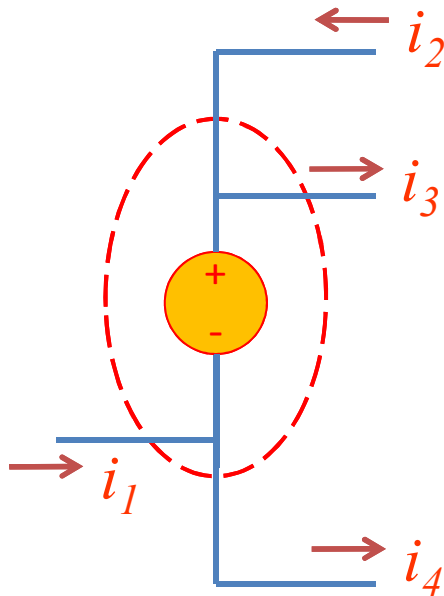


KCL: IN=OUT

$$i_1 + i_2 = i_3 + i_4$$

Must define a supernode if a voltage source appears when doing nodal analysis...
(unless one end of voltage source connected to reference node)

1. Define a reference node.
2. Label remaining nodes.
3. Apply KCL + ohm to all nodes **and supernodes**
4. **Apply KVL to loop with voltage source**

Nodal Analysis Example

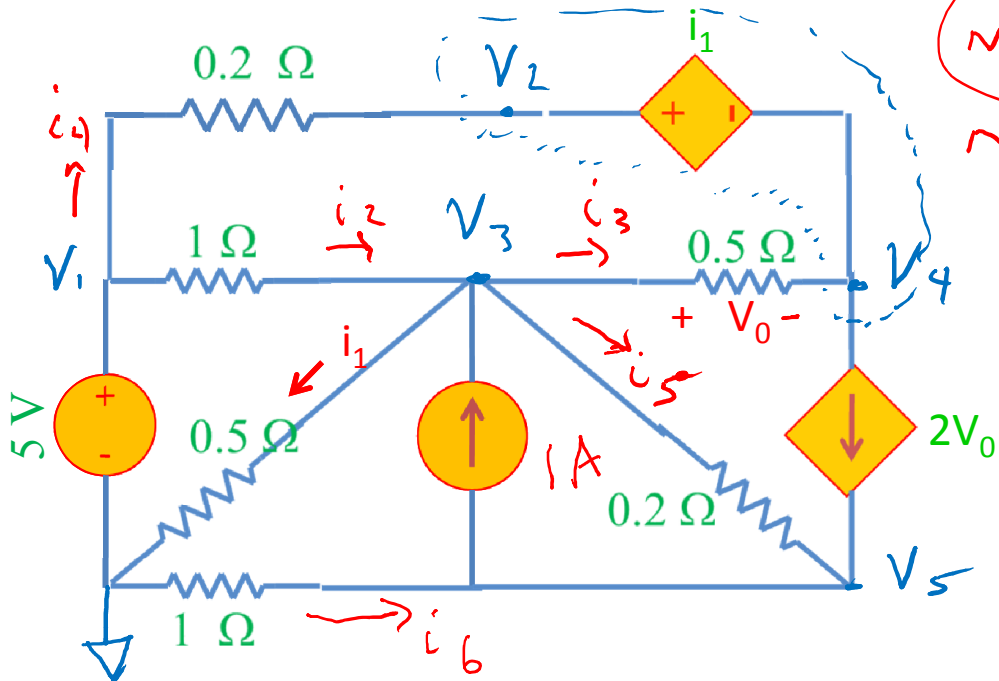

N1: $V_1 = 5V$

N2:

N3: $1N = out$

$i_2 + 1A$

$= i_3 + i_1 + i_5$

$$\frac{V_1 - V_3}{1} + 1A = \frac{V_3 - V_4}{0.5} + \frac{V_3 - 0}{0.5} + \frac{V_3 - V_5}{0.2}$$

N4


N5: $1N = out$

$$2V_0 + \frac{V_3 - V_5}{0.2} + \frac{0 - V_5}{1} = 1A$$

$$\frac{V_1 - V_2}{0.2} + \frac{V_3 - V_4}{0.5} = 2(V_3 - V_4)$$

SN: $i_4 + i_3 = 2V_0$

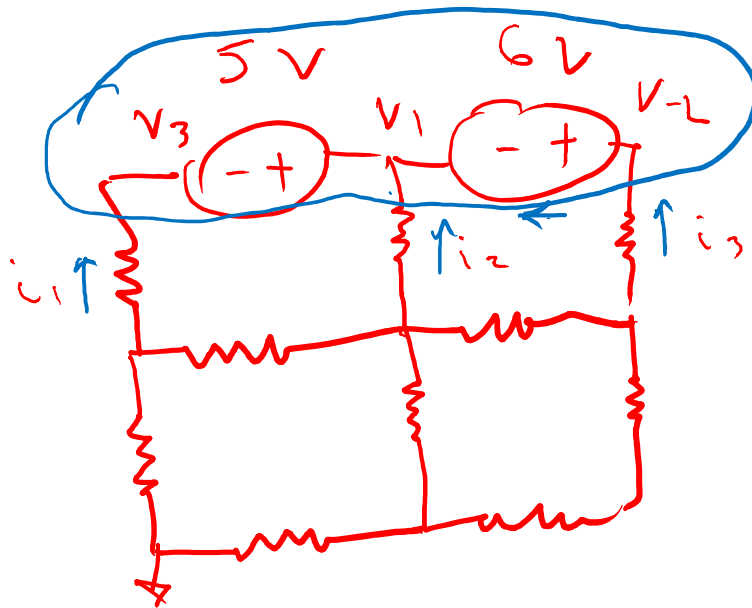KVL @ V_{source} $V_2 - V_4 = i_1 = \frac{V_3 - 0}{0.5}$





$$1N = 0uT$$

$$V_1 - V_3 = 5$$

$$V_2 - V_1 = 6V$$

$$V_2 - V_3 = 5 + 6V$$

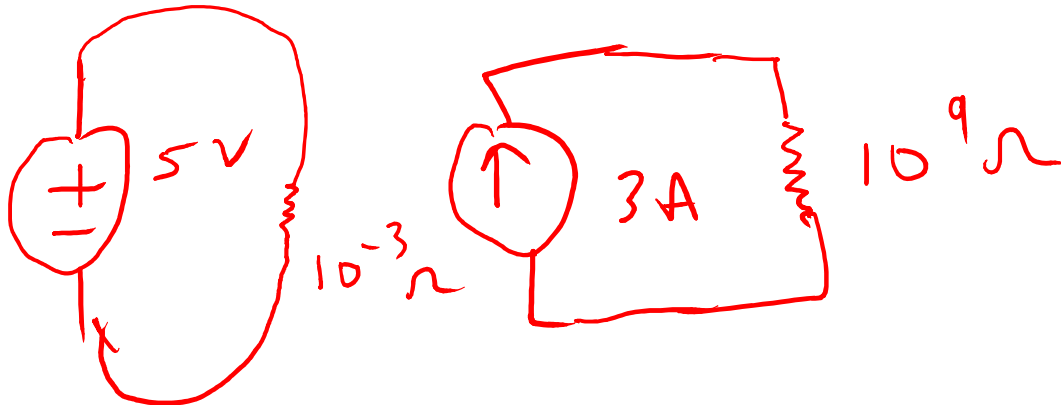

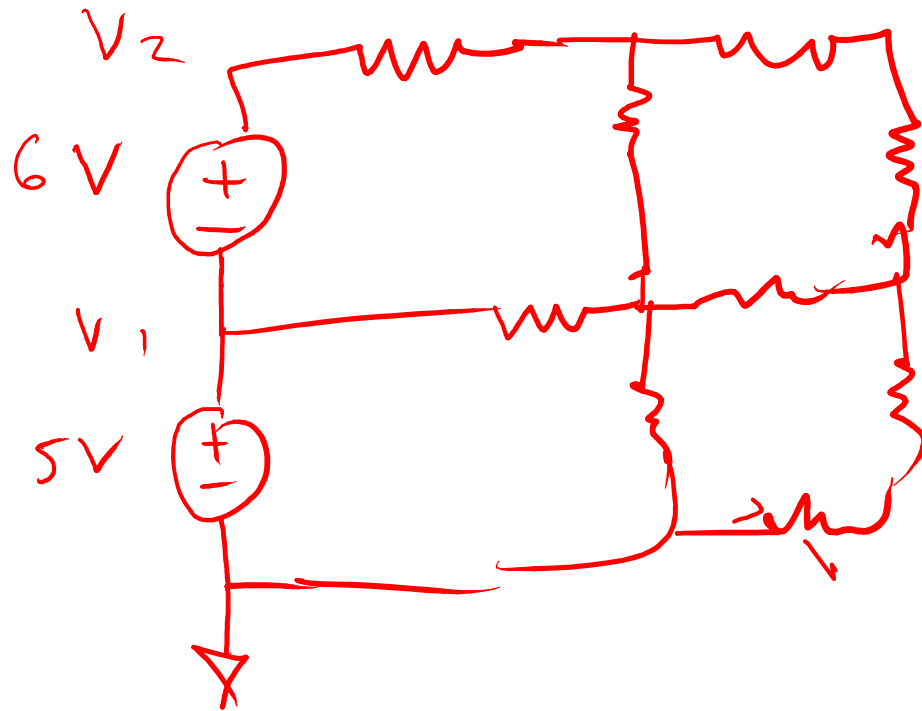


$$v_1 = 5V$$

$$v_2 = 11V$$

$$v_2 - v_1 = 6V$$


Nodal analysis example

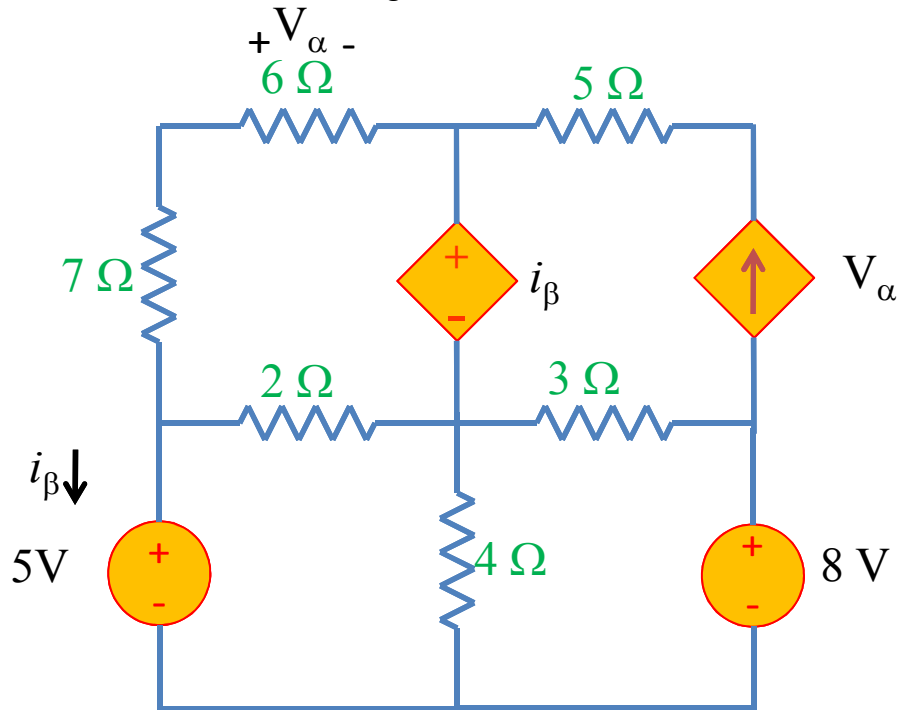Find the currents and voltages in this circuit:



Nodal analysis example

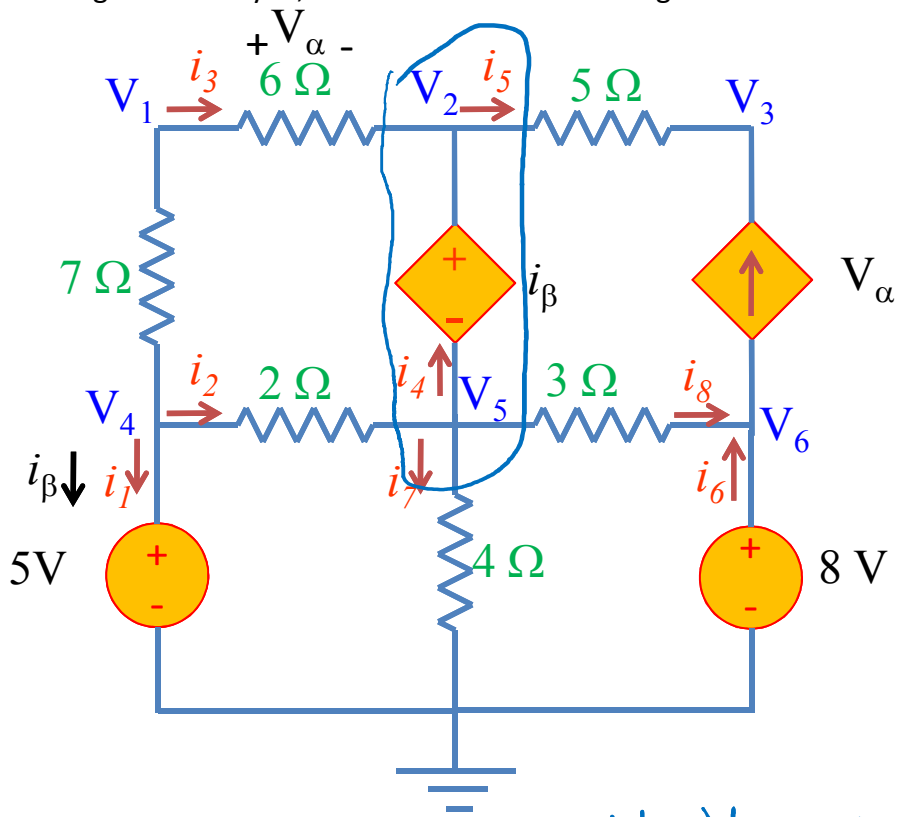Using nodal analysis, find the currents and voltages in this circuit:



N1: $i_N = \text{out}$ $i_3 = i_3$
 $\frac{V_4 - V_1}{7} = \frac{V_1 - V_2}{6}$

N2: $i_N = 0$

N3: $i_N = \text{out}$ $i_5 + V_2 = 0$
 $\frac{V_2 - V_3}{5} + V_1 - V_2 = 0$

N4: $V_4 = 5$ (voltage)

N5: $i_N = 0$

N6: $V_6 = 8$

SN: $i_N = \text{out}$ $i_3 + i_2 = i_5 + i_8 + i_7$

$$\frac{V_1 - V_2}{6} + \frac{V_4 - V_5}{2} = \frac{V_2 - V_3}{5} + \frac{V_5 - V_6}{3} + \frac{V_5 - 0}{4}$$

KVL @ $V_{\text{source } \beta}$:

$$\boxed{V_2 - V_5 = i_\beta} = -i_2 - i_3 = -\left(\frac{V_4 - V_5}{2}\right) - \left(\frac{V_4 - V_1}{7}\right)$$

$$\begin{array}{cccccccc}
 & \text{---} & V_1 & + & \text{---} & V_2 & + & \text{---} & V_3 & + & \text{---} & V_4 & + & \text{---} & V_5 & + & \text{---} & V_6 & = & \text{---} \\
 N1 & -\frac{1}{7} & + & \frac{1}{6} & & -\frac{1}{6} & & & 0 & & & \frac{1}{7} & & & 0 & & & 0 & = & 0
 \end{array}$$

N3

N4

N6

SN

KVL@
SN

6x6 solve $v_1 - v_6$.
then solve $i_1 - i_2$


Mesh analysis summary

Based on KVL, use mesh currents as circuit variables.

1. Assign mesh currents i_1, i_2, \dots, i_n
2. Apply KVL + Ohm's law to each mesh
3. Supermesh (if there is a current source present):
 - CASE 1: current source only in one mesh.
 - Already have the current for that mesh => no need to write KVL for that mesh
 - CASE 2: current source exists between two meshes. => create a supermesh
 - Apply KVL to the supermesh
 - Apply KCL to a node in the branch where two meshes intersect
1. Solve the equations for i_1, i_2, \dots, i_n
(e.g. using Kramer's rule)
2. Then solve for voltages using Ohm's law

Mesh Analysis-Introduction


What is a Mesh?

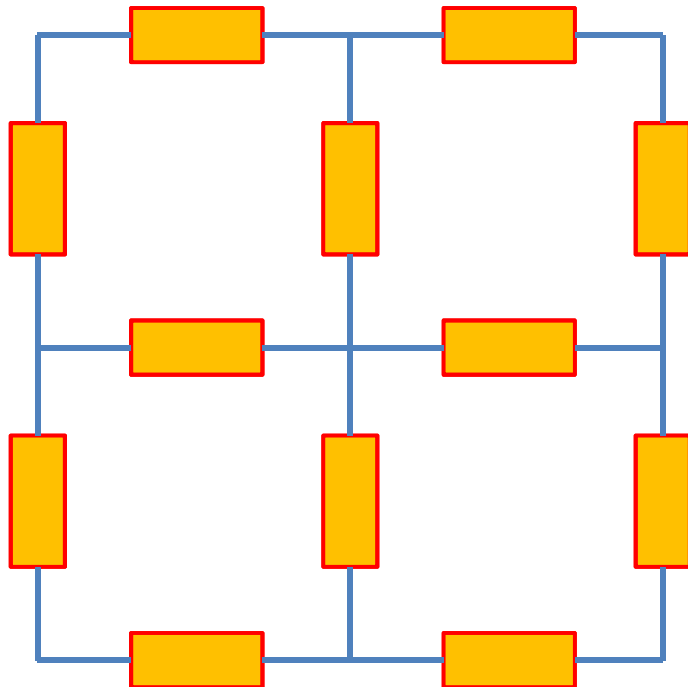

- A loop is a closed path with no node passed more than once.
- A mesh is a loop that does not contain any other loops within it.

Mesh Analysis-Introduction

Mesh Current vs. Element Current

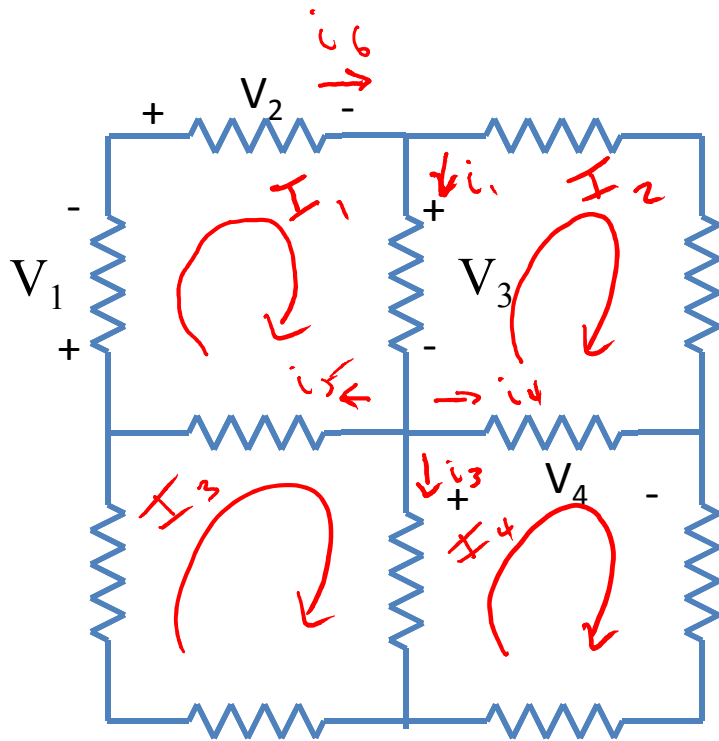

- The current through a mesh is known as mesh current.
- Direction of the mesh current is arbitrary-conventionally assumed to be clockwise.
- The current through an element can be the same as mesh current or the subtraction of two mesh currents.


$$i_1 = I_1 - I_2$$

$$i_4 = I_4 - I_2$$

$$i_6 = I_1$$

Mesh analysis example

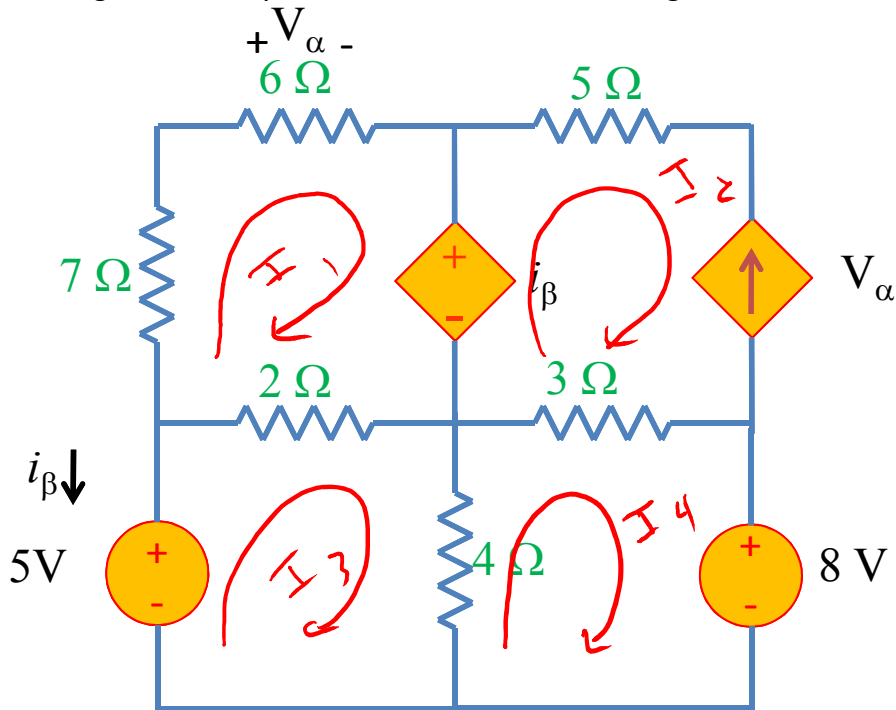Using mesh analysis, find the currents and voltages in this circuit:



$$M1 \quad I_1 \cdot 7\Omega + I_1 \cdot 6 + i_\beta + (I_1 - I_3) \cdot 2 - I_2$$

$$M2 \quad \text{SM BUT LUCKY}$$

$$I_2 = -V_\alpha \quad (\text{FRICK})$$


$$= -(I_1 \cdot 6)$$

$$M3 \quad -5 + 2(I_3 - I_1) + 4(I_3 - I_4) = 0$$

$$M4 \quad (I_4 - I_3) \cdot 4 + 3(I_4 - I_2) + 8 = 0$$

4 EQ 4 unknowns
Find I_1, I_2, I_3, I_4

Thevenin, Norton Theorems:

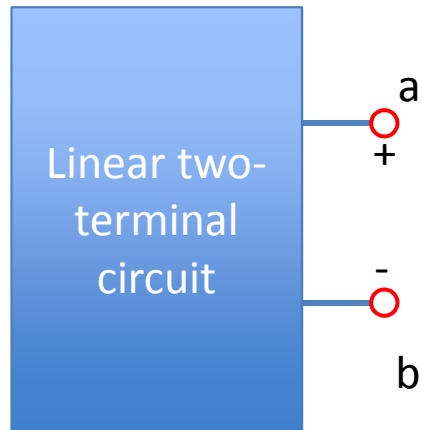

Thevenin:

1. **Calculating V_{th} :**
Connect nothing to a-b. Calculate voltage. This is V_{th} .

2. **Calculating R_{th} :**

Method 1:

Connect terminal a to b (short).

Calculate the current from a to b. This is call $I_{short\ circuit}$.

$$R_{th} = V_{th} / I_{short\ circuit}$$

Method 2:

Find the input resistance looking into terminals a-b after all the independent sources have been turned off.


(Voltage sources become shorts, current sources become opens.)

Trick (if dependent sources present):


Apply a 1 A current source to terminals a-b, find V_{ab}

$$R_{th} = V_{ab} / 1A.$$

Equivalent to:

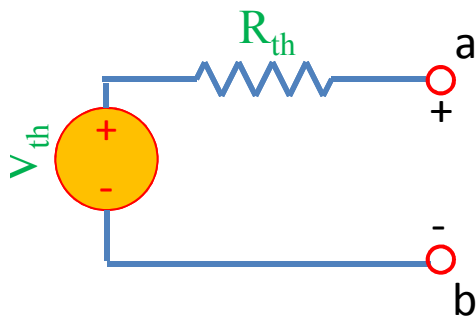

Equivalent to:

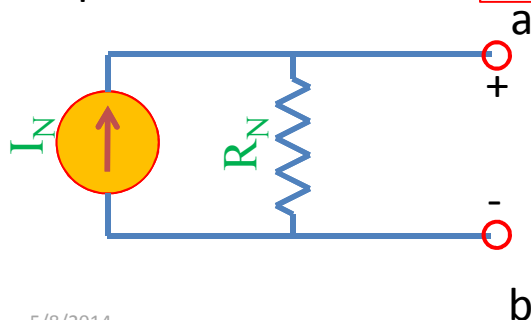

Norton:

1. **Calculating R_N :**
 $R_N = R_{th}$ (same method as 2 above)

2. **Calculating I_N :**


$$I_N = V_{th} / R_{th}$$

OR:

$$I_N = I_{short\ circuit}$$

Find the Thevenin & Norton equivalent circuit of the circuit below with respect to terminals a and b:

Example problem

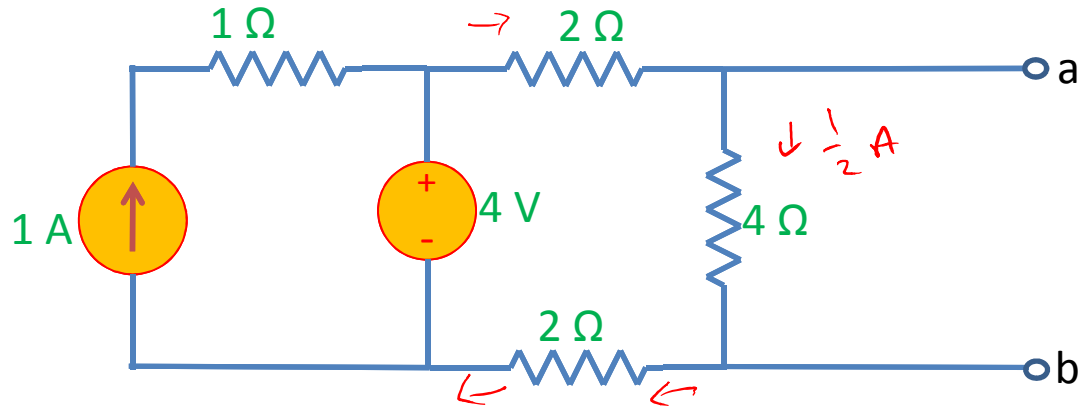

$$V_{ab} = 2\text{V} \\ = V_{th}$$

