


## Announcements:

1. Midterm solutions poster
  - A. Error needs to be corrected
2. Quiz due next Monday
3. HW due in 2 weeks
  - A. Only 1 HW between now and next midterm

# EECS 70A: Network Analysis


## Lecture 5

# Nodal analysis example

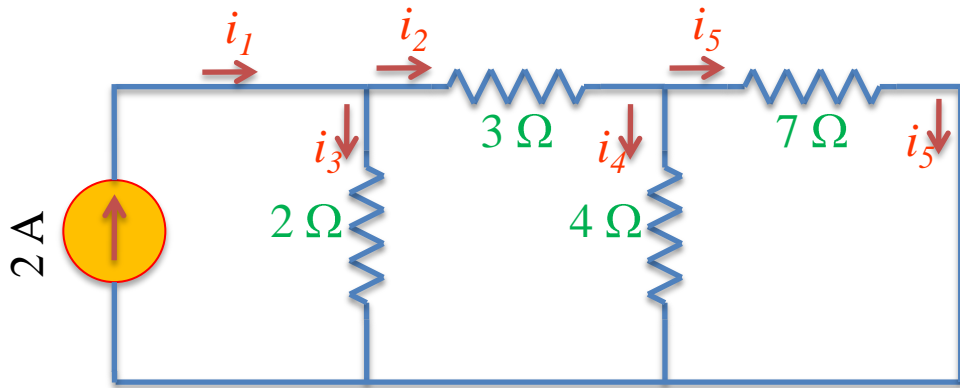

Computer crashed during lecture so notes from 2010 example attached. Replay recording has actual problems as solved in lecture.

# Nodal analysis example

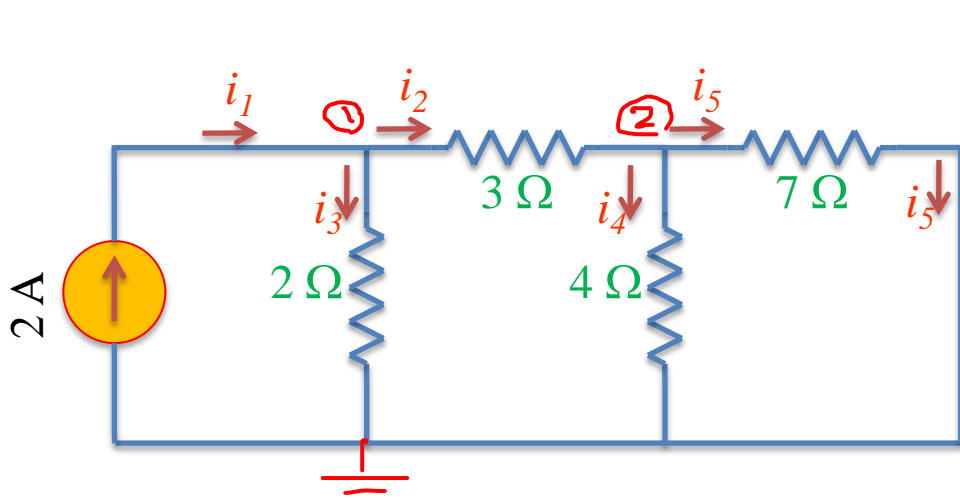

$$\textcircled{1} \quad -i_1 + i_3 + i_2 = 0$$

$$\star \quad 2A + \frac{V_1}{2\Omega} + \frac{V_1 - V_2}{3\Omega} = 0$$

$$\textcircled{2} \quad -i_2 + i_4 + i_5 = 0$$

$$\star \star \quad \frac{V_2 - V_1}{3\Omega} + \frac{V_2}{4\Omega} + \frac{V_2}{7\Omega} = 0$$

$$\star \rightarrow V_1 \left( \frac{1}{2} + \frac{1}{3} \right) - \frac{V_2}{3} = -2 \xrightarrow{\times 6} \begin{cases} 5V_1 - 2V_2 = -12 \\ -28V_1 + 61V_2 = 0 \end{cases}$$

$$\star \star \rightarrow \frac{-V_1}{3} + V_2 \left( \frac{1}{3} + \frac{1}{4} + \frac{1}{7} \right) = 0 \xrightarrow{\times 84} \begin{cases} 5V_1 - 2V_2 = -12 \\ -28V_1 + 61V_2 = 0 \end{cases}$$


$$V_1 = \frac{\Delta_1}{\Delta} = \frac{\begin{vmatrix} -12 & -2 \\ 0 & 61 \end{vmatrix}}{\begin{vmatrix} 5 & -2 \\ -28 & 61 \end{vmatrix}} = \frac{-12 \times 61 - 0}{5 \times 61 - (-2) \times (-28)} = \frac{732}{249} = 2.93 \text{ V}$$

$$V_2 = \frac{\Delta_2}{\Delta} = \frac{\begin{vmatrix} 5 & -2 \\ -28 & 0 \end{vmatrix}}{249} = \frac{0 - (-12) \times (-28)}{249} = 1.35 \text{ V}$$

$$i_3 = \frac{2.93 \text{ V}}{2\Omega}$$


$$i_2 = \frac{V_1 - V_2}{3\Omega} = 0.53 \text{ A}$$

# Nodal analysis example

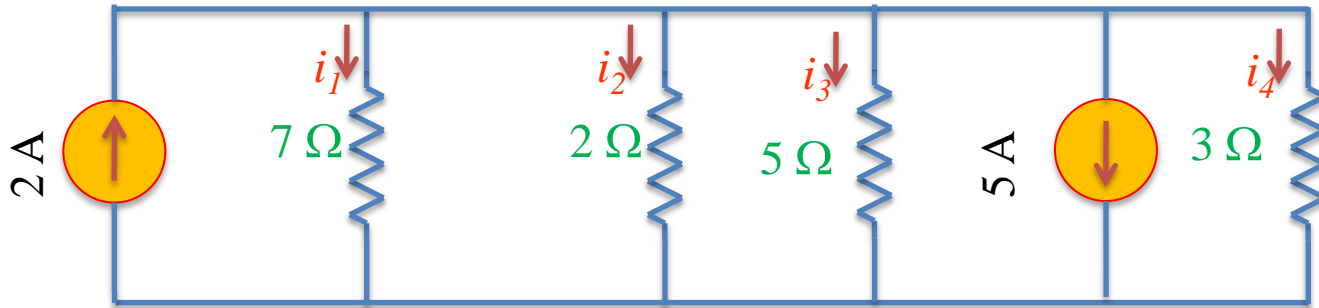

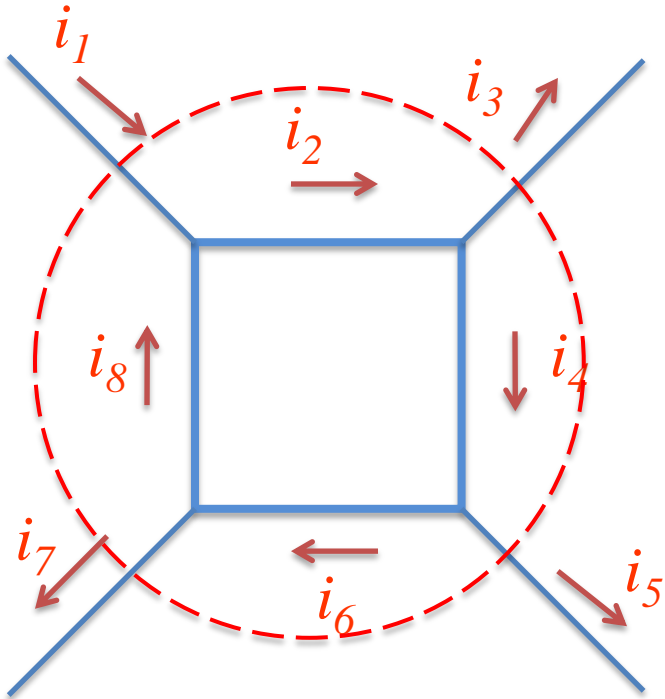
# KCL examples

From Lecture 3, Week 2: Find a relationship among  $i_1, i_2, i_3, i_4, \dots$



# “Supernode”

A node with a voltage source in it...

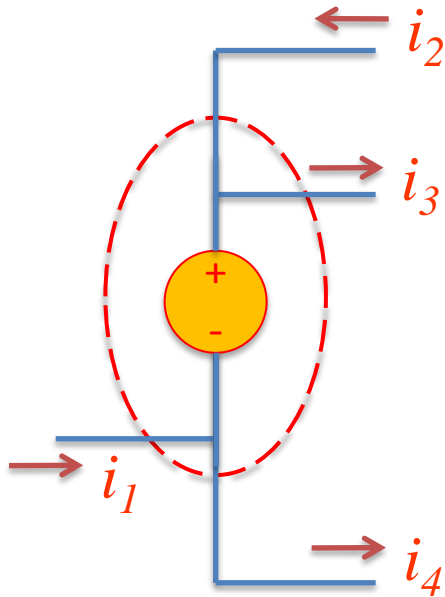


KCL:

*Must* define a supernode if a voltage source appears when doing nodal analysis...  
(unless one end of voltage source connected to reference node)

1. Define a reference node.
2. Label remaining nodes.
3. Apply KCL + ohm to all nodes **and supernodes**
4. **Apply KVL to loop with voltage source**

# Example nodal w/voltage source

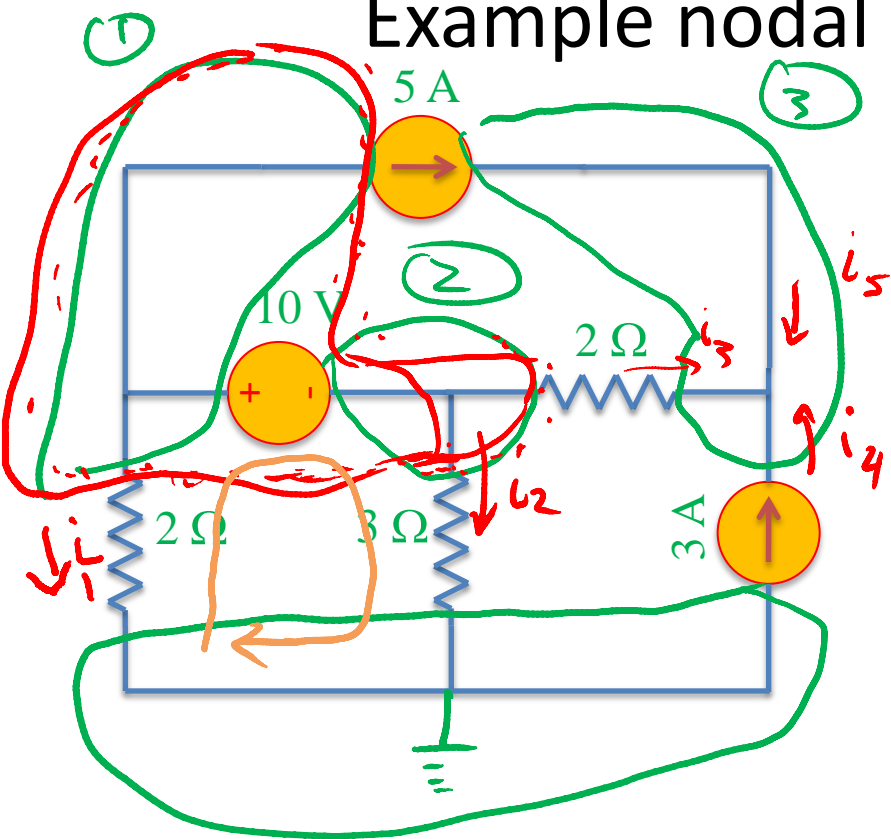

$$i_3 + i_4 + i_5 = 0$$

$$\frac{V_2 - V_3}{2\Omega} + 3A + 5A = 0$$

$$0 = 5A + i_3 + i_2 + i_1 = 0$$

$$= 5A + \frac{V_2 - V_3}{2\Omega} + \frac{V_2 + 0}{3\Omega} + \frac{V_1 + 0}{2\Omega}$$

KVL

$$-(V_1 + 0) + 10V + (V_2 + 0) = 0$$

- Announcements:
1. Announcements

# EECS 70A: Network Analysis

## Lecture 6




# Today's Agenda

- Review of Nodal Analysis
- Mesh Analysis
  - Introduction
    - What is a Mesh?
    - Mesh Current
  - Method
- Mesh Analysis with Current Source

# Mesh Analysis-Introduction


## What is a Mesh?

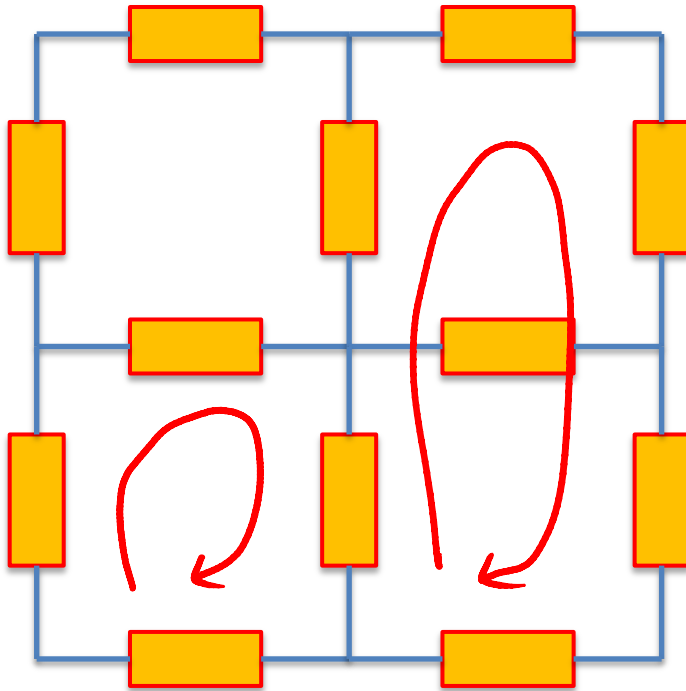

- A loop is a closed path with no node passed more than once.
- A mesh is a loop that does not contain any other loops within it.

# Mesh Analysis-Introduction

## Mesh Current vs. Element Current

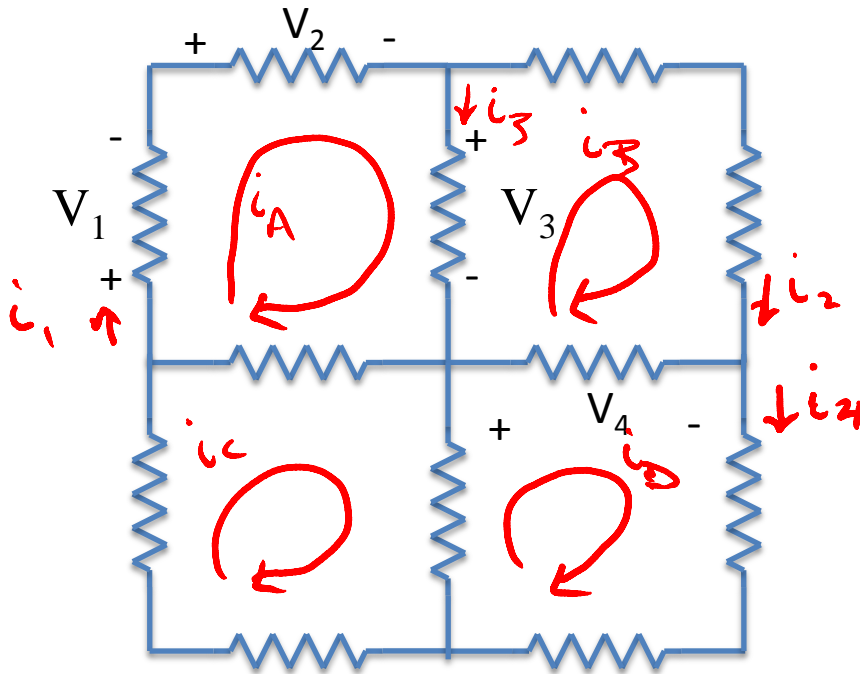

- The current through a mesh is known as mesh current.
- Direction of the mesh current is arbitrary-conventionally assumed to be clockwise.
- The current through an element can be the same as mesh current or the subtraction of two mesh currents.


$$i_A = i_1$$

$$i_3 = i_A - i_B$$

$$i_4 = i_D$$
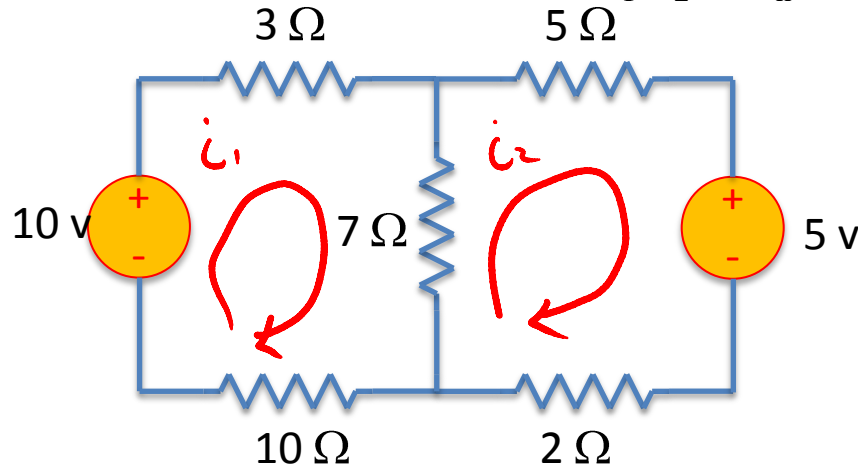
# Mesh Analysis-Method

- Assign mesh currents  $i_1, i_2, \dots, i_n$
- Apply KVL+ Ohm's law to each mesh
- Solve the equations for  $i_1, i_2, \dots, i_n$



$$-10 + (i_1)(3\Omega) + (i_1 - i_2)(7\Omega) + (i_1)(10\Omega) = 0$$

$$-(i_1 - i_2)(7\Omega) + (i_2)(5\Omega) + 5V + (i_2)(2\Omega) = 0$$

~~\*~~~~\*~~

# Mesh Analysis with Current Sources


- CASE 1: current source only in one mesh.

LUCK

already have the current for that mesh => no need to write

KVL for that mesh


$$i_2 = -5A$$

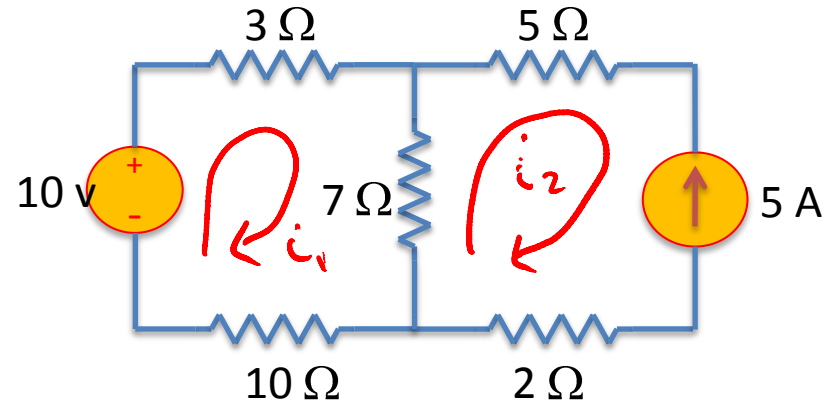
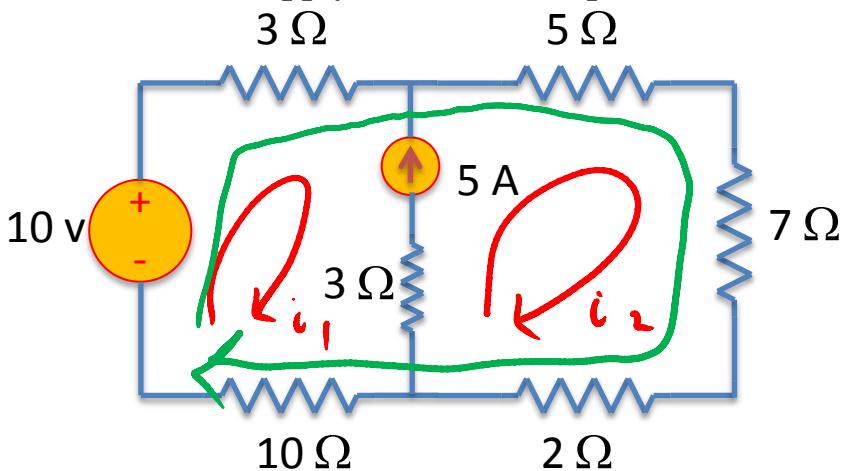
# Mesh Analysis with Current Sources

- CASE 2: current source exits between two meshes. => create a supermesh

- Apply KVL to the supermesh
- Apply KCL to the supermesh




$$-10V + (i_1)(3\Omega) + (i_2)(5\Omega) + i_2 7\Omega + i_2 2\Omega + i_1 10\Omega = 0$$

$$i_1 + 5A = i_2$$

(\*)

(\*) (\*)

# Mesh Analysis - Example

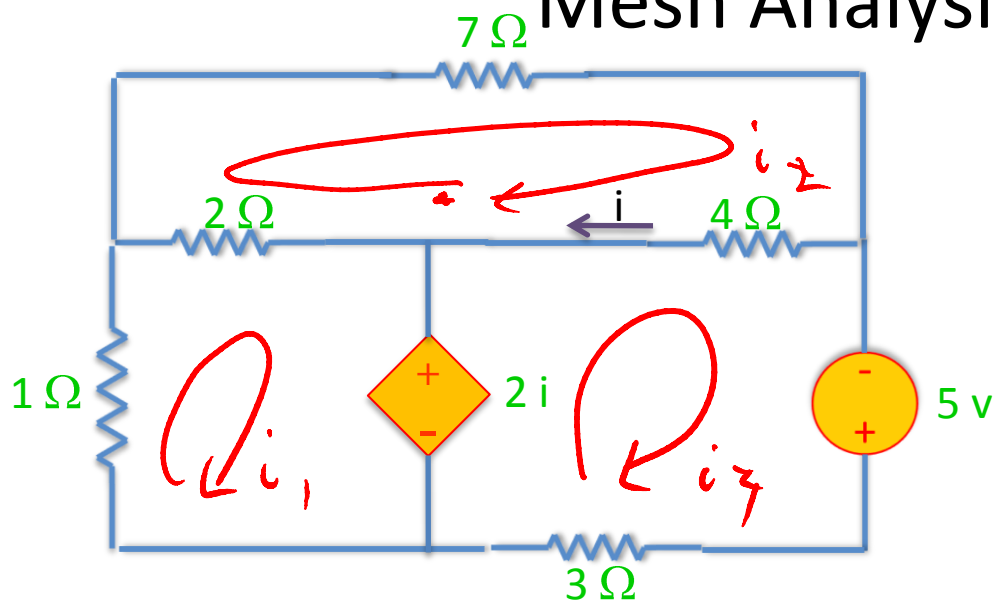

$$i_1 \cdot 1\Omega + (i_1 - i_2) \cdot 2\Omega + 2(i_2 - i_3) = 0$$

$$(i_2 - i_1) \cdot 2\Omega + i_2 \cdot 7\Omega + (i_2 - i_3) \cdot 4\Omega = 0$$

$$-(2i_1) + (i_3 - i_2) \cdot 4\Omega - 5V + i_3 \cdot 3\Omega = 0$$

(\*)

(\*) (\*)

(\*) (\*) (\*)