

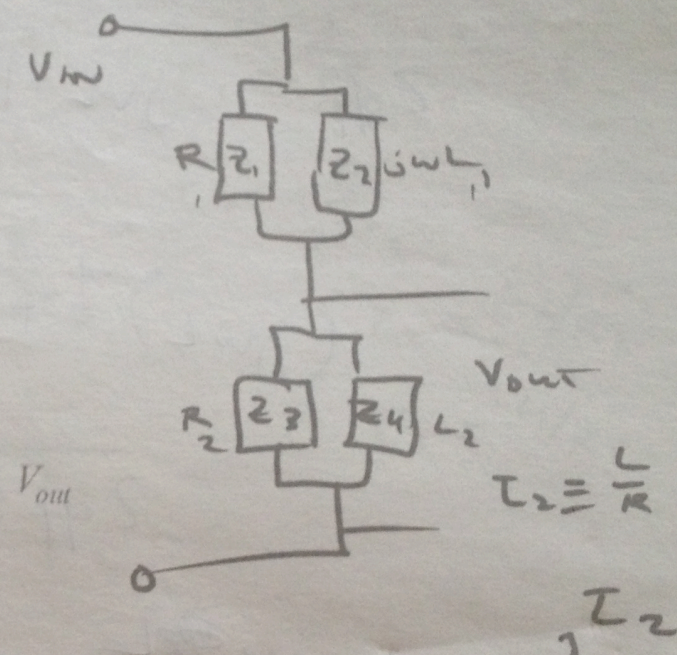


Example Transfer function

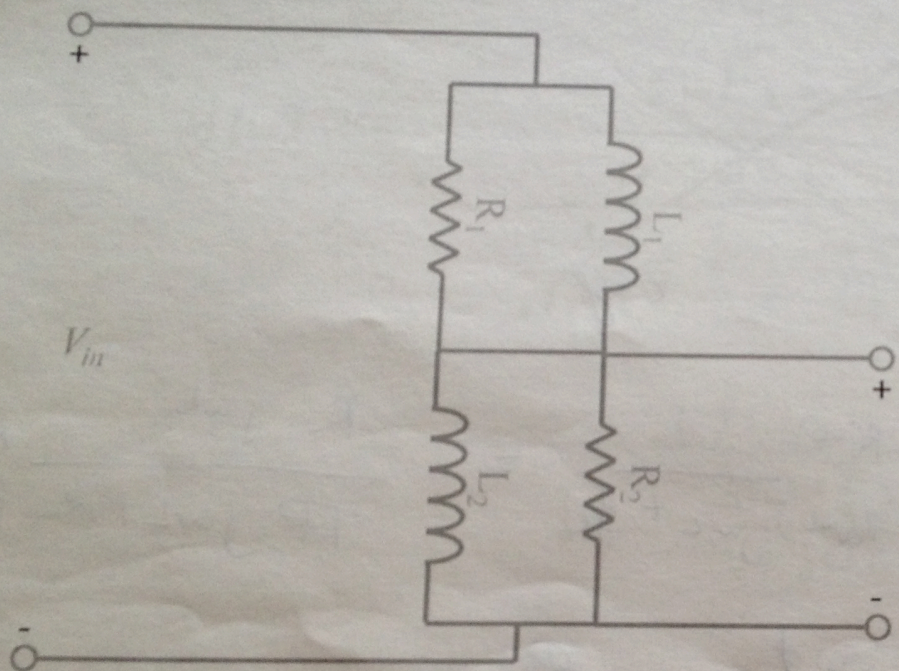

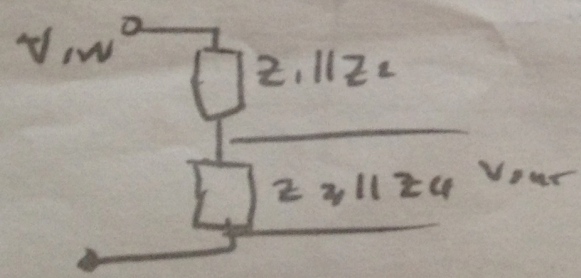Calculate $H(\omega)$ for this circuit. Sketch the magnitude of $H(\omega)$ vs. ω .



$$\frac{V_{out}}{V_{in}} = \frac{(Z_3 \parallel Z_4)}{(Z_3 \parallel Z_4) + (Z_1 \parallel Z_2)}$$

$$= H(\omega) = \frac{j\omega L_2}{1 + j\omega \tau_2} \cdot \frac{Z_1 \parallel Z_2 + \frac{j\omega L_1}{1 + j\omega \tau_2}}{Z_1 \parallel Z_2 + \frac{j\omega L_1}{1 + j\omega \tau_2}}$$

$$Z_{\text{eff}} = j\omega L \parallel R$$

$$(j\omega L)^{-1} + R^{-1} = Z_{\text{eff}}^{-1}$$

$$Z_{\text{eff}} = \frac{R(j\omega L)}{R(j\omega L) \frac{1}{j\omega L} + \frac{1}{R}} = \frac{R j\omega L}{\cancel{R} j\omega L + R \frac{1}{R}}$$

$$= \frac{j\omega \cancel{R} L}{j\omega \cancel{R} L + R \frac{1}{R}} = \frac{j\omega L}{1 + j\omega L/R}$$

R || L

$$\frac{Ls}{1 + j\omega\tau}$$

$$\tau \equiv \frac{L}{R}$$

$$H(\omega) =$$

$$\frac{j\omega L_2}{1 + j\omega\tau_2} + \frac{j\omega L_1}{1 + j\omega\tau_1}$$

$$\tau_1 = \frac{L_1}{R_1}$$

$$\tau_2 = \frac{L_2}{R_2}$$

$$\tau_2 = L_2/R_2$$

$$\tau_1 = L_1/R_1$$

$$= \frac{1}{1 + \frac{1 + j\omega\tau_2}{1 + j\omega\tau_1} \frac{L_1}{L_2}}$$

