


EECS 70A:
Network Analysis Homework #2

The homework is due Thursday 4/16/2014 before 6 pm.


You can choose either way to turn in your homework

- 1) Turn it in during any of the discussions (Highly recommended)
- 2) Turn it in during office hour EH 3404 (Thursday 4:00 - 6:00pm)
- 3) EEE Dropbox


Problem 1: (VCCS) Find i_1 . Is current flowing from b to c or from c to b?

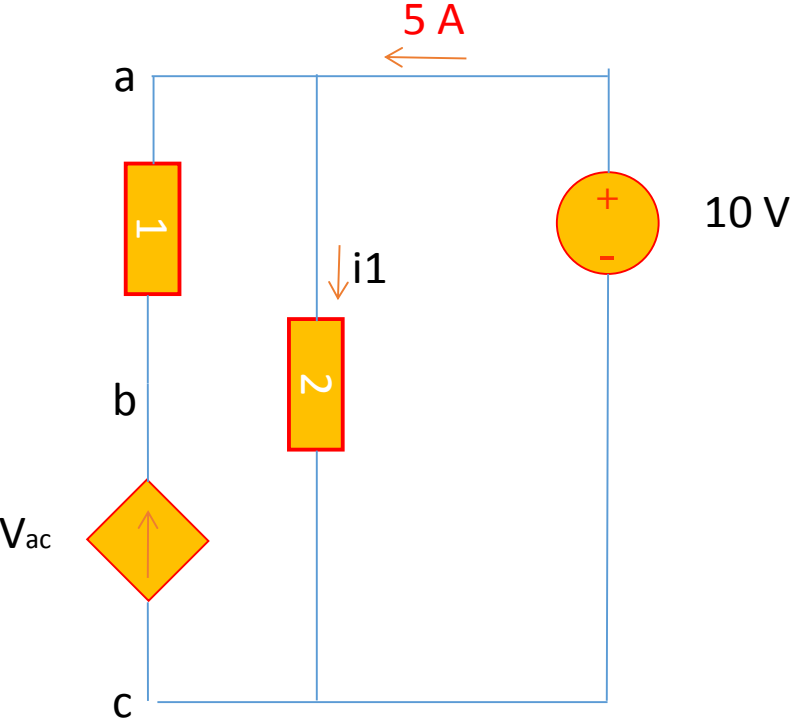


Problem 2 : (CCVS) Find i_1 , i_2 . Find V_{bc}

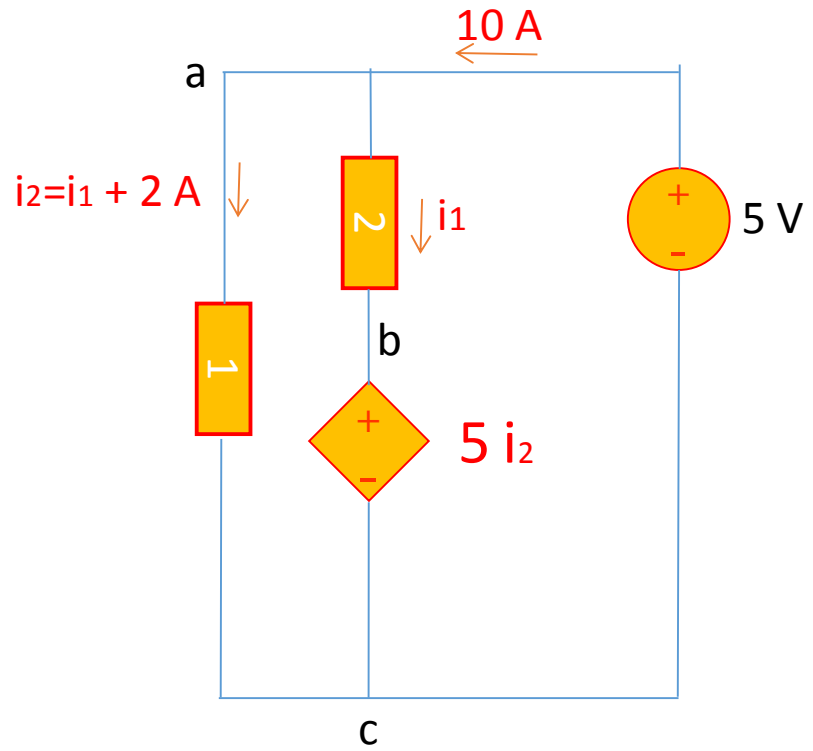


Problem 3: (VCVS) Find V_{bc} , i_1 .

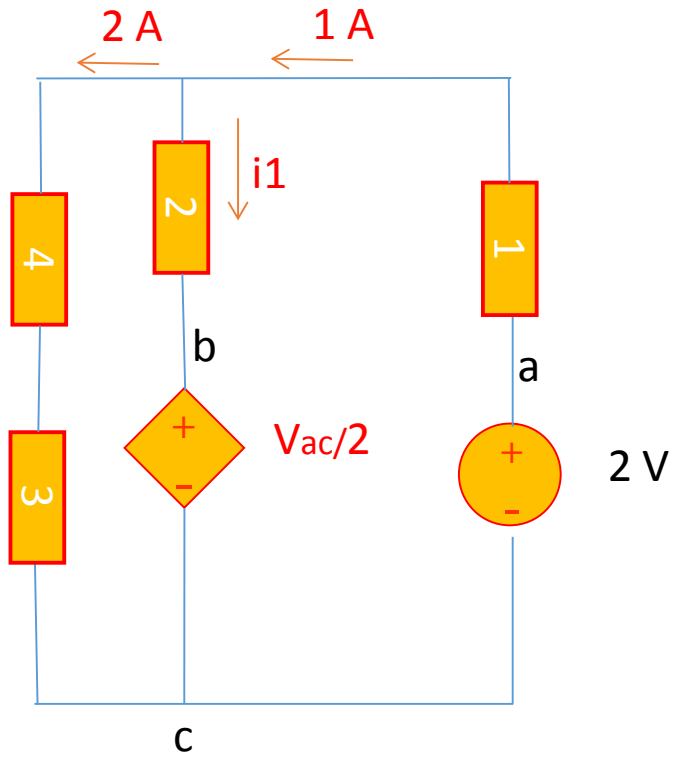


Problem 4: Solve for Req. You may use the parallel notation discussed in class

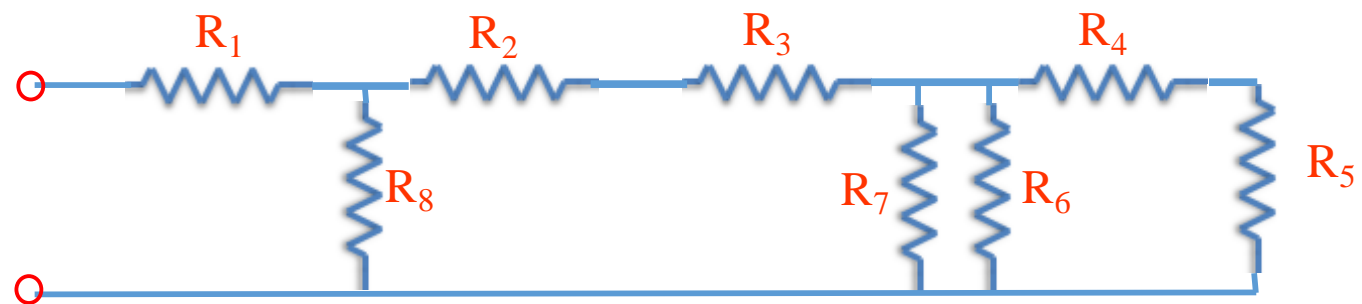

Problem 5: Solve for Req. You may use the parallel notation discussed in class.

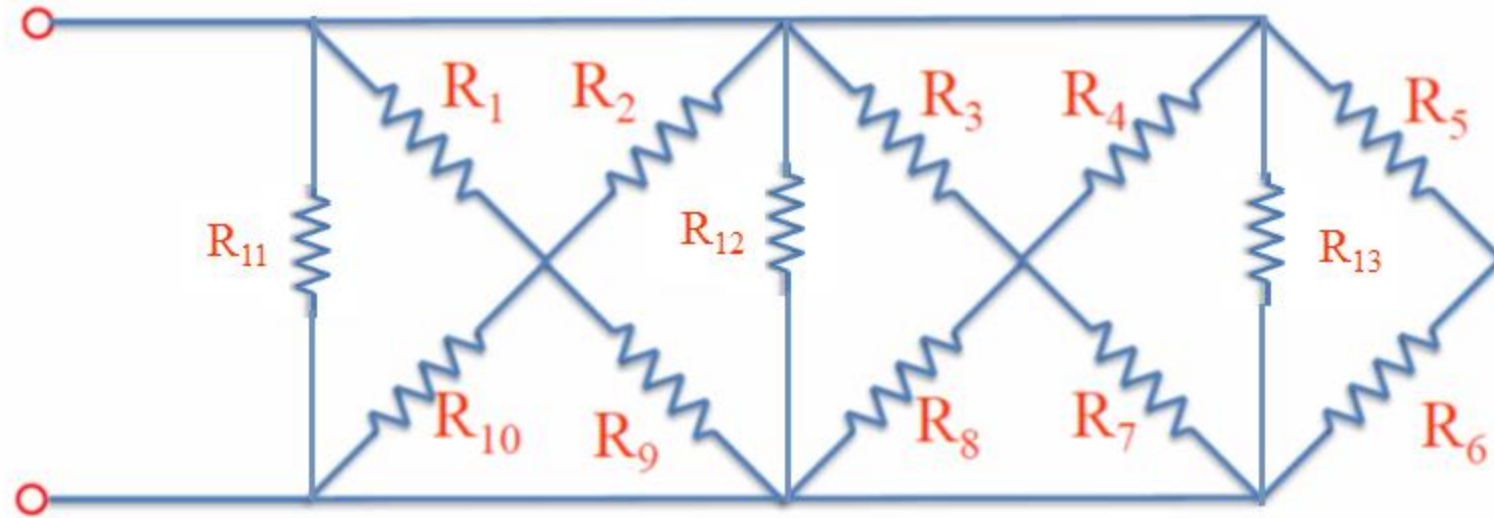


Problem 6: Solve for Req. Each resistor is R_0 ohms.

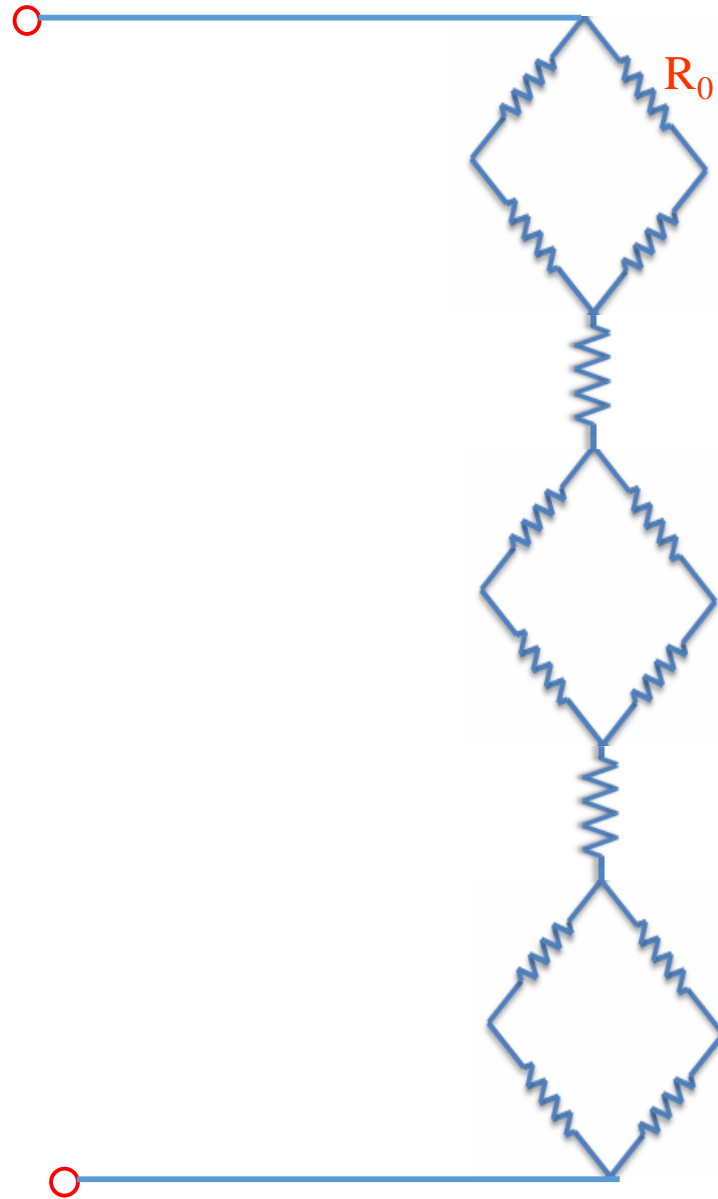


Problem 7: Potentiometer.

In the circuit below, the wiper divides the potentiometer resistance between $2(1 - \alpha)R_2$ and $2\alpha R_2$, where $0 < \alpha < 1$. Find the ratio of the power dissipated in R_1 to the power supplied by the voltage source (P_1/P_s) as a function of α .

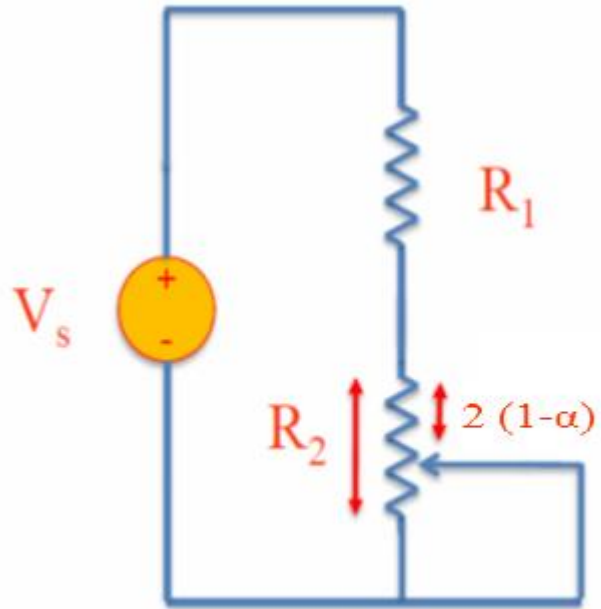


Problem 8: KVL & Ohm law. Find V_1 , V_2 and V_3 and the current flowing in the circuit below

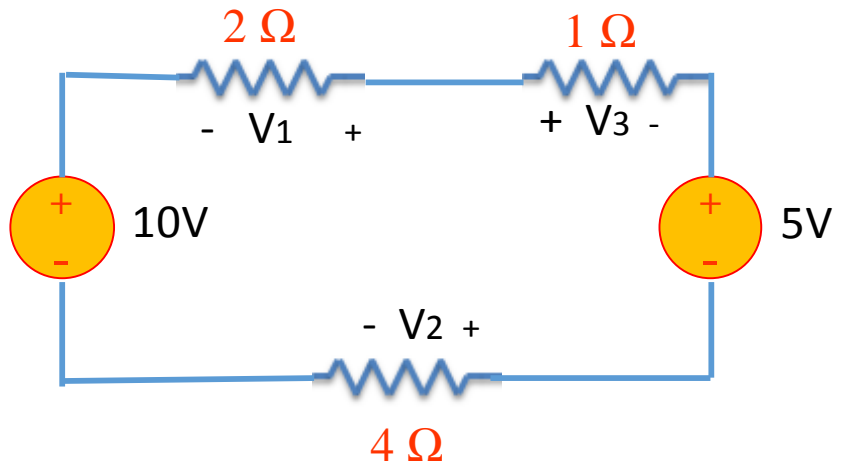

Problem 9: KVL, KCL & Ohm Law .

Find i_1 through i_3 in the circuit below.

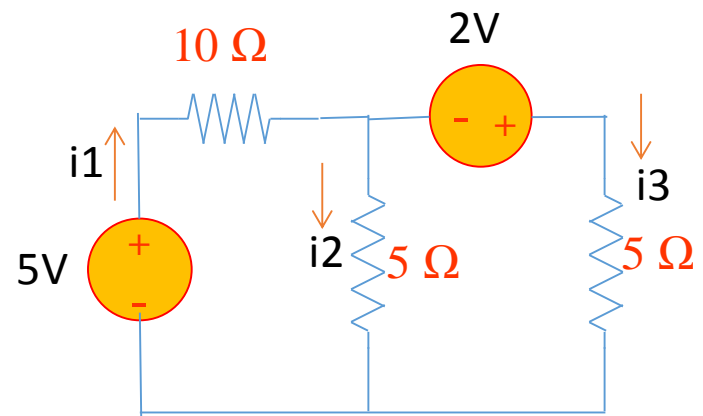

Problem 10: KVL, KCL & Ohm Law.

Find V_1 through V_4 and i_1 through i_3 in the circuit below.

