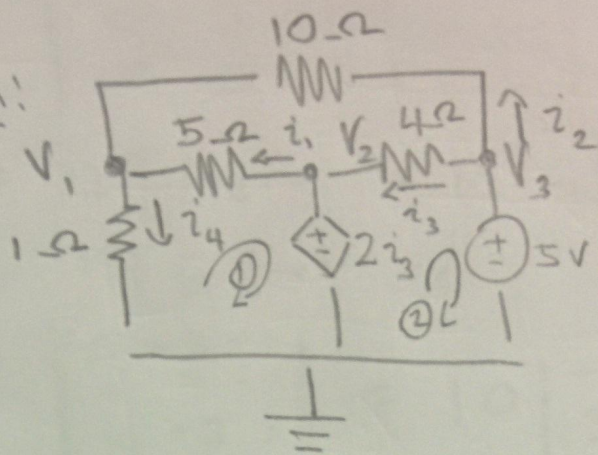


1) Given:



Determine: All node voltages

Solve:

$$\text{Node } i_1 + i_2 = i_4 \Rightarrow \frac{V_2 - V_1}{5} + \frac{V_3 - V_1}{10} = \frac{V_1}{1}$$

$$2V_2 - 2V_1 + V_3 - V_1 = 10V_1$$

$$13V_1 - 2V_2 - V_3 = 0$$

Loop ①

$$-i_4 - 5i_1 + 2i_3 = 0$$

$$-\frac{V_1}{1} - 5\left(\frac{V_2 - V_1}{5}\right) + 2\left(\frac{V_3 - V_2}{4}\right) = 0$$

$$-2V_1 - 2V_2 + 2V_1 + V_3 - V_2 = 0$$

$$0V_1 + 3V_2 - V_3 = 0$$

Loop ②

$$-2i_3 - 4i_3 + 5 = 0$$

$$3 \times \left[\frac{V_3 - V_2}{4} \right] = 5$$

$$0V_1 + 3V_3 - 3V_2 = 10$$

$$\begin{bmatrix} 13 & -2 & -1 \\ 0 & 3 & -1 \\ 0 & -3 & 3 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 10 \\ 0 \\ 10 \end{bmatrix}$$

$$D = \begin{vmatrix} 13 & -2 & -1 \\ 0 & 3 & -1 \\ 0 & -3 & 3 \end{vmatrix} = 13 \begin{vmatrix} 3 & -1 \\ -3 & 3 \end{vmatrix} + 0 + 0$$

$$= 13 [(3 \cdot 3) - (-3 \cdot -1)] = 13 [9 - 3]$$

$$= 13 [6] = 78$$

$$A = \begin{vmatrix} 0 & -2 & -1 \\ 0 & 3 & -1 \\ 10 & -3 & 3 \end{vmatrix} = 10 \begin{vmatrix} -2 & -1 \\ 3 & -1 \end{vmatrix} + 0 + 0$$

$$= 10 [(-2 \cdot -1) - (3 \cdot -1)] = 10 [2 + 3]$$

$$= 50$$

$$B = \begin{vmatrix} 13 & 0 & -1 \\ 0 & 0 & -1 \\ 0 & 10 & 3 \end{vmatrix} = 13 \begin{vmatrix} 0 & -1 \\ 10 & 3 \end{vmatrix} + 0 + 0$$

$$= 13 [(0 \cdot 3) - (-1 \cdot 10)] = 13 [0 + 10]$$

$$= 130$$

$$C = \begin{vmatrix} 13 & -2 & 0 \\ 0 & 3 & 0 \\ 0 & -3 & 10 \end{vmatrix} = 13 \begin{vmatrix} 3 & 0 \\ -3 & 10 \end{vmatrix} + 0 + 0$$

$$= 13 [(3 \cdot 10) - (-3 \cdot 0)] = 13 [30 - 0]$$

$$= 390$$

$$V_1 = \frac{A}{D} = \frac{50}{78} = 0.641025 \text{ V}$$

$$V_2 = \frac{B}{D} = \frac{130}{78} = 1.666666 \text{ V}$$

$$V_3 = \frac{C}{D} = \frac{390}{78} = 5 \text{ V}$$

$$i_1 = \frac{V_2 - V_1}{5} = \frac{1.666666\text{V} + 0.641025\text{V}}{5} = 0.205127\text{A}$$


$$i_2 = \frac{V_3 - V_1}{10} = \frac{5\text{V} + 0.641025\text{V}}{10} = 0.435897\text{A}$$

$$i_3 = \frac{V_3 - V_2}{4} = \frac{5\text{V} + 1.666666\text{V}}{4} = 0.833335\text{A}$$

$V_1 = 0.641\text{V}$	$i_1 = 0.205\text{A}$
$V_2 = 1.67\text{V}$	$i_2 = 0.436\text{A}$
$V_3 = 5\text{V}$	$i_3 = 0.833\text{A}$
	$i_4 = 0.641\text{A}$

$$i_4 = \frac{V_1}{1} = 0.641025$$

2] Given:

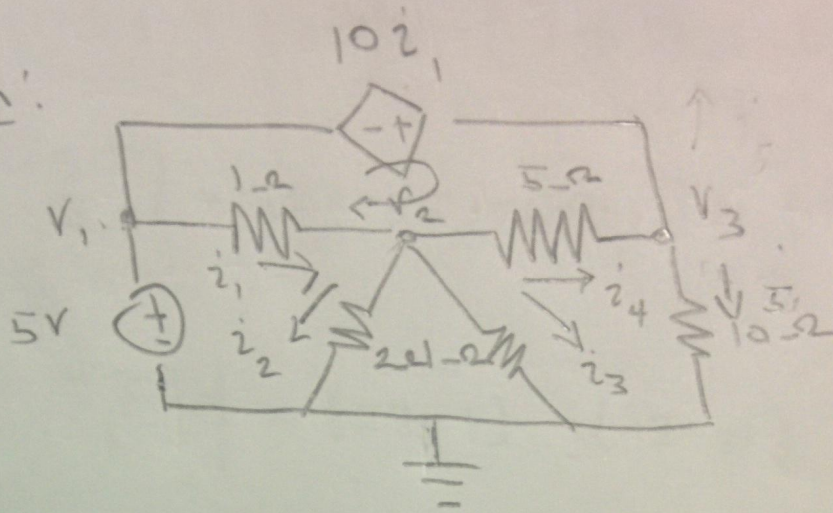

Determine:

All voltages & currents
Nodal analysis

Solve:

ground $V_1 = 5V$

node $i_1 = i_2 + i_3 + i_4$

$$\frac{V_1 - V_2}{1} = \frac{V_2}{2} + \frac{V_2}{1} + \frac{V_2 - V_3}{5}$$

$$10V_1 - 10V_2 = 5V_2 + 10V_2 + 2V_2 - 2V_3$$

$$10V_1 - 27V_2 + 2V_3 = 0$$

But $V_1 = 5V \therefore 27V_2 - 2V_3 = 50$

loop: $-10i_1 - 5i_4 - i_1 = 0$

$$11i_1 + 5i_4 = 0$$

$$11\left(\frac{V_1 - V_2}{1}\right) + 5\left(\frac{V_2 - V_3}{5}\right) = 0$$

$$11V_1 - 11V_2 + V_2 - V_3 = 0$$

$$11V_1 - 10V_2 - V_3 = 0$$

But $V_1 = 5V \therefore 10V_2 + V_3 = 55$

$$\begin{bmatrix} 27 & -2 \\ 10 & 1 \end{bmatrix} \begin{bmatrix} V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 50 \\ 55 \end{bmatrix}$$

$$V_1 = 5 \text{ V}$$

$$V_2 = 3.404 \text{ V}$$

$$V_3 = 20.95 \text{ V}$$


$$I_1 = \frac{V_1 - V_2}{1} = 1.596 \text{ A}$$

$$I_2 = \frac{V_2}{2} = 1.702 \text{ A}$$

$$I_3 = \frac{V_2}{1} = 3.404 \text{ A}$$

$$I_4 = \frac{V_2 - V_3}{5} = -3.509 \text{ A}$$

P3)

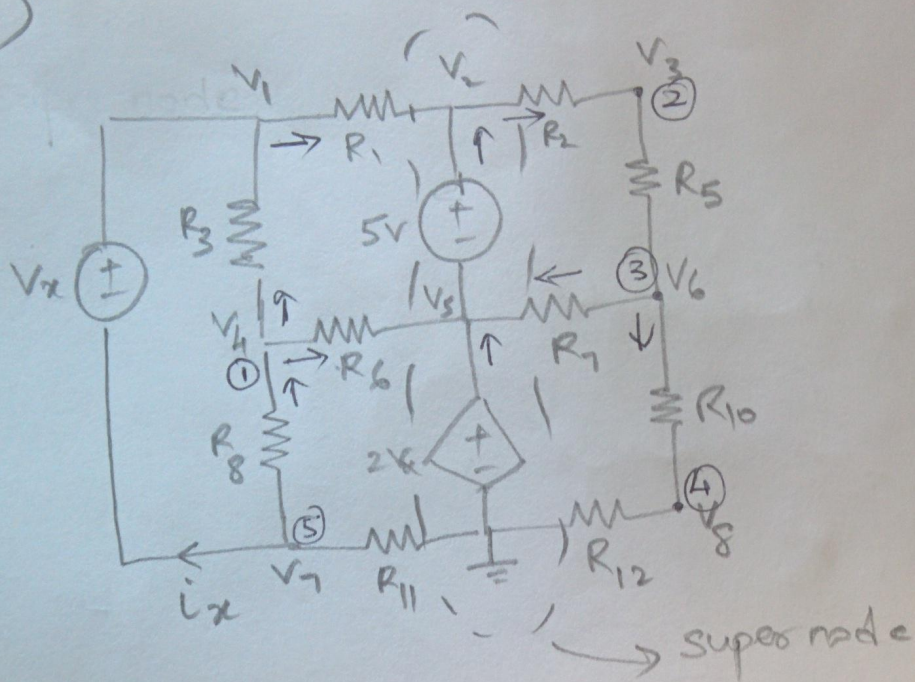

⑨ super node

$$\frac{V_1 - V_2}{R_1} + \frac{V_8}{R_{12}} + \frac{V_4 - V_5}{R_6} + \frac{V_6 - V_5}{R_7} = \frac{V_7}{R_{11}} + \frac{V_2 - V_3}{R_2}$$

$$V_1 \left(\frac{1}{R_1} \right) + V_2 \left(-\frac{1}{R_1} - \frac{1}{R_2} \right) + V_3 \left(\frac{1}{R_2} \right) + V_4 \left(\frac{1}{R_6} \right) + V_5 \left(-\frac{1}{R_6} - \frac{1}{R_7} \right) \\ + V_6 \left(\frac{1}{R_7} \right) + V_7 \left(-\frac{1}{R_{11}} \right) + V_8 \left(\frac{1}{R_{12}} \right) = 0 \rightarrow *$$

⑨ node ①

$$\frac{V_7 - V_4}{R_8} = \frac{V_4 - V_1}{R_3} + \frac{V_4 - V_5}{R_6}$$

$$V_1 \left(-\frac{1}{R_3} \right) + V_4 \left(\frac{1}{R_3} + \frac{1}{R_6} + \frac{1}{R_8} \right) + V_5 \left(-\frac{1}{R_6} \right) + V_7 \left(-\frac{1}{R_8} \right) = 0 \\ \rightarrow \#$$

node (2)

$$\frac{V_2 - V_3}{R_2} = \frac{V_3 - V_6}{R_5}$$

$$V_2 \left(\frac{1}{R_2} \right) + V_3 \left(-\frac{1}{R_2} - \frac{1}{R_5} \right) + V_6 \left(\frac{1}{R_5} \right) = 0 \rightarrow *$$

node (3)

$$\frac{V_3 - V_6}{R_5} = \frac{V_6 - V_5}{R_7} + \frac{V_6 - V_8}{R_{10}}$$

$$V_3 \left(\frac{1}{R_5} \right) + V_6 \left(-\frac{1}{R_5} - \frac{1}{R_7} - \frac{1}{R_{10}} \right) + V_5 \left(\frac{1}{R_7} \right) + V_8 \left(\frac{1}{R_{10}} \right) = 0 \rightarrow *$$

node (4)

$$\frac{V_4 - V_8}{R_{10}} = \frac{V_8}{R_{12}}$$

$$\frac{V_4}{R_{10}} + V_8 \left(-\frac{1}{R_{10}} - \frac{1}{R_{12}} \right) = 0 \rightarrow *$$

Also, we know

$$V_5 = 2V_x \quad \text{or} \quad V_x = \frac{V_5}{2}$$

$$V_x - V_5 = 5 \rightarrow *$$

$$V_1 - V_7 = V_x \quad \text{or} \quad V_1 - V_7 - \frac{V_5}{2} = 0 \rightarrow *$$

node (5)


$$\frac{V_1}{R_{11}} + \frac{V_7}{R_8} + V_4 \left(-\frac{1}{R_8} \right) = -I_x \rightarrow *$$

$$\begin{bmatrix}
 \frac{1}{R_1} & -\left(\frac{1}{R_1} + \frac{1}{R_2}\right) & \frac{1}{R_2} & \frac{1}{R_6} & -\left(\frac{1}{R_6} + \frac{1}{R_7}\right) & \frac{1}{R_7} & -\frac{1}{R_{11}} & \frac{1}{R_{12}} \\
 -\frac{1}{R_3} & 0 & 0 & \left(\frac{1}{R_3} + \frac{1}{R_6} + \frac{1}{R_8}\right) & -\frac{1}{R_6} & 0 & -\frac{1}{R_8} & 0 \\
 0 & \frac{1}{R_2} & -\left(\frac{1}{R_2} + \frac{1}{R_5}\right) & 0 & 0 & \frac{1}{R_5} & 0 & 0 \\
 0 & 0 & \frac{1}{R_5} & 0 & \frac{1}{R_7} & -\left(\frac{1}{R_5} + \frac{1}{R_7} + \frac{1}{R_{10}}\right) & 0 & \frac{1}{R_{10}} \\
 0 & 0 & 0 & \frac{1}{R_{10}} & 0 & 0 & 0 & -\left(\frac{1}{R_{10}} + \frac{1}{R_{11}}\right) \\
 0 & 1 & 0 & 0 & -1 & 0 & 0 & 0 \\
 1 & 0 & 0 & 0 & -1/5 & 0 & -1 & 0 \\
 \frac{1}{R_{11}} & 0 & 0 & -\frac{1}{R_8} & 0 & 0 & 0 & 0
 \end{bmatrix}$$

$\times \begin{bmatrix} V_1 \\ V_2 \\ V_3 \\ \vdots \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \end{bmatrix}$

* Since i_x is not given,
 Answer is in terms of i_x .

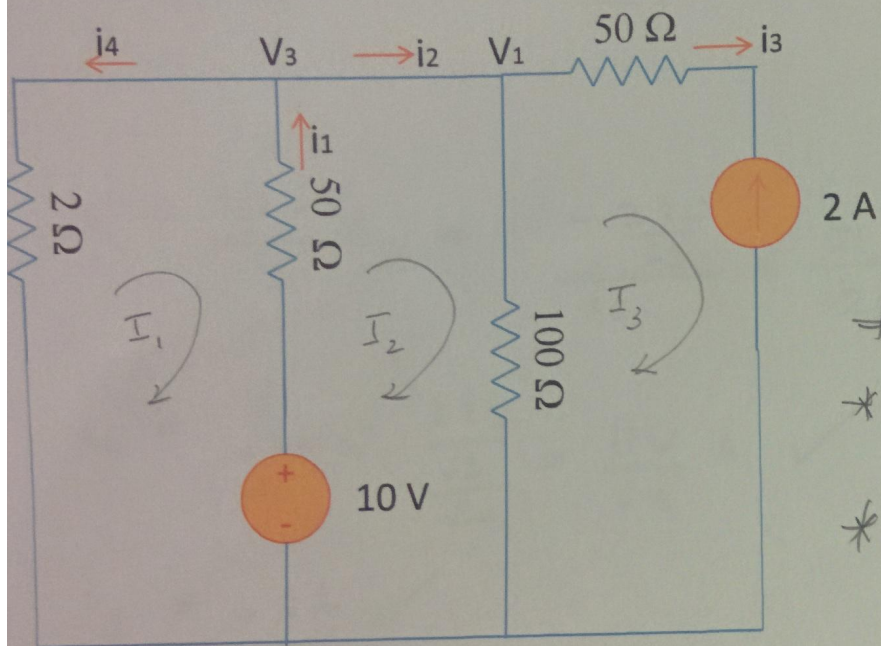Problem 4: use mesh analysis to find all the currents and node voltages.



$$\textcircled{1} 2I_1 + 50(I_1 - I_2) + 10V = 0$$

$$\textcircled{2} 50(I_2 - I_1) + 100(I_2 - I_3) - 10 = 0$$

$$\textcircled{3} I_3 = -2A$$

$$+ 52I_1 - 50I_2 = -10V$$

$$* -50I_1 + 150I_2 - 100I_3 = 10V$$

$$* I_3 = -2A$$

$$I_1 = -\frac{110}{53}$$

$$I_2 = -\frac{519}{265}$$

$$I_3 = -2$$

$$i_4 = I_2 - I_1 = \frac{31}{265} A$$

$$i_2 = I_2 = -\frac{519}{265} A$$

$$i_4 = \frac{110}{53} A$$


$$i_3 = -2A$$

$$\begin{bmatrix} 52 & -50 & 0 \\ -50 & 150 & -100 \\ 0 & 0 & 1 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} -10 \\ 10 \\ -2 \end{bmatrix}$$

$$V_3 = V_1 = \frac{220}{53} V$$

$$V_B = 2(i_4) = 2\left(\frac{110}{53}\right) A = \frac{220}{53} V$$

5] Given:

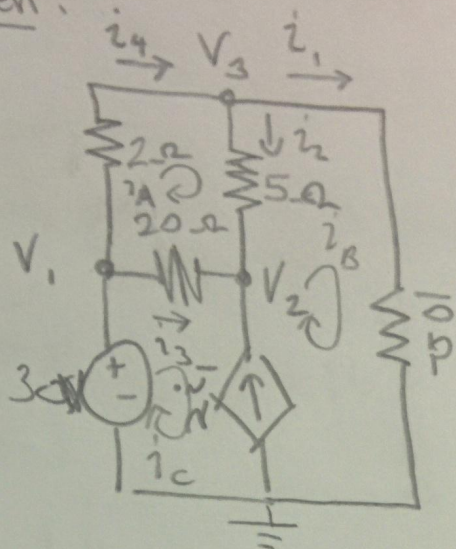


use mesh analysis

Determine: currents & voltages

Solve:

Mesh A: $2i_A + 5(i_A - i_B) + 20(i_A - i_C) = 0$
 $27i_A - 5i_B - 20i_C = 0$

Mega Mesh:

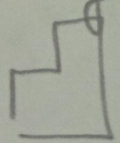

$-30 + 20(i_C - i_A) + 5(i_B - i_A) + 10i_B = 0$
 $-25i_A + 15i_B + 20i_C = 30$

Node

$2i_1 = i_B - i_C$ $i_1 = i_B$
 $2i_B = i_B - i_C$
 $i_B - i_C = 0$

$$\begin{bmatrix} 27 & -5 & -20 \\ -5 & 3 & 4 \\ 0 & 1 & -1 \end{bmatrix} \begin{bmatrix} i_A \\ i_B \\ i_C \end{bmatrix} = \begin{bmatrix} 0 \\ 30 \\ 0 \end{bmatrix}$$

$$\begin{vmatrix} 27 & -5 & -20 \\ -5 & 3 & 4 \\ 0 & 1 & -1 \end{vmatrix} = -64$$

$$i_A = \frac{A}{D} = 2.34375 \text{ A}$$

$$i_B = \frac{B}{D} = 2.53125 \text{ A}$$

$$i_C = \frac{C}{D} = 2.53125 \text{ A}$$

$$A = \begin{vmatrix} 0 & -5 & -20 \\ 6 & 3 & 4 \\ 0 & 1 & -1 \end{vmatrix} = -150$$

$$B = \begin{vmatrix} 27 & 0 & -20 \\ -5 & 6 & 4 \\ 0 & 0 & -1 \end{vmatrix} = -162$$

$$i_1 = i_B = 2.53125$$

$$i_2 = i_A - i_B = 2.34375 - 2.53125$$

$$= -0.1875$$

$$i_3 = i_C - i_A = 2.53125 - 2.34375$$

$$= 0.1875$$

$$i_4 = i_A = 2.34375 \text{ A}$$

$$V_1 = 30 \text{ V}$$

$$i_3 = \frac{V_1 - V_2}{20} \Rightarrow V_2 = V_1 - 20i_3$$

$$= 30 - 20(0.1875)$$

$$= 26.25 \text{ V}$$

$$i_2 = \frac{V_3 - V_2}{5} \Rightarrow V_3 = 5i_2 + V_2$$

$$= 5(-0.1875) + 26.25 \text{ V}$$

$$= 25.3125$$

$$i_1 = 2.53 \text{ A}$$

$$V_1 = 30 \text{ V}$$


$$i_2 = -0.188 \text{ A}$$

$$V_2 = 26.25 \text{ V}$$

$$i_3 = 0.188 \text{ A}$$

$$V_3 = 25.3 \text{ V}$$

$$i_4 = 2.34 \text{ A}$$

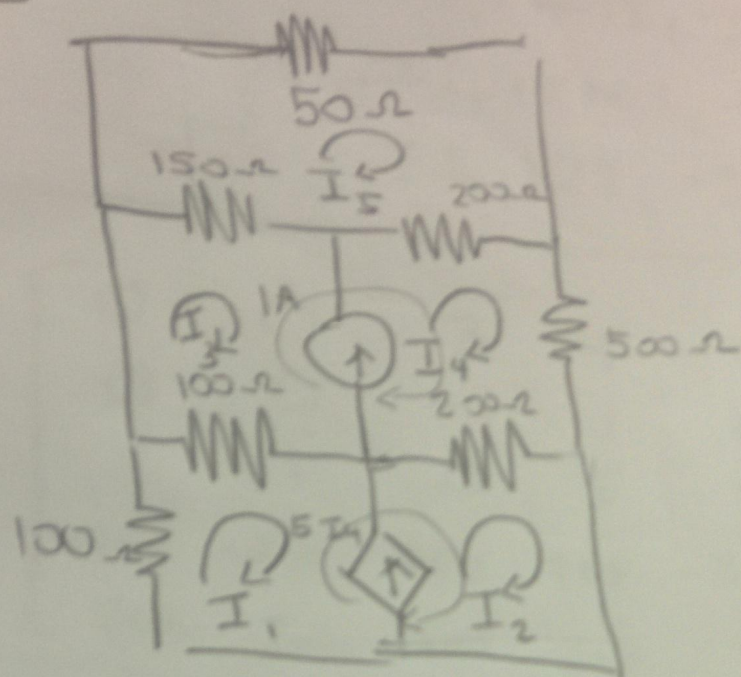

Determine: Mesh Matrix

Solve:

Mesh 5: $50 I_5 + 200 (I_5 - I_4) + 150 (I_5 - I_3) = 0$
 $-150 I_3 - 200 I_4 + 400 I_5 = 0$
 $3 I_3 + 4 I_4 - 8 I_5 = 0$




$1 A = I_4 - I_3 \Rightarrow -I_3 + I_4 = 1$




$5 I_4 = I_2 - I_1 \Rightarrow I_1 - I_2 + 5 I_4 = 0$

Mesh

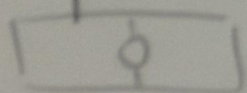

Mesh $150 (I_3 - I_5) + 200 (I_4 - I_5) + 500 I_4$
 $+ 200 (I_4 - I_2) + 100 (I_3 - I_1) = 0$
 $-100 I_1 - 200 I_2 + 250 I_3 + 900 I_4 + 350 I_5 = 0$

Mega Mesh

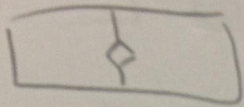


$$100I_1 + 100(I_1 - I_3) + 200(I_2 - I_4) = 0$$

$$200I_1 + 200I_2 - 100I_3 - 200I_4 = 0$$

$$2I_1 + 2I_2 - I_3 - 2I_4 = 0$$

$$\begin{bmatrix} 0 & 0 & 3 & 4 & -8 \\ 0 & 0 & -1 & 1 & 0 \\ 1 & -1 & 0 & 5 & 0 \\ -100 & -200 & 250 & 900 & -350 \\ 200 & 200 & -100 & -200 & 0 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \\ I_4 \\ I_5 \end{bmatrix} = \begin{bmatrix} 0 \\ -1 \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

P7) To find R_{TH} ,

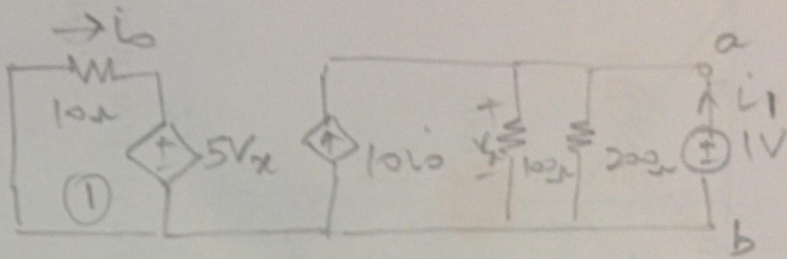

$$V_x = 1V$$

∴ In loop ①,


$$-5V_x = 10i_0 \Rightarrow i_0 = -0.5$$

⑥ node 'a',

$$10i_0 + I_1 = \frac{1}{100} + \frac{1}{200}$$

$$\therefore I_1 = 5.015 A$$
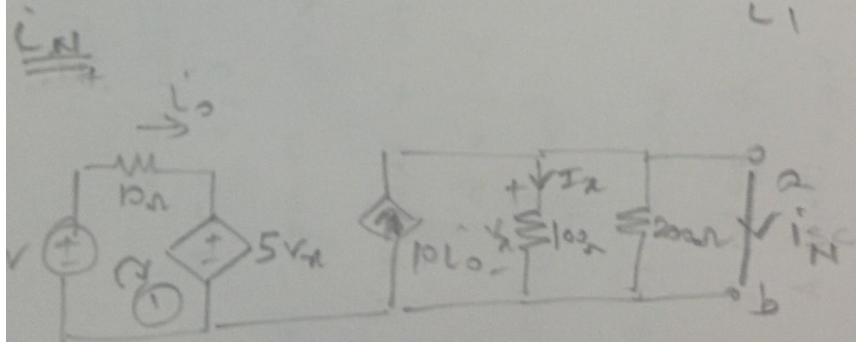
$$\therefore R_{TH} = \frac{1}{I_1} = \frac{1}{5.015} \Omega$$





KVL in loop 1


$$\therefore -5 + 10i_0 + 5V_x = 0$$

$$i_0 = \frac{5}{10} = 0.5 A$$


$$\therefore I_N = 5 A$$

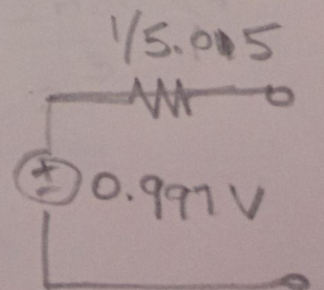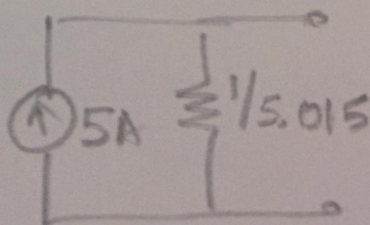

R_{TH} , Ignore independent sources

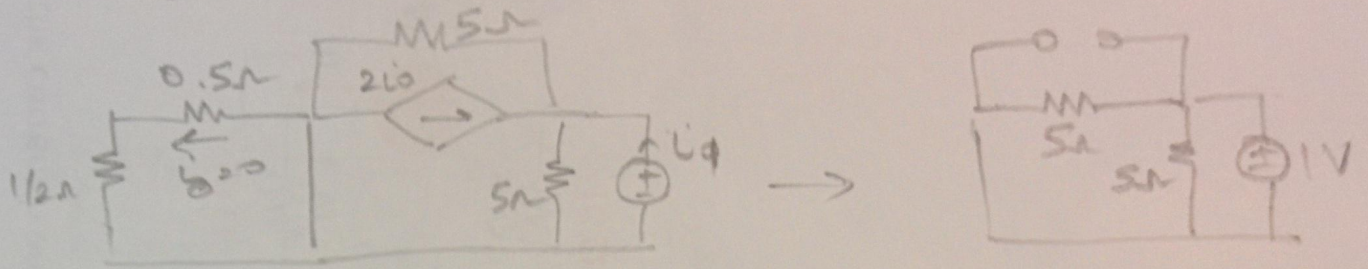


$$i_o = 0$$

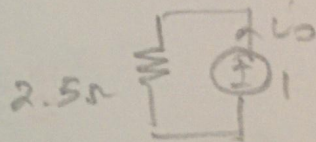

$$i_o = 1/2.5$$

$$R_N = R_{TH} = 1/i_o = 2.5 \Omega$$

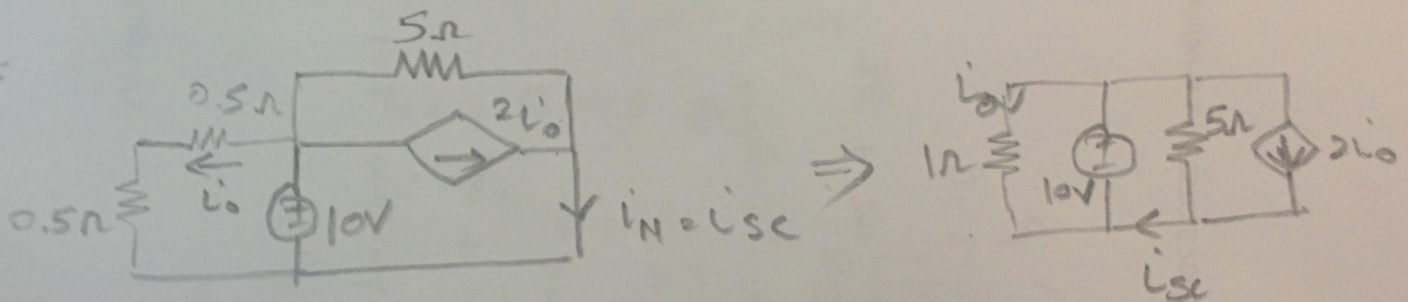

$$i_o = \frac{10}{1} = 10 \text{ A}$$

$$\begin{aligned} i_{sc} &= \frac{10}{5} + 2i_o \\ &= \frac{10}{5} + 2 \times 10 \\ &= 12 \text{ A} \end{aligned}$$

