


EECS 70A: Network Analysis Homework #5

- The homework is due Friday 6/05/2015 at 5:30pm

You can choose either way to turn in your homework.

- 1) Turn it in during discussions
- 2) Turn it in during TA office hour
- 3) EEE Dropbox


Problem 1: Find the transfer function of the circuit

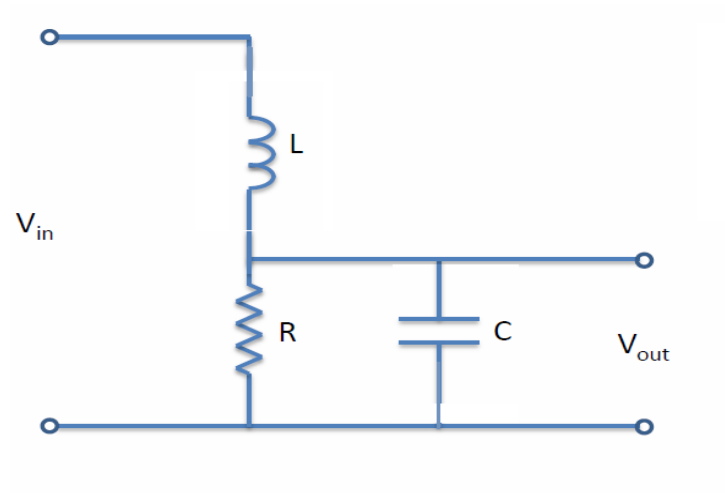

Problem 2: Given $H_\omega = \frac{1}{1+j\omega\tau_1} * \frac{1}{1+j\omega\tau_2}$, where $\tau_2 > \tau_1$, please draw the Bode plot (only magnitude) of the transfer function.

Extra credit: Try to design a circuit having such a transfer function

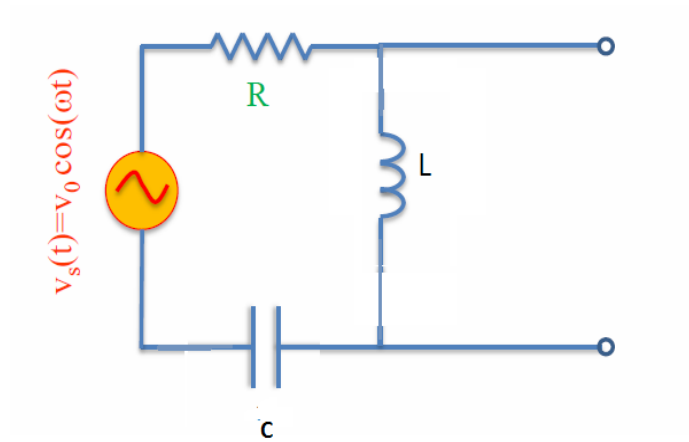Problem 4: Find V_{th} and Z_{th} , and draw the Thevenin equivalent circuit for the following circuit.



Problem 5: Given the transfer function $H(\omega)$ of a system, if the input is $V_{in} = \text{Re}(\sum_n a_n e^{j\omega_n t})$ then the output can be expressed as $V_{out}(t) = \text{Re}[\sum_n a_n H(\omega_n) e^{j\omega_n t}]$ where $H(\omega) = |H(\omega)| e^{j\Phi(\omega)}$.

Now, for a system, the Bode plot of its transfer function is illustrated in the next page, and $\omega_o \tau = 1$.

If the input voltage is $V_{in}(t) = \text{Re}(1 \cdot e^{j\omega_1 t} + 1 \cdot e^{j\omega_2 t})$

Find the output voltage for the following cases:

a) $\omega_1 = 0.01\tau^{-1}$ $\omega_2 = 10\tau^{-1}$

b) $\omega_1 = 0.1\tau^{-1}$ $\omega_2 = 100\tau^{-1}$

