



1) (a)  $v(t) = 2\cos(\omega t + \pi/12)$


$V = x + jy$  ?  $V = re^{j\phi}$  ?

$v(t) = V_m \cos(\omega t + \phi)$

$V_m = 2$   $\phi = \pi/12$

$V_m = r = 2$

$V = 2e^{j\pi/12}$

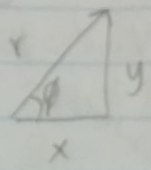

$x = r \cos \phi = 2 \cos \frac{\pi}{12} = 1.932$

$y = r \sin \phi = 2 \sin \frac{\pi}{12} = 0.518$

$V = 1.932 + j(0.518)$

(b)  $i(t) = 4\sin(\omega t + \pi/8)$


$I = x + jy$  ?  $I = re^{j\phi}$  ?

$i(t) = I_m \cos(\omega t + \phi)$

$\theta = \frac{\pi}{8}$

$\phi = \frac{\pi}{8} - \frac{\pi}{2} = \frac{\pi}{8} - \frac{4\pi}{8} = -\frac{3\pi}{8}$

$r = I_m = 4$

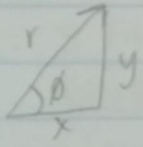

$x = r \cos \phi = 4 \cos(-\frac{3\pi}{8}) = 1.531$

$y = r \sin \phi = 4 \sin(-\frac{3\pi}{8}) = -3.696$

$I = 4e^{(-3\pi/8)j}$


$I = 1.531 - 3.696j$

(c)  $V = 2 + 1j = 2 + j$   $v(t) = ?$

$v(t) = V_m \cos(\omega t + \phi)$

$x = 2$   $y = 1$

$V_m = r = \sqrt{5}$

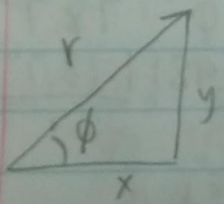

$x^2 + y^2 = r^2$

$2^2 + 1^2 = r^2$

$4 + 1 = r^2$

$r = \sqrt{5}$

$\tan \phi = \frac{y}{x} = \frac{1}{2}$

$\phi = 26.57^\circ$


$v(t) = \sqrt{5} \cos(\omega t + 26.57^\circ)$

(d)  $I = 4 + 2j$   $i(t) = ?$

$i(t) = I_m \cos(\omega t + \phi)$

$x = 4$   $y = 2$

$I_m = r = 2\sqrt{5}$

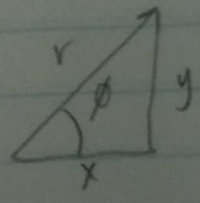

$x^2 + y^2 = r^2$

$4^2 + 2^2 = r^2$

$16 + 4 = r^2$

$r = \sqrt{20} = 2\sqrt{5}$

$\tan \phi = \frac{y}{x} = \frac{2}{4} = \frac{1}{2}$

$\phi = 26.57^\circ$

$i(t) = 2\sqrt{5} \cos(\omega t + 26.57^\circ)$

P2

Given:  $I(t) = 2 \cos(\underline{10t} + 30^\circ)$ ,  $\omega = 10 \text{ rad/s}$

$$\underline{I} = 2 \angle 30^\circ$$

$$Z_C = \frac{1}{j\omega C} = \frac{-j}{(10 \text{ rad/s})(100 \times 10^{-3} \text{ F})} = -j \Omega$$

$$Z_{eq} = 5 \Omega \parallel -j \Omega$$

$$Z_{eq} = \left( \frac{1}{5} - \frac{1}{j} \right)^{-1} = 0.9805 \angle -78.69^\circ$$

$$V = I \cdot Z_{eq} = 2 \angle 30^\circ \cdot 0.9805 \angle -78.69^\circ$$

$$\underline{V} = 1.961 \angle -48.69^\circ$$


$$i = \frac{V}{R} = \frac{1.961 \angle -48.69^\circ}{5}$$

$$i = 0.3922 \angle -48.69^\circ$$

$$\boxed{V(t) = 1.961 \cos(10t - 48.69^\circ)}$$

$$\boxed{i(t) = 0.3922 \cos(10t - 48.69^\circ)}$$

3

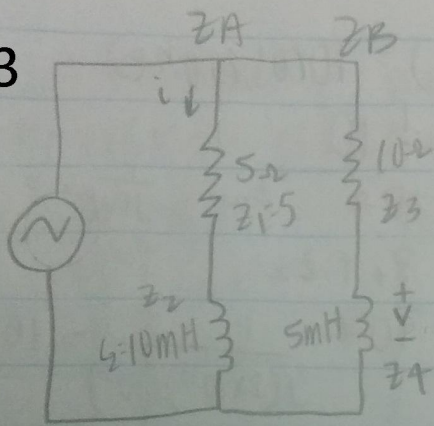

$$V_s(t) = 20 \cos(100t) \quad \omega = 100$$

$$V_s = 20 \angle 0^\circ = 20$$

$$z_1 = 5 \Omega \quad z_2 = j\omega(10 \text{mH}) \quad z_3 = 10 \Omega \quad z_4 = j\omega(5 \text{mH})$$

$$z_A = 5 + j\omega(10 \times 10^{-3}) = 5 + j(100)(10 \times 10^{-3})$$

$$z_A = 5 + j$$

$$I_{iA} = V_s / z_A = 20 / (5 + j)$$

$$= \frac{20(5 - j)}{(5 + j)(5 - j)} = \frac{100 - 20j}{25 + 1} = \frac{100 - 20j}{26}$$

$$I_{iA} = 3.846 - 0.769j$$

$$(3.846^2) + (-0.769)^2 = i^2$$

$$i = 3.921$$

$$\tan \phi = \frac{-0.769}{3.846} \quad \phi = -11.31^\circ$$

$$i(t) = 3.921 \cos(100t - 11.31^\circ) \text{ A}$$

$$z_B = 10 + j\omega(5 \times 10^{-3}) = 10 + j(100)(5 \times 10^{-3}) = 10 + 0.5j$$

$$V_s = I_B z_B$$

$$I_B = \frac{V_s}{z_B} = \frac{20}{(10 + 0.5j)(10 - 0.5j)} = \frac{200 - 10j}{100.25} = 1.995 - 0.0998j$$

$$V_3 = I_B z_3 = (1.995 - 0.0998j)(10) = 19.95 - 0.998j$$


$$V_s - V_3 = 20 - 19.95 + 0.998j = 0.05 + 0.998j$$

$$0.05^2 + 0.998^2 = i^2 \quad \tan \phi = \frac{0.998}{0.05} \quad \phi = 87.132^\circ$$

$$i = 0.999$$

$$v(t) = 0.999 \cos(100t + 87.1^\circ)$$

4.

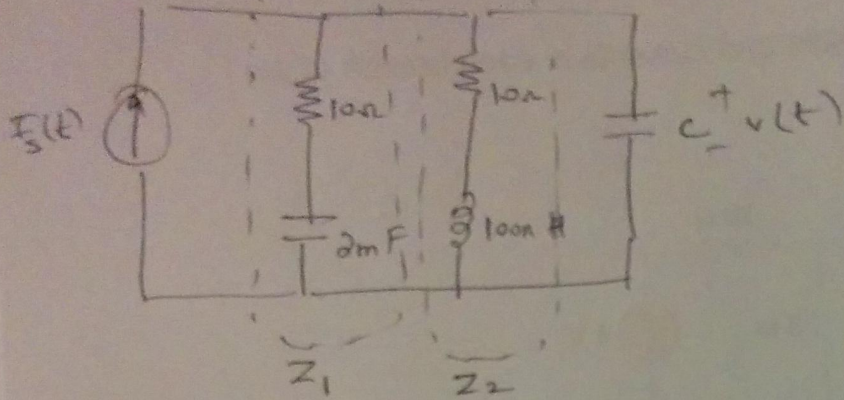


$$Z_1 = 10 + \frac{1}{j10^6 \times 2m} = 10 + j(500\mu)$$

$$Z_2 = 10 + j10^6 \times 100n = 10 + j0.1$$


$$Z = Z_1 \parallel Z_2 = 5 + 0.025j$$

$$\underline{I_c} = \frac{Z}{Z + Z_c} \cdot \underline{I_s}$$
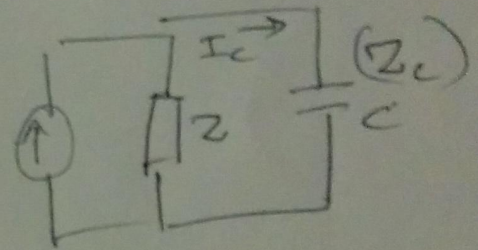
$$\underline{V} = Z_c \cdot \underline{I_c} \\ = \frac{Z_c \cdot Z}{Z + Z_c} \cdot \underline{I_s}$$



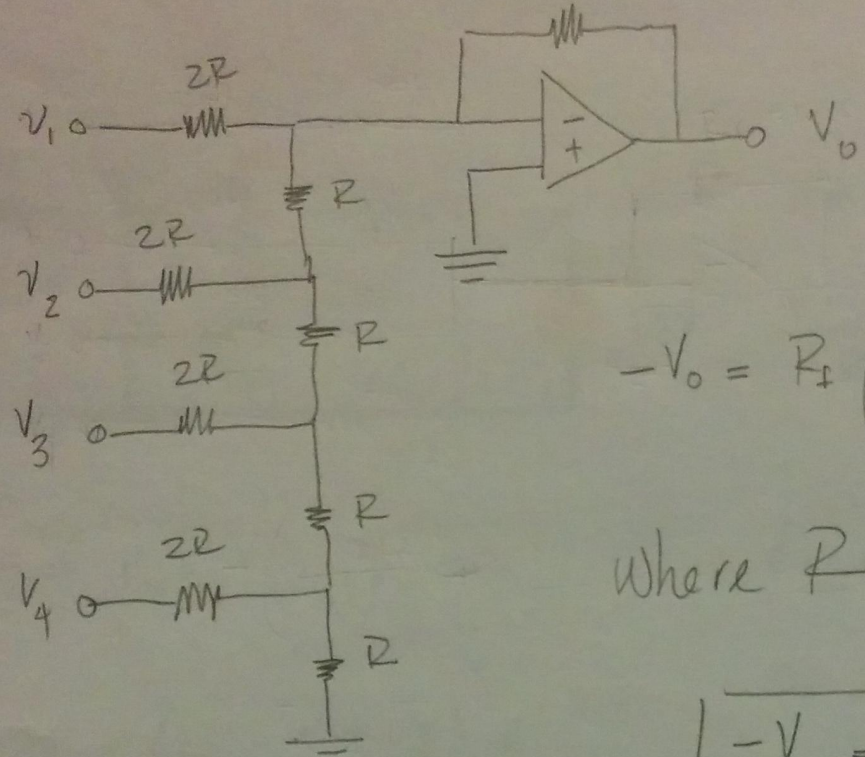Problem 6. Design a 4 - bit ( 4 input) D/A converter using an op-amp and 9 resistors. Let  $R_f = 10\text{ k}\Omega$  and  $R = 5\text{ k}\Omega$ . Find the output voltage for the input  $V_i = [1\ 0\ 0\ 1]$ .




$$-V_o = R_f \left( \frac{V_1}{2R} + \frac{V_2}{4R} + \frac{V_3}{8R} + \frac{V_4}{16R} \right)$$

Where  $R_f = 5 \times 2R$

$$-V_o = 1.125\text{ V}$$


$$V_o = -1.125\text{ V}$$

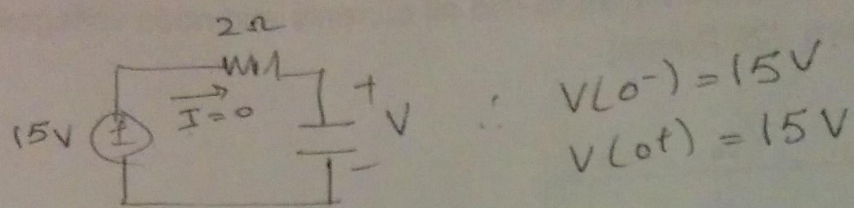7. At  $t < 0$ , the capacitor is completely charged. Hence, is represented by



At  $t > 0$ , the thevenin resistance connected to the capacitor is


$$R_{TH} = 2 \parallel 6 = 1.5 \Omega$$

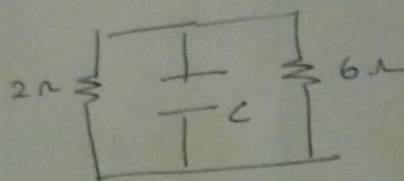

$\therefore$  The time-constant

$$\tau = R_{TH} C = 1.5 \times \frac{1}{3} = 0.5 \text{ s}$$

At  $t = \infty$ , the circuit is,

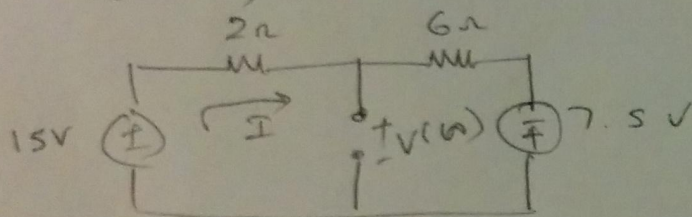

$$-15 + 2I + 6I + 7.5 = 0$$

$$8I = 22.5$$

$$I = 2.8125$$

$$\therefore V(\infty) = 15 - 2I = 9.375$$

$$\therefore V(t) = V(\infty) + [V(0) - V(\infty)] e^{-t/\tau}$$

$$V(t) = (9.375 + 5.625 e^{-2t}) \text{ for } t > 0,$$

at  $t = 0.5$

$$V(t) = 7.63 \text{ V}$$

## Problem 5

using KVL:  $V_s = V_1 + V_2$

$$V_2 = iR$$

$$i = C \frac{dV_1}{dt}$$

therefore  $V_s = RC \cdot \frac{dV_1}{dt} + V_1 \Rightarrow \frac{dV_1}{dt} + \frac{V_1}{RC} = \frac{V_0 \cos \omega t}{RC}$  (\*)

The solution should obey the form of  $A \cos \omega t + B \sin \omega t$

Assume  $V_1 = A \cos \omega t + B \sin \omega t$

Then  $\frac{dV_1}{dt} = -A\omega \sin \omega t + B\omega \cos \omega t$ , substitute into (\*)

$$-A\omega \sin \omega t + B\omega \cos \omega t + \frac{A}{RC} \cos \omega t + \frac{B}{RC} \sin \omega t = \frac{V_0}{RC} \cos \omega t$$

$$(B\omega + \frac{A}{RC}) \cos \omega t + (\frac{B}{RC} - A\omega) \sin \omega t = \frac{V_0}{RC} \cos \omega t$$

Compare the coefficients.

$$\begin{cases} B\omega + \frac{A}{RC} = \frac{V_0}{RC} \\ \frac{B}{RC} - A\omega = 0 \end{cases} \Rightarrow B = A\omega RC$$

$$A\omega RC \cdot \omega + \frac{A}{RC} = \frac{V_0}{RC} \Rightarrow A = \frac{V_0}{RC(\omega^2 RC^2 + 1)} = \frac{V_0}{\omega^2 RC^2 + 1}$$

$$B = A\omega RC = \frac{\omega RC}{\omega^2 RC^2 + 1} \cdot V_0$$

$$V_1 = A \cos \omega t + B \sin \omega t$$

$$= \frac{V_0}{1 + \omega^2 RC^2} \cos \omega t + \frac{\omega RC}{\omega^2 RC^2 + 1} V_0 \sin \omega t$$

$$= \sqrt{\left(\frac{V_0}{1 + \omega^2 RC^2}\right)^2 + \left(\frac{V_0 \omega RC}{1 + \omega^2 RC^2}\right)^2} \cos(\omega t + \varphi)$$

$$\text{where } \varphi = \arctan\left(\frac{-\frac{\omega RC V_0}{\omega^2 RC^2 + 1}}{\frac{V_0}{\omega^2 RC^2 + 1}}\right) = \arctan(-\omega RC)$$

$$\therefore V_1 = \frac{V_0}{\sqrt{1 + \omega^2 RC^2}} \cos(\omega t + \varphi), \quad \varphi = \arctan(-\omega RC)$$

$$V_2 = V_S - V_1$$

$$= V_0 \cos \omega t - \frac{V_0}{\sqrt{1 + \omega^2 R^2 C^2}} \cos(\omega t + \phi)$$

where  $\phi = \text{atan}(\omega RC)$