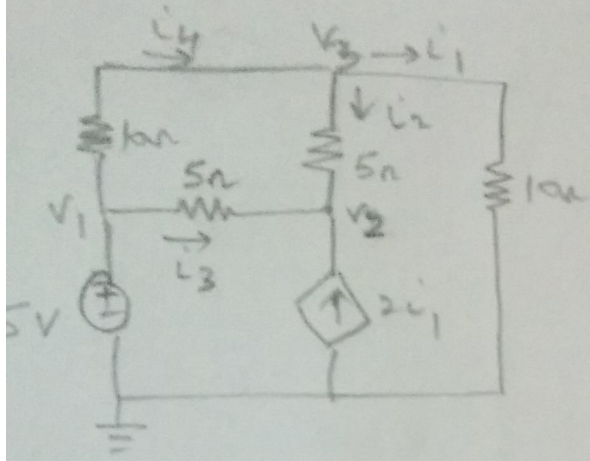


Question 1.



$$V_1 = 5 \text{ V}$$

$$i_1 = \frac{V_3}{10}$$

⊙ node 2.

$$\frac{V_1 - V_2}{5} + \frac{V_3 - V_2}{5} + 2i_1 = 0$$

$$\frac{5 - V_2}{5} + \frac{V_3 - V_2}{5} + 2 \times \frac{V_3}{10} = 0$$

$$\text{or } 2V_2 - 2V_3 = 5 \quad \text{--- (1)}$$

⊙ node 3,

$$\frac{5 - V_3}{10} = \frac{V_3}{10} + \frac{V_3 - V_2}{5}$$

$$\text{or } -2V_2 + 4V_3 = 5 \quad \text{--- (2)}$$

Solving (1) & (2)

$$\underline{V_2} = \frac{15}{2} \text{ V} = 7.5 \text{ V}$$

$$\underline{V_3} = 5 \text{ V}$$


$$\underline{i_1} = \frac{5}{10} = 0.5 \text{ A}$$

$$\underline{i_2} = \frac{V_3 - V_2}{5} = -0.5 \text{ A}$$

$$\underline{i_3} = \frac{V_1 - V_2}{5} = -0.5 \text{ A}$$

$$\underline{i_4} = \frac{V_1 - V_3}{10} = 0 \text{ A}$$

Question 2

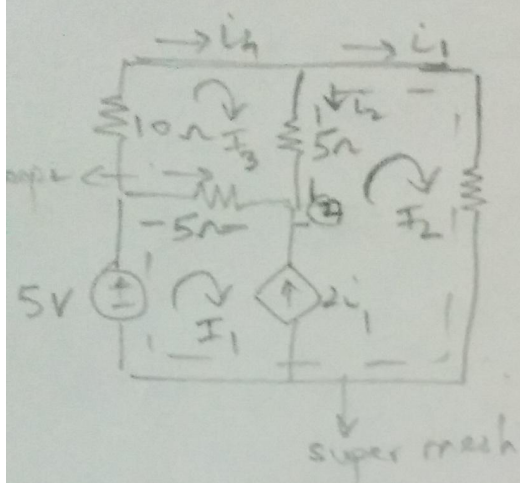

in super mesh,

$$-5 + 5(I_1 - I_3) + 5(I_2 - I_3) + 10I_2 = 0$$

$$5I_1 + 15I_2 - 10I_3 = 5 \quad \text{--- (1)}$$

in loop 2,

$$10I_3 + 5(I_3 - I_2) + 5(I_3 - I_1) = 0$$

$$-5I_1 - 5I_2 + 20I_3 = 0 \quad \text{--- (2)}$$

$$I_2 = I_1$$

at node 2, $2i_1 = I_2 - I_1$

or $I_1 = -I_2$

$$\Rightarrow I_2 = -I_1 \text{ or } I_1 + I_2 + 0I_3 = 0 \quad \text{--- (3)}$$

Substituting $I_2 = -I_1$ in (1) & (2) & solving,

$$I_1 = -0.5 \text{ A}$$

$$I_2 = 0.5 \text{ A}$$

$$I_3 = 0 \text{ A}$$

$$i_1 = 0.5 \text{ A}$$

$$i_2 = -0.5 \text{ A}$$

$$i_3 = -0.5 \text{ A}$$

$$i_4 = 0 \text{ A}$$

$$\Rightarrow V_3 = 0.5 \times 10 = 5 \text{ V}$$


$$V_3 = 5 \text{ V}$$

$$\frac{5V_2}{5} = I_1$$

or

$$V_2 = \frac{15}{2}$$

Question 3 :

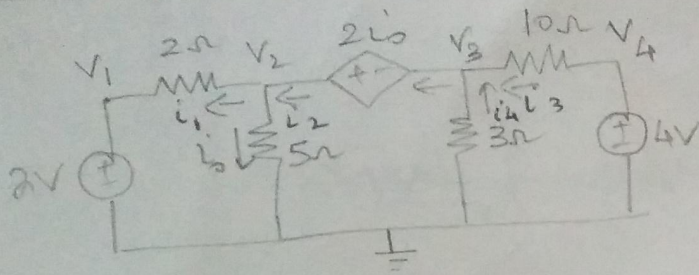

$$\underline{V_1 = 2V}$$

$$\underline{V_4 = 4V}$$

⑨ super node 2 - 3,

$$\frac{V_2 - V_1}{2} + \frac{V_2}{5} = -\frac{V_3}{3} + \frac{V_4 - V_3}{10}$$

$$\frac{V_2 - 2}{2} + \frac{V_2}{5} = -\frac{V_3}{3} + \frac{4 - V_3}{10}$$

$$0.7V_2 - 1 = -0.433V_3 + 0.4$$

$$0.7V_2 = -0.433V_3 + 1.4 \quad \text{--- (1)}$$

$$V_2 - V_3 = 2i_0 \quad \text{and} \quad i_0 = \frac{V_2}{5}$$

$$\Rightarrow 0.6V_2 = V_3$$

substituting in (1)

$$0.7V_2 = -0.433 \times 0.6V_2 + 1.4$$

$$0.7V_2 = -0.26V_2 + 1.4$$

$$\underline{V_2 = 1.46V}$$

$$\underline{V_3 = 0.875V}$$

$$i_1 = \frac{V_2 - V_1}{2} = -0.27A$$


$$i_0 = \frac{V_2}{5} = 0.29A$$

$$i_2 = 0.02A$$

$$i_4 = \frac{-V_3}{3} = -0.29A$$

$$i_3 = \frac{V_4 - V_3}{10} = 0.3A$$

Question 4

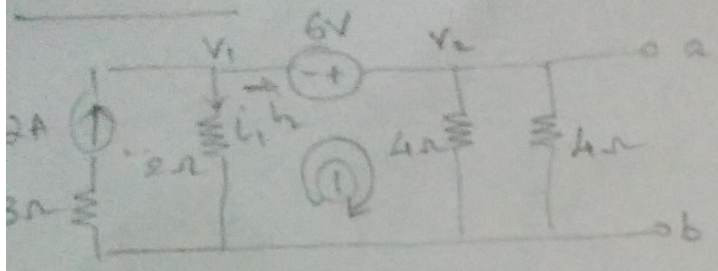

$$V_2 - V_1 = 6V$$

$$I_1 + I_2 = 2 \quad \text{--- (1)}$$

KVL around loop 1

$$-2I_1 - 6 + I_2(4||4) = 0$$

$$2I_2 - 2I_1 = 6 \quad \text{--- (2)}$$


solving (1) & (2)

$$I_2 = 2.5 A$$

$$I_1 = -0.5 A$$

$$\therefore V_{TH} = 4 \left(\frac{I_2}{2} \right) = 5 V$$

To find I_N ,


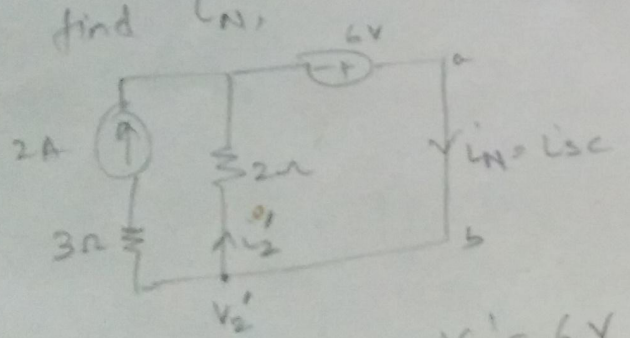


at node 2', $V_{2'} = 6V$


$$I_N = 2 + \frac{V_{2'}}{2}$$

$$I_N = 2 + \frac{6}{2} = 5 A$$

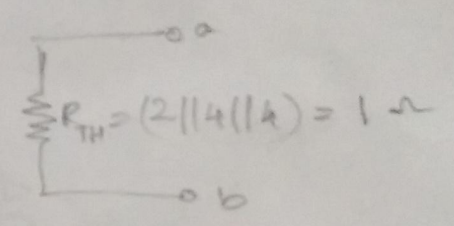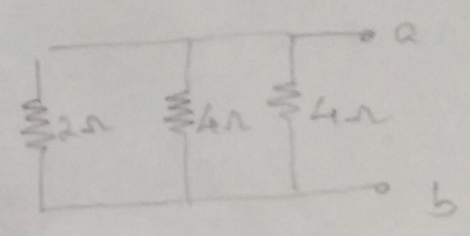To find R_{TH} , short the voltage source & open the current source.



Thevenin circuit,

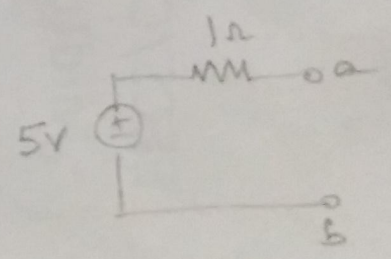

Norton circuit,

