




10th week lectures: Benchmarking Nanoelectronics



Transistor AC properties


“Normal active” bias

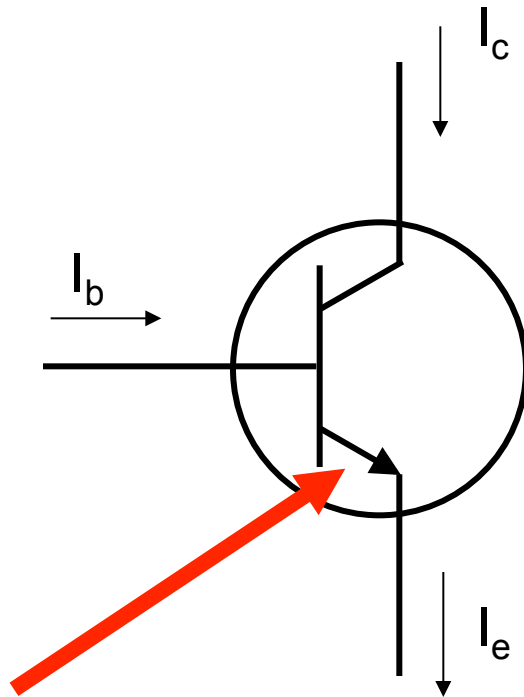

Like a diode.

- E-B forward bias
($V_b > V_e$)
- C-B reverse bias
($V_c > V_b$)
- $I_{ce} = 100 I_{be} = b I_{be}$

Global dc properties

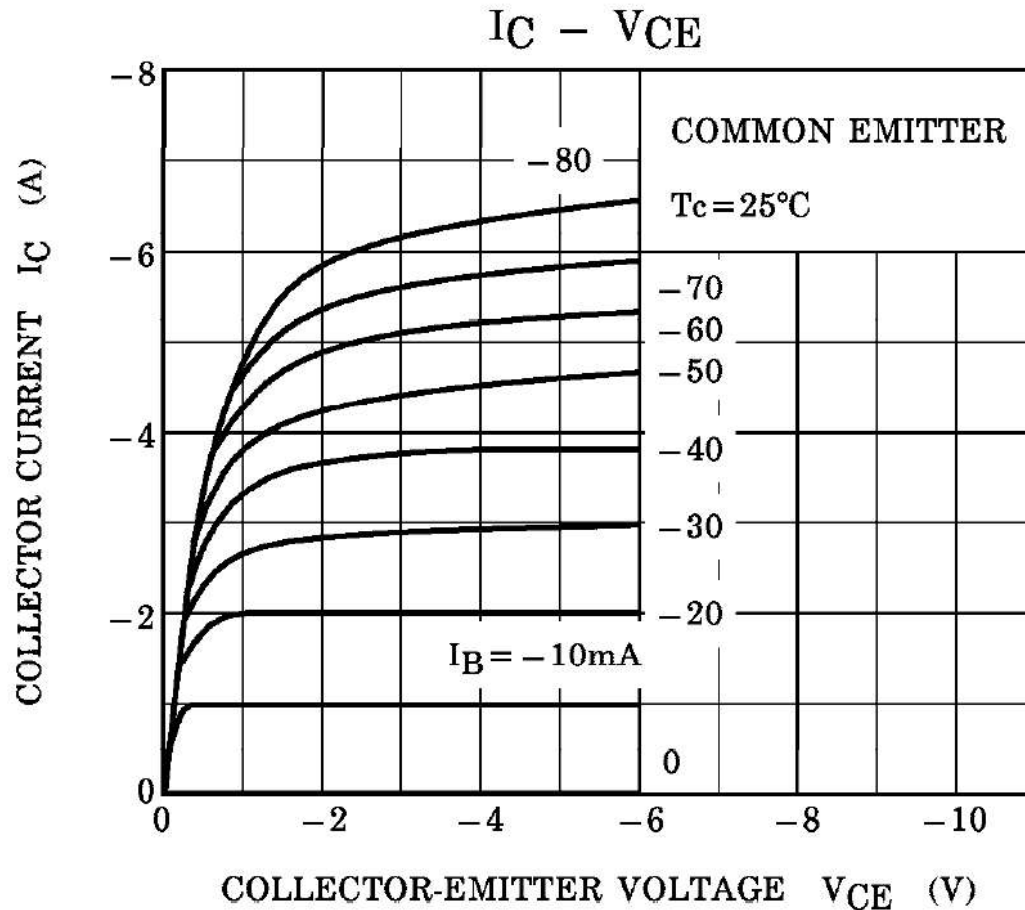


Note
Early effect.

It is assumed you know this, so it is rare to see on data sheets!

<http://www.toshiba.com/taec/components/Datasheet/2SA1244DS.pdf>

ac properties: notation

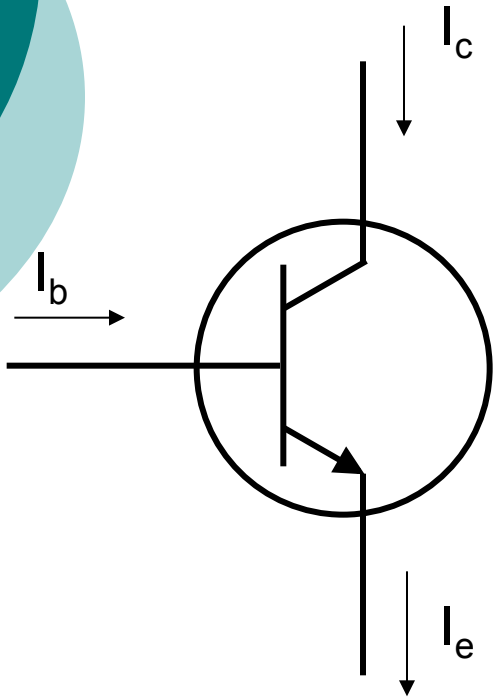

I_E dc


i_e ac

$$i_E \text{ total} = I_E + i_e$$

We will use equivalent circuit #1 (implicitly).

ac properties


common-emitter configuration

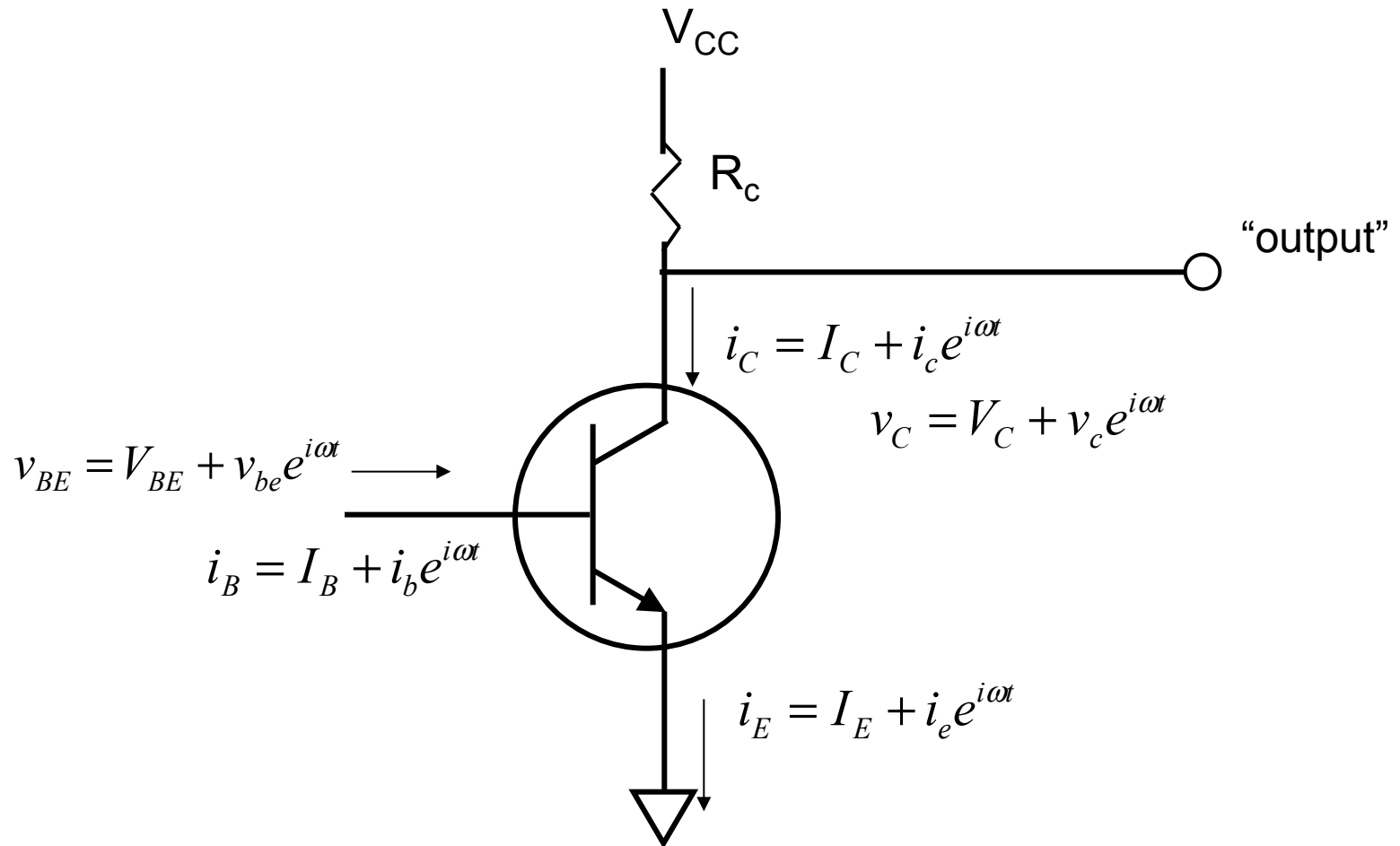

Note: three terminal device has three-terminal equivalent ac circuit.

dc analysis

common-emitter configuration

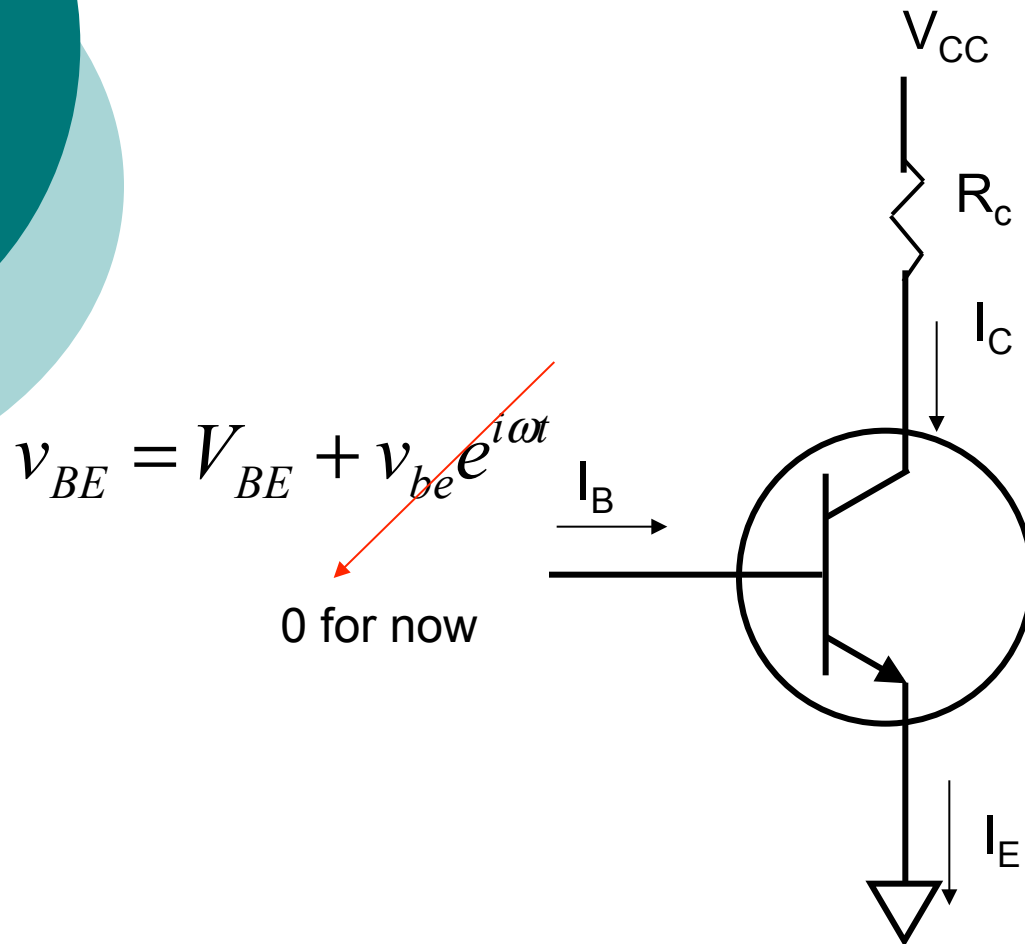


$$I_C = I_S e^{eV_{BE}/kT}$$

$$I_E = I_C / \alpha$$

$$I_B = I_C / \beta$$


$$V_C = V_{CE} = V_{CC} - I_C R_C$$

ac analysis

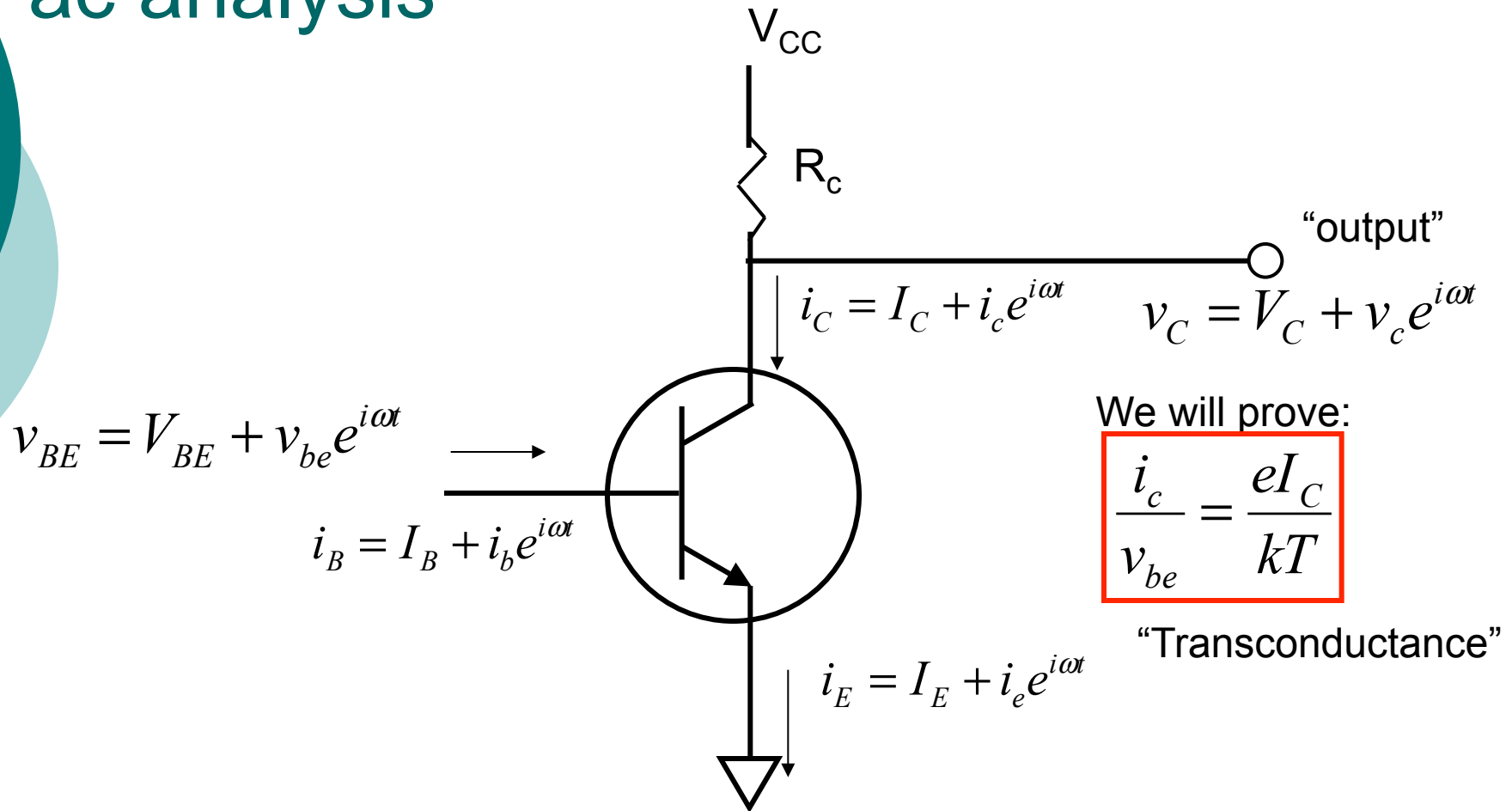

Note: three terminal device has three-terminal equivalent ac circuit.

Transconductance

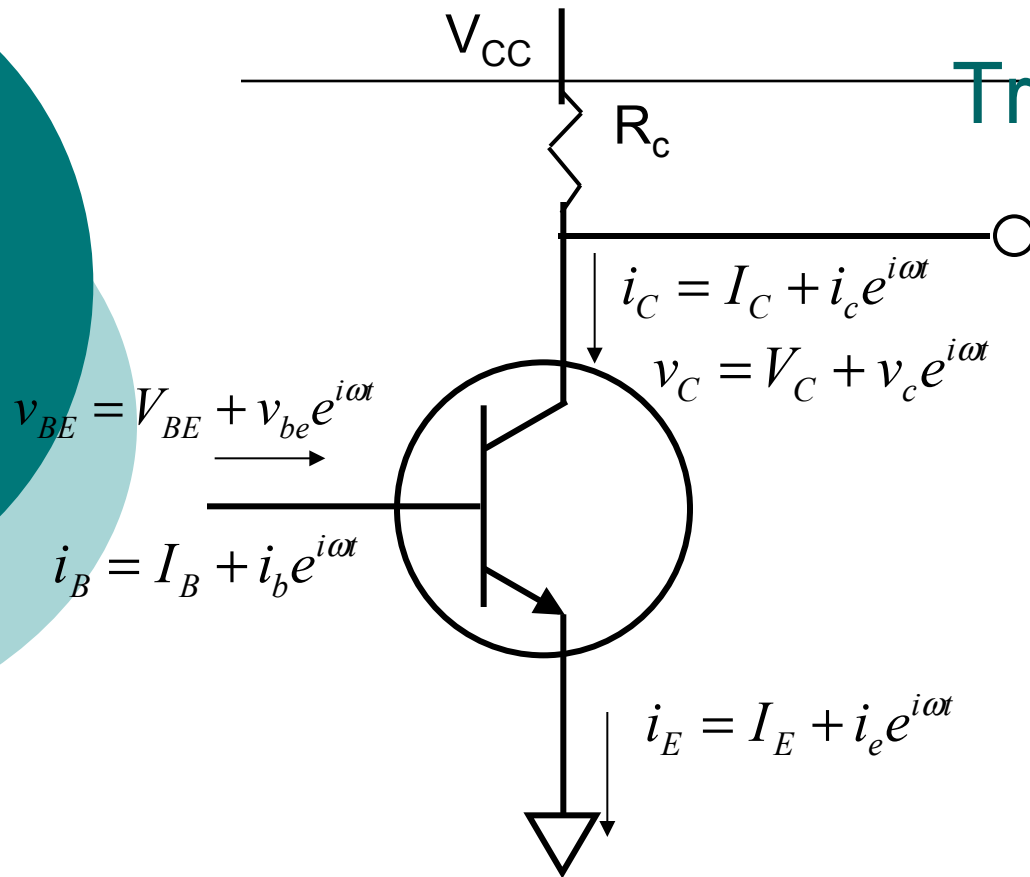

$$v_{BE} = V_{BE} + v_{be} e^{i\omega t}$$

$$i_C = I_S e^{e v_{BE} / kT}$$

$$= I_S e^{e(V_{BE} + v_{be} e^{i\omega t}) / kT}$$

$$= I_S e^{e V_{BE} / kT} e^{e v_{be} e^{i\omega t} / kT}$$

$$= I_C e^{e v_{be} e^{i\omega t} / kT}$$

$$e^x \approx 1 + x \text{ for small } x$$

$$i_C \approx I_C \left(1 + \frac{e v_{be}}{kT} e^{i\omega t} \right)$$

But

$$i_C = I_C + i_c e^{i\omega t}$$


So

$$i_c = I_C \frac{e v_{be}}{kT} \Rightarrow \frac{i_c}{v_{be}} = \frac{e I_C}{kT}$$

Typical number is 40 mA/V.

g_m

Input impedance

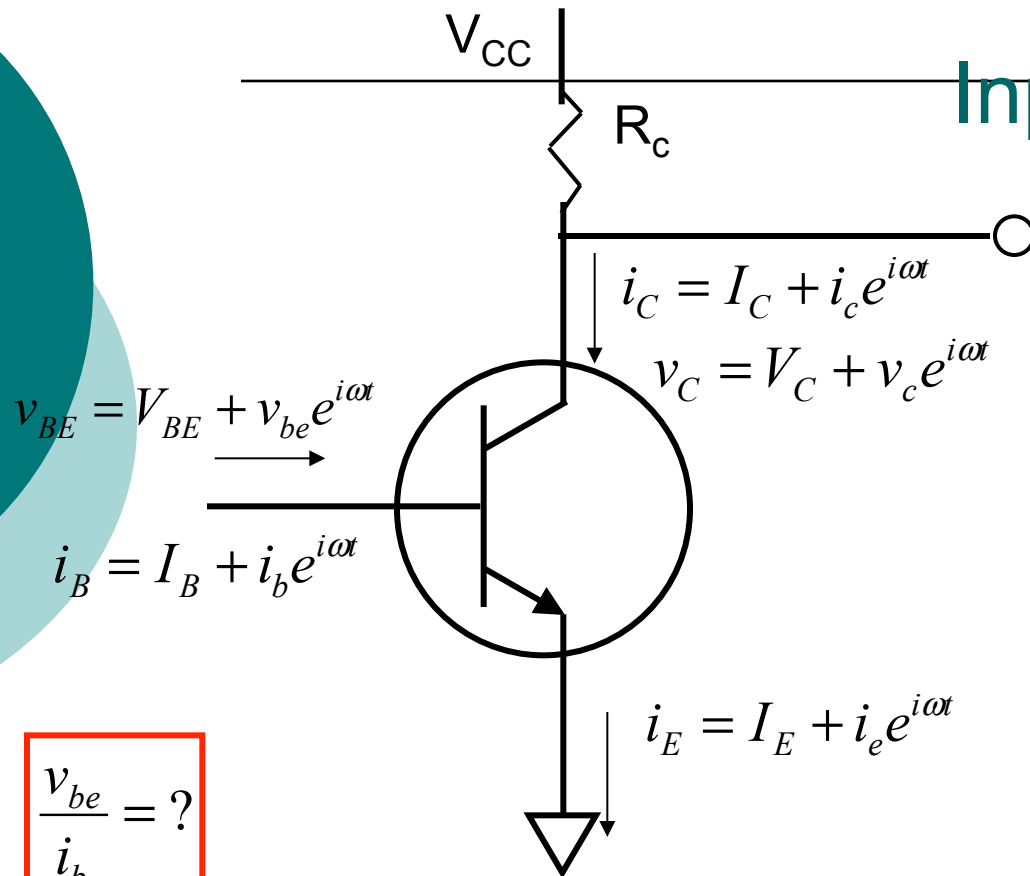

$$\frac{v_{be}}{i_b} = ?$$

$$i_B = \frac{i_C}{\beta} = \frac{I_C + i_c e^{i\omega t}}{\beta} = \frac{I_C}{\beta} + \frac{1}{\beta} I_C \frac{e v_{be}}{kT} e^{i\omega t}$$

But

$$i_B = I_B + i_b e^{i\omega t}$$


So

$$i_b = \frac{1}{\beta} I_C \frac{e v_{be}}{kT} = \frac{g_m}{\beta} v_{be}$$

So

$$\frac{v_{be}}{i_b} = \frac{g_m}{\beta}$$

What is typical input impedance?

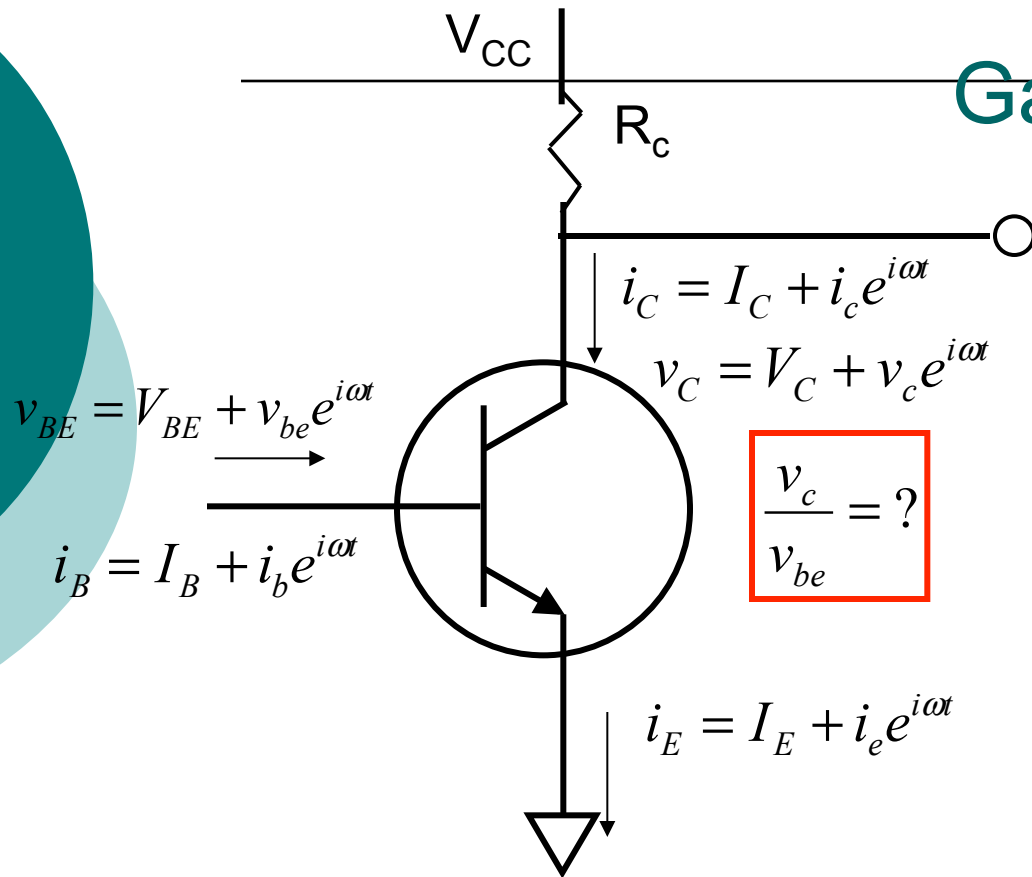

Gain

$$\begin{aligned}
 v_C &= V_{CC} - i_C R_C \\
 &= V_{CC} - (I_C + i_c e^{i\omega t}) R_C \\
 &= (V_{CC} - I_C R_C) + i_c R_C e^{i\omega t} \\
 &= V_C + i_c R_C e^{i\omega t}
 \end{aligned}$$

Bu

$$v_C = V_C + v_c e^{i\omega t}$$

So

:


$$v_c = -i_c R_C = -g_m v_{be} R_C$$

So

$$\frac{v_c}{v_{be}} = g_m R_C$$

What is typical gain?

Summary

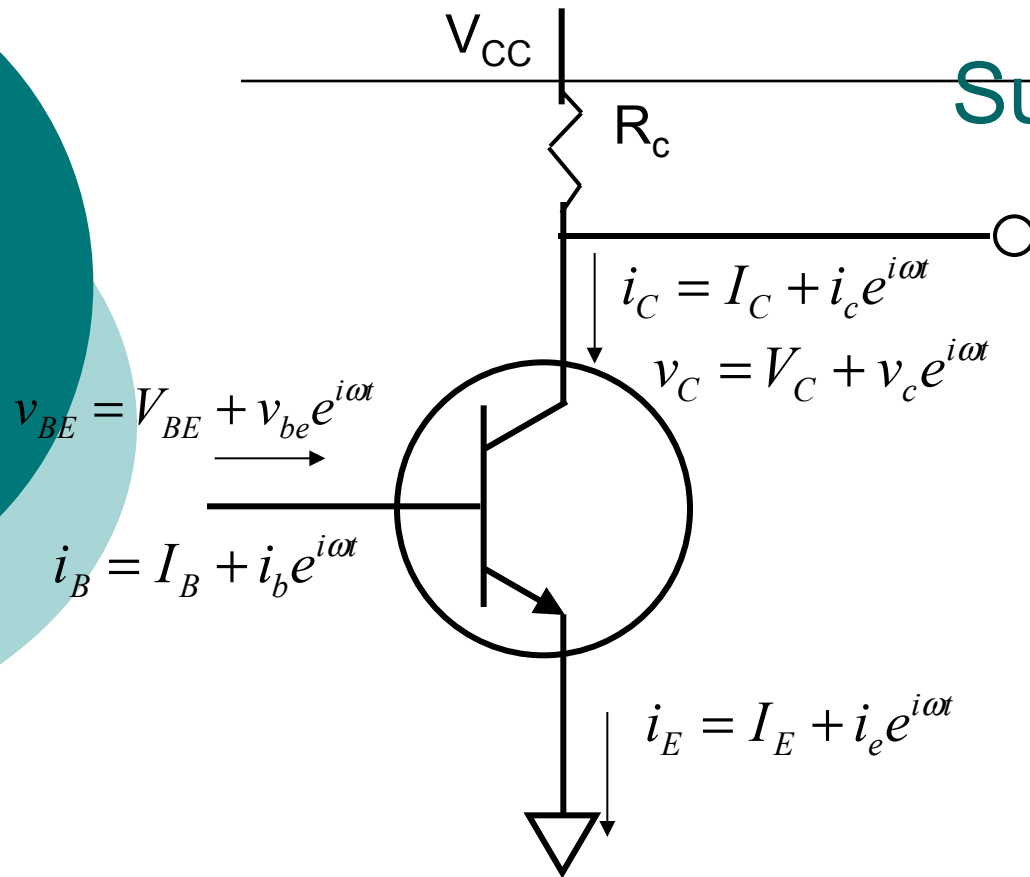

$$i_b = \frac{g_m}{\beta} v_{be}$$

input imp.

$$i_c = \frac{eI_C}{kT} v_{be}$$

transcond.

In *matrix* form:


$$\begin{pmatrix} i_b \\ i_c \end{pmatrix} = \begin{pmatrix} \frac{g_m}{\beta} & 0 \\ \frac{eI_C}{kT} & 0 \end{pmatrix} \begin{pmatrix} v_{be} \\ v_c \end{pmatrix}$$




Admittance (Y) *matrix*

AC equivalent circuit:

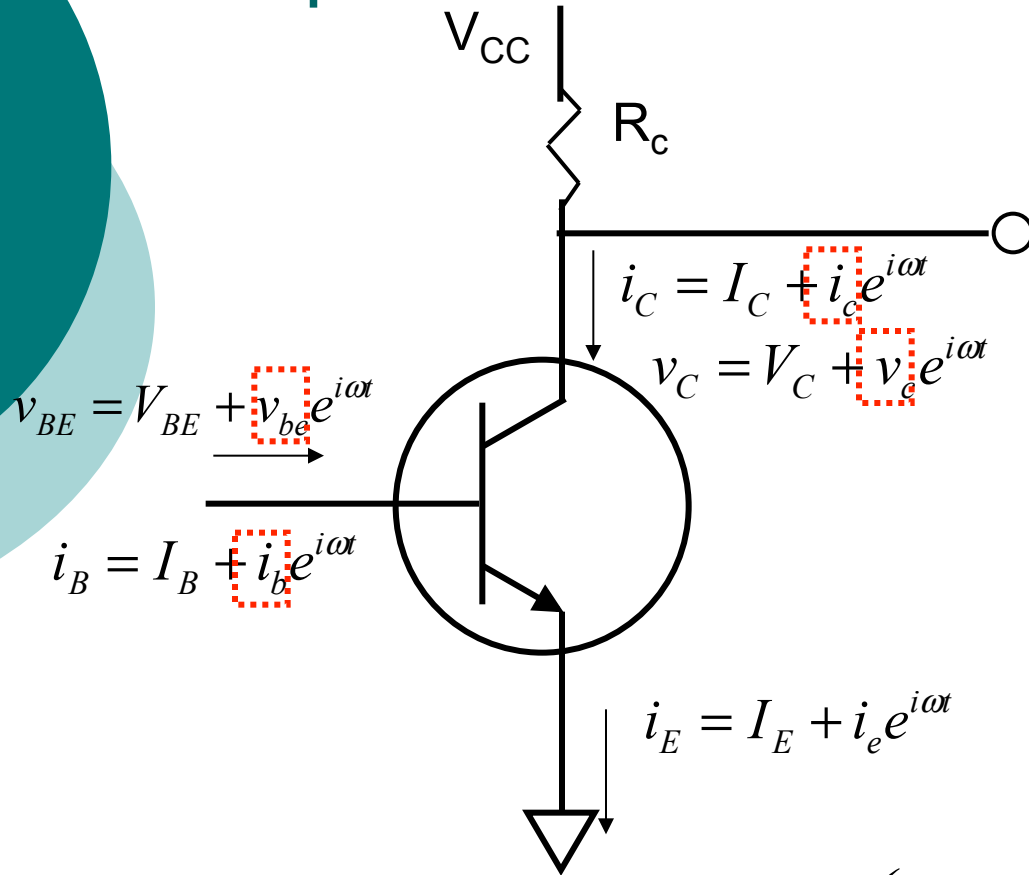If we are only interested in ac components, life can be simplified:




Hybrid π model:

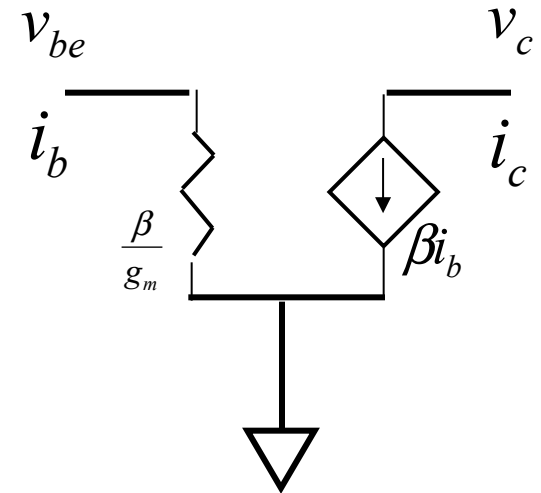


$$\begin{pmatrix} i_b \\ i_c \end{pmatrix} = \begin{pmatrix} \frac{g_m}{\beta} & 0 \\ \frac{eI_C}{kT} & 0 \end{pmatrix} \begin{pmatrix} v_{be} \\ v_c \end{pmatrix}$$

T model

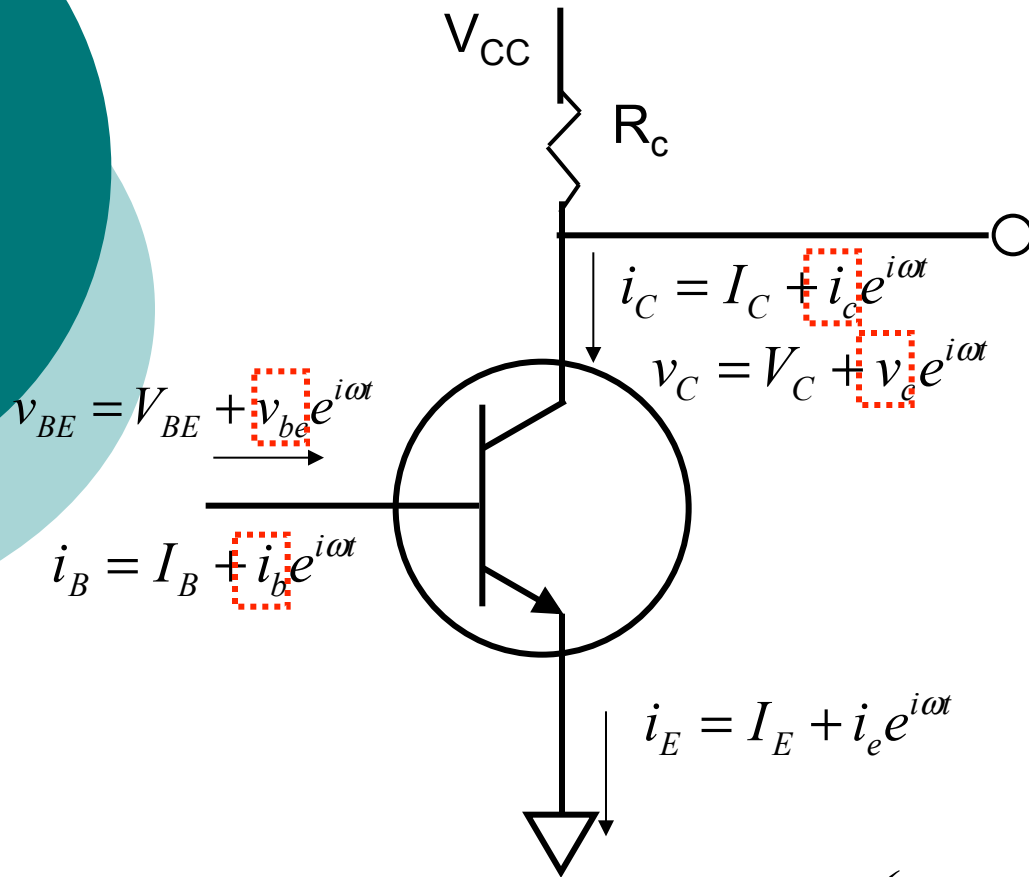If we are only interested in ac components, life can be simplified:



T model:

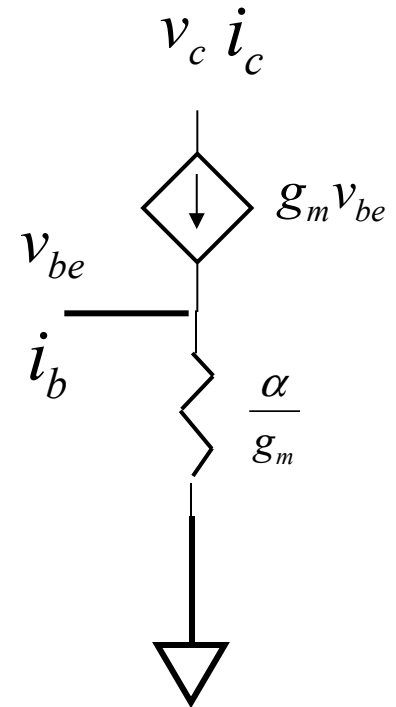

$$\begin{pmatrix} i_b \\ i_c \end{pmatrix} = \begin{pmatrix} \frac{g_m}{\beta} & 0 \\ \frac{eI_C}{kT} & 0 \end{pmatrix} \begin{pmatrix} v_{be} \\ v_c \end{pmatrix}$$

Rules for ac analysis


- From complete circuit, calculate dc currents and voltages
- For ac analysis only:
 - dc voltage source -> short circuit
 - dc current source -> open circuit
- Replace transistor with μ or T-model
- Now solve (simplified) ac circuit

Next


- Generalized y -parameters
- not just common emitters
- Capacitances
- y -parameters from doping profile
- Definition of f_T

AC equivalent circuit:

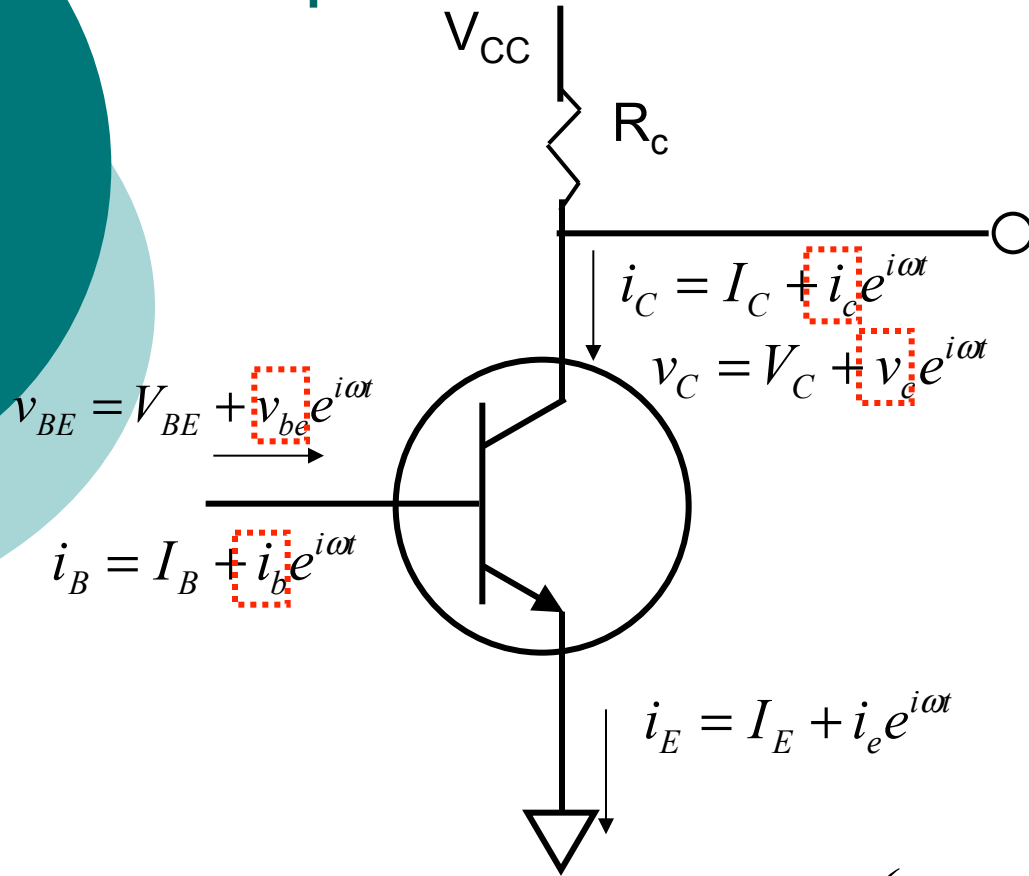If we are only interested in ac components, life can be simplified:



Hybrid π model:

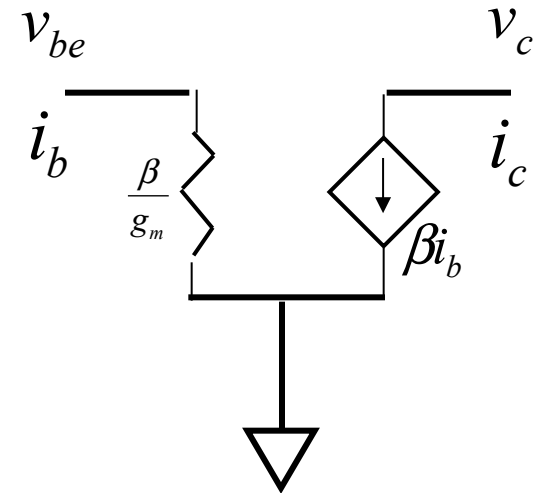

$$\begin{pmatrix} i_b \\ i_c \end{pmatrix} = \begin{pmatrix} \frac{g_m}{\beta} & 0 \\ \frac{eI_C}{kT} & 0 \end{pmatrix} \begin{pmatrix} v_{be} \\ v_c \end{pmatrix}$$

Discuss easy interpretation of π model.

General admittance matrix


Last lecture, we had emitter grounded.

Called common emitter configuration:

$$\begin{pmatrix} i_b \\ i_c \end{pmatrix} = \begin{pmatrix} \frac{g_m}{\beta} & 0 \\ \frac{eI_C}{kT} & 0 \end{pmatrix} \begin{pmatrix} v_{be} \\ v_c \end{pmatrix}$$

In general:
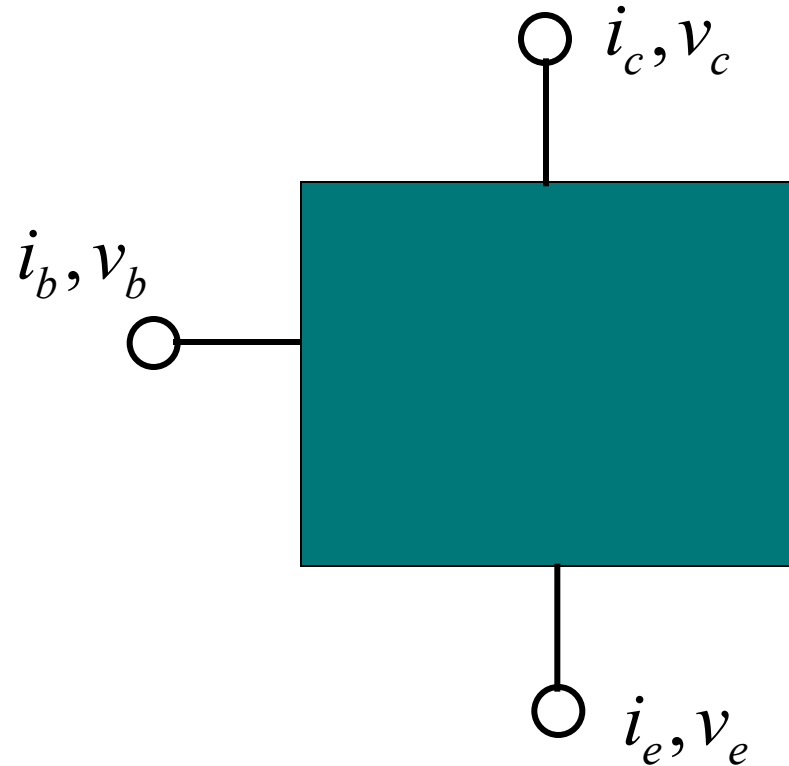
$$\begin{pmatrix} i_e \\ i_b \\ i_c \end{pmatrix} = \begin{pmatrix} \cdot & \cdot & \cdot \\ \cdot & \cdot & \cdot \\ \cdot & \cdot & \cdot \end{pmatrix} \begin{pmatrix} v_e \\ v_b \\ v_c \end{pmatrix}$$



Y-matrix has 9 elements, but once you know 4 you know them all because:

$$i_e = i_b + i_c$$

and:

$$v_{cb} + v_{be} = v_{ce}$$

See book about details procedure to get 9 parameters from only 4.

Three configurations:

Common emitter configuration ($v_e=0$):

$$\begin{pmatrix} i_b \\ i_c \end{pmatrix} = \begin{pmatrix} y_{bb} & y_{bc} \\ y_{cb} & y_{cc} \end{pmatrix} \begin{pmatrix} v_b \\ v_c \end{pmatrix} = [y]_e \begin{pmatrix} v_b \\ v_c \end{pmatrix}$$

Common base configuration ($v_b=0$):

$$\begin{pmatrix} i_e \\ i_c \end{pmatrix} = \begin{pmatrix} y_{ee} & y_{ec} \\ y_{ce} & y_{cc} \end{pmatrix} \begin{pmatrix} v_e \\ v_c \end{pmatrix} = [y]_b \begin{pmatrix} v_e \\ v_c \end{pmatrix}$$



Easiest to calculate from doping profile.


Common collector configuration ($v_c=0$):

$$\begin{pmatrix} i_b \\ i_e \end{pmatrix} = \begin{pmatrix} y_{bb} & y_{be} \\ y_{eb} & y_{ee} \end{pmatrix} \begin{pmatrix} v_b \\ v_e \end{pmatrix} = [y]_c \begin{pmatrix} v_b \\ v_e \end{pmatrix}$$

Generalized ρ model:

Regardless of which configuration you use, the following ρ model applies:
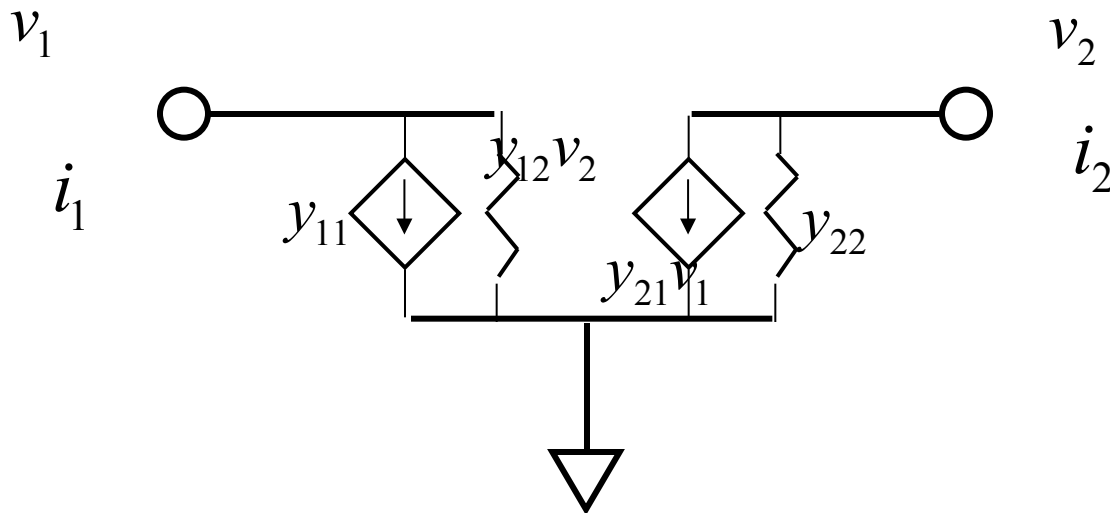
$$\begin{pmatrix} i_1 \\ i_2 \end{pmatrix} = \begin{pmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{pmatrix} \begin{pmatrix} v_1 \\ v_2 \end{pmatrix}$$



Common emitter: 1=base, 2=collector

Common base: 1=emitter, 2=collector


Common collector: 1=base, 2= emitter



You might be used to
 $V=IR$

General impedance matrix
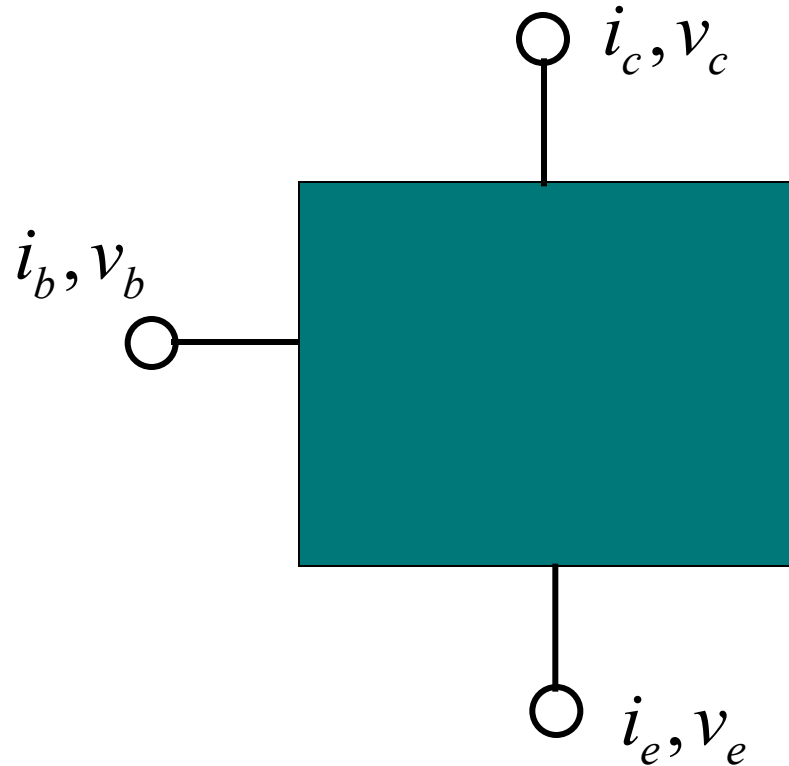
$$\begin{pmatrix} v_e \\ v_b \\ v_c \end{pmatrix} = \begin{pmatrix} \cdot & \cdot & \cdot \\ \cdot & \cdot & \cdot \\ \cdot & \cdot & \cdot \end{pmatrix} \begin{pmatrix} i_e \\ i_b \\ i_c \end{pmatrix}$$



Y-matrix has 9 elements, but once you know 4 you know them all because:

h matrix:

$$\begin{pmatrix} v_1 \\ i_2 \end{pmatrix} = \begin{pmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{pmatrix} \begin{pmatrix} i_1 \\ v_2 \end{pmatrix}$$

Common emitter: 1=base, 2=collector

Common base: 1=emitter, 2=collector

Common collector: 1=base, 2= emitter

Note: In general, matrix elements depend on dc currents, dc voltages, and frequency. Spec. sheet (or model) will provide the matrix elements as a table vs. frequency, usually for only one bias current.

Common emitter h matrix:

$$\begin{pmatrix} v_b \\ i_c \end{pmatrix} = \begin{pmatrix} h_{11e} & h_{12e} \\ h_{21e} & h_{22e} \end{pmatrix} \begin{pmatrix} i_b \\ v_c \end{pmatrix}$$

- Early effect:

Collector voltage changes current gain (β).


- β depends on frequency *and* collector voltage.
- How do we define frequency at which $\beta = 1$?
- At $v_c = 0$. This is h_{21e}

$$i_c = h_{21e} i_b + h_{22e} v_c \rightarrow h_{21e} i_b$$


- We define f_T such that:

$$|h_{21e}(f_T)| = 1$$

AC equivalent circuit:

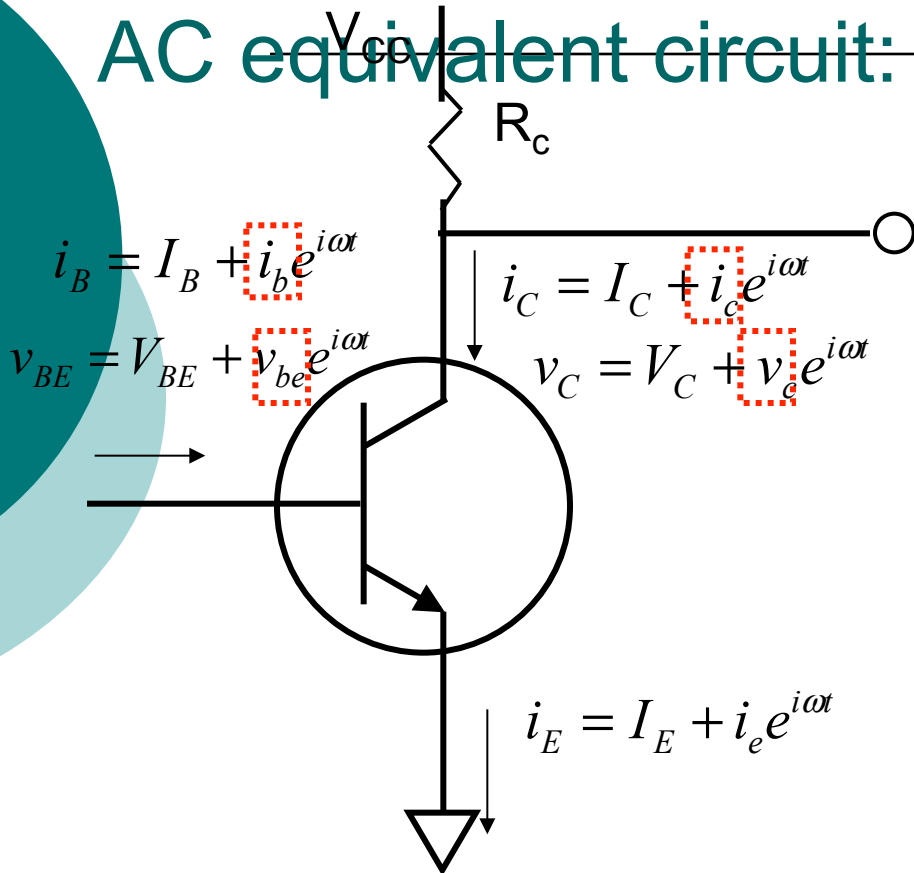

Hybrid π model:
Red is new for ac:

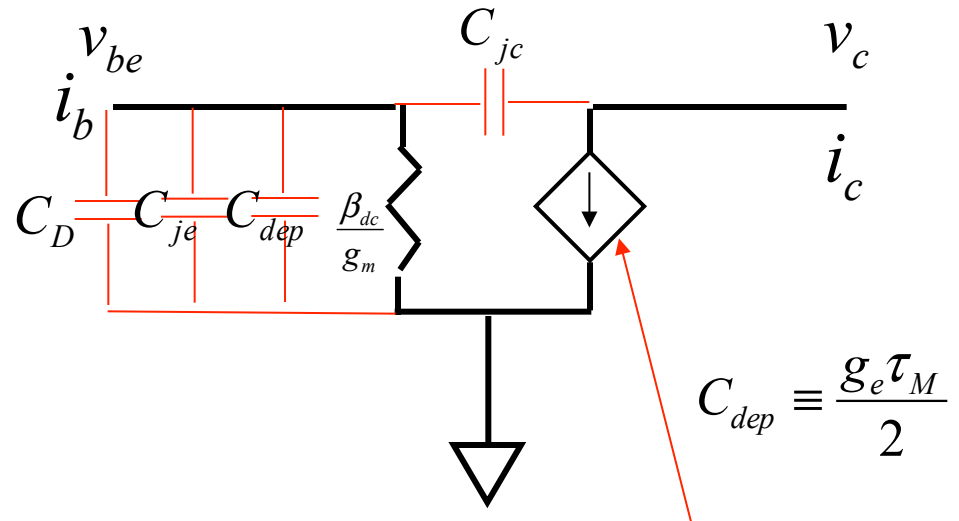


$$C_{dep} \equiv \frac{g_e \tau_M}{2}$$


$$\left(1 - \frac{X_B^2}{2L_n^2}\right) g_e \left[1 - i \frac{\omega}{3\omega_0}\right] e^{\omega\tau_M/2} v_{be}$$

- Circuit model good only for low frequencies
- At high frequencies computer must be used!
- That concludes our derivation of intrinsic HBT behavior.
- Next will include parasitics, and discuss f_T , f_{max}

Goal for today:

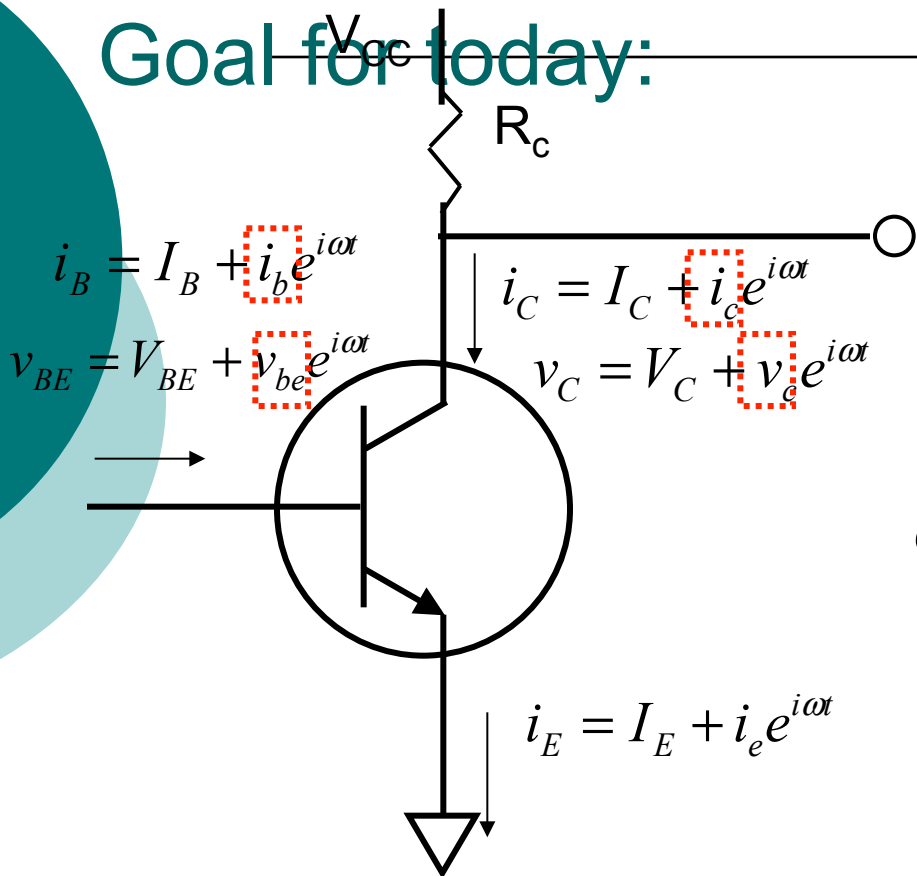

Hybrid π model:
Red is new for ac:

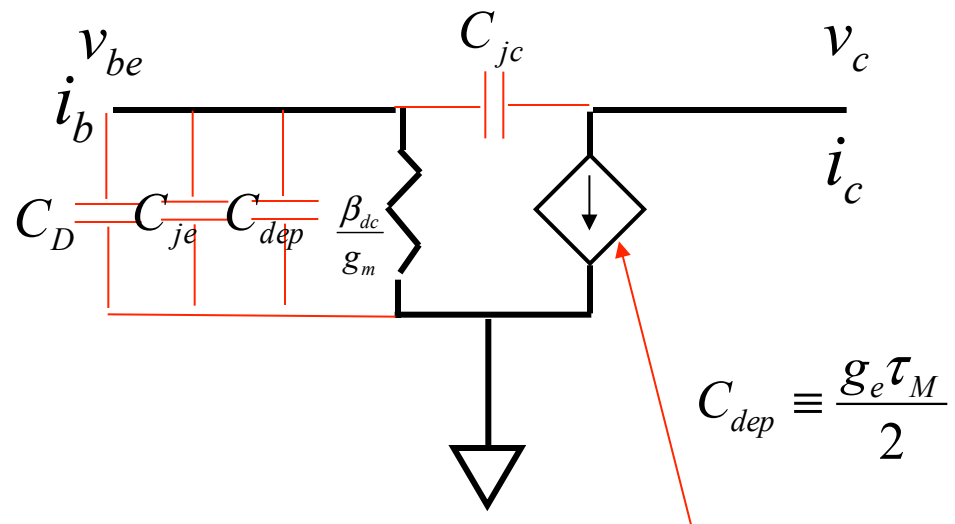


$$\left(1 - \frac{X_B^2}{2L_n^2}\right) g_e \left[1 - i \frac{\omega}{3\omega_0}\right] e^{\omega\tau_M/2} v_{be}$$


Parasitics

f_T , f_{max}

Common-Emitter AC equivalent circuit:

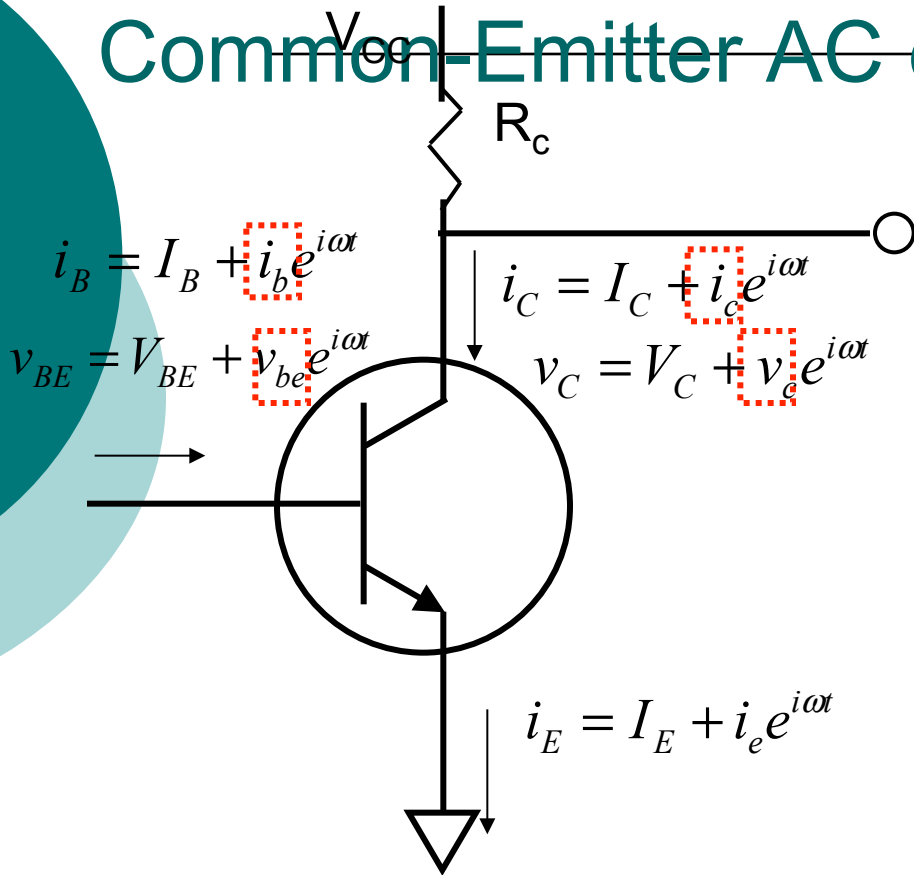

Hybrid p model:
Red is new for ac:

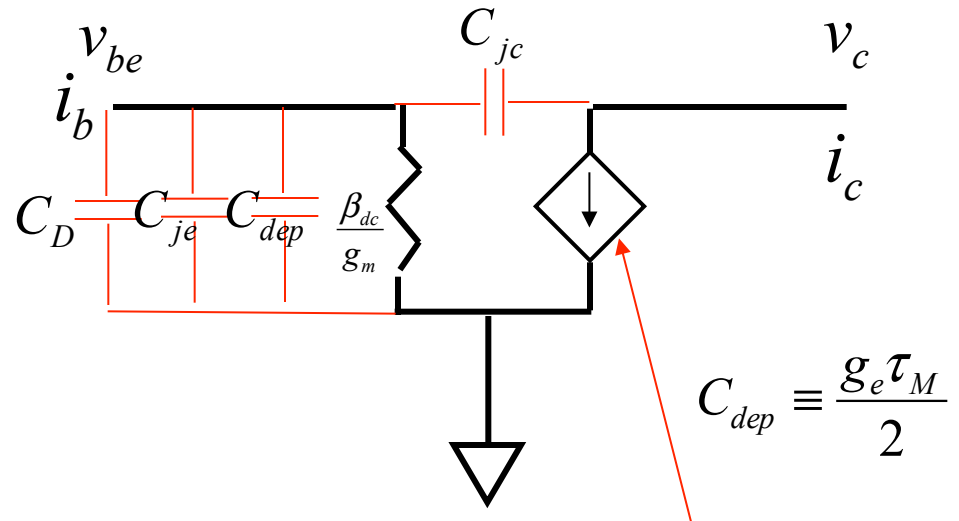



$$\left(1 - \frac{X_B^2}{2L_n^2}\right) g_e \left[1 - i \frac{\omega}{3\omega_0}\right] e^{\omega\tau_M/2} v_{be}$$

- Circuit model good only for low frequencies
- At high frequencies computer must be used!

Hybrid π model:

simplified:

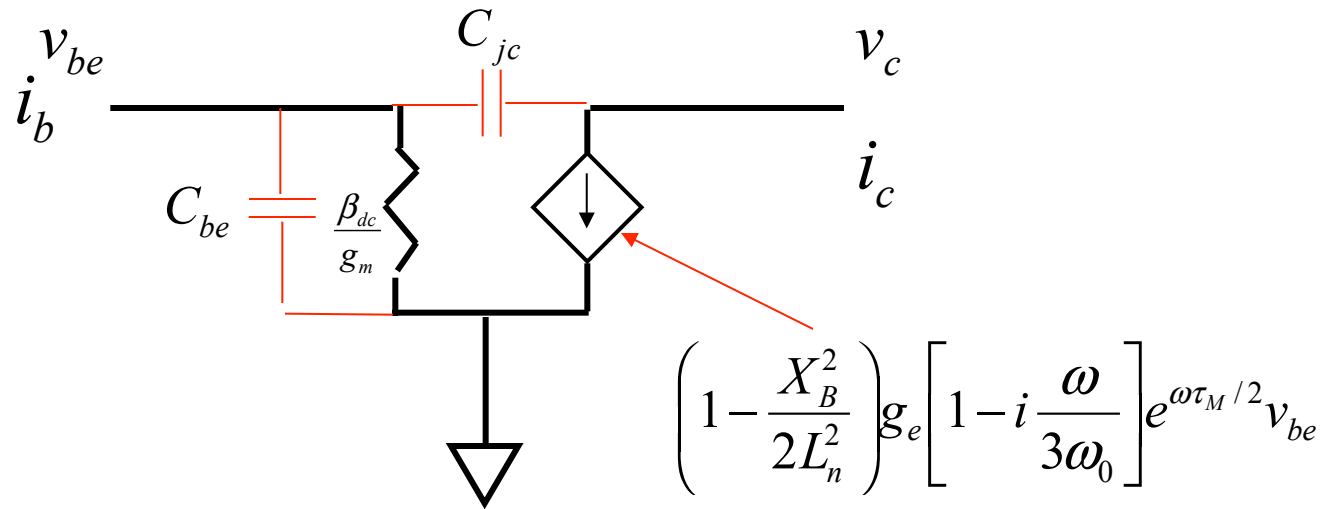

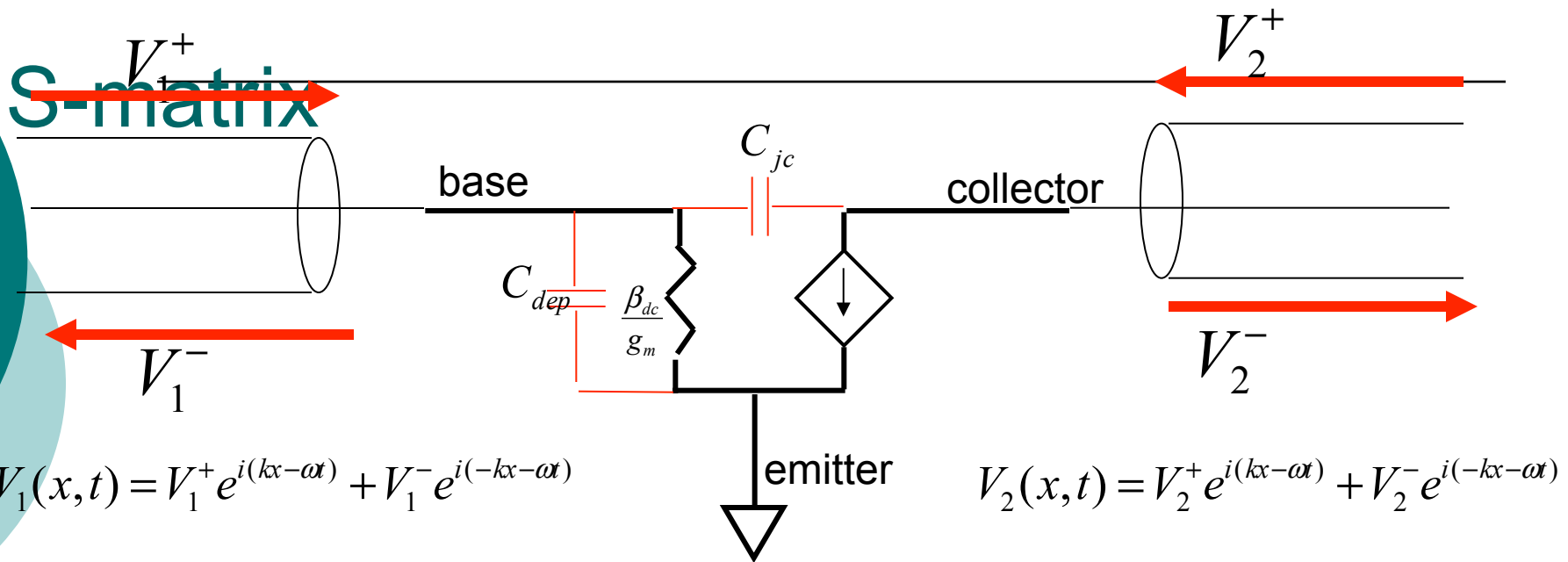

$$\begin{pmatrix} V_1^- \\ V_2^- \end{pmatrix} = \begin{pmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{pmatrix} \begin{pmatrix} V_1^+ \\ V_2^+ \end{pmatrix}$$

$$V_1^- = S_{11} V_1^+ + S_{12} V_2^+$$

$$V_2^- = S_{21} V_1^+ + S_{22} V_2^+$$


S-parameters

TOSHIBA


2SA1245

This is what you see on data sheets.
Related to input impedance, output impedance
and gain vs. frequency.
=> Need to discuss ac performance.

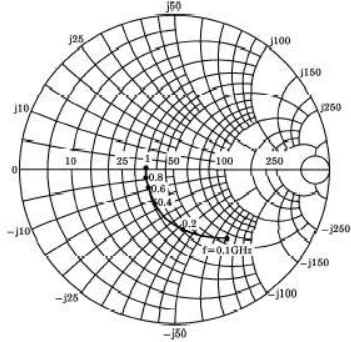
S_{11e}
 $V_{CE} = -5V$
 $I_C = -10mA$
 $T_a = 25^\circ C$
(UNIT : Ω)



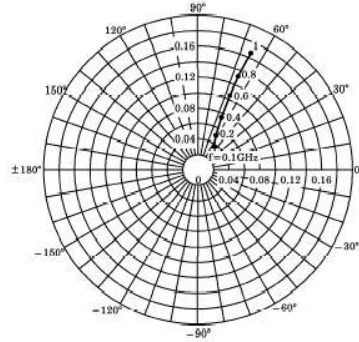
S_{12e}
 $V_{CE} = -5V$
 $I_C = -10mA$
 $T_a = 25^\circ C$



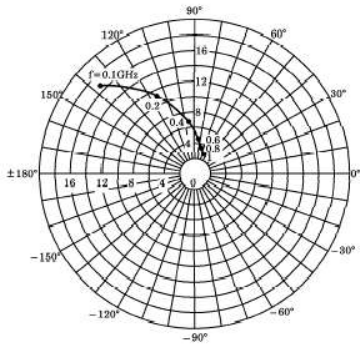S_{21e}
 $V_{CE} = -5V$
 $I_C = -10mA$
 $T_a = 25^\circ C$



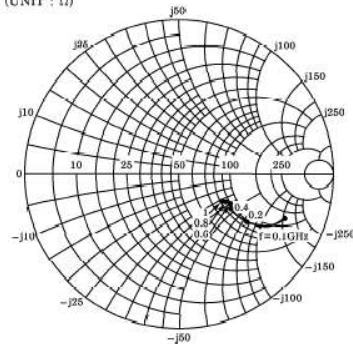S_{22e}
 $V_{CE} = -5V$
 $I_C = -10mA$
 $T_a = 25^\circ C$
(UNIT : Ω)




Summary of parameters


- Impedance matrix ($V=IR \rightarrow V=IZ$)
- Admittance matrix ($I=YV$)
- h-matrix (combination)
- ABCD matrix (combination)
- S-matrix (microwave reflections and transmissions)

“If you know one, then you know them all...”
See Liu, page 249 for conversions.

Measurement techniques

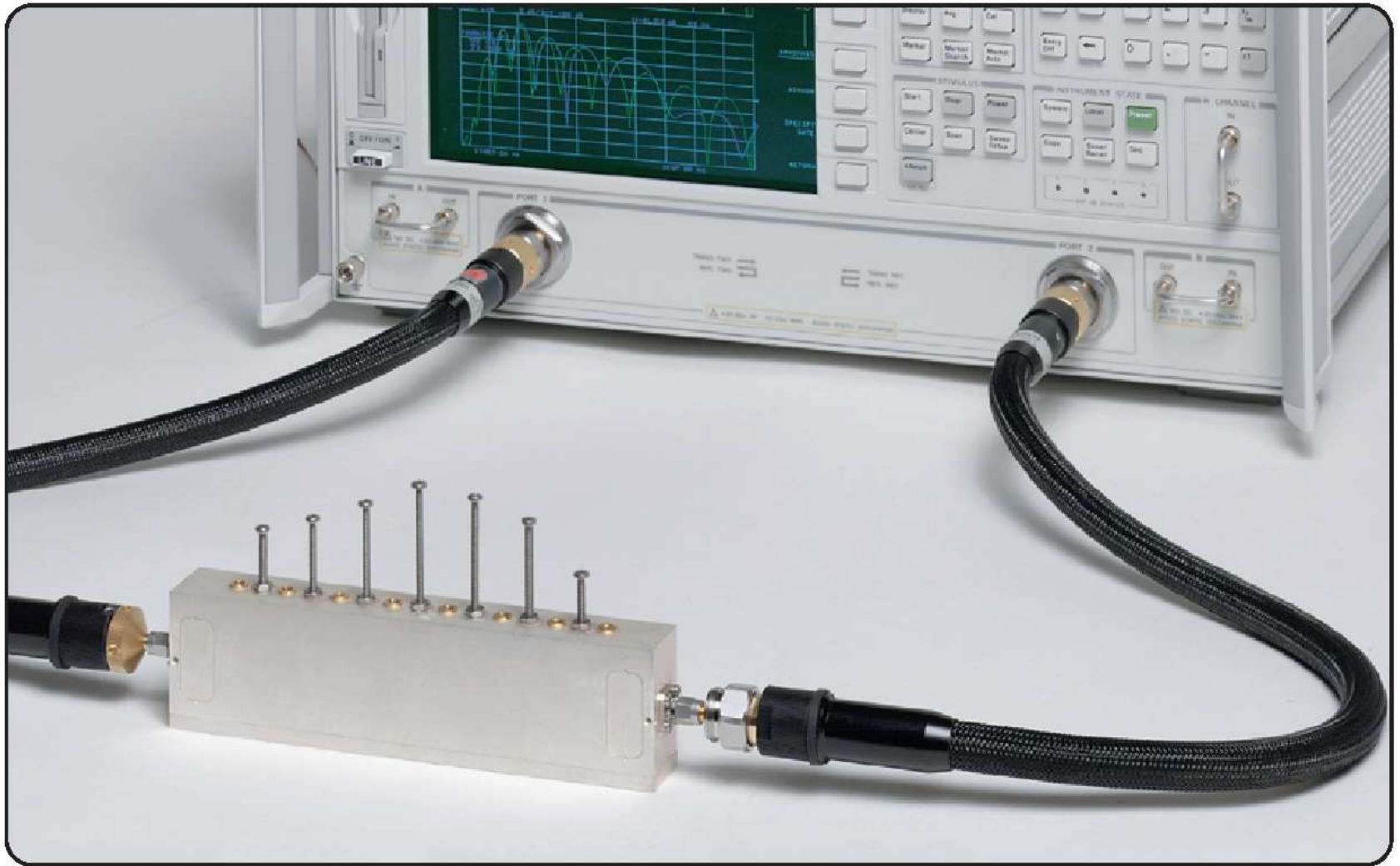

Nanotechnology

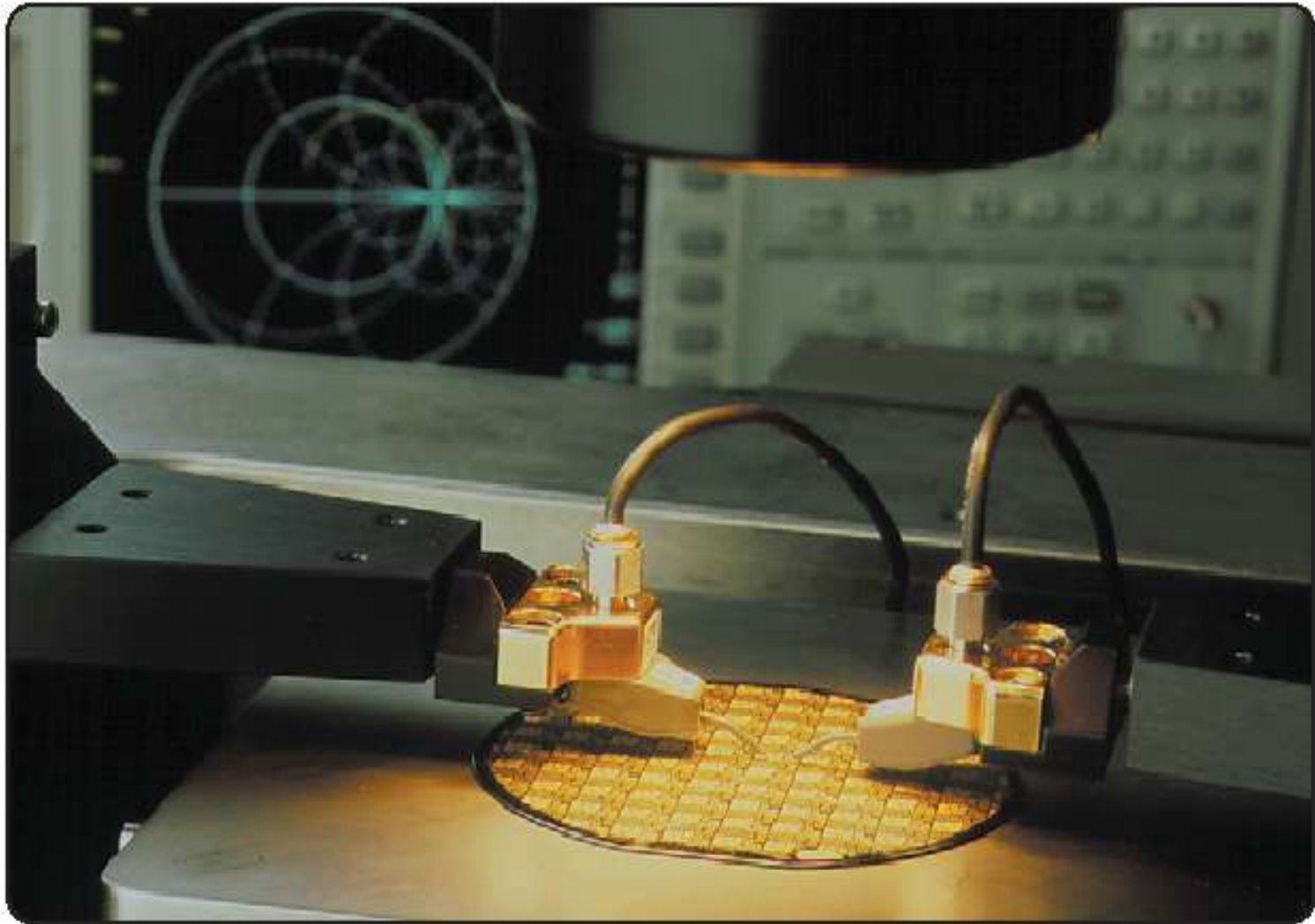

Cost (*rough estimates*)

- 10 GHz: \$50,000
- 20 GHz: \$70,000
- 40 GHz: \$90,000
- 110 GHz: \$250,000
- > 110 GHz: very expensive

For cost and difficulty reasons, parameters of transistor not always measure all the way up to f_T , but extrapolated.

These are only estimates. Contact vendor for actual prices.

Example



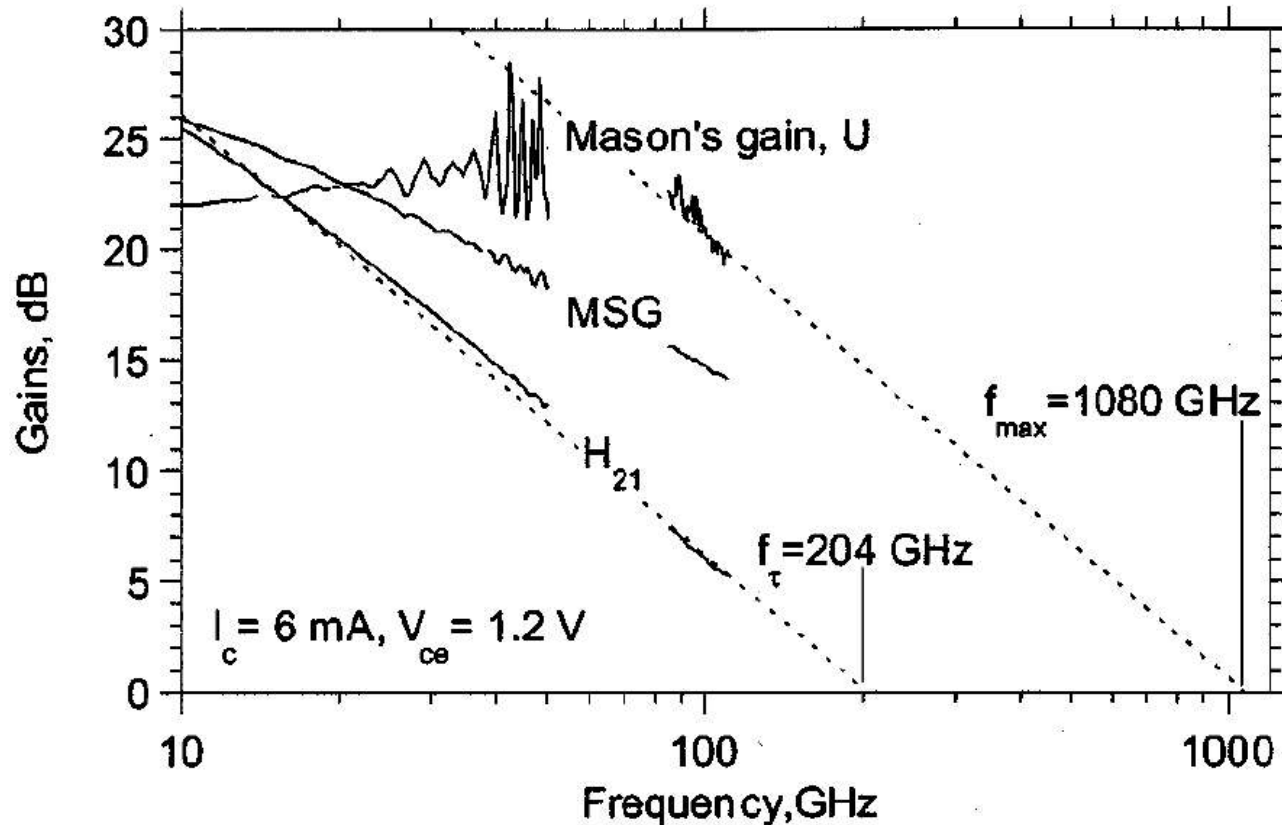


Fig. 14. Gains of a $0.4 \mu\text{m} \times 6 \mu\text{m}$ emitter and $0.7 \mu\text{m} \times 10 \mu\text{m}$ collector HBT fabricated using electron-beam lithography. Theoretical -20 dB/decade (H_{21} , U) gain slopes are indicated. The device exhibits an *extrapolated* 1.08 THz f_{\max} .

Parasitics:

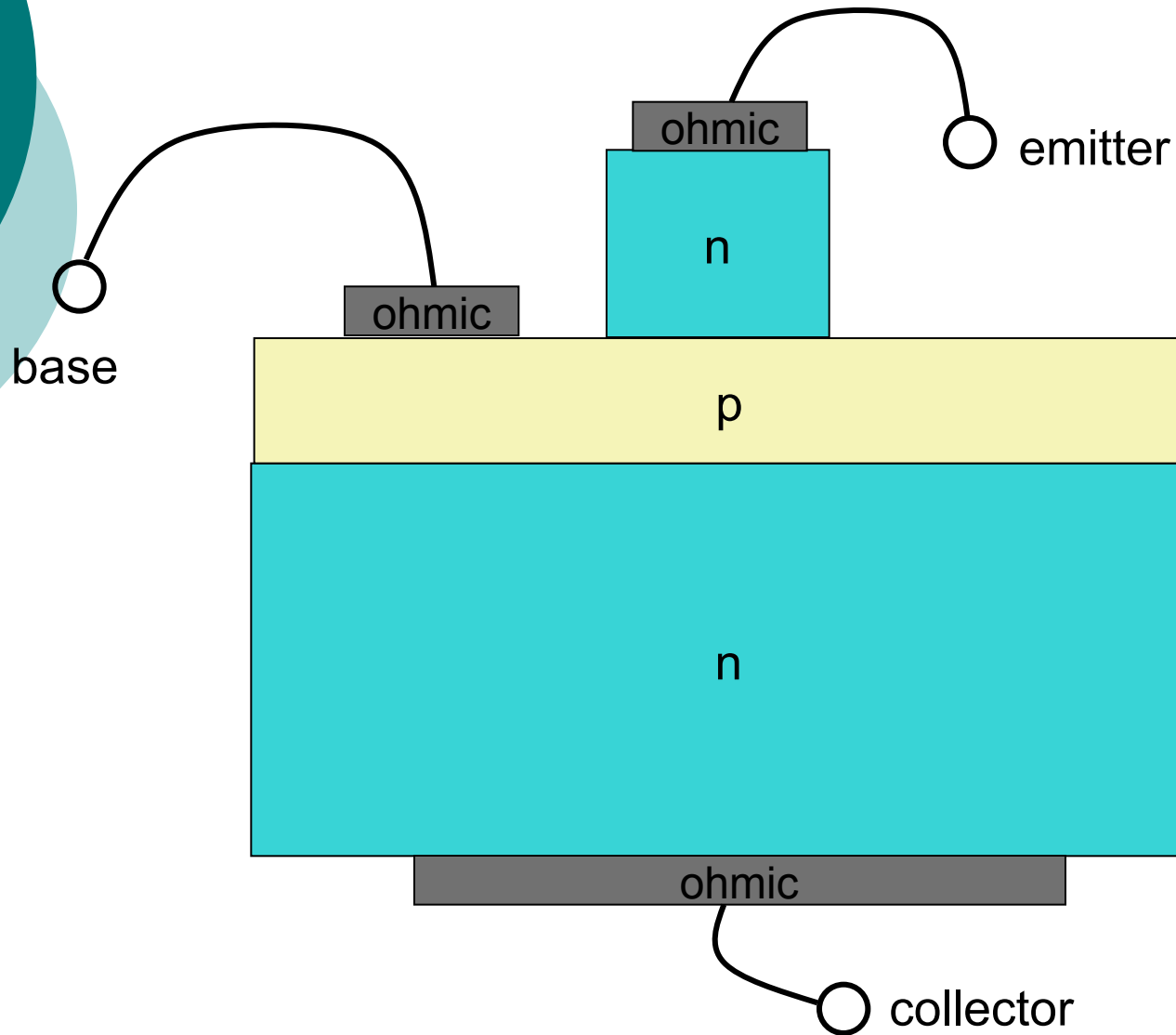

Parasitics:

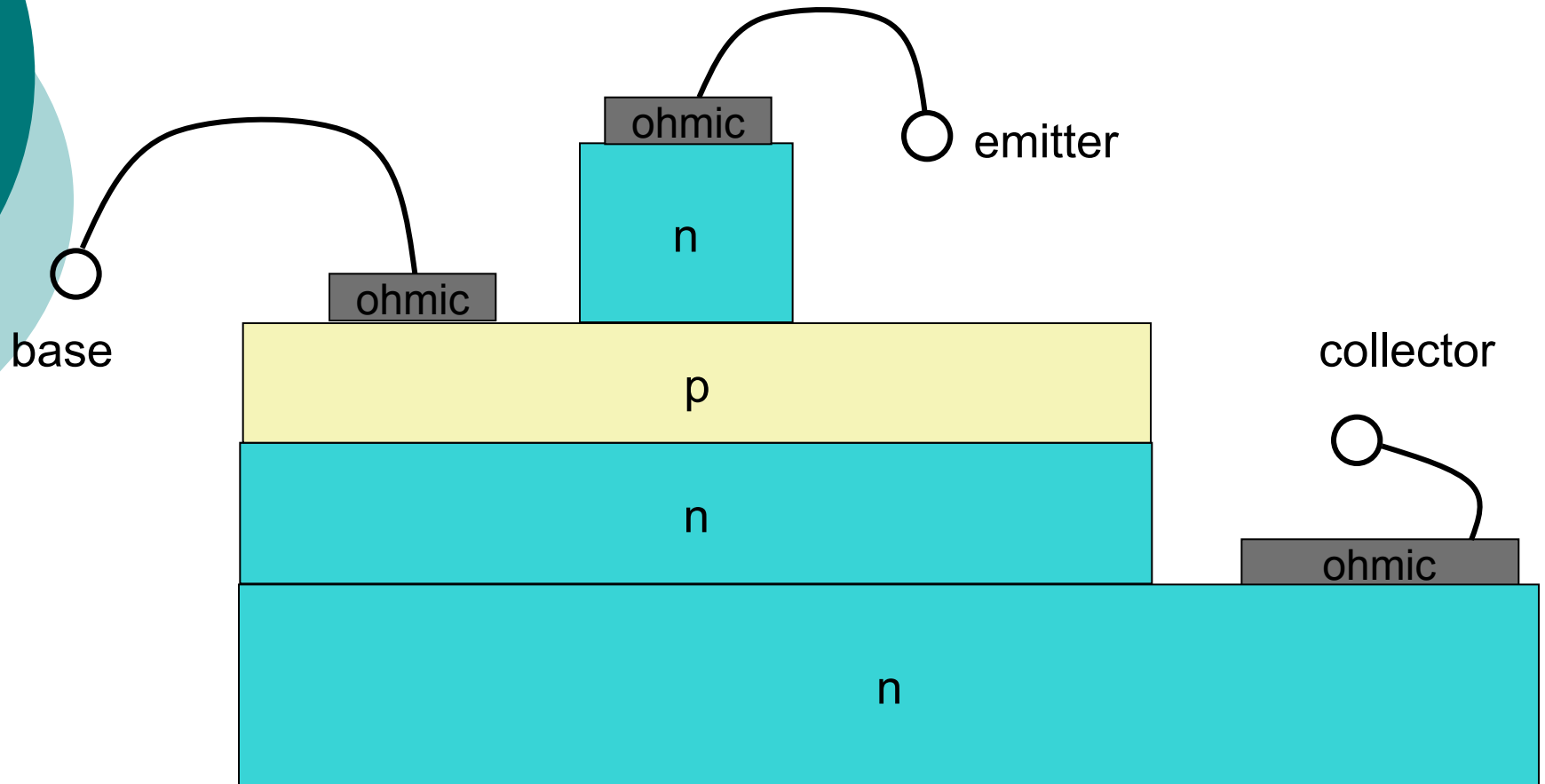

Ohmic contact

Specific contact resistance typically 10^{-6} ohm-micron²
(Discuss on board.)

$$R_{EE} = \frac{\rho_{\sigma E}}{A_E} = \frac{\rho_{\sigma E}}{L_E W_E}$$


For a distributed contact, things are a little more complicated.
(Draw distributed RC network on board, discuss.)

A solution is:

$$R_{BB} = \frac{\sqrt{R_{SHB} \rho_{\sigma B}}}{L_E} \coth \left(W_B \sqrt{\frac{R_{SHB}}{\rho_{\sigma B}}} \right)$$


R_{SHB} is R per square (discuss)

Emitter “epi” resistance:

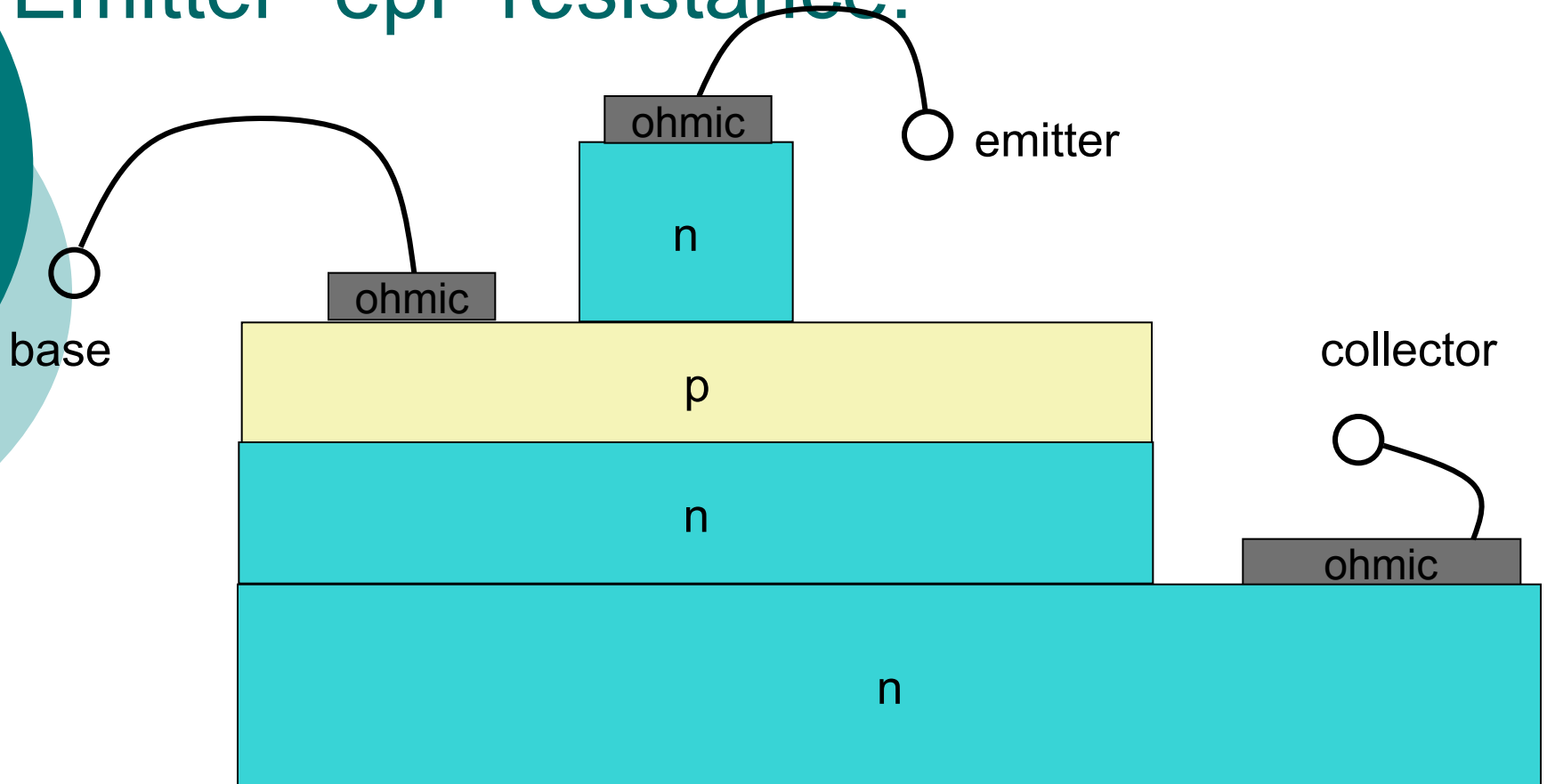


$$R_{E(epi)} = \rho_{E(epi)} \frac{X_{E(epi)}}{L_E W_E} \quad (\text{discuss})$$

Base “epi” resistance:

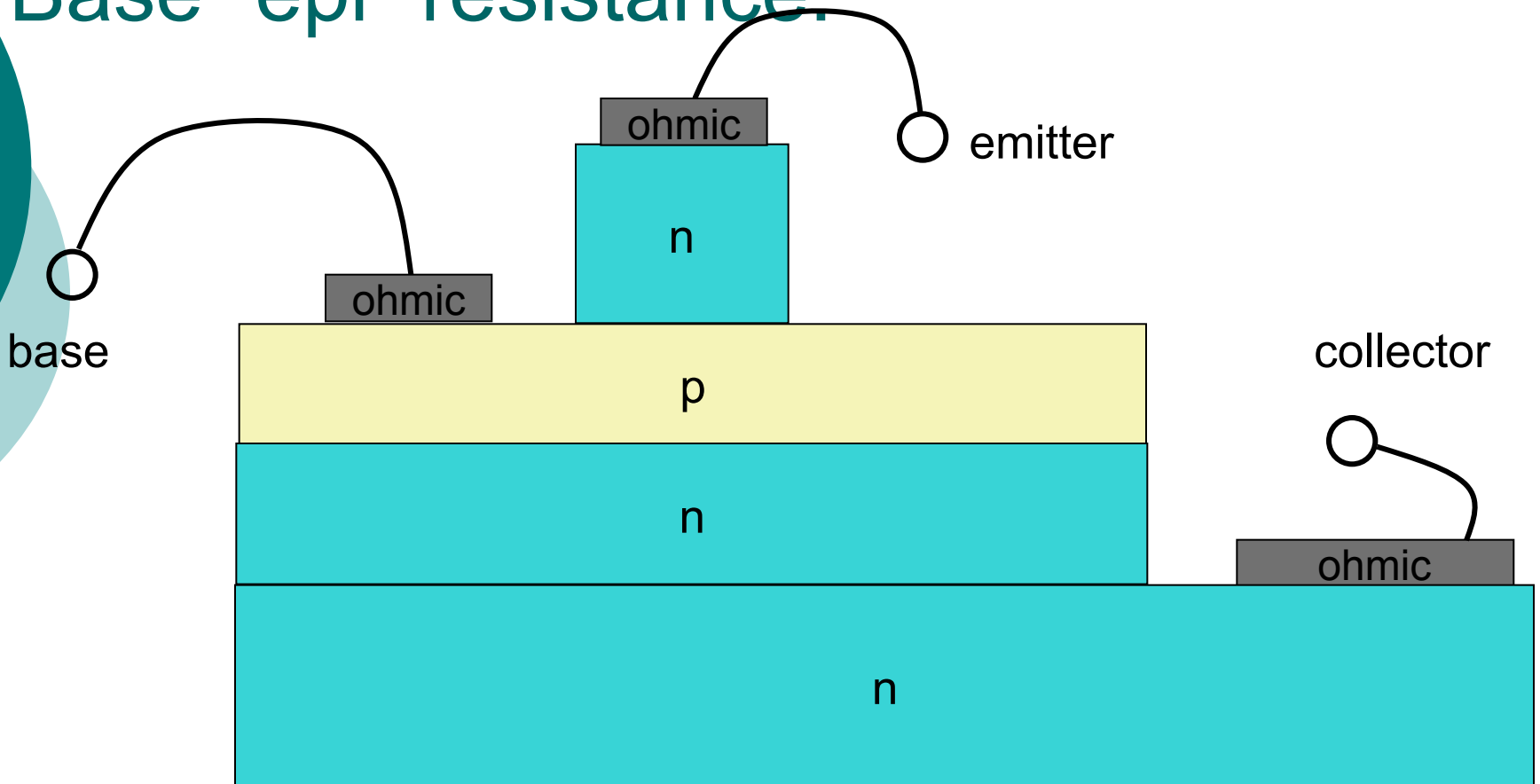


$$R_{Bx(epi)} \quad (\text{discuss})$$

Emitter “epi” resistance:

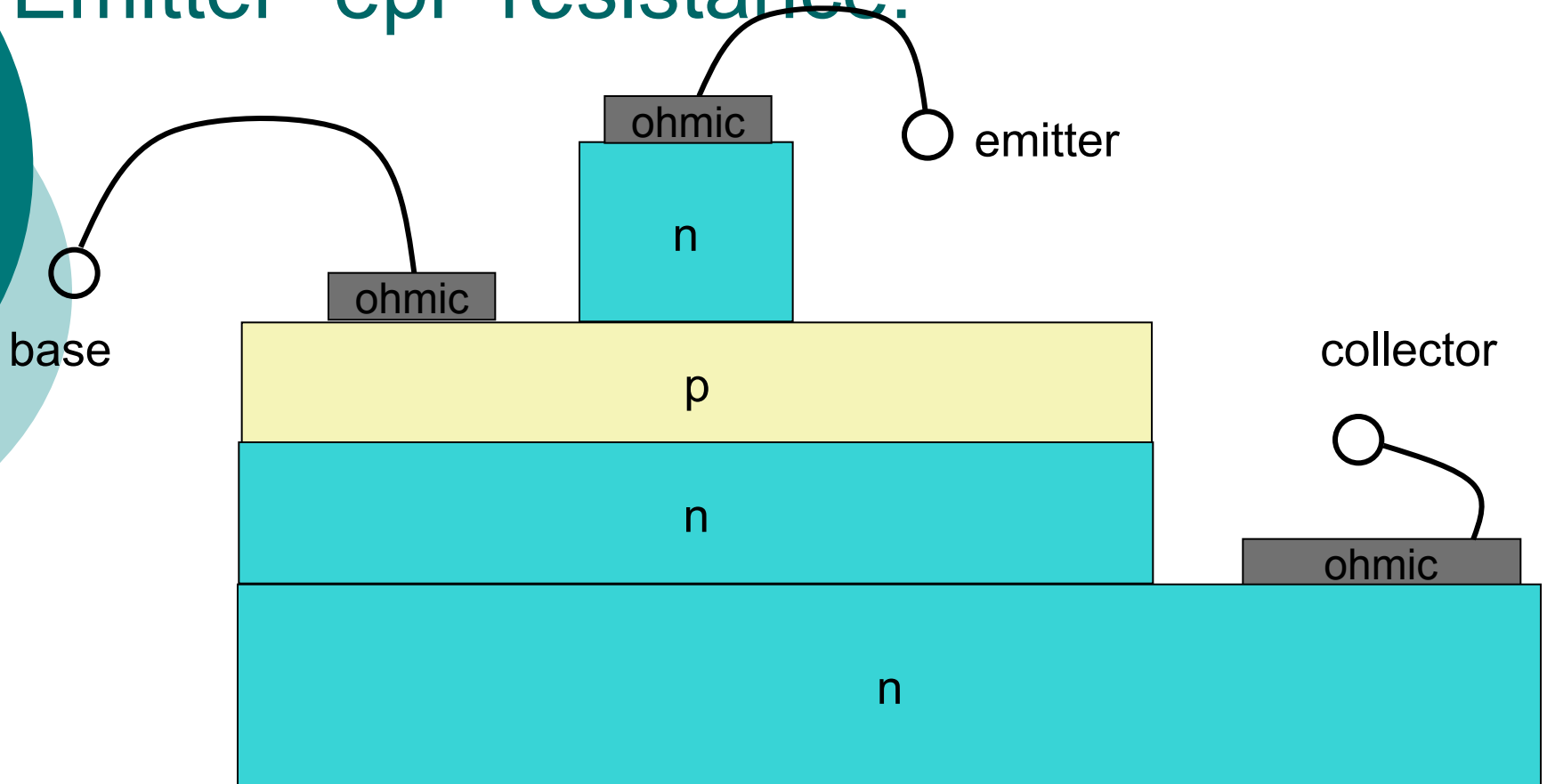

$$R_{E(epi)} = \rho_{E(epi)} \frac{X_{E(epi)}}{L_E W_E} \quad (\text{discuss})$$


Collector “epi” resistance:

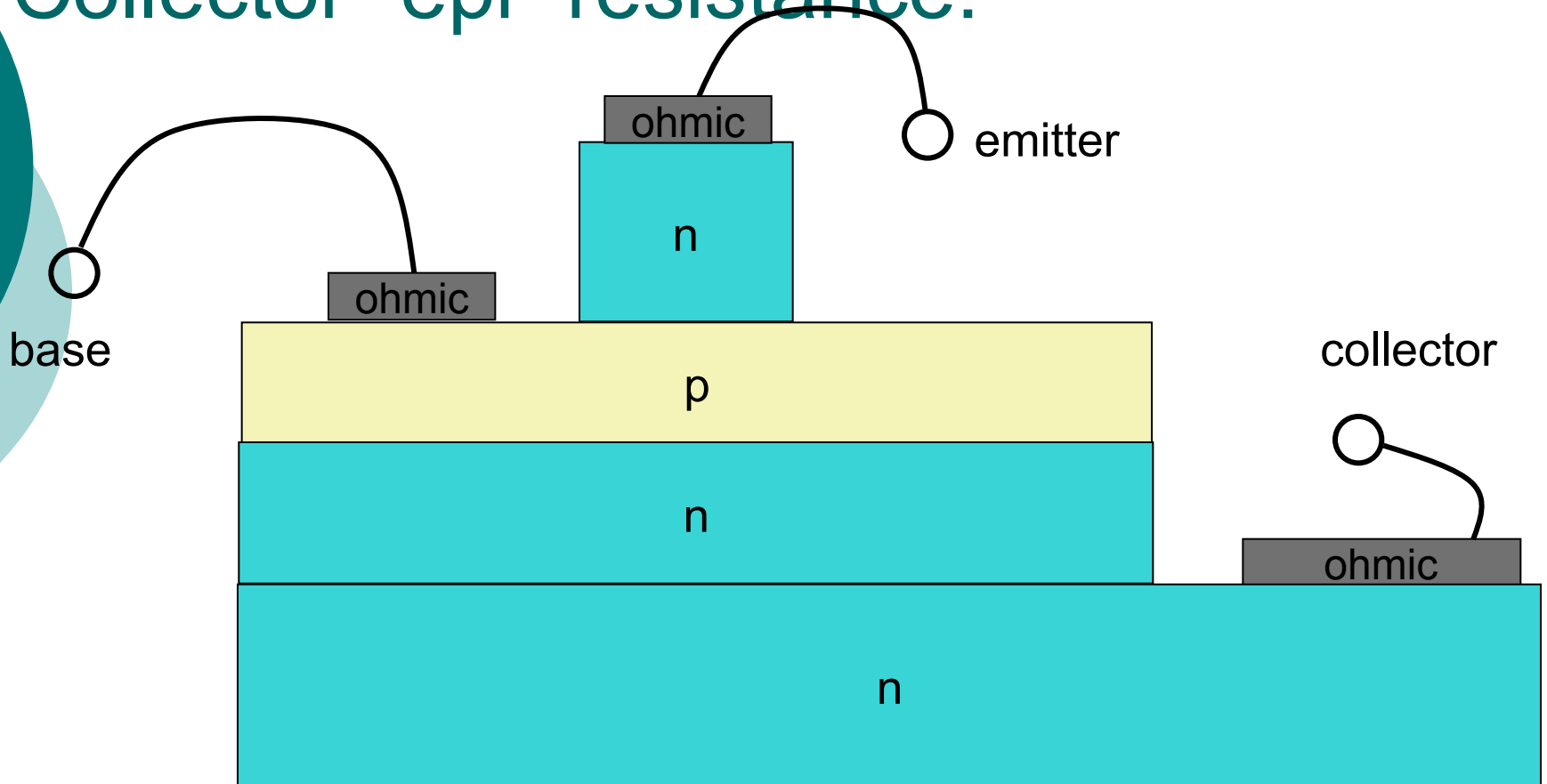

$$R_{C(epi)} = \rho_{C(epi)} \frac{X_{C(epi)}}{L_E W_E}$$

(discuss)
(also discuss spreading effect)

Parasitics: In summary

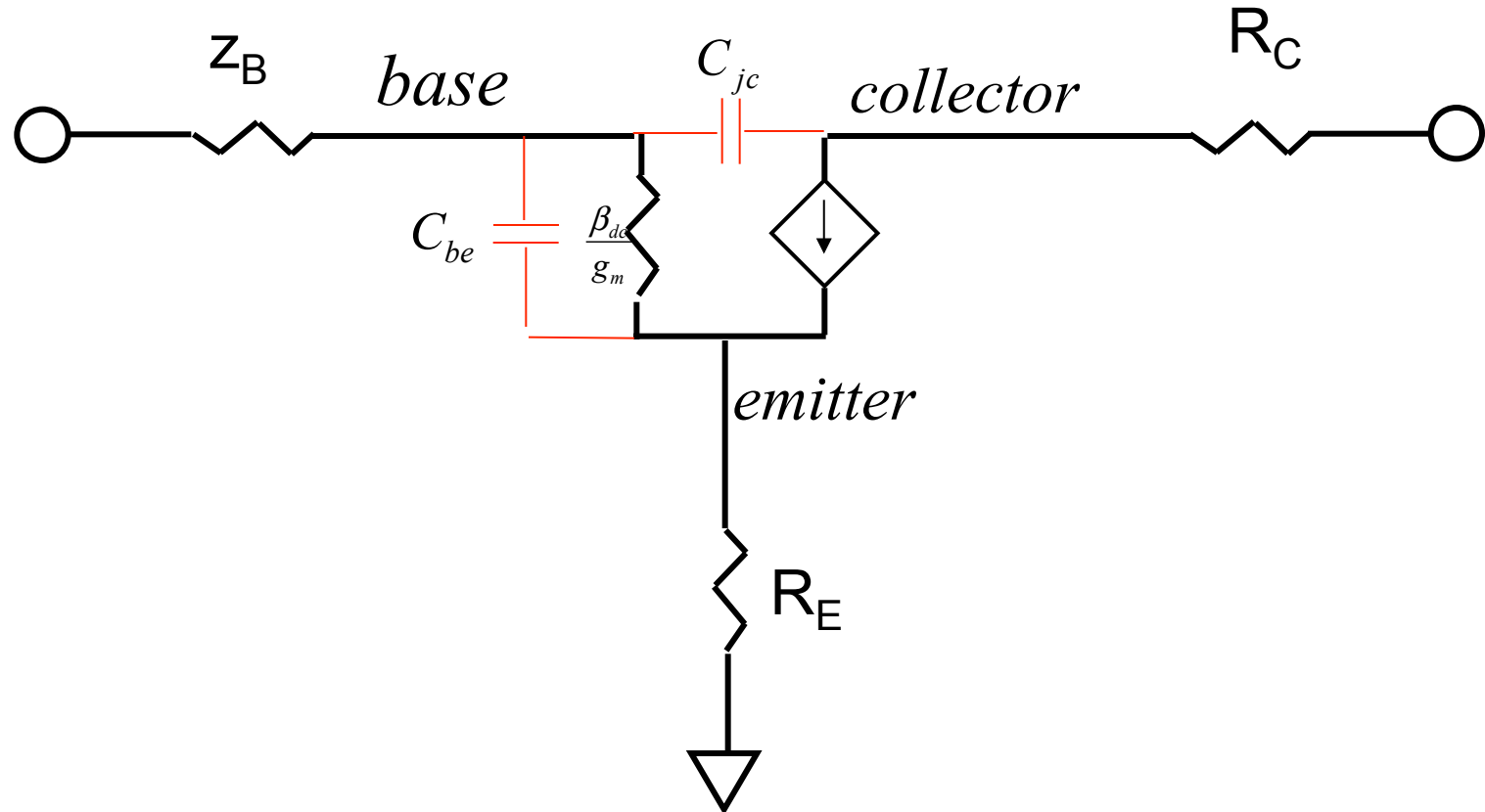

Total parasitics include contact, epi, and metal layer resistance. Sometimes inductance also added in.

f_T :

$$\begin{pmatrix} v_b \\ i_c \end{pmatrix} = \begin{pmatrix} h_{11e} & h_{12e} \\ h_{21e} & h_{22e} \end{pmatrix} \begin{pmatrix} i_b \\ v_c \end{pmatrix}$$

- Early effect:
Collector voltage changes current gain (β).
- β depends on frequency *and* collector voltage.
- How do we define frequency at which $\beta = 1$?
- At $v_c=0$. This *is* h_{21e}

$$i_c = h_{21e}i_b + h_{22e}v_c \rightarrow h_{21e}i_b$$

- We define f_T such that:

$$|h_{21e}|(f_T) = 1$$



 f_T

$$f_T = \frac{1}{2\pi\tau_{ec}}$$

$$\tau_{ec} = \tau_e + \tau_b + \tau_{sc} + \tau_c$$

Emitter charging time

$$\tau_e = \frac{kT}{eI_C} (C_{je} + C_{jc})$$

Time to charge up junction capacitors.

Base transit time

$$\tau_e = \frac{X_B^2}{2D_{nB}}$$

Time to charge up base minority carriers.
Or: time to diffuse from emitter to collector.
(Built in field helps a lot here.)

Space-charge transit time

$$\tau_e = \frac{X_{dep}}{2v_{sat}}$$

Or: time to *drift* through space charge of base-collector junction.

Collector charging time

$$\tau_c = (R_E + R_C) \cdot C_{jc}$$

Time to charge collector junction capacitor through parasitic resistors.

f_T :

$$\begin{pmatrix} v_b \\ i_c \end{pmatrix} = \begin{pmatrix} h_{11e} & h_{12e} \\ h_{21e} & h_{22e} \end{pmatrix} \begin{pmatrix} i_b \\ v_c \end{pmatrix}$$

“It can be shown that...”

$$h_{21e} = \frac{\alpha_{T0}}{(1 - \alpha_{T0}) + i(f / f_T)} \quad \alpha_{T0} \equiv 1 - \frac{X_B^2}{2L_n^2}$$

Discuss rolloff, low frequency value.

f_{\max} :

In real circuits, we do not want to short circuit the output!

Unilateral power gain: if impedance matching network is set up so that there is no reverse transmission ($S_{12}=0$), in that case the power gain is called the *unilateral power gain*.

“It can be shown that...”

$$U = \frac{|z_{21} - z_{12}|^2}{4[\operatorname{Re}(z_{11})\operatorname{Re}(z_{22}) - \operatorname{Re}(z_{12})\operatorname{Re}(z_{21})]}$$

“It can be shown that...”

$$U = \frac{\alpha_{T0}^2 \omega_T}{4 \operatorname{Re}(z_b) C_{jc} \omega^2}$$

$$f_{\max} = \sqrt{\frac{f_T}{8\pi r_b C_{jc}}}$$


Discuss r_b dependence,
want heavily doped base.
Need for HBT.



Field Effect Devices

- MOSFET
- JFET
- MESFET
- HEMT

Si MOSFET:

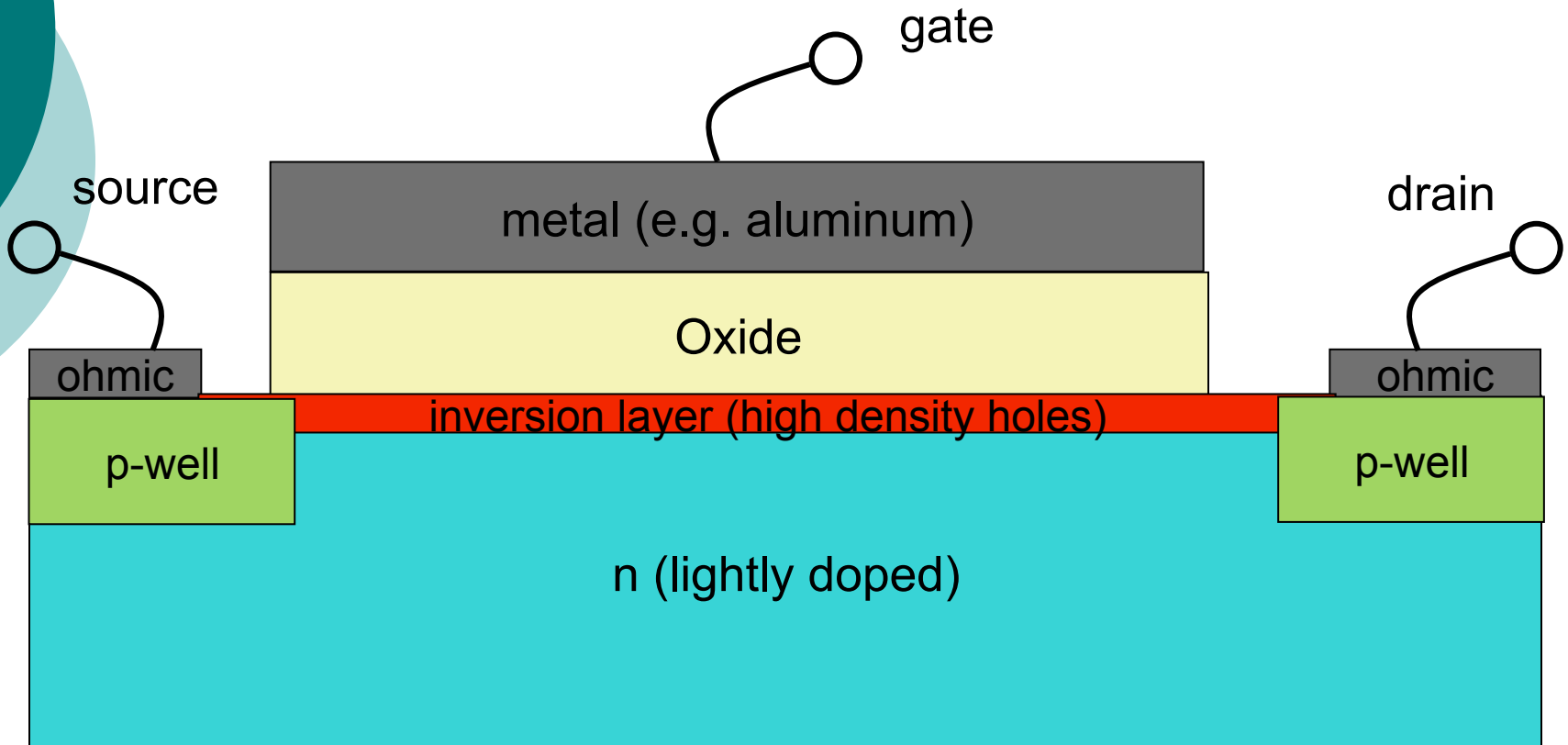

- Gate has high input resistance (10^{12} W)
- Si covered in ECE 277A.
- No oxide for GaAs, so need different type of device.

Non-oxide transistors

- JFET: Junction Field Effect Transistor
- MESFET: Metal Electron Semiconductor Field Effect Transistor
- HEMT: High Electron Mobility Transistor
 - Also called:
 - MODFET Modulation Doped Field Effect Transistor
 - TEGFET Two-Dimensional Electron Gas Field Effect Transistor
 - pHEMT Pseudomorphic HEMT
 - HFET Heterojunction Field Effect Transistor

Integrating:

$$I_D = \mu \cdot C_{ox} (V_{GS} - V_T - V_{CS}(x)) \cdot \frac{\partial V_{CS}(x)}{\partial x} \cdot W$$


$$\int_0^L I_D dx = \int_0^L \mu \cdot C_{ox} (V_{GS} - V_T - V_{CS}(x)) \cdot \frac{\partial V_{CS}(x)}{\partial x} \cdot W dx$$

$$= \int_{V_{CS}(0)}^{V_{CS}(L)} \mu \cdot C_{ox} (V_{GS} - V_T - V_{CS}(x)) \cdot \partial V_{CS}(x) \cdot W = doable$$


$$I_D = \frac{W \cdot \mu \cdot C_{ox}}{L} \left[(V_{GS} - V_T) V_{DS} - \frac{V_{DS}^2}{2} \right]$$

FET I-V curves

I_{DS}

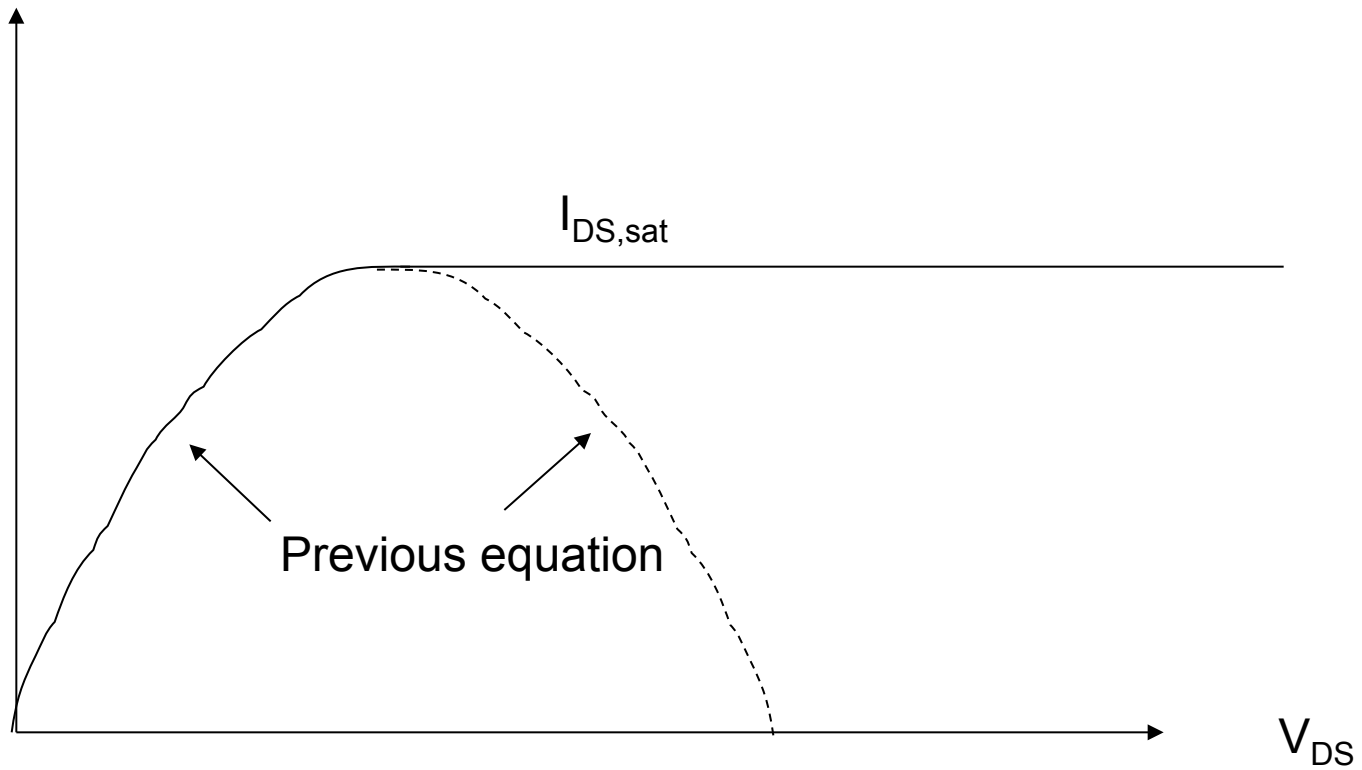

Velocity saturation

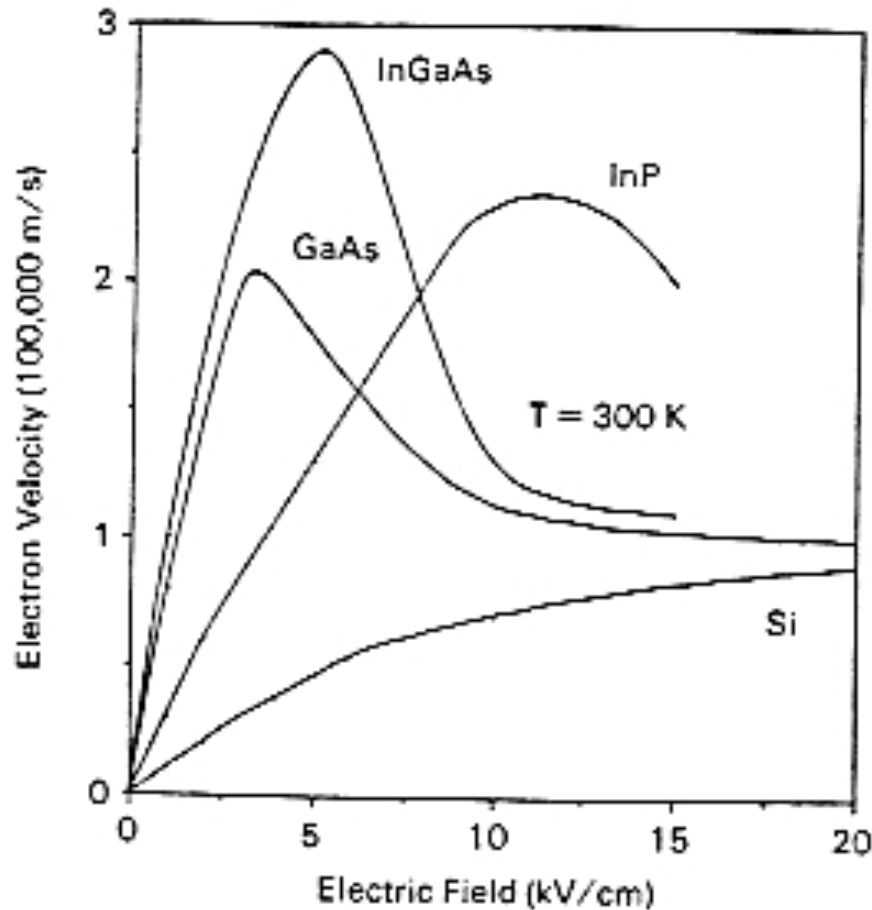



$$v = \mu \cdot E$$

$$\rightarrow v_{sat}$$

From Shur, Physics of Semiconductor Devices

FET AC properties

AC equivalent circuit:

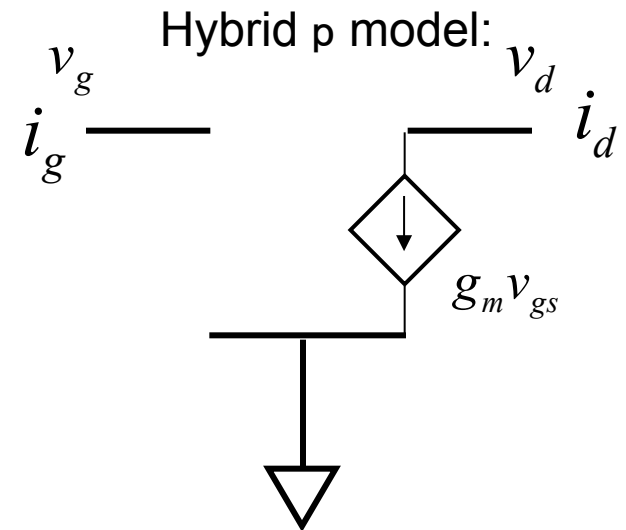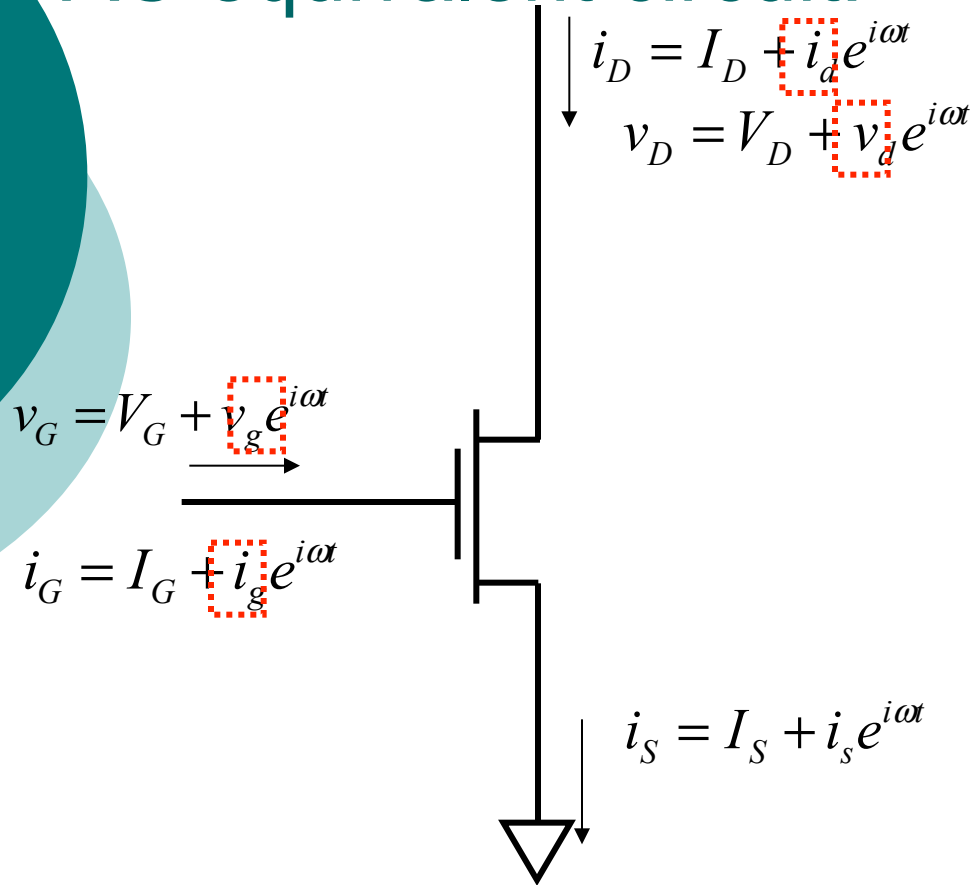

$$\begin{pmatrix} i_g \\ i_d \end{pmatrix} = \begin{pmatrix} 0 & 0 \\ g_m & 0 \end{pmatrix} \begin{pmatrix} v_g \\ v_d \end{pmatrix}$$

This is the common-source Y-matrix. You can get all the matrices from it.




What about capacitances?


Book sticks to long channel devices, well below transit time frequency.

Modern devices are short and f_T is the transit time frequency.


AC equivalent circuit:

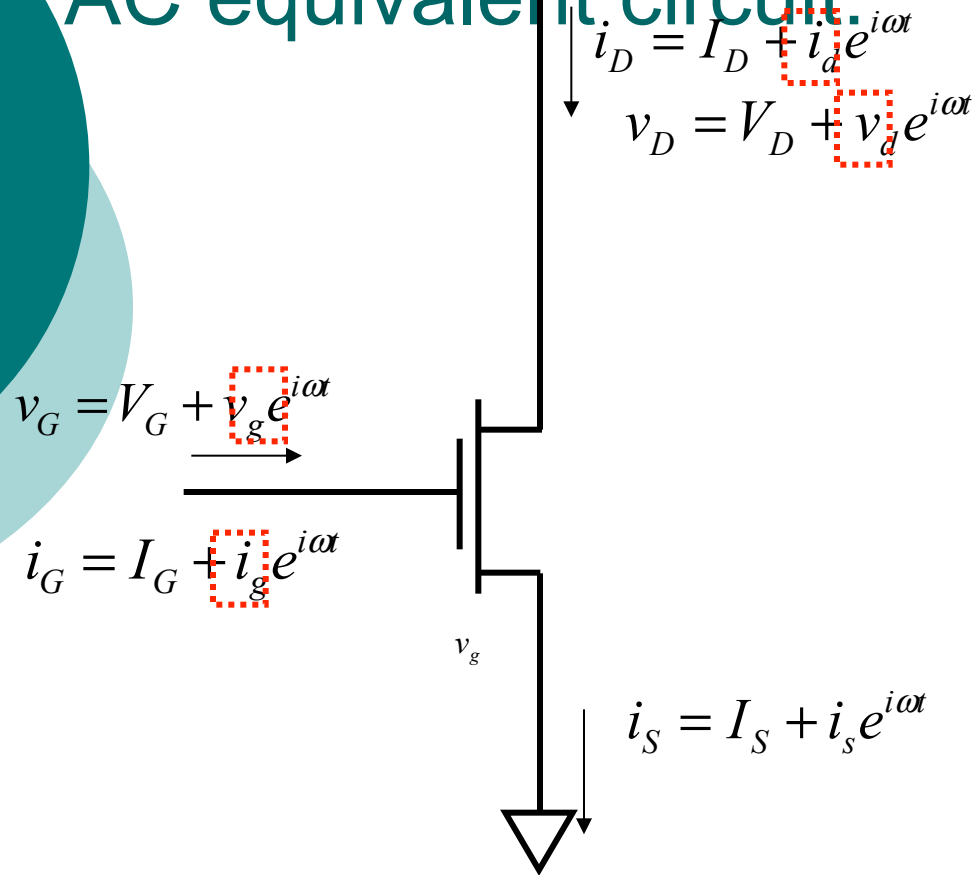

Hybrid p model:

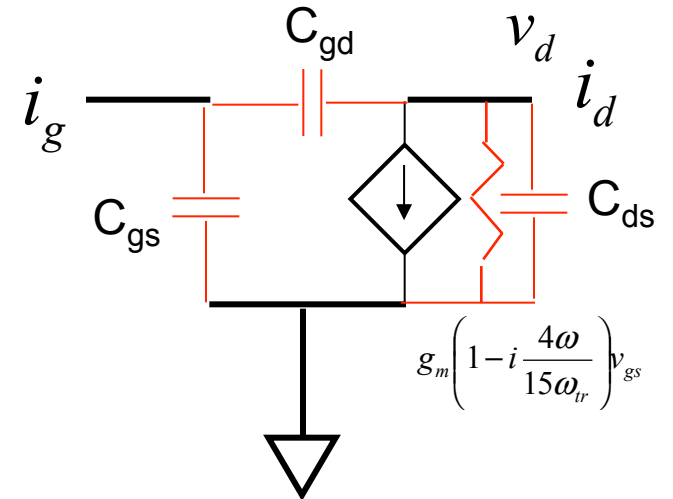

C_{gs} dominates.

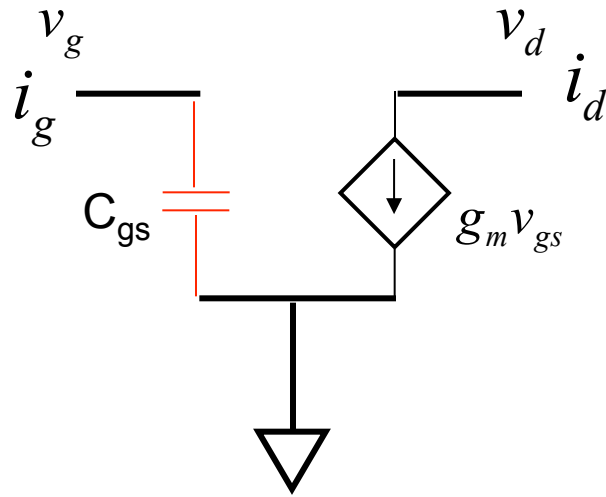
f_T Hybrid π model:

When current flowing through capacitor is equal to $g_m v_{gs}$
 then the frequency is f_T .

$$i_g = v_{gs} (\omega C_{gs}) \quad i_d = g_M v_{gs}$$

$$\text{At } f_T \quad g_M v_{gs} = v_{gs} (\omega_T C_{gs})$$
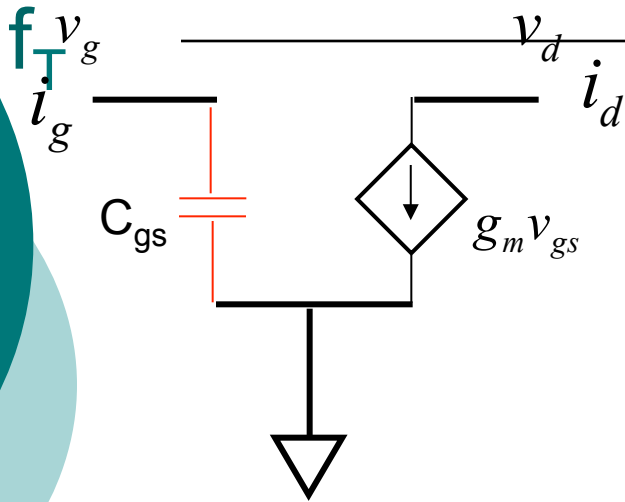
$$\Rightarrow \omega_T = \frac{g_M}{C_{gs}} \Rightarrow f_T = \frac{g_M}{2\pi C_{gs}}$$



$$f_T = \frac{g_M}{2\pi C_{gs}}$$

In HW#6, you will prove for the long-channel device:

$$g_M = \frac{W\mu C'_{ox}}{L} (V_{GS} - V_T)$$

$$C'_{ox} \sim C_{gs} / (LW)$$

$$f_T \rightarrow \frac{1}{2\pi} \frac{\mu(V_{GS} - V_T)}{L^2}$$


For a short-channel device,

$$g_M = v_{sat} WC'_{ox}$$


$$f_T \rightarrow \frac{v_{sat}}{2\pi L} = \frac{1}{2\pi\tau_{tr}}$$

So book model is only good for frequencies much less than f_T .

Quasi-static AC equivalent circuit:

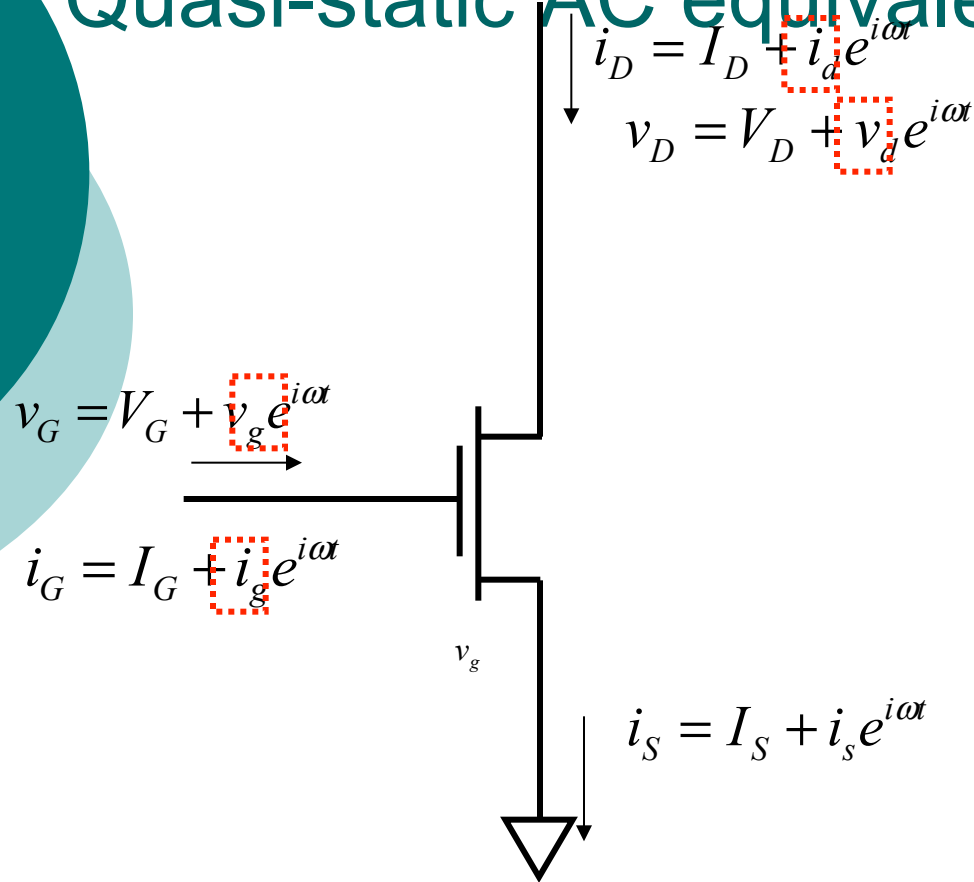


Hybrid π model:

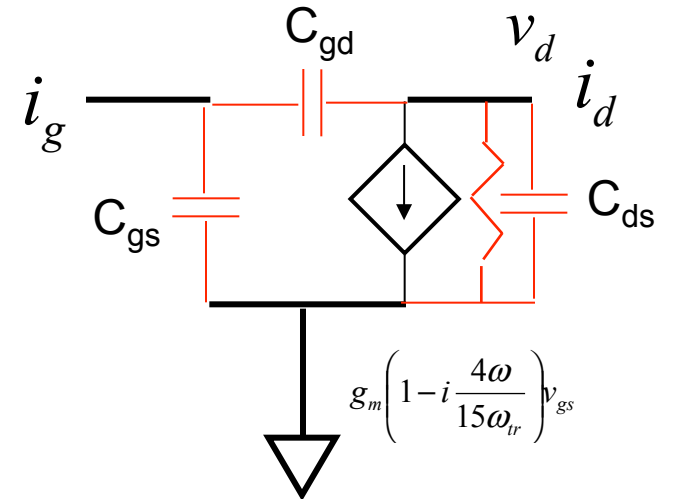


Non-quasi static model:

Hybrid p model:

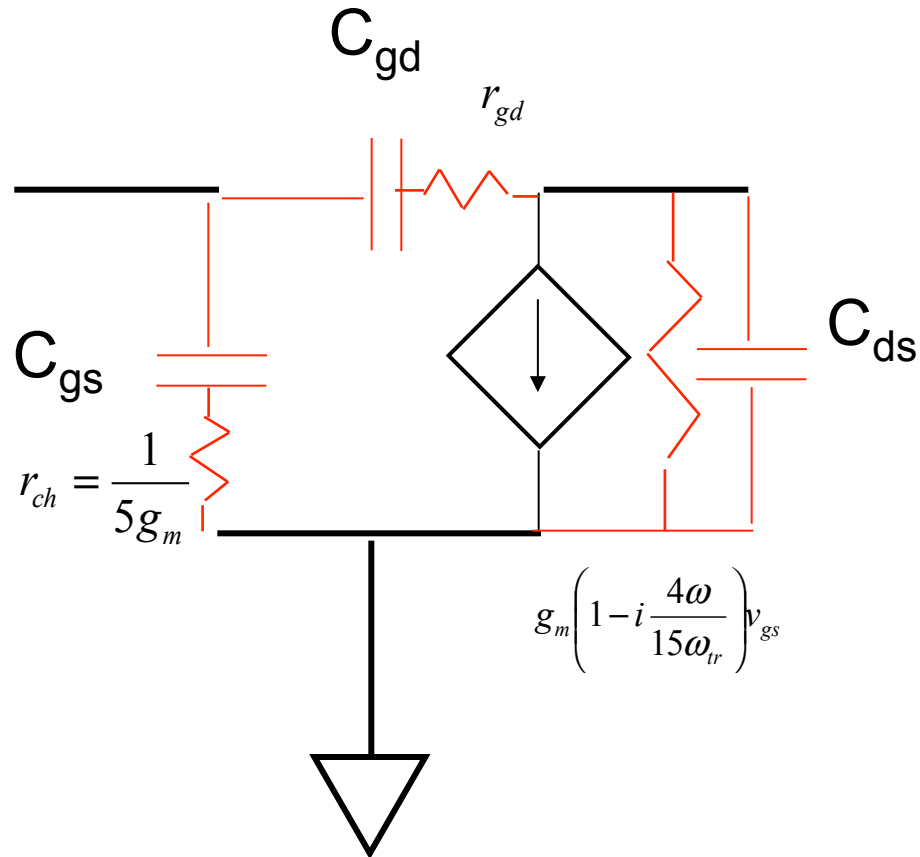

Non-quasi static model in saturation:

Hybrid p model:

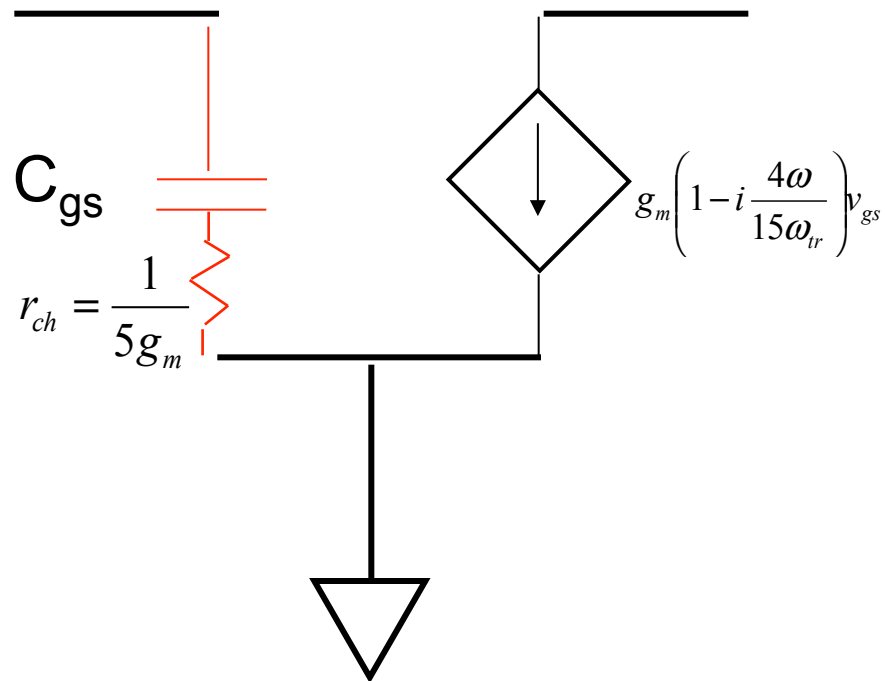

v_g

i_g


v_d

i_d

Parasitics: Gate resistance:

$$R_g = \frac{1}{3} \frac{W}{L} R_{square}$$

v_g
 i_g

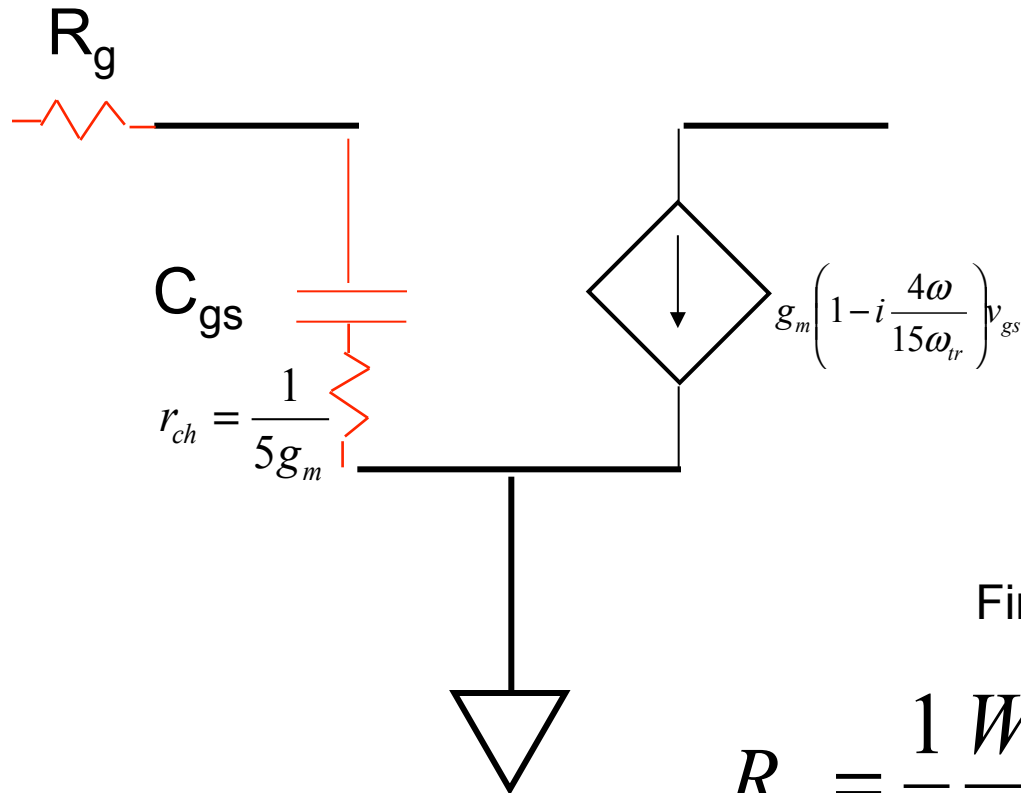


Fingers:

$$R_g = \frac{1}{3} \frac{W}{L} R_{square} \frac{1}{N}$$

Parasitics: Source/Drain resistance:


v_g
 i_g

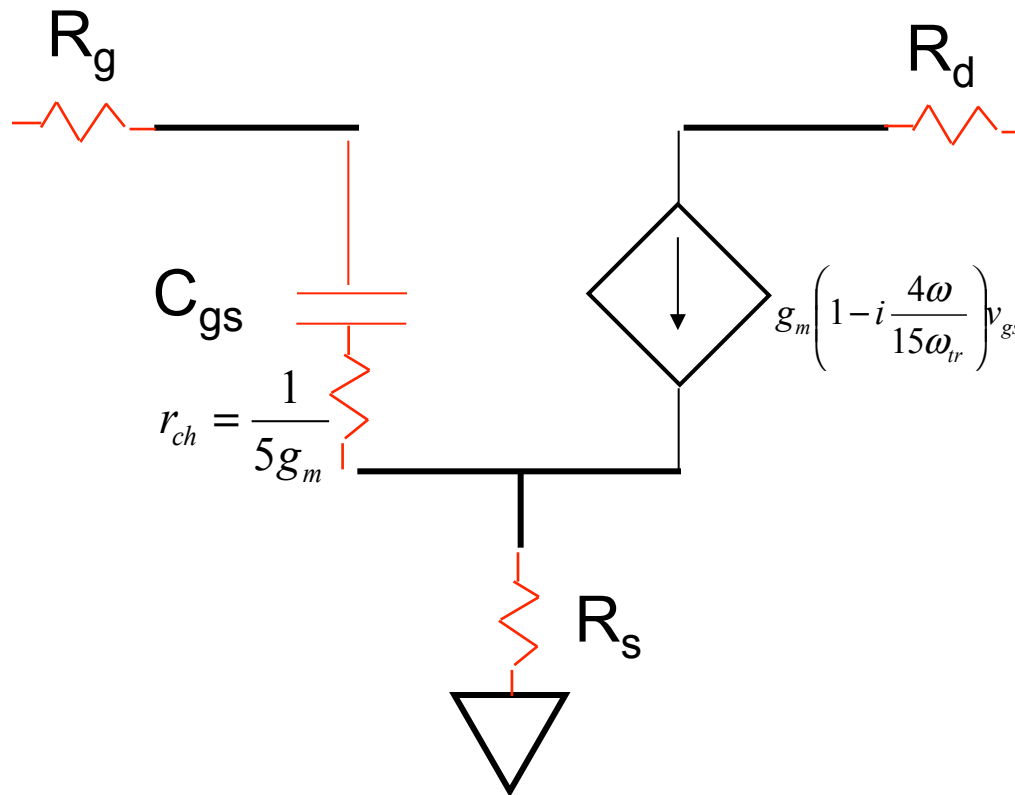

v_d
 i_d

f_T v_g i_g

$$\frac{1}{2\pi f_T} = \frac{C_{gg,t}}{g_m} + \frac{C_{gg,t}}{g_m} (R_S + R_D)g_d + (R_S + R_D)C_{gd,t}$$

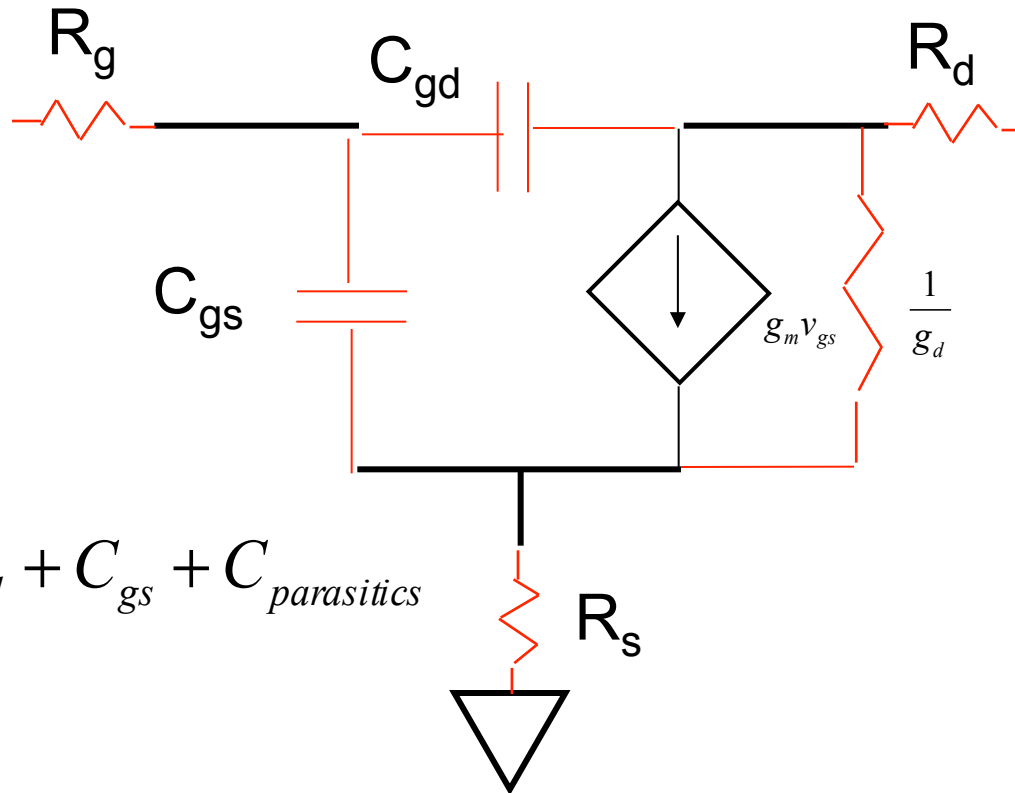 v_d i_d 

$$C_{gg,t} \equiv C_{gd} + C_{gs} + C_{parasitics}$$

f_{MAX}

$$f_{MAX} = \sqrt{\frac{f_T}{8\pi R_G C_{gd,t} \left[1 + \left(\frac{2\pi f_T}{C_{gd,t}} \right) \Psi \right]}}$$

$$\Psi \equiv (R_S + R_D) \frac{C_{gg,t}^2 g_d^2}{g_m^2} + (R_S + R_D) \frac{C_{gd,t} C_{gg,t} g_d}{g_m} + \frac{C_{gg,t}^2 g_d}{g_m^2}$$

f_{max} helped by fingers.

f_T not helped by fingers.

f_{MAX} sometimes larger, sometimes smaller than f_T .

RF CMOS


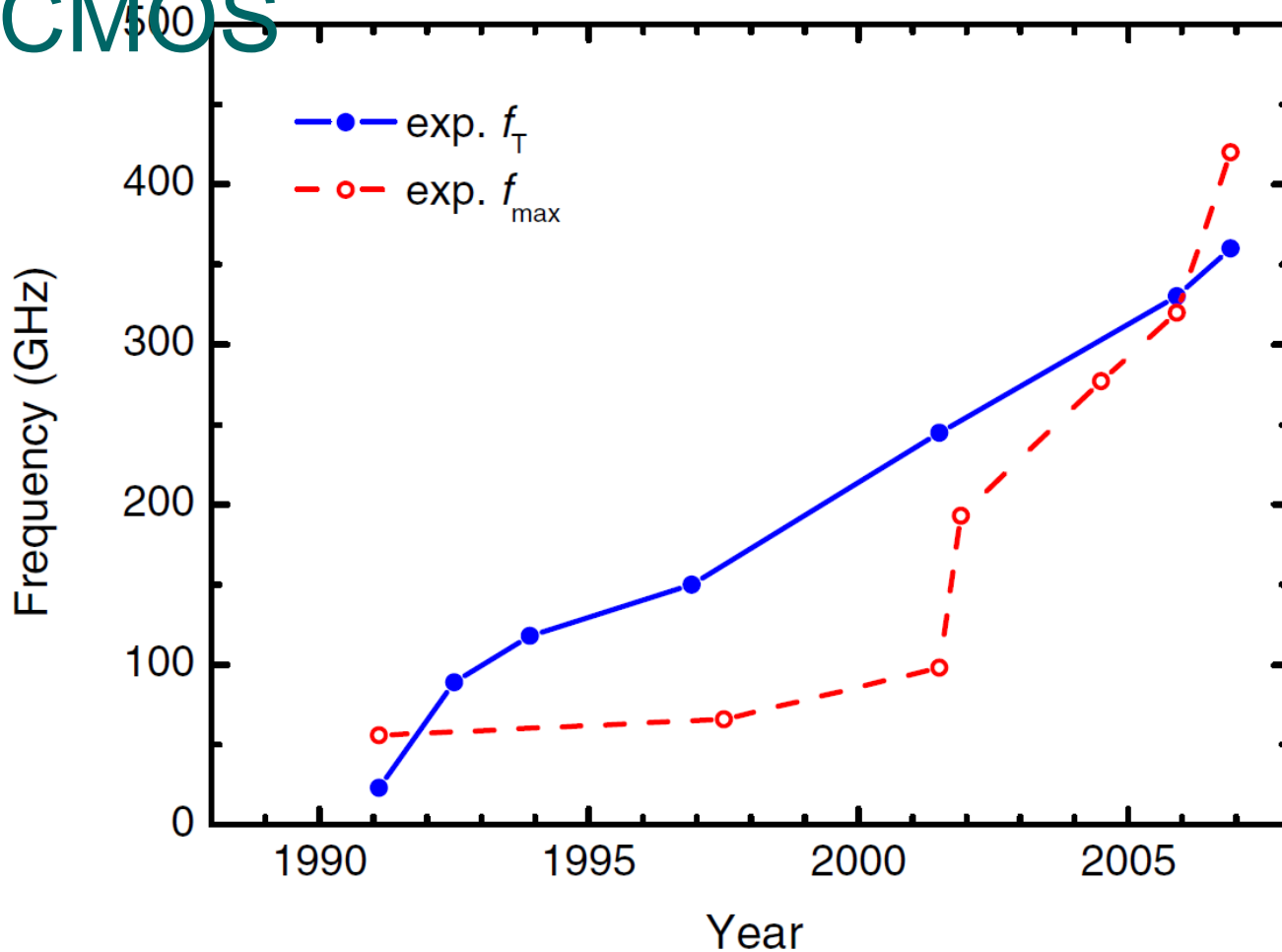


Fig. 1. Evolution of the record cutoff frequency f_T and the record maximum frequency of oscillation f_{max} of RF Si MOSFETs versus time.


F. Schwierz and J. J. Liou, "RF Transistors: Recent Developments and Roadmap toward Terahertz Applications", *Solid-State Electronics*, **51**, 1079-1091, (2007).

Cutoff frequency (f_T)

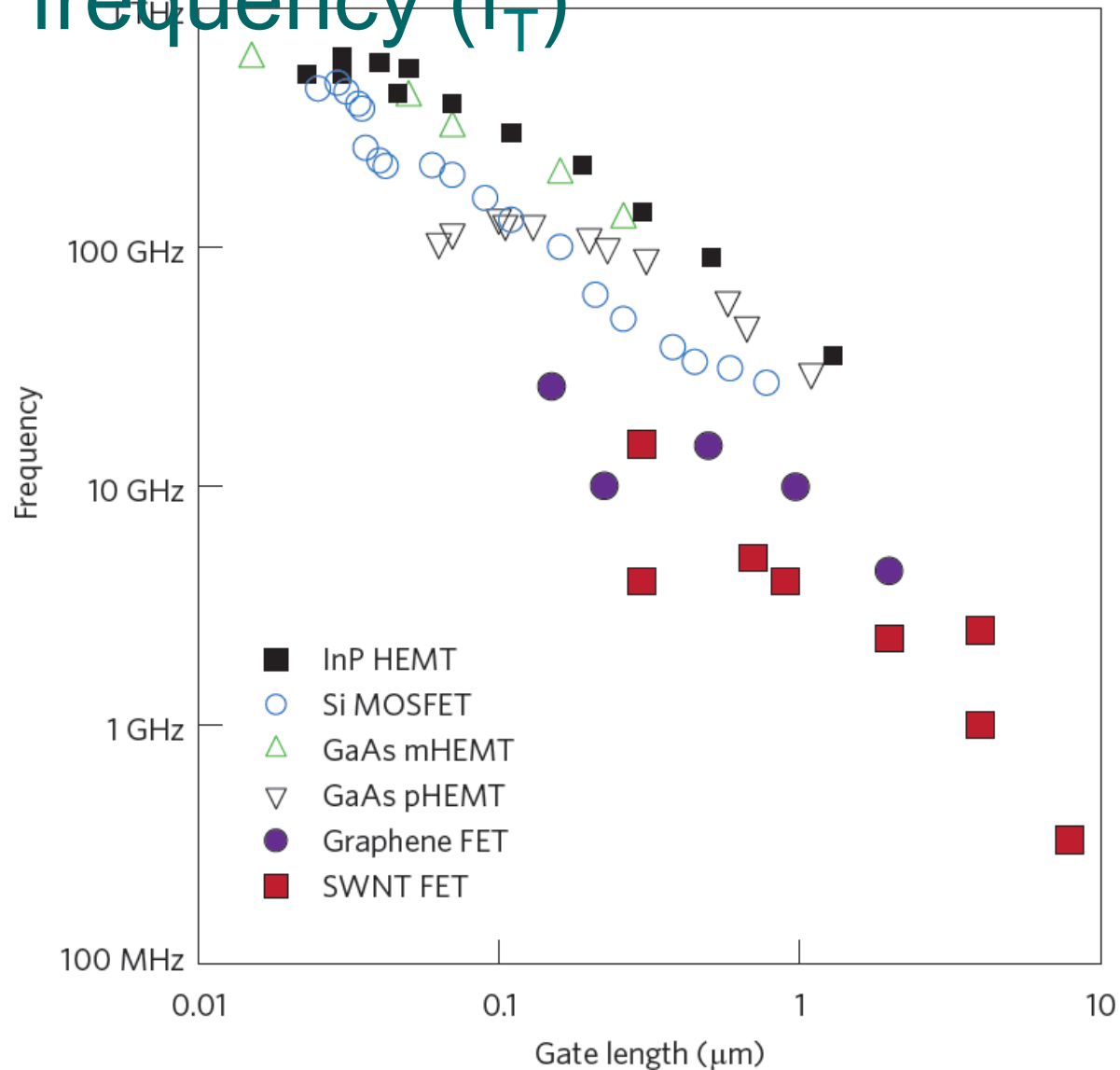


C. Rutherglen, D. Jain and P. Burke, "Nanotube Electronics for Radiofrequency Applications", *Nature Nanotechnology*, **4**, 811-819, (2009).

III-V f_{max}

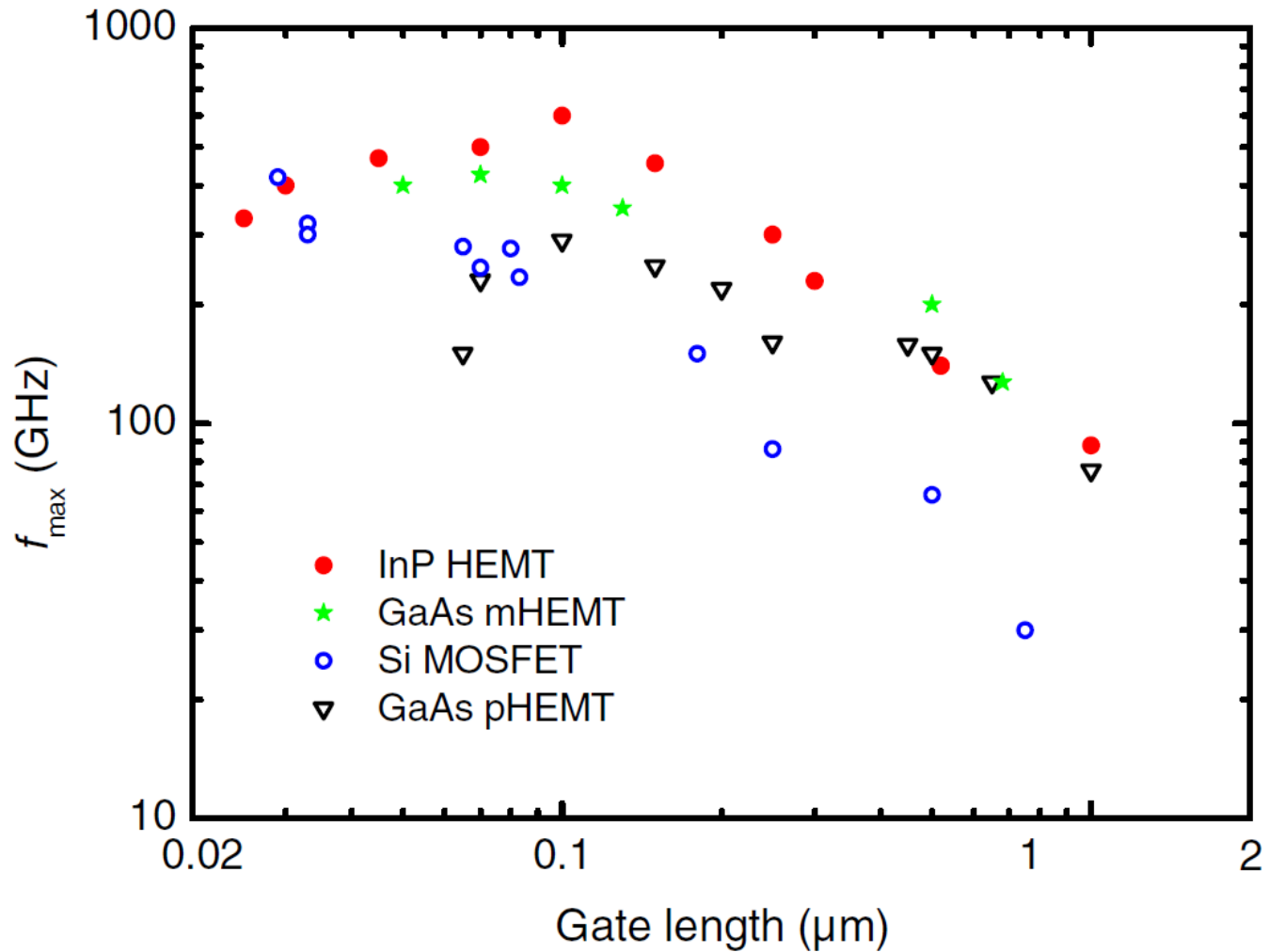

F. Schwierz and J. J. Liou, "RF Transistors: Recent Developments and Roadmap toward Terahertz Applications", *Solid-State Electronics*, **51**, 1079-1091, (2007).

f_T vs f_{Max}

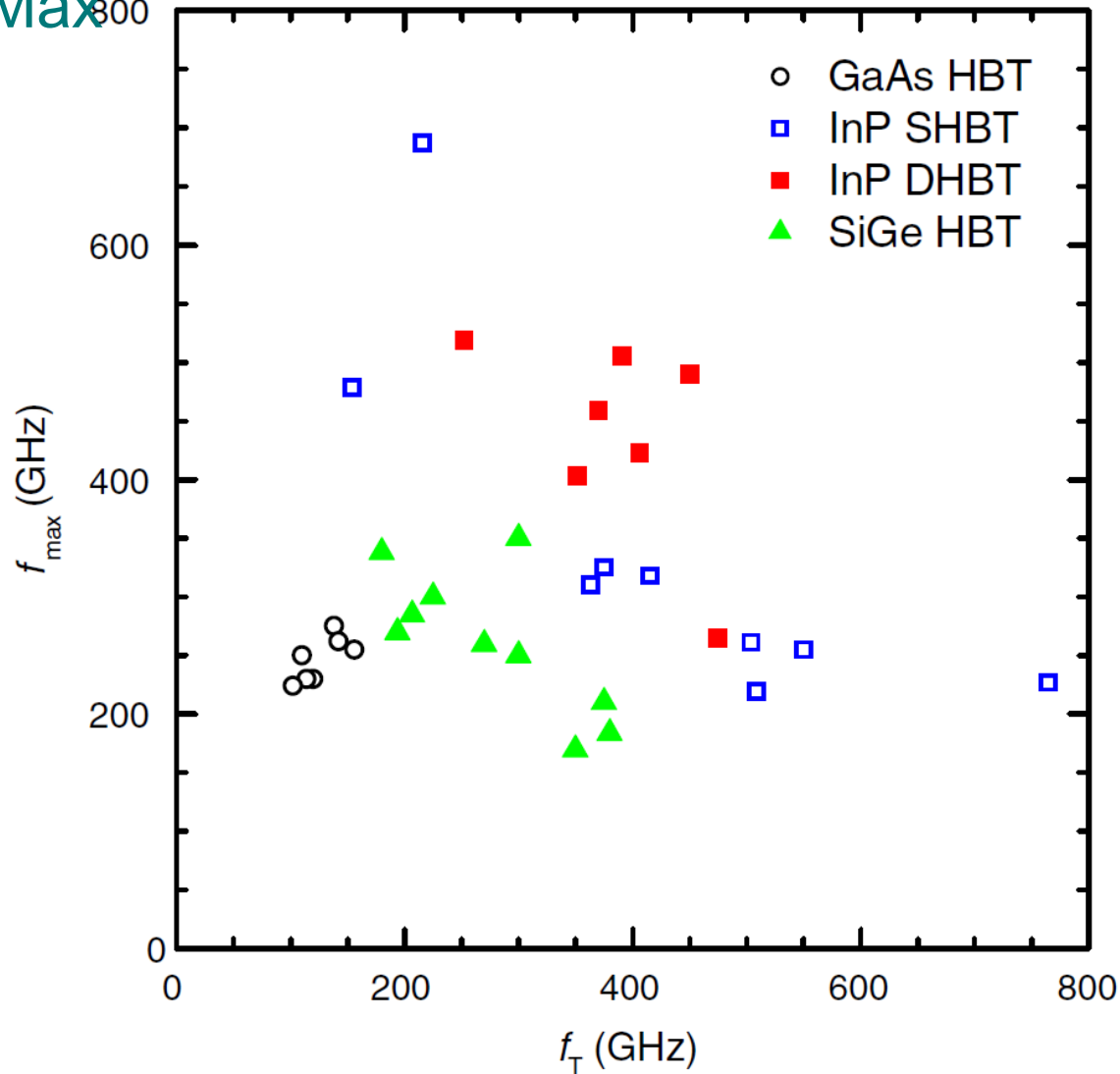

F. Schwierz and J. J. Liou, "RF Transistors: Recent Developments and Roadmap toward Terahertz Applications", *Solid-State Electronics*, **51**, 1079-1091, (2007).