

## EECS / CSE 70A MIDTERM #1

### GRADING RUBRIC

#### Problem 1.

a.

Step	Points
Recognizing parallel combination $4\Omega \parallel 4\Omega$	1
Recognizing parallel combination $2\Omega \parallel 2\Omega$	1
Application of the parallel resistors formula (in either step 4 or step 5)	1
$4\Omega \parallel 4\Omega = 2\Omega$	1
$2\Omega \parallel 2\Omega = 1\Omega$	1
Recognizing series combination $2\Omega + 1\Omega = 3\Omega$	1
Recognizing series combination $4\Omega + 2\Omega = 6\Omega$	1
Recognizing parallel combination $2\Omega \parallel 3\Omega \parallel 6\Omega$	1
Application of the parallel resistors formula with 3 resistors OR Calculating parallel combinations with 2 resistors at a time, twice	1
Final answer = $1\Omega$	1
<b>Total</b>	<b>10</b>

b.

Step	Points
Recognizing parallel combinations $3\Omega \parallel 3\Omega \parallel 3\Omega$	3
Application of the parallel resistors formula in step 3	1
$3\Omega \parallel 3\Omega \parallel 3\Omega = 1\Omega$	1
$(2\Omega + 2\Omega) \parallel 0\Omega = 0\Omega$ , OR recognizing $(2\Omega + 2\Omega)$ being shorted, = $0\Omega$	2
Recognizing series combinations $1\Omega + 3\Omega + 1\Omega$	2
Final answer = $5\Omega$	1
<b>Total</b>	<b>10</b>

**Problem 2.**

Step	Points
KCL equation at Node 1 in terms of node voltages	2
KCL equation at Node 2 in terms of node voltages	2
Recognizing that Node 3 voltage is set by the voltage source	2
Writing the expressions for currents $i_1$ through $i_4$	2
Using units in first and last steps (intermediate calculations may be left without units)	1
Carrying out the calculation steps correctly and clearly	2
Final Answers (Should be filled in the table)	
$V_1 = -1V$	2
$V_2 = 2V$	2
$V_3 = 6V$	2
$i_1 = 1A$	2
$i_2 = -4A$	2
$i_3 = -1A$	2
$i_4 = -1A$	2
<b>Total</b>	<b>25</b>

**Problem 3.**

Step	Points
KVL Loop equation for Mesh B	4
KVL Loop equation for Supermesh (A & C, OR, A & B & C)	5
$i_2 = I_A - I_B$ (accepted if inserted in step 1 or 2)	2
$i_3 = I_C - I_B$ (accepted if inserted in step 1 or 2)	2
$I_C + 1 = I_A$	2
Solving equations using Cramer's rule, elimination, and/or substitution	5
Final Answers	
$I_A = i_1 = 5/9 A$	1
$I_B = 1/9 A, I_C = -4/9 A$	1
$i_2 = 4/9 A, i_3 = -5/9 A$	1
$v_1 = 4\Omega (-I_C) = 16/9 V$	1
$v_2 = 2i_2 + 1\Omega (I_C) = 4/9 V$	1
<b>Total</b>	<b>25</b>

**Problem 4.**

Step	Points
Mesh count = 20	5
Node count = 30	5
Remarks: Not counting the reference node/ground received full score Any systematic approach received credit	-
<b>Total</b>	<b>10</b>

**Problem 5.**

Step	Points
Solving the open circuit voltage for Thevenin voltage source	Any two on the left
Solving the short circuit current for Norton current source	
Solving for $R_{eq} = R_{Th} = R_{No}$ by killing all independent sources	
Remark for the steps above: For attempting with correct approach 2pts, calculation steps 3pts	-
Finding any of $V_{th}$ , $I_{No}$ , $R_{Th}$ using $V_{th} = I_{No} \times R_{Th}$	2
Drawing the correct Thevenin equivalent network	2
Annotating the correct source voltage and resistance in Thevenin circuit	2
Drawing the correct Norton equivalent network	2
Annotating the correct source current and resistance in Norton circuit	2
<b>Total</b>	<b>20</b>