

EECS / CSE 70A MIDTERM #1

GRADING RUBRIC

Problem 1.

Step	Points
Recognize/use/state $V_+ = V_-$ (2pts.) and no current $i_+ = i_- = 0$ (2pts.)	4
Finding V_o in terms of V_1 and V_- (Correct attempt 2pts. Result 2pts.)	4
Finding V_+ in terms of V_2 (Correct attempt 2pts. Result 2pts.)	4
Find V_o in terms of V_1 and V_2	3
Total for part (a) 15pts	
Substitute V_1 and V_2 values in V_o	2
Find i_1 (Correct expression 2pts. Correct value 1pt)	3
Find i_2 (Correct expression 2pts. Correct value 1pt)	3
Total for part (b) 8pts	
Units (Initial equations 1pt. Final results 1pt.)	2
Total	25

Problem 2.

Step	Points
Recognize that the inductor is short circuit at $t = 0^-$	2
Recognize that 12Ω is short circuited at $t = 0^-$	2
Find $i_L(t = 0^-)$ (Correct expression 2pts, result 1pt.)	3
Total for steps regarding $t = 0^-$ 7pts	
For transient period, writing the correct time constant equation	2
After switch is open, using/recognizing correct resistance	2
Finding the correct time constant value	2
Total for steps regarding transient period 6pts	
Recognize source free discharge or Reason justify $i_L(\infty) = 0$	2
Give the generic formula for $i_L(t)$ when $t > 0$	2
Correct final result for $i_L(t)$ (If the numbers are wrong due to a mistake in previous steps, still given 1pt)	2
Total for steps regarding $i_L(t)$ 6pts	
Attempt calculating v_L using i_L and/or recognize $v_L(\infty) = 0$	2
Use $v_L = L di_L/dt$, or $v_L = (-1/\tau)L i_L$	1
Formula for $v_L(t)$	1
Final correct result for $v_L(t)$	1
Total for steps regarding $v_L(t)$ 5pts	
Units	1
Total	25

Problem 3.

Approach 1: First finding V, then I

Step	Points
Finding the source voltage phasor V_s	3
Impedance terms (R & $j\omega L$)	3
Voltage division expression $V = (j\omega L/(R + j\omega L))V_s$	3
Some simplifications/manipulations toward polar/exponential or rectangular/Cartesian form for V	4
Arriving at a polar/exponential or rectangular/Cartesian form	2
Correct final expression for the phasor V (answer to part (a))	1
Applying Ohm's law $I = V/Z_L$	2
Some simplifications/manipulations toward polar/exponential or rectangular/Cartesian form for I	4
Arriving at a polar/exponential or rectangular/Cartesian form	2
Correct final expression for the phasor I (answer to part (b))	1
Total	25

Approach 2: First finding I, then V

Step	Points
Finding the source voltage phasor V_s	3
Impedance terms (R & $j\omega L$)	3
Equivalent impedance $Z_{eq} = R + j\omega L$ (series combination)	1
Applying Ohm's law $I = V_s/Z_{eq}$	2
Some simplifications/manipulations toward polar/exponential or rectangular/Cartesian form for I	4
Arriving at a polar/exponential or rectangular/Cartesian form	2
Correct final expression for the phasor I (answer to part (b))	1
Applying Ohm's law $V = IZ_L$	2
Some simplifications/manipulations toward polar/exponential or rectangular/Cartesian form for V	4
Arriving at a polar/exponential or rectangular/Cartesian form	2
Correct final expression for the phasor V (answer to part (a))	1
Total	25

Problem 4.

Step	Points
Impedance of capacitor = $1/(j\omega C)$	3
Impedance of inductor = $j\omega L$	3
Equivalent impedance expression for series combination $Z_{eq}(\omega) = R + 1/(j\omega C) + j\omega L$	4
Simplifications/manipulations toward $x + jy$ form	3
Arriving at an $x + jy$ form	2
Correct value of x (answer to part (b))	1
Correct value of y (answer to part (c))	1
Equating the imaginary part to zero, $\text{Im}(Z_{eq}(\omega)) = 0$	3
Obtaining some equation equivalent to $\omega = 1/\sqrt{LC} = \sqrt{(10^6/4)}$	3
Calculating numerical value of ω , 500	1
Correct unit of ω , rad/s	1
Total	25