


EECS/CSE 70A Network Analysis I

Homework #1


Due on or before

4/5/2016, Tuesday 6.00pm at ELH 110


Problem 1: Find the power absorbed or supplied by the element.

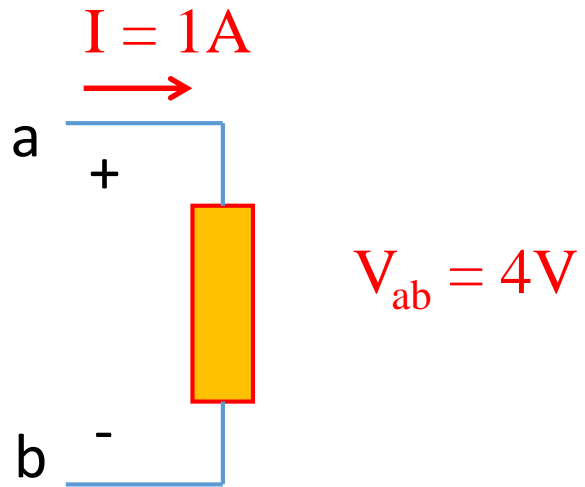

Problem 2: Find the power absorbed or supplied by the element.

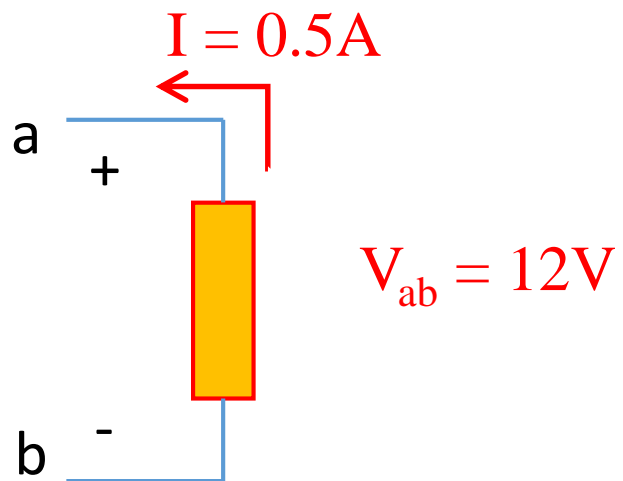

Problem 3: Find the current I_3 flowing through element 3.

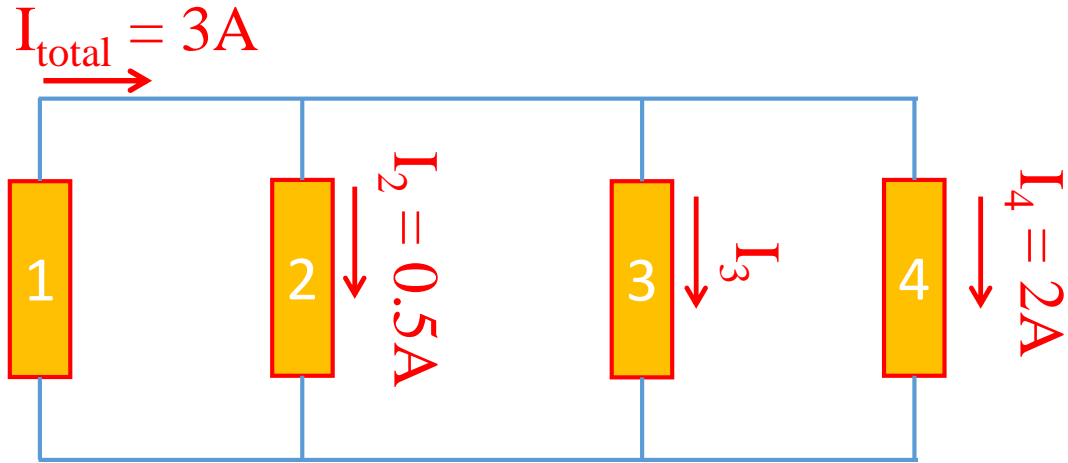

Problem 4:

- Find I_2
- Find the power absorbed or supplied by element 2
- Find the power absorbed or supplied by element 1
- Is element 1 a source or a sink? Repeat for elements 2 and 3.

