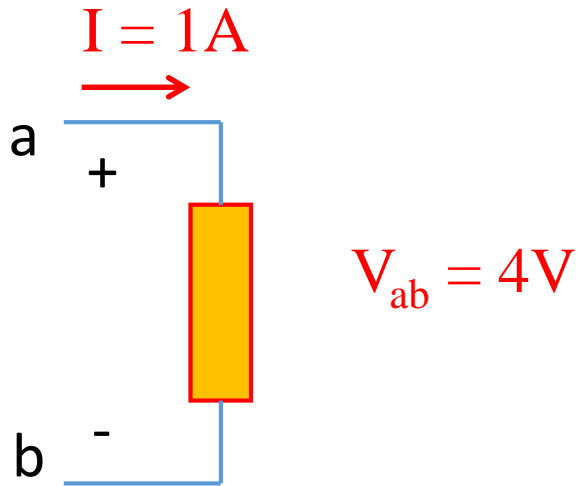


EECS/CSE 70A Network Analysis I

Homework #1 Solution Key

Problem 1: Find the power absorbed or supplied by the element.




Problem 1 Solution

$$P = V_{ab}I_{ab} \quad \text{where } I_{ab} = I = 1A$$

$$P = (4V) \times (1A) = 4W$$

$P > 0$, therefore the element is a power sink (it absorbs power)

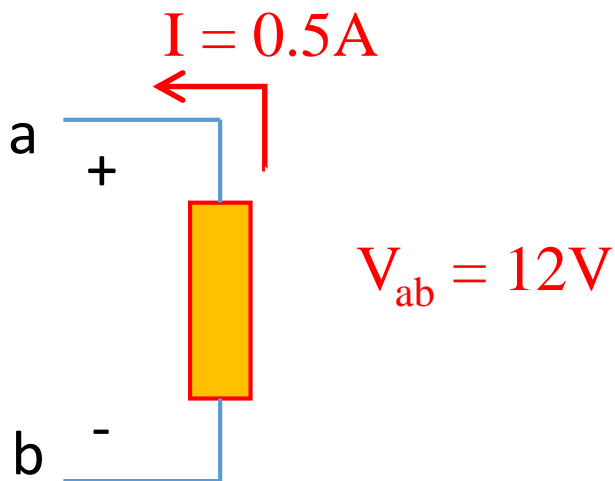Problem 2: Find the power absorbed or supplied by the element.




Problem 2 Solution

$$P = V_{ab}I_{ab} \quad \text{where } I_{ab} = -I = -0.5A$$


$$P = (12V) \times (-0.5A) = -6W$$

$P < 0$, therefore the element is a power source (it supplies power)

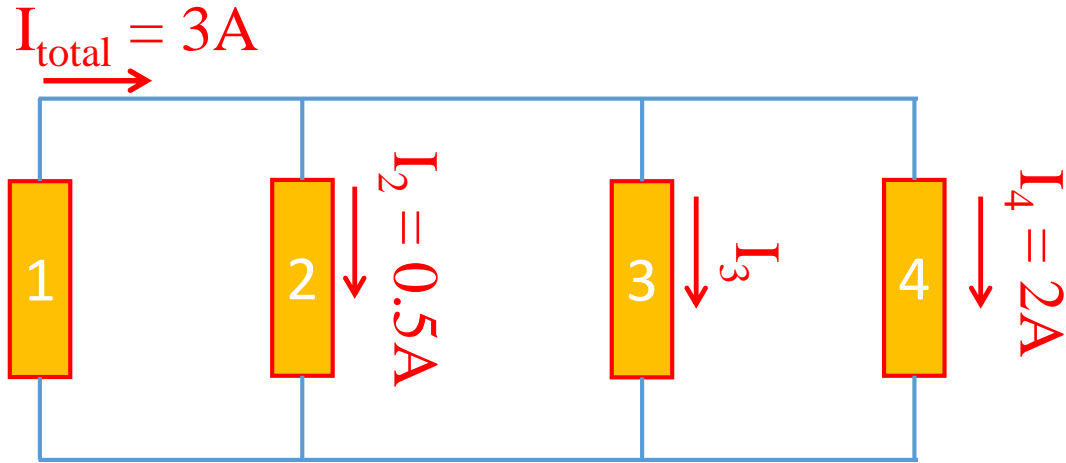Problem 3: Find the current I_3 flowing through element 3.



Problem 3 Solution

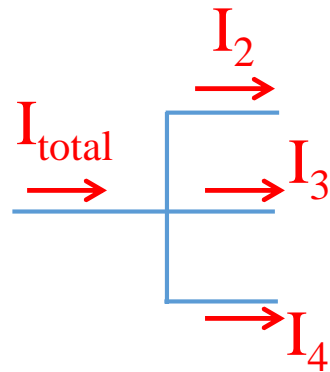

$$I_{\text{total}} = I_2 + I_3 + I_4$$


$$I_3 = I_{\text{total}} - I_2 - I_4$$

$$I_3 = 3\text{A} - 0.5\text{A} - 2\text{A}$$

$$I_3 = 0.5\text{A}$$

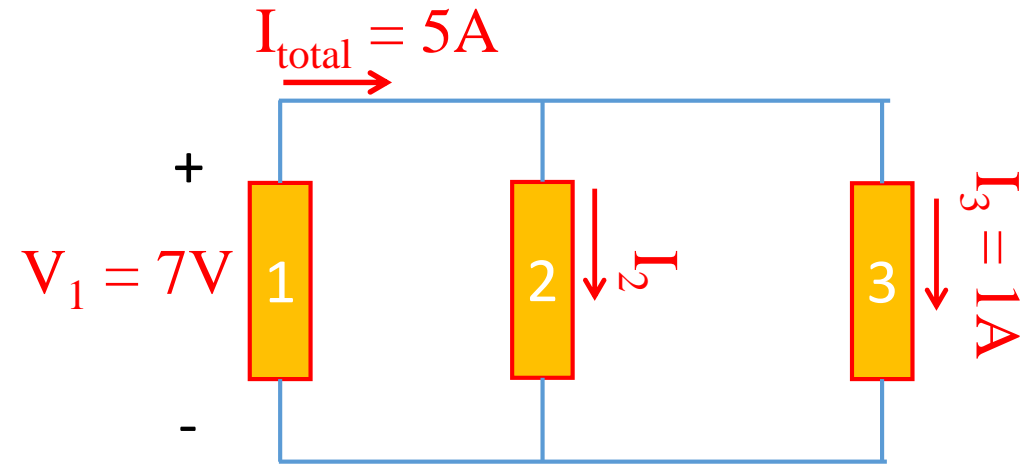Problem 4:

- Find I_2
- Find the power absorbed or supplied by element 2
- Find the power absorbed or supplied by element 1
- Is element 1 a source or a sink? Repeat for elements 2 and 3.



Problem 4 Solution

a) $I_{\text{total}} = I_2 + I_3$


$$I_2 = I_{\text{total}} - I_3$$

$$I_2 = 5\text{A} - 1\text{A} = 4\text{A}$$

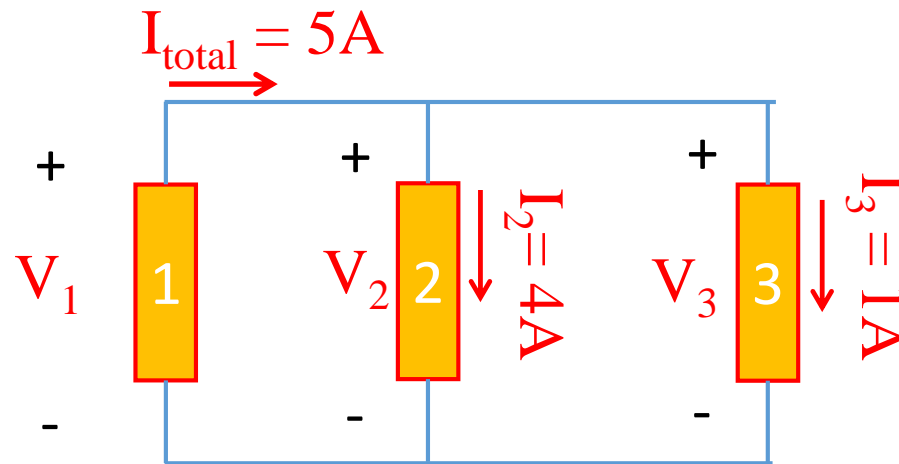- b) $P_2 = V_2 I_2$ with V_2 shown in the schematic on the right

$$V_1 = V_2 = V_3 = 7\text{V}$$


$$P_2 = V_2 I_2 = 7\text{V} \times 4\text{A} = 28\text{W}$$



cont'd on next page

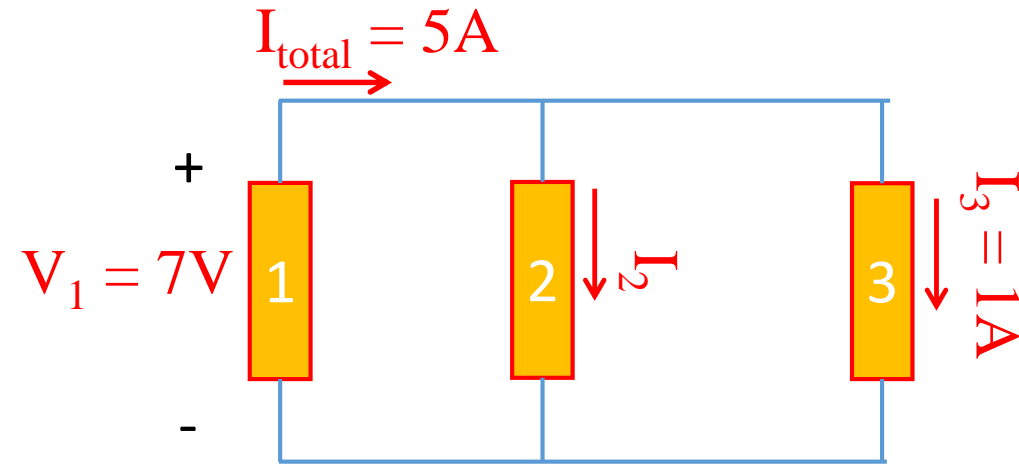
Problem 4:

- Find I_2
- Find the power absorbed or supplied by element 2
- Find the power absorbed or supplied by element 1
- Is element 1 a source or a sink? Repeat for elements 2 and 3.



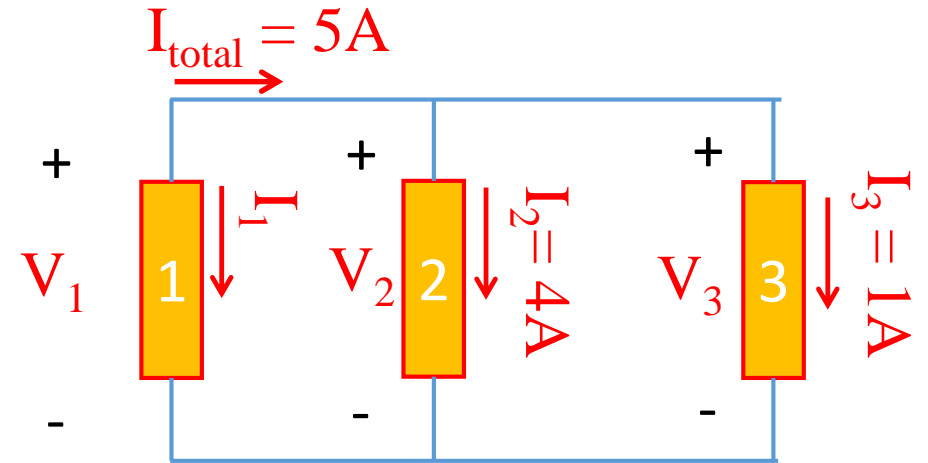Problem 4 Solution

- $P_1 = V_1 I_1$ where $I_1 = -I_{\text{total}} = -5\text{A}$
 $P_1 = V_1 I_1 = (7\text{V}) \times (-5\text{A}) = -35\text{W}$
- $P_1 = -35\text{W} < 0$ element 1 is a power source
 $P_2 = 28\text{W} > 0$ element 2 is a power sink



$$P_1 + P_2 + P_3 = 0 \text{ (power balance)}$$

$$P_3 = -P_1 - P_2 = -(-35\text{W}) - 28\text{W} = 7\text{W} \quad \text{OR} \quad P_3 = V_3 I_3 = (7\text{V}) \times (1\text{A}) = 7\text{W}$$

$$P_3 = 7\text{W} > 0 \text{ element 3 is a power sink}$$