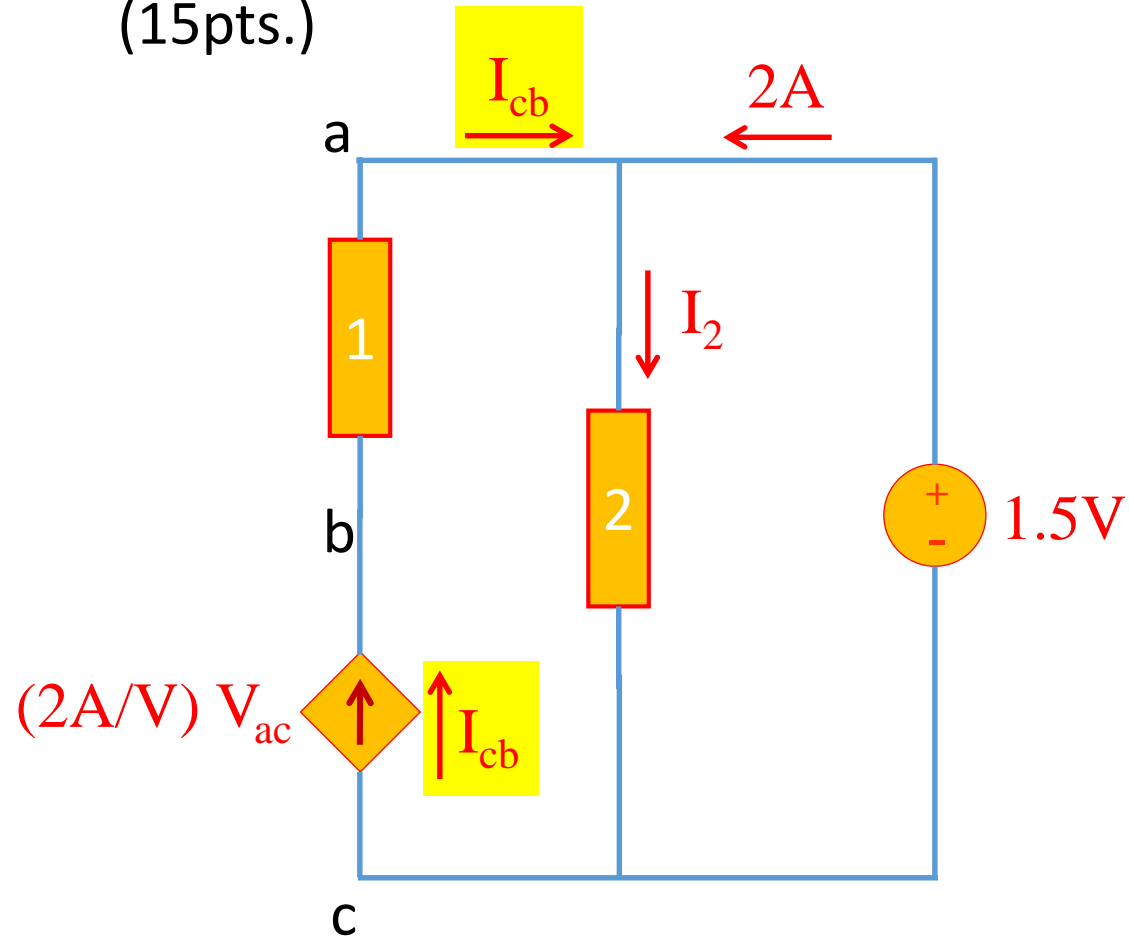


EECS/CSE 70A Network Analysis I

Homework #2 Solution Key

Problem 1: (VCCS) Find I_{cb} and I_2 .
(15pts.)



Problem 1 Solution

I_{cb} is the current of the voltage-controlled current source flowing from c to b.


$$I_{cb} = (2A/V) V_{ac} \quad \text{where } V_{ac} = 1.5V$$

$$I_{cb} = (2A/V) \times 1.5V = 3A$$

KCL at the top node

$$I_2 = I_{cb} + 2A = 5A$$

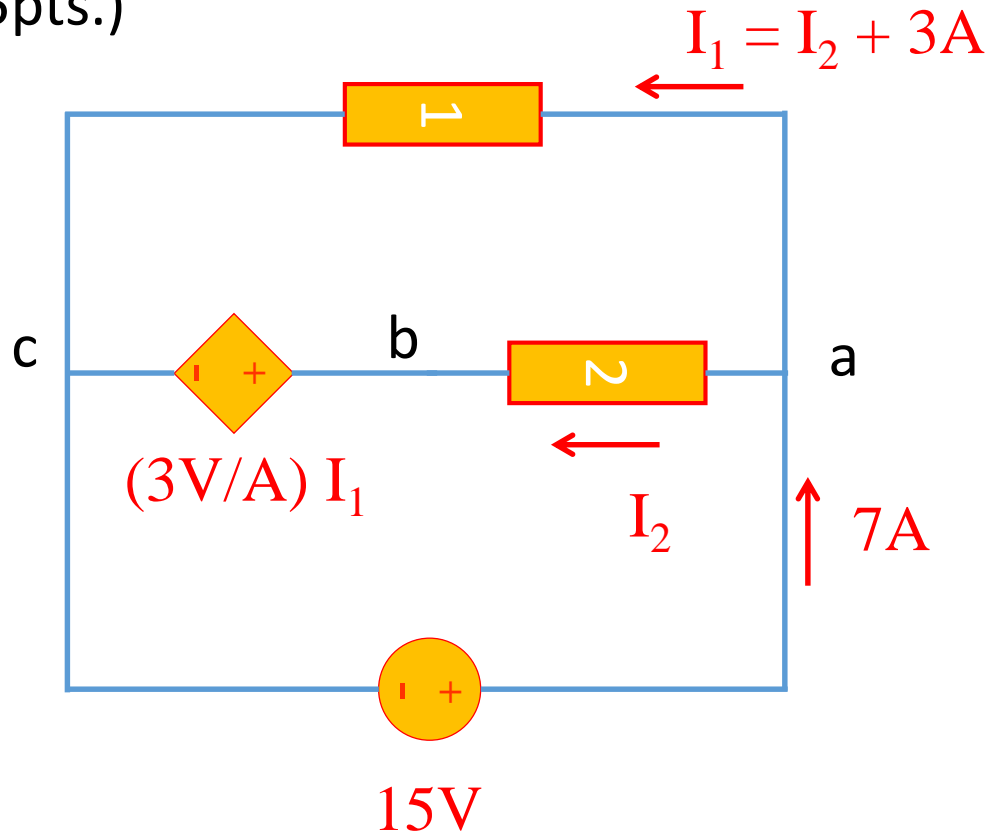Problem 2: (CCVS) Find I_1 , I_2 and V_{bc}
(15pts.)



where $V_{ac} = 1.5V$

Problem 2 Solution

Apply KCL at node a.

$7A = I_1 + I_2$ where $I_1 = I_2 + 3A$ is given

Substitute $I_2 = I_1 - 3A$

$$7A = I_1 + I_1 - 3A$$

$$10A = 2I_1$$


$$I_1 = 5A,$$

$$I_2 = I_1 - 3A = 2A$$

V_{bc} is the voltage across the current-controlled voltage source

$$V_{bc} = (3V/A) \times 5A = 15V$$

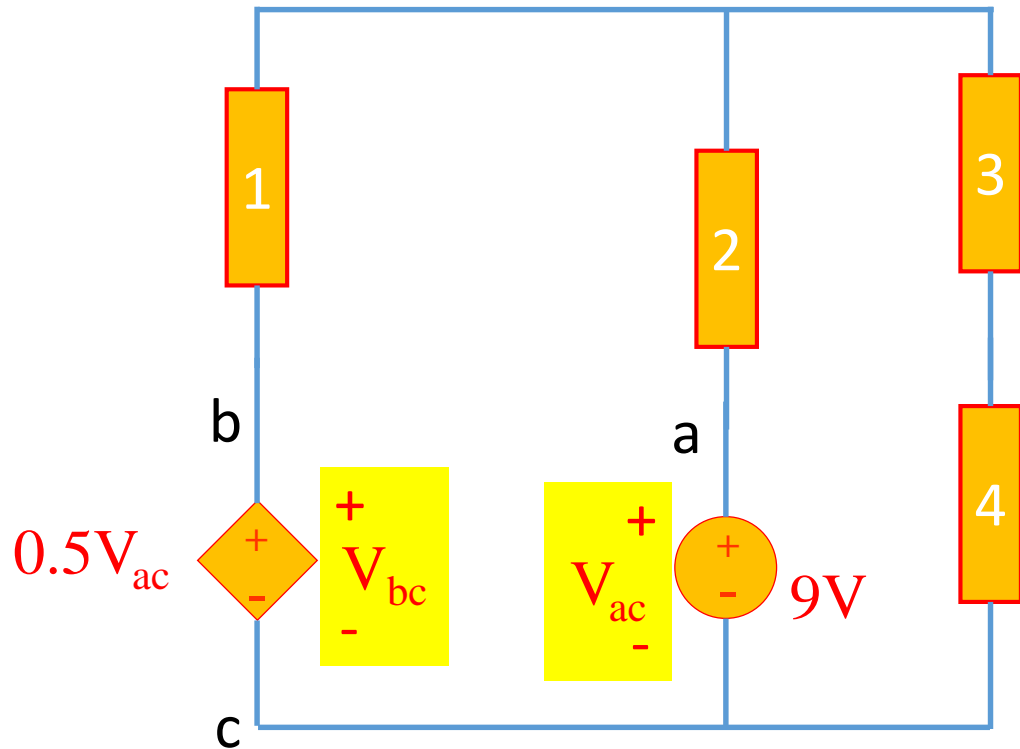Problem 3: (VCVS) Find V_{bc} and V_{ab} .
(15pts.)



Problem 3 Solution

V_{bc} is the voltage across the voltage-controlled voltage source

$$V_{bc} = 0.5V_{ac}$$


V_{ac} is the voltage across 9V voltage source, $V_{ac} = 9V$

$$V_{bc} = 0.5 \times 9V = 4.5V$$

$$V_{ab} = V_{ac} + V_{cb} \quad \text{where } V_{cb} = -V_{bc}$$

$$V_{ab} = V_{ac} - V_{bc} = 9V - 4.5V = 4.5V$$

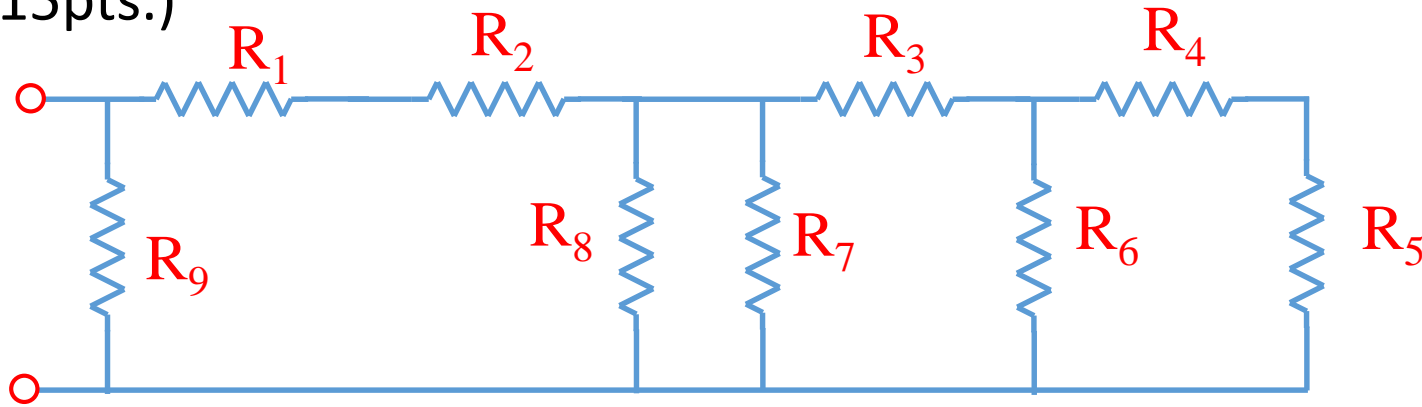
Problem 4: Find R_{eq} . Please use the parallel sign “//” as discussed in class.
(15pts.)



Problem 4 Solution

$$R_{eq} = \left[\left(\left(\left[(R_4 + R_5) \parallel R_6 \right] + R_3 \right) \parallel R_7 \parallel R_8 \right) + R_1 + R_2 \right] \parallel R_9$$

Problem 5: Find R_{eq} .
(15pts.)

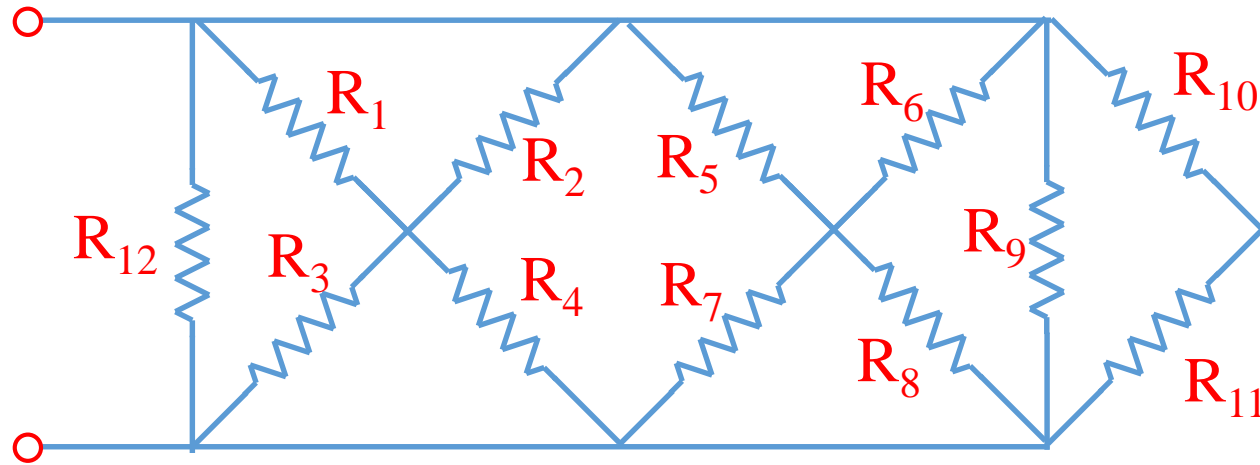


Problem 5 Solution


$$R_{eq} = (R_{10} + R_{11}) \parallel R_9 \parallel [(R_5 \parallel R_6) + (R_7 \parallel R_8)] \parallel [(R_1 \parallel R_2) + (R_3 \parallel R_4)] \parallel R_{12}$$

See the same circuit drawn again on the next page where you can recognize the parallel and series components easily.

Problem 5: Find R_{eq} .
(15pts.)

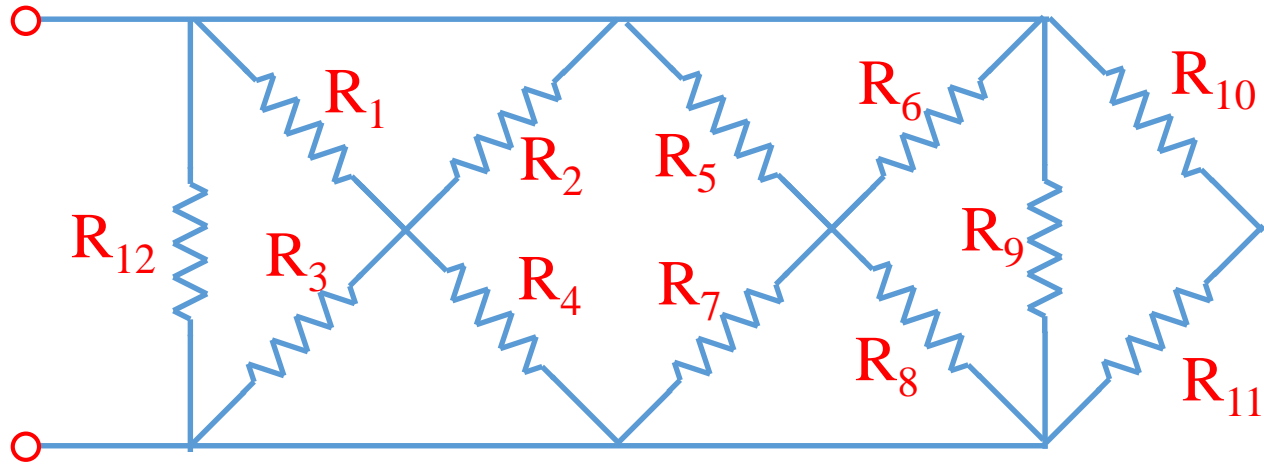


Problem 5 Solution cont'd

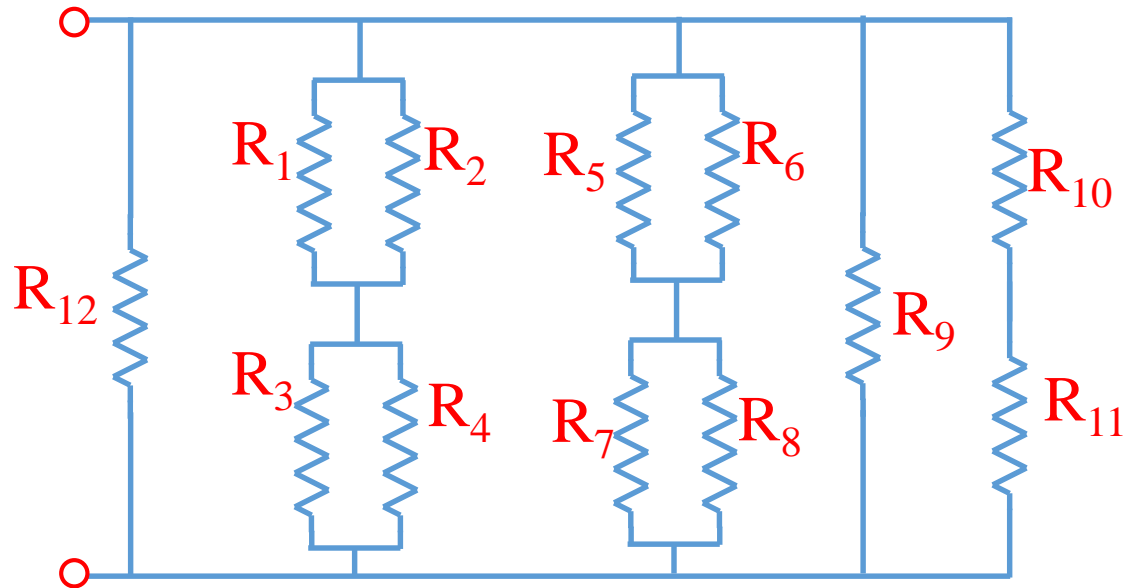

Problem 6: All of the resistors below are $R_0 \Omega$. Find R_{eq} .

(10pts.)

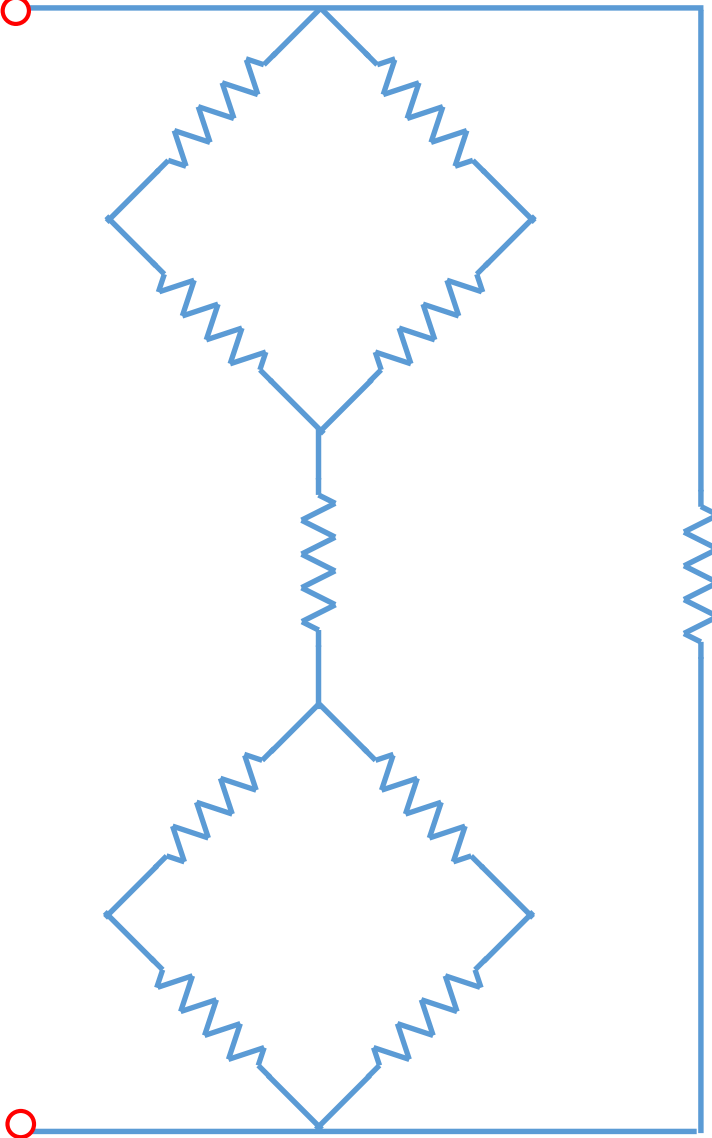

Problem 6 Solution


$$R_{eq} = \left\{ \left[(R_0 + R_0) \parallel (R_0 + R_0) \right] + R_0 + \left[(R_0 + R_0) \parallel (R_0 + R_0) \right] \right\} \parallel R_0$$

$$R_{eq} = \left\{ \left[\underbrace{(R_0 + R_0)}_{2R_0} \parallel \underbrace{(R_0 + R_0)}_{2R_0} \right] + R_0 + \left[\underbrace{(R_0 + R_0)}_{2R_0} \parallel \underbrace{(R_0 + R_0)}_{2R_0} \right] \right\} \parallel R_0$$

$$= \left\{ \left[\underbrace{2R_0 \parallel 2R_0}_{R_0} \right] + R_0 + \left[\underbrace{2R_0 \parallel 2R_0}_{R_0} \right] \right\} \parallel R_0$$


$$= \{ R_0 + R_0 + R_0 \} \parallel R_0 = 3R_0 \parallel R_0 = \left(\frac{1}{3R_0} + \frac{1}{R_0} \right)^{-1} = \frac{3R_0}{4}$$

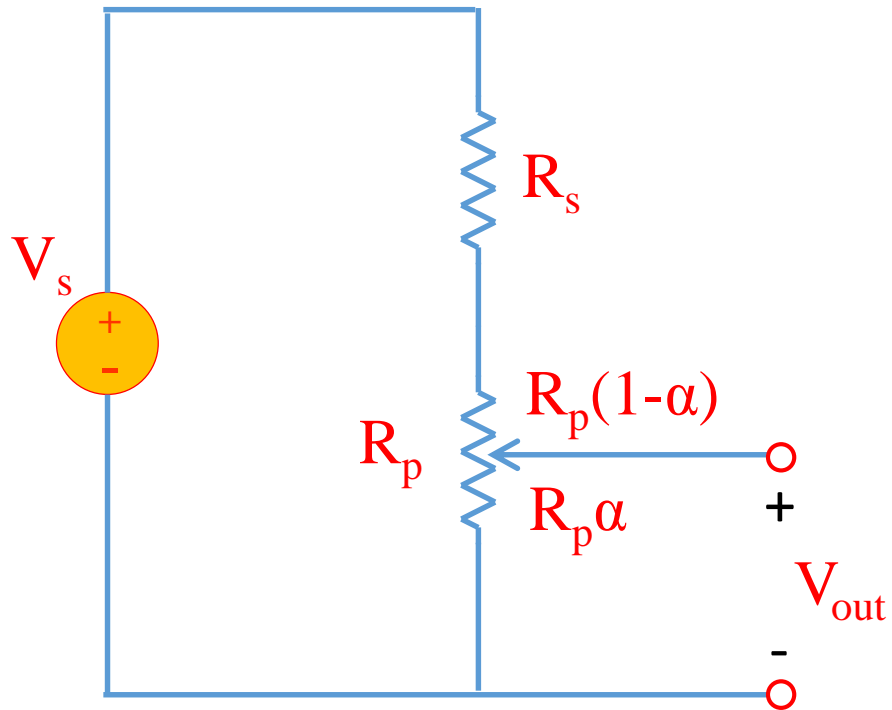Problem 7: (Potentiometer) In the circuit below, the wiper divides the potentiometer resistance R_p between two resistances $R_p(1-\alpha)$ and $R_p\alpha$ where $0 < \alpha < 1$. α is a parameter modeling the wiper's position. Find the output voltage V_{out} as a function of V_s , R_s , R_p and α . (15pts.)



Problem 7 Solution

The circuit is equivalent to

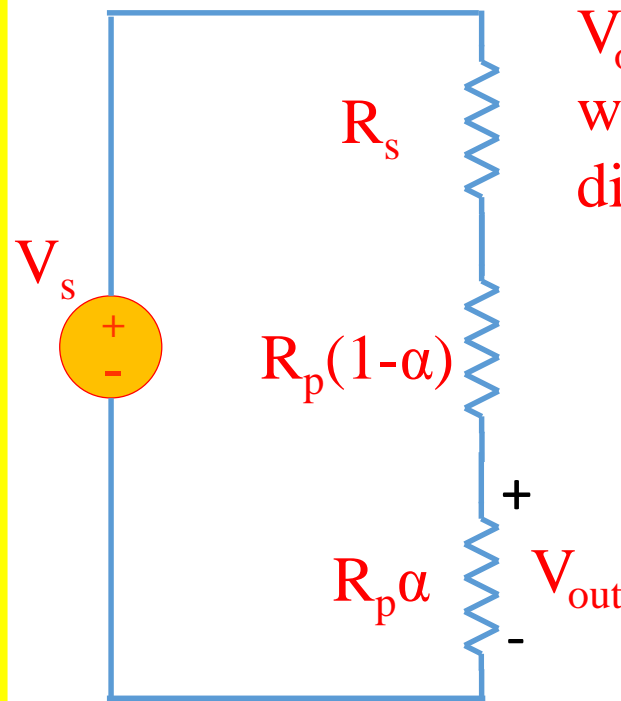

V_{out} is the voltage across $R_p\alpha$ which can be found by voltage division as

$$V_{out} = \frac{R_p\alpha}{R_s + R_p(1-\alpha) + R_p\alpha} V_s$$

$$= \frac{R_p\alpha}{R_s + R_p} V_s$$