

# EECS/CSE 70A Network Analysis I


## Homework #4

Due on or before


5/17/2016, Tuesday 6.00pm at ELH 110

(You can turn in homework assignments during any of the discussion sessions and office hours before the deadline)

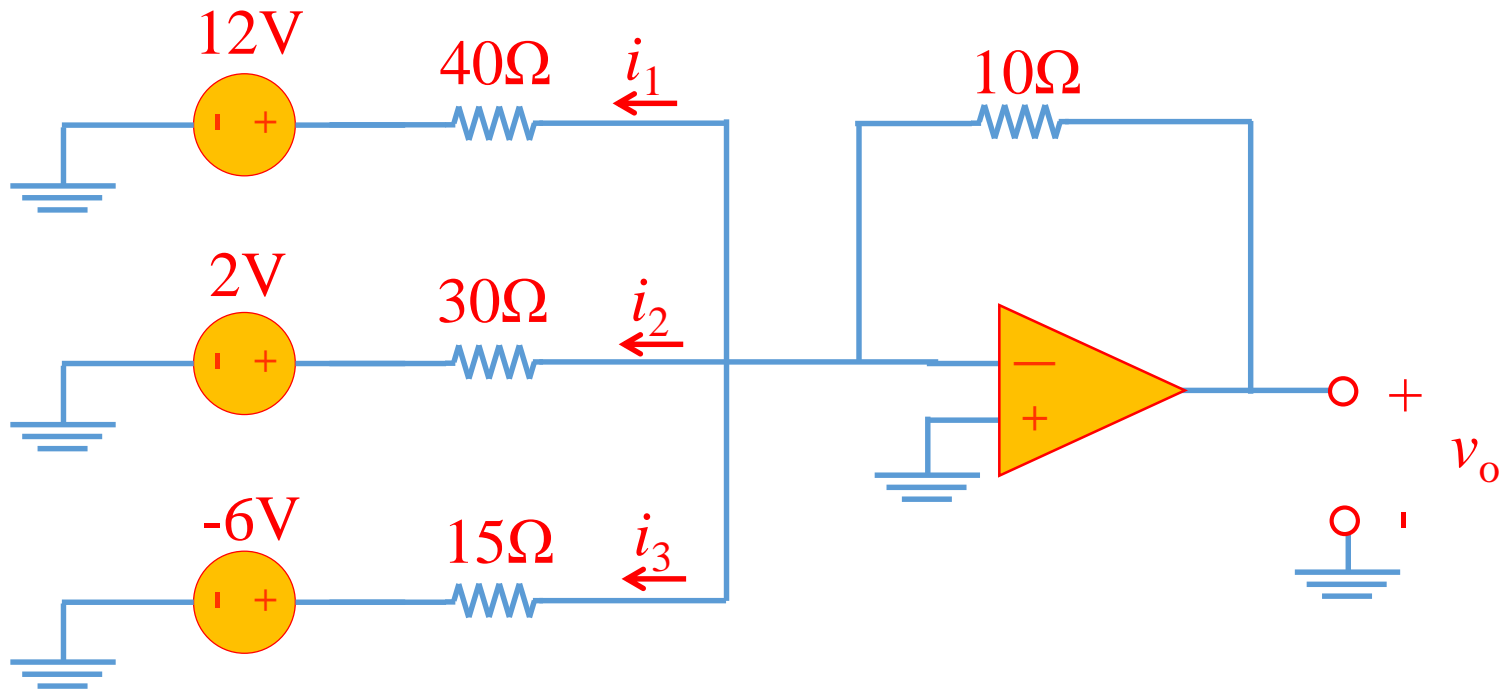Problem 1: (Ideal Opamp) Find currents  $i_1$ ,  $i_2$ ,  $i_3$  and the output voltage  $v_o$  (30pts.)



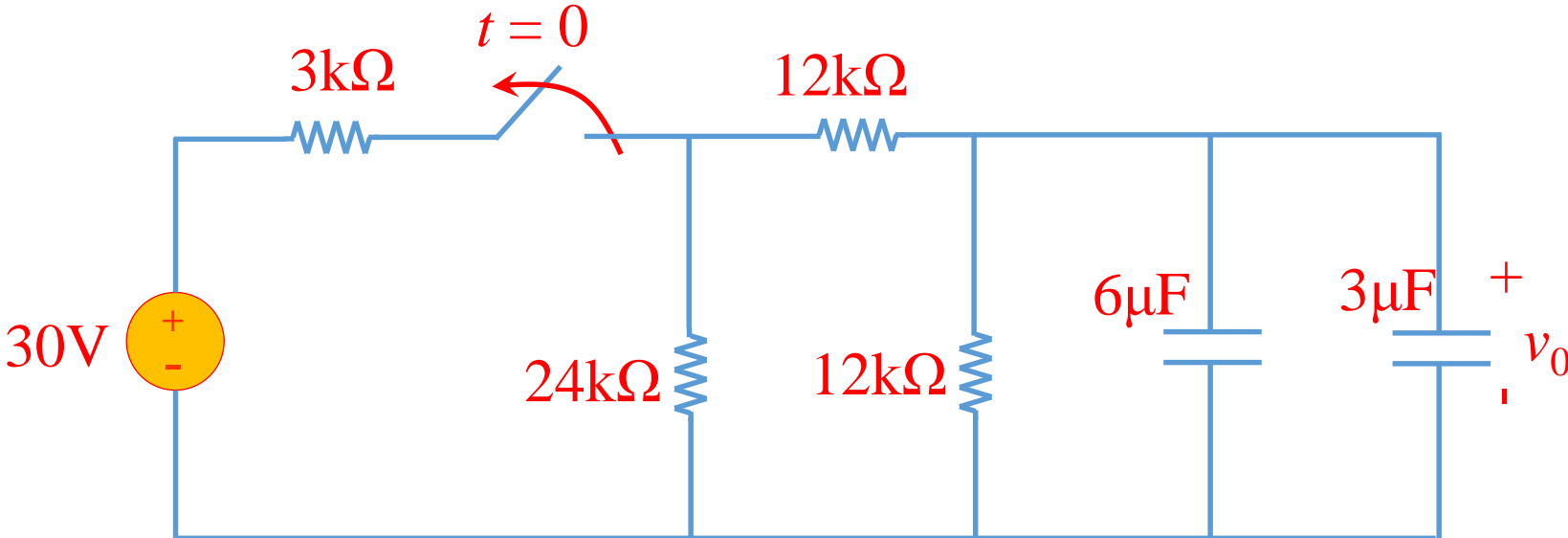Problem 2: (RC circuit) Write the expression for the voltage  $v_0$  for  $t > 0$ . Please clearly show the time constant calculation, initial and steady state voltage across the  $3\mu\text{F}$  capacitor (35pts.)



Problem 3: (RL circuit) Write the expressions first for the current  $i_0$  and then the voltage  $v_0$  for  $t > 0$ . Please clearly show the time constant calculation, initial and steady state current through the inductor. (35pts.)

